



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

DIGITAL ELECTRONICS

EC-EE

Date of Test : 19/01/2024

ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (c) | 13. (c) | 19. (a) | 25. (d) |
| 2. (b) | 8. (b) | 14. (c) | 20. (c) | 26. (a) |
| 3. (a) | 9. (b) | 15. (b) | 21. (d) | 27. (a) |
| 4. (c) | 10. (d) | 16. (a) | 22. (d) | 28. (a) |
| 5. (b) | 11. (b) | 17. (b) | 23. (b) | 29. (b) |
| 6. (d) | 12. (d) | 18. (b) | 24. (c) | 30. (c) |

DETAILED EXPLANATIONS

1. (b)


In J-K flip-flop

J	K	Output
1	0	Set
0	1	Reset
0	0	Hold
1	1	Racearound

2. (b)

$$\begin{aligned}
 X \oplus Y &= \overline{X \odot Y} = \overline{\overline{XY}} + XY \\
 &= (\overline{XY})(\overline{XY}) \\
 &= (X + Y)(\bar{X} + \bar{Y}) \\
 &= \bar{X} + \bar{Y} \quad (\because X + Y = 1 \text{ which is given})
 \end{aligned}$$

3. (a)

 

4. (c)

The expression of Y can be written as

$$Y = (A)\bar{A}\bar{B} + (B)\bar{A}B + (B)A\bar{B} + (A)AB = \bar{A}B + AB = B$$

5. (b)

Dual slope A/D convertor has the highest accuracy among the given converters.


6. (d)

7. (c)

8. (b)

9. (b)

By properly arranging the given k-map.

 

$$\therefore f = \bar{B} + D$$

$$\therefore \text{Complement}, \quad f^C = B\bar{D}$$

10. (d)

11. (b)

The given circuit represents a 3-bit counter. So the count can be represented as

Clk	Q_2	Q_1	Q_0
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1


⇒ 5th clock pulse

$$\therefore Y = Q_2 \oplus Q_1 \oplus Q_0 \\ = 1 \oplus 0 \oplus 1 = 0$$

12. (d)

Test for Lockout

Present State			Present Input				Next State		
Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0	
0	0	0	1	0	1	1	0	1	1
0	0	1	1	1	1	1	0	1	1
0	1	0	1	0	1	1	1	1	0
1	0	1	1	1	1	0	0	0	1

 

Hence, the counter does not enter into lockout state.

13. (c)

Now, $X > Y$ if

(a) $X_2 = 1$

(b) $X_2 = 0$ and $X_1 X_0 > Y_1 Y_0$


$X_1 X_0$	00	01	11	10	
$Y_1 Y_0$	00	00	00	00	$(X_2 + X_1 + X_0)$
$X_1 X_0$	00	01	11	10	
$Y_1 Y_0$	00	01	11	10	$(X_2 + X_1 + \bar{Y}_1)$
$X_1 X_0$	00	01	11	10	$(X_2 + \bar{Y}_1 + \bar{Y}_0)$
$X_1 X_0$	00	01	11	10	$(X_2 + \bar{X}_1 + \bar{Y}_0)$

$$X_2 = 0$$

$X_1 X_0$	00	01	11	10	
$Y_1 Y_0$	00	1	1	1	
$X_1 X_0$	00	1	1	1	
$Y_1 Y_0$	01	1	1	1	
$X_1 X_0$	01	1	1	1	
$Y_1 Y_0$	11	1	1	1	
$X_1 X_0$	11	1	1	1	
$Y_1 Y_0$	10	1	1	1	
$X_1 X_0$	10	1	1	1	

$$X_2 = 1$$

14. (c)

 

$$X = \bar{B}(A + B) + \bar{A}(A + B)$$

$$= A\bar{B} + \bar{A}B = A \oplus B$$


$$Y = B(\bar{A}\bar{B})$$

$$= B(\bar{A} + \bar{B}) = \bar{A}B$$

The above circuit represents a half subtracter constructed using only NAND gates. Thus the truth table can be written as

A	B	Difference (X)	Borrow (Y)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

15. (b)

 

$$\text{Total conversion time, } (t) = 2^N T_C + \frac{V_a}{V_R} \cdot 2^N T_C$$

Where,

 N = Number of bits of converter T_C = Time period of the clock V_a = Analog voltage V_R = reference voltageThe largest V_a can be equal to V_R therefore,

$$V_a = V_R$$

$$t = 2^{N+1} T_C$$

$$t = 2^{12+1} \cdot T_C$$

$$t = 2^{13} \times \frac{1}{100 \times 10^3} \text{ sec}$$

$$t = \frac{8192}{10^5}$$

$$f < \frac{10^5}{8192}$$

$$\therefore f_{\max} = 12 \text{ Hz}$$

16. (a)

$$\begin{aligned} P &= \bar{B}\bar{C}A + \bar{B}C\bar{A} + B\bar{C}\bar{A} + BCA \\ &= \bar{A}[\bar{B}\bar{C} + \bar{B}C] + A[B\bar{C} + \bar{B}\bar{C}] \\ &= \bar{A}[B \oplus C] + A[\bar{B} \oplus \bar{C}] \end{aligned}$$

$$P = A \oplus B \oplus C$$

$$P(A, B, C) = \Sigma m(1, 2, 4, 7)$$

$$\begin{aligned} Q &= \bar{B}\bar{C} \cdot 0 + \bar{B}C\bar{A} + B\bar{C}\bar{A} + BC \\ &= \bar{B}C\bar{A} + B\bar{C}\bar{A} + BC(A + \bar{A}) \\ &= \bar{B}C\bar{A} + B\bar{C}\bar{A} + ABC + \bar{A}BC \end{aligned}$$

$$Q(A, B, C) = \Sigma m(1, 2, 3, 7)$$

17. (b)

From the given code converter we can write

$$x + (1\text{'s complement of } 0011) + 1 = \text{BCD}$$

$$x + 1100 + 1 = \text{BCD}$$


$$x + 1101 = \text{BCD}$$

$$x = \text{BCD} - 1101 = \text{BCD} + (2\text{'s complement of } 1101)$$

$$\therefore x = \text{BCD} + 0011 = \text{Excess-3 code}$$

18. (b)

By redrawing the given circuit,

 


$$\therefore y = \overline{(AB + X) \cdot \bar{C}} = \overline{(AB + (D + E)) \cdot C}$$

$$y = \bar{C} + (\bar{A} + \bar{B})(D + E)$$

19. (a)

$$F = \overline{A(B+C)}$$

 

20. (c)

From the given diagram,

$$J_1 = \bar{Q}_1 Q_2$$

$$K_1 = \bar{Q}_2$$

$$J_2 = K_2 = \bar{Q}_1$$

Also given, $Q_1 = 0$; $Q_2 = 0$ initially

Clk	Q_1	Q_2	J_1	K_1	J_2	K_2
0	0	0	0	1	1	1
1	0	1	1	0	1	1
2	1	0	0	1	0	0
3	0	0	0	1	1	1

 \therefore It is MOD-3 counter.

21. (d)

PS		NS		FF inputs	
Q_A	Q_B	Q_A	Q_B	J_B	k_B
0	0	1	1	1	x
1	1	1	0	x	1
1	0	0	1	1	x
0	1	0	0	x	1

On solving for J_B and k_B


Q_B	0	1
0	1	x
1	1	x

$$J_B = 1$$

Q_B	0	1
0	x	1
1	x	1

$$k_B = 1$$

22. (d)

 

23. (b)

$$\begin{aligned}
 f_2 &= \bar{x}_0x_1 + x_1x_2 + x_0\bar{x}_1\bar{x}_2 \\
 &= \bar{x}_0x_1x_2 + \bar{x}_0x_1\bar{x}_2 + x_0x_1x_2 + \bar{x}_0x_1x_2 + x_0\bar{x}_1\bar{x}_2 \\
 &= \Sigma m(1, 2, 6, 7)
 \end{aligned}$$

24. (c)

Given, initially, PQR is 010.

	$D_1 = R$	$D_2 = \overline{PR}$	$D_3 = Q \odot \overline{R}$	P	Q	R
Clk	D_1	D_2	D_3			
0	0	1	1	0	1	0
1	1	1	0	0	1	1
2				1	1	0

25. (d)

26. (a)

Input equations of flip-flops


$$T_A = BX, T_B = X, Y = AB$$

$$\begin{aligned}
 \text{State equations, } A(t+1) &= T'A + TA' \\
 &= (BX)'A + (BX)A' \\
 &= AB' + AX' + A'BX \\
 B(t+1) &= T'B + TB' \\
 &= X'B + XB' = X \oplus B
 \end{aligned}$$

State table:

Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

State diagram:

 

27. (a)

$$000 \xrightarrow{1^{\text{st}} \text{ CLK}} 100 \xrightarrow{2^{\text{nd}} \text{ CLK}} 010 \xrightarrow{3^{\text{rd}} \text{ CLK}} 101$$

The op-amp circuit is a R-2R Ladder DAC with digital input 101. Therefore,

$$V_0 = -\left(\frac{R_f}{R}\right) \times \left(\frac{V_{ref}}{2^3}\right) \times (\text{Decimal equivalent of } 101)$$

$$V_0 = \frac{-R}{R} \times \frac{5}{8} \times 5$$

$$V_0 = -3.125 \text{ V}$$

28. (a)

$$\begin{array}{r}
 \begin{array}{r} 1\ 0\ W\ 1\ Z \\ \times \quad 1\ 1\ 1\ 1 \\ \hline \end{array} \\
 \begin{array}{r} (10)(10) \ 1\ 1\ 0\ 0 \\ 1\ 0\ W\ 1\ Z \\ (10) \ 1\ 0\ W\ 1\ Z \\ 1\ 0\ W\ 1\ Z \\ \hline 1\ 0\ W\ 1\ Z \end{array} \\
 \begin{array}{r} 1\ 0\ 1\ 0\ 1\ 1\ 0\ 0\ Z \\ \downarrow \quad \downarrow \quad \downarrow \\ Y = 1 \quad Z = 1 \end{array} \\
 \begin{array}{r} 1 + W + 1 + Z = \underline{\underline{100}}(W = 1) \\ \downarrow \\ \text{Carry} \end{array} \\
 \end{array}$$

$\Theta 15_{10} = (1111)_2$

$$\therefore (WYZ)_2 = (111)_2 = 7$$

29. (b)

There are three data paths (flop A to flop B, flop A to flop C, flop B to flop C). Setup time is used for deriving the maximum clock frequency.

$$\text{Path } A \rightarrow B: t_{\text{CLK}} > t_{\text{CLK} \rightarrow Q} + t_s = 9 + 2 \Rightarrow t_{\text{CLK}} > 11 \text{ ns}$$

$$\begin{aligned} \text{Path } A \rightarrow C: \quad t_{\text{CLK}} &> t_{\text{CLK} \rightarrow Q} + t_s + t_{pd} = 9 + 2 + 4 \Rightarrow t_{\text{CLK}} > 15 \text{ ns} \\ &\quad t_{\text{clk}} > 15 \text{ nsec} \end{aligned}$$

$$f_{\max} = \frac{1}{t_{\text{clk}} \text{ (min)}} = \frac{1}{15 \times 10^{-9}} = 66.67 \text{ MHz}$$

30. (c)

We know that

$$t_{\text{setup}} \leq t_{\text{clk}} - t_{pd, D} - t_{pd, CL}$$

for maximum setup time,

$$\begin{aligned} t_{\text{setup}} &= t_{\text{clk}} - t_{pd, D} - t_{pd, CL} \\ &= 25 - 6 - \max(11, 9) \\ &= 25 - 6 - 11 \\ &= 8 \text{ ns} \end{aligned}$$

