



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

DC MACHINE

ELECTRICAL ENGINEERING

Date of Test : 06/07/2023

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (b) | 13. (b) | 19. (b) | 25. (b) |
| 2. (a) | 8. (b) | 14. (a) | 20. (c) | 26. (c) |
| 3. (b) | 9. (d) | 15. (d) | 21. (a) | 27. (b) |
| 4. (b) | 10. (b) | 16. (a) | 22. (a) | 28. (a) |
| 5. (d) | 11. (a) | 17. (c) | 23. (a) | 29. (a) |
| 6. (a) | 12. (c) | 18. (b) | 24. (a) | 30. (d) |

DETAILED EXPLANATIONS


1. (b)

Back emf is given by,

$$E_b = \frac{NP\phi Z}{A \times 60}$$

$$= \frac{1000 \times 0.15 \times 100}{60} = 250 \text{ V}$$
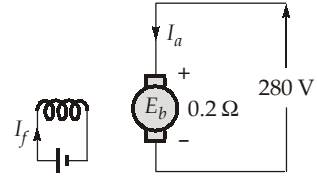
$$I_a = \frac{280 - 250}{0.2} = 150 \text{ A}$$



2. (a)

Let, induced emf = x

$$x + I_a r_a = 300 \text{ V} \tag{... (i)}$$

When load is reduced to half,

$$x + \frac{I_a r_a}{2} = 250 \text{ V} \tag{... (ii)}$$

Solving equation (i) and (ii), we get

$$\text{Induced emf, } x = 200 \text{ V}$$

3. (b)

For maximum efficiency,

Constant loss = losses proportional to square of variable

$$\text{Cu loss} = I^2 R$$

Brush loss $\propto I$ (so it is not included in constant losses)

So, Constant loss = $150 + 200 + P_i$

$$150 + 200 + P_i = 400$$

$$P_i = 50 \text{ W}$$

4. (b)

The motor and generator are identical

DC supply given to motor,

$$V = 1 \text{ p.u.}$$

Current in both motor and generator

$$I_{am} = I_{ag} = 1 \text{ p.u.}$$

$$R_{am} = R_{ag} = 0.02 \text{ p.u.}$$

Back emf in motor, $E_m = V - I_{am} R_{am}$

$$E_m = 1 - 1 \times 0.02 = 0.98 \text{ p.u.}$$

Also

$$E_m I_m = E_g I_{ag}$$

\Rightarrow

$$E_m = E_g = 0.98 \text{ p.u.}$$

Terminal voltage of generator,

$$V_g = E_g - I_{ag} \cdot R_{ag}$$

$$= 0.98 - 1 \times 0.02 = 0.96 \text{ p.u.}$$

$$\text{Load resistance} = \frac{V_g}{I_g} = \frac{0.96}{1.0} = 0.96 \text{ p.u.}$$

5. (d)

For series motor,

 $T \rightarrow$ Torque

$$T \propto I_a^2$$

or,

$$I_a \propto \sqrt{T}$$

...(i)

and also,

$$E_b \propto N\phi$$

or

$$E_b \propto NI_a$$

(as $\phi \propto I_a$)

$$N \propto \frac{E_b}{I_a}$$

From equation (i),

$$N \propto \frac{E_b}{\sqrt{T}}$$

6. (a)

$$T = K\phi I_a = 300$$

$$E = V - I_a R_a = K\phi\omega$$

$$600 - 0.5 I_a = 2\pi \times \frac{1500}{60} \times \frac{300}{I_a}$$

$$0.5I_a^2 - 600I_a + 47123.8 = 0$$

$$I_a = 84.49 \text{ A}$$

$$K\phi = 3.55 \text{ Nm/A}$$

$$I_a' = \frac{T}{(K\phi)'} = \frac{300}{0.9 \times 3.55} = 93.89 \text{ A}$$

7. (b)

Rotation speed = 600 rpm

$$N = \frac{600}{60} = 10 \text{ rev/sec}$$

Peripheral velocity of commutator,

$$\begin{aligned} V_p &= \pi DN \\ &= \pi \times 50 \times 10 \text{ cm/sec} \end{aligned}$$

As we know,

$$V_p \times t_c = \text{Brush width}$$

$$\therefore \text{Time of commutation, } t_c = \frac{2}{\pi \times 50 \times 10} = 1.273 \text{ msec}$$

8. (b)

$$\text{Back emf, } E_b = \frac{P\phi NZ}{60A} \quad (A = P \text{ for lap winding})$$

$$= \frac{0.6 \times 10^{-3} \times 750 \times 2000}{60} = 15 \text{ V}$$

9. (d)

We know that, emf generated,

$$E = \frac{P\phi NZ}{60A} = \phi \times 50 \times 18 \times \frac{9000}{60} \times \frac{4}{2}$$

$$357 = \phi \times 50 \times 18 \times \frac{9000}{60} \times \frac{4}{2}$$

Flux per pole, $\phi = 1.32 \text{ mWb}$

10. (b)

Field current, $I_f = \frac{250}{125} = 2 \text{ A}$

No load armature current, $I_{a0} = 16 - 2 = 14 \text{ A};$

Constant losses, $P_K = (250 \times 14 - (14)^2 \times 0.2) + 250 \times 2 = 3960.8 \text{ W}$

$$I_a = 152 - 2 = 150 \text{ A}$$

$$P_L = I_a^2 R_a + P_K = (150)^2 \times 0.2 + 3960.8 = 8.461 \text{ kW}$$

$$P_{in} = 250 \times 152 = 38 \text{ kW}$$

$$\therefore \text{Efficiency, } \eta_n = \frac{38 - 8.461}{38} \times 100 = 77.73\%$$

11. (a)

Series excited and should have polarity opposite to that of the next main pole in the direction of rotation of armature.

12. (c)

$$\begin{aligned} \text{Compensating winding, AT/pole} &= \text{armature AT/pole} \times \frac{\text{Pole arc}}{\text{Pole pitch}} \\ &= 19000 \times 0.7 = 13300 \end{aligned}$$

$$\text{Turn/pole} = \frac{AT_{cw} / \text{pole}}{\text{Armature current}} = \frac{13300}{1000} = 13.3 \approx 14$$

No. of compensating conductor per pole,


$$14 \times 2 = 28$$

$$\text{AT for airgap under interpole} = \frac{B_g}{\mu_0} l_g = \frac{0.3}{4\pi \times 10^{-7}} \times 1 \times 10^{-2} = 2387.324 \text{ ATs}$$

$$\text{Net AT for interpole} = 19000 + 2387.324 - 14000$$

$$\text{No. of turns in interpole} = \frac{19000 + 2387.324 - 14000}{1000} \approx 8$$

13. (b)

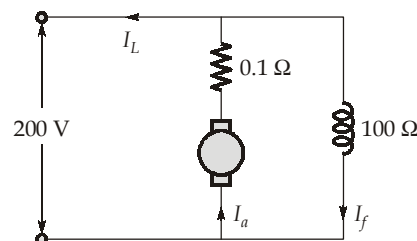

As generator:

$$\text{Load current, } I_{L1} = \frac{60 \times 1000}{200} = 300 \text{ A}$$

$$\text{Armature current, } I_{a1} = I_{L1} + I_f = 300 + \frac{200}{100} = 302 \text{ A}$$

Generator induced emf, $E_{g1} = V_t + I_{a1}R_a + \text{brush drop}$

$$E_{g1} = 200 + 2 + 302 \times 0.1 = 232.2 \text{ V}$$

When belt breaks it will behave as motor then

$$I_{L2} = \frac{5000}{200} = 25 \text{ A}$$

Now,

$$I_{a2} = I_{L2} - I_f = 25 - 2 = 23 \text{ A}$$

$$E_{b2} = 200 - 2 - 23 \times 0.1 = 195.7 \text{ V}$$

as $E \propto N\phi$ or $E \propto N$ $\phi \rightarrow \text{constant}$

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{232.2}{195.7} = \frac{500}{N_2}$$

$$\Rightarrow \text{Speed, } N_2 = 421.4 \text{ rpm}$$

14. (a)

$$AT_{CW}/\text{Pole} = AT_a(\text{peak}) \times \frac{\text{Pole arc}}{\text{Pole pitch}}$$

$$= 20000 \times 0.8 = 16000$$

$$AT_a(\text{peak}) \text{ interpolar region} = 20000 - 16000 = 4000$$

$$AT_i = AT_a(\text{peak}) + \frac{B_i}{\mu_0} l_{gl}$$

$$= 4000 + \left[\frac{0.3}{4\pi \times 10^{-7}} \times 1.2 \times 10^{-2} \right] = 6865 \text{ AT/P}$$


$$N_i = \frac{6865}{1000} \approx 7 \text{ turns}$$

15. (d)

$$\text{No load loss} = 200 \times 10 = 2000 \text{ W}$$


$$I_f = \frac{200}{100} = 2 \text{ A}$$
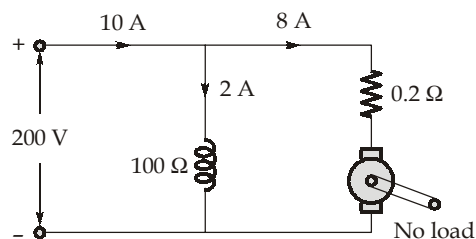
$$\begin{aligned} \text{Core loss} &= (200 \times 8) - (8^2 \times 0.2) \\ &= 1587.2 \text{ W} \end{aligned}$$



At load:
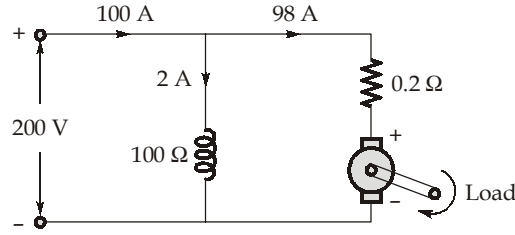
$$\text{Stray load loss} = 0.5 \times 2000 = 1000 \text{ W}$$




$$P_L = (I_a^2 R_a + V_{\text{brush}} I_a + P_{\text{stray}}) + (P_{\text{core}} + P_{\text{shunt field}})$$

$$P_L = (98^2 \times 0.2) + (2 \times 98) + 1000 + 1587.2 + (200 \times 2)$$

$$P_L = 5.104 \text{ kW}$$

16. (a)

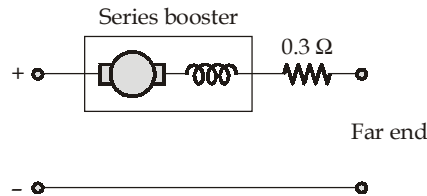

$$\text{Load current} = 200 \text{ A}$$

$$\text{Voltage rise due to booster} = 50 \text{ V}$$

$$\begin{aligned} \text{Voltage drop in feeder} &= I_L \times \text{feeder resistance} \\ &= 200 \times 0.3 = 60 \text{ V} \end{aligned}$$


$$\begin{aligned} \text{Voltage difference between station bus-bar and far end of the feeder.} \\ &= 60 - 50 = 10 \text{ V} \end{aligned}$$

17. (c)

For an over compounded dc generator, percentage of compounding = voltage regulation

$$\begin{aligned} \% \epsilon_R &= \left(\frac{E_a - V}{V} \right) \times 100 = \left(\frac{I_a R_a}{V} \right) \times 100 \\ &= \left(\frac{800 \times 0.02}{500} \times 100 \right) = \frac{16}{5} = 3.2\% \end{aligned}$$

18. (b)

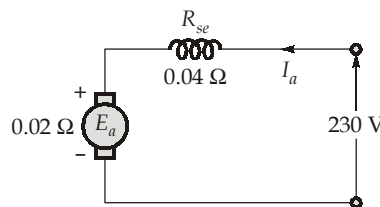

Armature power developed,

$$\begin{aligned} &= \text{shaft power} + \text{rotational losses} \\ &= 1.5 \text{ kW} + 0.1 \text{ kW} \end{aligned}$$

$$E_b I_a = 1.6 \text{ kW}$$

Back emf is given by,

$$E_b = \frac{NP\phi Z}{A \times 60} = \frac{N \times 0.035 \times 500}{60} \quad (\text{For lap } A = P)$$

and armature current, $I_a = \frac{230 - E_b}{0.06}$

$$E_b \left(\frac{230 - E_b}{0.06} \right) = 1600$$

$$230 E_b - E_b^2 - 96 = 0$$

$$E_b = 229.58 \text{ V}$$

$$\text{Speed, } N = \frac{60 E_b}{\phi Z} = \frac{60 \times 229.58}{0.035 \times 500}$$

$$N = 787.13 \text{ rpm}$$

19. (b)

Load characteristic is

$$T_L \propto N^2$$

For dc series motor, torque-current relation is given by

$$T_d \propto I_a^2$$

$$\therefore \frac{I_{a2}}{I_{a1}} = \frac{N_2}{N_1}$$

$$\frac{I_{a2}}{15} = \frac{750}{1500}$$

$$I_{a2} = 7.5 \text{ A}$$

Case-I:

$$E_{a1} = 200 - 15 \times (0.03 + 0.05)$$

$$E_{a1} = 198.8 \text{ V}$$

Case-II:

When additional resistance added in series with the armature circuit,

$$I_{a2} = 7.5 \text{ A,}$$

$$N_2 = 750 \text{ rpm}$$

Now,

$$E_a \propto \phi \omega_m$$

$$\frac{E_{a2}}{E_{a1}} = \frac{N_2 I_{a2}}{N_1 I_{a1}}$$

(In dc series motor $\phi \propto I_a$)

$$\frac{E_{a2}}{198.8} = \frac{750 \times 7.5}{1500 \times 15}$$


$$E_{a2} = 49.7 \text{ V}$$

$$E_{a2} = 200 - 7.5(0.08 + R_{\text{ext}}) = 49.7$$

$$0.08 + R_{\text{ext}} = \frac{200 - 49.7}{7.5}$$

$$R_{\text{ext}} = 20.04 - 0.08$$

$$= 19.96 \text{ } \Omega$$

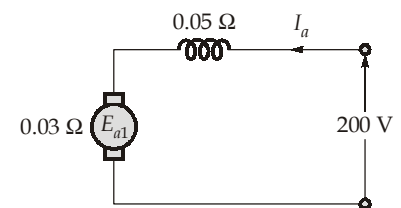

20. (c)

We know that,

$$\text{Torque, } T \propto \phi I_a$$

$$\text{So, } \frac{T_1}{T_2} = \frac{\phi_1 I_{a1}}{\phi_2 I_{a2}}$$

$$T_2 = \frac{\phi_2 I_{a2}}{\phi_1 I_{a1}} \times T_1$$

$$\text{Given, } \phi_2 = 1.2 \phi_1, I_{a1} = 40 \text{ A, } I_{a2} = 60 \text{ A}$$

$$\text{Torque developed, } T_2 = 1.2 \times \frac{60}{40} \times 20 = 36 \text{ N-m}$$

21. (a)

$$\begin{aligned} \text{Output power, } P_0 &= 240 \times 100 \\ &= 24000 \text{ W} \end{aligned}$$

$$\text{Shunt field current, } I_f = 3 \text{ A,}$$

$$\text{Armature current, } I_a = 100 + 3 = 103 \text{ A}$$

$$\text{Series field current, } I_{se} = \frac{0.04}{0.04 + 0.01} \times 100 = 80 \text{ A}$$

$$I_d = 100 - 80 = 20 \text{ A}$$

$$\begin{aligned} E_a &= V_t + I_L R_{fe} + I_s R_s + I_a R_a \\ &= 240 + 100 \times 0.03 + 80 \times 0.01 + 103 \times 0.05 \\ &= 248.95 \text{ V} \end{aligned}$$

$$\begin{aligned} V_f &= E_a - I_a R_a \\ &= 248.95 - 103 \times 0.05 = 243.8 \text{ V} \end{aligned}$$

$$\text{Hence, } R_f = \frac{243.8}{3} = 81.267 \Omega$$

Copper losses :

$$\text{Armature : } I_a^2 R_a = 103^2 \times 0.05 = 530.45 \text{ W}$$

$$\text{Series field : } I_s^2 R_s = 80^2 \times 0.01 = 64 \text{ W}$$

$$\text{Shunt field : } I_f^2 R_f = 3^2 \times 81.267 = 731.4 \text{ W}$$

$$\text{Diverter resistance: } I_d^2 R_d = 20^2 \times 0.04 = 16 \text{ W}$$

$$\text{Feeder resistance: } I_L^2 R_{fe} = 100^2 \times 0.03 = 300 \text{ W}$$

$$\begin{aligned} \text{Total copper loss : } P_{cu} &= 530.45 + 64 + 731.4 + 16 + 300 \\ &= 1641.85 \text{ W} \end{aligned}$$

Thus, the power developed is

$$\begin{aligned} P_d &= P_0 + P_{cu} = 24000 + 1641.85 \\ &= 25641.85 \text{ W} \end{aligned}$$

The power input is,

$$\begin{aligned} P_{in} &= P_d + P_r \\ &= 25641.85 + 2000 \\ &= 27641.85 \text{ W} \end{aligned}$$

Hence, the efficiency is

$$\eta = \frac{P_0}{P_{in}} = \frac{24000}{27641.85} = 0.8682 \text{ (or) } 86.82\%$$

22. (a)

For series DC motor,

$$T \propto I^2$$

as torque is constant means current also remains constant

$$T = \frac{E_b I_a}{\omega}$$

as both T and I_a as constant

$$E_b \propto \omega$$

In case of series connection $E_b \approx V/2$ for parallel connection, $E_b \approx V$

So speed becomes double

23. (a)

The shunt field current is

$$I_f = \frac{120}{40} = 3\text{A}$$

For maximum efficiency,

$$I_{Lm}^2 (R_a + R_s) = P_r + I_f^2 (R_a + R_s + R_f)$$

$$I_{Lm}^2 (0.05 + 0.02) = 3^2 (0.05 + 0.02 + 40) + 2000$$

or,

$$I_{Lm} = 183.64\text{ A}$$

Thus the power output at maximum efficiency is :

$$P_0 = 120 \times 183.64 = 22036.8\text{ W}$$

The total copper loss is

$$\begin{aligned} P_{cu} &= I_a^2 (R_a + R_s) + I_f^2 R_f \\ &= (183.64)^2 \times 0.07 + (3)^2 \times 40 \\ &= 2720.65\text{ W} \end{aligned}$$

The power developed at maximum efficiency is

$$\begin{aligned} P_d &= P_0 + P_{cu} \\ &= 22036.8 + 2720.65 = 24757.45\text{ W} \end{aligned}$$

The power input : $P_{in} = 24757.45 + 2000 = 26757.45\text{ W}$


Hence, the maximum efficiency is :

$$\eta = \frac{22036.8}{26757.45} = 0.8235 \quad (\text{or}) \quad 82.35\%$$

24. (a)

Open circuit ($I_a = 0$), then

$$V_t = E_a = 250\text{ V at } 3000\text{ rpm}$$

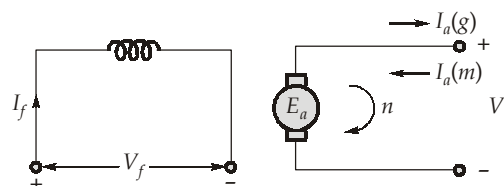Now, $V_t = 255\text{ V}$ As $V_t > E_a$, the machine is acting as a motor

$$I_a = \frac{V_t - E_a}{R_a} = \frac{255 - 250}{0.05} = 100 \text{ A}$$

The current flowing into the positive terminal in opposition to E_a , therefore

$$\begin{aligned} \text{Electromagnetic power} &= E_a I_a = 250 \times 100 \\ &= 25 \text{ kW} = \text{mechanical power output} \\ \text{Speed} &= 3000 \text{ rpm} \end{aligned}$$

or,
$$\frac{3000 \times 2\pi}{60} = 314.16 \text{ rad/s}$$

Electromagnetic torque,

$$T_{em} = \frac{E_a I_a}{\omega_m} = \frac{25 \times 10^3}{314.16} = 79.58 \text{ N-m}$$

25. (b)

$$AT_{cw/pole} = \frac{I_a Z}{2AP} \left(\frac{\text{Pole arc}}{\text{Pole pitch}} \right)$$

$$\therefore N_{cw/pole} = \frac{Z}{2AP} \left(\frac{\text{Pole arc}}{\text{Pole pitch}} \right) = \frac{286}{2 \times 6 \times 6} \times 0.7 = 2.78$$

Compensating conductor/pole

$$= 2.78 \times 2 = 5.56 \approx 6 \text{ (nearest integer)}$$

26. (c)

Firing angle, $\alpha = 0^\circ$

$$\frac{3\sqrt{2} V_l}{\pi} \cos \alpha = 230$$

$$V_l = 170.31 \text{ V}$$

At Speed, $N = 1500 \text{ rpm}$

$$\text{Back emf, } E_1 = 230 - 20 \times 0.6 = 218 \text{ V}$$

At half rated torque,

$$\text{Current, } I_2 = \frac{1}{2} \times 20 = 10 \text{ A}$$

$$\text{Back emf, } E_2 = -\frac{900}{1500} \times 218 = -130.8 \text{ V}$$

$$\frac{3\sqrt{2}}{\pi} V_l \cos \alpha = -130.8 + 10 \times 0.6$$

$$\alpha = 122.86^\circ$$

27. (b)

$$T = K\phi I_a$$

$$K\phi = \frac{10}{10} = 1 \text{ Nm/A}$$

Now,

$$T = 25 \text{ Nm}$$

$$K\phi I_a = 25$$

$$I_a = 25 \text{ A}$$

$$V = E + I_a R_a$$

$$200 = K\phi\omega + 25 \times 0.2$$

$$\omega \times 1 = 195$$

$$\frac{2\pi N}{60} = 195$$

$$N = 1862.11 \text{ rpm}$$

28. (a)

At no load;

$$\text{Back emf, } E_{b0} = V_t - I_{a0} (R_a)$$

$$E_{b0} = 220 - 3(0.5)$$

$$E_{b0} = 218.5 \text{ V}$$

At full load;

$$\text{Back emf, } E_{bfl} = V_t - I_{afl} (R_a)$$

$$= 220 - 45 (0.5)$$

$$E_{bfl} = 197.5 \text{ V}$$

As flux is given constant;

then, we can write; $E_b \propto N$

$$\text{or, } \frac{E_{bfl}}{E_{b0}} = \frac{N_{fl}}{N_0}$$

$$N_{fl} = \left(\frac{197.5}{218.5} \right) \times 1500$$

$$= 1355.83 \approx 1356 \text{ rpm}$$

29. (a)

The motor and generator are identical.

DC supply given to motor

$$V = 1 \text{ p.u.}$$

Current in both motor and generator

$$I_{am} = I_{ag} = 1 \text{ p.u.}$$

Armature resistance, $R_{am} = R_{ag} = 0.015 \text{ p.u.}$

$$\text{Back emf in motor, } E_m = V - I_{am} \cdot R_{am}$$

$$E_m = 1 - (1 \times 0.015)$$

$$= 0.985 \text{ p.u.}$$

As rotational losses are negligible,

Power output of motor = Power input to generator

$$\text{or, } E_m I_{am} = E_g \cdot I_{ag}$$


$$\text{or, } E_m = E_g = 0.985 \text{ p.u.}$$

Terminal voltage of generator

$$V_g = E_g - I_{ag} \cdot R_{ag} = 0.985 - (1 \times 0.015) = 0.97 \text{ p.u.}$$

$$\text{Load resistance} = \frac{V_g}{I_g} = \frac{0.97}{1.0} = 0.97 \text{ p.u.}$$

30. (d)

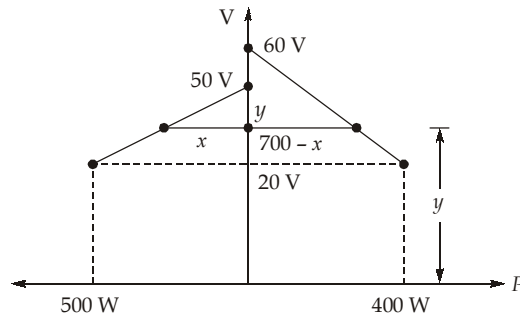

From similarity of triangles for generator 1,

$$\frac{50 - y}{x} = \frac{50 - 20}{500}$$

$$50 - y = 0.06 x$$

$$0.06 x + y = 50$$

...(i)

For second triangle,

$$\frac{60 - y}{700 - x} = \frac{60 - 20}{400}$$

$$60 - y = 70 - 0.1 x$$

$$0.1 x - y = 10$$

...(ii)

Solving the equations (i) and (ii), we get

$$y = 27.5 \text{ V}$$

$$\text{Voltage} = 27.5 \text{ V}$$

