

**ESE GATE PSUs**

**State Engg. Exams**

**MADE EASY**  
**WORKBOOK 2025**



**Detailed Explanations of  
Try Yourself *Questions***

**ELECTRICAL ENGINEERING**

**Power Electronics & Drives**



# 1

## Power Semiconductor Devices



### Detailed Explanation of Try Yourself Questions

#### T1 : Solution

(c)

Devices mentioned in figure 2 and 4 allow current flow in both direction.

#### T2 : Solution

(d)

$$\begin{aligned}\left(\frac{di}{dt}\right)_{\max} &= \left(\frac{V_{s\max}}{L}\right) \\ &= \frac{\sqrt{2} \times 230}{15 \times 10^{-6}} = 21.685 \text{ A}/\mu\text{s}\end{aligned}$$

$$\begin{aligned}\left(\frac{dv}{dt}\right)_{\max} &= R_s \left(\frac{di}{dt}\right)_{\max} = 10 \times 21.685 \\ &= 216.85 \text{ V}/\mu\text{sec}\end{aligned}$$

#### T3 : Solution

(d)

KVL in the loop is,  $-V + L \frac{di}{dt} = 0$

$$V = L \frac{di}{dt}$$

$$dt = \frac{L}{V} di$$

Integrating on both sides,  $\int dt = \int \frac{L}{V} di$

$$t_{\min} = \frac{0.1}{100} \times 4 \times 10^{-3} = 4 \mu\text{s}$$

∴ The minimum width of the gating pulse required to properly turn on the SCR is 4 μs.

**T4 : Solution**

(a)

During interval  $t_2$ , voltage starts decreasing and becomes zero and current starts increasing and becomes constant ( $I$ ), so transition is turn on.

$$\int dt = \int \frac{L}{V} di$$

During  $t_1$  interval,

power loss =  $vi$

$$E_1 = \text{Energy loss} = \int v i dt = V \int i dt$$

$V$  is constant during this period,  $v = V$

$\int i dt$  represents area under  $i$ - $t$  curve

$$\int i dt = \frac{1}{2} \times I \times t_1$$

$$E_1 = V \int i dt = \frac{1}{2} V I t_1 \quad \dots(i)$$

During  $t_2$  interval, Power loss =  $vi$

$$E_2 = \text{Energy loss} = \int v i dt = I \int v dt$$

$i$  is constant during this period  $i = I$


$\int v dt$  represents area under  $v$ - $t$  curve

$$\int v dt = \frac{1}{2} V I t_2$$

$$E_2 = I \int v dt = \frac{1}{2} V I t_2 \quad \dots(ii)$$


Total energy lost during the transition
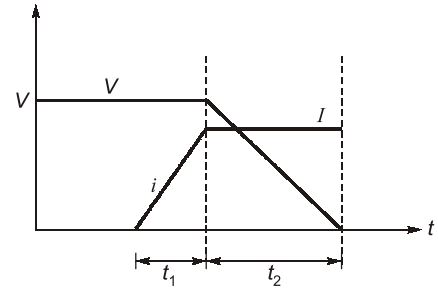
$$E = E_1 + E_2 = \frac{1}{2} V I t_1 + \frac{1}{2} V I t_2$$



**T5 : Solution**

(b)

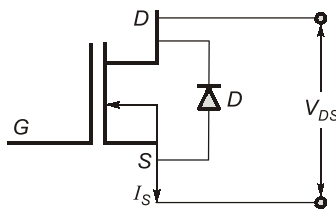

When reverse current flows through diode  $D$ .


So,  $I_S < 0$  and  $V_{DS} = 0$

When MOSFET is in ON state,

$$I_S > 0 \text{ and } V_{DS} = 0$$


When MOSFET is in OFF state,

$$I_S = 0 \text{ and } V_{DS} > 0$$

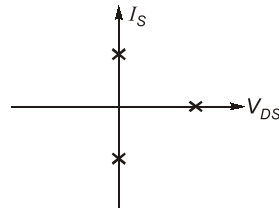

### T6 : Solution

(c)

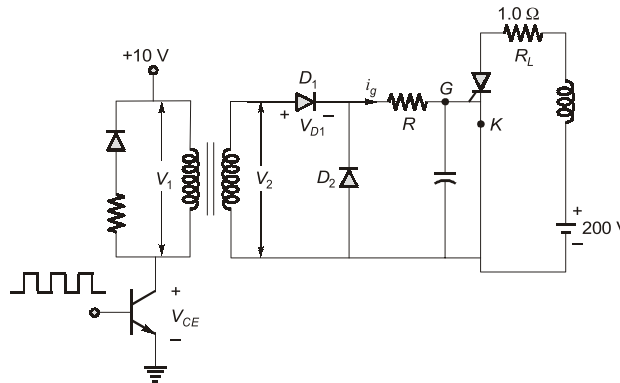

When the pulses are applied to the base of the transistor. Transistor operates in ON state. So, the forward voltage drop in transistor  $V_{CE} = 1 \text{ V}$ .

$$V_1 = 10 - V_{CE} = 10 - 1 = 9 \text{ V}$$

$$V_2 = V_1 \left( \frac{1}{1} \right) = V_1 = 9 \text{ V} \quad [\text{turn ratio } 1 : 1]$$

$D_1$  is forward biased and voltage drop in diode  $V_{D1} = 1 \text{ V}$ .

$D_2$  is reversed biased and acts as open circuit.

Capacitor behaves as open circuit for DC voltage. Forward voltage drop of gate cathode junction

$$V_{gk} = 1 \text{ V}$$

Voltage drop across resistor  $R$ ,


$$V_R = V_2 - V_{D1} - V_{gk} = 9 - 1 - 1 = 7 \text{ V}$$

To ensure turn -ON of SCR,

$$R = \frac{V_R}{I_{g(\max)}} = \frac{7}{150 \text{ mA}} \approx 47 \Omega$$

**T7 : Solution**

(a)

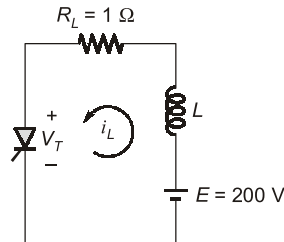

Forward voltage drop of SCR during ON-state

$$V_T = 1 \text{ V}$$

$$E - \frac{L di_a}{dt} - R i_a - V_T = 0$$

$$\Rightarrow 200 - 0.15 \frac{di_a}{dt} - i_a - 1 = 0$$

$$\Rightarrow i_a = 199(1 - e^{-t/0.15})$$

Gate pulse width required = time taken by  $i_a$  to rise upto  $I_L = T$

$$\Rightarrow 250 \times 10^{-3} = 199(1 - e^{-T/0.15})$$

$$T = 188.56 \mu\text{s}$$

Width of the pulse,  $T = 188.56 \mu\text{s}$


Magnitude of voltage,  $V = 10 \text{ V}$

Voltage second rating of  $PT$

$$VT = T = 10 \times 188.56 \mu\text{s} = 1885.6 \text{ V-s} \approx 2000 \mu\text{s}$$


**T8 : Solution**

(d)

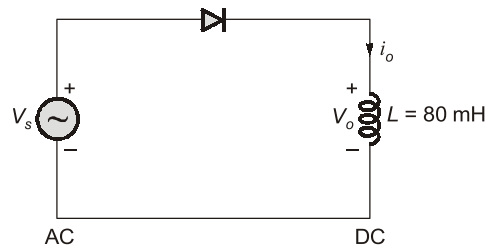

$$V_s = 230 \cos \omega t$$

$$\omega = 314 \text{ rad/sec}$$

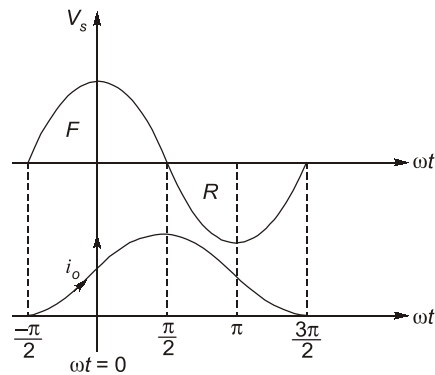

Diode will turn on at  $\omega t = -\frac{\pi}{2}$

Applying KVL

$$V_s = V_o$$

$$V_m \cos \omega t = L \frac{di}{dt}$$

$$\int di = \int \frac{V_m \cos \omega t}{L} dt$$

$$i_o = \frac{V_m}{\omega L} \sin \omega t + K$$

At  $\omega t = -\frac{\pi}{2}$ ,

$$i_o = 0$$

$$0 = \frac{V_m}{\omega L} \sin\left(-\frac{\pi}{2}\right) + K$$

$$K = \frac{V_m}{\omega L}$$


$$i_o = \frac{V_m}{\omega L} \sin \omega t + \frac{V_m}{\omega L}$$

At  $\omega t = \frac{\pi}{2}$

$$\begin{aligned} i_{\text{peak}} &= \frac{V_m}{\omega L} \sin \frac{\pi}{2} + \frac{V_m}{\omega L} \\ &= \frac{2V_m}{\omega L} = \frac{2 \times 230}{314 \times 80 \times 10^{-3}} \\ &= 18.31 \text{ A} \end{aligned}$$

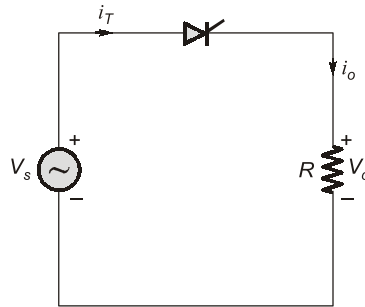**T9 : Solution**

$$(I_T)_{\text{RMS rating}} = 35 \text{ A}$$



$$i_T = i_o$$

$$\begin{aligned} \text{Form factor} &= \frac{(I_T)_{\text{RMS}}}{(I_T)_{\text{Avg}}} \\ &= \frac{I_{or}}{I_o} \\ &= \frac{V_{or}/R}{V_o/R} \\ &= \frac{V_{or}}{V_o} \\ \text{Form factor} &= \frac{\frac{V_m}{\sqrt{2 \times 2\pi}} \left\{ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right\}^{\frac{1}{2}}}{\frac{V_m}{2\pi} [1 + \cos \alpha]} = 3.98 \end{aligned}$$

Put  $\alpha = \frac{\pi}{6}$

**Note :** At  $\alpha = 0$ , conduction angle of SCR is maximum.

$$\begin{aligned} (I_T)_{\text{Avg rating}} &= \frac{(I_T)_{\text{RMS Rating}}}{\text{Form Factor}} \\ &= \frac{35}{FF} \\ &= \frac{35}{3.98} = 8.79 \end{aligned}$$

**T10 : Solution**

$$\begin{aligned} \text{Energy} &= \int_0^{T_1} V \cdot i \, dt + \int_0^{T_2} v \cdot i \, dt \\ &= V \left[ \frac{1}{2} I T_1 \right] + I \left[ \frac{1}{2} V T_2 \right] \end{aligned}$$

$$= 600 \left[ \frac{150}{2} \times 1 \times 10^{-6} \right] + 100 \left[ \frac{1}{2} \times 600 \times 1 \times 10^{-6} \right]$$

Energy = 75 mJ

**T11 : Solution**

(c)

Derating factor = 1 – String efficiency

$$0.2 = 1 - \frac{6000}{n_s \times 1000} = 1 - \frac{1000}{n_p \times 200}$$

$$n_s = 7.5 \approx 8$$

$$n_p = 6.25 \approx 7$$

**T12 : Solution**

(b)

$$P_{\text{avg}} = I_{\text{rms}}^2 \cdot R_{\text{ON}}$$

$$R_{\text{ON}} = 0.15 \, \Omega \text{ and } I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^\pi 10t \, dt} = \frac{10}{\sqrt{6}}$$

$$P_{\text{avg}} = \frac{100}{6} \times 0.15 = 2.50 \, \text{W}$$





# 2

## Controlled and Uncontrolled Rectifiers



### Detailed Explanation of Try Yourself Questions

#### T1 : Solution

(b)

Average output voltage

$$V_0 = \frac{2V_m}{\pi} \cos \alpha = \frac{2\sqrt{2} \times 230}{\pi} \cos 45^\circ = 146.42 \text{ V}$$

$$I_0 = \frac{V_0}{R} = \frac{146.42}{10} = 14.642 \text{ A}$$

Reactive power input to the converter is

$$\begin{aligned} Q_i &= \frac{2V_m}{\pi} I_0 \sin \alpha \\ &= \frac{2\sqrt{2} \times 230}{\pi} \times 14.642 \times \sin 45^\circ \\ Q_i &= 2143.92 \text{ VAR} \end{aligned}$$

#### T2 : Solution

$$\begin{aligned} V_0 &= L \frac{di}{dt} = V_s \\ \int di &= \int \frac{V_s}{L} dt = \int \frac{100 \sin \omega t}{L} dt \\ i_0 &= -\frac{100}{\omega L} \cos \omega t + K \end{aligned}$$

$$\omega t = 100\pi \times 2.5 \times 10^{-3} = \frac{\pi}{4}$$

$$i_0(t = 2.5 \text{ ms}) = 0$$

$$\frac{-100 \cos 45^\circ}{100\pi \times 31.83 \times 10^{-3}} + K = 0$$

$$K = 7.07$$

$$i_0 = -10 \cos \omega t + 7.07$$

$$i_{0, \text{peak}} = -10 \cos \pi + 7.07 \\ = 17.07 \text{ A}$$

**T3 : Solution**

The half-wave diode rectifier uses a step-up transformer, therefore, ac voltage applied to rectifier  
 $= 230 \times 460 \text{ V} = V_s$

Average value of load voltage

$$V_0 = \frac{V_m}{\pi} = \frac{\sqrt{2} \times 460}{\pi} = 207.04 \text{ V}$$

Output dc power,  $P_{dc} = \frac{V_0^2}{R} = \frac{207.04^2}{60} = 714.43 \text{ W}$


It is seen from the table that *TUF* for 1-phase half-wave diode rectifier is 0.2865.

$$\therefore \text{VA rating of transformer} = \frac{P_{dc}}{TUF} = \frac{714.43}{0.2865} = 2493.65 \text{ VA}$$

So, choose a transformer with 2.5 kVA (next round figure) rating.

**T4 : Solution**

(1.05)

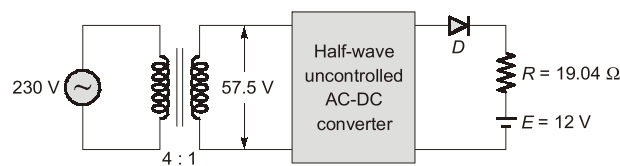


Input to the converter,  $V_s = \left(\frac{1}{4}\right) 230 = 57.5 \text{ V}$

Diode conducts when  $V_s \geq E$

$$V_m \sin \theta_1 = E$$

$$57.5\sqrt{2} \sin \theta_1 = 12$$
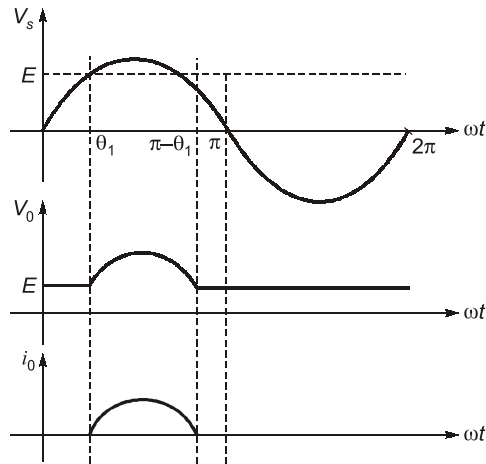
$$\theta_1 = 8.486^\circ \text{ or } 0.148 \text{ rad}$$



Charging current flows during  $\theta_1 \leq \omega t \leq \pi - \theta_1$  and can be expressed as,

$$I_0 = \frac{1}{2\pi} \int_0^{2\pi} i_0 d\omega t = \frac{1}{2\pi} \int_{\theta_1}^{\pi - \theta_1} \left( \frac{V_m \sin \omega t - E}{R} \right) d\omega t$$

$$I_0 = \frac{1}{2\pi R} [2V_m \cos \theta_1 - E(\pi - 2\theta_1)]$$

$$= \frac{1}{2\pi \times 19.04} [2 \times 57.5\sqrt{2} \times \cos 8.486^\circ - 12 \times (\pi - 2 \times 0.148)]$$

$$= 1.05 \text{ A}$$

**T5 : Solution**

(d)


$$\alpha = 60^\circ, V_{YB} = V_{ML} \sin \omega t \text{ (Ref)}$$

Lower limit,

$$L = 60 + \alpha = 120^\circ = \frac{2\pi}{3} \text{ rad}$$

Upper limit,
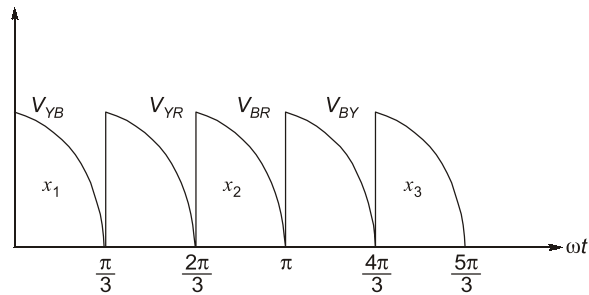
$$U = 120 + \alpha = 180^\circ = \pi \text{ rad}$$




$$x_1 \rightarrow V_{RY}$$

$$x_2 \rightarrow V_{YB}$$


$$x_3 \rightarrow V_{BR}$$

**T6 : Solution**

(b)

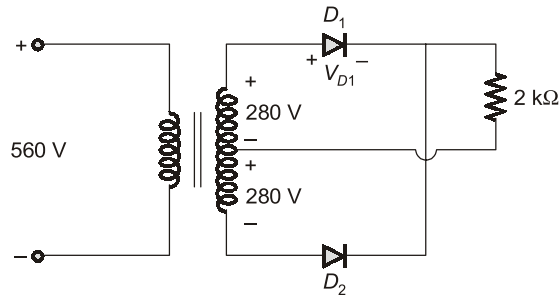

$$V_s = 280\sqrt{2} \sin \omega t$$

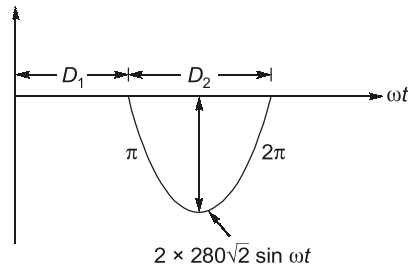

$$\text{P.I.V.} = 2 \times 280\sqrt{2}$$

The rms voltage across diode

$$= 280\sqrt{2} = 395.3 \text{ V}$$

**T7 : Solution**

(c)

Frequency of the voltage source,  $f = 50 \text{ Hz}$

Time period,  $T = \frac{1}{f} = \frac{1}{50} = 20 \text{ ms}$ .

During positive half cycle of the source voltage,  $0 < t < \frac{T}{2}$ , energy is stored in the inductor and current increases.

During negative half cycle of the source voltage,  $\frac{T}{2} \leq t \leq T$ , current decreases and energy stored in the inductor is delivered to source.

**T8 : Solution**

(b)

$$V_s = 100\sqrt{2} \sin(100\pi t)$$

$$i = 10\sqrt{2} \sin\left(100\pi t - \frac{\pi}{3}\right) + 5\sqrt{2} \sin\left(300\pi t + \frac{\pi}{4}\right) + 2\sqrt{2} \sin\left(500\pi t - \frac{\pi}{6}\right) \text{ A}$$

$$\begin{aligned} \text{Active power} &= V_{sr} I_{s1} \cos \phi_1 \\ &= 100 \times 10 \times \cos 60^\circ \\ &= 500 \text{ W} \end{aligned}$$

**T9 : Solution**

(b)

Rms value of input voltage,

$$V_{\text{rms}} = \frac{100\sqrt{2}}{\sqrt{2}} = 100 \text{ V}$$

Rms value of current,

$$I_{\text{rms}} = \sqrt{\left(\frac{10\sqrt{2}}{\sqrt{2}}\right)^2 + \left(\frac{5\sqrt{2}}{\sqrt{2}}\right)^2 + \left(\frac{2\sqrt{2}}{\sqrt{2}}\right)^2} = 11.358 \text{ A}$$

Let input power factor  $\cos \phi$

$$V_{\text{rms}} I_{\text{rms}} \cos \phi = \text{active power drawn by the converter}$$

$$\Rightarrow 100 \times 11.358 \times \cos \phi = 500 \text{ W}$$

$$\Rightarrow \cos \phi = 0.44$$

**T10 : Solution**

(c)

$$i_s \propto \frac{I_a}{n} \cdot \cos \frac{n\pi}{6} \quad \text{where } n \in 1, 3, 5$$

For  $n = 3$ ,


$$i_s = 0$$

For  $n = 5$ ,

$$i_s \propto -\frac{I_a}{5}$$

Lowest harmonic present is fifth harmonic. Its frequency =  $50 \times 5 = 250 \text{ Hz}$ .

**T11 : Solution**

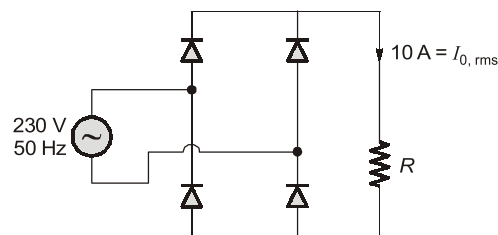


$$I_{0,rms} = \frac{V_s}{R} \Rightarrow R = \frac{230}{10} = 23 \Omega$$

**T12 : Solution**

(c)

$T_1$  and  $T_4$  gets forward biased, when

$$V_m \sin \theta_1 \leq E$$

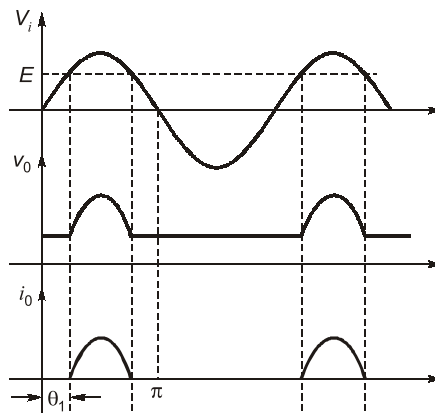

$I_{avg}$  = (Average current)

$$= \frac{1}{2\pi R} \int_{\theta_1}^{\pi - \theta_1} (V_m \sin \omega t - E) d\theta$$

$$\begin{aligned} \therefore I_0(\text{avg}) &= \frac{1}{2\pi R} [2V_m \cos \theta - E(\pi - 2\theta_1)] \\ &= \frac{1}{2\pi \times 2} [2 \times (230 \times \sqrt{2}) \cos \theta_1 - 200(\pi - 2\theta_1)] \end{aligned}$$


where,

$$\begin{aligned} \theta_1 &= \sin^{-1} \left( \frac{E}{V_m} \right) \\ &= \sin^{-1} \left( \frac{200}{230 \times \sqrt{2}} \right) = 38^\circ = 0.66 \text{ rad} \end{aligned}$$

$$\therefore I_0(\text{avg}) = \frac{1}{2\pi \times 2} [2\sqrt{2} \times 230 \cos 38^\circ - 200(\pi - 2 \times 0.66)] = 11.9 \text{ A}$$
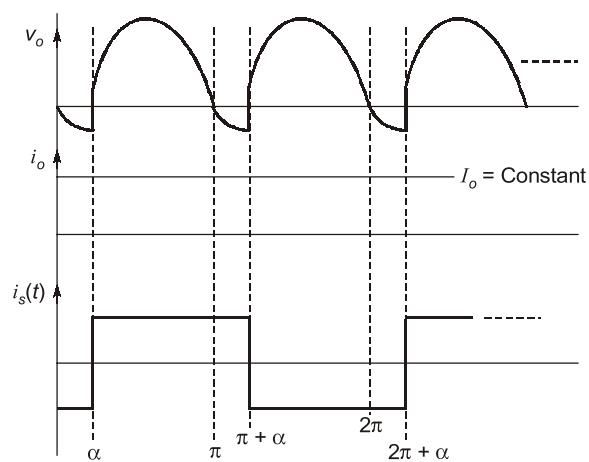
### T13 : Solution

Output waveforms of highly inductive load (without F.W. diode).



Fourier series of supply current is given as

$$i_s(t) = \sum_{n=1,3,5}^{\infty} \frac{4I_o}{n\pi} \sin n\omega_o t$$

Frequency components present in supply current is  
1<sup>st</sup>, 3<sup>rd</sup>, 5<sup>th</sup>, 7<sup>th</sup> : all odd frequencies.

Two most dominant harmonics are 3<sup>rd</sup> and 5<sup>th</sup>, i.e., 150 Hz and 250 Hz.

Two most dominant frequencies are 1<sup>st</sup> and 3<sup>rd</sup>, i.e., 50 Hz and 150 Hz.

Except fundamental, all other frequencies are harmonics in supply current.

**T14 : Solution**

1- $\phi$ , SCR bridge rectifier

$$\alpha = 45^\circ, R = 10 \Omega$$

supply 230 V, 50 Hz

$$L_s = 2.28 \text{ mH}, \mu = ?$$

$$\Delta V_d = \frac{V_m}{\pi} [\cos \alpha - \cos(\alpha + \mu)] = 4f L_s I_o$$

$$V_o = \frac{2V_m}{\pi} \cos \alpha - 4f L_s I_o \text{ (with } L_s)$$

$$I_o R = \frac{2V_m}{\pi} \cos \alpha - 4f L_s I_o$$

Find  $I_o$

$$I_o \times 10 = \frac{2 \times 230\sqrt{2}}{\pi} \cdot \cos 45 - 4 \times 50 \times 2.28 \times 10^{-3} I_o$$

$$I_o(10 + 0.456) = 146.42$$

$$I_o = \frac{146.49}{10.456} = 14.0036 \text{ A}$$

$$\begin{aligned} \Delta V_{d0} &= \frac{230\sqrt{2}}{\pi} [\cos 45 - \cos(45 + \mu)] \\ &= 4 \times 50 \times 2.28 \times 10^{-3} \times 14 = 6.384 \end{aligned}$$

$$\cos 45^\circ - \cos(45^\circ + \mu) = 0.061659$$

$$45 + \mu = 49.80 \Rightarrow \mu = 4.80^\circ$$

**T15 : Solution**

$$V_o = 2 \frac{V_m}{\pi} \cos \alpha = 2 \frac{200\pi}{\pi} \cos 120^\circ$$

$$V_o = -200 \text{ V}$$

$$|V_o| = 200 \text{ V}$$

Power balance equation,

$$EI_o = I_o^2 R + V_o I_o$$


$$800 I_o = I_o^2(20) + 200 I_o \Rightarrow I_o = 30 \text{ A}$$

$$I_o = I_{or}$$

Power fed to source

$$= V_o I_o = 200 \times 30 = 6 \text{ kW}$$

## T16 : Solution

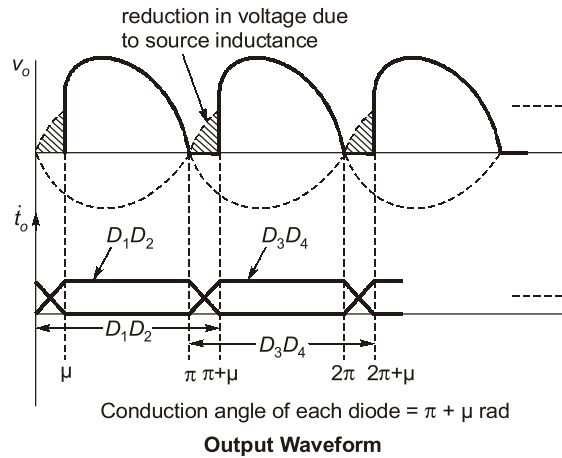

$$V_{\alpha(\text{avg})} = \frac{2V_m}{\pi} \quad (\because \text{without } L_s)$$

$$V_{\alpha(\text{avg})} = \frac{1}{\pi} \int_{\mu}^{\pi} V_m \sin \omega t \cdot d\omega t \quad (\because \text{with } L_s)$$

$$= \frac{V_m}{\pi} [1 + \cos \mu]$$

$$\Delta V_{do} = V_{\alpha(\text{avg})} - V_{\alpha(\text{avg})} = \frac{V_m}{\pi} [1 - \cos \mu]$$

and

On equating,

$$\frac{V_m}{\pi} [1 - \cos \mu] = 4fL_s I_o$$

$$\frac{220\sqrt{2}}{\pi} (1 - \cos \mu) = 4 \times 50 \times 10 \times 10^{-3} \times 14$$

On solving,

$$\mu = 44.17^\circ$$

So, conduction angle of each diode

$$\gamma_D = 180^\circ + \mu = 180^\circ + 44.17^\circ = 224.17^\circ$$

## T17 : Solution

$$V_o = \frac{V_m}{2\pi} (3 + \cos \alpha)$$

$$E_b I_o = 1600 \text{ W}$$

$$I_o = \frac{1600}{80} = 20 \text{ A}$$

$$V_o = E_b + I_o R_a$$

$$\frac{V_m}{2\pi} (3 + \cos \alpha) = 80 + (20 \times 2)$$



$$\frac{80\pi}{2\pi}(3 + \cos \alpha) = 80 + 40$$

$$\alpha = 90^\circ$$

**T18 : Solution**

(0.78)

$$V_{sr} I_{sr} \cos \phi = V_0 I_0$$



For single-phase fully controlled converter,

$$I_0 = I_{sr} = 10 \text{ A}$$

$$\cos \phi = \frac{V_0}{V_{sr}} = \frac{180}{230} = 0.78$$

**T19 : Solution**

(a, c, d)

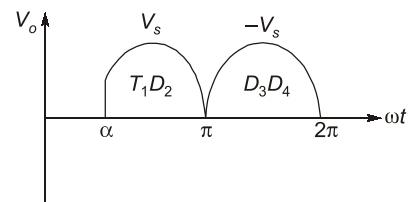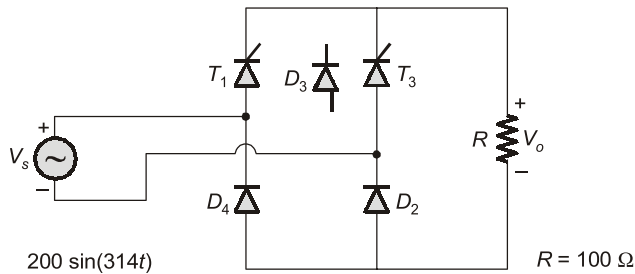

$$V_o = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t + \int_{\pi}^{2\pi} -V_m \sin \omega t d\omega t \right]$$

$$V_o = \frac{V_m}{2\pi} [3 + \cos \alpha]$$

$$= \frac{200}{2\pi} [3 + \cos 60^\circ] = 111.4 \text{ V}$$

$$I_o = \frac{V_o}{R} = \frac{111.4}{100} = 1.114 \text{ A}$$

$$I_{T1, \text{avg}} = \frac{1}{2\pi} \int_{\alpha}^{\pi} \frac{V_m \sin \omega t}{R} d\omega t$$

$$I_{T1} = \frac{V_m}{2\pi R} [1 + \cos \alpha] = \frac{200}{2\pi \times 100} [1 + \cos 60^\circ]$$

$$= 0.4774 \text{ A}$$

$$\text{Power drawn by load } P_o = V_{o, \text{rms}} I_{o, \text{rms}} = \frac{V_o^2}{R}$$



# 3

## Choppers



### Detailed Explanation of Try Yourself Questions

#### T1 : Solution

Circuit turnoff time,

$$t_c = \frac{CV_s}{I_0} = \frac{8 \times 10^{-6} \times 250}{20} = 1 \times 10^{-4} \text{ s}$$

Maximum value of duty cycle,

$$\begin{aligned} \alpha_{\max} &= (1 - 2ft_c) \\ &= (1 - 2 \times 250 \times 1 \times 10^{-4}) \end{aligned}$$

$$\alpha_{\max} = 0.95$$


maximum load or output voltage,

$$\begin{aligned} V_{0, \max} &= V_s[\alpha_{\max} + 2ft_c] \\ &= 250[0.95 + (2 \times 250 \times 1 \times 10^{-4})] \end{aligned}$$

$$V_{0, \max} = 250 \text{ V}$$

#### T2 : Solution

(24)

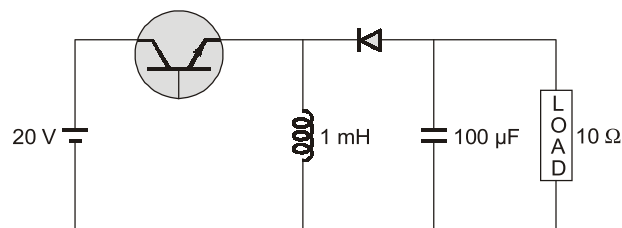

$$\alpha = 0.75, \quad f = 25 \text{ kHz}$$

Assume continuous conduction:

$$V_o = \frac{\alpha V_s}{1 - \alpha} = \frac{0.75 \times 20}{1 - 0.75}$$

$$V_o = 60 \text{ V}$$

$$I_o = \frac{V_o}{R} = \frac{60}{10} = 6 \text{ A}$$

$$I_L = \frac{I_o}{1 - \alpha} = \frac{6}{1 - 0.75} = 24 \text{ A}$$

$$\Delta I_L = \frac{\alpha V_s}{f_L}$$

$$= \frac{0.75 \times 60}{25 \times 10^3 \times (1 \times 10^{-3})} = 1.8 \text{ A}$$

$$I_{L \min} = I_L - \frac{\Delta I_L}{2} = 24 - \frac{1.8}{2} = 24 - 0.9$$


$$(I_{L \min} = 23.1 \text{ A}) > 0$$

∴ Continuous conduction assumption is correct.

$$I_L = 24 \text{ A}$$

**T3 : Solution**

(c)

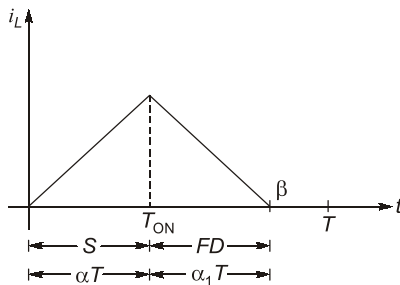

S → ON :

KVL :

$$-V_s + V_L + V_o = 0$$

$$V_L = V_s - V_o$$


$$L \frac{di_L}{dt} = V_s - V_o$$

$$\frac{di_L}{dt} = \frac{V_s - V_o}{L}$$

R ↑, I\_o ↓

∴ I\_L ↓ ∴ Area ↓ ∴ β ↓ ∴ V\_o ↑
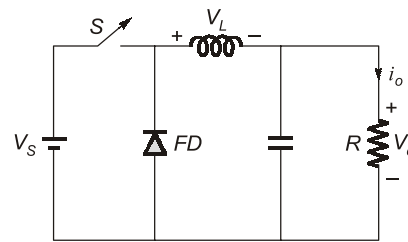
$$\uparrow V_o = \frac{\alpha V_s}{\beta \downarrow}$$



S → OFF, FD → ON



$$V_L + V_o = 0$$

$$V_L = -V_o$$

$$L \frac{di_L}{dt} = -V_o$$

$$\frac{di_L}{dt} = \frac{-V_o}{L}$$

## T4 : Solution

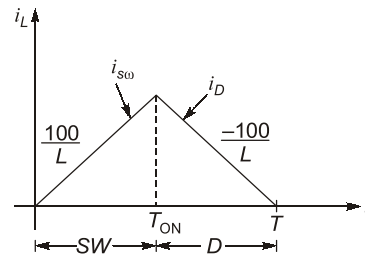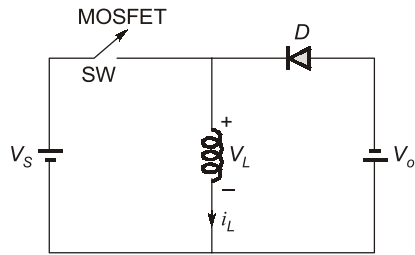

$$f = 1000 \text{ kHz}$$

$$T = 10 \mu\text{sec}$$

$$\alpha = 0.5$$

$$T_{\text{ON}} = \alpha \cdot T = \alpha \times 10 \mu\text{sec} = 0.5 \times 10 \mu\text{sec} = 5 \mu\text{sec}$$

$$V_s = R_{DS} i_{sw} + L \frac{di_L}{dt} \quad (\text{Neglect } R_{DS} i_{sw})$$

$$V_s = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{V_s}{L} = \frac{100}{L}$$

$$V_o = \frac{\alpha V_s}{1 - \alpha} \quad (\text{at } \alpha = 0.5)$$

$$V_o = V_s = 100 \text{ V}$$

At the boundary,

$$0 \geq t \leq T_{\text{ON}}$$

$\therefore$

$$i_{sw} = \frac{100}{L} t$$

$$I_{sw, \text{rms}} = \left\{ \frac{1}{T} \int_0^{T_{\text{ON}}} i_{sw}^2 dt \right\}^{\frac{1}{2}}$$

$$= \frac{1}{T} \int_0^{T_{\text{ON}}} \left( \frac{100}{L} t \right)^2 dt$$

$$T = \frac{1}{f} = 10 \mu\text{sec}$$

$$T_{\text{ON}} = \alpha T = 5 \mu\text{sec}$$

$$L = 100 \mu\text{H}$$


$$I_{sw, \text{rms}}^2 = \frac{1}{T} \int_0^{T_{\text{ON}}} \left( \frac{100}{L} t \right)^2 dt = 4.1667 \text{ A}^2$$

Condition power loss in MOSFET

$$= I_{sw, \text{rms}}^2 \cdot R_{DS} = 4.1667 \times 1 = 4.1667 \text{ W}$$

**T5 : Solution**

(c)

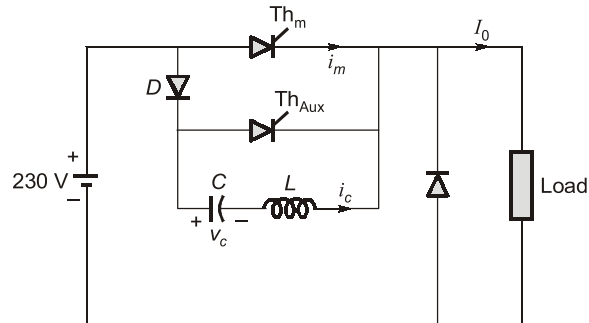

At  $t = 0^-$ ,  $v_c = V_s$ ,  $i_c = 0$  and  $i_{T1} = I_0$ .

At  $t = 0$ ,  $Th_{Aux}$  is triggered, a resonant current  $i_c$  designs to flow from  $C$  through  $Th_{Aux}$ ,  $L$  and back to  $C$ . This resonant current is given by

$$i_c = -V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$$

$$= -I_p \sin \omega_0 t$$

After half a cycle of  $i_c \left\{ t_1 = \frac{\pi}{\omega_0} \right\}$ ;

$i_c = 0$ ,  $v_c = -V_s$  and  $i_{T1} = I_0$ . As  $i_c$  tends to reverse,  $Th_{Aux}$  is turned off.

When  $v_c = -V_s$ , right hand plate has positive polarity, resonant current  $i_c$  now builds up through  $C$ ,  $L$ ,  $D$  and  $Th_m$ . As this current  $i_c$  grows opposite to forward thyristor current of  $Th_m$ , net forward current  $i_m = I_0 - i_c$  begins to decrease. Finally when  $i_c$  in the reversed direction attains the value  $I_0$ ,  $i_m$  is reduced to zero and  $Th_m$  is turned off.

$$i_m = I_0 - i_c$$

$$= I_0 - I_p \sin \omega_0 \Delta t = 0$$

$$\Delta t = \frac{1}{\omega_0} \sin^{-1} \left( \frac{I_0}{I_p} \right)$$

So,  $Th_m$  is turned off between

$$t_1 < t < t_1 + \Delta t$$

$$t_1 = \frac{\pi}{\omega_0} = \pi \sqrt{LC}$$

$$= \pi \times \sqrt{10 \times 25.28}$$

$$= 50 \mu \text{ sec}$$

Option (c) is correct.

Since, commutation of  $Th_m$  starts from  $t_1 = 50 \mu \text{sec}$ .

**T6 : Solution**

(1.60)

Checking for continuous conduction mode

$$\Delta I_L = \frac{\alpha V_S}{fL} = \frac{0.6 \times 15}{25 \times 10^3 \times 1 \times 10^{-3}} = 0.36 \text{ A}$$

$$\frac{\Delta I_L}{2} = 0.18 \text{ A}$$

$$I_{L,\min} = I_L - \frac{\Delta I_L}{2} = I_S - \frac{\Delta I_L}{2}$$

$$= (9.375 - 0.18) = 9.195 > 0$$

As it is continuous conduction

$$V_0 = \frac{V_S}{1-\alpha} = \frac{15}{1-0.6} = 37.5 \text{ V}$$

$$I_0 = \frac{V_0}{R} = \frac{37.5}{10} = 3.75 \text{ A}$$

$$\frac{V_0}{V_S} = \frac{I_S}{I_0} = \frac{1}{1-\alpha}$$


$$I_S = \frac{I_0}{1-\alpha} = \frac{3.75}{1-0.6} = 9.375 \text{ A}$$

$$R_{\text{in}} = \frac{V_S}{I_S} = \frac{15}{9.375} = 1.6 \Omega$$

**T7 : Solution**

(b)

Stepdown chopper:

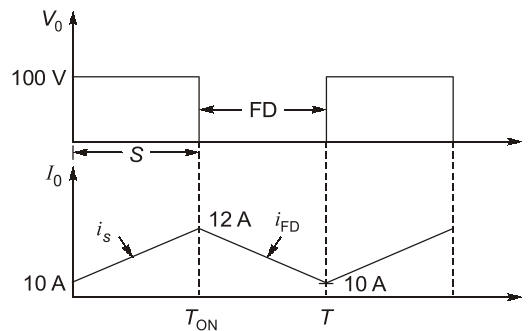

$$\tau = \frac{L}{R} = \frac{40 \cdot 10^{-3}}{5} = 8 \cdot 10^{-3}$$

$$V_0 = \alpha V_S$$

S → ON:

$$V_S = R i_s + L \frac{d i_s}{d t}$$

$$\begin{aligned} i_s &= \frac{V_s}{R} \left(1 - e^{-t/8.10^{-3}}\right) + 10 \cdot e^{-t/8.10^{-3}} \\ &= \frac{100}{5} \left(1 - e^{-t/8.10^{-3}}\right) + 10 \cdot e^{-t/8.10^{-3}} \\ &= 20 \left(1 - e^{-t/8.10^{-3}}\right) + 10 \cdot e^{-t/8.10^{-3}} \end{aligned}$$

$$i_s = 20 - 10 e^{-t/8.10^{-3}}$$

At  $t = T_{ON}$ ,  $i_s = 12 \text{ A}$

$$\therefore 12 \text{ A} = 20 - 10 e^{-T_{ON}/8.10^{-3}}$$

$$10 e^{-T_{ON}/8.10^{-3}} = 8$$

$$e^{-T_{ON}/8.10^{-3}} = 0.8$$

$$\frac{-T_{ON}}{8.10^{-3}} = -0.223$$

$$T_{ON} = 1.785 \times 10^{-3} = 1.785 \text{ ms}$$

FD  $\rightarrow$  ON:

$$\begin{aligned} i_{FD} &= 12 \cdot e^{-t'/\tau} \\ &= 12 \cdot e^{-t'/8.10^{-3}} \end{aligned}$$

At  $t' = T_{OFF}$ ,  $i_{FD} = 10 \text{ A}$

$$10 = 12 \cdot e^{-T_{OFF}/8.10^{-3}}$$

$$e^{-T_{OFF}/8.10^{-3}} = \frac{10}{12}$$

$$\frac{-T_{OFF}}{8.10^{-3}} = -0.182$$

$$T_{OFF} = 1.458 \text{ ms}$$

$$\text{Time ratio} = \frac{T_{ON}}{T_{OFF}} = \frac{1.785}{1.458} = 1.22$$

Alternate Solution :

$$I_{\alpha(\text{avg})} = \frac{I_{\alpha(\text{max})} + I_{\alpha(\text{min})}}{2}$$

$$I_{\alpha(\text{avg})} = \frac{12 + 10}{2} = 11 \text{ A}$$

$$\begin{aligned} V_{\alpha(\text{avg})} &= I_{\alpha(\text{avg})} \times R \\ &= 11 \times 5 = 55 \text{ V} \end{aligned}$$

and

$$V_{\alpha(\text{avg})} = \frac{T_{\text{on}}}{T} V_s$$


$$\frac{55}{100} = \frac{T_{\text{on}}}{T}$$

$$\frac{T_{off}}{T} = \frac{T - T_{on}}{T} = \frac{45}{100} T$$

So,

$$\frac{T_{on}}{T_{off}} = \frac{55}{45} = \frac{11}{9} = 1.222$$

**T8 : Solution**

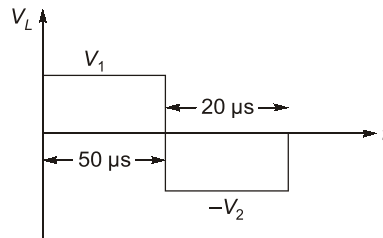

$$V_1 \times 50 \mu\text{sec} = V_2 \cdot 20 \mu\text{sec} = 0$$

$$\frac{V_1}{V_2} = \frac{2}{5}$$

**T9 : Solution**

(2500)

On the verge of discontinuity

$$L = L_c \text{ (critical inductance)}$$

$$I_{L,\text{min}} = 0$$

$$I_{L(\text{avg})} - \frac{\Delta I_L}{2} = 0 \Rightarrow I_{L(\text{avg})} = \frac{\Delta I_L}{2}$$

$$I_{L(\text{avg})} = \frac{D(1-D) \cdot V_s}{2fL} \quad \{ \because I_{L(\text{avg})} = I_{o(\text{avg})} \}$$

$$\frac{V_{o(\text{avg})}}{R} = \frac{D(1-D)V_s}{2fL}$$


$$\frac{36}{R} = \frac{60 \times 0.4 \times 0.6}{2 \times 100 \times 10^3 \times 5 \times 10^{-3}}$$

On solving,  $R = 2500 \Omega$

**T10 : Solution**

(Sol)

$$\frac{V_o}{V_s} = \frac{1}{1-\alpha}$$

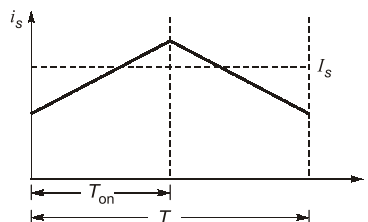



$$\frac{400}{360} = \frac{1}{1-\alpha}$$

$$\alpha = 0.1$$

$$V_s I_s = \text{Power}$$

$$360 I_s = 4000 \Rightarrow I_s = 11.1 \text{ A}$$

Neglecting ripple in  $i_s$ ,

$$I_{\text{switch (rms)}} = I_s \left( \frac{T_{\text{on}}}{T} \right)^{1/2}$$

$$= I_s \sqrt{\alpha} = 11.1 \sqrt{0.1} = 3.5 \text{ A}$$

**T11 : Solution**

Buckboost converter,

$$V_0 = \frac{\alpha V_s}{1-\alpha}$$

$$V_s = 50 \text{ V}$$



$$\alpha = 0.6$$

$$V_0 = 75 \text{ V}$$

$$\frac{V_0}{V_s} = \frac{I_s}{I_0} = \frac{\alpha}{1-\alpha} = \frac{0.6}{1-0.6} = \frac{0.6}{0.4} = \frac{3}{2}$$

$$I_0 = \frac{V_0}{R} = \frac{75}{5} = 15 \text{ A}$$
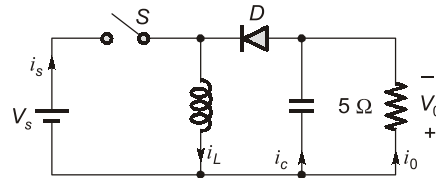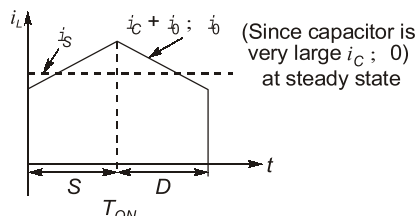
$$I_s = \frac{\alpha}{1-\alpha} \cdot I_0 = \frac{3}{2} \times 15 = 22.5 \text{ A}$$



Since capacitor is very large  $i_C = 0$  at steady state

$$(i_L)_{\text{avg}} = (i_s)_{\text{avg}} + (i_0)_{\text{avg}}$$

$$I_L = I_s + I_0$$

$$I_L = 22.5 + 15 = 37.5 \text{ A}$$

$\therefore$

$$I_L = 37.5 \text{ A}$$

$$\Delta I_L = \frac{\alpha V_S}{fL} = \frac{0.6 \times 50}{10 \times 10^3 \times (0.6 \times 10^{-3})} = 5 \text{ A}$$

$$(i_L)_{\text{peak}} = I_L + \frac{\Delta I_L}{2} = 37.5 + \frac{5}{2} = 40 \text{ A}$$

∴ Peak value of current drawn from source  
=  $(i_L)_{\text{peak}} = 40 \text{ A}$

**T12 : Solution**

(a, c)

$$I_o = 10 \text{ A}$$

$$\alpha = 0.45$$

$$f = 80 \text{ kHz}$$

$$L = 10 \text{ mH}$$

$$C = 120 \mu\text{F}$$

$$I_S = I_L = \frac{I_o}{1-\alpha} = \frac{10}{1-0.45} = 18.18 \text{ A}$$

$$\Delta V_C = AV_o = \frac{\alpha I_o}{fC} = \frac{0.45 \times 10}{80 \times 10^3 \times 120 \times 10^{-6}} = 0.468 \text{ V}$$

$$I_{s0} = \alpha I_S = 0.45 \times 18.18 = 8.18 \text{ A}$$

**T13 : Solution**

(a)

Apply boundary conditions,

$$I_L = \frac{\Delta I_L}{2}$$

Inductor current,  $I_L = \frac{I_o}{1-D}$

$$\therefore \frac{I_o}{1-D} = \frac{DV_s}{2fL}$$

$$\frac{V_s}{R(1-D)^2} = \frac{DV_s}{2fL}$$

$$f = \frac{D(1-D)^2 R}{2L} = \frac{0.6 \times (1-0.6)^2 \times 50}{2 \times 100 \times 10^{-6}}$$

$$f = 24 \text{ kHz}$$

■■■■

# 4

## Inverters



### Detailed Explanation of Try Yourself Questions

#### T1 : Solution

$$R_{\Delta} = 30 \Omega/\text{phase}$$

$$R_Y = 10 \Omega/\text{phase}$$


$$V_{0, \text{line}} = V_s \sqrt{\frac{2}{3}}$$

$$V_{0, \text{phase}} = \frac{V_s \sqrt{2}}{3} = \frac{600\sqrt{2}}{3} = 200\sqrt{2} \text{ V}$$

$$P_0 = \frac{3V_{0, \text{phase}}^2}{R} = \frac{3 \times (200\sqrt{2})^2}{10} = 24 \text{ kW}$$

#### T2 : Solution

(a)

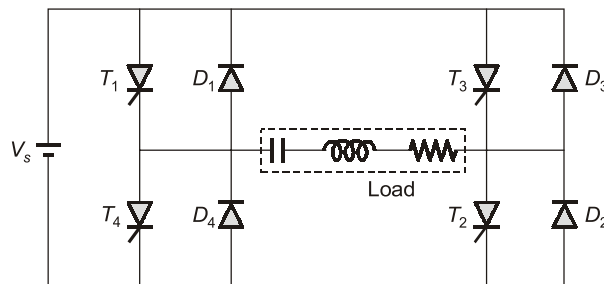

(a) Distortion factor,

$$g = \frac{\text{Fundamental RMS Voltage}}{\text{Total RMS Voltage}}$$

$$g = \frac{V_{o1}}{V_{or}}$$

For 1-phase full bridge,

$$V_{o1} = \frac{2\sqrt{2}}{\pi} V_s$$

$$V_{or} = V_s$$

$$\therefore g = \frac{2\sqrt{2}}{\pi} = 0.9$$

Total harmonic distortion,

$$\text{THD} = \sqrt{\frac{1}{g^2} - 1}$$

$$\text{THD} = 48.34\%$$

(b) For 1-phase full bridge

Fourier series of output voltage

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$

For RLC load

$$Z_n = R + j(X_{Cn} - X_{Ln})$$

$$|Z_n| = \sqrt{R^2 + (X_{Cn} - X_{Ln})^2}$$

$$\phi_n = \tan^{-1} \left( \frac{X_{Cn} - X_{Ln}}{R} \right)$$

Therefore, fourier series of load current

$$i_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi |Z_n|} \sin(n\omega t - \phi_n)$$

(c) Distortion factor,  $g = \frac{I_{o1}}{I_{or}}$

$$n^{\text{th}} \text{ harmonic current, } I_{on} = \frac{4V_s}{n\pi Z_n} \sin(n\omega t - \phi_n)$$

$$\therefore I_{o1} = \frac{4V_s}{\pi Z_n} \sin(\omega t - \phi_1)$$

$$\text{Rms output current, } I_{or} = \sqrt{I_{o1}^2 + I_{o3}^2 + I_{o5}^2 + \dots}$$

$$g = \frac{I_{o1}}{I_{or}} = 0.988$$

$$\text{THD\%} = \left( \sqrt{\frac{1}{g^2} - 1} \right) \times 100 = 15.55\%$$

(d) Load power,  $P = I_{or}^2 R$   
Considering only fundamental component of load current,

$$I_{or} = (I_{o1})_{\text{rms}}$$

$$(I_{o1})_{\text{rms}} = \frac{4V_s}{\pi Z_1} \times \frac{1}{\sqrt{2}}$$

$$= \frac{4 \times 220}{\pi \times \sqrt{\frac{1}{\omega C} - \omega L}} \times \frac{1}{\sqrt{2}}$$

$$= 19.402$$

$$P = I_{o1}^2 R = 2258.74 \text{ W}$$

Average DC source current,

$$I_s = \frac{1}{\pi} \int_0^\pi \sqrt{2} I_{o1} \sin(\omega t + 54^\circ) d\omega t$$

$$= 10.52 \text{ A}$$

(e) Conduction angle of diode,

$$\phi = \tan^{-1} \left( \frac{\frac{1}{\omega C} - \omega L}{R} \right)$$

$$= 54^\circ \text{ or } \frac{3}{10} \pi$$

Conduction time of diode,

$$\omega t_c = 54^\circ \text{ or } \frac{3}{10} \pi$$

$$t_c = 3 \text{ mS}$$

Conduction angle of transistor,

$$\pi - \phi = 126^\circ \text{ or } \frac{7}{10} \pi$$

Conduction time of transistor,

$$\omega t_c = 126^\circ \text{ or } \frac{7}{10} \pi$$

$$t_c = 7 \text{ mS}$$

(f)

$$(V_{o1})_{\text{rms}} = \frac{4V_s}{\sqrt{2} \times \pi} = 198.07 \text{ V}$$

$$(I_{o1})_{\text{rms}} = \frac{(V_{o1})_{\text{rms}}}{Z} = \frac{198.07}{\sqrt{k^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}} = 19.402$$

$$\phi_1 = 54^\circ \text{ or } \frac{3}{10} \pi$$

$$(I_{T1})_{\text{peak}} = 19.402 \times \sqrt{2} = 27.44 \text{ A}$$

$$(I_{T1})_{\text{rms}} = \left[ \frac{1}{2\pi} \int_0^{\frac{7}{10}\pi} (I_m \sin \omega t)^2 d(\omega t) \right]^{1/2}$$

$$= 12.66 \text{ A}$$

**T3 : Solution**

For 120° mode

$$V_L = \frac{V_S}{\sqrt{2}}$$

For  $\Delta$  load :

$$V_{Ph} = V_L = \frac{V_S}{\sqrt{2}}$$

$$I_{Phase} = \frac{V_{Ph}}{r} = \frac{V_S}{\sqrt{2}r} = \frac{200}{\sqrt{2} \times 15}$$

$$P = 3I_{Phase}^2 r = 3 \times \left( \frac{200}{\sqrt{2} \times 15} \right)^2 \times 15$$

$$= 4 \text{ kW}$$

**T4 : Solution**

(d)

**T5 : Solution**

(d)

As  $V_o < 0$ , ( $Q_3$ ,  $D_3$ ) and ( $Q_4$ ,  $D_4$ ) should work.

Also  $P = v_o i_o$

As  $I_o > 0$

$P < 0$


Power is being feedback.

So,  $D_3$  and  $D_4$  are working.

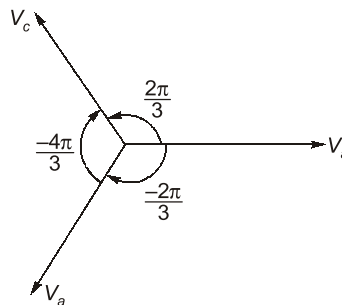**T6 : Solution**

$$V_a = V_{1m} \sin \omega t + V_{5m} \sin(5\omega t) + V_{7m} \sin(7\omega t)$$

$$V_b = V_{1m} \sin\left(\omega t - \frac{2\pi}{3}\right) + V_{5m} \sin 5\left(\omega t - \frac{2\pi}{3}\right) + V_{7m} \sin 7\left(\omega t - \frac{2\pi}{3}\right)$$



$$V_b = V_{1m} \sin\left(\omega t - \frac{2\pi}{3}\right) + V_{5m} \sin\left(5\omega t + \frac{2\pi}{3}\right) + V_{7m} \sin\left(7\omega t - \frac{2\pi}{3}\right)$$

**T7 : Solution**

(b)

- The circuit shown in the figure is a single phase bridge auto sequential commutated inverter (1-phase ASCI).
- Thyristor pairs  $T_1, T_2$  and  $T_3, T_4$  are alternatively switches to obtain a nearly square wave load current. Two commutating capacitors, one  $C_1$  in the upper half and the other  $C_2$  in the lower half are connected as shown.
- Diodes  $D_1$  to  $D_4$  are connected in series with each SCR to prevent the commutation capacitors from discharging into the load.

The inverter output frequency is controlled by adjusting the period  $T$  through the triggering circuits of thyristors.

The theoretical maximum output frequency obtainable

$$f_{\max} = \frac{1}{4RC} = \frac{1}{4 \times 10 \times 0.1 \times 10^{-6}} = 250 \text{ kHz}$$

**T8 : Solution**

(a)

Device used in current source inverter (CSI) must have reverse voltage blocking capacity. Therefore, devices such as GTOs, power transistors and power MOSFETs cannot be used in a CSI. So, a diode is added in series with the devices for reverse blocking.

**T9 : Solution**

(c)

$$\begin{aligned} V_S &= 600 \text{ V} \\ M_A &= 1 \\ \hat{V}_{L1} &= \sqrt{3} M_A \cdot \frac{V_S}{2} \\ V_{L1, \text{rms}} &= \left( \frac{\sqrt{3}}{2\sqrt{2}} \right) M_A V_S \\ &= \frac{\sqrt{3}}{2\sqrt{2}} \times 600 = 367.4 \text{ V} \end{aligned}$$

**T10 : Solution**

The output voltage  $V_0$  can be represented by Fourier series as under:

$$V_0 = \sum_{n=1,3,5,\dots}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

where,

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega t \, d(\omega t)$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega t \, d(\omega t)$$

$$a_n = \frac{1}{\pi} \left[ \int_0^{\alpha} 100 \cos \omega t d(\omega t) + \int_{\alpha}^{180^{\circ}-\alpha} (-100) \cos \omega t d(\omega t) \right. \\ \left. + \int_{180^{\circ}-\alpha}^{180^{\circ}} 100 \cos \omega t d(\omega t) + \int_{180^{\circ}}^{180^{\circ}+\alpha} -100 \cos \omega t d(\omega t) \right. \\ \left. + \int_{180^{\circ}+\alpha}^{360^{\circ}-\alpha} 100 \cos \omega t d(\omega t) + \int_{360^{\circ}-\alpha}^{360^{\circ}} -100 \cos \omega t d(\omega t) \right]$$

$$a_n = \frac{100}{\pi} [\sin \alpha - \sin(180^{\circ} - \alpha) + \sin \alpha + \sin(180^{\circ}) - \sin(180^{\circ} - \alpha) \\ - \sin(180^{\circ} + \alpha) + \sin 180^{\circ} + \sin(360^{\circ} - \alpha) - \sin(180^{\circ} + \alpha) \\ - \sin 360^{\circ} + \sin(360^{\circ} - \alpha)]$$

$$a_n = 0$$

$$b_n = \frac{1}{\pi} \left[ \int_0^{\alpha} 100 \sin \omega t d(\omega t) + \int_{\alpha}^{180^{\circ}-\alpha} -100 \sin \omega t d(\omega t) \right. \\ \left. + \int_{180^{\circ}-\alpha}^{180^{\circ}} 100 \sin \omega t d(\omega t) + \int_{180^{\circ}}^{180^{\circ}+\alpha} -100 \sin \omega t d(\omega t) \right. \\ \left. + \int_{180^{\circ}+\alpha}^{360^{\circ}-\alpha} 100 \sin \omega t d(\omega t) + \int_{360^{\circ}-\alpha}^{360^{\circ}} -100 \sin \omega t d(\omega t) \right]$$

$$b_n = \frac{100}{\pi} [-\cos \alpha + 1 + \cos(180^{\circ} - \alpha) - \cos \alpha - \cos 180^{\circ} + \cos(180^{\circ} - \alpha) \\ + \cos(180^{\circ} + \alpha) - \cos 180^{\circ} - \cos(360^{\circ} - \alpha) + \cos(180^{\circ} + \alpha) \\ + \cos 360^{\circ} - \cos(360^{\circ} - \alpha)]$$


$$b_n = \frac{100}{\pi} [4 - 8 \cos \alpha] = 50\sqrt{2}$$

$$\cos \alpha = 0.22231 = 77.15^{\circ}$$

**T11 : Solution**

$$V_{o1} = 230 \text{ V}$$

$$\hat{V}_{o1} = 230\sqrt{2}$$

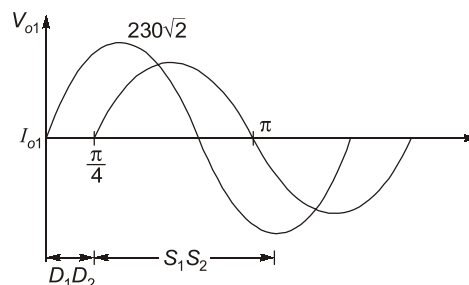

$$\hat{I}_{o1} = \frac{V_{o1}}{|Z_1|} = \frac{230\sqrt{2}}{\sqrt{R^2 + (X_L - X_C)^2}}$$



$$= \frac{230\sqrt{2}}{\sqrt{2^2 + (8-6)^2}} = 115 \text{ A}$$

$$\phi_1 = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{8-6}{2}\right) = 45^\circ = \frac{\pi}{4}$$

$$i_{o1} = 115 \sin\left(\omega t - \frac{\pi}{4}\right)$$

$$I_{s1,rms} = \left\{ \frac{1}{2\pi} \int_{\pi/4}^{\pi} 115^2 \sin^2\left(\omega t - \frac{\pi}{4}\right) d\omega t \right\}^{\frac{1}{2}}$$

$$I_{s1,rms} = \left\{ \frac{1}{2\pi} \int_0^{3\pi/4} 115^2 \sin^2 \omega t d(\omega t) \right\}^{\frac{1}{2}} = 54.826 \text{ A}$$

**T12 : Solution**

Applying fourier series

$$a_n = 0$$

$$b_n = \frac{4V_s}{n\pi} [1 - \cos n\alpha_1 + \cos n\alpha_2]$$

To eliminate 3<sup>rd</sup> and 5<sup>th</sup> harmonic

$$b_3 = 1 - \cos 3\alpha_1 + \cos 3\alpha_2 = 0$$

$$b_5 = 1 - \cos 5\alpha_1 + \cos 5\alpha_2 = 0$$

$$\alpha_1 = 17.83^\circ$$

$$\alpha_2 = 37.96^\circ$$

**T13 : Solution**


(a) Rms output voltage,

$$V_{or} = V_s \left[ \frac{2d}{\pi} \right]^{1/2}$$

$$= 141.42 \text{ V}$$

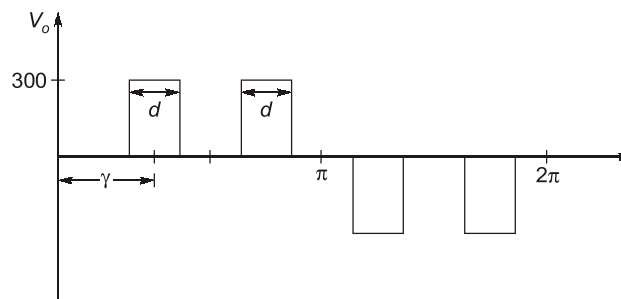(b) Fourier series of output voltage waveform

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{8V_s}{n\pi} \sin n\gamma \sin \frac{nd}{2} \sin n\omega t$$



Peak value of 3<sup>rd</sup> harmonic,

$$\hat{V}_{o3} = \frac{8V_s}{3\pi} \sin(3 \times 45^\circ) \sin \frac{3 \times 20}{2}$$

$$\hat{V}_{o3} = 90.03 \text{ V}$$

(c) Rms value of fundamental voltage,

$$(V_{o1})_{\text{rms}} = \frac{\frac{8V_s}{\pi} \sin \gamma \sin \frac{d}{2}}{\sqrt{2}}$$

$$(V_{o1})_{\text{rms}} = 66.328 \text{ V}$$

(d) 5<sup>th</sup> harmonic voltage,

$$\begin{aligned} V_{o5} &= \frac{8V_s}{5\pi} \sin(5 \times 45^\circ) \sin \frac{5 \times 20}{2} \\ &= -82.76 \end{aligned}$$

■ ■ ■ ■

# 5

## Resonant Converters and Power Electronics Applications (Drives & SMPS)



### Detailed Explanation of Try Yourself Questions

#### T1 : Solution

At  $t = 0$ , steady state exists and therefore, generated torque = load torque

$$T_e = T_L$$

In general, the dynamic equation for the motor load combination is  
generated torque = inertia torque + friction torque + load torque

$$T_e = J \frac{d\omega_m}{dt} + D\omega_m + T_L$$

As friction torque is zero,

$$D\omega_m = 0$$

The differential equation, governing the speed of the drive at  $t > 0$ ,

$$T_e = J \frac{d\omega_m}{dt} + T_L$$

$$100 = 0.01 \frac{d\omega_m}{dt} + 40 \quad \dots(i)$$

$$\frac{d\omega_m}{dt} = 6000$$

$$dt = \frac{d\omega_m}{6000}$$

Its integration gives,  $t = \frac{\omega_m}{6000} + A \quad \dots(ii)$

Initial speed at  $t = 0^+$  remains 500 rpm. Therefore,

$$\omega_{m0} = \frac{2\pi \times 500}{60} = \frac{100\pi}{6} \text{ rad/sec}$$

Substituting this value in equation (ii),

$$0 = \frac{1}{6000} \times \frac{100\pi}{6} + A \quad \text{or} \quad A = \frac{-\pi}{360}$$

$$t = \frac{\omega_m}{6000} - \frac{\pi}{360}$$

Final speed, 
$$\omega_m = \frac{2\pi \times 1000}{60} = \frac{200\pi}{6} \text{ rad/sec}$$

$$t = \frac{200\pi}{6000 \times 6} - \frac{\pi}{360} = \frac{\pi}{360} \text{ sec} = 0.0873 \text{ sec}$$

$\therefore$  Time taken for the speed to reach 1000 rpm = 0.0873 sec  $\simeq$  87.3 msec

**T2 : Solution**

(a)

**T3 : Solution**

(c)

**T4 : Solution**

(a)

$$V_s = 400 \text{ V}$$

$$R_a = 0.2 \ \Omega$$

$$K_m = 1.2 \text{ V-s/rad}$$

$$I_o = 300 \text{ A (constant)}$$

$$N_{\min} = ?, N_{\max} = ?$$

$$E_b = V_o + I_o R_a$$

$$[V_o = (1 - \alpha)V_s]$$

$$k_m \frac{2\pi}{60} N = V_o + I_o R_a$$

$$\left[ E_b = k_m \omega = k_m \frac{2\pi}{60} N \right]$$

$$k_m \frac{2\pi}{60} N_{\min} = (V_o)_{\min} + I_o R_a$$

$$k_m \frac{2\pi}{60} N_{\min} = 0 + I_o R_a$$

$$\frac{1.2 \times 2\pi}{60} N_{\min} = 300 \times 0.2$$

$$N_{\min} = 477 \text{ rpm}$$

Similarly,

$$k_m \frac{2\pi}{60} N_{\max} = V_o + I_o R_a$$

$$k_m \frac{2\pi}{60} N_{\max} = V_s + I_o R_a$$

$$1.2 \times \frac{2\pi}{60} N_{\max} = 400 + 300 \times 0.2$$

$$N_{\max} = 3660 \text{ rpm}$$

**T5 : Solution**

$$N_{S1} = 3000 \text{ rpm} \quad (\text{synchronous speed at 50 Hz})$$

$$N_1 = 2850 \text{ rpm} \quad (\text{motor speed at 50 Hz})$$

$$S_{FL} = \frac{3000 - 2850}{3000} = 0.05 \quad (\text{rated slip at 50 Hz})$$

where, by ( $V/f$ ) control,


$$N_{S2} = 3000 \left( \frac{40}{50} \right) = 2400 \text{ rpm} \quad (\text{synchronous speed at 40 Hz})$$

$\therefore$   $N_2 =$  New running speed of motor

$$N_{s2} \left( 1 - \frac{S_{FL}}{2} \right) = 2400 \left( 1 - \frac{0.05}{2} \right) = 2340 \text{ rpm}$$

**T6 : Solution**

(a)

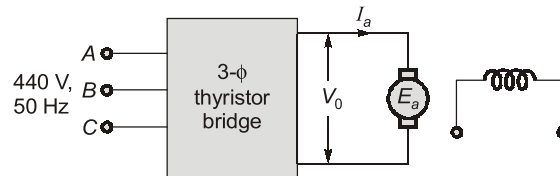

For a separately excited DC motor

$$\text{Back emf} = E_a = V_0 - I_a R_a$$

Since, losses are neglected  $R_a$  can be neglected

So,

$$E_a \approx V_0$$

$$V_0 = E_a = k_a \phi N$$

$$V_0 \propto N$$

...(i)

At rated voltage  $V_0 = 440 \text{ V}$  and  $N = 1500 \text{ rpm}$  so, at half the rated speed.  $\left( \frac{N}{2} = 750 \text{ rpm} \right)$  output voltage of the bridge ( $V_0$ ) is 220 V.

If  $I_a$  is the average value of armature current rms value of supply current will be

$$I_s = I_a \sqrt{\frac{2}{3}}$$

Power delivered to the motor

$$P_0 = V_0 I_a$$

Input VA to the thyristor bridge


$$S_{in} = \sqrt{3} V_s I_s$$

Input power factor

$$= \frac{P_0}{S_{in}} = \frac{V_0 I_a}{\sqrt{3} V_s I_s} = \frac{220 \times I_a}{\sqrt{3} \times 440 \times I_a \sqrt{\frac{2}{3}}} = 0.354$$

**T7 : Solution**

(4.98)

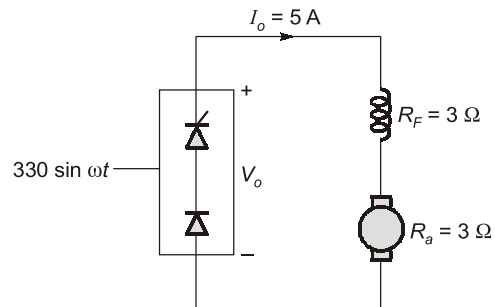

$$\alpha = 45^\circ$$

$$N = 1450 \text{ rpm}$$

$$T_a \propto \phi I_a$$

$$T_a = K_m I_o$$

(If flux is constant)

$$E_b = K_m \omega = K_m \frac{2\pi}{60} N$$

$$V_o = E_b + I_a (R_a + R_F)$$

$$\frac{V_m}{\pi} (1 + \cos \alpha) = K_m \frac{2\pi}{60} N + 5(3 + 3)$$

$$\frac{330}{\pi} (1 + \cos 45^\circ) = K_m \frac{2\pi}{60} \times 1456 + 5 \times (3 + 3)$$

$$K_m = 0.98 \text{ V-s/rad}$$

$$T = 0.98 \times 5 = 4.9 \text{ Nm}$$

**T8 : Solution**

At rated torque,

$$I_o = 100 \text{ A}$$

$$V_o = E_b + I_o R_a$$

$$V_o = K_m \frac{2\pi}{60} \cdot N + I_o R_a$$

$$220 = K_m \frac{2\pi}{60} \times 2100 + 100 \times 0.1$$

$$K_m = 0.955$$




$$V_o = E_b + I_o R_a$$

$$\alpha V_s = k_m \cdot \frac{2\pi}{60} N + I_o R_a$$

$$0.4 \times 250 = 0.955 \times \frac{2\pi}{60} N + 100 \times 0.1$$

$$N = 900 \text{ rpm}$$

**T9 : Solution**

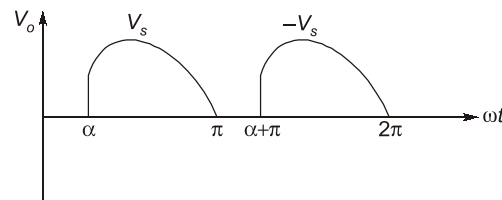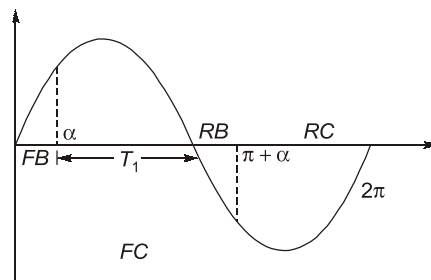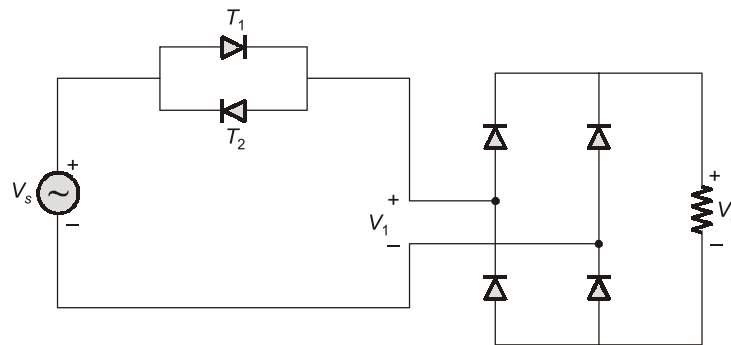

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left\{ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right\}^{\frac{1}{2}}$$

$$V_{or} = \frac{V_m}{2}$$

∴

$$I_{or} = \frac{V_{or}}{R} = \frac{V_m}{2R} = \frac{200\sqrt{2}}{2 \times \frac{10}{\sqrt{2}}} = 20 \text{ A}$$

