



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

DIGITAL ELECTRONICS

EC-EE

Date of Test : 28/08/2025

ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (c) | 7. (c) | 13. (b) | 19. (a) | 25. (d) |
| 2. (d) | 8. (a) | 14. (c) | 20. (d) | 26. (c) |
| 3. (d) | 9. (d) | 15. (c) | 21. (b) | 27. (c) |
| 4. (b) | 10. (b) | 16. (c) | 22. (a) | 28. (d) |
| 5. (c) | 11. (d) | 17. (a) | 23. (d) | 29. (d) |
| 6. (d) | 12. (a) | 18. (b) | 24. (b) | 30. (b) |

DETAILED EXPLANATIONS

1. (c)

$$\begin{aligned}
 (EOB)_H - (ABF)_H &= (34C)_H \\
 (34C)_H &= (001101001100)_2 = (1514)_8 \\
 7\text{'s compliment} &= (6263)_8 \\
 8\text{'s compliment} &= (6263)_8 + 1 \\
 &= (6264)_8
 \end{aligned}$$

2. (d)


3. (d)

$$Y = \overline{C}\overline{D} + (\overline{A} \cdot \overline{B})(\overline{D}C) + \overline{C}DS = Y = \overline{C}\overline{D} + (\overline{D} + \overline{C})(\overline{A} + \overline{B}) + \overline{C} + \overline{D} + \overline{S}$$

4. (b)

Redrawing the circuit

A	B	C	D	f
X	X	X	0	0
0	0	0	1	1
0	0	1	1	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	0
1	1	1	1	1

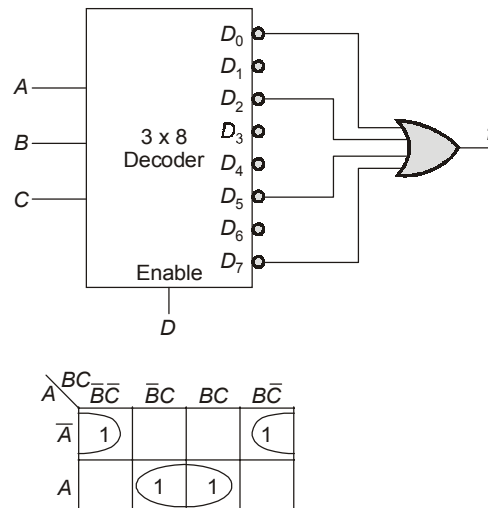

$$f = D(\overline{A}\overline{C} + AC)$$

5. (c)

ECL is fastest logic family. So, ECL RAM's are used as cache memory.

In ROM, data can be read from random locations.

6. (d)

Inhibitor - If one of the input of AND gate or OR gate is complemented, the gate is called inhibitor.

So output of inhibitor are

$$\begin{aligned}
 A\overline{B}, \quad \overline{A} + B \\
 \overline{\overline{A}B}, \quad A + \overline{B}
 \end{aligned}$$

7. (c)

For a 12 bit BCD number

Range is 000 to 999

$$\text{Step size} = \frac{10.24}{999} = 10.25 \text{ mV}$$

8. (a)

Conversion time for an n-bit successive approximation type ADC = nT_{clk} (independent of the input voltage)

Given

$$n = 8$$

Therefore,

$$\begin{aligned} T_{\text{conversion}} &= 8 T_{\text{clk}} \\ &= \frac{8}{f_{\text{clk}}} \\ &= \frac{8}{10 \times 10^6} \\ &= 800 \text{ nsec} \end{aligned}$$

9. (d)

$$Y = \overline{A}\overline{B}\overline{C} \cdot (\overline{A}BC + \overline{A}BD + B\overline{C})$$

$$Y = (\overline{A} + B + \overline{C})(\overline{A}BC + \overline{A}BD + B\overline{C})$$

$$Y = \overline{A}BC + \overline{A}BD + \overline{A}B\overline{C} + B\overline{C} + \overline{A}B\overline{C}D$$

$$Y = \overline{A}BC + \overline{A}BD + B\overline{C}$$

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$				
$\overline{A}B$	1	1	1	1
AB	1	1		
$A\overline{B}$				

$$Y = B\overline{C} + \overline{A}B = B[\overline{A} + \overline{C}]$$

10. (b)

From the combinational logic,

Assuming D is input, Q_n is present state and Q_{n+1} is the next state, then

$$R = \overline{D \oplus Q_n} \quad \text{and} \quad S = D \oplus Q_n$$

Characteristic equation of R-S flip flop.

$$Q_{n+1} = S + \overline{R}Q_n$$

So,

$$\begin{aligned} Q_{n+1} &= (D \oplus Q_n) + (\overline{D \oplus Q_n})Q_n \\ &= (D \oplus Q_n) + (D \oplus Q_n)Q_n \\ &= (D \oplus Q_n)(1 + Q_n) \\ &= D \oplus Q_n \\ &= D\overline{Q_n} + \overline{D}Q_n \end{aligned}$$

For $D = 0$,

$$Q_{n+1} = Q_n$$

For $D = 1$,


$$Q_{n+1} = \overline{Q_n}$$

So, the circuit represent a T flip-flop.


11. (d)

AB	$\overline{A}\overline{B}$	$\overline{A}B$	AB	$A\overline{B}$
$\overline{C}\overline{D}$	1	1	1	1
$\overline{C}D$			1	
CD	1		1	1
$C\overline{D}$	1	1	1	1
 
$$F = \overline{D} + \overline{B}C + AB$$



12. (a)

 

$$\text{Total conversion time, } (t) = 2^N T_C + \frac{V_a}{V_R} \cdot 2^N T_C$$

where, N = Number of bits of converter

T_C = Time period of the clock

V_a = analog voltage

V_R = Reference voltage

The largest V_a can be equal to V_R , therefore,

$$\begin{aligned} V_a &= V_R \\ t &= 2^{N+1} T_C \end{aligned}$$

$$\frac{1}{f_{\max}} = 2^{13+1} \cdot \frac{1}{f_c}$$

$\therefore$

$$\begin{aligned} f_c &= 2^{14} \times f_{\max} = 16384 \times 2 \\ f_c &= 32768 \text{ Hz} \end{aligned}$$

13. (b)

$$(5330)_y = 5y^3 + 3y^2 + 3y + 0$$

$$= 5y^3 + 3y^2 + 3y$$

$$(1425)_x = x^3 + 4x^2 + 2x + 5$$

and,

$$(50)_y = 5y$$

$$(15)_x = x + 5$$

Hence,

$$5y^3 + 3y^2 + 3y + x^3 + 4x^2 + 2x + 5 = (5y + x + 5)^2$$

Putting the values of x and y from the options

$$\left. \begin{matrix} x = 7 \\ y = 6 \end{matrix} \right\} \text{ satisfies the given equation.}$$

$$\therefore (x, y) = (7, 6)$$

14. (c)

This is an asynchronous counter, $\overline{Q_3Q_2}$ is connected to $\overline{CLR}$ input which means when Q_3Q_2 both are '1' then circuit will be reset to 000 state.

Clock	Q_3	Q_2	Q_1
Initial	0	0	0
1 st	0	0	1
2 nd	0	1	0
3 rd	0	1	1
4 th	1	0	0
5 th	1	0	1
6 th	1	1	0

$\Rightarrow$ Counter will be reset

15. (c)


$$f_1 = \Sigma m(0, 1, 4, 5)$$

$$f_2 = \Sigma m(2, 3, 6, 7)$$

As f_1 and f_2 are independent outputs

$$\text{So, } y = f_1 \cdot f_2 = 0$$

16. (c)

 

$$G_1 = \text{NOT} = \overline{A}$$

$$G_2 = \text{NOR} = \overline{C + D} = \overline{C} \cdot \overline{D}$$

17. (a)

From the state transition diagram we can write,

A	Q	Q ⁺
0	0	1
0	1	1
1	0	1
1	1	0

$$Q^+ = \bar{A}\bar{Q} + \bar{A}Q + A\bar{Q}$$

$$= \bar{A} + A\bar{Q}$$

$$Q^+ = \bar{A} + \bar{Q} = \overline{A \cdot Q}$$

$$Q^+ = D$$

For D flip flop,

So from option (a), we have

$$Q^+ = D = \overline{Q \cdot A}$$

18. (b)

State table

X	Y	Q	Q ⁺
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Excitation table
for XY

Q	Q ⁺	X	Y
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1

Conversion of XY-flip-flop to D flip-flop.

D	Q	Q ⁺	X	Y
0	0	0	0	X
0	1	0	X	0
1	0	1	1	X
1	1	1	X	1

D	Q	
	$\bar{Q}$	Q
$\bar{D}$	0	X
D	1	X

$X = D$

D	Y	
	$\bar{Y}$	Y
$\bar{D}$	X	0
D	X	1

$Y = D$

19. (a)

$$I_{OL(max)} = 32 \text{ mA}$$

$$I_{IL(max)} = 1.6 \text{ mA}$$

$$I_{OH(max)} = 400 \text{ } \mu\text{A}$$

$$I_{IH(max)} = 10 \text{ } \mu\text{A}$$

$$\text{fanout (HIGH)} = \frac{I_{OH}}{I_{IH}} = \frac{400}{10} = 40$$

$$\text{fanout LOW} = \frac{I_{OL}}{I_{IL}} = \frac{32}{1.6} = 20$$

$$\therefore \text{The overall fanout} = \text{Min} (40, 20) = 20$$

Therefore, statements (a) is correct.

20. (d)

Since 16 ICs are used to form 32 kB RAM, each IC would provide

$$\frac{32k \times 8}{16} = 16 \text{ Kbits}$$

14 Address bits



2^{14} cells/memory locations




16 K cells



16 K bits



Since 16 K cells provide a capacity of 16 Kbits, so cell size must be 1 bit.

21. (b)

 


	A	B	C	Y
$t < 10 \text{ ns}$	1	1	0	0
$10 \text{ ns} < t < 20 \text{ ns}$	1	0	0	1
$20 \text{ ns} < t < 30 \text{ ns}$	1	0	1	1
$30 \text{ ns} < t < 40 \text{ ns}$	1	0	0	0
$40 \text{ ns} < t$	1	0	0	1

Alternate:

  

$\Rightarrow$ option (b) is correct.

22. (a)

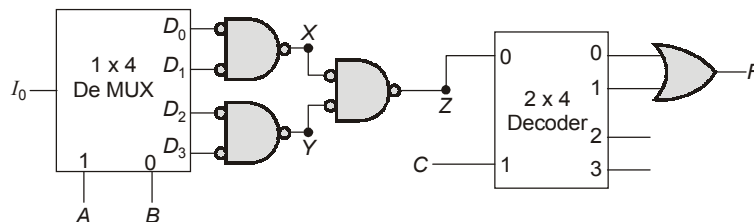

$$X = \overline{D_0} \overline{D_1} I_0 = (D_0 + D_1) I_0$$

$$= (\overline{A} \overline{B} + \overline{A} B) I_0 = \overline{A} I_0$$




$$Y = \overline{D_2} \overline{D_3} I_0 = (D_2 + D_3) I_0$$

$$= (A \overline{B} + A B) I_0 = A I_0$$

$$\begin{aligned} Z &= (\overline{X \cdot Y}) = X + Y \\ &= \bar{A} \cdot I_0 + A I_0 = I_0 \\ F &= (\bar{Z} \bar{C} + Z \bar{C}) = \bar{C}(\bar{I}_0 + I_0) \\ &= \bar{C} \end{aligned}$$

23. (d)
State Table

A	B	Q_{n+1}	J	K
0	0	$\bar{Q}_n$	1	1
0	1	1	1	0
1	0	Q_n	0	0
1	1	0	0	1

   


24. (b)

$$\begin{aligned} \text{Full scale reading} &= \text{Resolution} \times (2^n - 1) = 2 \times 10^{-3} \times (2^8 - 1) \\ &= 510 \text{ mA} \end{aligned}$$

$$\text{Error} = \pm \frac{0.5}{100} \times 0.51 = 2.55 \text{ mA}$$

$$\begin{aligned} \text{Analog output} &= \text{Decimal equivalent} \times \text{Resolution} \\ &= 170 \times 2 \pm 2.55 \text{ mA} \\ &= (340 \pm 2.55) \text{ mA} \end{aligned}$$

25. (d)
Drawing switch equivalent

 

From this Y is

$$Y = [ADF + ABC + (E + G)DBC + (E + G)F]'$$


$$Y = [ADF + ABC + (E + G)(DBC + F)]'$$

26. (c)
Output of counter

D_3	D_2	D_1	D_0	I_1	I_0	Y_2
0	0	0	0	0	1	0
0	0	0	1	1	1	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	0	0	0
1	0	0	0	0	0	0
1	0	0	1	1	0	1

$$\text{Duty cycle} = \frac{3}{10} \times 100 = 30\%$$

27. (c)

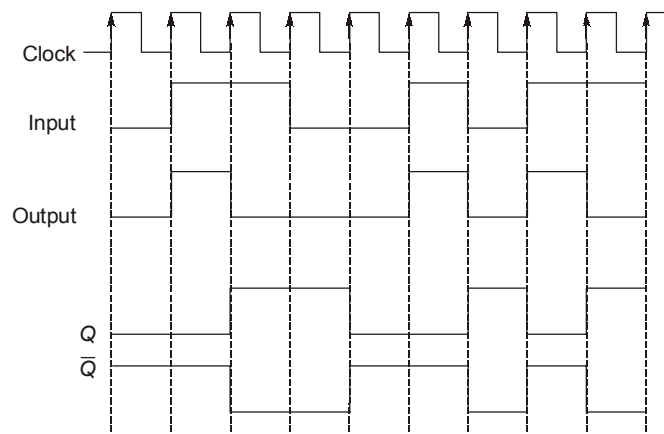

By checking all the options. Option (c) correctly matches.

28. (d)
NMOS requires less silicon area for fabrication.

29. (d)
An ADC must perform at a rate equal to at least twice the frequency of the highest component of the input. (according to Nyquist criterion)
If f_m is the highest frequency component in the message signal, then

$$T_{\text{conv}} = 100 \mu\text{sec/sample} \leq \frac{1}{2f_m \text{ (samples/sec)}}$$

i.e.,

$$f_m \leq \frac{1}{2 \times 100 \times 10^{-6}}$$

$$f_m \leq 5 \text{ kHz}$$

30. (b)
In ripple counter, $S = 4t_{pd} = 4 \times 20 = 80 \text{ nsec}$
In synchronous counter, $R = t_{pd} = 20 \text{ nsec}$ [$\because$ all the flip-flops are clocked simultaneously in synchronous counter]

■■■■