



MADE EASY

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ANALOG ELECTRONICS

ELECTRICAL ENGINEERING

Date of Test : 14/09/2025


ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (c) | 13. (b) | 19. (c) | 25. (b) |
| 2. (b) | 8. (d) | 14. (a) | 20. (a) | 26. (b) |
| 3. (c) | 9. (d) | 15. (c) | 21. (a) | 27. (c) |
| 4. (a) | 10. (c) | 16. (b) | 22. (a) | 28. (b) |
| 5. (a) | 11. (a) | 17. (c) | 23. (b) | 29. (d) |
| 6. (b) | 12. (a) | 18. (d) | 24. (c) | 30. (a) |

DETAILED EXPLANATIONS

1. (b)

The circuit can be redrawn as

 

Case (I): when $V_{in}(t) > 4\text{ V}$


The diode D will be in OFF state and $V_{in}(t) = V_0(t)$.

Case (II): when $V_{in}(t) < 4\text{ V}$

The diode D will be in ON state and $V_{out}(t) = 4\text{ V}$.

 2. (b)

By drawing the small signal equivalent model of the transistor by deactivating all the supply voltages, we get,



Now, the resistance seen by the source is equal to,

$$R_{in} = R_s + (R_1 \parallel R_2 \parallel r_{\pi})$$

$$r_{\pi} = 2.74\text{ k}\Omega \quad (\text{given})$$

Thus,


$$\begin{aligned} R_{in} &= 0.5 \times 10^3 + (2.74\text{ k} \parallel 93.7\text{ k} \parallel 6.3\text{ k}) \\ &= (0.5 + 1.87) \times 10^3 \Omega = 2.37\text{ k}\Omega \end{aligned}$$

3. (c)


The three figures are equivalent except in the first figure the resistance R_1 should have been a parallel combination of R_1 and R_2 and in the second figure the direction of dependent current source is not correct for the V_{π} polarity.

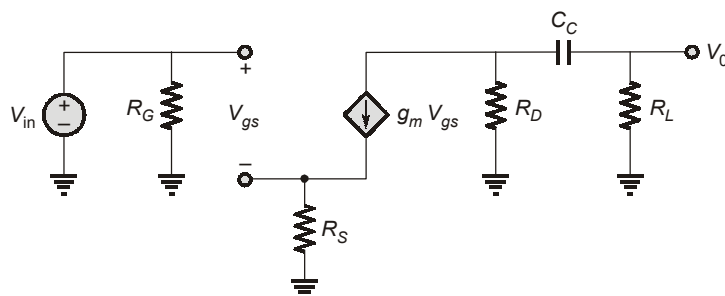4. (a)

The small signal equivalent of the circuit can be drawn as,



 Now, the time constant for capacitor C_C can be calculated by short circuiting the input voltage source thus the resultant circuit becomes



$$\therefore \tau_s = R_{eq} C_C = (R_D + R_L) C_C$$


$$\therefore f_L = \frac{1}{2\pi(R_D + R_L)C_C}$$

$$\Rightarrow C_C = \frac{1}{2\pi(R_D + R_L)f_L} = \frac{1}{2\pi(6.7 + 10) \times 10^3 \times 20}$$

$$C_C = 0.477 \mu\text{F}$$

 5. (a)

The basic mode of a phase lock loop can be represented as



6. (b)

The current through base resistor,

$$I_B = I_1 - 1 \text{ mA}$$

$$= \frac{6}{3\text{k}} - 1 \text{ mA} = 1 \text{ mA}$$

Apply KVL in base circuit,


$$-6 + 0.7 + 265(1 + \beta)I_B = 0$$

$$265(1 + \beta)I_B = 5.3$$


$$(1 + \beta) = \frac{5.3}{265 \times 10^{-3}}$$

$$1 + \beta = \frac{5.3}{0.265}$$

$$\beta = 20 - 1 = 19$$

 

7. (c)

 

$$\frac{V_1(s)}{V_i(s)} = -\frac{R_2 + \frac{1}{sC_2}}{R_1}$$

$$\frac{V_o(s)}{V_1(s)} = -\frac{R}{R} = -1$$

So,

$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{R_2}{R_1} + \frac{1}{sR_1C_2} = \frac{R_2}{R_1} \left(1 + \frac{1}{s\tau} \right); \tau = R_2 C_2 \\ &= K \left(1 + \frac{1}{s\tau} \right) \end{aligned}$$

It works as proportional + Integral controller.

8. (d)

$$I_{D1} = I_{D2} = K_n (V_{GS} - V_t)^2$$

$$\begin{aligned} I_D &= \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} (V_{GS} - V_t)^2 \\ &= 0.1 (5 - 2)^2 = 0.9 \text{ mA} \end{aligned}$$

9. (d)


In the given circuit, the feedback resistor R_F is not directly connected to the output node and directly connected to the input node. Hence, the feedback topology present in the circuit is Current-Shunt.

Current-Shunt topology is also known as Shunt-Series topology.

10. (c)

$$\begin{aligned} \text{Voltage gain, } \frac{V_o}{V_{in}} &\approx \frac{-h_{fe} \cdot R_C}{h_{ie}} \\ A_V &\approx \frac{-150 \times 3 \text{ k}\Omega}{3 \text{ k}\Omega} \approx -150 \end{aligned}$$

11. (a)

 

Apply KCL at node 'a'

$$\frac{5 - V_1}{1} = \frac{V_1 - V_o}{1}$$

$$\begin{aligned} 5 - V_1 &= V_1 - V_0 \\ -V_0 &= 5 - 2V_1 \\ V_0 &= 2V_1 - 5 \end{aligned} \quad \dots(i)$$

Apply KCL at node 'b'

$$\frac{V_1}{2} + \frac{V_1}{3} + \frac{V_1 - V_0}{2} = 0$$

$$V_1 \left[\frac{1}{2} + \frac{1}{3} + \frac{1}{2} \right] = \frac{V_0}{2}$$

$$V_1 \left[\frac{4}{3} \right] = \frac{V_0}{2}$$

$$V_1 = \frac{3}{8} V_0 \quad \dots(ii)$$

From equation (i) and (ii), we get

$$V_1 = \frac{3}{8} (2V_1 - 5)$$

$$8V_1 = 6V_1 - 15$$

$$2V_1 = -15$$

$$V_1 = -7.5 \text{ Volt}$$

Load current, $i_L = \frac{V_1}{3K} = \frac{-7.5}{3K} = -2.5 \text{ mA}$

12. (a)

For upper MOSFET,

$$V_{DS} = 8 - V_a$$

$$V_{GS} - V_T = 6 - V_a - 2 = 4 - V_a$$

Upper MOS will be in saturation because

$$V_{DS} > V_{GS} - V_T$$

For lower MOS,

$$V_{DS} = V_a$$

$$V_{GS} - V_T = V_a - 2$$

So,

$$V_{DS} > V_{GS} - V_T$$

Hence both MOS will be in saturation

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$

$$I_{D1} = \mu_n C_{ox} (9) (4 - V_a)^2$$

$$I_{D2} = \mu_n C_{ox} (4) (V_a - 2)^2$$

But

$$I_{D1} = I_{D2}$$

$$\therefore \mu_n C_{ox} (9) (4 - V_a)^2 = \mu_n C_{ox} (4) (V_a - 2)^2$$

$$\frac{9}{4} = \left(\frac{V_a - 2}{4 - V_a} \right)^2$$

$$\frac{3}{2} = \frac{V_a - 2}{4 - V_a}$$


$$12 - 3V_a = 2V_a - 4$$

$$16 = 5V_a$$

$$V_a = \frac{16}{5} = 3.2 \text{ Volts}$$

13. (b)


At upper Threshold point,

 

$$\therefore \frac{R_2 V_{TH} + 6.7(1)}{R_2 + 1} = 0$$

$$V_{TH} = \frac{-6.7}{R_2}$$

At lower Threshold point,

 

$$\frac{R_2 V_{TL} - 6.7(1)}{R_2 + 1} = 0$$


$$V_{TL} = \frac{6.7}{R_2}$$

Given that, $|V_{TH} - V_{TL}| = 2$

$$\frac{13.4}{R_2} = 2$$

$$R_2 = 6.7 \text{ k}\Omega$$

14. (a)

 

$$V_1 = 0$$

Apply KCL at node-1

$$\frac{V_{in} - 0}{10} = \frac{0 - V_2}{R}$$

$$-\left[\frac{V_{in}}{10} \times R\right] = V_2 \quad \dots(i)$$

Apply KCL at node-2

$$\frac{V_2}{R} + \frac{V_2}{10} + \frac{V_2 - V_0}{5} = 0$$

$$V_2 \left[\frac{1}{R} + \frac{1}{10} + \frac{1}{5} \right] = \frac{V_0}{5} \quad \dots(ii)$$

From equation (i) and (ii), we get

$$\frac{-V_{in} \cdot R}{10} \left[\frac{1}{R} + \frac{3}{10} \right] = \frac{V_0}{5}$$

$$\frac{R}{10} \left[\frac{10 + 3R}{10R} \right] = \frac{-V_0}{V_{in}} \times \frac{1}{5}$$

$$\frac{10 + 3R}{20} = \left(\frac{-V_0}{V_{in}} \right)$$

Given that, $\frac{V_0}{V_{in}} = -6$

$$\frac{10 + 3R}{20} = 6$$

$$10 + 3R = 120$$


$$R = \frac{110}{3} \text{ k}\Omega$$

$$R = 36.66 \text{ k}\Omega$$

 15. (c)

$$\text{Line regulation} = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100\%$$

By replacing the zener diode with its equivalent circuit, we get,



$$I = \frac{V_{in} - V_{zo}}{4410 \Omega}$$

$$V_z = V_{zo} + IR_z = V_{zo} + \frac{10}{4410}(V_{in} - V_{zo})$$

$$= V_{zo} + \frac{1}{441}(V_{in} - V_{zo}) = \frac{440}{441}V_{zo} + \frac{1}{441}V_{in}$$

$$V_{out} = \left(1 + \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega}\right)V_z = 2V_z = \frac{880}{441}V_{zo} + \frac{2}{441}V_{in}$$

$$\Delta V_{out} = \frac{\partial V_{out}}{\partial V_{in}} \times \Delta V_{in}$$

$$\frac{\Delta V_{out}}{\Delta V_{in}} = \frac{\partial V_{out}}{\partial V_{in}} = \frac{2}{441}$$

$$\text{Line regulation} = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100 = \frac{2}{441} \times 100 \approx 0.454\%$$

16. (b)

Case I : When $V_{in} < 0 \text{ V}$

When $V_{input} < 0 \text{ V}$, then the diode D_1 will be in forward biased and diode D_2 will be OFF, hence the output is equal to 0 V , which is shown in figure-1.

 


Figure (1)

Case II : $0 < V_{in} < 20 \text{ V}$

D_1 is ON and D_2 is ON.

The equivalent circuit is shown in figure (2).

From the figure it is clear that the output

$$V_{out} = V_{in}$$

Thus it will be a straight line when plotted in the transfer curve [part (2)].

 


Figure (2)

Case III : For $V_{\text{input}} > 20 \text{ V}$


$D_1 = \text{OFF}$ and $D_2 = \text{ON}$

Thus, the output will be a constant voltage V_{out} .

$$V_{\text{out}} = \frac{20}{20+10} \times 30 \text{ V} \quad (\because \text{voltage division})$$

Thus, $V_{\text{out}} = 20 \text{ V}$

 Hence, the output response can be drawn as



17. (c)

Now,

$$I_{\text{in}} = I_{D1} + I_{D2}$$

and

$$V_{D1} = V_{D2}$$

(\because diodes are in parallel)

thus,

$$V_T \ln \left(\frac{I_{D1}}{I_{s1}} \right) = V_T \ln \left(\frac{I_{D2}}{I_{s2}} \right)$$

\Rightarrow

$$\frac{I_{D1}}{I_{s1}} = \frac{I_{D2}}{I_{s2}}$$

$$I_{D1} = \left(\frac{I_{D2}}{I_{s2}} \right) \cdot I_{s1}$$

Now,

$$I_{\text{in}} = I_{D2} + I_{D2} \left(\frac{I_{s1}}{I_{s2}} \right)$$

$$I_{\text{in}} = \left(1 + \frac{I_{s1}}{I_{s2}} \right) I_{D2}$$

\Rightarrow


$$I_{D2} = \frac{I_{\text{in}}}{1 + \frac{I_{s1}}{I_{s2}}}$$

Now, I_{s1} and I_{s2} are reverse saturation currents of the diodes and $I_s \propto A$.

Thus the above equation can be written as,

$$I_{D2} = \frac{I_{\text{in}}}{1 + \frac{I_{s1}}{I_{s2}}} = \left(\frac{I_{\text{in}}}{1 + \frac{A_1}{A_2}} \right)$$

18. (d)

 

Apply KVL in loop-1,

$$\begin{aligned} -10 + I + I &= 0 \\ 2I &= 10 \\ I &= 5 \text{ A} \end{aligned}$$

Applying KVL in the loop shown,

we get,

$$\begin{aligned} V_1 &= -5 - 5 + 10 - 5 - 5 + V_2 \\ V_1 - V_2 &= -10 \text{ V} \end{aligned}$$

 \therefore voltage across resistor,

$$R = V_R = V_1 - V_2 = -10 \text{ V}$$

19. (c)

$$\frac{I_{D1}}{I_{D2}} = \frac{\frac{\mu_n C_{ox}}{2} \left(\frac{W_1}{L} \right) (V_{GS1} - V_t)^2}{\frac{\mu_n C_{ox}}{2} \left(\frac{W_2}{L} \right) (V_{GS2} - V_t)^2}$$

$$V_{GS1} = 3 \text{ V}; \quad V_{GS2} = 2 \text{ V};$$

$$I_{D1} = I_{D2} = 120 \mu\text{A}$$

$$\therefore 1 = \frac{W_1 (3 - 1)^2}{W_2 (2 - 1)^2}$$

$$\therefore 1 = \frac{W_1 (4)}{W_2}$$

$$W_2 = 4 W_1$$

$$I_{D1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W_1}{L} \right) (V_{GS1} - V_t)^2$$


$$120 \mu = \frac{120 \mu}{2} \left(\frac{W_1}{1 \mu} \right) (3 - 1)^2$$

$$1 = \frac{W_1}{2 \mu} \times 4$$

$$W_1 = 0.5 \mu\text{m}$$

$$\therefore W_2 = 4 \times W_1 = 4 \times 0.5 \mu = 2 \mu\text{m}$$

20. (a)

 

$$12 - i \times 8 \times 10^3 - 0.7 = 0$$

Now,
$$i = \frac{12 - 0.7}{8 \times 10^3} = 1.4125 \text{ mA}$$

$$i = I_{C1} + 2I_b = (\beta + 2)I_b$$


$$I_b = \frac{i}{\beta + 2} = \frac{1.4125}{202} = 6.99 \mu\text{A} \approx 7 \mu\text{A}$$

$$I_{C2} = 200I_b = 200 \times 7 \mu = 1.4 \text{ mA}$$

$$\begin{aligned} \therefore V_2 &= 30 - I_{C2} \times 10k \\ V_2 &= 30 - 1.4 \times 10 \\ &= 16 \text{ V} \end{aligned}$$

 21. (a)

From the circuit given, after observation, we can conclude that D_2 will be ON and D_1 will be OFF.



$$\therefore V_1 = -0.9 - 0.7 - 1.8 = -3.4 \text{ V}$$

22. (a)

Apply KVL in the loop (L_1) shown in figure.

$$-4 + 0.7 + 8i - 0.7 = 0$$


$$8i = 4$$

$$i = 0.5 \text{ mA}$$

$$\therefore I_{E2} = 1 \text{ mA} - 0.5 \text{ mA} = 0.5 \text{ mA}$$

As,
$$I_{C2} \approx I_{E2}$$

 
$$\begin{aligned} \therefore V_0 &= 15 - 7.5 I_{C2} \\ &= 15 - 7.5 \times 0.5 \\ V_0 &= 11.25 \text{ volt} \end{aligned}$$



 23. (b)

The first step in the analysis consists of determining the quiescent operating point. For this purpose we assume that $V_i = 0$.

$$\therefore I_B = \frac{V_{BB} - 0.7}{100k} = \frac{3 - 0.7}{100k} = 23 \mu A$$



$$\begin{aligned} I_C &= \beta I_B = 100 \times 23 \mu = 2.3 \text{ mA} \\ \therefore V_C &= 10 - I_C \cdot R_C \\ &= 10 - 2.3 \times 3 = 3.1 \text{ V} \end{aligned}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{(2.3 / 0.99) \text{ mA}} = 10.8 \Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{2.3 \text{ mA}}{25 \text{ mV}} = 92 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{92} = 1.09 \text{ k}\Omega$$

$$\therefore V_{be} = V_i \times \frac{r_\pi}{r_\pi + R_{BB}}$$


$$V_{be} = V_i \times \frac{1.09}{101.09} = 0.011 V_i$$

$$\begin{aligned} \therefore V_0 &= -g_m V_{be} R_C \\ &= -92 \times 0.011 V_i \times 3 \\ &= -3.04 V_i \end{aligned}$$

$$\therefore A_V = \frac{V_0}{V_i} = -3.04 \approx -3$$

24. (c)

For the circuit shown above,

 

Emitter current of both transistors is,

$$I_E = 0.5 \text{ mA}$$

∴ Base current of both transistor is,

$$I_B = \frac{0.5 \text{ mA}}{\beta + 1} = \frac{0.5 \text{ mA}}{101} = 4.95 \mu\text{A}$$

Apply KVL in the loop shown in above figure,


$$\begin{aligned} \therefore V_A &= 10\text{K} \times 4.95 \mu + 0.7 + 0.7 + 10\text{K} \times 4.95 \mu + 3 \\ &= 4.499 \\ V_A &= 4.5 \text{ V} \end{aligned}$$

25. (b)

For $V_p = 1 \text{ V}$ and R_L reduced, the lowest value possible for while the output remaining an undistorted sine wave of 10 V peak can be found from

$$\begin{aligned} i_{0 \text{ max}} &= 20 \text{ mA} = \frac{10 \text{ V}}{R_{L \text{ min}}} + \frac{10 \text{ V}}{9 \text{ k}\Omega + 1 \text{ k}\Omega} \\ 19 \text{ mA} &= \frac{10 \text{ V}}{R_{L \text{ min}}} \\ R_{L \text{ min}} &= \frac{10 \text{ V}}{19 \text{ mA}} = 526 \Omega \end{aligned}$$

26. (b)

 

$$V_G = V_{DD} \times \frac{R_{G2}}{R_{G1} + R_{G2}} = \frac{10}{10 + 10} \times 10 = 5 \text{ V}$$

$$R_G = (10 \parallel 10) = 5 \text{ k}\Omega$$

$$V_{GS} = (V_G - I_D \times R_S) = (5 - 6I_D)$$

Assuming the saturation mode of operation

$$I_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$\left(\frac{5 - V_{GS}}{6} \right) = \frac{1}{2} \times 1 (V_{GS} - 1)^2$$

$$5 - V_{GS} = 3V_{GS}^2 + 3 - 6V_{GS}$$

$$3V_{GS}^2 - 5V_{GS} - 2 = 0$$

$$V_{GS} = 2, -\frac{1}{3}$$

$$V_{GS} = 2 \text{ V}$$

$$\therefore I_D = \left(\frac{5-2}{6} \right) = 0.5 \text{ mA}$$

$$V_{DS} = 10 - 0.5 \times 12 = 4 \text{ V}$$

$$\therefore V_{DS} > (V_{GS} - V_t)$$

\therefore Assumption is correct.

27. (c)

$$V_0 \text{ (offset due to } V_{I0}) = V_{I0} \frac{R_1 + R_f}{R_1} = (4 \text{ mV}) \frac{5 \text{ k}\Omega + 500 \text{ k}\Omega}{5 \text{ k}\Omega} = 404 \text{ mV}$$

$$V_0 \text{ (offset due to } I_{I0}) = I_{I0} R_f = (150 \text{ nA}) (500 \text{ k}\Omega) = 75 \text{ mV}$$

Resulting in a total offset,

$$\begin{aligned} V_0 \text{ (total offset)} &= V_0 \text{ (offset due to } V_{I0}) + V_0 \text{ (offset due to } V_{I0}) \\ &= 404 + 75 = 479 \text{ mV} \end{aligned}$$

28. (b)

We assume that both diodes are conducting, then voltage at point-B, $V_B = 0$ and $V = 0$. The current in D_1 is obtained from

$$I_{D1} = \frac{10 - 0}{5} = 2 \text{ mA}$$

The node equation at B is

$$I_{D2} + 2 = \frac{0 - (-10)}{10}$$

Which yields $I_{D2} = -1 \text{ mA}$. Since this is not possible our assumption is not correct. We start again assumption that D_2 is off and D_1 is on. The current I_{D1} is given

$$I_{D1} = \frac{10 - (-10)}{15} = 1.33 \text{ mA}$$

and the voltage at node-B is

$$V_B = -10 + 10 \times 1.33 = +3.3 \text{ V}$$

Thus D_2 is reverse biased as assumed and the final result is $V = 3.33 \text{ V}$.

29. (d)

$$g_{m0} = \frac{2I_{DSS}}{|V_p|} = \frac{2(8\text{mA})}{6} = 2.67 \text{ ms}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GSQ}}{V_p} \right) = 2.67 \text{ mS} \left(1 - \frac{(-2.6)}{(-6)} \right) = 1.51 \text{ mS}$$

$$r_d = 50 \text{ k}\Omega$$

$$Z_i = R_G = 1 \text{ M}\Omega$$

$$r_d > 10R_D$$

$$Z_0 = R_D = 3.3 \text{ k}\Omega$$

Therefore,

With $r_{d'}$

$$= \frac{-g_m R_D}{1 + g_m R_s + \frac{R_D + R_s}{r_d}}$$

$$A_V = \frac{-(1.51 \text{ mS})(3.3 \text{ k}\Omega)}{1 + (1.51 \text{ mS})(1 \text{ k}\Omega) + \frac{3.3 \text{ k}\Omega + 1 \text{ k}\Omega}{50 \text{ k}\Omega}}$$

$$= \frac{-4.983}{1 + 1.51 + 0.086} = -1.92$$

30. (a)

The amplifier gain is calculated to be

$$A = A_1 A_2 A_3$$

$$= \left(1 + \frac{R_f}{R_1} \right) \left(\frac{-R_f}{R_2} \right) \left(\frac{-R_f}{R_3} \right)$$

$$= \left(1 + \frac{470}{4.3} \right) \left(\frac{-470}{33} \right) \left(\frac{-470}{33} \right)$$

$$= (110.3) (-14.24) (-14.24) = 22.2 \times 10^3$$

So that,

$$V_0 = AV_i = 22.2 \times 10^3 \times 80 \mu\text{V}$$

$$= 1.78 \text{ V}$$

