



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Noida | Bhopal | Hyderabad | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

Electrical Engineering

CLASS TEST
2016

EE

Electrical Measurement


Date : 30/07/2016

ANSWERS

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (d) | 7. (a) | 13. (c) | 19. (c) | 25. (c) |
| 2. (a) | 8. (a) | 14. (c) | 20. (d) | 26. (b) |
| 3. (d) | 9. (b) | 15. (a) | 21. (c) | 27. (b) |
| 4. (a) | 10. (a) | 16. (c) | 22. (c) | 28. (a) |
| 5. (b) | 11. (b) | 17. (d) | 23. (c) | 29. (d) |
| 6. (c) | 12. (d) | 18. (b) | 24. (b) | 30. (d) |

Explanation

1. (d)

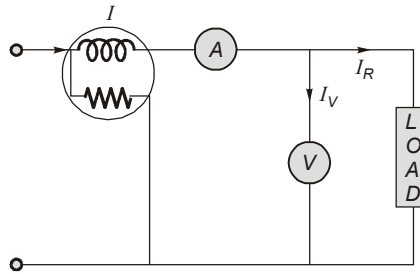

$$V = (0.2 + 0.2) \times 5 + 200 = 202 \text{ V}$$

$$I = 5 \text{ A}$$

Wattmeter reading,

$$P = VI \cos \phi = 202 \times 5 \times 1 = 1010 \text{ Watt}$$

2. (a)

The overall uncertainty

$$\omega_x = \sqrt{\omega_{x_1}^2 + \omega_{x_2}^2 + \omega_{x_3}^2} = \sqrt{1^2 + 1^2 + 3^2} = \sqrt{11} \%$$

3. (d)

Phase shift between the inputs of the CRO = 0, so pattern will be a straight line.

4. (a)

In Maxwell bridge

$$L = CR_2R_3 = 20 \times 10^{-6} \times 250 \times 400 = 2 \text{ H}$$

5. (b)

In De-sauty's bridge

$$\begin{aligned} C_1 &= C_2 \frac{R_2}{R_1} = 200 \times 10^{-6} \times \frac{2000}{1000} \\ &= 400 \mu\text{F} \end{aligned}$$

6. (c)

At balance condition,

$$\frac{1000}{R_x + j\omega L_x} = \frac{R_s}{(j\omega R_s C_s + 1) \times 1000}$$

$$\text{or, } 10^6(j\omega R_s C_s + 1) = R_s(R_x + j\omega L_x)$$

equating real and imaginary terms,

$$10^6 = R_s R_x$$

$$\Rightarrow R_x = \frac{10^6}{R_s} = 1000 \Omega$$

$$\begin{aligned} \text{and } 10^6 C_s &= L_x \\ \Rightarrow L_x &= 10^6 \times 0.5 \times 10^{-6} \\ &= 0.5 \text{ H} \end{aligned}$$

7. (a)

At balance condition,

$$Z_4 = \frac{150\angle 0^\circ \times 250\angle -40^\circ}{200\angle 30^\circ}$$

$$= 187.5\angle -70^\circ \Omega$$

8. (a)

At balance condition,

$$\frac{1000}{R_x + j\omega L_x} = \frac{R_s}{(j\omega R_s C_s + 1) \times 1000}$$

or, $10^6(j\omega R_s C_s + 1) = R_s(R_x + j\omega L_x)$

equating real and imaginary terms,

$$10^6 = R_x R_s$$

$$\Rightarrow R_x = \frac{10^6}{R_s} = 1000 \Omega$$

and $10^6 C_s = L_x$

$$\Rightarrow L_x = 10^6 \times 0.5 \times 10^{-6} = 0.5 \text{ H}$$

9. (b)

equivalent impedance,

$$Z = \frac{\left(\frac{1}{j\omega C}\right)(R + j\omega L)}{R + j\omega L + \left(\frac{1}{j\omega C}\right)} = \frac{R + j\omega(L - \omega^2 L^2 C - CR^2)}{1 + \omega^2 C^2 R^2 - 2\omega^2 LC + \omega^4 L^2 C^2}$$

So, the effective reactance,

$$X_{\text{eff}} = \frac{\omega \{L(1 - \omega^2 LC) - CR^2\}}{1 + \omega^2 C^2 R^2 - 2\omega^2 LC + \omega^4 L^2 C^2}$$

Since, X_{eff} is small, we have, $\omega^2 LC \ll 1$.

So, $\omega^2 LC$ can be neglected.

$$\therefore X_{\text{eff}} = \frac{\omega(L - CR^2)}{1 + \omega^2 C(CR^2 - 2L)}$$


If the resistance is noninductive,

then, $L - CR^2 = 0$

$$\Rightarrow R = \sqrt{\frac{L}{C}}$$

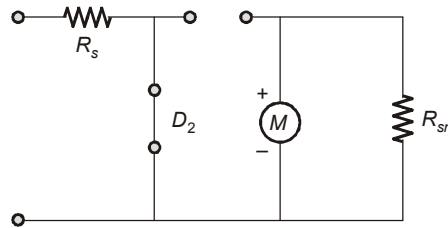10. (a)

During negative half-cycle circuit can be redrawn as shown below



From above circuit it is clear that during negative half-cycle meter is open circuited due to diode D_2 . Reverse saturation current is the current that flows in diode when reverse voltage is applied without D_2 , even though diode is open circuited, voltage across D_1 is AC voltage. With diode D_2 ON, the voltage across diode D_1 is zero.

11. (b)

instantaneous value of voltage across 1 mH inductor is

$$\begin{aligned} V_L &= L \frac{dI}{dt} = 1 \times 10^{-3} \frac{d}{dt} (0.5 + 0.3 \sin \omega t - 0.2 \sin 2\omega t) \\ &= 1 \times 10^{-3} \times \omega (0.3 \cos \omega t - 0.4 \cos 2\omega t) \end{aligned}$$

Put, $\omega = 10^6$ rad/sec then,

$$V_L = 300 \cos \omega t - 400 \cos 2\omega t$$

Hence, reading of electrostatic voltmeter across 1 mH inductor is

$$\begin{aligned} V_L &= \sqrt{\left(\frac{300}{\sqrt{2}}\right)^2 + \left(\frac{400}{\sqrt{2}}\right)^2} \\ V_L &= 354 \text{ V} \end{aligned}$$

12. (d)

Inductance, $L = (200 + 40\theta - 4\theta^2 - \theta^3) \mu\text{H}$

\therefore Rate of change of inductance,

$$\frac{dL}{d\theta} = (40 - 8\theta - 3\theta^2) \mu\text{H/rad}$$

For, $\theta = \frac{\pi}{2}$

$$\frac{dL}{d\theta} = 40 - 8 \times \frac{\pi}{2} - 3 \cdot \left(\frac{\pi}{2}\right)^2 = 20 \mu\text{H/rad}$$

and deflection, $\theta = \frac{1}{2} \cdot \frac{I^2}{K} \cdot \frac{dL}{d\theta}$

with $I = 1.5$ A, we have $\theta = \frac{\pi}{2}$ and $\frac{dL}{d\theta} = 20 \times 10^{-6}$ H/rad

$$\frac{\pi}{2} = \frac{1}{2} \times \frac{(1.5)^2}{K} \times 20 \times 10^{-6}$$

or, $K = 14.32 \times 10^{-6}$ Nm/rad

∴ spring constant, $K = 14.32 \times 10^{-6} \text{ Nm/rad}$

$$\text{Deflection, } \theta = \frac{1}{2} \times \frac{I^2}{14.32 \times 10^{-6}} (40 - 8\theta - 3\theta^2) \times 10^{-6}$$

$$\text{or, } 3\theta + 36.64\theta^2 - 40 = 0$$

$$\begin{aligned} \text{or, } \theta &= 1.008 \text{ radian} \\ &= 57.8^\circ \end{aligned}$$

13. (c)

Let,

L_C = length of capillary tube which would be occupied by mercury contained in the bulb when it is not heated; mm

$L_C + \Delta L_C$ = length of capillary tube which would be occupied by mercury contained in the bulb when heated, mm

A_C = Area of capillary tube; mm^2

α_V = coefficient of volumetric expansion/ $^\circ\text{C}$ and $\Delta\theta$ = change in temperature; $^\circ\text{C}$

It should be noted that there will be only a change in length of mercury column since it is given that the bulb has a zero expansion material and hence there will be no changes in its area and length. This is true of capillary tube as well.

Sensitivity,

$$S = \frac{(L_C + \Delta L_C) - L_C}{\Delta\theta} = \frac{\Delta L_C}{\Delta\theta} = 2.5 \text{ mm}/^\circ\text{C}$$

$$\text{Now, } A_C(L_C + \Delta L_C) = A_C(L_C + \alpha_V L_C \Delta\theta)$$

∴ length of capillary tube,

$$\begin{aligned} L_C &= \frac{1}{\alpha_V} \cdot \frac{\Delta L_C}{\Delta\theta} = \frac{1}{0.181 \times 10^{-3}} \times 2.5 = 13.8 \times 10^3 \text{ mm} \\ &= 13.8 \text{ m} \end{aligned}$$

14. (c)

from the modified De-Sauty bridge

$$\frac{R_2}{R_3} = \frac{r_1}{R_4 + r_4} = \frac{C_4}{C_1}$$


$$\begin{aligned} r_1 &= \frac{R_2(R_4 + r_4)}{R_3} = \frac{2000 \times (4.8 + 0.4)}{2850} \\ &= 3.65 \Omega \end{aligned}$$

$$\text{and, } C_1 = \frac{R_3 C_4}{R_2} = \frac{2850 \times 0.5 \times 10^{-6}}{2000} = 0.7125 \mu\text{F}$$

$$\begin{aligned} \text{and } \tan \delta_1 &= \omega C_1 r_1 = \\ &= 2\pi \times 450 \times 0.7125 \times 10^{-6} \times 3.65 = 7353.1 \times 10^{-6} \\ &= 0.007351 \\ r_1 &= \tan^{-1}(0.007351) = 0.42^\circ \end{aligned}$$

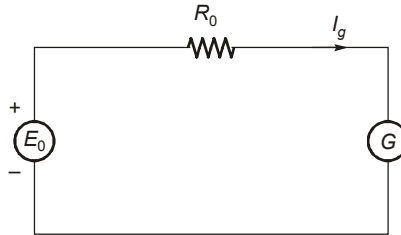15. (a)

The Thevenin equivalent circuit of the bridge is shown in figure below.



R_0 = resistance of circuit looking into terminals 'd' and 'c' with terminals 'a' and 'b' short circuits.

$$R_0 = \frac{RS}{R+S} + \frac{PQ}{P+Q}$$

$$R_0 = \frac{1 \times 5}{1+5} + \frac{1 \times Q}{1+Q}$$

$$R_0 = 0.833 + \frac{Q}{1+Q} \text{ k}\Omega \quad \dots(1)$$

Now,

$$R_0 + G = \frac{E_0}{I_g} = \frac{24 \times 10^{-3}}{13.6 \times 10^{-6}}$$

$$= 1.765 \text{ k}\Omega = 1765 \Omega$$

$$R_0 = 1765 - G$$

$$= (1765 - 100) \Omega$$

$$= 1665 \Omega$$

$$= 1.665 \text{ k}\Omega$$

Put, the value of $R_0 = 1.665 \text{ k}\Omega$ in equation (1) then, we get

$$0.833 + \frac{Q}{1+Q} = 1.665$$

or,

$$\frac{Q}{1+Q} = 1.665 - 0.833$$

or,

$$\frac{Q}{1+Q} = 0.832$$

\therefore

$$Q = 4.95 \text{ k}\Omega$$

16. (c)

For type - 1; error = $I^2 R_C$

For type - 2; error = $\frac{V^2}{R_P}$

so,

$$I^2 R_C = \frac{V^2}{R_P} = \frac{(200)^2}{10,000}$$

\Rightarrow

$$R_C = \frac{(200)^2}{10,000 \times (20)^2} = 0.01 \Omega$$

17. (d)

$$V = 230 \text{ Volt, } I = 5 \text{ A, } \cos \phi = pf = 0.1$$

$$R_p = 10 \text{ k}\Omega, L_p = 100 \text{ mH} = 0.1 \text{ H}$$

$$\therefore \beta = \tan^{-1} \left(\frac{\omega L_p}{R_p} \right) = 0.18^\circ$$

$$\phi = \cos^{-1}(0.1) = 84.26^\circ$$

Method I

$$\text{True power} = P_T = VI \cos \phi = 115 \text{ Watt}$$

Reading for lagging pf,

$$P_{read} = VI \cos(\phi - \beta) \cos \beta$$

$$= 118.6 \text{ watt}$$

$$\% \text{ error} = \frac{118.6 - 115.0}{115.0} \times 100$$

$$= 3.14\%$$

Method II

$$\% \text{ error} = \tan \phi \cdot \tan \beta \times 100$$

$$= \tan(84.26^\circ) \times \tan(0.18^\circ) \times 100$$

$$= 3.14\%$$

18. (b)

At balance,

$$Z_1 Z_4 = Z_2 Z_3$$

$$\frac{10 \times 10^3 \times X_C}{10 \times 10^3 + X_C} \times Z = 500 \times 10^3$$

$$\text{as, } X_C = \frac{1}{j\omega C} = \frac{1}{j \times 100\pi \times 100 \times 10^{-9}} = -j \frac{10^5}{\pi}$$

$$\therefore \frac{-j10^4 \times 10^5}{\pi \left(10^4 - \frac{j \times 10^5}{\pi} \right)} \times 2 = 5 \times 10^5$$

$$\Rightarrow \frac{-j10^3}{1000\pi - j10^4} (R + jX) = 5$$

$$\Rightarrow -jR + X = 5\pi - j5 \times 10$$

$$\Rightarrow R = 50 \Omega$$

$$\text{and } L = \frac{5}{2 \times 50} = 50 \text{ mH}$$

19. (c)

$$\text{units} = \pm 0.2\%$$

$$\text{Tens} = \pm 0.1\%$$

$$\text{Hundreds} = \pm 0.05\%$$

$$\text{Thousands} = \pm 0.02\%$$

$$400 \Omega \text{ error} = \pm 4000 \times \frac{0.02}{100} = \pm 0.8 \Omega$$

$$\text{For hundred error} = \pm 300 \times \frac{0.05}{100} = \pm 0.15 \Omega$$

$$\text{For tenth error} = \pm 20 \times \frac{0.1}{100} = \pm 0.02 \Omega$$

$$\text{For unit error} = \pm 5 \times \frac{0.2}{100} = \pm 0.01 \Omega$$

$$\begin{aligned} \text{Hence, total error} &= \pm(0.8 + 0.15 + 0.02 + 0.01) \\ &= \pm 0.98 \Omega \end{aligned}$$

$$\text{Limiting error} = \frac{0.98}{4325} \times 100 = 0.0226\%$$

20. (d)

Current through PMMC ammeter,

$$I = 0.9 \times 10^{-3} = \frac{1.8}{1.8 \times 10^3 + R_a}$$


Where, R_a is the ammeter resistance

$$R_a + 1.8 \times 10^3 = 2 \times 10^3$$


$$\Rightarrow R_a = 200 \Omega$$

Since, the pointer swings to 1 mA mark, it is under-damped.

Underdamped System:

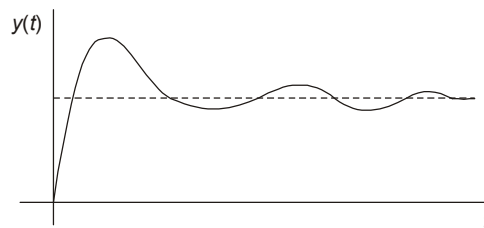

Critically Damped System:

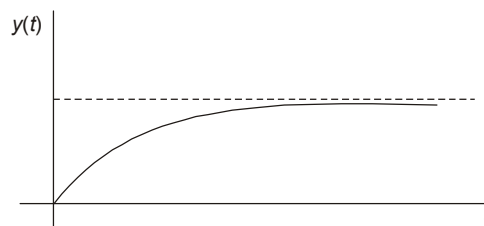

So, from the above, the system has shown a value higher than the steady state value, Hence it is underdamped system.

21. (c)

Reading of the true rms meter

$$\begin{aligned}
 V_{\text{rms(true)}} &= \sqrt{\frac{1}{T_0} \int_0^{T_0} V^2(t) dt} = \sqrt{\frac{1}{2\pi} \left[\int_0^{T_0} V^2(t) dt \right]} \\
 &= \sqrt{\frac{1}{2\pi} \int_0^{\pi/2} (3V)^2 dt + \frac{1}{2\pi} \int_{\pi/2}^{2\pi} (-1V)^2 dt} \\
 &= \sqrt{\frac{9}{2\pi} \times (t)_0^{\pi/2} + \frac{1}{2\pi} (t)_{\pi/2}^{2\pi}} \text{ V} \\
 &= \sqrt{\frac{9}{2\pi} \times \frac{\pi}{2} + \frac{1}{2\pi} \times \frac{3\pi}{2}} \text{ V} = \sqrt{\frac{9}{4} + \frac{3}{4}}
 \end{aligned}$$

$$V_{\text{rms}} = \sqrt{\frac{12}{4}} \text{ V}$$

$$V_{\text{rms}} = \sqrt{3} \text{ V}$$

22. (c)


$$C_2 = 106 \mu\text{F}$$

$$C_4 = 0.35 \mu\text{F}$$

$$R_4 = 318 \Omega$$

$$R_3 = 130 \Omega$$
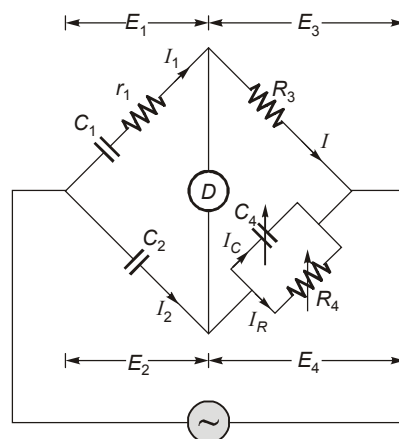
$$C_1 = C_2 \left(\frac{R_4}{R_3} \right) = 259.29 \mu\text{F}$$



Schering Bridge

23. (c)

Error in reading of first meter

$$= \text{FSD} \times \text{accuracy}$$

$$= 20 \times \frac{\pm 0.1}{100} = \pm 0.02$$

Error in reading of second meter

$$= 10 \times \frac{\pm 0.2}{100} = \pm 0.02$$

Error in reading of third meter

$$= 5 \times \frac{\pm 0.5}{100} = \pm 0.025$$

Error in reading of fourth meter

$$= 1 \times \frac{\pm 1.00}{100} = \pm 0.01$$

Third meter has maximum error.

24. (b)

 $I = 0$, means the potential difference between 'AB' and 'AD' is same so the bridge is balanced.

At bridge balance condition.

so, $Z_1 Z_4 = Z_2 Z_3$

$$(R_1 + j\omega L_1) \cdot \left(R_4 + \frac{1}{j\omega C_4} \right) = R_2 R_3$$

$$R_1 R_4 + \frac{L_1}{C_4} = R_2 R_3$$

Similarly, for phase angles also equal for

$$\underline{|\theta_2 + \theta_3|} = \underline{|\theta_1 + \theta_4|}$$

$$\tan^{-1} \left(\frac{\omega L_1}{R_1} \right) - \tan^{-1} \left(\frac{1}{\omega C_4 R_4} \right) = 0 + 0$$

$$\tan^{-1} \left(\frac{\omega L_1}{R_1} \right) = \tan^{-1} \left(\frac{1}{\omega C_4 R_4} \right)$$

$$\frac{\omega L_1}{R_1} = \frac{1}{\omega C_4 R_4}$$

$$\text{So, } 2 \omega L_1 = \frac{2 R_1}{\omega C_4 R_4}$$

25. (c)


Since r is negligible and P, Q, p and q have large values, the effect of ratios arms can be neglected for the purpose of calculation of current,

$$\therefore I = \frac{E}{R_b + R + S} \quad \dots(1)$$

and
$$R = \frac{P}{Q} \cdot S = \frac{1000}{1000} \times 0.001 = 0.001 \Omega$$

From (1),
$$I = \frac{100}{5 + 0.001 + 0.001} \cong 20 \text{ A}$$

26. (b)

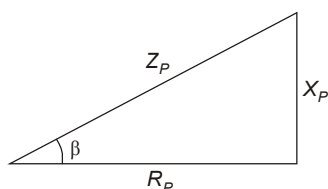

$$V_L = 220 \text{ V,}$$

$$I_L = 4 \text{ A,}$$

$$\cos \phi = 0.1,$$

$$R_p = 10,000 \Omega$$

$$\text{True power} = V_L I_L \cos \phi = 220 \times 4 \times 0.1 = 88 \text{ W}$$

Error due to pressure coil inductance of 100 mH

$$L = 100 \text{ mH}$$

$$\Rightarrow X_p = \omega L = 2\pi f L \quad (\text{Assume } f = 50 \text{ Hz})$$

$$= \pi \times 50 \times 100 \times 10^{-3}$$

$$X_p = 31.415 \Omega$$

$$R_p = 10,000 \Omega$$

From impedance triangle of potential coil.

$$Z_p = \sqrt{X_p^2 + R_p^2}$$

$$\therefore \tan \beta = \frac{X_p}{R_p}$$

$$\therefore \beta = \tan^{-1} \left(\frac{X_p}{R_p} \right) = \tan^{-1} \left(\frac{31.415}{10000} \right) = 0.18^\circ$$

$$\begin{aligned} \% \text{ error} &= \tan \beta \cdot \tan \phi \times 100 \\ &= \tan (0.18) \cdot \tan [\cos^{-1} (0.1)] \times 100 \\ &= 3.141 \times 10^{-3} \times 9.949 \times 100 \\ &= 3.125 \end{aligned}$$

27. (b)

$$\begin{aligned}
 V_0 &= \frac{V_R}{2^n} (a_{n-1} 2^{n-1} + a_{n-2} 2^{n-2} + \dots + a_1 2^1 + a_0 2^0) \\
 &= \frac{6.5}{2^6} (2^4 + 2^3 + 2^2) = 6.5 \times \frac{28}{64} \\
 &= 2.84 \text{ V}
 \end{aligned}$$

28. (a)

Steady deflection, $\theta = \frac{1}{2} \frac{V^2}{K} \cdot \frac{dc}{d\theta}$

When, $\theta = \frac{\pi}{2} \text{ rad,}$

$$\frac{dc}{d\theta} = \frac{2\theta K}{V^2} = \frac{2 \times \frac{\pi}{2} \times 5 \times 10^{-6}}{(2 \times 10^3)^2} = 3.93 \times 10^{-12} \text{ F/rad}$$

Change in capacitance when reading from 0 to 2000 V

$$= 3.93 \times 10^{-12} \times \frac{\pi}{2} = 6.17 \text{ pF}$$

Therefore, capacitance when reading is 2000 V

$$\begin{aligned}
 C &= 15 + 6.17 \\
 &= 21.17 \text{ pF}
 \end{aligned}$$

29. (d)

$$\text{Velocity of beam} = V_{ox} = \left(\frac{2eE_a}{m} \right)^{\frac{1}{2}}$$

$$= \left[\frac{2 \times 1.6 \times 10^{-19} \times 2000}{9.1 \times 10^{-31}} \right]^{\frac{1}{2}}$$

$$V_{ox} = 26.5 \text{ m/s}$$

30. (d)

$$r_d = 1000 \Omega, I_{FS} = 50 \times 10^{-6} \text{ A}$$

The dc sensitivity,

$$\begin{aligned}
 S_{dc} &= \frac{1}{50 \times 10^{-6}} = 20000 \Omega/\text{V} \\
 &= 20 \text{ k}\Omega/\text{V}
 \end{aligned}$$

For a full wave rectifier circuit,

$$\text{ac sensitivity, } S_{ac} = 20000 \times 0.9 = 18000 \Omega/\text{V} = 18 \text{ k}\Omega/\text{V}$$

$$\therefore \text{ Resistance of multiplier} = R_s = S_{ac} \times V_{rms} - R_m - 2r_d$$

$$\begin{aligned}
 R_s &= S_{ac} \times 10 - R_m - 2r_d \\
 &= 180000 - 1000 - 2000 = 177000 \Omega \\
 &= 177 \text{ k}\Omega
 \end{aligned}$$

