



MADE EASY
Leading Institute for ESE, GATE & PSU's

ESE 2025 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

Electronics & Telecommunication Engineering

Test-2 : Digital Circuits + Signals and Systems
+ Microprocessors & Microcontroller [All topics]

Name :

Roll No :

Test Centres	Student's Signature
Delhi <input type="checkbox"/> Bhopal <input type="checkbox"/> Jaipur <input type="checkbox"/> Pune <input type="checkbox"/> Kolkata <input type="checkbox"/> Hyderabad <input checked="" type="checkbox"/>	

Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	
Q.2	
Q.3	
Q.4	
Section-B	
Q.5	
Q.6	
Q.7	
Q.8	
Total Marks Obtained	

Signature of Evaluator

Cross Checked by

IMPORTANT INSTRUCTIONS

CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.

DONT'S

1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

DO'S

1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

Section A : Digital Circuits + Signals and Systems + Microprocessors & Microcontroller

Q.1 (a) Design a 3-bit binary counter using T-flip-flops.

[12 marks]

Sol.


Given : no of bits = 3

we Req = 3-flip flop for implementation

Flip-flop : T-flip-flop

Design : Up-Counter

000 to 111

 


⇒ It will Count up to 0 to 111 ⇒ 3-bit upCounter

Truth table must for full marks

- Q.1 (b) (i) Draw the circuit for interfacing 512 bytes of memory to 8085 microprocessor using 3×8 decoder.
- (ii) Write an assembly language program to move a block of Data of 16 bytes starting from address 2050H to another location starting from 2070H in 8085 microprocessor.
- [7 + 5 marks]

Ans

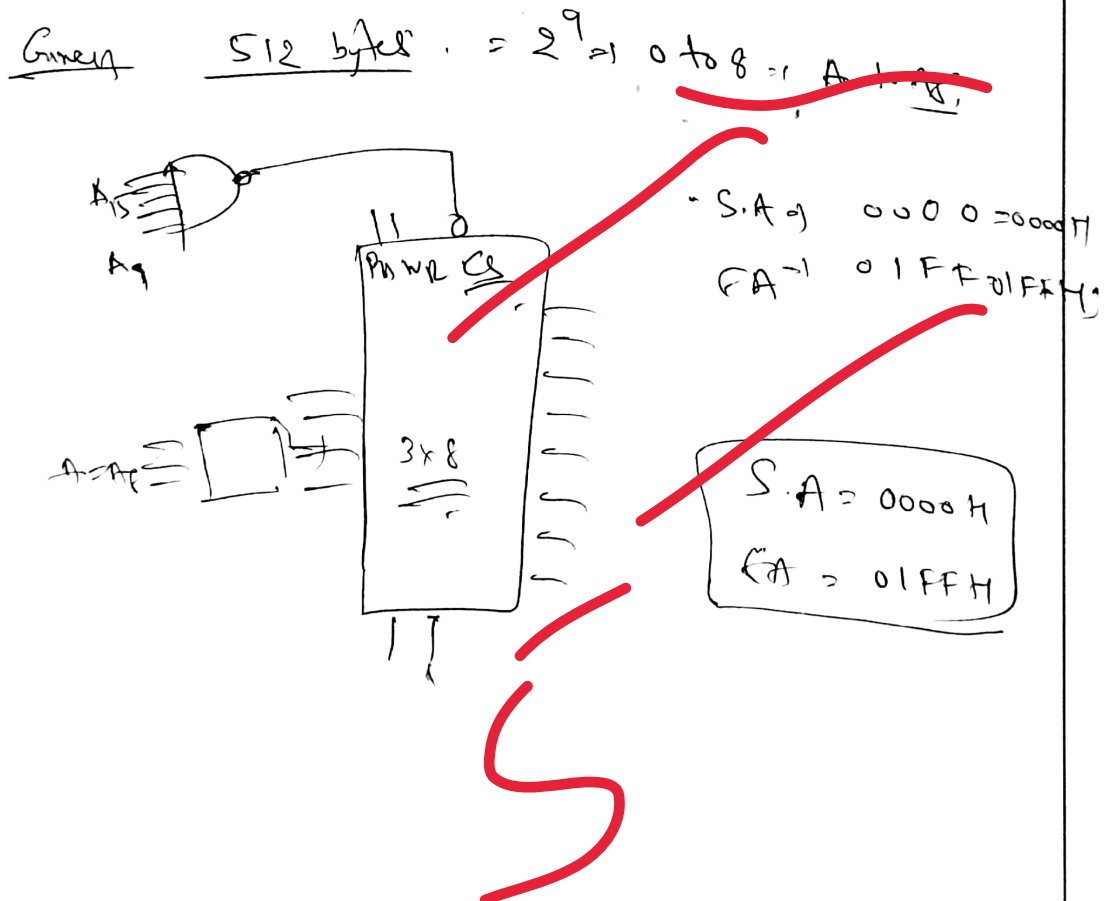



- Q.1 (c) (i) Draw the signal flow graph (Butterfly structure) for the computation of 8-point IDFT using inverse Radix-2 DIF-FFT.
- (ii) State and prove Initial-value theorem of z-transform.

[8 + 4 marks]

(11)

(i)


z-TransformInitial value theorem:

$$\lim_{n \rightarrow 0} x(n) = \lim_{z \rightarrow \infty} (1 - z^{-1}) X(z)$$

Initial value of discrete signal can be calculated by finding final value by put $[z \rightarrow 1] : (1 - z^{-1})$

multiply:

(12)

 

8-point Twiddle DFT.

$$W_8^0 = 1$$

$$W_N^{kv} = e^{-j \frac{2\pi}{N} kv}$$


$$W_8^1 = -j$$

$$W_8^2 = \frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}}$$


$$W_8^3 = \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}}$$

Q.1 (d)

 - (i) Draw the timing diagram for the logic circuit in the figure shown with outputs of G_1 , G_2 and G_3 with input waveform A and B as indicated.



 - (ii) Consider the serial in-serial out shift register which is used to provide time delay from input to output.




Draw and calculate the output and delay provided by the above shift register in clear steps.

[6 + 6 marks]


Sol

Given $G_2 = AB$, $G_3 = \overline{A}B$, $G_1 = G_2 + G_3$

 $G_3 = \overline{A+B}$ $G_1 = AB + \overline{A}B = A \oplus B$



11

 


→ Given: SISO = serial input serial o/p:

$$Time \Rightarrow (n+1) T_{clk}$$

$$Time = 15 T_{clk} = 15 \times 1 \mu s = 15 \mu s$$

delay:

 

- Q.1 (e) Consider the signal $y(t) = e^{-2t}u(t)$ is the output of a causal all-pass system for which the system function is


$$H(s) = \frac{s-1}{s+1}$$

- (i) Find and sketch at least two possible inputs $x(t)$ that could produce $y(t)$.
 (ii) From the solutions obtained in part (i), what is the input $x(t)$ if it known that a stable system exists that will have $x(t)$ as an output and $y(t)$ as the input? Find the impulse response $h(t)$ for this system.

[6 + 6 marks]

Sol.
 
$$y(t) = e^{-2t}u(t) \quad H(s) = \frac{s-1}{s+1}$$



$$Y(s) = H(s)X(s)$$

$$\frac{1}{(s+2)} = \frac{s-1}{s+1} \cdot X(s)$$

$$X(s) = \frac{s+1}{(s-1)(s+2)}$$

$$X(s) = \frac{A}{s-1} + \frac{B}{s+2}$$

$$= \frac{2}{3} \cdot \frac{1}{s-1} + \frac{1}{3} \cdot \frac{1}{s+2}$$

$$x(t) = \frac{2}{3}e^t + \frac{1}{3}e^{-2t}$$

→ two input
that produce $y(t)$

$$y(t) = \frac{2}{3}e^t + \frac{1}{3}e^{-2t}$$

(ii)

from part $y(t) = \frac{2}{3}e^t + \frac{1}{3}e^{-2t}$

if input $x(t) = \frac{1}{3}e^{-2t}$ then output

will produce stable o/p. for the input.

if $x(t) = \frac{1}{3}e^{2t}$ will get RFBOL

on other hand $\frac{2}{3}e^{+t}$ pole $\therefore \boxed{S=1}$ right

side it will become unstable

$$H(s) = ? \quad y(t) = e^{2t} \rightarrow \boxed{x(t) = \frac{1}{3}e^{-2t}}$$

$$Y(s) = H(s) \times X(s)$$

$$\frac{1}{s-2} = \frac{1}{3} \cdot \frac{1}{s+2} \cdot H(s)$$


$$\boxed{H(s) = 3} \quad \boxed{x(t) = 3u(t)}$$

- Q.2 (a) Implement the state diagram and sequential circuit diagram using JK flip-flops for 3-bit Gray code counter. [20 marks]

Sol:

Gray Code Counter: $n=3$ -bits

State diagram: 0, 1, 3, 2, 6, 7, 5, 4

 



Truth Table


Q_2, Q_1, Q_0	Q_2^T, Q_1^T, Q_0^T	$J_2, K_2, J_1, K_1, J_0, K_0$
0 0 0	0 0 1	0 x 0 x 1 x
0 0 1	0 1 1	0 x 1 x x 0
0 1 0	1 1 0	1 x x 0 0 x
0 1 1	0 1 0	0 x x 0 x 1
1 0 0	0 0 0	x 1 0 x 0 x
1 0 1	1 0 0	x 0 0 x x 1
1 1 0	1 1 1	x x x 0 1 x
1 1 1	1 1 0	x 0 x 0 x 0

Excitation Table for T.K-01g

Q ₀ Q ₁	Q ₀ Q ₁
0 0	0 x
0 1	1 x
1 0	x 1
1 1	x 0

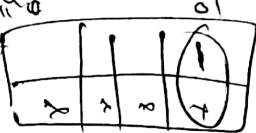J_2  $\rightarrow J_2 = \bar{Q}_1 Q_0$


K_2  $\rightarrow K_2 = \bar{Q}_1 \bar{Q}_0$

J_1  $= J_1 = \bar{Q}_0 Q_1$

K_1  $K_1 = 0$

J_0  $J_0 = \bar{Q}_1 + Q_1 = 1$

Seq. Circuit.

 

Q.2(b)

- (i) Determine and sketch $y(t)$, the convolution of the two signals given below:

$$x(t) = \begin{cases} 2, & -1 \leq t \leq 1 \\ 1, & 1 < t \leq 3 \\ 0, & \text{elsewhere} \end{cases}$$

$$\text{and } h(t) = 2\delta(t+1) + \delta(t+2)$$

- (ii) The output $y(t)$ of a causal LTI system is related to the input $x(t)$ by the equation

$$\frac{dy(t)}{dt} + 10y(t) = \int_{-\infty}^{\infty} x(\tau)z(t-\tau)d\tau - x(t)$$


$$\text{where, } z(t) = e^{-t}u(t) + \delta(t)$$

Determine the impulse response of the system.

[10 + 10 marks]

Sol
 
$$x(t) = 2[u(t+1) - u(t-1)] + u(t-1) - u(t-3)$$



$$h(t) = 2\delta(t+1) + \delta(t+2)$$

$$y(t) = [x(t) * h(t)]$$

$$y(t) = [2u(t+1) - 2u(t-1) + u(t-1) - u(t-3)] * [2\delta(t+1) + \delta(t+2)]$$

Property: $\{x(t) * \delta(t-t_0)\} = x(t-t_0)$

$$y(t) = 2u(t+1+1) - 2u(t-1+1) + u(t+1+1) - u(t-3+1)$$


$$+ 2u(t+1+2) - 2u(t-1+2) + u(t+2) - u(t-3+2)$$




$$y(t) = 4u(t+2) - 4u(t) + 2u(t-1) - 2u(t-3) + u(t+2) - 4u(t-1) - 2u(t-3)$$

$$y(t) = 5u(t+2) - 4u(t) + 2u(t+3) - 2u(t-3) + u(t+1)$$
 
$$y(t) = 2u(t+3) + 5u(t+2) - 4u(t) - 4u(t-1) - 2u(t-3)$$



y(t)

 

1.

$$y(t) = \frac{1}{s+10} \Rightarrow \frac{1}{s+10} = \frac{1}{s+10} \Rightarrow \frac{1}{s+10} = \frac{1}{s+10}$$

$$\frac{dy(t)}{dt} + 10y(t) = 1$$

$$(s+10)y(s) = \frac{1}{s+10} \Rightarrow y(s) = \frac{1}{(s+10)^2}$$

$$\frac{1}{(s+10)^2} = \frac{A}{s+10} + \frac{B}{(s+10)^2}$$

$$y(t) = \frac{1}{9} e^{-10t} + \frac{2}{9} t e^{-10t}$$

Q.2 (c) (i) Interface 4 KB memory to 8085 with starting address A000H. Design address decoding circuit using (i) 3 x 8 decoder and (ii) using only NAND gates.

(ii) Write an algorithm and assembly language program, to perform the multiplication of two 8 bit numbers using 8085.

[10 + 10 marks]

Ans.

1.

Starting address = A000H

memory = 4KB = 2¹² B

A₁₅ - A₁₁ = (A000 - FFFF)

⇒ A₁₅ - A₁₂ - A₁₁ - A₁₀ - A₉ - A₈ - A₇ - A₆ - A₅ - A₄ - A₃ - A₂ - A₁ - A₀

1010

0

0

0

⇒ A000

1010

1


1

1

⇒ AFFF

Decoding circuit = A₁₅ A₁₄ A₁₃ A₁₂

 $\frac{A_{15}}{A_{14}}$
 $\frac{A_{13}}{A_{12}}$
 $\frac{A_{11}}{A_{10}}$
 $\frac{A_9}{A_8}$
 $\frac{A_7}{A_6}$
 $\frac{A_5}{A_4}$
 $\frac{A_3}{A_2}$
 $\frac{A_1}{A_0}$



$SA = A000$

$EA = AFFF$

\Rightarrow Designed 2×8 and NAND of 4KB Port

(15)

Given: multiplication of two 8 bits numbers

Let say take: ~~10H, 20H~~ \Rightarrow 15H, 25H

Program:

~~MOV B, #15H~~

Program:

MOV B, #15H

MOV A, #25H

MUL A

STA 1000H

HLT




\Rightarrow

$$\begin{array}{r} 15 \\ \times 25 \\ \hline 375 \end{array}$$



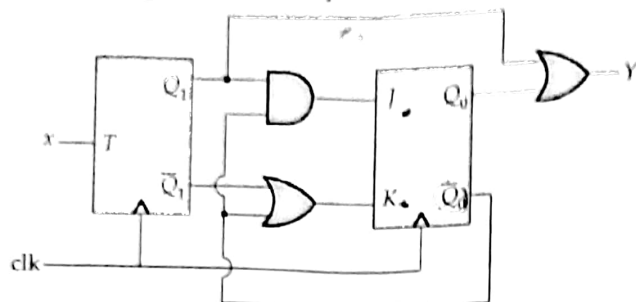Q.3 (a) (i) Draw the state diagram of the sequential circuit shown in figure below:



(ii) Find the z-transform of the given signal $x[n]$ using scaling in the z-domain property.

$$x[n] = a^n \sin(\omega_0 n) u[n].$$

[10 + 10 marks]

~~Ans~~

Truth Table =

x	Q_1	Q_0
0	0	0
1	0	1
0	1	0
1	1	1

Q_1	Q_0
0	0
0	1
1	0
1	1

Q_1	Q_0
0	0
0	1
1	0
1	1

x	Q_1	Q_0
0	0	0
1	0	1
0	1	0
1	1	1

Q_1	Q_0
0	0
0	1
1	0
1	1

Q_1	Q_0
0	0
0	1
1	0
1	1

Q_1	Q_0
0	0
0	1
1	0
1	1

Sol.

$$J_0 = Q_1 \bar{Q}_0 \quad ; \quad T_1 = x = \text{input}$$

$$K_0 = \bar{Q}_1 + \bar{Q}_0 \quad ; \quad Y = Q_1 + Q_0$$

input = x;

output = y;

Initial State, Q_1, Q_0

next state, Q_1, Q_0

Present		next state	output
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

(ii)

$$x(n) = a^n \sin(\omega_0 n) u(n)$$

$$\Downarrow$$

applying Z-Transform

$$X(z) = \sin(\omega_0) u(n)$$

$$\Downarrow$$

$$X(z) \Rightarrow \frac{z^2 - z \sin \omega_0}{z^2 + z \cos \omega_0 + 1}$$

$$\Downarrow$$

$$a^n x(n) \Rightarrow X\left(\frac{z}{a}\right) \text{ - property: multiplication}$$

$$X(z) \Rightarrow \frac{\left(\frac{z}{a}\right)^2 - \left(\frac{z}{a}\right) \sin \omega_0}{\left(\frac{z}{a}\right)^2 + 2\left(\frac{z}{a}\right) \cos \omega_0 + 1}$$

$$X_{ZC} = \frac{\frac{Z^L}{a^2} - \frac{Z \sin \omega a}{a}}{}$$

$$\frac{Z^2}{a^2} - \frac{2Z \sin \omega a}{a} + 1$$

$$X_{ZC} = \frac{Z^2 - a^2 \sin^2 \omega a}{Z^2 - 2aZ \sin \omega a + a^2}$$


8

 - Q.3 (b) (i) Implement the following Boolean function using $3 \times 4 \times 2$ PLA, also write the PLA programming table.
- $$F_1(A, B, C) = \sum m(0, 1, 2, 4)$$
- $$F_2(A, B, C) = \sum m(0, 5, 6, 7)$$
- (ii) A 6-bit dual slope ADC uses a reference of 12 V and a fixed count of 010110. Convert the maximum input voltage accurately in digital form.

[15 + 5 marks]




$$F_1(A, B, C) = \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}B$$



$$F_2(A, B, C) = AC + AB + \bar{A}B\bar{C}$$

PLA: $3 \times 4 \times 2$

 

(ii)

$$V_R = 12V \quad n = 6 \text{ bits}$$

$$\text{Gent.} \Rightarrow (010110)_2$$

$$V_0 = \frac{V_{ref}}{2^n - 1} \times (\text{Digital})$$

$$V_0 = \frac{12}{2^6 - 1} \times (010110)_2$$


$$(010110) = 2 \times 1 + 2^2 \times 1 + 2^3 \times 1 = 8 + 4 + 2 = 14$$

$$V_0 = \frac{12}{63} \times 14$$

$$V_0 = 2.66 \text{ voltage}$$

$$V_0 \approx 2 \text{ accurately}$$

 Q.3 (c) Consider the sequential circuit given below:




- Find the count sequence of the circuit given above. Assume initial condition of flip-flop to be zero.
- If clock frequency is 160 kHz. Find the frequencies of Q_0 and Q_2 .
- Sketch the waveforms of clock, Q_0 , Q_1 , Q_2 and Q_3 .


[8 + 4 + 8 marks]

Sol:

Given:

 

CLK	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

 

(11)

$$f_{\text{input}} = 160 \text{ kHz};$$

$$f_{Q_0}, f_{Q_2} = ?$$

$$f_{Q_0} = \frac{f}{2} = \frac{160}{2} = 80 \text{ kHz};$$

$$f_{Q_2} = \frac{f}{8} = \frac{160}{8} = 20 \text{ kHz};$$

(12)




wave form

- Q.4 (a) (i) Explain how linear convolution is performed using DFT. Find the linear convolution of $x[n] = \{1, 1, 1\}$ and $h[n] = \{1, 1\}$ using DFT.
- (ii) Derive the relationship between discrete Fourier series coefficients (C_k) and discrete Fourier Transform $X(k)$ of a signal $x[n]$.

[15 + 5 marks]



 - Q.4 (b) (i) Implement the logic function $F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 7, 9, 10)$ using 4 : 1 MUX only. (Assume only inputs are available)
- (ii) Construct a 4 K × 8 RAM with 1 K × 8 RAM chips. The 1 K × 8 RAM is as shown below:



[10 + 10 marks]



Do not
write in
this margin





- Q.4 (c)
- (i) Write an 8051 assembly language program for converting the packed BCD number stored at the location 9000H into its equivalent binary number and store the result at 9001H.
 - (ii) Write an 8086 assembly language program to find the sum $\sum_{i=1}^{10} i$ and store the result in accumulator.

[12 + 8 marks]

**Section B : Digital Circuits + Signals and Systems
+ Microprocessors & Microcontroller**

Q.5 (a) (i) Find the Laplace transform of the function

$$f(t) = 2e^{-t} \cos 10t - t^4 + 6e^{-(t-10)} \text{ for } t > 0$$

(ii) Find the Fourier transform for the following signal:

$$x(t) = \frac{\sin(2\pi t)}{\pi(t-1)}$$

[8 + 4 marks]

Sol

(i) $f(t) = 2e^{-t} \cos 10t - t^4 + 6e^{-(t-10)} \text{ for } t > 0$

$$f(t) = 2e^{-t} \cos 10t$$

↓ L.T

$$f(s) = L\{2e^{-t} \cos 10t\}$$

$$f(s) = 2 \cdot \frac{s}{s^2 + 10^2} \Big|_{s \rightarrow s-1} = \frac{2(s-1)}{(s-1)^2 + 100} \quad \text{--- (2)}$$

$$f_2(t) = t^4$$

$$f_1(s) = \frac{4!}{s^5} \quad \therefore L\{t^n\} = \frac{n!}{s^{n+1}}$$

$$f_2(s) = \frac{24}{s^5} \quad \text{--- (2)}$$

$$f_3(s) = 6e^{-(t-10)} = 6e^{-t+10}$$


||

$$F_3(s) = 6 \frac{e^{+10s}}{s+1} \quad F\{x(t-t_0)\} = x(s)e^{-s \cdot t_0}$$

$$F_3(s) = \frac{6e^{10s}}{s+1} \quad \text{--- (3)}$$

$$F(s) = \frac{2(s+1)}{(s+1)-100} = \frac{24}{s^5} + \frac{6e^{10s}}{s+1}$$

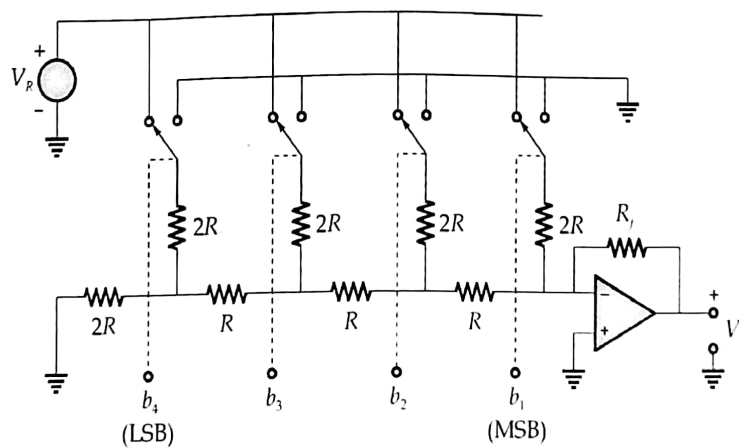Q.5 (b) Consider the R - $2R$, 4-bit converter shown below,



Assume the feedback resistance R_f of the op-amp is variable, the resistance $R = 5 \text{ k}\Omega$ and $V_R = 10 \text{ V}$. Determine the value of R_f that should be connected to achieve the following output conditions:

- The value of 1 LSB at the output is 1 V.
- An analog output of 8 V for a binary input of 1000.
- The actual maximum output voltage of 10 V.

[12 marks]

21

$$R = 5 \text{ k}\Omega; R_f = ?$$

$$V_R = 10 \text{ V}$$

Given: $R = 12 \text{ k}\Omega$ (adev)

The op voltage of given system.

$$V_o = \frac{V_R}{2^n - 1} \cdot \frac{R_F}{R} \quad (\text{Decimal Eg. binary})$$

① $1 \text{ LSB} = 1 \text{ V}$

② $V_o = 8$, Decimal Eg = $(1000) = 8$

③ $V_o = 10 \text{ V}$ - mark

④ $V_R = 10$, $R_F = \frac{V_R}{2^n - 1}$, $n = 4 \text{ bits}$

$$1 = \frac{10}{2^4 - 1}$$

⑤ $R_F = \frac{10}{2^4 - 1} \cdot \frac{R_F}{5} (8)$

$$R_F = \frac{5(2^4 - 1)}{10} = 7.5 \text{ k}\Omega$$

Q.5 (c) Compute and plot the convolution $y[n] = x[n] * h[n]$ using time domain approach

where $x[n] = \left(\frac{1}{2}\right)^{-(n-1)} u[-n-1]$ and $h[n] = u[n-1]$.

[12 marks]





Sol.

Given:

$$y[n] = x[n] * h[n]$$

$$x[n] = \left(\frac{1}{2}\right)^{-(n-1)} u[-n-1] \quad h[n] = u[n-1]$$
    
$$y[n] = \sum_{k=-\infty}^{\infty} x[k] h[n-k] \rightarrow \text{Convolution}$$



$$y(n) = \sum_{k=p}^{\infty} x(k) h(-k+n-1)$$

① ~~$k+n-1 > 0$~~ $k-1 > 0$

$$k > 0$$

② $k-1 > n$

$$-k > n+1$$

$$k < n+1$$

$$k+n-1 = -1$$

$$k+n=0$$

$$k=0$$

$$y(n) = \begin{cases} x(k) h(k), & k < -1 \\ 0, & k > -1 \end{cases}$$

$$x(n) = \left(\frac{1}{2}\right)^{n-1} u(n-1)$$

$$\Rightarrow \begin{cases} \frac{a}{1-a^2} & -\infty \text{ to } -1 \end{cases}$$

$$= \frac{1}{1-\frac{1}{4}} = \frac{1}{\frac{3}{4}} = \frac{4}{3} = \frac{1}{\frac{3}{4}} = \frac{4}{3}$$

$$x(n) = \begin{cases} \frac{2}{2} \end{cases}$$

$$y[n] = \left(\frac{1}{2}\right)^{n-1} u[n-1] + u[n-1]$$

$$= 2 \left(\frac{1}{2}\right)^{n-1} u[n-1] + u[n-1]$$

$$= 2 \left(\frac{1}{2}\right)^n u[n-1] + u[n-1]$$

$$= 2 \frac{z}{z-2} - \frac{z}{z-1} \cdot z$$

$$y(z) = 2 \frac{z}{(z+1)(z-2)}$$

Q.5 (d)

Explain the function of following pins of 8086 microprocessor:

1. $\overline{\text{BHE}}/\text{S7}$
2. $\text{MN}/\overline{\text{MX}}$
3. $\overline{\text{TEST}}$
4. READY
5. RESET
6. INTR

[12 marks]

Sol.

① $\overline{\text{BHE}}/\text{S7}$: In this pin in 8086 microprocessor goes high when low signal given, it will make state to hold in high, the test.

② $\text{MN}/\overline{\text{MX}}$: $\text{MN} = 1 = \text{high} = \text{ON}$
 $\overline{\text{MX}} = 0 = \text{low} = \text{PN}$

It will used to indicate min and maximum of signal.

③ Test: It will be used in rep. to test the signal that are available at the end of the instructions.

④ Ready: It will be Active high signal, where the up has the device they are available to take the signal or they are ready to transfer the signal.

RESET: It is used to Reset the μ at a point where all the pins come to a reset mode.

INTR: It is External interrupt hardware signal to indicate the μ to a interrupt request from the i/o device and External Communication.


Q.5 (e) Consider a three input Boolean function $f(a, b, c) = \sum m(0, 1, 2, 3, 7)$

- (i) Implement the function using a minimal network of 2×4 decoder and OR gates.
- (ii) Implement the function using a minimal network of 4×1 multiplexers.
- (iii) Implement the function using a minimal network of 2×1 multiplexers.

[4 + 4 + 4 marks]

Ans: ① $f(a, b, c) = \sum m(0, 1, 2, 3, 7)$

decoder:

 


(i)

4x1 mux

$$\sum (a, b, c) = \sum 0, 1, 2, 3, 7$$

	00	01	10	11
\bar{a}	0	1	2	3
a	4	5	6	7
	\bar{a}	\bar{a}	\bar{a}	1

 

$$\sum f(1, 0, 2, 3, 7)$$


(ii)

$$\underline{2 \times 1 \text{ MUX}}: \sum (a, b, c) = \sum 0, 1, 2, 3, 7$$

Truth table

	bc = 00	01	10	11
a	0	1	2	3
1	4	5	6	7
 
$$\Rightarrow \bar{a} + bc = \sum f(a, b, c)$$



a

Select line

Symbol: \bar{a} a

	00	01	10	11
bc	0	1	2	3
	4	5	6	7
	\bar{a}	\bar{a}	\bar{a}	1

- Q.6 (a) (i) Write an 8086 assembly language program to add the two BCD data 29H and 98 H and store the result in BCD form in the memory locations 2000 H : 3000 H and 2000 H : 3001 H.
- (ii) Explain the series of steps performed by 8086 microprocessor during processing of an interrupt request.

[10 + 10 marks]

Sol.

(ii) Interrupt Request:-

⇒ The Interrupt is the External Signal which is interrupt the ongoing execution of the

program : During the INTR:- The process

is going on its execution of current instruction

and then it will store the next instruction in the Stack pointer.

Then it will be executed the interrupt signal and then it will come back its original loop and then it will continue further instructions.

①

Given Data: $A = 29H$
 $B = 98H$

Add this and store in the $2000H : 2000H$ and
 $2000H : 2001H$

~~⇒ Program~~

~~⇒ MOV A, 29H~~

~~⇒ MOV B, A~~


~~* MOV C, 98H~~

~~⇒ ADD C~~

~~⇒ STA 2000H~~

~~HLT~~

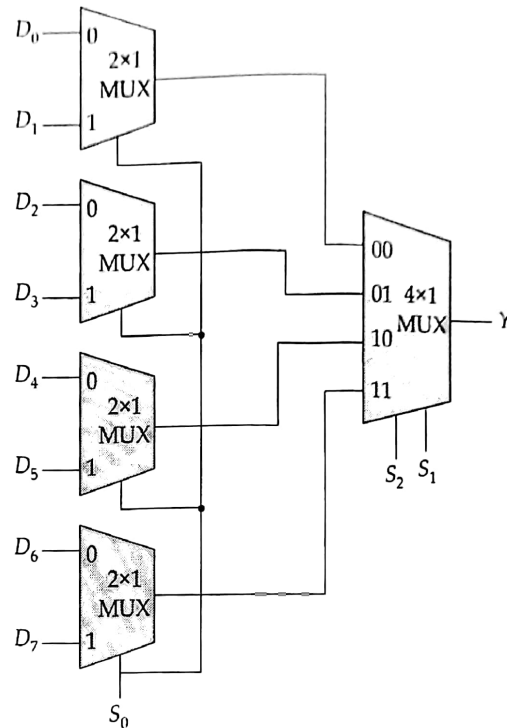
- Q.6 (b) (i) Minimize the SOP terms given for a Boolean function,
 $f(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$
 Implement the minimized function using NAND gates alone.
- (ii) Determine the logic equation for the output by constructing the truth table for the logic circuit shown in figure below:



[12 + 8 marks]

Sol:
 
$$f(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$$




$$f(A, B, C, D) = \bar{B}\bar{C} + \bar{A}\bar{D} + AC$$

It is used to implement using only
 NAND gate.


$$f(A, B, C, D) = \overline{A}C + \overline{A}D + BC$$

$$x = \overline{A}C + \overline{A}D$$


$$x = \overline{A}C + \overline{A}D$$

 
 
$$\underline{f(A, B, C)} = \overline{x + \overline{B}C} = \overline{x} \overline{\overline{B}C}$$



UNND Realization

 

(11)

4 x 1 = 4 marks

Ans

$$\text{output} = S_2 S_1 I_0 + S_2 S_1 I_1 + S_2 S_1 I_2 + S_2 S_1 I_3$$

$$I_0 = \text{from table: } S_0 D_0 + S_0 D_1$$

$$I_1 = \text{from table: } S_0 D_2 + S_0 D_3$$

$$I_2 = S_0 D_4 + S_0 D_5$$


$$I_3 = S_0 D_6 + S_0 D_7$$

$$\therefore \text{output} = S_2 S_1 [S_0 D_0 + S_0 D_1] + S_2 S_1 [S_0 D_2 + S_0 D_3]$$

$$+ S_2 S_1 [S_0 D_4 + S_0 D_5] + S_2 S_1 [S_0 D_6 + S_0 D_7]$$

 Q.6 (c)

A sequential circuit has two J-K flip flops A and B as shown below, two inputs x and y , and one output Z . The flip flop input equations and circuit output equation are




$$J_A = Bx + \bar{B}\bar{y}; \quad K_A = \bar{B}x\bar{y}$$

$$J_B = \bar{A}x; \quad K_B = A + x\bar{y}$$

$$Z = A\bar{x}\bar{y} + B\bar{x}\bar{y}$$

- (i) Draw the logic diagram of the circuit.
- (ii) Tabulate the state table.
- (iii) Derive the state equations for A and B.

[20 marks]

 

②


J_A	K_A	J_B	K_B	Q_A	Q_B	Q_A^+	Q_B^+	Y

$$J_A = Bn + By \quad J_B = Bny$$

$$J_B = An \quad J_B = A + ny$$

$$Z = Any + Bny \quad (A+B)ny$$

Logic diagram:

 

(15)

State table:

[illegible]

- Q.7 (a) (i) With a neat block diagram, explain the operation of counter type ADC. Give advantages and disadvantages of counter type ADC.
- (ii) Define fan-out of a gate. A two-input NAND gate specifications are given as
 $I_{OH(max)} = 0.4 \text{ mA}$, $V_{OH(min)} = 2.7 \text{ V}$, $V_{IH(min)} = 2 \text{ V}$,
 $V_{IL(max)} = 0.8 \text{ V}$, $V_{OL(max)} = 0.4 \text{ V}$, $I_{OL(max)} = 8 \text{ mA}$,
 $I_{IL(max)} = 0.4 \text{ mA}$, $I_{IH(max)} = 25 \mu\text{A}$, $t_{PLH} = t_{PHL} = 15 \text{ nsec}$
and supply voltage of 5 V. Determine
1. High state noise margin.
 2. Low state noise margin.
 3. Number of NAND gate inputs that can be driven from the output of a NAND gate of this type.

[12 + 8 marks]



Q.7 (b)

Each of the following arithmetic operation is correct in atleast one number system. Determine the possible bases in each operation.

(i) $3441 + 4235 = 7676$

(ii) $\frac{142}{7} = 16$

(iii) $23 + 44 + 14 + 32 = 223$

(iv) $21 \times 16 = 366$

(v) $\frac{302}{20} = 121$

(vi) $\sqrt{51} = 6$

[20 marks]

- Q.7 (c) (i) Consider a discrete-time low-pass filter whose impulse response $h[n]$ is known to be real and whose frequency response magnitude in the region $-\pi \leq \omega \leq \pi$ is given as,

$$\left| H(e^{j\omega}) \right| = \begin{cases} 1; & |\omega| \leq \frac{\pi}{3} \\ 0; & \text{otherwise} \end{cases}$$

Determine the real-valued impulse response $h[n]$ for this filter when the corresponding group-delay function is $\tau_g(\omega) = \frac{3}{2}$.

- (ii) Design a block level architecture of a 5 coefficient FIR filter by using appropriate number of multipliers, adders and registers. Assume that all the input operands are available in 4 bit, 2's complement fixed point representation. The architecture should give one output per clock cycle.

[10 + 10 marks]



- Q.8 (a) (i) Draw the block diagram of programmable peripheral interface 8255A.
 (ii) Explain BSR (Bit Set/Reset) mode of 8255A
 (iii) Write a BSR control word subroutine to set bits PC_7 and PC_3 and reset them after some delay, using the below I/O port addresses.

\overline{CS}								Hexadecimal Address	Port
A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0		
1	0	0	0	0	0	0	0	= 80H	A
1	0	0	0	0	0	0	1	= 81H	B
1	0	0	0	0	0	1	0	= 82H	C
1	0	0	0	0	0	1	1	= 83H	Control Register

[20 marks]



Q.8 (b) (i) Suppose we are given the following information about a continuous time periodic signal $x(t)$ with period 3 and Fourier series coefficients a_k :

1. $a_k = a_{k+2}$


2. $a_k = a_{-k}$

3. $\int_{-0.5}^{0.5} x(t) dt = 1$

4. $\int_{0.5}^{1.5} x(t) dt = 2$

Determine $x(t)$.

 (ii) A causal LTI system 'S' has the block diagram representation as shown in figure below.




Determine a differential equation relating the input $x(t)$ to the output $y(t)$ of this system.

[10 + 10 marks]



 Q.8 (c) Consider the state diagram of Moore machine shown below:



Get the excitation equations and Boolean equations for output Z of Mealy machine. Also design the Mealy machine using J-K flip-flop.

[20 marks]



0000

Space for Rough Work

