

Q1 a) Universal motor : $P=2$

$P_{input} = 300W$ L AC series motor. $Z = 960$

$R_a = 3.5 \Omega$; $V_t = 100V$

$N = 5000 \text{ rpm}$; $I_a = 4.6 A$.


Back emf. $E_b = \frac{PN\phi Z}{60A} \Rightarrow \phi = \frac{E_b \times 60}{N \times Z} \quad (1)$

$P_{input} = V_t I_a \cos \phi$

$[P=2=A]$

$300 = 100 \times 4.6 \times \cos \phi$

$\phi = 49.294^\circ$

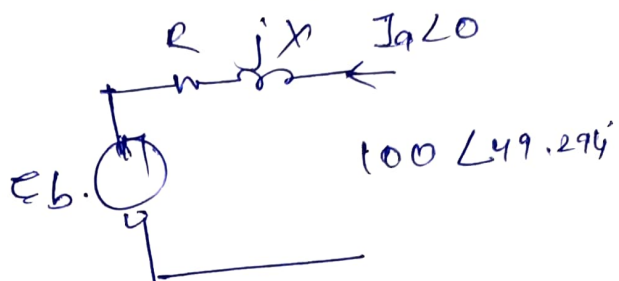

$100 \angle 49.294^\circ = I_a \angle 0 (R + jX) + E_b \angle 0$

$65.212 + j75.8 = 4.6 \times (3.5 + jX) + E_b$

$65.212 + j75.8 = 16.1 + E_b + j4.6X$

Comparing real & imag part.

$E_b = 65.212 - 16.1 = 49.112V$

$X = \frac{75.8}{4.6} = 16.478 \Omega$


Req value of emf is -

$E = \frac{1}{2} \frac{PN\phi Z}{60}$

$\phi = \frac{\sqrt{2} \times 49.112 \times 60}{5000 \times 960}$

$\phi = 0.868 \text{ mwb}$

$\Rightarrow 4 \text{ mwb}$

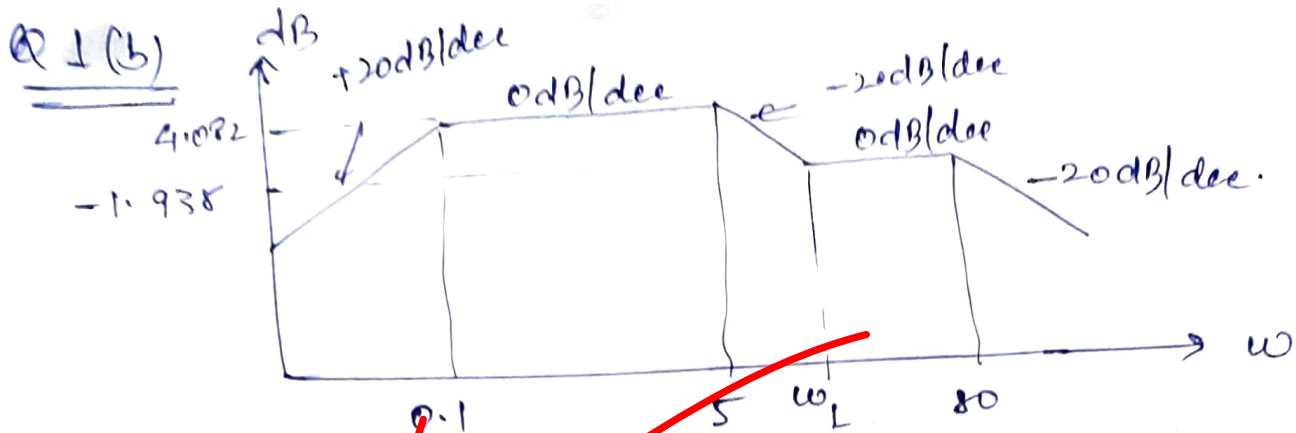

zero at: origin, w_1

poles at: $w = 0.1, 5, 80$.

$\therefore$ Let the transfer function be T.F. = $\frac{k s (\frac{s}{w_1} + 1)}{(\frac{s}{0.1} + 1)(\frac{s}{5} + 1)(\frac{s}{80} + 1)}$ -(1)

Eqn of line is given as:-
 $y = mx + c$.

$$y = 20 \log w + 20 \log k.$$

at $w = 0.1$ $y = 4.082 \text{ dB}$.

$$4.082 = 20 \log 0.1 + 20 \log k.$$

$$24.082 = 20 \log k.$$

$$k = 10^{-9992} \hat{=} 16. \quad \boxed{k = 16} \quad -(2)$$

Now to find w_1

$$\text{slope} = \frac{y_2 - y_1}{x_2 - x_1}$$

between $w = 5$ & $w = w_1$ slope = -20 dB/dec

$$-20 = \frac{-1.938 - 4.082}{\log w_1 - \log 5}.$$

$$\log w_1 - \log 5 = 0.301$$


$$w_1 = 9.9993$$

$$\boxed{w_1 \approx 10 \text{ s}} \quad (3)$$

From (1), (2) & (3)

$$T.F. = \frac{16 s \left(\frac{s}{10} + 1 \right)}{\left(\frac{s}{0.1} + 1 \right) \left(\frac{s}{5} + 1 \right) \left(\frac{s}{80} + 1 \right)}$$
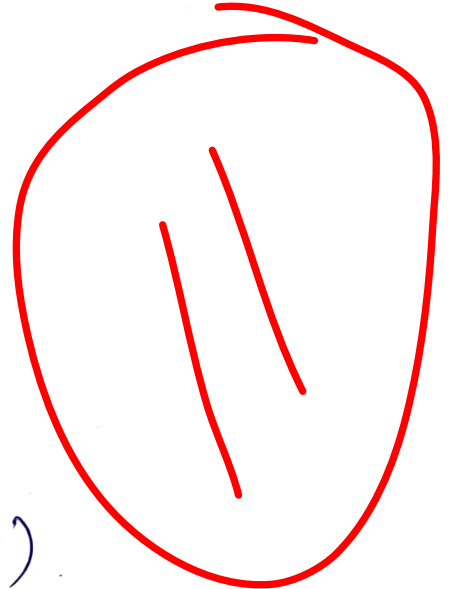
$$= \frac{16 s \frac{(s+10)}{10}}{\frac{1}{0.1 \times 5 \times 80} (s+0.1)(s+5)(s+80)}$$



$$\boxed{T.F. = \frac{64 s (s+10)}{(s+0.1)(s+5)(s+80)}} \quad \underline{\underline{= 0.25}}$$

Q.1 (c) conductor resistance

$$= 0.12 / \text{km}$$

$$= 0.12 / 10^3 \text{ m.}$$

$$= 10^{-4} \Omega / \text{m.}$$

$$\therefore R_{AB} = 60 \text{ m} \times 10^{-4} \frac{\Omega}{\text{m}}$$

$$= 6 \times 10^{-3} \Omega$$

$$R_{BC} = 80 \times 10^{-4} = 8 \times 10^{-3} \Omega ; R_{CD} = 90 \times 10^{-4} = 9 \times 10^{-3} \Omega$$

$$R_{DA} = 70 \times 10^{-4} = 7 \times 10^{-3} \Omega$$

Applying KVL in loop circuit

$$\begin{aligned} 0 &= I_1 R_{AB} + (I_1 - 100) R_{BC} + (I_1 - 170) R_{CD} + (I_1 - 220) R_{DA} \\ &= I_1 \times 6 \times 10^{-3} + (I_1 - 100) \times 8 \times 10^{-3} + (I_1 - 170) \times 9 \times 10^{-3} \\ &\quad + (I_1 - 220) \times 7 \times 10^{-3} \end{aligned}$$

$$0 = 6I_1 + 8I_1 - 800 + 9I_1 - 1530 + 7I_1 - 1540.$$

$$\boxed{I_1 = 129 \text{ A}}$$

(i). voltage at B

$$V_B = V_A - I_1 \times R_{AB}$$

$$= 240 - 129 \times 6 \times 10^{-3}$$


$$\boxed{V_B = 239.226 \text{ V}}$$

voltage at C

$$V_C = V_B - (I_1 - 100) \times R_{BC}$$

$$= 239.226 - 29 \times 8 \times 10^{-3}$$

$$\boxed{V_C = 238.994 \text{ V}}$$

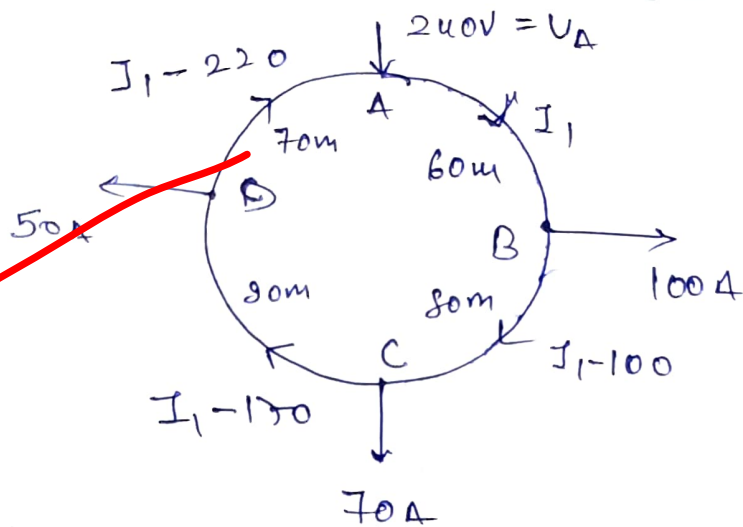

Voltage at D : $V_D = V_C - (I_1 - 170) \times 4 \times 10^{-3}$

$$= 238.994 + 41 \times 9 \times 10^{-3}$$


$$V_D = 239.363 \text{ V}$$

(ii). Interconnector resistance

$$= 100 \times 10^{-4} \Omega$$

$$R_C = 10^{-2} \Omega$$

Thevenin Equivalent at terminals A & C

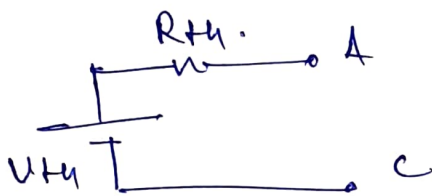

$$R_{th} = (R_{AB} + R_{BC}) \parallel (R_{CB} + R_{DA})$$


$$R_{th} = (14 \times 10^{-3}) \parallel (16 \times 10^{-3})$$

$$R_{th} = 7.466 \times 10^{-3} \Omega$$

$$V_{th} = V_A - V_C$$

$$= 240 - 238.994$$

$$= 1.006 \text{ V}$$

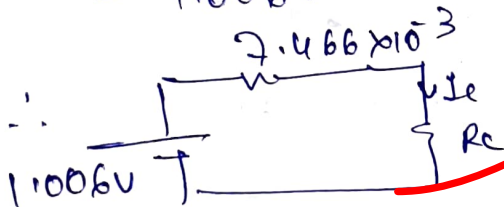

$$I_C = \frac{V_{th}}{R_{th} + R_C} = \frac{1.006}{7.466 \times 10^{-3} + 10^{-2}}$$

$$I_C = 57.597 \text{ A}$$

~~Voltage at B~~ $V_B =$

Apply KVL in loop

$$0 = I_2 \times 6 \text{ m} + (I_2 - 100) \times 8 \text{ m} + (I_2 - 112.403) \times 9 \text{ m} + (I_2 - 162.403) \times 7 \text{ m}$$

$$= 6I_2 + 8I_2 - 800 + 9I_2 - 1011.627 + 7I_2 - 1136.821$$

$$I_2 = 98.2816 \text{ A}$$

$\therefore$ Voltage at B $V_B = 240 - 98.2816 \times 6 \times 10^{-3}$

$$V_B' = 239.4103 \text{ V}$$

Voltage at C $V_C = V_B - (I_2 - 100) \times 8 \times 10^{-3}$

$$V_C' = 239.424 \text{ V}$$

Voltage at D $V_D = V_C - (I_2 - 100 + 10) \times 9 \times 10^{-3}$

$$V_D' = 239.5511 \text{ V}$$

(ii). Losses without inter connectors

$$= (129^2 \times 6 \times 10^{-3}) + (29^2 \times 8 \times 10^{-3}) + (41^2 \times 9 \times 10^{-3}) + (91^2 \times 7 \times 10^{-3})$$

$$= 179.67 \text{ W}$$

Losses with inter connectors

$$= (98.2816^2 \times 6 \times 10^{-3}) + (1.9184^2 \times 8 \times 10^{-3}) + (14.1214^2 \times 9 \times 10^{-3}) + (64.1214^2 \times 7 \times 10^{-3})$$

$$= 88.554 \text{ W}$$

$$\text{efficiency}(\eta) = \frac{\text{o/p}}{\text{i/p}} = \frac{\text{i/p} - \text{loss}}{\text{i/p}} = 1 - \frac{\text{loss}}{\text{i/p}}$$

$$\boxed{\eta \propto \text{loss}}$$

$$\therefore \text{change in efficiency} = |\Delta \eta| = \left| \frac{88.554 - 179.67}{179.67} \right| \times 100$$

$$\boxed{\Delta \eta = 50.71 \%}$$

ie. ' η ' improved by 50.71 % Av

Q.1 (d) NBFM $\phi_{FM}(t)$

i) Avg power = $8W = \frac{A_c^2}{2} \Rightarrow A_c = \sqrt{16}$
 $A_c = 4V$

$f_c = 100 \text{ kHz} = 10^5 \text{ Hz}$

(ii). $\beta = 0.5$ (iii). $s/p \text{ m(t)} = 6 \cos(300\pi t)$

$f_m = \frac{300\pi}{2\pi} = 150 \text{ Hz}$

NBFM is given as:-

$\phi_{FM}(t) = A_c \cos \left[2\pi f_c t + 2\pi K_f \int_0^t m(\tau) d\tau \right]$

$= A_c \cos \left[2\pi f_c t + 2\pi K_f \int_0^t 6 \cos 300\pi \tau d\tau \right]$

$= A_c \cos \left[2\pi f_c t + 2\pi K_f \cdot \frac{6 \sin 300\pi t}{300\pi} \right]$

$= A_c \cos \left[2\pi f_c t + \underbrace{0.04 K_f}_{\beta = 0.5} \sin 300\pi t \right]$

$\therefore K_f = \frac{0.5}{0.04} = 12.5 \text{ Hz/volt}$

$= A_c \cos [2\pi f_c t + \beta \sin 300\pi t]$

$= A_c \cos(2\pi f_c t) \cdot \cos(\beta \sin 300\pi t) - A_c \sin(2\pi f_c t) \cdot \sin(\beta \sin 300\pi t)$

for NBFM $\beta < 1$

for small θ , $\cos \theta \approx 1$
 $\sin \theta \approx \theta$

$$\therefore \phi_{FM}(t) = A_c \cos(2\pi f_c t) - A_c \sin(2\pi f_c t) (\beta \sin 300\pi t)$$

$$= A_c \cos(2\pi f_c t) - \frac{A_c \beta}{2} \cos 2\pi (f_c - f_m) t + \frac{A_c \beta}{2} \cos 2\pi (f_c + f_m) t$$

Substituting values of A_c , f_c , β , f_m in above eqⁿ.

$$\phi_{FM}(t) = 4 \cos(2\pi \times 10^5 t) - \cos 2\pi (99850 t) + \cos 2\pi (100150 t)$$

= Ans

Q1(e)

Two 6 pulse converter Bipolar HVDC-transmission
1000 MW $\pm$ 200 kV.

$$P = V \cdot I$$

crit in $\Rightarrow I = \frac{1000 \times 10^6}{400 \times 10^3} = 2500 \text{ A.}$
transmission line $= 2.5 \text{ kA.}$

$$I_{rms} = \frac{2500}{\sqrt{3}} = \cancel{1443.375} \text{ A.}$$
$$= 1443.375 \text{ A.}$$

~~peak~~ $= I$

for PIV rating, $PIV = \frac{V_{ml}}{2}.$

for $\alpha = 0.$

$$\frac{3V_{ml}}{\pi} \cos \alpha = 200 \times 10^3$$

$$V_{ml} = \frac{200 \times 10^3 \times \pi}{3} = 209.44 \text{ kV.}$$

$\therefore$ Two thyristor valves are connected.


$\therefore$ PIV of each thyristor valve $= \frac{V_{ml}}{2}$

$$= 104.719 \text{ kV}$$

$$= \underline{\underline{Ans}}$$

12

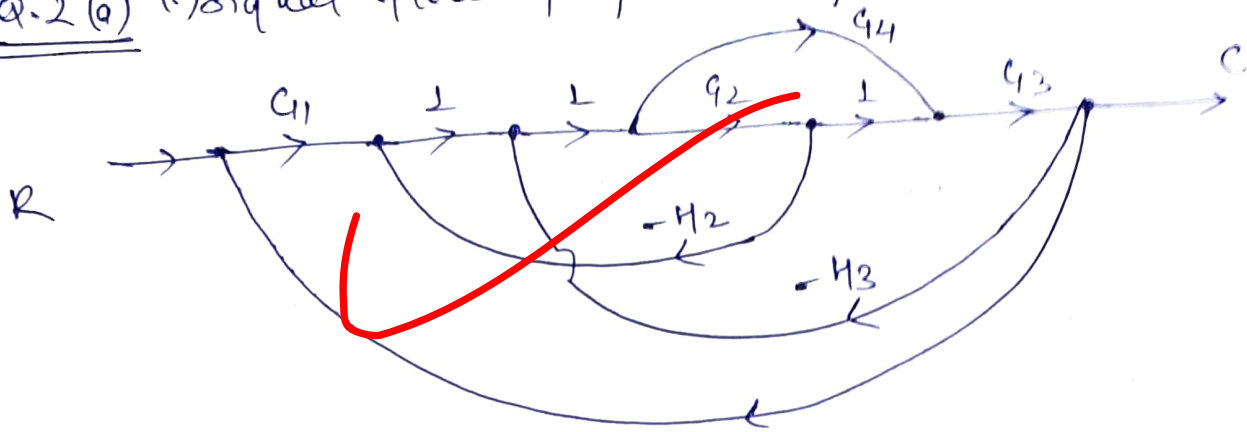Q.2(a) (1) Signal flow graph is given as:



By Mason's gain formula. -1

$$T.F = \frac{\sum P_k \cdot \Delta_k}{\Delta}$$

$$P_1 = G_1 G_2 G_3 ; P_2 = G_1 G_3 G_4$$

$$L_1 = -G_1 G_2 G_3 ; L_2 = -G_2 H_2 ; L_3 = -G_2 G_3 H_3$$

$$L_4 = -G_3 G_4 H_3 ; L_5 = -G_1 G_2 G_4$$

$$\therefore \Delta = 1 - (L_1 + L_2 + L_3 + L_4 + L_5)$$

$$\Delta_1 = 1 ; \Delta_2 = 1$$


$$\therefore T.F = \frac{G_1 G_2 G_3 + G_1 G_3 G_4}{1 + G_1 G_2 G_3 + G_2 H_2 + G_2 G_3 H_3 + G_3 G_4 H_3 + G_1 G_2 G_4}$$

$$= \frac{G_1 G_3 (G_2 + G_4)}{1 + G_1 G_2 G_3 + G_2 H_2 + G_2 G_3 H_3 + G_3 G_4 H_3 + G_1 G_2 G_4}$$

$$= \frac{G_1 G_3 (G_2 + G_4)}{1 + G_1 G_2 G_3 + G_2 H_2 + G_2 G_3 H_3 + G_3 G_4 H_3 + G_1 G_2 G_4}$$

$$= A_u$$

Q.2 (a) (i)

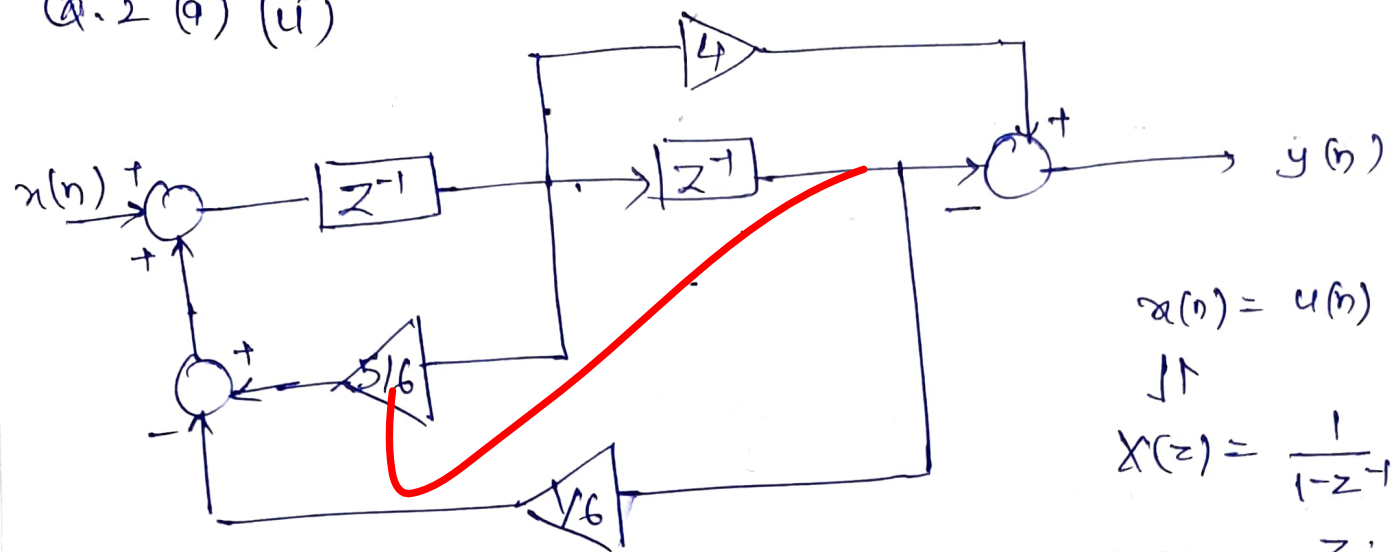

$$x(n) = u(n)$$

↓↑

$$X(z) = \frac{1}{1-z^{-1}}$$

$$X(z) = \frac{z}{z-1}$$

To obtain $\frac{Y(z)}{X(z)} = ?$

Using Mason's Gain Formula,

$$P_1 = 4z^{-1} + z^{-2} \quad P_2 = z^{-2}$$

$$L_1 = \frac{5}{6}z^{-1}, \quad L_2 = -\frac{1}{6}z^{-2}$$

$$\therefore \frac{Y(z)}{X(z)} = \frac{4z^{-1} + z^{-2}}{1 - \left(\frac{5}{6}z^{-1} - \frac{1}{6}z^{-2}\right)}$$

$$\frac{Y(z)}{X(z)} = \frac{24 \cdot 6 (4z+1)}{6z^2 - 5z + 1}$$

$$Y(z) = \frac{6(4z+1)}{6z^2 - 5z + 1} \cdot \frac{z}{(z-1)}$$

$$\frac{Y(z)}{z} = \frac{24z + 6}{(z-1)\left(z-\frac{1}{2}\right)\left(z-\frac{1}{3}\right)} \quad \text{--- (1)}$$

Very partial fraction

$$\frac{Y(z)}{z} = \frac{A}{z-1} + \frac{B}{z-1/2} + \frac{C}{z-1/3}$$

$$(24z+6) = A(z-1/2)(z-1/3) + B(z-1)(z-1/3) + C(z-1)(z-1/2)$$

Put $z=1$.	Put $z=1/2$.	Put $z=1/3$.
$30 = \frac{A}{3}$	$18 = -\frac{1}{12}B$	$14 = \frac{1}{9}C$
$A=90$	$B=-216$	$C=126$

$$\therefore Y(z) = 90 \frac{z}{z-1} - 216 \frac{z}{z-1/2} + 126 \frac{z}{z-1/3}$$

↑ Inverse Z transform.

$$y(n) = 90(1)^n u(n) - 216\left(\frac{1}{2}\right)^n u(n) + 126\left(\frac{1}{3}\right)^n u(n).$$

-(1)

Put $n=0$

$$y(0) = 90 - 216 + 126 = 0 \quad \text{Ans}$$

Put $n=\infty$

$$y(\infty) = 90 - 216 + 126 = 0 \quad \text{Ans}$$

Initial value theorem is given as -

$$y(n) \big|_{n=0} = \lim_{z \rightarrow \infty} [Y(z)] = \lim_{z \rightarrow \infty} \frac{6(4z+1) \cdot z}{(6z^2-5z+1)(z-1)}$$

$$y(0) = 0 \quad \text{Ans}$$

Final value theorem is given as -

$$y(n) \big|_{n=\infty} = \lim_{z \rightarrow 1} (1-z^{-1}) Y(z) = \lim_{z \rightarrow 1} \frac{6(4z+1)}{(6z^2-5z+1)(1-z^{-1})}$$

$$y(\infty) = 0 \quad \text{Ans}$$

$$= \lim_{z \rightarrow 1} \frac{z-1}{z} \cdot \frac{(24z+8)z}{(z-1)(z-1/2)(z-1/3)}$$

$$= \frac{24+8}{\frac{1}{2} \times \frac{2}{3}} = \underline{\underline{90}} \text{ Ans}$$

$$\boxed{y(\infty) = 90} \text{ Ans}$$

Q 2(b) PMDC motor

$$R_a = 4.2 \Omega$$

$$\text{for } V = 6V ; N = 12125 \text{ rpm} ; I_{a0} = 14.5 \text{ mA}$$

$$\text{no load ilp} = V \times I_{a0} = 6 \times 14.5 \times 10^{-3} = 0.087 \text{ W} \quad (1)$$

no load rotational loss

$$E_b = V - I_{a0} \times R_a = 6 - 14.5 \times 10^{-3} \times 4.2$$

$$E_b = 5.9391 \text{ V}$$

$$E_b = K \phi \omega_m$$

$$K \phi = \frac{5.9391}{2\pi \times \frac{12125}{60}} = 4.672 \times 10^{-3} \frac{\text{V}}{\text{r/sec}} \quad (2)$$

$$\text{Stalled condition re. } \omega_m = 0 \Rightarrow E_b = 0$$

$$\therefore I_a = \frac{V}{R_a} = \frac{6}{4.2} = 1.42857 \text{ A}$$


$$\text{Torque } T = K \phi \cdot I_a$$

$$= 4.672 \times 10^{-3} \times 1.42857$$

$$\text{Stalled torque } T = 6.6814 \times 10^{-3} \text{ N-m} \Rightarrow 4 \text{ mN}$$

$$\text{Stalled current } I_a = 1.42857 \text{ A}$$
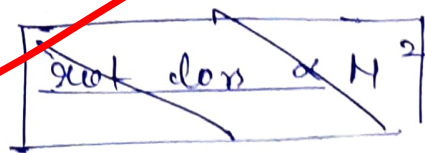
$$\text{for given ilp} = 1.6 \text{ W} = E_b \cdot I_a$$



Let N_2 be new speed

I_{a2} be new current

$$\text{new rot. loss} = P_{R2} = P_{R1} \times \left(\frac{N_2}{N_1} \right)^2$$

$$P_{R2} = 0.087 \times \left(\frac{N_2}{12125} \right)^2 \quad \text{--- (3)}$$

~~motor o/p = 1.6 - P_{R2}~~
 ~~$\geq 1.6 - 0.087 \times \left(\frac{N_2}{12125} \right)^2$~~

~~Also motor o/p $\Rightarrow E_b \cdot I_a$~~

~~$1.6 = E_b \cdot I_a \Rightarrow 1.6 = (6 - 4.2 I_a) \cdot I_a$~~

~~$1.6 = 6 I_a - 4.2 I_a^2$~~

~~on solving, $I_a = 1.073 \text{ A}$; $I_a = 0.354 \text{ A}$~~

 ~~$\downarrow$~~
~~rejected~~

~~$I_a = 0.354 \text{ A}$ Ans.~~

~~$\therefore E = 6 - 0.354 \times 4.2 = 4.5132 \text{ V}$~~

~~$\therefore \omega_2 = \frac{4.5132}{k\phi} = \frac{4.5132}{4.678 \times 10^{-3}} = 964.77 \text{ rad/s}$~~

~~$N_2 = 9212.88 \text{ rpm}$ Ans.~~

~~From eqn (3)~~

~~$P_{R2} = 0.087 \times \left(\frac{9212.88}{12125} \right)^2$~~

~~$P_{R2} = 0.05 \text{ W}$~~

~~$\eta = \frac{o/p}{i/p} = \frac{1.6 - 0.05}{6 \times 0.354} \times 100$~~

~~$\eta = 72.955\%$ Ans.~~

Q.2(c) (i). Universal Relay Torque Equation is given as:

$$T_d = K_1 I^2 + K_2 V^2 + K_3 VI \cos(\theta - \phi) - K_4$$

$K_1 I^2 \rightarrow$ Overcurrent ; $K_3 VI \cos(\theta - \phi) \rightarrow$ directional

$K_2 V^2 \rightarrow$ over voltage ; $K_4 \rightarrow$ spring restraining torque

$T_d \rightarrow$ deflecting torque

3 distance relays are :

1. Impedance Relay: (Voltage Restraint Overcurrent Relay)

$$T_d = K_1 I^2 - K_2 V^2$$


(i) for trip condition $T_d > 0$
i.e. $K_1 I^2 - K_2 V^2 > 0$.

$$\sqrt{\frac{K_1}{K_2}} > \frac{V}{I}$$

Here $\frac{V}{I} = Z_f$ (fault impedance)

& $\sqrt{\frac{K_1}{K_2}} = Z_L$ (line impedance).

$\therefore$ trip condition. $Z_f < Z_L$

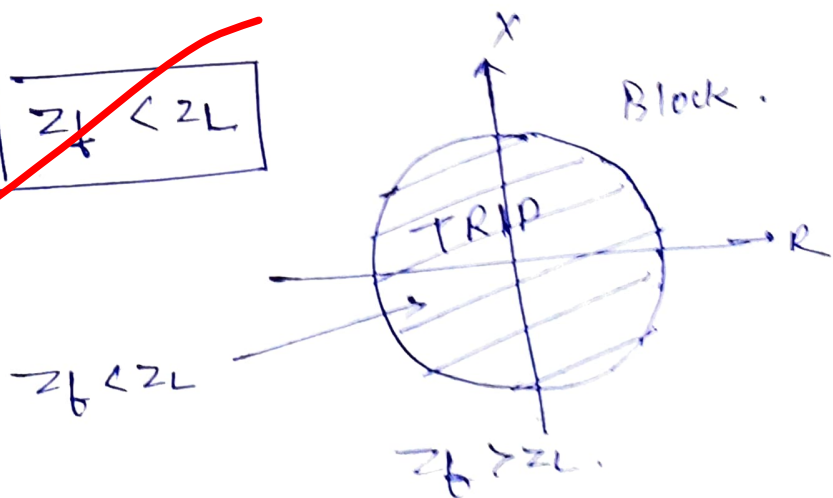

2. Mho / Admittance Relay: (Voltage restrained) (directional relay)


$$T_d = K_3 V I \cos(\theta - \alpha) - K_2 V^2$$

for trip condition: $T_d > 0$

$$K_3 V I \cos(\theta - \alpha) - K_2 V^2 > 0$$

$$\frac{K_3}{K_2} \cos(\theta - \alpha) > \frac{V}{I}$$
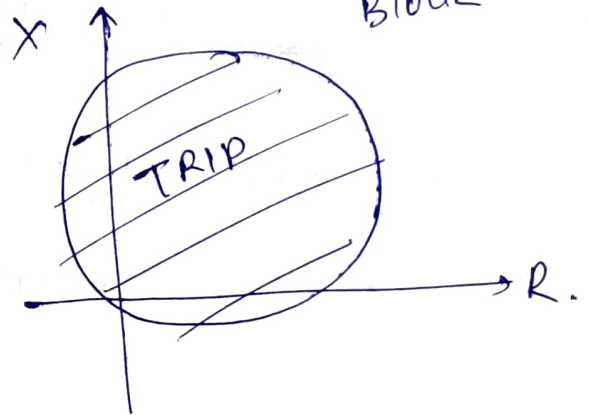
$$\frac{V}{I} = Z_f \quad ; \quad \frac{K_3}{K_2} \cos(\theta - \alpha) = Z_f$$



3. Reactance Relay:

(Directional restraint) (overcurrent relay)

$$T_d = K_1 I^2 - K_3 V I \cos(\theta - \alpha)$$

for trip condition $T_d > 0$


$$\text{ie. } K_1 I^2 - K_3 V I \cos(\theta - \alpha) > 0$$

$$\frac{K_1}{K_3} > \frac{V}{I} \cos(\theta - \alpha)$$

$$\text{for } \alpha = 90^\circ \Rightarrow \frac{K_1}{K_3} > Z_{\text{line}}$$

$$\Rightarrow \frac{K_1}{K_3} > X_f$$

$$\frac{K_1}{K_3} = X_f$$

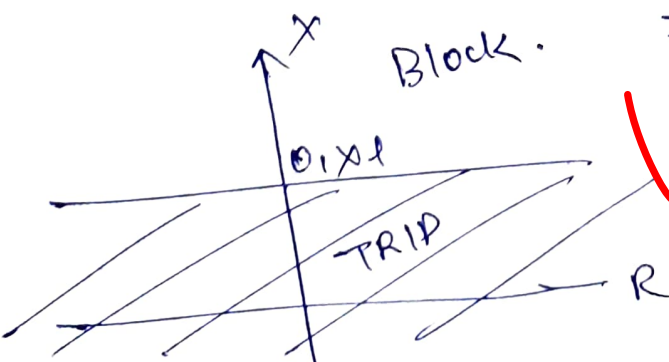

Q2c (ii). $V = 10 \text{ kV}$; $R_n = 10 \Omega$

out of balance current = 1.8 A

1. % of winding unprotected $\% W_u = \frac{I_n R_n}{V_{ph}} \times 100$

$$\% W_u = \frac{1.8 \times \frac{1000}{5} \times 10}{\frac{10 \times 10^3}{\sqrt{3}}} \times 100 = 62.3538\%$$

1. $\therefore$ % of winding protected = $100 - \% W_u$
 $= 37.6461\%$ Ans.

2. Let R_n be the value of resistance required to protect 80% of winding.

$\therefore$ % of winding unprotected = 20%.


$$\therefore 20\% = \frac{1.8 \times \frac{1000}{5} \times R_n}{\frac{10 \times 10^3}{\sqrt{3}}} \times 100$$

on solving

$$R_n = 3.2075 \Omega = R_n$$

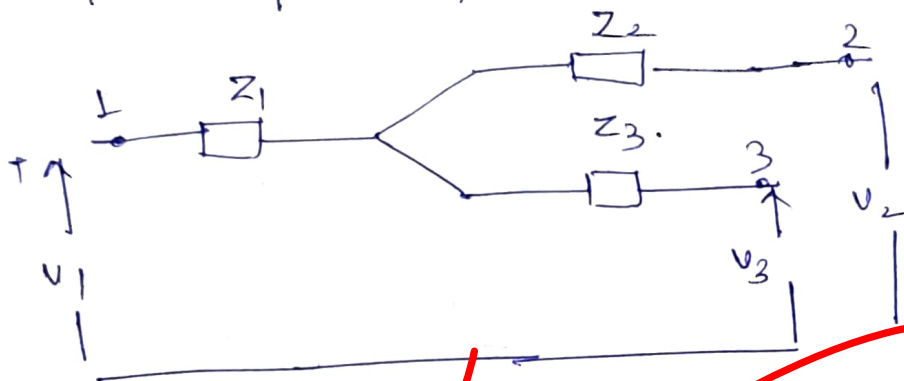- Q3(a) (a). 1° : 6.35 kV, 5 MVA
 2° : 1.91 kV, 2.5 MVA
 3° : 400 V, 2.5 MVA.

Eq. ckt. of 3 wdg. X_{mes} can be represented as:



$$\left. \begin{aligned} Z_{12} &= Z_1 + Z_2 \\ Z_{13} &= Z_1 + Z_3 \\ Z_{23} &= Z_2 + Z_3 \end{aligned} \right\} \text{--- (A)}$$

$$\text{(B)} \quad \left\{ \begin{aligned} Z_1 &= \frac{1}{2} (Z_{12} + Z_{13} - Z_{23}) \\ Z_2 &= \frac{1}{2} (Z_{12} + Z_{23} - Z_{13}) \\ Z_3 &= \frac{1}{2} (Z_{13} + Z_{23} - Z_{12}) \end{aligned} \right.$$

Z_{12} = SC impedance of wdg 1 & 2 with 3° open.

Z_{23} = SC impedance of wdg 2° & 3° with 1° open

Z_{13} = SC impedance of wdg 1° & 3° with 2° open

Let $S_B = 5 \text{ MVA}$

$$\therefore Z_{12} = \frac{500}{393.7} = 1.27 \Omega.$$

$$Z_{12}(\text{pu}) = 1.27 \times \frac{5}{(6.35)^2} = 0.15748 \text{ pu.}$$

$$\boxed{Z_{12}(\text{pu}) = 0.15748 \text{ pu}}$$

$$Z_{13} = \frac{900}{393.7} \times \frac{2.5}{6.35^2} = 0.14173 \text{ pu on own base}$$

on 5 MVA base $Z_{13} = 0.14173 \times \frac{5}{2.5} = 0.28346 \text{ pu}$

$$\boxed{Z_{13}(\text{pu}) = 0.28346 \text{ pu}}$$

$$Z_{23} = \frac{231}{1308.9} \times \frac{2.5}{1.91^2} \times \frac{5}{2.5} = 0.24013 \text{ pu.}$$

$$\boxed{Z_{23} = 0.24013 \text{ pu.}}$$

(i). $Z_{12} = 0.15748$; $Z_{13} = 0.2834$ pu; $Z_{23} = 0.2418$ pu
 Using eqn (B)

(ii). $\therefore Z_1 = \frac{1}{2} (0.15748 + 0.2834 - 0.2418) = 0.09954$ pu

$Z_2 = \frac{1}{2} (0.15748 + 0.2418 - 0.2834) = 0.05794$ pu

$Z_3 = \frac{1}{2} (0.2834 + 0.2418 - 0.15748) = 0.18386$ pu.


(ii) 3rd short circuit of 3rd terminals. i.e. $V_3 = 0$.

$\therefore I_{sc} = \frac{V_1}{Z_1 + Z_3} = \frac{1}{Z_{13}} = \frac{1}{0.2834} = 3.5285$ pu

1st short-circuit current

$I_{sc1} = 3.5285 \times \frac{5 \times 10^6}{6.35 \times 10^3}$

$I_{sc1} \approx 2778.41$ A

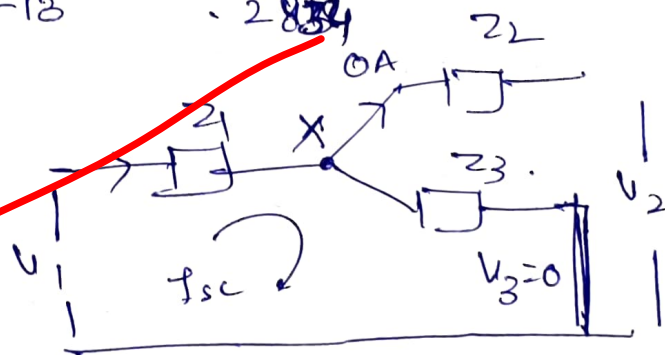

3rd short ckt current

$I_{sc3} = 3.5285 \times \frac{5 \times 10^6}{400/\sqrt{3}} = 76.394$ KA.

Voltage at 2nd terminal = $I_{sc} \times Z_3$


$= 3.5285 \times 0.18386$

$= 0.64875$ pu.

$= 0.64875 \times \frac{1.91 \times 10^3}{\sqrt{3}}$

$= 2.116$ KV
 $= P_m$

Q.2(b) (i)

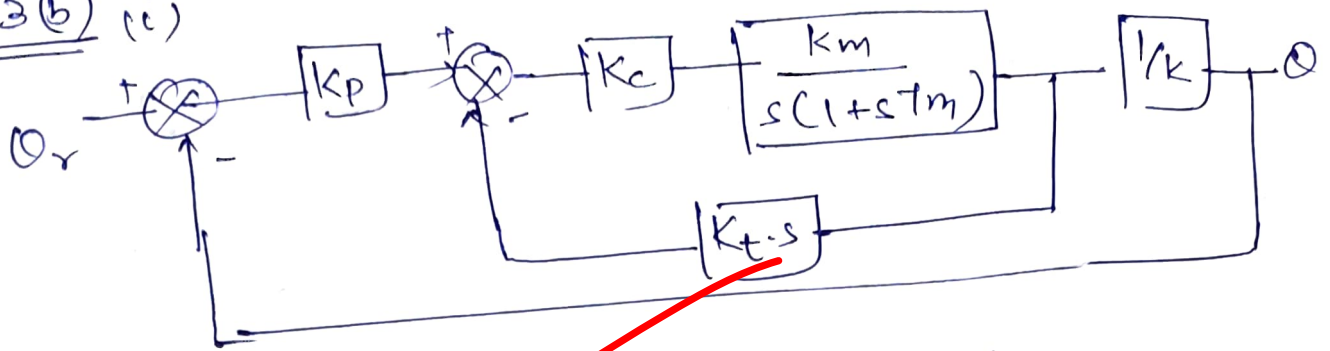

Using Mason's gain formula to find T.F.

$$T.F = \frac{\sum P_k \Delta_k}{\Delta} \quad P_1 = \frac{K_p \cdot K_c \cdot K_m}{K_s (1+sT_m)}$$

$$L_1 = -\frac{K_c K_m \cdot K_t \cdot s}{s(1+sT_m)} = -\frac{K_c K_m K_t}{(1+sT_m)}$$

$$L_2 = -\frac{K_p \cdot K_c \cdot K_m}{K_s (1+sT_m)}$$

$$\therefore T.F = \frac{K_p K_c K_m}{K_s (1+sT_m)}$$


$$1 + \frac{K_c K_m K_t}{1+sT_m} + \frac{K_p K_c K_m}{K_s (1+sT_m)}$$

$$T.F_1 = \frac{\frac{K_p K_c K_m}{K}}{s(1+sT_m)}$$

-(1)

$$1 + \left[\frac{K_c K_m K_t}{(1+sT_m)} + \frac{K_p K_c K_m}{K_s (1+sT_m)} \right]$$

or comparing with. 2nd T.F. is -

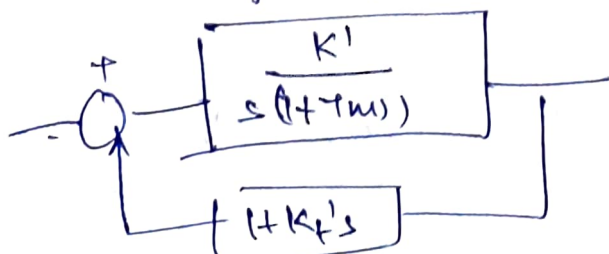

$$\Rightarrow T.F_2 = \frac{\frac{K'}{s(1+T_m)}}{1 + \frac{K' K_t}{(1+T_m s)} + \frac{K'}{s(1+T_m)}} \quad -(2)$$

On comparing eqn (1) & (2)

$$1 \quad \boxed{K' = \frac{K_p K_c K_m}{K}}$$

$$= A_m$$

$$s. K_c K_m K_t = K' K_t$$

$$K_c K_m K_t = \frac{K_p K_c K_m}{K} \cdot K_t$$

$$\boxed{K_t' = K \cdot K_t} = A_m$$

(ii) ~~OLTF~~ ^{num} / ^{deno} - num.

$$OLTF = \frac{\frac{K'}{s(1+Tms)}}{1 + \frac{K' \cdot K_t'}{(1+Tms)}} = \frac{K'}{s[1 + Tms + K'K_t']}$$

It is Type 1 system

$$\therefore K_v = \lim_{s \rightarrow 0} s G(s) = \lim_{s \rightarrow 0} \frac{K'}{s(1 + Tms + K'K_t')}$$

$$\boxed{K_v = \frac{K'}{1 + K'K_t'}} = \infty$$

(iii) 3.

$$ess \text{ with feedback} = e_s = \frac{1}{K_v}$$

$$\boxed{e_s = \frac{1 + K'K_t'}{K}}$$

for without feedback put $K_t' = 0$.

$$\therefore OLTF = \frac{K'}{s(1 + Tms)}$$

$$e_s = \frac{1}{K_v} = \lim_{s \rightarrow 0} \frac{1}{s \frac{K'}{s(1 + Tms)}} = \frac{1}{K'} \quad \boxed{e_s = 1/K'}$$


With the addition of feedback e_n ^{has increased}

e_n with feedback = $\frac{1}{K'} + K_f'$

e_n without feedback = $\frac{1}{K'} = \infty$

Q.3 (b) (ii)

$K=2$
 $a=6$

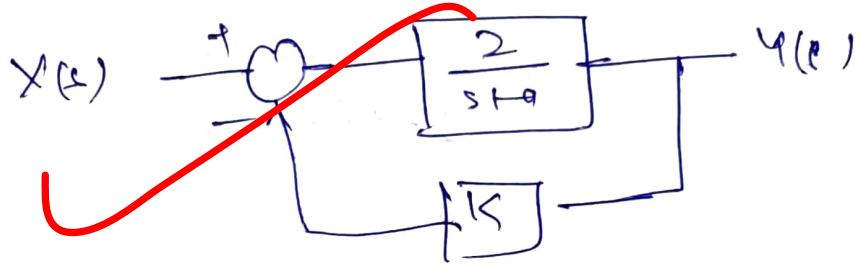

Sensitivity is given as : $S_K^T = \frac{\partial T/T}{\partial K/K}$

$T = T.F. = \frac{\frac{2}{s+a}}{1 + \frac{2K}{s+a}} = \frac{2}{s+a+2K}$

Sensitivity wrt. 'a' is $S_a^T = \frac{\partial T/T}{\partial a/a} = \frac{T}{a} \frac{\partial a}{\partial T}$

$S_a^T = \frac{\frac{a}{2}}{\frac{2}{s+a+2K}} \cdot \frac{0 - 2 \cdot 1}{(s+a+2K)^2} = \frac{-a}{(s+a+2K)}$

$S_a^T \Big|_{w=2} = \frac{-6}{2j + -6 + 2 \times 2}$

put $s=j\omega$
 $s=2j$

$|S_a^T| = 2.121 = \underline{A_u}$

Sensitivity wrt K is $S_{T_K} = \frac{\partial T / T}{\partial K / K} = -\frac{K}{T} \cdot \frac{\partial T}{\partial K}$

$$= \frac{\frac{K}{2}}{s + a + 2K} \cdot \frac{0 - 2 \cdot 2}{(s + a + 2K)^2} = \frac{-2K}{(s + a + 2K)^2}$$

$$S_{T_K} \Big|_{s=2} = \frac{-2 \times 2}{j^2 + 6 + 2 \times 2}$$

$$|S_{T_K}| = 0.3922 = \underline{\underline{A_m}}$$

18

Q.3 a)

	Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	D_2	D_1	D_0
1	0	0	1	0	1	1	0	1	1
3	0	1	1	1	0	0	1	0	0
4	1	0	0	1	1	1	1	1	1
7	1	1	1	1	1	0	1	1	0
6	1	1	0	1	0	1	1	0	1
5	1	0	1	0	1	0	0	1	0
2	0	1	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0	1

Excitation table of D FF is

Q	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

$$D_2 = \sum m(3, 4, 6, 7)$$

$$D_1 = \sum m(1, 4, 5, 7)$$

$$D_0 = \sum m(0, 1, 4, 6)$$

K-map for D_2

$Q_2 \backslash Q_1 Q_0$	$\bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$Q_1 \bar{Q}_0$	$Q_1 Q_0$
$\bar{Q}_2$			1 (3)	
Q_2	1 (4)		1 (6)	1 (7)

$$D_2 = Q_1 Q_0 + Q_2 \bar{Q}_0$$

K-map for D_1

$Q_2 \backslash Q_1 Q_0$	$\bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$Q_1 \bar{Q}_0$	$Q_1 Q_0$
$\bar{Q}_2$			1 (3)	
Q_2	1 (4)	1 (5)	1 (7)	


$$D_1 = \bar{Q}_1 Q_0 + Q_2 \bar{Q}_1 + Q_2 Q_0$$

K-map for D_0

$Q_2 \backslash Q_1 Q_0$	$\bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$Q_1 \bar{Q}_0$	$Q_1 Q_0$
$\bar{Q}_2$	1	1	0	0
Q_2	1	0	0	1

$$D_0 = \bar{Q}_2 Q_1 + Q_2 \bar{Q}_0$$

Circuit Implementation.

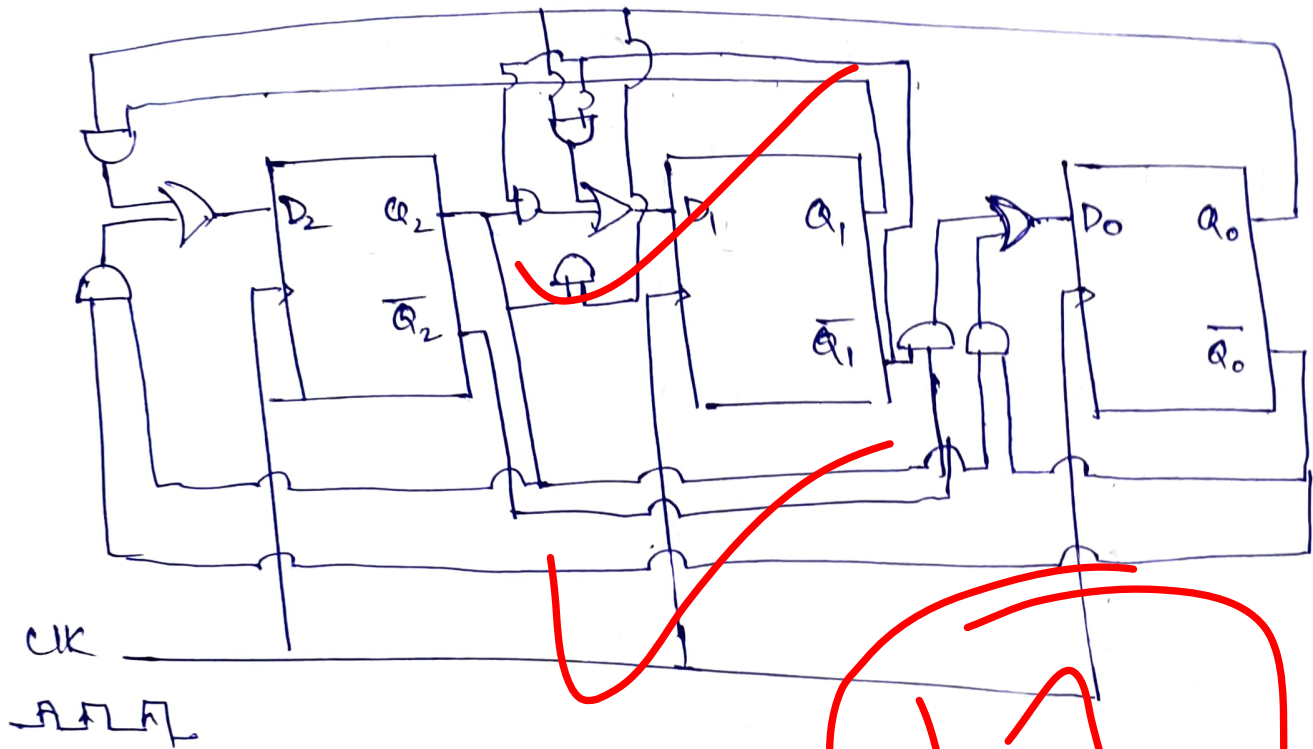

Q4(a) (i). 132 kV , 50 Hz , $X_L = 4 \Omega$; $C = 0.031 \text{ nF}$.

$$P_f = 0.5$$

$$L = \frac{4}{2\pi \times 50}$$

1. $f_{\text{res}} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{\frac{4}{2\pi \times 50} \times 0.031 \times 10^{-6}}}$

$$f_{\text{res}} = 8010.953 \text{ Hz}$$

2. Restriking voltage is given as-

$$\text{TRV} = K_1 K_2 K_3 V_m \sin\left(1 - \cos \frac{t}{\sqrt{LC}}\right)$$

$$K_1 = 1 \text{ (grounded fault)}$$

$$K_2 = 0.95 \text{ (given)}$$

$$K_3 = \sin\phi \text{ (power factor)}$$

$$= \sin(\cos^{-1} 0.5) = \frac{\sqrt{3}}{2}$$

$$\text{max TRV} = K_1 K_2 K_3 \times 2V_m$$

$$= 1 \times 0.95 \times \frac{\sqrt{3}}{2} \times 2 \times \frac{132 \times 10^3}{\sqrt{3}} \times \sqrt{2}$$

$$= 177.342 \text{ kV} \\ = \text{Ans.}$$

3. max value of RRRV

$$= K_1 K_2 K_3 \cdot \frac{V_m}{\sqrt{LC}}$$

$$= 1 \times 0.95 \times \frac{\sqrt{3}}{2} \times \frac{1}{\sqrt{\frac{4}{2\pi \times 50} \times 0.031 \times 10^{-6}}} \times \frac{132 \times 10^3}{\sqrt{3}} \times \sqrt{2}$$


$$\text{RRRV}|_{\text{max}} = 4.463 \text{ kV/\mu sec.}$$

$$\begin{aligned}
 4. \text{ Avg. RRRV} &= \frac{2 K_1 K_2 K_3 V_m}{\pi \sqrt{LC}} \\
 &= \frac{2 \times 1 \times 0.95 \times \frac{\sqrt{3}}{2} \times \frac{34 \times 10^3 \times \sqrt{2}}{15}}{\pi \times \sqrt{\frac{4}{2\pi \times 50} \times 0.031 \times 10^{-6}}} \\
 &= 2.841 \text{ kV / } \underline{\underline{\mu\text{sec. On}}}
 \end{aligned}$$

Q.4 (a). (ii) given CB rating: 1500 A, 2000 MVA, 33 kV,

1. Rated normal current $I_N = 1500 \text{ A}$
2. Breaking current $I_{BK \text{ on}} = \frac{2000 \times 10^6}{\sqrt{3} \times 33 \times 10^3}$
 $I_{BK \text{ on}} = 34.99 \text{ kA.}$
3. Making current $I_{mk} = 2.55 \times I_{BK \text{ on}}$
 $= 89.226 \text{ kA.}$
4. Short time rating current.
 Here $\frac{I_{BK}}{I_N} = \frac{34.99 \times 10^3}{1500} = 23.32 < 40$
 $\therefore \text{Short time rating current} = \underline{\underline{3 \text{ sec. On}}}$



Q.4(a). (iii) 3 core cable.

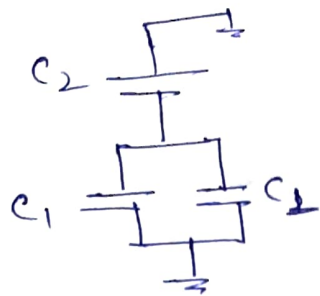

$$C_b = C_2 + 2C_1 \quad (1)$$

$$C_b = 0.4 \text{ MF/km.}$$

$$0.4 = C_2 + 2C_1.$$

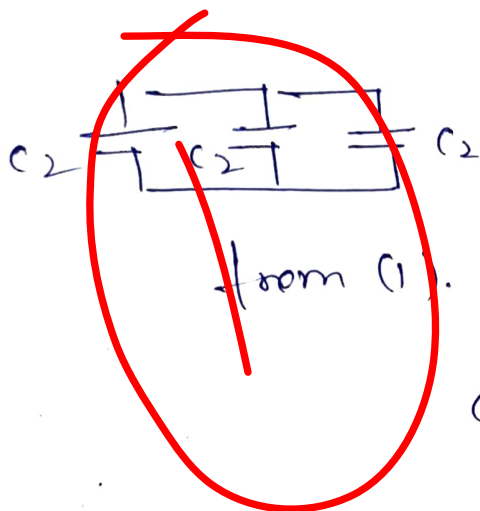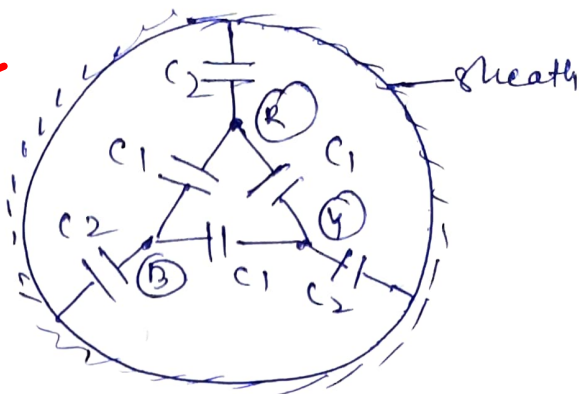

from (1).

$$C_a = 3C_2 \quad (2)$$

$$C_a = 0.625 \text{ MF/km}$$

$$C_2 = \frac{C_a}{3}$$

$$C_2 = \frac{0.625}{3}$$

$$= 0.20833 \text{ MF}$$

$$C_b = \frac{C_a}{2} + 2C_1$$

$$C_1 = \frac{3C_b - C_a}{2} = 0.2175 \text{ MF}$$

1. Capacitance between two conductors, C_{ph}


$$C_{ph} = 3C_1 + C_2$$

$$= 3 \times \frac{3C_b - C_a}{2} + \frac{C_a}{3}$$

$$C_{ph} = \frac{9C_b - C_a}{6}$$

$$= \frac{9 \times 0.4 - 0.625}{6}$$

$$C_{ph} = 0.49583 \text{ MF}$$

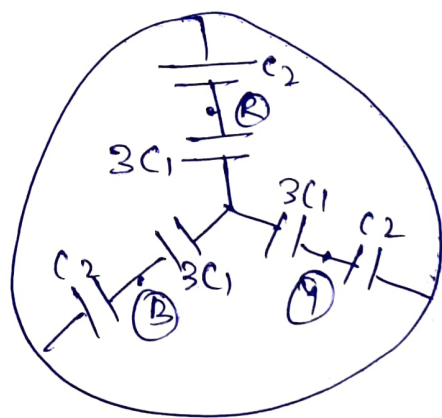


2. Capacitance between two bunched conductors & third conductor

$$C = 2C_1 + C_2$$

$$= 2 \times 0.2175 + 0.20833$$

$$C = 0.7833 \text{ MF} = A_{m1}$$

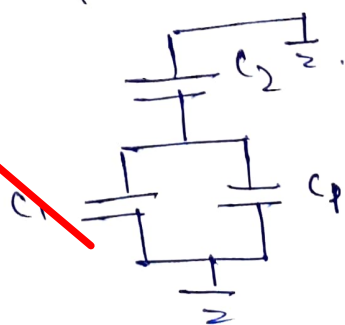

$$3. \quad I_c = \frac{V_{ph}}{X_c}$$

$$I_c = V_{ph} \cdot \omega C_{ph}$$

$$I_c = \frac{10 \times 10^3}{\sqrt{3}} \times 2\pi \times 50 \times 0.49583 \times 10^{-6}$$

$$I_c = 0.899 \text{ A} = I_{rms}$$



Q. 4(b)

Analog filter. $H_a(s) = \frac{5}{s^2 + 6s + 5}$

(i). digital filter using Bilinear z-transform

put $s = \frac{2}{T} \left(\frac{1-z^{-1}}{1+z^{-1}} \right)$

$$T = \frac{1}{fs} = \frac{1}{12}$$

$$H_a(s) = \frac{5}{s^2 + 6s + 5} = \frac{5}{(s+1)(s+5)}$$

$\downarrow$ $s = \frac{2}{T} \left(\frac{1-z^{-1}}{1+z^{-1}} \right)$ $\frac{1}{T} = 12$

$$H_a(z) = \frac{5}{\left[24 \left(\frac{1-z^{-1}}{1+z^{-1}} \right) + 1 \right] \left[24 \left(\frac{1-z^{-1}}{1+z^{-1}} \right) + 5 \right]}$$

$$= \frac{5 (1+z^{-1})^2}{(24 - 24z^{-1} + 1 + z^{-1})(24 - 24z^{-1} + 5 + 5z^{-1})}$$

$$= \frac{5 (z^{-2} + 2z^{-1} + 1)}{(25 - 23z^{-1})(29 - 21z^{-1})}$$

$$H_a(z) = \frac{5z^{-2} + 10z^{-1} + 5}{725 - 1192z^{-1} + 483z^{-2}} \quad \underline{\underline{\text{Ans}}}$$

Q. 4. (c) (i) $\Delta \phi$ VSI. $V_s = 450V$
 $R = 10\Omega$

Case 1 180° mode

o/p voltage is given as $V_L = V_s \sqrt{3}$

per phase o/p voltage = $V_L/\sqrt{3} = \frac{V_s \sqrt{3}}{3}$

1. RMS value of load current = $\frac{V_s \frac{\sqrt{3}}{3}}{R}$
 $= \frac{450 \times \frac{\sqrt{3}}{3}}{10} = 21.2132 A$

2. RMS value of thyristor current = $I_{T_{rms}} = \frac{21.2132}{\sqrt{3}}$

$= 15 A$ Ans
3. Load power = $3 \times I_{os}^2 R$
 $= 3 \times 21.2132^2 \times 10 = 13.5 kW$ Ans

Case 2: 120° mode

o/p voltage is given as $V_L = V_s/\sqrt{2}$

per phase o/p voltage = $V_L/\sqrt{3} = V_s/\sqrt{6}$

1. RMS value of load current = $\frac{V_s/\sqrt{6}}{R} = \frac{450/\sqrt{6}}{10}$
 $= 18.371 A$

2. RMS value of thyristor current = $\frac{18.371}{\sqrt{2}}$
 $= 12.99 A$

$$\begin{aligned}\text{Load power } P &= 3 \times I_{\text{or}}^2 \times R \\ &= 3 \times 18.3211^2 \times 10 \\ &= 101125 \text{ W} \\ &= \text{Ans.}\end{aligned}$$

Q. 4. (c) ii 3 ϕ , 3 pulse M-3 converter
3 ϕ supply: 230V, 50Hz $R = 10 \Omega$.

$$V_o = \frac{1}{2} V_{om}.$$

for 1 ϕ load for $\alpha \leq 30^\circ$ (assumed)

$$V_o = \frac{3V_{mL}}{2\pi} \cos \alpha.$$

$$\frac{1}{2} V_{om} = V_{om} \cos \alpha.$$

$$\cos \alpha = \frac{1}{2}$$

$\Rightarrow \alpha = 60^\circ \leftarrow$ This makes our assumption wrong.

$\therefore \alpha$ must be greater than ~~30~~ 30°

$$\therefore \text{for } \alpha > 30^\circ \quad V_o = \frac{3V_{mp}}{2\pi} \left[1 + \cos \left(\alpha + \frac{\pi}{6} \right) \right]$$

$$\frac{0.5 \times 3V_{mL}}{2\pi} = \frac{3V_{mp}}{2\pi} (1 + \cos(\alpha + 30^\circ))$$

$$0.5 \times 3 \times 230\sqrt{2} = 3 \times \frac{230\sqrt{2}}{\sqrt{3}} [1 + \cos(\alpha + 30^\circ)].$$

$$\boxed{\alpha = 67.6993^\circ}$$

$$\text{avg. load current } I_0 = \frac{V_0}{R} = \frac{0.5 \times \frac{3V_{mL}}{2\pi}}{10}$$

$$= \frac{0.5 \times 3 \times 230\sqrt{2}}{2\pi \times 10}$$

$$\boxed{I_0 = 7.765 \text{ A}}$$

$$\text{rms value of load current } I_{or} = \frac{V_{orm}}{R}$$

$$V_{orm} = \frac{V_{mL}}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin \left(2\alpha + \frac{\pi}{3} \right) \right]^{1/2}$$

$$= \frac{230\sqrt{2}}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - 67.7 \times \frac{\pi}{180} \right) + \frac{1}{2} \sin (2 \times 67.7 + 80) \right]^{1/2}$$

$$V_{orm} = 104.764 \text{ V}$$

$$\therefore I_{orm} = \frac{104.764}{10} = 10.4764 \text{ A}$$


$$\therefore \eta = \frac{o/p}{i/p} = \frac{V_0 \cdot I_0}{V_{or} \cdot I_{or}} = \frac{77.965 \times 7.765}{104.764 \times 10.4764} \times 100$$

$$= 54.93\%$$

Ans



Q5(b)

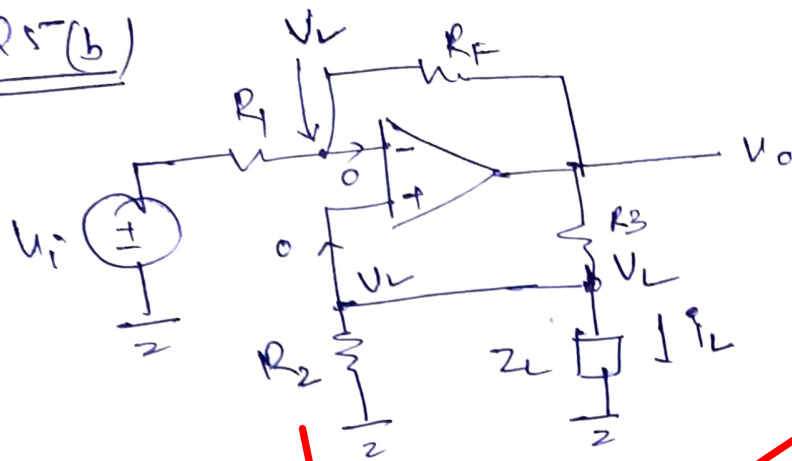

from ckt

$$I_L = \frac{V_L}{Z_L}$$

from concept of virtual ground.

$$V^- = V^+ = V_L$$

KCL at inverting terminal.

$$\frac{V_L - V_i}{R_1} + \frac{V_L - V_o}{R_F} = 0$$

$$V_L \left(\frac{1}{R_1} + \frac{1}{R_F} \right) - \frac{V_i}{R_1} - \frac{V_o}{R_F} = 0$$

Also $V_L = \frac{R_2 \parallel Z_L}{R_2 \parallel Z_L + R_3} \cdot V_o = \frac{\frac{R_2 Z_L}{R_2 + Z_L}}{\frac{R_2 Z_L}{R_2 + Z_L} + R_3} \times V_o$

$$V_L = \frac{R_2 Z_L}{R_2 Z_L + R_2 R_3 + R_3 Z_L} \times V_o$$


$$V_L = \frac{R_2 Z_L}{Z_L (R_2 + R_3) + R_2 R_3} \times V_o \quad \text{--- (1)}$$

KCL at node V_L .

$$\frac{V_o - V_L}{R_3} = \frac{V_L}{Z_L} + \frac{V_L}{R_2}$$

$$\frac{V_o}{R_3} = V_L \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{Z_L} \right)$$
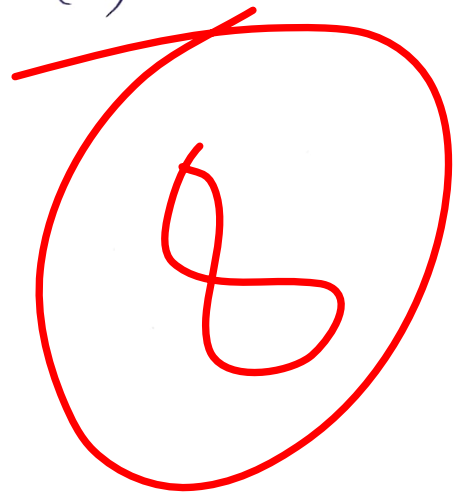
$$V_0 = V_L \cdot R_3 \left[\frac{(R_3 + R_2)Z_L + R_2 R_3}{R_2 R_3 Z_L} \right] \quad -(2)$$





Put eqⁿ (2) in (1)

$$V_L = \frac{R_2 Z_L}{(R_2 + R_3)Z_L + R_2 R_3} V_L$$

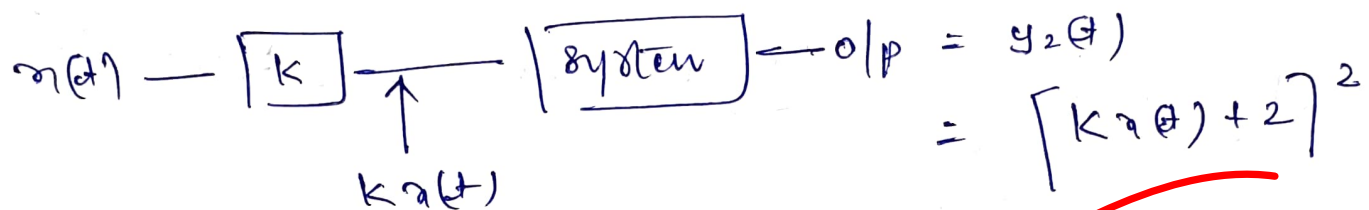
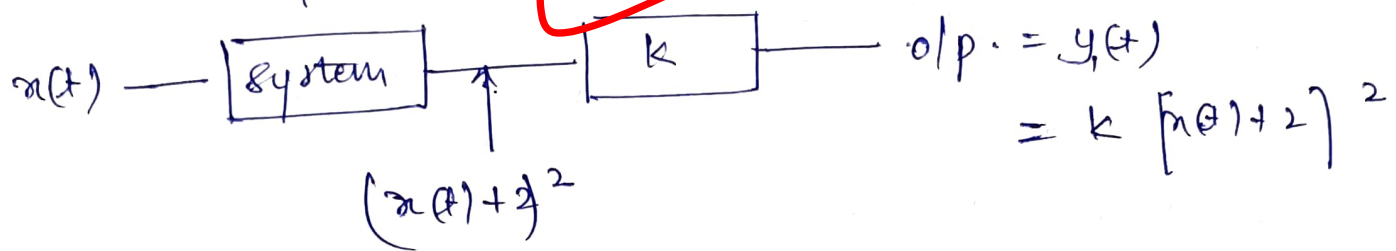
Q.5(c) (i). $T[f(x)] = y(x) = [2(x) + 2]^2$

System is causal $\therefore$ it doesn't depend on any future value.



$y_1(t) \neq y_2(t)$.

$\therefore$ non-linear.

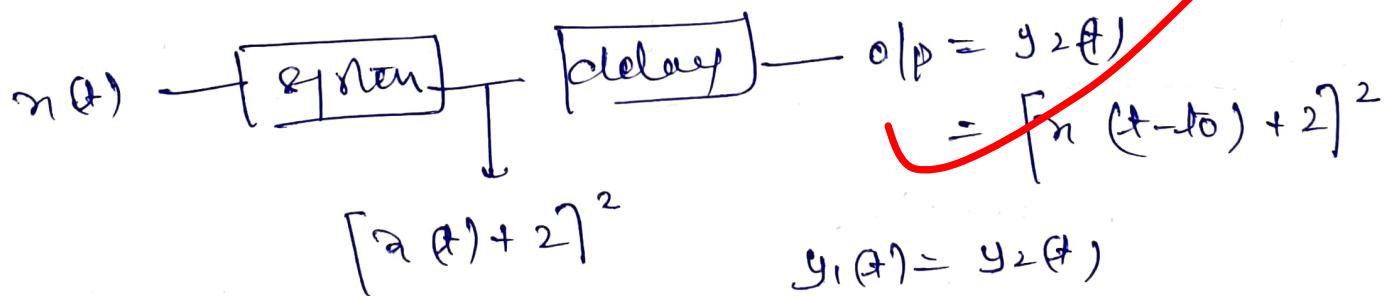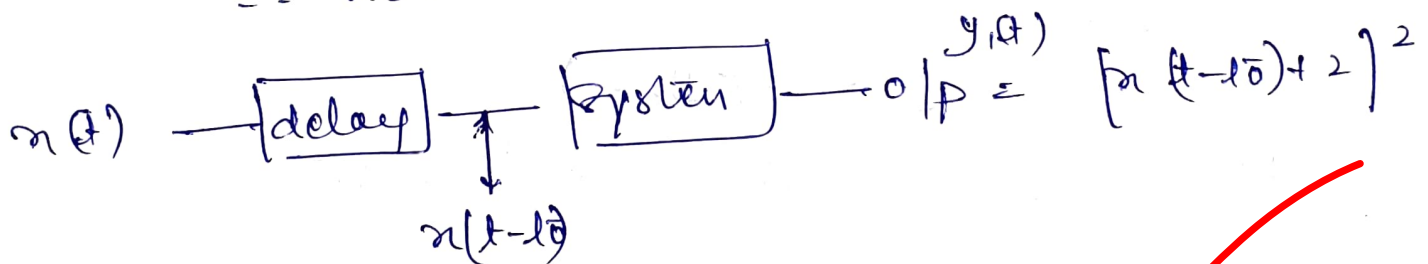

$y_1(t) = y_2(t)$

$\therefore$ System is Time invariant.

Hence System is Causal, non-linear & Time invariant.
= An.



(i). $y(t) = x(t^2 + t) + 2$.

Put $t = -2$ (say)

$$y(-2) = x[(-2)^2 - 2] + 2$$

$$y(-2) = x(2) + 2$$

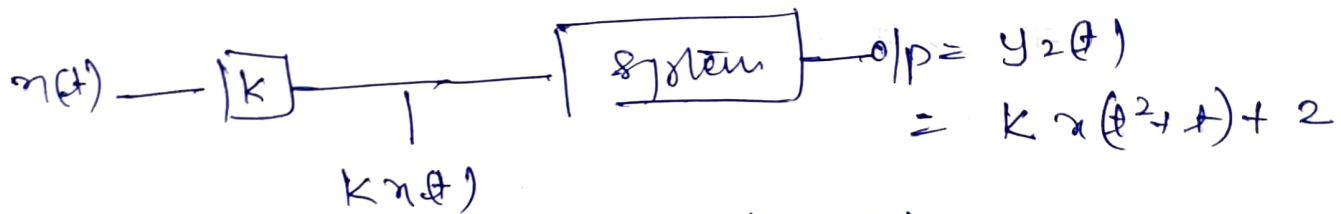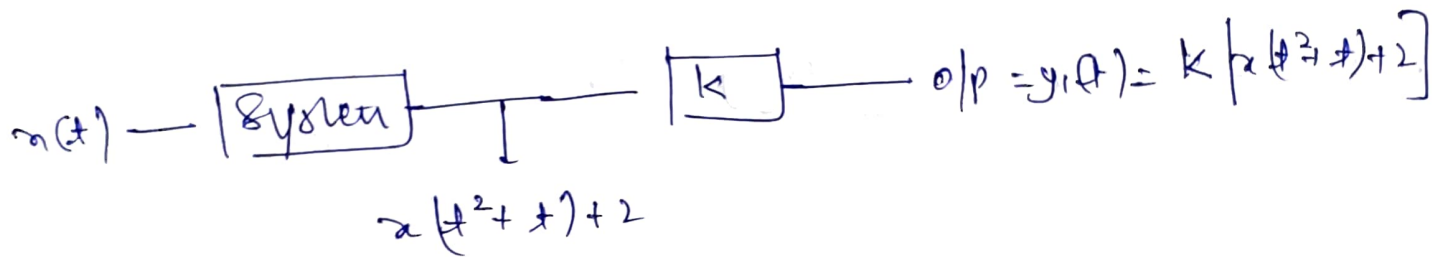Here o/p depend on future value of i/p
 $\therefore$ non casual



$$y_1(t) \neq y_2(t)$$

Hence system is non-linear.



$$y_1(t) = y_2(t)$$

System is time-invariant.

Hence system is: Non-casual, non-linear, time-invariant.

Q 5(a) 3 ϕ , 400 kVA, 800 Hz Sync gen.

$$N = 300 \text{ rpm}$$

$$V_t = 3300 \text{ V}$$

$$300 = \frac{120 \times 50}{P}$$

$$\boxed{P = 20}$$

$$\text{Slots} = 180$$

$$\text{Total no of conductors} = 180 \times 8 = 1440 \text{ conductors}$$

Peak mmf for a P pole m/c is -

$$F_m = \frac{4\sqrt{2}}{\pi} \times \frac{I}{P} \times K_w \cdot N \quad \text{ATs/pole.}$$

$$I = \frac{400 \times 10^3}{\sqrt{3} \times 3300} = 69.981 \text{ A.}$$

$$N = \text{no of turn/ph} = \frac{1440}{2 \times 3} = 240 \text{ turn/ph.}$$

$$K_w = \frac{\sin \frac{m\beta}{2}}{m \sin \beta/2}$$

$$m = \frac{180}{20 \times 3} = 3.$$

$$\beta = \frac{180^\circ}{180/20} = 20^\circ$$

$$= \frac{\sin \frac{3 \times 20}{2}}{3 \times \sin \frac{20}{2}} = 0.9598$$

$$\therefore F_m = \frac{4\sqrt{2}}{\pi} \times \frac{69.981}{20} \times 0.9598 \times 240$$


$$F_m = 1451.333 \text{ ATs/pole}$$

$$\begin{aligned} \text{Resulting mmf} &= 1.5 \times F_m \\ &= 2177 \text{ ATs/pole} \end{aligned}$$

Q.5 (e) Multiple pulse modulation:

Im MPM PWM,
multiple pulses are
obtained in the
o/p voltage waveform.

$$V_{0x} = V_k \sqrt{\frac{2d}{\pi}}$$

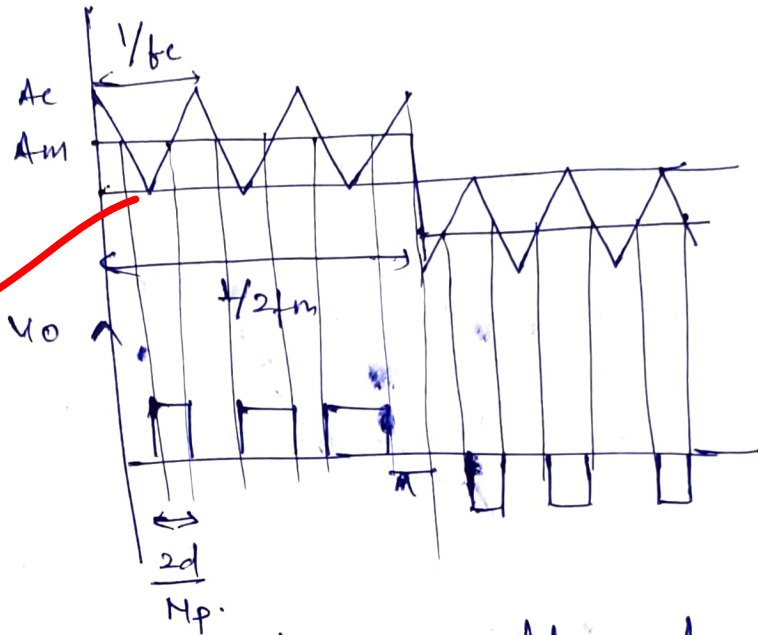


$N_c = \frac{f_c}{2f_m} \leftarrow$ This gives ^{N_p} no. of pulses obtained.

~~$$\frac{\Sigma d}{Np} = \frac{A_m}{A_c} \cdot \frac{\pi}{4p}$$~~ ← this gives pulse width.

The o/p voltage waveform is Odd Half Wave Symmetry.

$$\therefore a_0 = 0$$
$$b_n = 0.$$

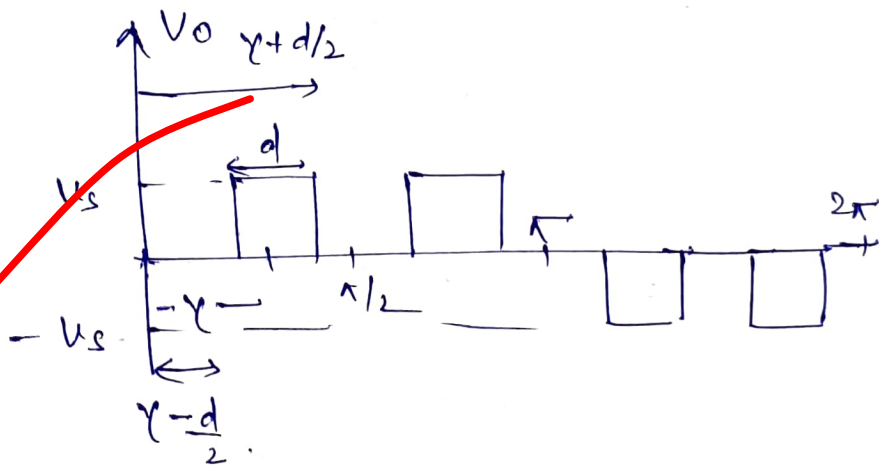

$$b_n = \frac{2}{\pi/2} \int_{\gamma-d/2}^{\gamma+d/2} V_s \sin n\omega t \, dx$$

$$= \frac{4}{\pi} V_s \left[-\frac{\cos n\omega t}{n} \right]_{\gamma-d/2}^{\gamma+d/2}$$


$$= \frac{4V_s}{\pi} \left[\cos n(\gamma - d/2) - \cos n(\gamma + d/2) \right]$$

$$b_n = \frac{8V_s}{\pi} \sin n\gamma \cdot \sin n\frac{d}{2}$$

$$\therefore \text{o/p voltage } V_o = \sum_{n=1,3,5}^{\infty} b_n \sin n\omega t$$

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{8V_s}{\pi} \sin n\gamma \cdot \sin n\frac{d}{2} \sin n\omega t$$

$$\gamma = \theta_1 + \theta_2$$

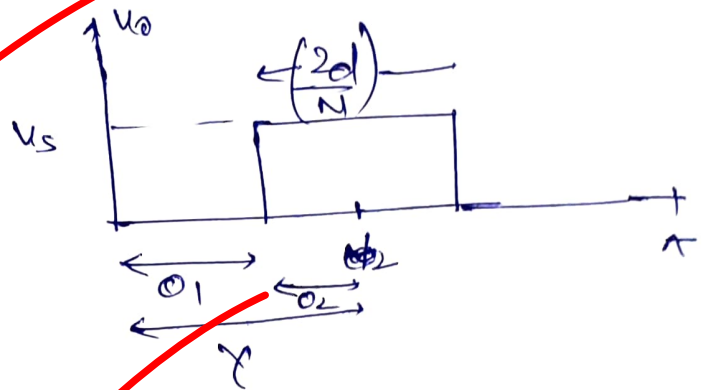

Let 'N' be no of pulses.

$$\therefore (N+1)\theta_1 = \pi - 2d$$

$$\theta_1 = \frac{\pi - 2d}{N+1}$$

$$\theta_2 = \frac{2d/N}{2}$$

$$\theta_2 = \frac{d}{N}$$

$$\therefore \gamma = \theta_1 + \theta_2 = \frac{\pi - 2d}{N+1} + \frac{d}{N}$$

