

**MADE EASY**

India's Best Institute for IES, GATE &amp; PSUs

**Delhi | Noida | Bhopal | Hyderabad | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna****Web:** www.madeeasy.in | **E-mail:** info@madeeasy.in | **Ph:** 011-45124612**CLASS TEST  
2019-2020****COMPUTER SCIENCE & IT****Date of Test : 11/09/2019****ANSWER KEY ➤ Digital Logic**

- |        |         |         |         |         |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (c)  | 13. (d) | 19. (d) | 25. (d) |
| 2. (a) | 8. (c)  | 14. (b) | 20. (c) | 26. (c) |
| 3. (b) | 9. (c)  | 15. (b) | 21. (d) | 27. (b) |
| 4. (d) | 10. (a) | 16. (a) | 22. (c) | 28. (b) |
| 5. (b) | 11. (a) | 17. (d) | 23. (c) | 29. (b) |
| 6. (c) | 12. (c) | 18. (c) | 24. (b) | 30. (b) |

## DETAILED EXPLANATIONS

### 1. (b)

For every combination of  $x, y, z$  the function value remains same for input  $\bar{x}, \bar{y}, \bar{z}$ .

x	y	z	$f(x, y, z) = f(\bar{x}, \bar{y}, \bar{z})$
0	0	0	either 0 or 1
1	0	1	
0	0	1	either 0 or 1
1	0	0	
0	1	0	either 0 or 1
1	1	1	
0	1	1	either 0 or 1
1	1	0	

Effectively there are only four rows for the truth table of the function  $f(x, y, z)$ .

$\therefore$  Total Boolean expressions possible is  $2^4 = 16$ .

### 2. (a)

$$\begin{aligned}
 (135)_x + (144)_x &= (323)_x \\
 \Rightarrow (x^2 + 3x + 5) + (x^2 + 4x + 4) &= 3x^2 + 2x + 3 \\
 \Rightarrow x^2 - 5x - 6 &= 0 \\
 \Rightarrow (x - 6)(x + 1) &= 0 \\
 \Rightarrow x &= 6 \quad [\because \text{base of a number cannot be -ve}]
 \end{aligned}$$

### 3. (b)

Let initial  $Q_1 = Q_0 = 0$

$J_0$	$K_0$	$J_1$	$K_1$	$Q_1$	$Q_0$
				0	0
1	1	0	1	0	1
1	1	1	1	1	0
0	1	0	1	0	0

It is a mod-3 counter ( $00 \rightarrow 01 \rightarrow 10 \rightarrow 00$ )

So,  $K = 3$


### 4. (d)

$$37 = 16 \times 2 + 5$$

After 37 clock pulses, the state of MOD-16 DOWN counter will be five states below the present state.

$$\begin{array}{r}
 0110(6) \\
 -0101(-5) \\
 \hline
 0001
 \end{array}$$

5. (b)

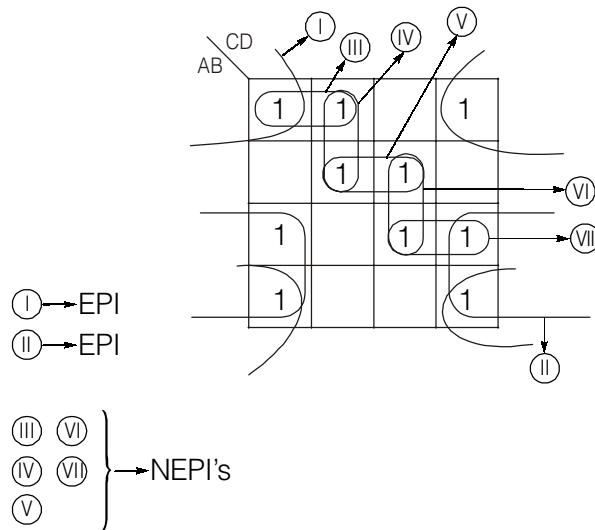


EPI = Essential Prime Implicant [which cover a minterm not covered by any other term]

NEPI = Non Essential Prime Implicant. Number of EPI's = 2, number of NEPI's = 5.

6. (c)

$$f = \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} = \bar{A}\bar{B}(C + \bar{C}) = \bar{A}\bar{B}$$

with  $2 \times 1$  multiplexer

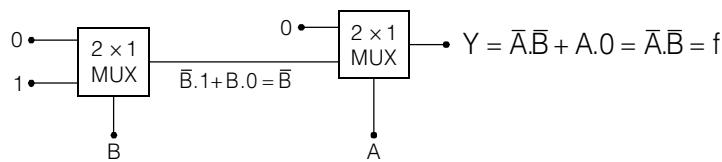

7. (c)

Range of signed 1's compliment number is  $-2^{n-1} + 1$  to  $2^{n-1} - 1$ .

8. (c)

$$\begin{aligned} (AB + B\bar{C} + \bar{A}C)(A + C) &= AB + AB\bar{C} + ABC + \bar{A}C \\ &= AB(1 + \bar{C} + C) + \bar{A}C \\ &= AB + \bar{A}C \end{aligned}$$

9. (c)

Multiplexer is a combinational circuit, converts parallel to serial data and it selects one of the several inputs and transmits to a single output.

10. (a)

$$\begin{aligned} (x \oplus y) &= \bar{x}y + x\bar{y} \\ &= \overline{xy + \bar{x}\bar{y}} \\ &= \overline{0 + \bar{x}\bar{y}} \quad (\text{as } xy = 0) \\ &= (x + y) \end{aligned}$$

11. (a)

$$(36)_7 = 7 \times 3 + 6 = (27)_{10}$$

$$(67)_8 = 8 \times 6 + 7 = (55)_{10}$$

$$(98)_{10} = 9 \times 10 + 8 = (98)_{10}$$


$$(34)_5 = 3 \times 5 + 4 = (19)_{10}$$

$$\therefore 27 + 55 + 98 + 19 = (199)_{10}$$

$$\begin{array}{r} 9|199\ 1 \\ 9\boxed{22}\ 4 \\ \hline 2 \end{array} \Rightarrow (199)_{10} = (241)_9 = 241$$

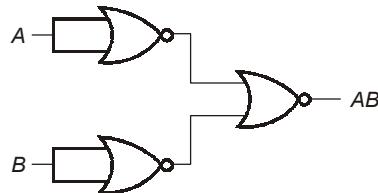12. (c)

$$\begin{aligned} f &= \overline{\bar{A} + \overline{B + \bar{C}(\overline{AB} + A\bar{C})}} \\ &= A \cdot \left[ B + \bar{C}(\overline{AB} + A\bar{C}) \right] && [\text{Demorgan's Law}] \\ &= A \cdot \left[ B + \bar{C}(\overline{AB} \cdot \overline{AC}) \right] && [\text{Demorgan's Law}] \\ &= A \cdot \left[ B + \bar{C}(\bar{A} + \bar{B})(\bar{A} + C) \right] && [\text{Demorgan's Law}] \\ &= A[B + \bar{C}(\bar{A} + \bar{B}C)] && [\text{Distributive property}] \\ &= A[B + \bar{A}\bar{C}] = AB + A\bar{A}\bar{C} \\ &= AB \text{ (AND gate to be implemented)} \end{aligned}$$



$\Rightarrow$  Minimum number of NOR gate required = 3

13. (d)

Clock	D	$Q_D$	T	$Q_T$
-	0	0	1	1
1	1	0	1	0
2	1	1	0	1
3	1	1	0	1
4	1	1	0	1

The circuit will be locked up in the state '11'. So state of circuit after 7 clock pulses is '11'.

14. (b)

$$\begin{aligned} T &\geq 3 \times 50 \text{ n sec} \\ T &\geq 150 \text{ n sec} \\ T_{\min} &= 150 \text{ nsec} \\ f_{\max} &= \frac{1 \times 10^9}{150} = 6.67 \text{ MHz} \end{aligned}$$

15. (b)

Total AND gates for a n-bit carry look ahead generator is  $1 + 2 + 3 + \dots + n = \frac{n(n+1)}{2}$

$$\text{Here } n = 5 \Rightarrow \frac{5(5+1)}{2} = 5 \times 3 = 15$$

16. (a)


Let us consider active high input

X \ YZ	00	01	11	10
0	0	1	1	0
1	0	1	0	1


$$\begin{aligned} F &= \Sigma(1, 3, 5, 6) = \Pi(0, 2, 4, 7) \\ &= (Y + Z) \cdot (X + Z) \cdot (\bar{X} + \bar{Y} + \bar{Z}) \end{aligned}$$

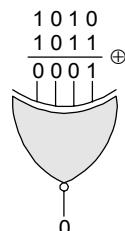17. (d)

In EX-NOR gate, if odd number of inputs are 1 then output is zero.



18. (c)

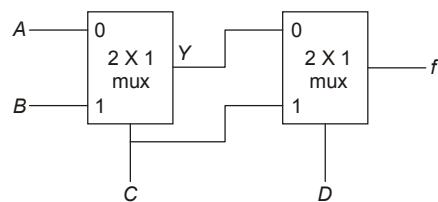

$$Y = A\bar{C} + BC$$

$$f = Y\bar{D} + CD$$

$$f = (A\bar{C} + BC)\bar{D} + CD = A\bar{C}\bar{D} + BCD + CD$$

$$\begin{aligned}
 &= A(B + \bar{B})\bar{C}\bar{D} + (A + \bar{A})C\bar{B}C\bar{D} + C\bar{D}(A + \bar{A})(B + \bar{B}) \\
 &= AB\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + ABC\bar{D} + \bar{A}BC\bar{D} + ABCD + A\bar{B}CD + \bar{A}BCD + \bar{A}\bar{B}CD \\
 f(A, B, C, D) = \Sigma m(3, 6, 7, 8, 11, 12, 14, 15)
 \end{aligned}$$

A Karnaugh map for four variables (A, B, C, D). The columns are labeled AB and the rows are labeled CD. The minterms are marked as follows:

		1	
		1	1
1		1	1
1		1	

19. (d)

$$\begin{aligned}
 f_1(A, B, C) &= \Sigma(2, 3, 4) \\
 f_2(A, B, C) &= \pi(0, 1, 3, 6, 7) = \Sigma(2, 4, 5)
 \end{aligned}$$

For function  $f$  to be zero:

$$\begin{aligned}
 f_3(A, B, C) &= \overline{[f_1(A, B, C) \cap f_2(A, B, C)]} \\
 &= \Sigma(0, 1, 3, 5, 6, 7)
 \end{aligned}$$

Maximum minterms possible are 6.

20. (c)

$$\begin{aligned}
 \text{Number of level-1 MUX} &= \frac{4}{2} = 2 \\
 \Rightarrow \text{Number of level-2 MUX} &= \frac{2}{2} = 1 \\
 \therefore \text{Total MUX required} &= 3
 \end{aligned}$$

21. (d)

$$\begin{array}{cccc}
 A = & a_2 & a_1 & a_0 \\
 B = & & b_1 & b_0 \\
 A \times B = & \overline{a_2b_0} & a_1b_0 & a_0b_0 \\
 & b_1a_2 & b_1a_1 & b_1a_0 \\
 \hline
 & b_1a_2 & (a_2b_0 + a_1b_1) & (a_1b_0 + b_1a_0) & a_0b_0 \\
 & C_3 & C_2 & C_1 & C_0
 \end{array}$$


Number of AND gates required  $X = 6$

Number of one bit full adders required  $Y = 3$

$$X + Y = 6 + 3 = 9$$

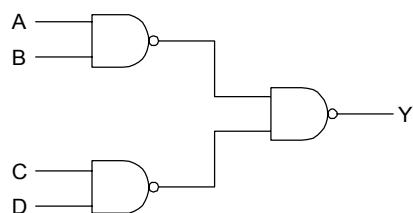22. (c)

$$Y = AB + CD = \overline{\overline{A}}\overline{\overline{B}} + \overline{\overline{C}}\overline{\overline{D}}$$



23. (c)

Let the base of the system is B

$$9 \times 8 \times 5 = (190)_B$$

$$(360)_{10} = (190)_B$$

$$360 = B^2 + 9B + 0$$

$$B^2 + 9B - 360 = 0$$

$$B = 15, \quad B = -24$$

Since base can not be negative.

$$\Rightarrow \text{Base } B = 15$$

24. (b)

$$\text{Decimal input} = 92$$


$$\text{BCD} = 10010010$$

$$\text{Output of Gray code converter} = 11011011$$

$$Y_0 \text{ corresponds to } I_m \text{ with } (S_n, \dots, S_0) \text{ is } = (11011011)_2$$

$$m = 219$$

25. (d)

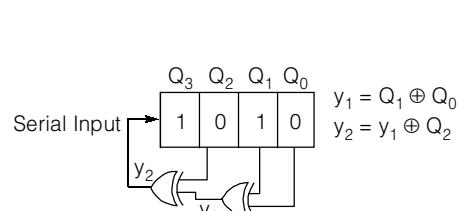

CLK pulse	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
1	0	1	0	0
2	1	1	0	1
3	2	0	1	0
4	3	0	0	1
5	4	0	0	0
6	5	1	0	0
7	6	0	1	0
	7	1	0	1

$$Q_3(t+1) = Q_0(t) \oplus Q_1(t) \oplus Q_2(t)$$

26. (c)

Consider characteristic equation of J-K Flip-Flop:  $Q_{2N+1} = J\bar{Q}_{2N} + \bar{K}Q_{2N}$

$$J = \bar{Q}_0; K = 1 \Rightarrow Q_{2N+1} = \bar{Q}_0 \bar{Q}_{2N} \quad \dots\dots(i)$$

$$\text{if } Q_0 = 1 \Rightarrow Q_{2N+1} = 0$$

$$\text{if } Q_0 = 0 \Rightarrow Q_{2N+1} = \bar{Q}_{2N}$$

Consider characteristic equation of D – Flip-Flop:  $Q_{N+1} = D$


$$Q_{N+1} = Q_2 \quad \dots\dots(ii)$$

Consider characteristic equation of T – Flip-Flop:  $Q_{N+1} = T \oplus Q_N$

$$Q_{N+1} = Q_1 \oplus Q_0 \quad \dots\dots(iii)$$

Using equations (i), (ii) and (iii)

Present State			Next State		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	1	0	1
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	0	1	0

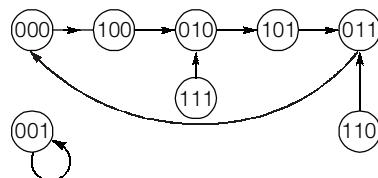

The number of used states = 5

$\therefore$  Modulus value of the counter = 5

27. (b)

$$A = (EC)_{16} \rightarrow (1032)_6$$

$$B = (20)_{10} \rightarrow (32)_6$$

$$C = (15)_8 \rightarrow (21)_6$$

$$S = A + B + C \quad \text{(add in base-6 and convert into base-10)}$$

$$= (1085)_{10}$$

## 28. (b)


To obtain a JK flip-flop from a T flip-flop, we first construct the characteristic table of JK flip-flop; and then obtain the excitation values for the T flip-flop as shown below:

J	K	$Q_n$	$Q_{n+1}$	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

Characteristic table of JK flip flop      Excitation values for T flip-flop

Now, assuming T to be an output, we solve it in terms of J, K,  $Q_n$  inputs. This gives the definition of the logic to be applied on the T input.

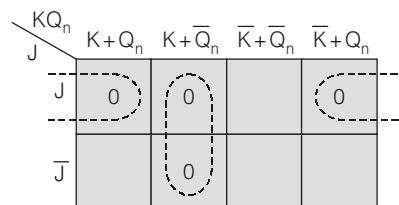Also, observing the given options, we solve for T using a maxterms map instead of using a minterms map, as shown below:



$$T = (J + Q_n) \cdot (K + \bar{Q}_n)$$

The circuit corresponding to this expression is given option (b).

## 29. (b)

$$F = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

$$F = \bar{A}C(\bar{B} + B) + A\bar{C}(\bar{B} + B)$$

$$F = \bar{A}C + A\bar{C}$$

$$F = A \oplus C$$

## 30. (b)

$$D_1 = Q_0, D_0 = Q_0 \odot Q_1$$

$$\Rightarrow (Q_1 Q_0) 00 \rightarrow 01 \rightarrow 10 \rightarrow 00 \rightarrow 01 \dots$$

