

**MADE EASY**

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | **E-mail:** info@madeeasy.in | **Ph:** 011-45124612

ANALOG CIRCUIT

ELECTRONICS ENGINEERING

Date of Test : 30/07/2025**ANSWER KEY ➤**

1. (c)	7. (c)	13. (c)	19. (a)	25. (b)
2. (d)	8. (c)	14. (a)	20. (d)	26. (d)
3. (a)	9. (c)	15. (c)	21. (c)	27. (c)
4. (b)	10. (d)	16. (c)	22. (c)	28. (d)
5. (c)	11. (c)	17. (a)	23. (d)	29. (b)
6. (a)	12. (b)	18. (a)	24. (c)	30. (d)

Detailed Explanations

1. (c)

The diode circuit is a two level clipper and the positive cycle is saturated at 8 V. Thus, diode D_1 will start conducting for $V_i > 8$ V. Thus V_1 should be -8 V. Similarly V_2 should be -6 V.

2. (d)

$$g_m = \frac{I_C}{V_{Th}} = \frac{0.5}{0.025} = 20 \text{ mA/V}$$

The value of

$$\begin{aligned} A_V &= g_m R_C \\ &= 20 \times 10^{-3} \times 7.5 \times 10^3 \\ &= 150 \text{ V/V} \end{aligned}$$

3. (a)

For $I_{in} > 0$, D_1 will be ON and $V_{out} = I_{in} R_1$.

For $I_{in} < 0$, D_2 will be ON and all the current will flow through D_2 . Since there will be no current flowing through resistance R_1 , thus $V_{out} = 0$.

4. (b)

$$I_D \propto \frac{(W)}{(L)}$$

$$\therefore \frac{I_{D1}}{I_{D2}} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2} = 2$$

and

$$r_o \propto \frac{1}{I_D}$$

$$\therefore \left(\frac{I_{D1}}{I_{D2}}\right) = \left(\frac{r_{o2}}{r_{o1}}\right) = 2$$

$$\therefore \frac{r_{o1}}{r_{o2}} = 0.5$$

5. (c)

Since the op-amp is connected in the negative feedback configuration. Thus, the concept of virtual ground will be applicable.

Thus,

$$V^+ = V^- = 0 \text{ V}$$

$$\therefore I_D = \frac{0 - (-10)}{20 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$\begin{aligned} \therefore V_o &= 10 - (10 \times 10^3) \times (0.5 \times 10^{-3}) \\ &= 10 - 5 = 5 \text{ V} \end{aligned}$$

6. (a)

$$T_{ON} = 0.693(R_a + R_b)C$$

To achieve 50% duty cycle, diode is connected across resistor R_b so that during the charging of the capacitor, R_b is bypassed and hence,

$$T_{ON} = 0.693 R_a C$$

$$T_{OFF} = 0.693 (R_b C)$$

In case of 50% duty cycle frequency = $\frac{1}{0.693(2RC)}$

Assuming $R_a = R_b = R$. Therefore,

$$20 \text{ k} = \frac{1}{0.693 \times 2 \times R \times C}$$

$$RC = 36 \times 10^{-6}$$


if $C = 1 \text{ nF}$, $R = 36 \text{ k}\Omega$

RC obtained will match our requirement.

Thus, option a is correct.

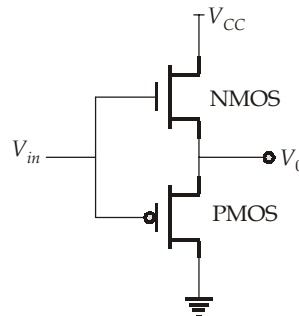7. (c)

If NMOS and PMOS of a CMOS inverter are interchanged, the circuit is:



If $V_{in} < V_{T'}$ NMOS is OFF and PMOS is ON and output is low.

If $V_{in} > V_{T'}$ NMOS is ON and PMOS is OFF and output is high.

Therefore, the circuit works as a buffer with weak levels.

8. (c)

We know, for CE BJT $\begin{cases} V_i = V_{BE} \\ V_o = V_{CE} \end{cases}$

↓

In saturation, $V_{CE} \rightarrow (V_{CE})_{sat}$

$I_{CE} \rightarrow (I_{CE})_{sat} \rightarrow \text{Constant}$

$\Delta I_C = 0$

$$I_E = I_B + I_C \rightarrow (\text{Universal})$$

↓

$$I_E = I_B + (I_C)_{sat} [\text{in saturation}]$$

$$\Delta I_E = \Delta I_B$$


In saturation, only I_C saturates.

9. (c)

The reverse saturation doubles for every 10° rise in temperature, thus disturbing the Q-point.

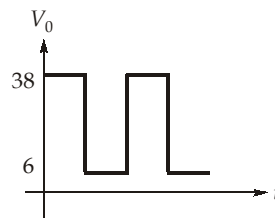
10. (d)

The circuit given in the question is a clamper circuit. The total signal will be clamped above the +6 V. So, the output waveform will be



Therefore, the maximum value of V_o is 38 V.

11. (c)

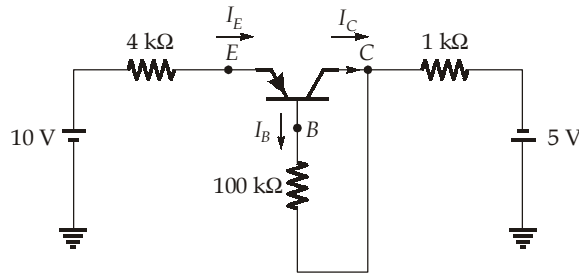

$$I_E = \frac{10 - V_E}{4 \text{ k}\Omega} = \frac{10 - 4}{4 \text{ k}\Omega} = 1.5 \text{ mA}$$

$$V_C = -5 + 1.5 = -3.5 \text{ V}$$

$$V_{EB} = V_E - V_B = 0.7 \text{ V}$$

$$V_B = 4 - 0.7 = 3.3 \text{ V}$$

$$V_{BC} = V_B - V_C = 3.3 - (-3.5) = 6.8 \text{ V}$$

$$I_B = \frac{V_{BC}}{100 \text{ k}\Omega} = 0.068 \text{ mA}$$

$$\frac{I_E}{I_B} = \beta + 1$$

$$\frac{1.5}{0.068} = \beta + 1$$

$$\beta = 21$$

12. (b)

Since the gate current is zero, then

$$I_{D1} = I_{D2} \text{ (Assuming both the transistor be in saturation region)}$$

$$\frac{1}{2}(200 \times 10^{-6})\left(\frac{500}{9}\right)(V_B - 0.4)^2(1 + 0.1 \times 0.9) = \frac{1}{2}(100 \times 10^{-6})(1.8 - V_B - 0.4)^2(1 + 0.1 \times 0.9)\left(\frac{500}{3}\right)$$


$$2(V_B - 0.4)^2 = 3(1.4 - V_B)^2$$

$$\sqrt{\frac{2}{3}}(V_B - 0.4) = (1.4 - V_B)$$

$$1.816V_B = 1.7264$$

$$V_B = 0.95 \text{ V}$$

13. (c)
For a MOS Circuit

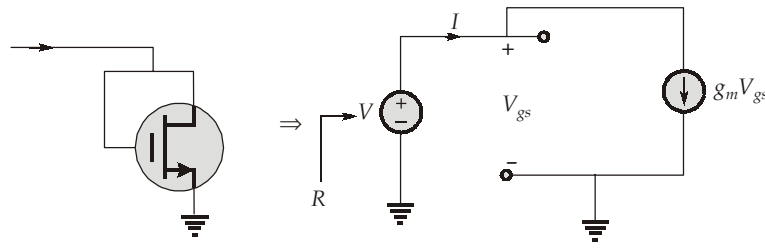


$$I = g_m V_{gs}$$


$$I = g_m V$$

$$R = \frac{V}{I} = \frac{1}{g_m}$$

Thus, the circuit can be viewed as

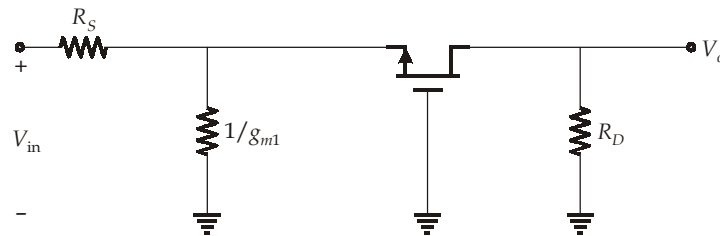

Let the circuit be drawn as

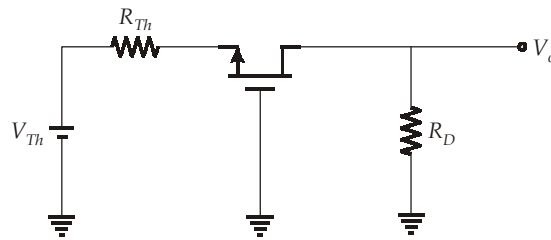

where

$$R_{Th} = \frac{1}{g_{m1}} \parallel R_s$$

and

$$V_{Th} = \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + R_s} \cdot V_{in}$$

Thus, the gain of this circuit is given as

$$V_o = \frac{g_{m2} R_D}{1 + g_{m2} R_s} V_{Th}$$


$$= \frac{g_{m2} R_D}{1 + g_{m2} R_s} \times \frac{1}{1 + g_{m1} R_s} V_{in}$$

$$= \frac{g_{m2} R_D}{1 + (g_{m1} + g_{m2}) R_s + g_{m1} g_{m2} R_s^2}$$


$$V_o \approx \frac{g_{m2} R_D}{1 + (g_{m1} + g_{m2}) R_s}$$

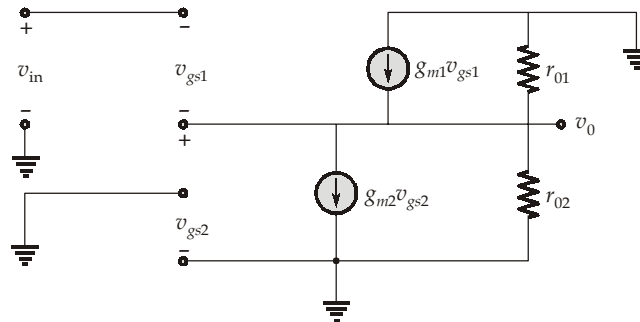14. (a)

Drawing the small signal equivalent model, we get



Thus, the circuit reduces to

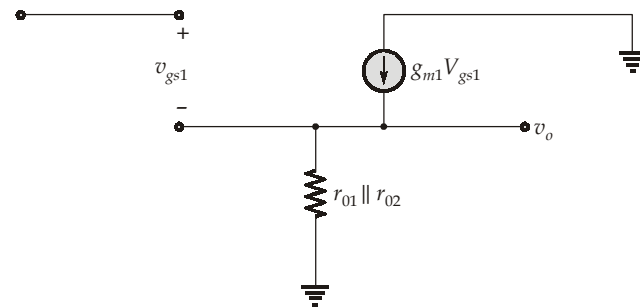

$\therefore$

and

$$v_o = (g_{m1} v_{gs1})(r_{o1} \parallel r_{o2})$$


$$v_{gs1} = v_{in} - v_o$$

$$v_o = g_{m1}(r_{o1} \parallel r_{o2})(v_{in} - v_o)$$

$$\frac{v_o}{v_{in}} = \frac{g_{m1}(r_{o1} \parallel r_{o2})}{1 + g_{m1}(r_{o1} \parallel r_{o2})}$$

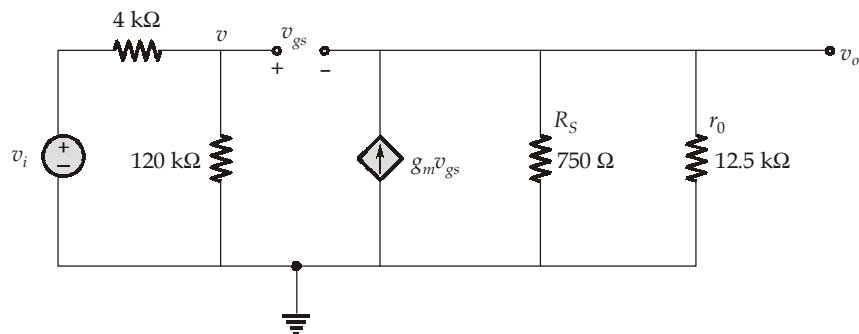15. (c)

The small signal equivalent model can be drawn as



The value of output voltage

$$v_o = g_m(R_s \parallel r_o)v_{gs}$$

Applying KVL we get

$$v - v_{gs} - g_m v_{gs}(R_s \parallel r_o) = 0$$

$$v = v_{gs}(1 + g_m(R_s \parallel r_o))$$

Substituting the value of v_{gs} , we get


$$v_o = \frac{g_m(R_s \parallel r_o)v}{1 + g_m(R_s \parallel r_o)}$$

$$\therefore v = \frac{R_i}{R_i + R_{si}} \times v_i$$

$$\therefore \frac{v_o}{v_i} = \frac{120}{120 + 4} \times \frac{(11.3)(0.75 \parallel 12.5)}{1 + 11.3(0.75 \parallel 12.5)}$$

$$A_V = \frac{v_o}{v_i} = 0.86$$

16. (c)

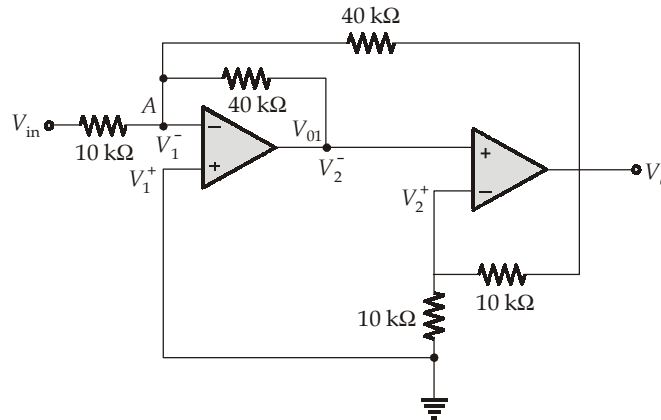

Apply KCL at node 'A'.

$$\frac{V_1^- - V_{in}}{10 \text{ k}\Omega} + \frac{V_1^- - V_{o1}}{40 \text{ k}\Omega} + \frac{V_1^- - V_o}{40 \text{ k}\Omega} = 0$$

$$V_1^- \left[\frac{1}{10 \text{ k}\Omega} + \frac{1}{40 \text{ k}\Omega} + \frac{1}{40 \text{ k}\Omega} \right] = \frac{V_{in}}{10 \text{ k}\Omega} + \frac{V_{o1}}{40 \text{ k}\Omega} + \frac{V_o}{40 \text{ k}\Omega}$$

Due to virtual ground, $V_1^- = V_1^+ = 0 \text{ V}$

$$\therefore \frac{V_{in}}{10 \text{ k}\Omega} + \frac{V_{o1}}{40 \text{ k}\Omega} + \frac{V_o}{40 \text{ k}\Omega} = 0 \quad \dots(1)$$

Now, $V_o = 2V_{o1}$

$$\therefore V_2^+ = \frac{V_o}{2}$$

$$\therefore V_2^- = V_2^+ = \frac{V_o}{2} = V_{o1}$$

$$\therefore V_o = 2V_{o1} \quad \dots(2)$$

From eqn. (1) and (2), we get


$$\frac{V_{in}}{10 \text{ k}\Omega} + \frac{V_o}{80 \text{ k}\Omega} + \frac{V_o}{40 \text{ k}\Omega} = 0$$

$$\frac{V_{in}}{10 \text{ k}\Omega} + \frac{3V_o}{80 \text{ k}\Omega} = 0$$

$$\frac{V_o}{V_{in}} = \frac{-8}{3} \text{ V/V}$$

17. (a)

Drawing the small signal model, we get

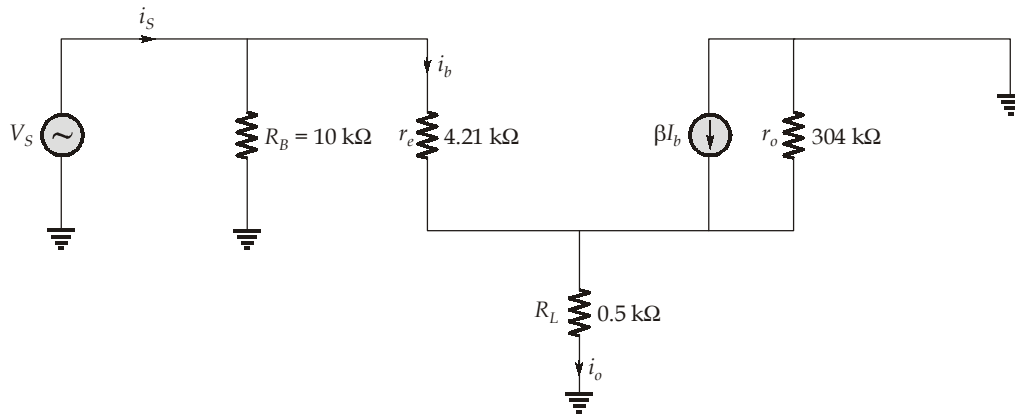

$$i_o = \frac{r_o}{r_o + R_L}(\beta + 1)i_b$$

$$i_b = \frac{R_B}{R_B + r_e + (R_L \parallel r_o)(1 + \beta)} i_s$$

$$\begin{aligned} A_i = \frac{i_o}{i_s} &= \frac{r_o}{r_o + R_L}(1 + \beta) \times \frac{R_B}{R_B + r_e + (R_L \parallel r_o)(1 + \beta)} \\ &= \frac{304 \times 10^3}{304 \times 10^3 + 500} \times 81 \times \frac{10 \times 10^3}{10 \times 10^3 + 4.21 \times 10^3 + (0.5 \text{ K} \parallel 304 \text{ K})(81)} \\ &= 0.998 \times 81 \times \frac{10 \times 10^3}{14.21 \text{ K} + 40.5 \text{ K}} = 14.8 \text{ V/V} \end{aligned}$$

18. (a)

$$\text{Line regulation} = \frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} \times 100$$

$$I = \frac{V_{\text{in}} - V_{Z0}}{4410 \Omega}$$

$$V_z = V_{z0} + IR_z = V_{z0} + \frac{10}{4410}(V_{\text{in}} - V_{z0})$$

$$V_{\text{out}} = \left(1 + \frac{10}{10}\right)V_z = 2V_z = \frac{880}{441}V_{z0} + \frac{2}{441}V_{\text{in}}$$

$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{2}{441} \times 100 = 0.45\%$$

19. (a)

∴

$$\beta = 98$$

$$1 \text{ mA} = 17I_B + I_C = \left(\frac{17}{\beta} + 1\right) \cdot I_C$$

$$I_C = \left(\frac{\beta}{17 + \beta}\right) \times 1 \text{ mA}$$

$$I_C = 0.85 \text{ mA}$$

∴

$$I_{C0} = I_{C1} = I_{C2} = \dots = I_{Cn} \quad (\because \text{all are having same value of } V_{BE})$$

Now,

$$V_o = nI_C(R) \\ = 16 \times 0.85 \times 10^{-3} \times 100 = 1.36$$

20. (d)

Since the value of voltage gain $A_V = \frac{v_o}{v_i}$ is equal to

$$A_V = \frac{v_o}{v_i} = \frac{-g_m R_D}{1 + g_m R_S}$$

where

$$g_m = 2\sqrt{\left(\frac{\mu_n C_{ox} W}{2L}\right) I_{DQ}}$$

$$= 2\sqrt{0.5 \times 2 \times 10^{-6}}$$

$$g_m = 2 \times 10^{-3} = 2 \text{ mA/V}$$

$\therefore$

$$A_V = \frac{-(2)(10)}{1 + 2 \times 3} = -2.85 \text{ V/V}$$

21. (c)

$$\frac{V_i}{R} = I_s e^{\frac{V_{BE}}{V_T}}$$


$$\frac{2}{1 \times 10^3} = 2 \times 10^{16} e^{\frac{V_{BE}}{V_T}}$$

$$V_T \ln 10^{13} = V_{BE}$$

$$V_{BE} = 0.78 \text{ V}$$

$$V_0 = -V_{BE} = -0.78 \text{ V}$$

22. (c)

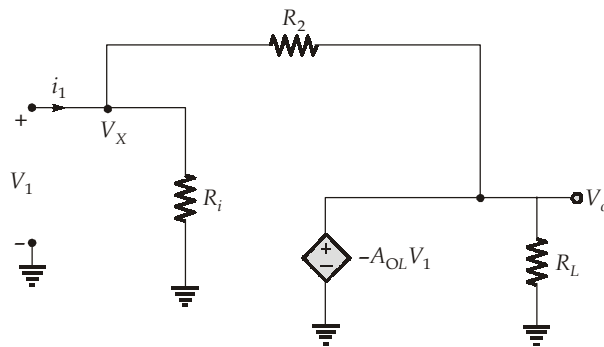

$$R_{in} = \frac{V_1}{i_1}$$

$$i_1 = \frac{V_X}{R_i} + \frac{V_X - (-A_{OL} V_1)}{R_2}$$

$$\{V_d = -V_1\}$$

$$i_1 = \frac{V_X}{R_i} + \frac{V_X + A_{OL} V_1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{i_1}{V_1} = \frac{1}{R_i} + \frac{1 + A_{OL}}{R_2}$$

$$(R_i = R_{eq})$$

$$R_{eq} = \left[\frac{1}{R_i} + \frac{1 + A_{OL}}{R_2} \right]^{-1}$$

$$R_{eq} = 0.1 \, \Omega$$

$$R_{in} = R_{eq} + 2000 \, \Omega$$

$$= 2000.1 \, \Omega$$

23. (d)

Let $Z_1 = R_1$ and $Z_2 = R_2 \parallel \frac{1}{sC_2}$

$$\frac{V_0(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

$$\frac{V_0(s)}{V_i(s)} = \frac{-R_2}{sR_1R_2C_2 + R_1} = \frac{-R_2/R_1}{sR_2C_2 + 1}$$

The dc gain k is $\frac{V_0(s)}{V_i(s)}$ at $s = 0$

$$\therefore k = \frac{-R_2}{R_1}$$

24. (c)


From the circuit,

$$V_0 = \begin{cases} 7 \, \text{V} ; & 7 \, \text{V} < V_i < 10 \, \text{V} \\ V_i ; & -5 \, \text{V} < V_i < 7 \, \text{V} \\ -5 \, \text{V} ; & -10 \, \text{V} < V_i < -5 \, \text{V} \end{cases}$$

$\therefore$ Only option (c) satisfies the above condition.

25. (b)

DC Analysis:

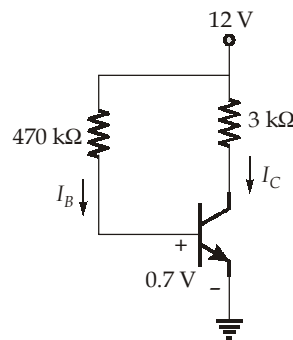


$$I_B = \frac{12 - 0.7}{470 \, \text{k}} = 24.04 \, \mu\text{A}$$

$$I_E = (1 + \beta)I_B = (101) \times 24.04 \, \mu\text{A} = 2.428 \, \text{mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{26 \, \text{mV}}{2.428 \, \text{mA}} = 10.71 \, \Omega$$

$$A_V = \frac{-R_C}{r_e} = \frac{-3 \, \text{k}\Omega}{10.71} = -280.11$$

26. (d)

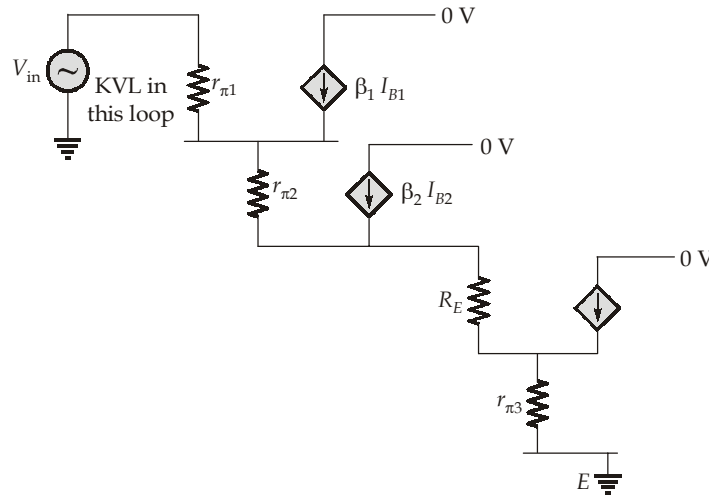By using the π model:

$$V_{in} = I_{B1} r_{\pi 1} + r_{\pi 2}(1 + \beta_1)I_{B1} + R_E(1 + \beta_2)I_{B2} + r_{\pi 3}(1 + \beta_2) I_{B2}$$

$$\text{where } I_{B2} = (1 + \beta_1)I_{B1}$$

thus on substitution option (d) is obtained.

27. (c)

In figure (II), current mirror circuit

$$\beta = 100, \frac{I_{C3}}{A_3} = \left(\frac{I_{C2}}{A_2} \right)$$

$$I_0 = \frac{A_3}{A_2} I_{C2} = \frac{A_3}{A_2} \left[\frac{I_{in}}{\left(1 + \frac{2}{\beta} \right)} \right]$$

$$I_0 = 3 \cdot \frac{2 \text{ mA}}{\left(1 + \frac{2}{100} \right)} = 5.88 \text{ mA}$$


In figure (I),

 $\Rightarrow$

$$3 \text{ V} = 0.7 + R_E I_0$$

 $\Rightarrow$
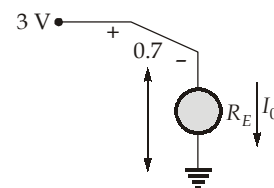
$$R_E = \frac{2.3}{I_0} = 0.39 \text{ k}\Omega$$



28. (d)

The fixed-bias circuit is shown below:


$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$\therefore V_{CE} = V_{CC} \text{ at } I_C = 0$$


$$\text{and } I_C = \frac{V_{CC}}{R_C} \text{ at } V_{CE} = 0$$

$$\therefore V_{CC} = 20 \text{ V}; \frac{V_{CC}}{R_C} = 10 \text{ mA}$$
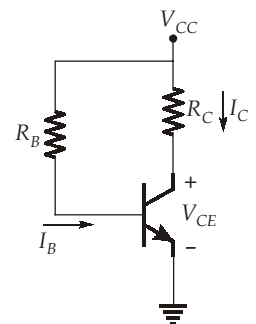
$$\Rightarrow R_C = \frac{20 \text{ V}}{10 \text{ mA}} = 2 \text{ k}\Omega$$



29. (b)

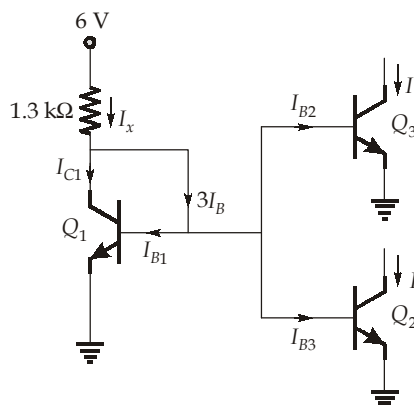

$$\begin{aligned} \therefore \quad I_x &= I_{C1} + I_{B1} + I_{B2} + I_{B3} & \{I_{B1} = I_{B2} = I_{B3} = I_B\} \\ I_x &= I_{C1} + 3I_B \end{aligned}$$


$$I_x = I_{C1} \left[1 + \frac{3}{\beta} \right] \quad \{ \because \beta \text{ is very large} \}$$

$$I_x \cong I_{C1} \cong I$$

$$I = \frac{6 - V_{BE}}{1.3 \text{ k}} = \frac{6 - 0.7}{1.3 \text{ k}} = 4.08 \text{ mA}$$

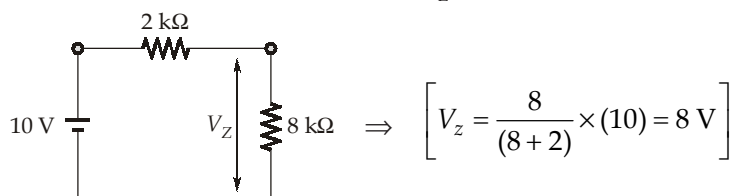30. (d)



For $(V_S = 10 \text{ V}) \rightarrow$ Zener in Breakdown $\Rightarrow (V)_{R_L} = V_z$



At Breakdown, $I_z = I_{z \text{ min}}$ ($V_s = 10 \text{ V}$)

$$I_S = I_{Z \text{ min}} + I_L$$
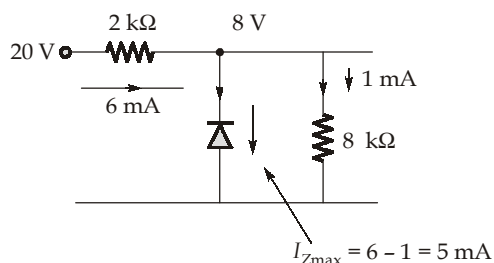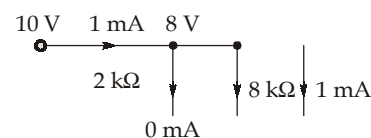
$$1 \text{ mA} = I_{Z \text{ min}} + I \text{ mA}$$



$$\therefore [I_{z \max} - I_{z \min} = 5 \text{ mA} - 0 \text{ mA} = 5 \text{ mA}]$$

