

**MADE EASY**

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

POWER SYSTEM-2

ELECTRICAL ENGINEERING

Date of Test : 15/11/2025

ANSWER KEY ➤

1. (a)	7. (d)	13. (b)	19. (c)	25. (a)
2. (c)	8. (d)	14. (b)	20. (c)	26. (b)
3. (a)	9. (a)	15. (b)	21. (b)	27. (b)
4. (b)	10. (b)	16. (d)	22. (c)	28. (c)
5. (c)	11. (a)	17. (b)	23. (b)	29. (b)
6. (d)	12. (d)	18. (b)	24. (b)	30. (d)

DETAILED EXPLANATIONS

1. (a)

Total Kinetic energy of the two machines,

$$\begin{aligned}
 &= G_1 H_1 + G_2 H_2 \\
 &= 400 \times 4 + 1600 \times 2 \\
 &= 4800 \text{ MJ}
 \end{aligned}$$

The equivalent H on the base of 200 MVA,

$$\begin{aligned}
 &= \frac{4800 \text{ MJ}}{200 \text{ MVA}} \\
 &= 24 \text{ MJ/MVA}
 \end{aligned}$$

2. (c)

$$\begin{aligned}
 \text{Minimum number of equations} &= 2n - m - 2 \\
 &= 2(112) - 20 - 2 \\
 &= 202
 \end{aligned}$$

3. (a)

$$\text{Line to line fault current, } |I_f| = \frac{\sqrt{3} \cdot E_a}{X_1 + X_2}$$

$$|I_f| = \frac{\sqrt{3}}{X_1 + X_2}$$

$$2 = \frac{\sqrt{3}}{X_1 + X_2}$$

$$X_1 + X_2 = \frac{\sqrt{3}}{2} \text{ p.u.}$$

$$\text{Line to ground fault current} = \frac{3 \cdot E_a}{X_1 + X_2 + X_0}$$

$$3 = \frac{3}{X_1 + X_2 + X_0}$$

$$\therefore \begin{aligned} X_1 + X_2 + X_0 &= 1 \\ X_0 &= 1 - (X_1 + X_2) \end{aligned}$$

$$X_0 = 1 - \frac{\sqrt{3}}{2}$$

$$\text{Zero sequence reactance, } X_0 = 0.134 \text{ p.u.}$$

4. (b)

Equivalent impedance of transmission line,

$$Z_{eq} = 0.1 \angle 85^\circ - j0.05$$

$$Z_{eq} = 0.05 \angle 80^\circ$$

Complex power flow through transmission line,

$$S_{12} = V_1 I_{12}^*$$

$$S_{12} = 1 \angle 8^\circ \left[\frac{1 \angle 8^\circ - 1 \angle 0^\circ}{0.05 \angle 80^\circ} \right]^*$$

$$= 20 \angle \delta [1 \angle (80^\circ - \delta) - 1 \angle 80^\circ]$$

$$S_{12} = 20 \angle 80^\circ - 20 \angle (80^\circ + \delta)$$

Real power flow through transmission line,

$$P_{12} = 20 \cos 80^\circ - 20 \cos (80^\circ + \delta)$$

$$1 = 20 \cos 80^\circ - 20 \cos (80^\circ + \delta)$$

$$\delta = \cos^{-1} \left[\frac{20 \cos 80^\circ - 1}{20} \right] - 80^\circ$$

$$\delta = 2.9^\circ$$

5. (c)

The rating of the machine, $G = 100$ MVA

Inertia constant, $H = 10$ MJ/MVA

Accelerating power, $P_a = 90$ MW - 60 MW = 30 MW

Angular momentum, $M = \frac{GH}{180f} = \frac{100 \times 10}{180 \times 50} = \frac{1}{9}$ MJ-s/electrical degree

$$\text{Acceleration, } \alpha = \frac{P_a}{M} = \frac{30}{1/9} = 270 \text{ elec. degree/s}^2$$

6. (d)

Size of Jacobian matrix $[J] = (2n - m - 2) \times (2n - m - 2)$

where,

n = total number of buses = 200

m = (reactive power support buses) +

(generator buses - one slack bus)

$$\therefore m = 40 + (30 - 1) = 69$$

$$\therefore [J] = (2 \times 200 - 69 - 2) \times (2 \times 200 - 69 - 2) \\ = (329 \times 329)$$

7. (d)

Total number of elements in the matrix

$$= 50 \times 50 = 2500$$

Total number of non-zero entries

$$= 2500 - (2500 \times 80\%) = 500$$

Out of 500 non-zero elements, 50 are diagonal elements and 450 are non-diagonal elements.

1 transmission line consists of 2 off diagonal element ($y_{ik} = y_{ki}$).

$$\therefore \text{No. of transmission lines} = \frac{450}{2} = 225$$

8. (d)

$$y_{10} = Y_{11} - y_{12} - y_{13} - y_{14} = -0.5 \quad (\therefore \text{Shunt element is present})$$

$$y_{20} = Y_{22} - y_{12} - y_{23} - y_{24} = -0.5 \quad (\therefore \text{Shunt element is present})$$

$$y_{30} = Y_{33} - y_{13} - y_{23} - y_{43} = -2 \quad (\therefore \text{Shunt element is present})$$

$$y_{40} = Y_{44} - y_{14} - y_{24} - y_{34} = 0$$

$\therefore$ Only bus 4 is not having shunt element.

9. (a)

$$P_{iK} = \frac{V_i V_K}{X} \sin \delta \quad \text{for lossless line}$$

P flows from higher voltage angle to lower voltage angle

$$Q_{iK} = \frac{V_i^2}{X} - \frac{V_i V_K}{X} \cos \delta$$

$\Rightarrow Q$ flows from higher voltage magnitude to lower voltage magnitude.

10. (b)

$$P_g = \frac{E_g E_m}{X_{dg} + X_T + X_{dm}} \sin(\delta_g - \delta_m)$$

$$0.5 = \frac{2 \times 1.3}{1.1 + 1.2 + 0.5} \sin(\delta_g - \delta_m)$$

$$(\delta_g - \delta_m) = \sin^{-1}\left(\frac{1.4}{2.6}\right) = 32.57^\circ$$

11. (a)

Given,

$$P_e = 50 \text{ MW}$$

$$\text{K.E.} = 800 \text{ MJ}$$

$$f = 50 \text{ Hz;}$$

$$\delta_0 = 10^\circ$$

$$\text{Time for 8 cycles} = \frac{8}{50} = 0.16 \text{ sec}$$

$$\text{Time for 4 cycles} = 0.08 \text{ sec}$$

$$P_a = 50 \text{ MW}$$

$$M = \frac{\text{K.E.}}{180 f} = \frac{GH}{180 \times f}$$

$$M = \frac{800}{180 \times 50} = 0.088$$

We know that, $M \frac{d^2 \delta}{dt^2} = P_a$

$$\frac{d^2 \delta}{dt^2} = \frac{P_a}{M}$$

Integrating twice we have,

$$\delta = \frac{P_a}{M} \left[\frac{t^2}{2} \right] + \delta_0 = \frac{50}{0.088} \left[\frac{0.08^2}{2} \right] + 10^\circ$$

$$\text{New value of power angle} = 1.81^\circ + 10^\circ = 11.81^\circ$$

12. (d)

Inertia constant, $H = 4 \text{ MW-sec/MVA}$
 $= 4 \text{ MJ/MVA}$

No load voltage, $V_1 = 1.2 \text{ p.u.}$

Infinite bus voltage, $V_2 = 1 \text{ p.u.}$

Total reactance, $X = X_G + X_L$

$$= 0.25 + 0.15$$

$$= 0.4 \text{ p.u.}$$

$$\text{Angular momentum, } M = \frac{GH}{\pi f} = \frac{1 \times 4}{\pi \times 50} = 0.0254$$

For 80% loading,

$$\sin \delta_0 = \frac{80}{100} = 0.8$$

$$\cos \delta_0 = \sqrt{1 - 0.8^2} = 0.6$$

$$\frac{dP_c}{d\delta} = \frac{V_1 V_2}{X} \cos \delta_0 = \frac{1.2 \times 1}{0.4} \times 0.6 = 1.8$$

$$f_n = \sqrt{\frac{\left| \frac{dP_e}{d\delta} \right|_{\delta_0}}{M}} = \sqrt{\frac{1.8}{0.0254}} = 8.41 \text{ rad/sec} = 1.34 \text{ Hz}$$

13. (b)

Sum of the line currents in a Δ is always zero

$$I_a + I_b + I_c = 0$$

$$I_b = -I_a$$

$$I_{a1} = \frac{1}{3} [I_a + \alpha I_b + \alpha^2 I_c] = \frac{1}{3} [I_a - \alpha I_a]$$

$$= \frac{I_a(1 - 1 \angle 120^\circ)}{3} = \frac{(10 \angle 0^\circ)(1 - 1 \angle 120^\circ)}{3}$$

$$I_{a1} = 5.77 \angle -30^\circ \text{ A}$$

14. (b)

Full load current of each alternator,

$$= \frac{20 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 1.05 \text{ kA}$$

Since the two identical alternators are operating in parallel

$$Z_1 = \frac{j0.18}{2} = j0.09 \text{ p.u.}$$

$$Z_2 = \frac{j0.15}{2} = j0.075 \text{ p.u.}$$

$$\begin{aligned} Z_0 &= j0.10 + 3R_n \\ &= j0.1 + 3 \times \frac{2 \times 20}{11^2} = j0.1 + 0.992 \end{aligned}$$

For an L-G fault,

$$\begin{aligned} \text{fault current, } I_f &= 3I_{a1} = \frac{3E_a}{Z_1 + Z_2 + Z_0} = \frac{3}{j0.09 + j0.075 + j0.1 + 0.992} \\ &= 2.92 \angle -14.96^\circ \text{ p.u.} \end{aligned}$$

$$\text{fault current, } I_f = 2.92 \times 1.05 = 3.066 \text{ kA}$$

Voltage drop across grounding resistor

$$= 3.066 \times 2 = 6.132 \text{ kV}$$

15. (b)

Voltage magnitude at bus-2,

$$V_2 = 1 - \frac{Z_{12}}{Z_{11}} = 1 - Z_{12} I_{f1} \quad \left(\because I_{f1} = \frac{1}{Z_{11}} \right)$$

$$0.9 = 1 - Z_{12} \times 12.5$$

$$Z_{12} = \frac{0.1}{12.5} = 0.008 \text{ p.u.}$$

and voltage magnitude at bus-1,

$$V_1 = 1 - \frac{Z_{12}}{Z_{22}} = 1 - Z_{12} \cdot I_{f2}$$

$$= 1 - 0.008 \times 10$$

$$= 1 - 0.08$$


$$V_1 = 0.92 \text{ p.u.}$$

16. (d)

Given,

$$X_1 = j0.2 \text{ p.u.}, \quad X_2 = j0.12 \text{ p.u.}$$
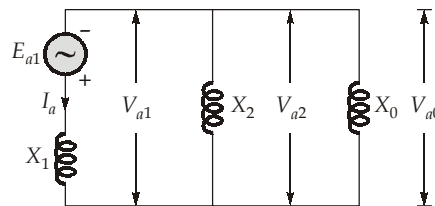
$$X_0 = j0.05 \text{ p.u.}, \quad X_n = X_f = 0$$



In the above diagram,

$$V_{a1} = V_{a2} = V_{a0}$$

$$V_{a1} = E_{a1} - I_a X_1$$

$$I_{a1} = \frac{E_a}{X_1 + (X_2 \parallel X_0)} = \frac{1}{0.2 + (0.12 \parallel 0.05)} = 4.25 \text{ p.u.}$$

$$V_{a1} = 1 - 4.25 \times 0.2 = 0.15 \text{ p.u.}$$

As we know, healthy phase is 'a',

So


$$V_a = V_{a0} + V_{a1} + V_{a2}$$

$$= 3 V_{a1} = 0.45 \text{ p.u.}$$

Actual voltage of healthy phase,

$$V_{a(\text{actual})} = 0.45 \times \frac{6.6}{\sqrt{3}} = 1.71 \text{ kV}$$

17. (b)

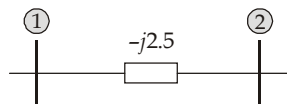 $\Rightarrow$

$$[Y_{\text{bus}}] = \begin{bmatrix} -j2.5 & j2.5 & 0 \\ j2.5 & -j2.5 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$[Y_{\text{bus}}]_{\text{mod}} = [Y_{\text{bus}}]_{\text{old}} - [Y'_{\text{bus}}]$$

$$= \begin{bmatrix} -j10 & j5 & j5 \\ j5 & -j10 & j5 \\ j5 & j5 & -j10 \end{bmatrix} - \begin{bmatrix} -j2.5 & j2.5 & 0 \\ j2.5 & -j2.5 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$[Y_{\text{bus}}]_{\text{mod}} = \begin{bmatrix} -j7.5 & j2.5 & j5.0 \\ j2.5 & -j7.5 & j5.0 \\ j5.0 & j5 & -j10 \end{bmatrix}$$

18. (b)

When

$$P_e = P_{\max} \sin \delta$$

$$P_e = 0.6 \times P_{\max};$$

$$\delta = \delta_0$$

$$\delta_0 = \sin^{-1}[0.6] = 36.86^\circ$$

$$M = \frac{H}{\pi f} = \frac{4}{\pi \times 60} = \frac{1}{15\pi} \text{ sec}^2/\text{rad}$$

$$\text{Frequency of oscillation} = \sqrt{\frac{\left(\frac{\partial P_e}{\partial \delta}\right)_{\delta_0}}{M}} = \sqrt{\frac{\left(\frac{1.1 \times 1}{1.35} \cos 36.87^\circ\right)}{\frac{1}{15\pi}}} = 5.54 \text{ rad/sec}$$

$$f_n = \frac{5.54}{2\pi} = 0.882 \text{ Hz}$$

19. (c)

For a solid LG fault,

Fault current is: $(I_F)_{LG} = \frac{3E}{(2X_1 + X_0 + 3X_n)}$ (Here, $X_1 \approx X_2$ for synchronous generator)

Similarly, for a solid 3- ϕ fault

$$(I_F)_{3-\phi} = \frac{E}{X_1}$$

For LG fault current to be less than 3- ϕ fault current,

$$\frac{3E}{2X_1 + X_0 + 3X_n} < \frac{E}{X_1}$$

or, $2X_1 + X_0 + 3X_n > 3X_1$

or, $X_n > \frac{1}{3}(X_1 - X_0)$

Hence, option (c) is correct.

20. (c)

In LLG fault,

$$I_{\text{positive}} + I_{\text{negative}} + I_{\text{zero}} = 0$$

Here, $j1.653 - j0.5 - j1.153 = 0$

Hence fault is double line to ground fault.

21. (b)

$$\text{Synchronizing power coefficient} = P_{\max} \cos \delta_0 = \frac{dP_e}{d\delta}$$

Here,

$$P_{\max} = 2,$$

$$\delta = 30^\circ$$

 $\therefore$

$$S_p = 2 \cos 30^\circ$$

$$= 2 \times \frac{\sqrt{3}}{2} = \sqrt{3}$$

22. (c)

$$Y_{11} = y_{11} + y_{12} + y_{13} = -j 2.86$$

$$Y_{22} = y_{12} + y_{22} + y_{23} = -j 6$$

$$Y_{33} = y_{13} + y_{23} + y_{33} = -j 8.86$$


$$Y_{12} = Y_{21} = -y_{12} = 0$$

$$Y_{13} = Y_{31} = -y_{13} = j 2.86$$

$$Y_{23} = Y_{32} = -y_{23} = j 2$$

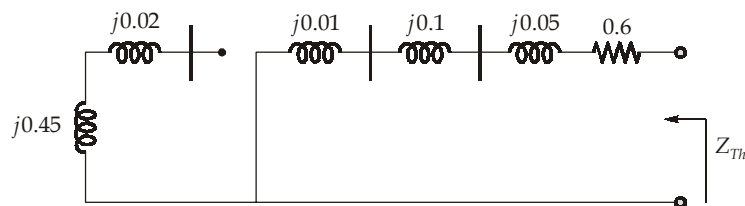23. (b)


The zero sequence impedance network from point P and ground



The Thevenin's equivalent zero sequence impedance

$$Z_{Th} = (0.6 + j 0.16) \text{ p.u.}$$

24. (b)

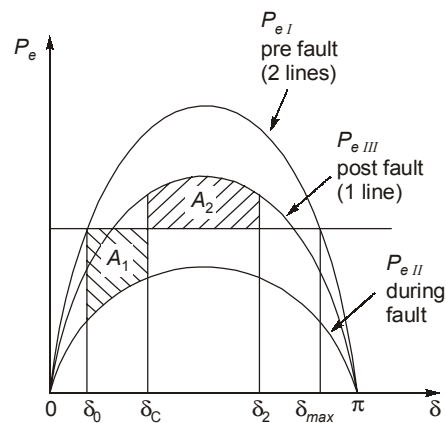

$$P_{\max I} = 2.0 \text{ pu,}$$

$$P_{\max II} = 0.5 \text{ pu,}$$

and,

$$P_{\max III} = 1.5 \text{ pu}$$

Initial loading

$$P_m = 1.0 \text{ pu}$$

$$\delta_0 = \sin^{-1} \left(\frac{P_m}{P_{\max I}} \right) = \sin^{-1} \frac{1}{2} = 0.523 \text{ rad}$$

$$\delta_{\max} = \pi - \sin^{-1} \left(\frac{P_{\max}}{P_{\max III}} \right) = \pi - \sin^{-1} \left(\frac{1}{1.5} \right) = 2.41 \text{ rad}$$

$$\cos \delta_{cr} = \frac{P_m (\delta_{\max} - \delta_0) - P_{\max II} \cos \delta_0 + P_{\max III} \cos \delta_{\max}}{P_{\max III} - P_{\max II}}$$

$$\cos \delta_{cr} = \frac{1.0(2.41 - 0.523) - 0.5 \cos 0.523 + 1.5 \cos 2.41}{1.5 - 0.5}$$


$$\delta_{cr} = 70.3^\circ$$

25. (a)

The earth fault is assumed to occur on the red phase. Taking red phase as the reference, its phase e.m.f.

$$E_R = \frac{11 \times 1000}{\sqrt{3}} = 6351 \text{ V}$$

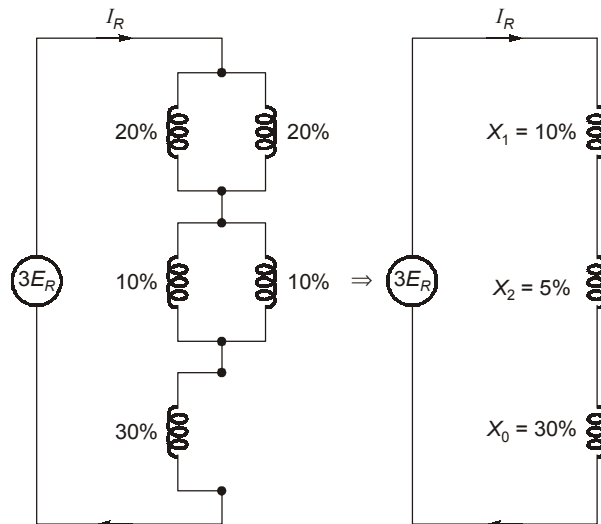For line to ground fault the equivalent circuit will be



The percentage reactances can be converted into ohmic values as under :

$$\% X = \frac{Z (MVA_b)}{(KV)^2} \times 100$$

$$Z = \frac{\% X \times (KV)^2}{(MVA_b) \times 100}$$

$$X_1 = \frac{10 \times (11)^2}{20 \times 100} = 0.605 \Omega$$

$$X_2 = \frac{5 \times 11^2}{20 \times 100} = 0.3025 \Omega$$

$$X_0 = \frac{30 \times 11^2}{20 \times 100} = 1.815 \, \Omega$$

$$\text{Fault current} \quad \vec{I}_R = \frac{3 \vec{E}_R}{X_1 + X_2 + X_0} = \frac{3 \times 6351}{j0.605 + j0.3025 + j1.815}$$

$$\vec{I}_R = -j 6998 \, \text{A}$$

$$|I_R| = 6998 \, \text{A}$$

26. (b)

Let the base kVA be 500 kVA and base voltage be 2.5 kV,


Per unit transient reactance of generator,

$$X_g' = \frac{j8}{100} = j0.08 \, \text{p.u.}$$

Per unit subtransient reactance of each motor,

$$X_m'' = j0.2 \times \frac{500}{250} = j0.4 \, \text{p.u.}$$

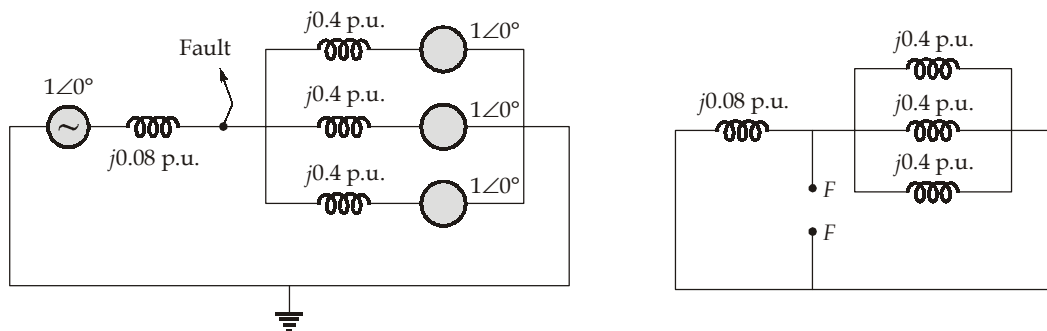Per unit reactance diagram is shown below,



Thevenin reactance when viewed from fault terminals,

$$X_{th} = \frac{\frac{j0.4}{3} \times j0.08}{\frac{j0.4}{3} + j0.08} = j0.05 \, \text{p.u.}$$

At fault location V_{th} = rated voltage,

$$\text{Fault current at } F, I_f = \frac{1}{j0.05} = -j20 \, \text{p.u.}$$

The generator contribution is,

$$I_g = -j20 \times \frac{j \frac{0.4}{3}}{j \frac{0.4}{3} + j0.08}$$

$$I_g = -j12.5 \, \text{p.u.}$$


Contribution of motors,

$$3I_m = I_f - I_g = -j20 - (-j12.5)$$

$$3I_m = -j7.5$$

$$I_m = -j2.5 \text{ p.u.}$$

27. (b)

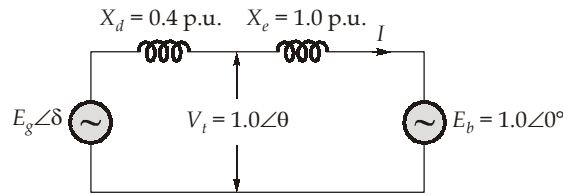

$$I = \frac{\vec{V}_t - \vec{E}_b}{jX_e} = \frac{1\angle\theta - 1\angle 0}{j1}$$

Also,

$$E_g = V_t + jX_d I$$

$$= 1\angle\theta + j0.4 \left[\frac{1\angle\theta - 1\angle 0}{j1} \right]$$

$$= 1\angle\theta + 0.4\angle\theta - 0.4$$

$$= 1.4\angle\theta - 0.4$$

$$E_g = (1.4 \cos \theta - 0.4) + j1.4 \sin \theta$$

Under steady state stability, angle of E_g is 90° , which means the real part of E_g is zero

Therefore, $1.4 \cos \theta - 0.4 = 0$

$$\theta = \cos^{-1} \left(\frac{0.4}{1.4} \right) = 73.40^\circ$$

Also

$$E_g = j1.4 \sin \theta$$

$$= 1.4 \sin (73.40) \angle 90^\circ$$

$$|E_g| = 1.34$$

$$\text{Maximum steady state power} = \frac{E_g \cdot E_b}{X} = \frac{1.34 \times 1.0}{1 + 0.4} = 0.9583 \text{ p.u.}$$

28. (c)

Reactive power supplied by capacitor to bus-1,

$$Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_2||V_1|}{X} \cos \delta$$

Given that,

$$Q_{21} = 0$$

$$\frac{|V_2|^2}{X} = \frac{|V_2||V_1|}{X} \cos \delta$$

$$|V_2| = |V_1| \cos \delta$$

Given that,

$$|V_1| = 1 \text{ p.u.}$$

$$|V_2| = \cos \delta \quad \dots(i)$$

Since load demand at bus 2 is 1 p.u. (real power). This real power can be supplied by generator S_{G1} only. So this power should flow through transmission line from bus 1 to bus 2

∴

$$P_{12} = 1 \text{ p.u.}$$

∴ real power flow from bus 1 to bus 2,

$$P_{12} = \frac{|V_1||V_2|}{X} \sin \delta$$

$$1 = \frac{1 \cdot \cos \delta}{0.5} \cdot \sin \delta$$

$$0.5 = \frac{\sin 2\delta}{2}$$

$$\sin 2\delta = 1$$

$$2\delta = 90^\circ$$

$$\delta = 45^\circ$$


∴ from equation (i),

$$|V_2| = \cos \delta = \cos 45^\circ = \frac{1}{\sqrt{2}}$$

Voltage at bus-2, $V_2 = \frac{1}{\sqrt{2}} \angle -45^\circ$

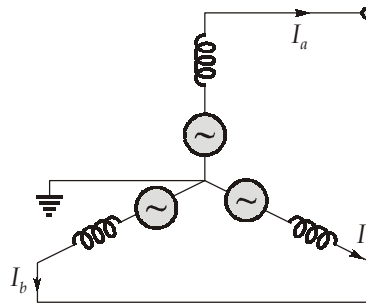29. (b)

Line-to line fault occurs on *b* and *c* phases of generator,




$$I_f = I_b = -I_c$$

$$I_a = 0$$

and

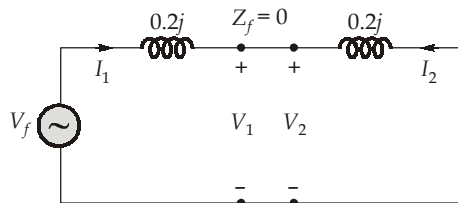The sequence network for line to line fault is



$$I_1 = \frac{V_f}{z_1 + z_2}$$

⇒

$$I_f = I_b = (\alpha^2 - \alpha)I_1 = -j\sqrt{3}I_1 = \frac{-j\sqrt{3}V_f}{z_1 + z_2}$$

and

$$I_{f \text{ p.u.}} = \frac{-j\sqrt{3} \times 1}{j0.2 + j0.2}$$


$$|I_{f \text{ p.u.}}| = \frac{\sqrt{3}}{0.4} = 4.33 \text{ p.u.}$$

$$\text{Base current} = \frac{25 \times 10^3}{\sqrt{3} \times 11} = 1312.16 \text{ A}$$

$$\text{Fault current, } I_f = 4.33 \times 1312.16 = 5.68 \text{ kA}$$

30. (d)

Existing system and bus matrix is

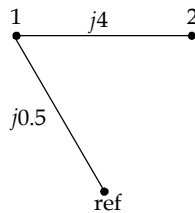

$$Z_{\text{Bus}} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix}$$

Modifying line with reactance $j2$ is equivalent to adding a line in parallel with impedance $j4$. Thus it is type-4 modification.

$$[Z_{\text{new}}] = [Z_{\text{old}}] - \frac{1}{Z_{11} + Z_{22} - 2Z_{12} + Z_s} \begin{bmatrix} \text{subtract} \\ 2^{\text{nd}} \text{ column} \\ \text{from first column} \end{bmatrix} [\text{Transpose}]$$

$$[Z_{\text{Bus}}]_{\text{new}} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix} - \frac{1}{j0.5 + j4.5 - 2(j0.5) + j4} \begin{bmatrix} j0 \\ -j4 \end{bmatrix} \begin{bmatrix} j0 & -j4 \end{bmatrix}$$


$$= \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix} - \frac{1}{j8} \begin{bmatrix} 0 & 0 \\ 0 & -16 \end{bmatrix}$$

$$= \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix} - \begin{bmatrix} 0 & 0 \\ 0 & -\frac{16}{j8} \end{bmatrix}$$


$$= \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 - \frac{j16}{8} \end{bmatrix} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j2.5 \end{bmatrix}$$

Alternative :


New system will

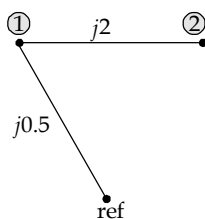

First branch :

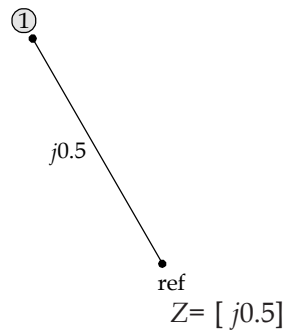

Type - 2 modification

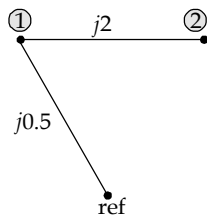

$$Z = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j0.5 + j2 \end{bmatrix} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j2.5 \end{bmatrix}$$

■■■■