



MADE EASY

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

DIGITAL CIRCUITS

EC-EE

Date of Test : 26/05/2026

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (a) | 7. (c) | 13. (c) | 19. (c) | 25. (c) |
| 2. (d) | 8. (c) | 14. (b) | 20. (b) | 26. (b) |
| 3. (a) | 9. (c) | 15. (c) | 21. (c) | 27. (a) |
| 4. (a) | 10. (c) | 16. (d) | 22. (b) | 28. (a) |
| 5. (c) | 11. (c) | 17. (a) | 23. (b) | 29. (c) |
| 6. (a) | 12. (c) | 18. (a) | 24. (c) | 30. (c) |

DETAILED EXPLANATIONS

1. (a)

$$\text{output, } f = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$

where,

$$S_0 = A; S_1 = B$$

$$I_0 = C; I_1 = \overline{C+D}; I_2 = CD; I_3 = 1$$

 \therefore

$$f = \overline{CBA} + (\overline{C+D})(\overline{BA}) + CDB\overline{A} + AB$$

$$= \overline{CBA} + (\overline{CD})(\overline{BA}) + CDB\overline{A} + AB$$

$$= \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} B C D + AB$$

$$f = \overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} C \overline{B} + \overline{A} C D + AB$$

$$[\because \overline{B} + BD = \overline{B} + D]$$

$$= A[B + \overline{C} \overline{D}] + \overline{A} C \overline{B} + \overline{A} C D$$

$$f = AB + A \overline{C} \overline{D} + \overline{A} C \overline{B} + \overline{A} C D$$

2. (d)

$$Q = AB + \overline{[(B+C)(BC)]}$$

$$= AB + \overline{[BC + \overline{BC}]}$$

$$= AB + \overline{BC}$$

$$= AB + \overline{B} + \overline{C}$$

$$Q = A + \overline{B} + \overline{C}$$

3. (a)

We have,

$$S = AB$$

 \therefore output of 2×1 MUX is,

$$f = \bar{S}I_0 + SI_1 = \overline{AB}(A \oplus B) + AB(A \oplus B)$$

$$= (A \oplus B)[\overline{AB} + AB] = (A \oplus B)[1]$$

$$f = A \oplus B$$

4. (a)

Given,

$$(5456)_8$$

$$\begin{array}{cccc} \overline{5} & \overline{4} & \overline{5} & \overline{6} \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 101 & 100 & 101 & 110 \end{array}$$

$$(101100101110)_2$$

For Hexadecimal number, grouping 4 binary bits

$$\begin{array}{ccc} \overline{1011} & \overline{0010} & \overline{1110} \\ \downarrow & \downarrow & \downarrow \\ B & 2 & E \end{array}$$

 \therefore

$$(5456)_8 \longrightarrow (B2E)_{16}$$

5. (c)

Number of quantization levels for 12-bit DAC

$$= 2^{12} = 4096$$

$$\text{Resolution} = \frac{1}{2^{12} - 1} = 0.244 \times 10^{-3}$$

The smallest reading possible which corresponds to 1 LSB is $0.244 \times 10^{-3} \times 10$

$$= 2.44 \text{ mV}$$

6. (a)

A	B	C
0	0	0 (Q_1 : OFF, Q_2 : OFF, Q_3 : ON)
0	1	1 (Q_1 : OFF, Q_2 : ON, Q_3 : OFF)
1	0	1 (Q_1 : ON, Q_2 : OFF, Q_3 : OFF)
1	1	1 (Q_1 : ON, Q_2 : ON, Q_3 : OFF)

7. (c)

$$(00110010) = (50)_{10}$$

$$1 \text{ V} = K \times 50 \Rightarrow K = 20 \text{ mV}$$

The largest output will occur for an input of $(11111111)_2 = (255)_{10}$

$$V_{\text{out(max)}} = 20 \text{ mV} \times (255)_{10} \\ = 5.10 \text{ V}$$

8. (c)

The given circuit is a Binary Ripple Up Counter. The output is cleared when $Q_B Q_C = 11$ corresponding to the state

$$\begin{array}{ccc} Q_C & Q_B & Q_A \\ 1 & 1 & 0 \end{array} \rightarrow \text{Mod 6 ripple counter}$$

9. (c)

When, $P = 0$,

$$Q_1 \rightarrow \text{ON}, Q_2 \rightarrow \text{OFF} \Rightarrow Y = Q$$

When, $P = 1$,

$$Q_1 \rightarrow \text{OFF}, Q_2 \rightarrow \text{ON} \Rightarrow Y = \bar{Q}$$

$$\text{Output} = \bar{P}Q + P\bar{Q}$$

$$Y = \bar{P}Q + P\bar{Q}$$

$$Y = P \oplus Q$$

$$Y = P \odot \bar{Q}$$

10. (c)

$$f = \bar{x}\bar{y} + \bar{x}y + x\bar{y}$$

$$= \bar{x}(\bar{y} + y) + x\bar{y}$$

$$= \bar{x} + x\bar{y}$$

$$= (\bar{x} + x) \cdot (\bar{x} + \bar{y}) = \bar{x} + \bar{y} = \overline{x \cdot y}$$

Thus it works as NAND gate.

11. (c)
Given output of 4×1 MUX,

$$f = \Sigma m(0, 2, 3, 4, 7)$$

By using K-map,

	BC	00	01	11	10
A	0	1		1	1
	1	1		1	

∴ $f = \bar{B}\bar{C} + BC + \bar{A}B\bar{C}$

The output function of 4×1 MUX can be written as,

$$f = I_0\bar{B}\bar{C} + I_1\bar{B}C + I_2B\bar{C} + I_3BC$$

On comparing,

$$I_0 = 1$$

$$I_1 = 0$$

$$I_2 = \bar{A}$$

$$I_3 = 1$$

12. (c)
The truth table is,

X	Y	Z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

For A:

	YZ	00	01	11	10
X	0			1	
	1		1	1	1

$$A = YZ + XY + XZ$$

For B:

	YZ	00	01	11	10
X	0		1		1
	1	1		1	

$$B = \Sigma m(1, 2, 4, 7) = X \oplus Y \oplus Z$$

For C:

YZ X	00	01	11	10
0	1			1
1	1			1

$$C = \bar{Z}$$

13. (c)

$$(10)_{10} = (1010)_2$$

[Switches D_3 and D_1 are closed]

The current flowing in $12.5 \text{ k}\Omega$ branch,

$$I_3 = \frac{5 \text{ V}}{12.5 \text{ k}\Omega} = 0.4 \text{ mA}$$

The current flowing in $50 \text{ k}\Omega$ branch,


$$I_1 = \frac{5 \text{ V}}{50 \text{ k}\Omega} = 0.1 \text{ mA}$$

$$V_{\text{out}} = -[(0.4) \text{ mA} + 0.1 \text{ mA}] \times 20 \text{ (k}\Omega) = -10 \text{ V}$$

14. (b)


$$F(A, B, C) = \Sigma(1, 3, 5, 6)$$

	D_0	D_1	D_2	D_3
\bar{A}	0	①	2	③
A	4	⑤	⑥	7
	0	1	A	\bar{A}

 


15. (c)

Present State	Inputs		Next State
	J	K	
Q_n			Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

 16. (d)
OR-AND logic is equivalent to NOR-NOR logic, hence we get

$$Y = (X_1 + \overline{X_1} + X_2) \cdot (X_2 + \overline{X_1} + X_2)$$



$$Y = (X_1 + \overline{X_1} \cdot \overline{X_2}) \cdot (X_2 + \overline{X_1} \cdot \overline{X_2})$$

$$Y = (X_1 + \overline{X_2})(X_1 + \overline{X_1})(X_2 + \overline{X_1})(X_2 + \overline{X_2})$$

$$Y = (X_1 + \overline{X_2})(X_2 + \overline{X_1})$$

$$Y = X_1 X_2 + \overline{X_1} \cdot \overline{X_2} = X_1 \odot X_2 = \overline{X_1 \oplus X_2}$$

17. (a)

$$\% \text{ resolution} = \frac{1}{2^n - 1} \times 100$$

$$0.4 = \frac{1}{2^n - 1} \times 100$$

$$2^n - 1 = \frac{100}{0.4} = 250$$

$$2^n = 251$$

$$\Rightarrow n = \log_2 251 \approx 8$$

$$n = 8$$

18. (a)

The output B for the given full subtractor can be written in K-Map as,

B	ca	00	01	11	10
b	0	0	1	1	1
	1	0	0	1	0

Borrow,

$$B = ca + \overline{b}a + \overline{b}c$$

19. (c)

$$Y = [(A \cdot B + C) \cdot \overline{D}] \cdot [ABC]$$

$$= (AB\overline{D} + C\overline{D}) \cdot (ABC)$$


$$= ABC\overline{D} + ABC \cdot \overline{C}\overline{D}$$

$$Y = ABC\overline{D}$$

20. (b)

Option	Signed Magnitude	2's Complement
(a)	-0	-32
(b)	-16	-16
(c)	-24	-8
(d)	-31	-1

21. (c)

 


$$Q_{n+1} = D = Q \oplus X$$

For $X = 0$, $Q_{n+1} = Q_n$ and for $X = 1$, $Q_{n+1} = \overline{Q_n}$.

Therefore, the given circuit acts as T flip-flop for $T = X$.

22. (b)

 

If $V_A = +3\text{ V}$ and $V_B = 0$, D_1 is ON and D_2 is OFF,

Thus, $V_{out} = V_A = +3\text{ V}$

If uncertain we can assume both D_1 and D_2 are forward-biased immediately facing a conflict:

D_1 enforces a voltage of $+3\text{ V}$ at the output whereas D_2 shorts V_{out} to $V_B = 0$. This assumption is therefore incorrect.

The symmetry of the circuit with respect to V_A and V_B suggest that $V_{out} = +3\text{ V}$ if $V_A = 0$ and $V_B = +3\text{ V}$. If $V_A = V_B = 0$, both the diodes D_1 and D_2 are OFF, with $V_{out} = 0\text{ V}$. The circuit, thus operates as a logical OR - gate.

23. (b)

From the given digital circuit,

$$D_0 = \overline{Q_0 + Q_2}$$

Initially, $Q_0 = 0$; $Q_1 = 0$, $Q_2 = 0$

\therefore $D_0 = 1$

Clk	Q ₀	Q ₁	Q ₂
0	0	0	0
1	1	0	0
2	0	1	0
3	1	0	1
4	0	1	0
5	1	0	1
6	0	1	0

The given circuit is MOD-2 counter.

24. (c)

Given, input frequency, $f_i = 96 \text{ kHz}$

After MOD-6 counter, $f' = \frac{f_i}{6} = \frac{96 \text{ K}}{6} = 16 \text{ kHz}$

After Decade counter, $f_0 = \frac{f'}{10} = \frac{16 \text{ kHz}}{10} = 1.6 \text{ kHz}$

25. (c)

The given logic function can be written as,

$$f(A, B, C, D) = \Sigma m(0, 4, 5, 10, 11, 13, 15)$$

Using K-map:

CD \ AB	00	01	11	10
00	1			
01	1	1		
11		1	1	
10			1	1

Total prime implicants = 6 ($AC'D'$, $A'BC'$, $BC'D$, ABD , ACD and $AB'C$)

Number of essential prime implicants = 2 ($A'C'D'$ and $AB'C$)

26. (b)

Given, $f_1(A, B, C) = \Sigma m(2, 3, 4)$

$$f_2(A, B, C) = \pi M(0, 1, 5, 6, 7) = \Sigma m(2, 3, 4)$$

For f_{out} to be zero, the function f_3 should be equal to,

$$f_3(A, B, C) = \Sigma m(2, 3, 4)$$

\therefore The maximum number of possible minterms = 3.

27. (a)

From the given number, the minimum value of 'x' can be written as, "12 + 1 = 13" ($\because C = 12$)

Therefore, the least decimal equivalent

$$\begin{aligned} &= 10 \times 13^2 + 11 \times 13^1 + 12 \times 13^0 \\ &= 1690 + 143 + 12 = (1845)_{10} \end{aligned}$$

28. (a)

In a 4-bit ripple counter, four flip-flops (FF0 to FF3) are used. The input frequency of flip-flop FF0 is ' f ' and its output waveform frequency is $f/2$ which is applied as input of FF1. Consequently, the output waveform frequency of FF1 is $f/4$ which is used as input of FF2.

Then output waveform frequency of FF2 is $f/8$ which is used as input of FF3. Therefore, the output waveform frequency of FF3 is $f/16$ and the time period is

$$T = \frac{1}{\text{Frequency}} = \frac{16}{f}$$

Since, time period of the last flip-flop (FF3) is 128 microseconds.

$$\therefore T = \frac{16}{f} = 128 \times 10^{-6}$$

$$\therefore f = \frac{16}{128 \times 10^{-6}} = 125 \text{ kHz}$$

\therefore The clock frequency of a 4-bit ripple counter is,

$$f = 125 \text{ kHz}$$

29. (c)

15's complement is equivalent to

$$\begin{array}{r} \text{F F F} \\ - \text{B B D} \\ \hline (\text{4 4 2})_{16} \end{array}$$

30. (c)

Since, given that, $V_{\text{out}} = 0.2 \text{ V}$ for 00001

\therefore the weight of LSB is 0.2 V.

The the weight of other bits in weighted D/A converter can be obtained as 0.4 V, 0.8 V, 1.6 V and 3.2 V respectively.

For a digital input of 11111, the value of output, $V_{\text{out}} = 3.2 + 1.6 + 0.8 + 0.4 + 0.2 = 6.2 \text{ V}$.

