



MADE EASY

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

DIGITAL CIRCUITS

EC-EE

Date of Test : 20/05/2026

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (a) | 13. (d) | 19. (d) | 25. (c) |
| 2. (d) | 8. (c) | 14. (c) | 20. (a) | 26. (a) |
| 3. (a) | 9. (b) | 15. (b) | 21. (a) | 27. (a) |
| 4. (b) | 10. (c) | 16. (c) | 22. (c) | 28. (a) |
| 5. (d) | 11. (a) | 17. (c) | 23. (a) | 29. (b) |
| 6. (b) | 12. (a) | 18. (c) | 24. (a) | 30. (d) |

DETAILED EXPLANATIONS

1. (b)

$$X = 1010.010$$

$$X + (-Y)$$

$$Y = 0111.111$$

Taking 2's complement of Y

$$Y = \begin{array}{r} 1000.000 \\ +1 \\ \hline 1000.001 \end{array}$$

$$X + (-Y) = \begin{array}{r} 1010.010 \\ +1000.001 \\ \hline 0010.011 \end{array}$$

2. (d)

By checking the options, we found that only option (d) meets both the requirements


$$Y = (A \odot B) + C$$

When A and B are same then $Y = 1 + C = 1$.

When A and B are different then $Y = 0 + C = C$.

 3. (a)

Bubbled OR Gate is equivalent to NAND Gate and Bubbled AND Gate is equivalent to NOR Gate. Hence, the circuit can be redrawn as



LED will emit light when $Z = 0$.

(i) For $A = 0, B = 0$: $X = 1, Y = 0$. Hence, $Z = 0$

(ii) For $A = 1, B = 0$: $X = 0, Y = 0$. Hence, $Z = 1$

(iii) For $A = 0, B = 1$: $X = 0, Y = 0$. Hence, $Z = 1$

(iv) For $A = 1, B = 1$: $X = 0, Y = 1$. Hence, $Z = 0$

Therefore, LED emits light for $A = 0, B = 0$ and $A = 1, B = 1$.

4. (b)

We know that, For dual slope integrating type ADC,

$$\text{analog input, } V_a = \frac{V_R}{2^n} \times N$$

where, $V_a = 5 \text{ V}, V_R = 10 \text{ V}, n = 4$

the equivalent digital number, $N = 2^n \times \frac{V_a}{V_R}$

$$N = 2^4 \times \frac{5}{10} = 8 = (1000)_2$$

5. (d)

Clear signal is $\overline{Q_A \cdot Q_D}$

As it is a synchronous clear.

∴ The counter will get clear on the next positive edge of the clock pulse.

Counter counts states from 0 to 9.

∴ It is decade counter.

6. (b)

In successive approximation analog to digital converter, the conversion time is independent of input analog voltage.

7. (a)

$$\begin{aligned} \text{Maximum delay} &= \frac{t_{PHL} + t_{PLH}}{2} \cdot n \\ &= \frac{(22 + 15)}{2} \times 4 = 37 \times 2 = 74 \text{ nsec} \end{aligned}$$

8. (c)

$$\begin{aligned} F &= (A + D)(B \oplus C) + AD' \\ F &= (A + D)(B'C + BC') + AD' \\ F &= DB'C + DBC' + AB'C + ABC' + AD' \end{aligned}$$

Using redundancy theorem, $XY + \bar{X}Z + YZ = XY + \bar{X}Z$. Hence,

$$D(B'C) + D'A + A(B'C) = DB'C + D'A$$

Therefore,

$$F = DB'C + DBC' + D'A + ABC'$$

Again using redundancy theorem,

$$\begin{aligned} F &= DB'C + DBC' + D'A \\ F &= BCD + B'CD + AD' \end{aligned}$$

9. (b)

$$\bar{Z} = (P + A) \cdot (Q + \bar{A})$$

$$\bar{Z} = PQ + \bar{A}P + AQ$$


We have, $\bar{Z} = \overline{\bar{A} + B} = A \cdot \bar{B}$. Comparing, we get

$$P = 0, Q = \bar{B}$$

10. (c)

$$\begin{aligned} (2 \times 2048) + (6 \times 128) + 22 &= (2^1 \times 2^{11}) + [(2^2 + 2^1) \times 2^7] + (2^4 + 2^2 + 2^1) \\ &= 2^{12} + 2^9 + 2^8 + 2^4 + 2^2 + 2^1 \\ &= (1001100010110)_2 \end{aligned}$$

11. (a)

 

Let the output of 4×1 MUX is X ,

$$\therefore X = \bar{S}_1\bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1\bar{S}_0 I_2 + S_1 S_0 I_3$$

where, $S_1 = A, S_0 = B, I_1 = A$

$$X = \bar{A}\bar{B}(0) + \bar{A}B(A) + A\bar{B}(1) + AB(1)$$

$$= \bar{A}\bar{B} + AB$$

$$X = A$$

Output of 2×1 MUX, $Y = \bar{S}I_0 + SI_1$

where, $S = C; I_1 = X, I_0 = B$

$$\therefore Y = \bar{C}B + CX$$

$$Y = \bar{C}B + CA$$

12. (a)

Given, Full scale input voltage

$$V_{FS} = 10 \text{ V}$$

$$\text{resolution} = 5 \text{ mV}$$

We know that,

Resolution of ADC, $R = \frac{V_{FS}}{2^n - 1}$

$$5 \times 10^{-3} = \frac{10}{2^n - 1}$$

$$2^n - 1 = \frac{10}{5 \times 10^{-3}}$$

$$2^n - 1 = 2000$$



$$2^n = 2001$$

$$n = 11$$

[2 Marks, MCQ]

 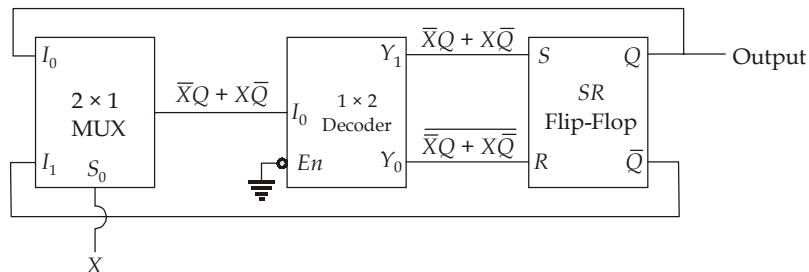13. (d)

The MUX in the circuit is working as an EX-OR gate and the 1×2 decoder as a NOT gate. Thus the circuit could be redrawn as



Thus, the circuit will function as a T -flip flop

$$\therefore \begin{aligned} S &= X \oplus Q_n \\ R &= \overline{X \oplus Q_n} \end{aligned}$$

For SR-flip flop, $Q_{n+1} = S + \bar{R}Q_n = (Q_n \oplus X) + \overline{(Q_n \oplus X)}Q_n = (X \oplus Q_n)(1 + Q_n)$
 $Q_{n+1} = X \oplus Q_n$

Excitation equation for T-flip flop.


14. (c)

	BQ			
A	00	01	11	10
0	0	0	0	0
1	1	1	0	1
	$A\bar{B}$			$A\bar{Q}$

$$\therefore Q^+ = A\bar{B} + A\bar{Q} = A(\bar{B} + \bar{Q}) = A\bar{B}\bar{Q}$$

15. (b)

Cycles of clock

 


So, value of counter output after five clock pulses will be number of times count has increased from 0 i.e., 2.

16. (c)

	D_0	D_1	Q_0	Q_1
	\bar{Q}_0	$Q_0 \oplus \bar{Q}_1$	0	0
→	1	1	1	1
	0	1	0	1
	1	0	1	0
	0	0	0	0

17. (c)

 


$$\begin{aligned} 100 &= \frac{32 \times 10^3}{2N \times 2^N} \\ 2N \times 2^N &= 32 \times 10 \\ 2 \times N \times 2^N &= 2^5 \times 5 \times 2 \\ \therefore N &= 5 \end{aligned}$$

Number of flip flops required = N for ripple counter + N for Johnson counter
 $5 + 5 = 10$

 18. (c)

First stage of the circuit behaves as inverter. Hence, the circuit can be redrawn as below:



19. (d)

$$F_1 = \bar{A}\bar{C} + \bar{B}C = \bar{A}\bar{C}(B + \bar{B}) + (A + \bar{A})\bar{B}C$$

$$= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C + \bar{A}\bar{B}C$$

$$= \Sigma m(0, 1, 2, 5)$$


$$F_2 = \bar{A}\bar{B} + B\bar{C} = \bar{A}\bar{B}(C + \bar{C}) + B\bar{C}(A + \bar{A})$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + AB\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$= \Sigma m(0, 1, 2, 6)$$

Hence, $F' = F_1 + F_2 = \Sigma m(0, 1, 2, 5, 6)$
 
$$F = \Sigma m(3, 4, 7) = \pi M(0, 1, 2, 5, 6)$$



20. (a)

When $F = 0$, the output of latch does not change i.e.,

$$Q^+ = Q$$

When $F = 1$, the latch is in the toggle mode i.e.,

$$Q^+ = \bar{Q}$$

Hence,

$$Q^+ = \bar{F}Q + F\bar{Q} = F \oplus Q$$

21. (a)

$$000 \xrightarrow{1^{\text{st}} \text{ CLK}} 100 \xrightarrow{2^{\text{nd}} \text{ CLK}} 010 \xrightarrow{3^{\text{rd}} \text{ CLK}} 101$$


The op-amp circuit is a R-2R Ladder DAC with digital input 101. Therefore,

$$V_0 = -\left(\frac{R_f}{R}\right) \times \left(\frac{V_{ref}}{2^3}\right) \times (\text{Decimal equivalent of } 101)$$


$$V_0 = \frac{-R}{R} \times \frac{5}{8} \times 5$$

$$V_0 = -3.125 \text{ V}$$

22. (c)

 


Using NAND Gates,

 

By grouping 0's in K-Map and writing F in maxterms, we get

$$F = (B + C) \cdot (\bar{B} + D)$$

 

Therefore, $m + n = 4 + 4 = 8$

23. (a)

There are three data paths (flop A to flop B, flop A to flop C, flop B to flop C). Setup time is used for deriving the maximum clock frequency.


Path A → B: $t_{\text{CLK}} > t_{\text{CLK} \rightarrow Q} + t_s = 9 + 2 \Rightarrow t_{\text{CLK}} > 11 \text{ ns}$

Path A → C: $t_{\text{CLK}} > t_{\text{CLK} \rightarrow Q} + t_s + t_{pd} = 9 + 2 + 4 \Rightarrow t_{\text{CLK}} > 15 \text{ ns}$

$$t_{\text{clk}} > 15 \text{ nsec}$$

$$f_{\text{max}} = \frac{1}{t_{\text{clk}} (\text{min})} = \frac{1}{15 \times 10^{-9}} = 66.67 \text{ MHz}$$

24. (a)

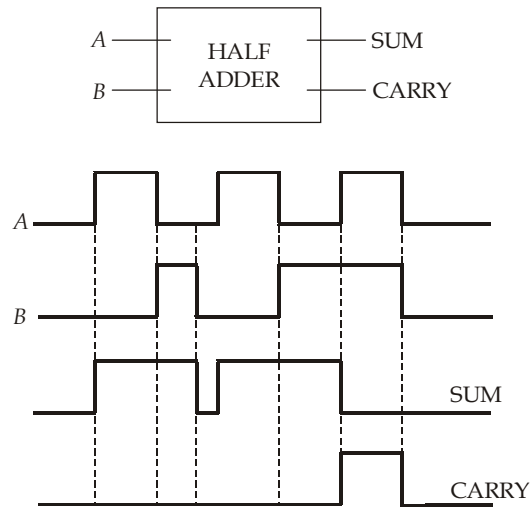

25. (c)

$$\text{Sum, } S = A \oplus B$$

$$\text{Difference} = S \oplus C = A \oplus B \oplus C$$

$$= (\overline{AB} + \overline{A\overline{B}})C + (\overline{AB} + A\overline{B})\overline{C}$$

$$= (\overline{A\overline{B}} + AB)C + (\overline{AB} + A\overline{B})\overline{C}$$

$$= \overline{A}\overline{B}C + ABC + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

$$\text{Borrow, } B = \overline{S}C$$

$$= (\overline{A \oplus B})C$$

$$= (AB + \overline{A}\overline{B})C$$

$$= ABC + \overline{A}\overline{B}C$$


$$B = \Sigma m(1, 7)$$

$$D = \Sigma m(1, 2, 4, 7)$$

and

26. (a)

Present State	Input	Next State	Output
S	L	S ⁺	P
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

 

27. (a)

Clk	Output
0	0 1 1 0
1	0 0 1 1
2	0 0 0 1
3	0 0 0 0

28. (a)

In serial-in/serial-out shift register, one bit of data is shifted one at a time. From Q_0 to Q_3 total 4-bit shifting takes place.

∴ The time delay between serial input, and the Q_3 output, $d = \frac{4}{200 \text{ kHz}} = 20 \times 10^{-6} \text{ sec.}$


29. (b)

Present state		FF Input		Next state	
Q_1	Q_0	T_1	T_0	Q_1^+	Q_0^+
0	0	0	1	0	1
0	1	1	1	1	0
1	0	1	0	0	0

Hence, the counter counts the sequence 00, 01, 10.

 30. (d)

The output signal can be plotted as below:



$$V_{\text{avg}} = \frac{1}{(T/2)} \int_{\tau}^{T/2} 1 \cdot dt = \frac{2}{T} \left[\frac{T}{2} - \tau \right] = 1 - \frac{2\tau}{T}$$

