



MADE EASY

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

POWER ELECTRONICS

ELECTRICAL ENGINEERING

Date of Test : 20/06/2026

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (c) | 13. (b) | 19. (d) | 25. (c) |
| 2. (c) | 8. (a) | 14. (c) | 20. (a) | 26. (b) |
| 3. (b) | 9. (d) | 15. (b) | 21. (a) | 27. (a) |
| 4. (b) | 10. (a) | 16. (d) | 22. (a) | 28. (b) |
| 5. (d) | 11. (b) | 17. (d) | 23. (b) | 29. (a) |
| 6. (b) | 12. (c) | 18. (c) | 24. (d) | 30. (b) |

DETAILED EXPLANATIONS

1. (b)

The fourier series of output voltage when single pulse modulation is used is,

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin \frac{n\pi}{2} \sin nd \sin n\omega t$$

$$V_{o1(max)} = \frac{4V_s}{\pi} \sin \frac{\pi}{2} \sin d$$

Since, the output voltage is free from 5th harmonic,

$$2d = \frac{2\pi}{5}$$

$$d = 36^\circ$$

$$V_{o1,max} = \frac{4 \times 400}{\pi} \cdot \sin \frac{\pi}{2} \sin(36^\circ)$$

$$V_{o1,max} = 299.35 \text{ V} \approx 300 \text{ V}$$

2. (c)

We know,

$$\text{String efficiency, } \eta = \frac{\text{Current rating of configuration}}{\text{Current rating of 1 SCR} \times \text{Number of SCR's in string}}$$

...(i)

$$\eta = \frac{960}{40 \times 30} = \frac{24}{30} = 0.80$$

$$\begin{aligned} \text{Derating factor} &= 1 - \text{string efficiency} \\ &= 1 - 0.8 = 0.2 \end{aligned}$$

For 50% decrease in rating factor

$$\text{New derating factor} = \frac{0.2 \times 50}{100} = 0.1$$

$$\therefore \text{New efficiency} = 0.9$$

Using equation (i), we get


$$0.9 = \frac{960}{40 \times n}$$

$$\Rightarrow n = \frac{960}{40 \times 0.9} = 26.66 \approx 27$$

$$\text{Decrease in no. of parallel SCR} = 30 - 27 = 3$$

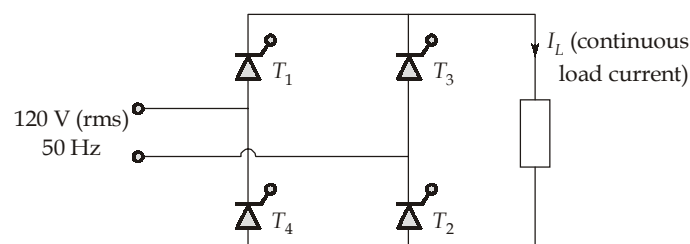3. (b)

For a single phase fully controlled bridge circuit



$$V_{\text{mean}} = \frac{2}{\pi} \times V_m \cos \alpha - 2V_T$$

Where, V_m is peak sinusoidal value, α is firing angle and V_T is thyristor voltage drop

For $V_m = 120\sqrt{2} \text{ V}$,

$$\alpha = 45^\circ$$

$$\begin{aligned} V_{\text{mean}} &= \frac{2}{\pi} \times 120\sqrt{2} \cos 45^\circ - 2 \times (1.5) \\ &= \frac{2}{\pi} \times 120\sqrt{2} \times \frac{1}{\sqrt{2}} - 3 = 73.39 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Peak value of voltage across each thyristor} &= V_{\text{max}} \\ &= 120\sqrt{2} = 169.71 \text{ V} \end{aligned}$$

4. (b)

For 1- ϕ full bridge converter, boundary condition

$$V_m \sin \omega t = E$$

$$\sin \omega t = \frac{E}{V_m}$$

or
$$\omega t = \sin^{-1} \left(\frac{E}{V_m} \right) = \sin^{-1} \left(\frac{100}{200} \right) = 30^\circ$$

In above case ωt is given as $100t$

\therefore When $100t > 30^\circ$ then thyristors are forward biased and can be triggered.

5. (d)


If factor of safety = 2

Allowable values:

$$I_p = \frac{250}{2} = 125 \text{ A}$$

$$\left(\frac{di}{dt} \right)_{\text{max}} = \frac{60}{2} = 30 \text{ A}/\mu\text{s}$$
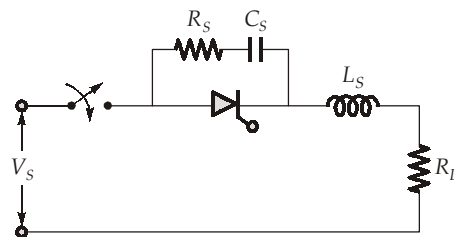
$$\left(\frac{dv}{dt} \right)_{\text{max}} = \frac{200}{2} = 100 \text{ V}/\mu\text{s}$$



Also know,
$$V_s = L_s \left(\frac{di}{dt} \right)$$

$$400 = L_s \left(\frac{60}{2} \right)$$


$$L_s = \frac{800}{60} = 13.33 \mu\text{H}$$

We know,
$$V_S = \frac{L_S}{R_S} \left(\frac{dV}{dt} \right)$$

So,
$$R_S = \frac{800}{60 \times 400} \times \frac{200}{2} = 3.33 \Omega$$

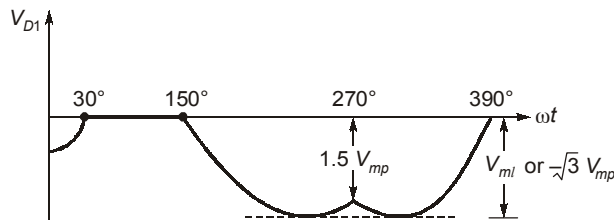6. (b)

PIV of a diode in 3-phase bridge rectifier is V_{ml} or $\sqrt{3} V_{mp}$.



7. (c)

$$f_{\max} = \frac{1}{4RC}$$

$$T_{\min} = 4RC = 1.2 \text{ sec}$$

8. (a)

Fourier series expressions of output voltage is

$$V_{o,n} = \sum_{n=1,3,5}^{\infty} \frac{4V_{dc}}{n\pi} \sin n\omega t \text{ V}$$

Harmonic factor for 5th harmonic

$$\text{H.F.} = \frac{V_{5,\text{rms}}}{V_{1,\text{rms}}} = \frac{\frac{4 \times 64}{\sqrt{2} \times 5\pi}}{\frac{4 \times 64}{\sqrt{2} \times \pi}} \times 100 = \frac{1}{5} \times 100$$

$$\text{H.F.} = 20\%$$

9. (d)

$$V_o = V_s D \left(\frac{N_2}{N_1} \right) = 200 \times 0.35 \times 2 = 140 \text{ V}$$

$$\Delta V_o = \frac{1-D}{8L_c C f^2} \times V_o = 218.8 \text{ mV}$$

10. (a)

In a single-phase sinusoidal bipolar PWM inverter, the harmonics are of the form $Kp \pm l$ (p is the carrier ratio) where K is odd and l is even or K is even and l is odd.

11. (b)

Maximum value of line voltage,

$$V_{ml} = \sqrt{2} V_l = 230\sqrt{2} \text{ V}$$

Average output voltage,

$$V_0 = \frac{3V_{ml}}{\pi} = 310.60 \text{ V}$$

$$V_0 = E + I_0 R$$

$$\frac{V_0 - E}{R} = I_0 = \frac{310.60 - 240}{8} = 8.82 \text{ A}$$

As current is ripple free,

$$I_{0r} = I_0 = 8.82 \text{ A}$$

RMS value of fundamental component of source current,

$$I_{s1} = \frac{2\sqrt{3}}{\pi} \times \frac{I_0}{\sqrt{2}}$$


RMS value of source current,

$$I_s = \left[\frac{I_0^2 \times 2\pi}{\pi \times 3} \right]^{1/2} = \sqrt{\frac{2}{3}} I_0$$

Current distortion factor,

$$CDF = \frac{I_{s1}}{I_s} = \frac{2\sqrt{3}I_0}{\sqrt{2}\pi} \times \frac{\sqrt{3}}{\sqrt{2}I_0} = \frac{3}{\pi} = 0.955$$


12. (c)

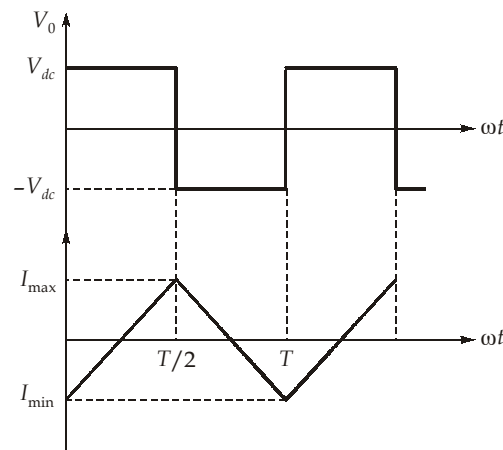

At $t = 0$,

S_1, S_2 : switches are closed

S_3, S_4 : switches are open

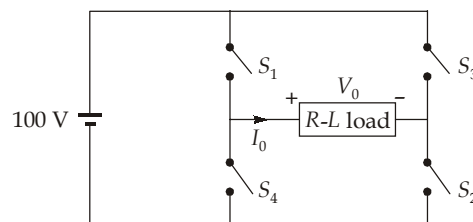

Output power,

$$P = I_{0r}^2 R$$

$$V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$

$$V_{\text{on-rms}} = \frac{2\sqrt{2}}{n\pi} V_s$$

$$Z_n = \sqrt{R^2 + (n\omega L)^2}$$

$$I_{\text{on-rms}} = \frac{V_{\text{on}}}{|Z_n|}$$

| n | $V_{\text{on-rms}}$ | $ Z_n $ | $I_{\text{on-rms}}$ |
|---------|-------------------------|-----------------------|-------------------------|
| $n = 1$ | $V_{o1} = 90 \text{ V}$ | $ Z_1 = 12.71\Omega$ | $I_{o1} = 7.08\text{A}$ |
| $n = 3$ | $V_{o3} = 30 \text{ V}$ | $ Z_3 = 25.59\Omega$ | $I_{o3} = 1.17\text{A}$ |
| $n = 5$ | $V_{o5} = 18 \text{ V}$ | $ Z_5 = 40.5\Omega$ | $I_{o5} = 0.44\text{A}$ |
| $n = 7$ | V_{o7} | | $I_{o7} = 0.23\text{A}$ |

$$I_{or} = \sqrt{I_{o1}^2 + I_{o3}^2 + I_{o5}^2 + I_{o7}^2} = 7.19 \text{ A}$$

$$P = (7.19)^2 \times 10 = 516.96 \text{ W}$$

13. (b)

Due to source inductance,

Average reduction in output voltage,

$$\begin{aligned} \Delta V_{d0} &= 4fL_s I_0 \\ &= 4 \times 50 \times (12 \times 10^{-3}) \times 16 = 38.4 \text{ V} \end{aligned}$$

$$\Delta V_{d0} = \frac{V_m}{\pi} [\cos \alpha - \cos(\alpha + \mu)]$$

As $\alpha = 0^\circ$ for diodes

$$38.4 = \frac{V_m}{\pi} [1 - \cos \mu]$$

$$38.4 = \frac{230\sqrt{2}}{\pi} [1 - \cos \mu]$$

$$\cos \mu = 1 - 0.37$$

$$\mu = \cos^{-1} 0.63$$

$$\mu = 50.95^\circ$$

∴ Conduction angle of diode

$$= 180^\circ + 50.95^\circ$$

$$= 230.95^\circ$$

14. (c)

Output voltage of Buck boost converter,

$$\begin{aligned} V_0 &= \frac{-D}{1-D} V_s = \frac{-0.3 \times 28}{1-0.3} \\ &= \frac{-0.3}{0.7} \times 28 = -12 \text{ V} \end{aligned}$$

Average current through inductor,

$$I_L = \frac{V_s D}{R(1-D)^2} = \frac{28 \times 0.3}{5(0.7)^2} = 3.42 \text{ A}$$

15. (b)

$$m_i = \text{modulation index} < 1$$

$$V_{01(\text{peak})} = \frac{m_i V_{dc}}{2} = \frac{0.8 \times 200}{2} = 80 \text{ V}$$

$$I_{01(\text{peak})} = \frac{V_{01\text{peak}}}{\sqrt{R^2 + (\omega L)^2}} = \frac{80}{\sqrt{8^2 + (12)^2}}$$

$$= \frac{80}{14.422} = 5.547 \approx 5.55 \text{ A}$$

16. (d)

$$\text{Total energy loss, } E_{\text{total}} = E_{t1} + E_{t2}$$

$$E_{t1} = \int_0^{t_1} V_i \cdot dt$$

As voltage across the switch is constant ie. 500 V

$$= 500 \int_0^{t_1} i \cdot dt = 500 \times \frac{1}{2} \times (0.4 \times 10^{-6}) \times 40 = 4 \text{ mJ}$$

Similarly $E_{t2} = \int_0^{t_2} V_i \cdot dt$

As switch current is constant ie. 30 A

$$E_{t2} = 30 \int_0^{t_2} V \cdot dt = 30 \times \frac{1}{2} \times (0.4 \times 10^{-6}) \times 500 = 3 \text{ mJ}$$

∴ total energy loss in process

$$= 4 \text{ mJ} + 3 \text{ mJ} = 7 \text{ mJ}$$

17. (d)

Assuming continuous conduction mode of buck boost converter

$$V_0 = \frac{\alpha}{1-\alpha} V_d$$


$$10 = \left(\frac{\alpha}{1-\alpha} \right) 15$$

$$\frac{\alpha}{1-\alpha} = 1.5$$

$$2.5 \alpha = 1$$

$$\alpha = 0.4$$

Checking for boundary conditions,

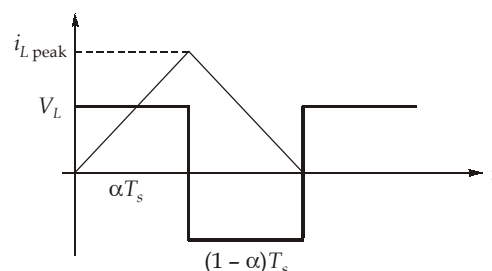

$$I_{OB, \max} = \frac{V_0}{2fL} = \frac{10}{2 \times 20 \times 10^3 \times 50 \times 10^{-6}} = 5 \text{ A}$$

$$I_{OB} = I_{OB, \max} (1 - \alpha)^2 = 5(1 - 0.4)^2 = 5 \times 0.36 = 1.8 \text{ A}$$

$$P_0 = V_0 I_0$$

$$10 = 10 I_0 \text{ or } I_0 = 1 \text{ A}$$

As output current is less than calculated I_{OB}

∴ Mode of operation : Discontinuous mode and value of duty ratio,

$$\alpha' = \frac{V_0 \sqrt{I_0}}{V_d \sqrt{I_{OB, \max}}} = \frac{10 \sqrt{1}}{15 \sqrt{5}} = 0.298$$

18. (c)

For given 3- ϕ rectifier,

$$V_{0, \text{rms}} = \frac{V_{ml}}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin \left(2\alpha + \frac{\pi}{3} \right) \right]^{1/2}$$

As $\alpha = \frac{\pi}{4} = 0.785$

$$= \frac{220\sqrt{2}}{2\sqrt{\pi}} \left[(2.618 - 0.785) + \frac{1}{2} \sin(90^\circ + 60^\circ) \right]^{1/2}$$

$$= \frac{220\sqrt{2}}{2\sqrt{\pi}} \left[(1.833) + \frac{1}{2} \times \frac{1}{2} \right]^{1/2} = 126.67 \text{ V}$$

The rms current $= \frac{V_{0, \text{rms}}}{R} = \frac{126.67}{20} = 6.33 \text{ A}$

Power consumed by the load,

$$= (6.33)^2 \times 20$$

$$= 801.38 \text{ W}$$


19. (d)

Current distortion factor for single phase semi converter,

$$\text{CDF} = \frac{2\sqrt{2} \cos\left(\frac{\alpha}{2}\right)}{\sqrt{\pi(\pi - \alpha)}}$$

$$= \frac{2\sqrt{2} \cos\left(\frac{45}{2}\right)}{\sqrt{\pi\left(\pi - \frac{\pi}{4}\right)}} = \frac{2.613}{\sqrt{\frac{3\pi^2}{4}}} = \frac{2.613}{2.721} = 0.960$$

20. (a)

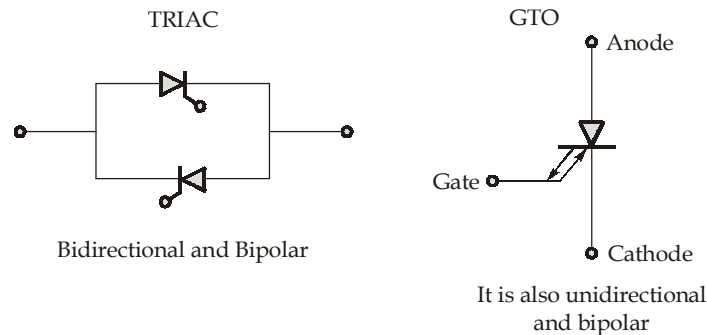

21. (a)

Average voltage with internal inductance (L_s)

$$V_{0 \text{ avg}} = \frac{3V_{mL}}{\pi} \cos \alpha - \frac{3\omega L_s I_0}{\pi} \quad \dots(i)$$

$$V_{0 \text{ avg}} = \frac{3V_{mL}}{\pi} \cos(\alpha + \mu) + \frac{3\omega L_s I_0}{\pi} \quad \dots(ii)$$

Where,

 $V_{mL} \rightarrow$ maximum line voltage $\alpha \rightarrow$ firing angle $\mu \rightarrow$ overlap angle $L_s \rightarrow$ internal inductance $I_0 \rightarrow$ load current

Subtract equation (i) from (ii),

$$\frac{3V_{mL}}{\pi} [\cos \alpha - \cos(\alpha + \mu)] = \frac{6\omega L_s I_0}{\pi}$$

$$\frac{3 \times 400 \times \sqrt{2}}{3.14} [\cos 36.86^\circ - \cos(36.86^\circ + \mu)] = \frac{6 \times 2\pi \times 50 \times 3.2 \times 10^{-3} \times 20}{3.14}$$

$$\cos 36.86^\circ - 0.07105 = \cos(36.86^\circ + \mu)$$

$$36.86^\circ + \mu = \cos^{-1} 0.729$$

$$\mu = 43.192^\circ - 36.86^\circ$$

$$= 6.33^\circ$$

$$\text{Fundamental power factor} = \cos\left(\alpha + \frac{\mu}{2}\right) = \cos\left(36.86^\circ + \frac{6.33^\circ}{2}\right) = 0.7657$$

22. (a)

The value of softness factor,

$$\text{S.F.} = \frac{t_b}{t_a} = 0.5 = \frac{1}{2}$$

$$t_a = 2 t_b$$

reverse recovery time,

$$t_{rr} = t_a + t_b = 8 \mu\text{sec}$$

$$3 t_b = 8 \mu\text{sec}$$

$$t_b = \frac{8}{3} \mu\text{sec}$$

$$t_a = 2t_b = \frac{16}{3} \mu\text{sec}$$

$$\frac{di}{dt} = \frac{I_{RM}}{t_a}$$

$$I_{RM} = t_a \frac{di}{dt} = \frac{16}{3} \mu\text{sec} \times 10 \text{ A}/\mu\text{sec} = \frac{160}{3} \text{ A}$$

$$Q_{RR} = \frac{1}{2} \times I_{RM} \times t_{rr}$$

$$= \frac{1}{2} \times \frac{160}{3} \times 8 = 213.33 \mu\text{C}$$

23. (b)


Rms value of fundamental component of the load current,

$$I_{01} = \frac{V_{01}}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{230}{\sqrt{4 + 4}}$$

$$I_{01} = 81.317 \text{ A}$$

$$\text{Phase angle, } \phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}(1)$$

$$\phi = 45^\circ$$

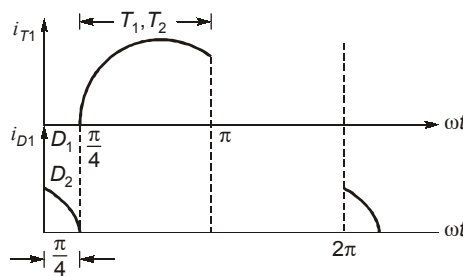

The rms value of diode current,

$$I_{D \text{ rms}} = \sqrt{\frac{1}{2\pi} \int_0^{\pi/4} (I_m \sin \omega t)^2 d\omega t} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi/4} \left[\frac{1 - \cos 2\omega t}{2} \right] d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \left[\frac{\pi}{8} - \left(\frac{\sin 2\omega t}{4} \right)_0^{\pi/4} \right]}$$

$$I_{D \text{ rms}} = I_m \cdot 0.1507$$

$$= \sqrt{2} \times 81.317 \times 0.1507$$

$$I_{D \text{ rms}} = 17.33 \text{ A}$$

24. (d)

$$\text{Output voltage } (V_0) = 36 \text{ V}$$

$$\text{Input voltage } (V_s) = 24 \text{ V}$$

For Buck-boost converter

$$V_0 = \frac{DV_s}{1-D}$$

$$36 = \frac{24D}{1-D}$$

$$\Rightarrow 36 - 36D = 24D$$

$$60D = 36$$

$$\Rightarrow D = 0.6$$

$$\Delta I_L = \frac{DV_s}{Lf}$$

At the boundary,

$$I_{L\text{avg}} - \frac{\Delta I_L}{2} = 0$$

$$\frac{I_0}{1-D} = \frac{\Delta I_L}{2}$$

$$\frac{144/36}{1-0.6} = \frac{0.6 \times 24}{2 \times 20 \times 10^3 \times L}$$

$$L = \frac{0.4}{4} \times \frac{0.6 \times 24}{2 \times 20 \times 10^3} = 36 \mu\text{H}$$

$$\left[I_{L\text{avg}} = \frac{I_0}{1-D} \right]$$

25. (c)

At rated condition,

$$P = 2.7 \text{ kW} = 2700 \text{ W}$$

$$V = 180 \text{ V}$$

$$I_{\text{rated}} = \frac{2700}{180} = 15 \text{ A}$$

$$\text{back emf} = E_b = 180 - 15 \times 0.5 = 172.5 \text{ V}$$

Now, at duty ratio of 0.6

$$V = 200 \times 0.6 = 120 \text{ V}$$

and at 70% of rated torque

$$\text{armature current} = 0.7 \times 15 = 10.5 \text{ A}$$

$$\begin{aligned} \text{back emf } (E'_b) &= 120 - 10.5 \times 0.5 \\ &= 114.75 \text{ V} \end{aligned}$$

We know,

$$\text{back emf} \propto \text{speed}$$

$$\frac{E_b}{E'_b} = \frac{N_{\text{rated}}}{N}$$

$$\frac{172.5}{114.75} = \frac{1200}{N}$$

$$N = 798.26 \text{ rpm}$$

26. (b)

It is single phase half bridge inverter

$$\frac{V_s}{2} = 20$$

or $V_s = 40 \text{ V}$

The fundamental component of output voltage is

$$V_{01} = \frac{2V_s}{\sqrt{2\pi}} = \frac{2 \times 40}{\sqrt{2} \times \pi} = 18 \text{ V}$$

$$Z = \sqrt{1^2 + 1^2} = \sqrt{2} \Omega$$

$$I_{01} = \frac{18}{\sqrt{2}} = 12.728 \text{ A}$$

$$P = I_{01}^2 R = (12.728)^2 \times 1$$

$$P = 162.00 \text{ W}$$

27. (a)

$$\% \text{ THD} = \frac{\sqrt{V_{0,\text{rms}}^2 - V_{1,\text{rms}}^2}}{V_{1,\text{rms}}} \times 100$$

$$\begin{aligned} \text{Rms value of output voltage} &= V_s \sqrt{\frac{2d}{\pi}} \\ \text{Pulse width, } 2d &= 150^\circ \quad (\text{given}) \\ d &= 75^\circ \end{aligned}$$

$$V_{0,\text{rms}} = V_s \sqrt{\frac{2 \times 75}{180}} = 0.9128 V_s$$

$$V_{01,\text{rms}} = \frac{4V_s}{\sqrt{2\pi}} \sin \frac{\pi}{2} \sin 75^\circ = 0.87 V_s$$

$$\% \text{ THD} = \frac{\sqrt{(0.9128 V_s)^2 - (0.87 V_s)^2}}{0.87 V_s} \times 100$$

$$\% \text{ THD} = 31.75\%$$

28. (b)

With T as the time of a cycle,

$$\text{The average power loss} = \frac{1}{T} \int_0^{2T/3} V_f \cdot I_f dt$$

$$P = \frac{2}{3} \cdot V_f \cdot I_f$$

and $V_f = 0.80 + (0.015 \times 50)$
 $V_f = 1.55 \text{ V}$

$\therefore P = \frac{2}{3} \times 1.55 \times 50 = 51.67 \text{ W}$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{2T/3} (50)^2 dt}$$

$$I_{\text{rms}} = 50\sqrt{\frac{2}{3}} = 40.82 \text{ A}$$

29. (a)

Hence it is mentioned in the given data that there is no losses.

$$V_0 = \frac{3V_{mL}}{\pi} \cos \alpha = E$$

Since, back emf $E \propto N$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$E_1 = 2E_2 \quad \left(\because N_2 = \frac{1}{2}N_1 \right)$$

So,
$$E_2 = \frac{E_1}{2} = \frac{V_0}{2} = 220 \text{ V}$$


$$\frac{3 \times \sqrt{2} \times 440}{\pi} \cos \alpha = 220$$

$$\cos \alpha = \frac{220 \times \pi}{3 \times \sqrt{2} \times 440} = 0.3702$$

Input power factor of the supply

$$= \frac{3}{\pi} \cos \alpha = \frac{3}{\pi} \times 0.3702 = 0.353$$

30. (b)

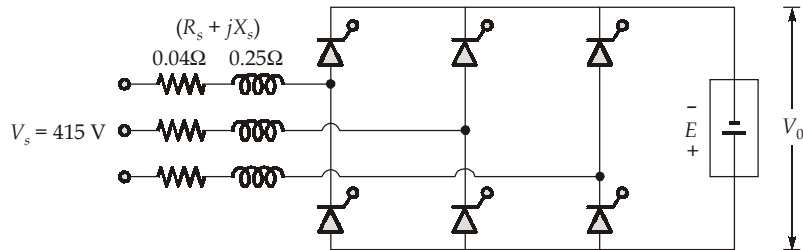

$$\begin{aligned} V_{0x} &= \frac{3V_{mL}}{\pi} \cos \alpha - 2I_0R_s - 2V_T - \frac{3\omega L_s I_0}{\pi} \\ &= \frac{3 \times \sqrt{2} \times 415}{\pi} \cos 145^\circ - (2 \times 80 \times 0.04) - (2 \times 1.5) - \left(\frac{3 \times 0.25 \times 80}{\pi} \right) \\ &= -487.5898 = -E \end{aligned}$$

$\therefore E = 487.5898 \approx 487.6 \text{ V}$

