



**MADE EASY**

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune

Web: [www.madeeasy.in](http://www.madeeasy.in) | E-mail: [info@madeeasy.in](mailto:info@madeeasy.in) | Ph: 011-45124612

# ANALOG CIRCUIT

## ELECTRONICS ENGINEERING

Date of Test : 09/06/2026

### ANSWER KEY >

1. (c)	7. (d)	13. (d)	19. (a)	25. (c)
2. (c)	8. (c)	14. (d)	20. (a)	26. (c)
3. (b)	9. (d)	15. (a)	21. (b)	27. (c)
4. (c)	10. (d)	16. (d)	22. (b)	28. (d)
5. (a)	11. (a)	17. (a)	23. (c)	29. (d)
6. (a)	12. (c)	18. (c)	24. (c)	30. (b)

## Detailed Explanations

1. (c)

% Regulation for a half wave rectifier can be given as

$$\begin{aligned} \% \text{ regulation} &= \frac{R_f}{R_L} \times 100 = \frac{12}{750} \times 100 \\ &= \frac{8}{5} = 1.6\% \end{aligned}$$

2. (c)

$$I_B = \frac{I_C}{\beta} = \frac{4 \times 10^{-3}}{50} = 0.08 \text{ mA}$$

$$V_C = R_B I_B + 0.7 \text{ V} \quad [ \because V_{CE} = V_C - V_E = V_C ]$$

$$\begin{aligned} R_B &= \frac{V_C - 0.7}{I_B} = \frac{2.5 - 0.7}{0.08} \times 10^3 \\ &= \frac{1.80}{0.08} \times 10^3 = \frac{180}{8} \times 10^3 = 22.5 \text{ k}\Omega \end{aligned}$$

$$I_0 = I_E = (1 + \beta)I_B = I_C + I_B = 4 + 0.08 = 4.08 \text{ mA}$$

$$R_B \propto \frac{1}{I_B} \propto \frac{1}{I_0}$$

3. (b)

Given that,

$$A_{OL} = 400$$

$$A_{CL} = 200$$

We know that,

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}} = 200$$

$$\Rightarrow \frac{400}{1 + \beta \times 400} = 200$$

$$1 + 400\beta = 2$$

$$\beta = \frac{1}{400} = 0.0025$$

4. (c)

Feedback topology	Input impedance	Output impedance
Voltage series	increases	decreases
Voltage shunt	decreases	decreases
Current series	increases	increases
Current shunt	decreases	increases

5. (a)

A 25-V peak signal across a 16- $\Omega$  load provides a peak load current of

$$I_L(P) = \frac{V_L(P)}{R_L} = \frac{25}{16} = 1.5625 \text{ A}$$

The dc value of the current drawn from the power supply is then

$$I_{dc} = \frac{2}{\pi}(I_L(P)) = \frac{2}{\pi} \times 1.5625$$

$$= 0.9947 \text{ A}$$

The input power delivered by the supply voltage is

$$P_i(\text{dc}) = V_{CC}I_{dc} = 40 \times 0.9947$$

$$= 39.788 \text{ W}$$

The output power delivered to the load is

$$P_o(\text{ac}) = \frac{V_L^2(P)}{2R_L} = \frac{25 \times 25}{2 \times 16} = 19.53125 \text{ W}$$

Efficiency of amplifier,

$$\% \eta = \frac{P_o(\text{ac})}{P_i(\text{dc})} \times 100 = \frac{19.53125}{39.788} \times 100$$

$$= 49.0883\%$$

$$\cong 49.09\%$$


6. (a)

By observation, we can say when


$$V_{in} \geq 2 \text{ V}; \text{ Diode is OFF.}$$

$$V_{in} < 2 \text{ V}; \text{ Diode is ON.}$$

Circuit when Diode is OFF:

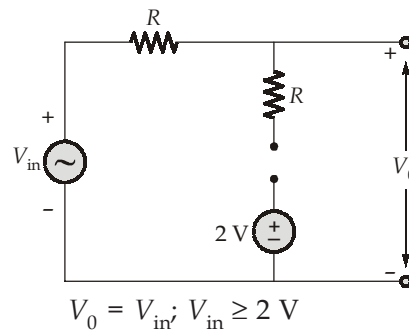

Circuit when Diode is ON;

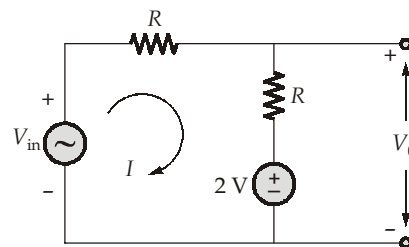

$$I = \frac{V_{in} - 2}{2R}$$

$$V_0 = 2 + I \cdot R$$

$$= 2 + \left( \frac{V_{in} - 2}{2R} \right) \cdot R = 2 + \frac{V_{in} - 2}{2}$$

$$V_0 = \frac{V_{in}}{2} + 1; V_{in} < 2 \text{ V}$$

Now,

7. (d)

We have;

$$\alpha = 0.98$$

 $\alpha =$  current gain in CB mode.

 $\therefore$  Current gain in the CC mode ( $\gamma$ )

$$\gamma = 1 + \beta$$

where;

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{0.02} = 49$$

 $\therefore$ 


$$\gamma = 1 + 49 = 50$$

8. (c)

For MOS to conduct,  $V_{GS} > V_T$ Here,  $V_{GS} = 1$  V and  $V_T = 2$  V

Hence, MOS is in CUT-OFF region.

Now, modified circuit will be;

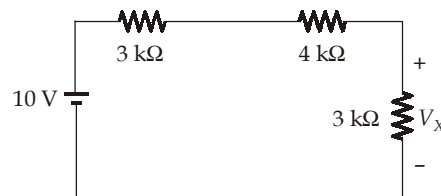
 $\therefore$ 

$$V_X = 10 \times \frac{3}{3 + 4 + 3}$$

$$= 3 \text{ Volt}$$

9. (d)

For saturation region;

$$V_{SD} \geq V_{SG} - |V_T|$$

$$5 - I(2) \geq 5 - 1$$

$$5 - 2I \geq 4$$

$$1 \geq 2I$$

$$I \leq 0.5 \text{ mA} \Rightarrow \text{maximum value of 'I' will be } 0.5 \text{ mA}$$

10. (d)

Assume Diode is ON;

$$\text{Gate voltage } (V_G) = 2 - 0.7$$

$$= 1.3 \text{ Volt}$$

We know, current into gate terminals of MOS is not possible.

$$V_G < V_D$$

 $\Rightarrow$  Flow of current into the gate terminals of MOS through the 10  $\Omega$ . resistor which is not possible.

Hence, diode will be OFF.

 $\therefore$ 

$$V_G = V_D = 1.5 \text{ Volt} \Rightarrow \text{MOS is in saturation.}$$

Now,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{1}{2} \times 0.4 \times (1.5 - 0.3)^2$$

$$= 0.29 \text{ mA}$$

11. (a)

Transistor  $Q_1$  is in saturation region (as  $V_{DS} = V_{GS} > V_{GS} - V_T$ );

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$0.8 = \frac{1}{2} \times 0.2 \times 10 \times (V_{GS} - 0.6)^2$$

$$0.8 = (V_{GS} - 0.6)^2$$

$$0.89 = V_{GS} - 0.6$$

$$V_{GS} = 1.5 \text{ Volt}$$

Now;

$$I_D = \frac{V_{DD} - V_{GS}}{R_X}$$

$$0.8 = \frac{10 - 1.5}{R_X}$$

$$R_X = 10.62 \text{ k}\Omega$$

12. (c)

For non-interacting stages,

$$f'_H = f_H \sqrt{(2^{1/n} - 1)}$$

$$= 30 \times 10^3 \sqrt{2^{1/3} - 1}$$

$$= 30 \times 10^3 \times 0.5098 = 15.2947 \times 10^3$$

$$= 15.2947 \text{ kHz}$$

$$f'_L = \frac{f_L}{\sqrt{2^{1/n} - 1}} = \frac{25}{\sqrt{2^{1/3} - 1}}$$

$$= 25 \times 1.9614 = 49.036 \text{ Hz}$$

13. (d)

Given data,

$$V_1 = 80 \mu\text{V}; V_2 = -40 \mu\text{V}$$

$$\text{CMRR} = 50$$

$$A_{dM} = 40 \times 10^3$$

$$\text{CMMR} = 50 = \frac{A_{dM}}{A_{cM}}$$

$$A_{cM} = \frac{40000}{50} = 800$$

$$V_{dM} = V_1 - V_2 = [80 - (-40)] \times 10^{-6}$$

$$= 120 \times 10^{-6} \text{ V}$$

$$V_{cM} = \frac{V_1 + V_2}{2} = \frac{80 - 40}{2} = 20 \mu\text{V}$$

$$V_0 = V A_{dM} + A_{cM} V_{cM}$$

$$= 120 \times 10^{-6} \times 4 \times 10^4 + 800 \times 20 \times 10^{-6}$$

$$= 480 \times 10^{-2} + 1.6 \times 10^{-2} = 481.6 \times 10^{-2}$$

$$= 4.816 \text{ V}$$

14. (d)

The common mode gain of BJT differential amplifier is given as

$$A_{cm} = \frac{-R_C}{2R_E}$$

Since, the resistance of ideal current source is very high, hence  $A_{cm}$  decreases and the CMRR of the amplifier is increased.

15. (a)


We have,

$$V_{in} = 16 \sin \omega t \text{ V}$$

$$(V_{in})_{peak} = 16 \text{ V}$$

When input voltage is at peak value, diode  $D$  will be ON and peak current will flow through the diode.

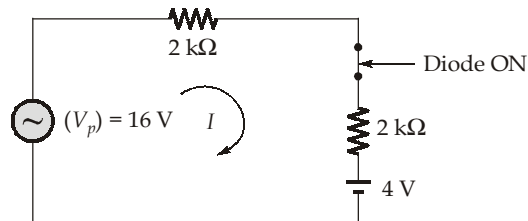Now, simplified circuit with peak input voltage is drawn below:



$$\therefore I = \frac{16 - 4}{2 + 2} = \frac{12}{4} = 3 \text{ mA}$$

$\therefore R_1$  and  $R_2$  have equal resistance value.

$$\therefore \text{Current through } R_1 = \frac{I}{2} = \frac{3}{2} = 1.5 \text{ mA}$$

16. (d)

$\therefore \beta$  is very large, base current can be assume to be zero.

$$\text{Voltage at base of BJT is } V_B = V_Z + V_{BE}$$

$$V_B = 7.3 + 0.7 = 8 \text{ volt}$$

$$\text{Now; } V_B = V_0 \times \frac{2}{2+3}$$

$$8 = V_0 \times \frac{2}{5}$$

$$V_0 = 20 \text{ volt}$$

$$\therefore I_{peak} = \frac{(V_{in})_{peak} - V_0}{2} \text{ mA}$$

$$= \frac{30 - 20}{2} = \frac{10}{2} = 5 \text{ mA}$$

17. (a)

For maximum symmetrical swing, operating point should be at middle of load line.

$$\text{i.e., } V_{CE} = \frac{V_{CC}}{2} = \frac{10}{2} = 5 \text{ V}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 5}{0.5} = 10 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{10}{100} = 0.1 \text{ mA}$$

$$\text{Now; } R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{10 - 0.7}{0.1 \text{ mA}} = 93 \text{ k}\Omega$$

18. (c)

We know;

$$I_C = \alpha \cdot I_E + I_{co}$$

$$= 0.98 \times 1 + 10 \times 10^{-3}$$

$$= 0.99 \text{ mA}$$

But;

$$I_E = I_C + I_B$$

$$1 = 0.99 + I_B$$

∴

$$I_B = 0.01 \text{ mA} = 10 \mu\text{A}$$

19. (a)

From given circuit:

$$V_G = V_D = 5 \text{ V}$$

Now;

$$I_D = \frac{V_{DD} - V_D}{10} = \frac{15 - 5}{10}$$

$$= 1 \text{ mA}$$

Now;

$$V_S = I_D \cdot (1) - 2$$

$$= -1 \text{ V}$$

∴

$$V_{DS} = 6 \text{ V and } V_{GS} = 6 \text{ V}$$

Hence, MOS is in saturation region.

We know;

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$I_D = \frac{1}{2} K_n (V_{GS} - V_T)^2$$

$$\text{Transconductance } (g_m) = \frac{\partial I_D}{\partial V_{GS}} = \frac{2I_D}{V_{GS} - V_T}$$


$$= \frac{2 \times 1}{6 - 1} = \frac{2}{5} \text{ m}\mathcal{U}$$

$$g_m = 0.4 \text{ m}\mathcal{U} = 0.4 \text{ mS}$$

20. (a)

With DC source; capacitor act as open circuit.

Now, given circuit can be modified as:

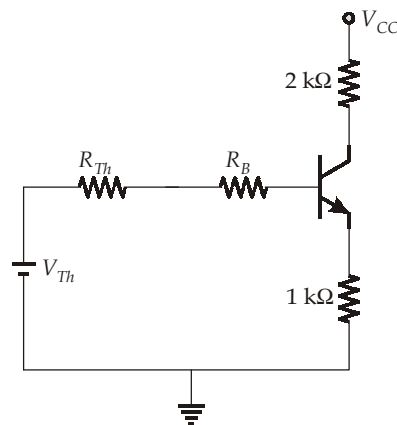

$$V_{Th} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

$$R_{Th} = \frac{R_1 \cdot R_2}{R_1 + R_2} = 5 \text{ k}\Omega$$

Stability factor because of  $I_{CO}$  is defined as:

$$S = \frac{\partial I_C}{\partial I_{CO}} = \frac{1 + \beta}{1 - \beta \left( \frac{\partial I_B}{\partial I_C} \right)}$$

Applying KVL in the base-emitter loop,

$$V_{Th} - I_B (R_{Th} + R_B) - (I_B + I_C) = 0$$

$$V_{Th} - I_B (R_{Th} + R_B + 1) - I_C = 0$$

Differentiating w.r.t  $I_C$  we get

$$\frac{\partial I_B}{\partial I_C} = \frac{-1}{R_{Th} - R_B + 1}$$

The stability factor, is thus given as

$$S = \frac{1 + \beta}{1 + \beta \left( \frac{1}{R_{Th} + R_B + 1} \right)}$$

$$20 = \frac{51}{1 + 50 \left( \frac{1}{5 + R_B + 1} \right)}$$

$$1 + \frac{50}{6 + R_B} = \frac{51}{20}$$

$$\frac{50}{6 + R_B} = \frac{31}{20}$$

$$1000 = 186 + 31R_B$$

$$R_B = 26.25 \text{ k}\Omega$$

21. (b)

$$\frac{1}{f_H} = 1.1 \sqrt{\frac{1}{f_1^2} + \frac{1}{f_2^2} + \dots + \frac{1}{f_n^2}}$$

$$t_r = 1.1 \sqrt{t_{r1}^2 + t_{r2}^2}$$

$$t_r = 1.1 \sqrt{(0.35)^2 + (0.43)^2}$$

$$t_r = 0.61 \text{ msec}$$

22. (b)

Applying superposition theorem to determine the output, we have

$$\begin{aligned} V_o &= -\frac{R_2}{R_1} \cdot V_1 + \left( \frac{R_4}{R_3 + R_4} \right) \cdot \left( 1 + \frac{R_2}{R_1} \right) \cdot V_2 \\ &= -10V_1 + 10.0833V_2 \end{aligned}$$

Now, the differential input voltage is given as

$$V_d = V_2 - V_1$$

and common mode input voltage,

$$V_c = \frac{V_1 + V_2}{2}$$

Thus,

$$V_1 = V_c - \frac{V_d}{2}$$

$$V_2 = V_c + \frac{V_d}{2}$$

∴

$$V_o = (10.0833) \left[ V_c + \frac{V_d}{2} \right] - 10 \left[ V_c - \frac{V_d}{2} \right]$$

$$V_o = 10.042 V_d + 0.0833 V_c$$

Comparing the equation from the standard result,

i.e.  $V_o = A_d V_d + A_c V_c$

We get,  $A_d = 10.042$

$$A_c = 0.0833$$

∴  $(\text{CMRR})_{\text{dB}} = 20 \log_{10} \left[ \frac{10.042}{0.0833} \right] = 41.63 \text{ dB}$

23. (c)

For FET Colpitt's oscillator, the frequency of oscillation is given by,

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{L} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{9.2 \times 10^{-6}} \left[ \frac{1}{10 \times 10^{-6}} + \frac{1}{1.32 \times 10^{-6}} \right]}$$

$$f_0 = 48.59 \text{ kHz}$$

24. (c)

The output of op-amp is connected to RC circuit which acts as differentiator. The output of differentiator is connected to diode. So, the circuit generates positive pulses and acts as a zero crossing detector.

25. (c)

The given circuit is a Wien Bridge oscillator.

Frequency of sinusoidal oscillation  $f = \frac{1}{2\pi \sqrt{R_s C_s R_p C_p}}$

$$= \frac{1}{2\pi \sqrt{11 \times 22 \times 0.01 \times 0.047 \times 10^{-6}}}$$

$$= 471.9 \text{ Hz}$$


Gain of non inverting amplifier

$$|A| \geq 1 + \frac{R_s}{R_p} + \frac{C_p}{C_s}$$


$$|A| \geq 1 + \frac{11}{22} + \frac{0.01}{0.047}$$

$$|A| \geq 1.713$$

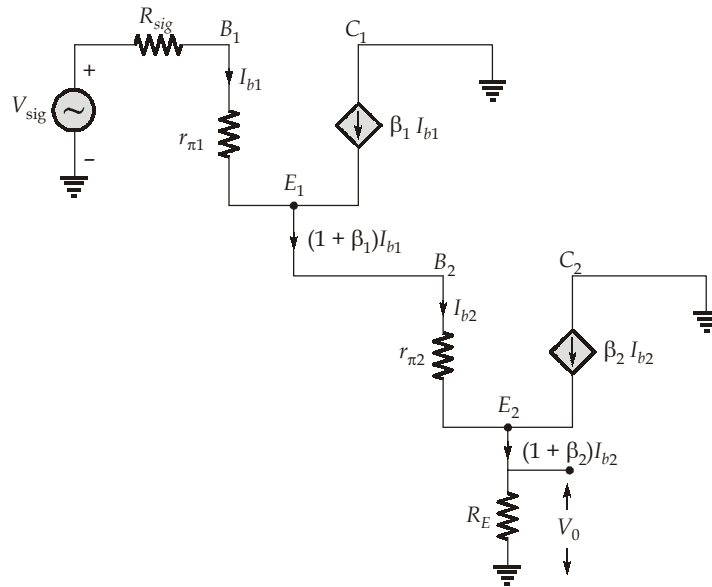26. (c)  
The small signal equivalent of the given circuit can be drawn as



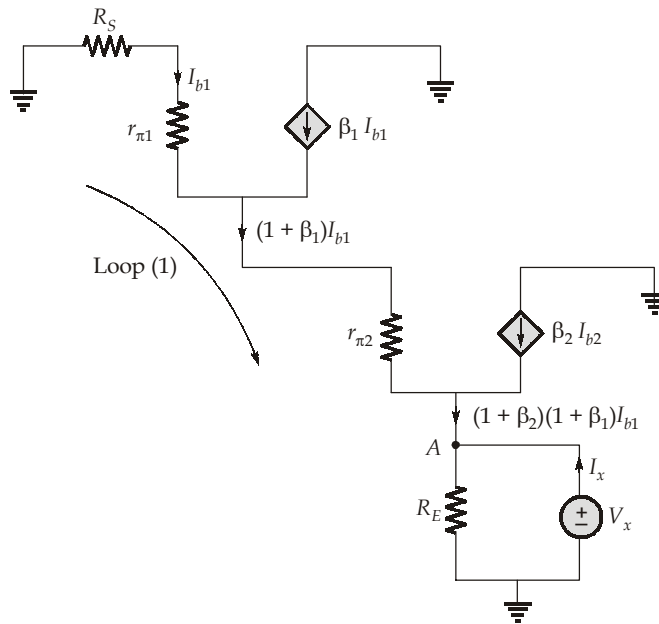For  $R_{out}$  disable the input source and apply test signal. Therefore, the modified circuit is given as;



Applying KVL in loop (1), we get,

$$(R_s + r_{\pi 1})I_{b1} + r_{\pi 2}(1 + \beta_1)I_{b1} + V_x = 0$$

$$\therefore I_{b1} = \frac{-V_x}{R_s + r_{\pi 1} + r_{\pi 2}(1 + \beta_1)} \quad \dots(1)$$


Applying Nodal analysis at node A we get,

$$\frac{V_x}{R_E} = I_x + (1 + \beta_1)(1 + \beta_2)I_{b1}$$

$$V_x \left[ \frac{1}{R_E} + \frac{(1 + \beta_1)(1 + \beta_2)}{R_s + r_{\pi 1} + r_{\pi 2}(1 + \beta_1)} \right] = I_x \quad \text{[from (1)]}$$

$$\therefore R_{out} = \frac{V_x}{I_x} = R_E \parallel \left[ \frac{(R_s + r_{\pi 1})}{(1 + \beta_1)(1 + \beta_2)} + \frac{r_{\pi 2}}{(1 + \beta_2)} \right]$$

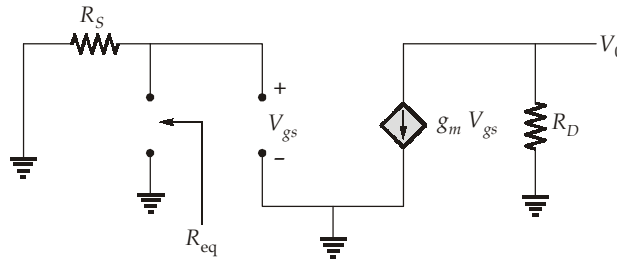27. (c)  
The equivalent resistance seen from  $C_{in}$  is given as



$$\therefore R_{eq} = R_S = 1.3 \text{ k}\Omega$$

$$\text{The pole frequency } f = \frac{1}{2\pi R_{eq} C_{in}}$$

$$\therefore f = \frac{1}{2\pi \times 1.3 \times 10^3 \times 9 \times 10^{-9}} = 13.6 \text{ kHz}$$

28. (d)  
The gain with feedback amplifier at high frequency is given as,

$$A_f = \frac{A}{1 + \beta A}$$

where,

$$A = \frac{A_0}{1 + \frac{j\omega}{\omega_2}} \quad \dots(\text{given})$$

$$\therefore A_f = \frac{\frac{A_0}{1 + j \frac{\omega}{\omega_2}}}{1 + \beta \frac{A_0}{1 + j \frac{\omega}{\omega_2}}}$$

$$\therefore A_f = \frac{A_0}{1 + \frac{j\omega}{\omega_2} + \beta A_0} = \frac{A_0}{(1 + \beta A_0) \left[ 1 + \frac{j\omega}{\omega_2(1 + \beta A_0)} \right]}$$

$$A_f = \frac{\frac{A_0}{(1 + \beta A_0)}}{1 + \frac{j\omega}{\omega_2(1 + \beta A_0)}} = \frac{A_{f0}}{1 + \frac{j\omega}{\omega_{2f}}}$$

where  $\omega_{2f} = \omega_2(1 + \beta A_0)$  ...(1)

Substituting  $\omega_{2f} = 10^6$  rad/sec,  $\omega_2 = 10^5$  rad/sec and  $A_0 = 10000$  in equation (1), we get


$$10^6 = 10^5 [1 + \beta \times 10000]$$

$$10 - 1 = \beta \times 10000$$

$$\beta = \frac{9}{10000} = 0.0009$$

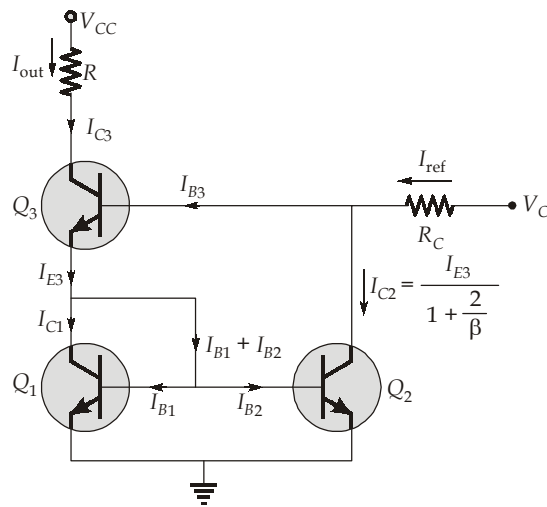29. (d)

The given circuit diagram is Wilson current mirror:



From the figure,

$$I_{E3} = I_{C1} + I_{B1} + I_{B2}$$

Since,  $Q_1$  and  $Q_2$  are perfectly matched. $\therefore$ 

$$I_{C1} = I_{C2} \text{ and } I_{B1} = I_{B2}$$

 $\therefore$ 

$$I_{E3} = \left(1 + \frac{2}{\beta}\right) I_{C1} = \left(1 + \frac{2}{\beta}\right) I_{C2}$$

 $\therefore$ 

$$I_{C2} = \frac{I_{E3}}{1 + \frac{2}{\beta}} \quad \dots(1)$$

$$I_{\text{ref}} = I_{B3} + I_{C2}$$

and

$$I_{\text{ref}} = I_{B3} + \frac{I_{E3}}{1 + \frac{2}{\beta}} \quad \text{[from (1)]}$$

 $\therefore$ 

$$I_{\text{ref}} = \frac{I_{C3}}{\beta} + \left(\frac{1}{1 + \frac{2}{\beta}}\right) \left(\frac{1 + \beta}{\beta}\right) I_{C3}$$

 $\therefore$ 

$$I_{\text{ref}} = I_{C3} \left[ \frac{1}{\beta} + \frac{1 + \beta}{2 + \beta} \right] \quad \dots(2)$$

We have,

$$I_{C3} = I_{\text{out}} \quad \text{[from the figure]}$$

 $\therefore$ 


$$I_{\text{ref}} = I_{\text{out}} \left[ \frac{2 + \beta + \beta + \beta^2}{\beta(2 + \beta)} \right]$$

$$I_{\text{out}} = \frac{I_{\text{ref}}}{1 + \frac{2}{\beta(2 + \beta)}}$$

 $\therefore$ 

$$\frac{I_{\text{out}}}{I_{\text{ref}}} = \frac{1}{1 + \frac{2}{\beta(2 + \beta)}}$$

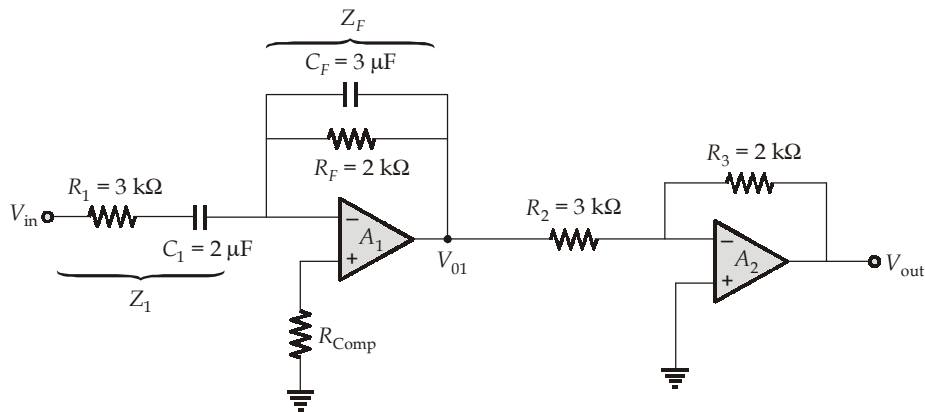30. (b)  
The given op-amp based circuit is



$A_1$  is practical differentiator and  $A_2$  is inverting amplifier and  
 $R_1 C_1 = R_F C_F$  ... (1)

For  $A_1$  op-amp, the transfer function is given as

$$\frac{V_{01}}{V_{in}} = \frac{-Z_F}{Z_1}$$

where,  $Z_F = \frac{R_F}{1 + sR_F C_F}$  and  $Z_1 = \frac{sR_1 C_1 + 1}{sC_1}$

$$\therefore \frac{V_{01}}{V_{in}} = \frac{-sR_F C_1}{(1 + sR_F C_F)(1 + sC_1 R_1)}$$

$$\therefore \frac{V_{01}}{V_{in}} = \frac{-sR_F C_1}{(1 + sR_1 C_1)^2} \quad \dots[\text{from (1)}] \quad \dots(2)$$

For  $A_2$  op-amp, the transfer function  $\left(\frac{V_0}{V_{01}}\right)$  is given as

$$\frac{V_0}{V_{01}} = \frac{-R_3}{R_2} \quad \dots(3)$$

The overall transfer function is given as

$$\frac{V_0}{V_{in}} = \frac{V_{01}}{V_{in}} \times \frac{V_0}{V_{01}} = - \left[ \frac{sR_F C_1}{(1 + sR_1 C_1)^2} \right] \left[ \frac{-R_3}{R_2} \right] \quad \text{from (2) and (3)}$$

$$\left| \frac{V_0}{V_{in}} \right| = \frac{R_3}{R_2} \left[ \frac{\omega R_F C_1}{1 + (\omega R_1 C_1)^2} \right] \quad \dots(4)$$

Substituting the given values in equation (4) we get,

$$\left| \frac{V_0}{V_{in}} \right| = \left( \frac{2}{3} \right) \left[ \frac{100 \times 2 \times 10^3 \times 2 \times 10^{-6}}{1 + (100 \times 3 \times 10^3 \times 2 \times 10^{-6})^2} \right]$$

$$\left| \frac{V_0}{V_{in}} \right| = \frac{10}{51}$$

