

**MADE EASY**

Leading Institute for IES, GATE &amp; PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune

Web: [www.madeeasy.in](http://www.madeeasy.in) | E-mail: [info@madeeasy.in](mailto:info@madeeasy.in) | Ph: 011-45124612

# ELECTRICAL & ELECTRONICS MEASUREMENTS

## ELECTRICAL ENGINEERING

Date of Test : 18/07/2026

### ANSWER KEY ➤

- |        |         |         |         |         |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (b)  | 13. (c) | 19. (c) | 25. (d) |
| 2. (d) | 8. (c)  | 14. (b) | 20. (b) | 26. (b) |
| 3. (c) | 9. (b)  | 15. (c) | 21. (d) | 27. (d) |
| 4. (b) | 10. (a) | 16. (b) | 22. (b) | 28. (d) |
| 5. (c) | 11. (c) | 17. (b) | 23. (d) | 29. (d) |
| 6. (b) | 12. (a) | 18. (a) | 24. (a) | 30. (b) |

1. (b)

Given, meter constant = 450 rev per kWhr

Load current = 12 A at 0.8 p.f. lag

Voltage rating = 230 V

Total power consumed by load,

$$230 \times 12 \times 0.8 = 2208 \text{ W or } 2.208 \text{ kW}$$

In one hour no. of revolution =  $2.208 \times 450 = 993.60$  rev per hour


$$\text{No. of revolutions in a minute} = \frac{993.60}{60} = 16.56 \text{ rpm}$$

2. (d)

We know,

$$\frac{f_y}{f_x} = \frac{\text{No. of Horizontal tangencies}}{\text{No. of Vertical tangencies}}$$

$$\frac{4200}{700} = \frac{6}{1}$$

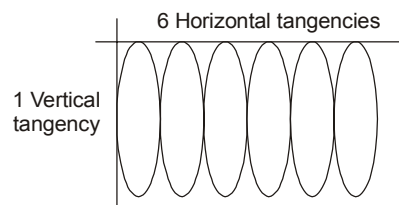


Hence option (d) is correct.

3. (c)

We can represent ammeter setup as

$$\begin{aligned} \text{Multiplying factor, } m &= 1 + \frac{R_m}{R_{sh}} = 1 + \frac{2000}{0.4} \\ &= 50001 \end{aligned}$$
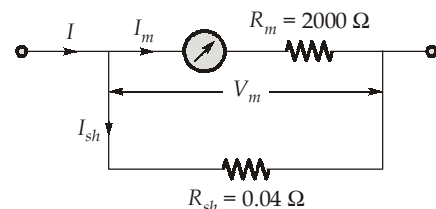
$$\text{Meter current, } I_m = \frac{V_m}{R_m} = \frac{1}{2000} = 0.5 \text{ mA}$$



4. (b)

Value of resistor,  $R_1 = 2 \times 10^4 \pm 7\%$ 

$$\begin{aligned} \text{i.e. } R_1 &= 20000 \pm \frac{7}{100} \times 20000 \\ &= (20000 \pm 1400) \Omega \end{aligned}$$

Value of resistor,  $R_2 = 6 \times 10^3 \pm 4\%$ 

$$= 6000 \pm \frac{6000 \times 4}{100} = (6000 \pm 240) \Omega$$

Series network =  $(26000 \pm 1640) \Omega$ 

$$\text{The tolerance limit} = \frac{1640}{26000} \times 100 = 6.307 \approx 6.31\%$$

5. (c)

Limiting error can be calculated using

$$P = I^2 R$$

Taking log on both sides

$$\ln P = 2 \ln I + \ln R$$

$$\frac{\partial R}{R} = \frac{\partial P}{P} - \frac{2\partial I}{I}$$

$$\begin{aligned} \text{So limiting error, } \frac{\partial R}{R} &= \pm \left( \frac{\partial P}{P} + \frac{2\partial I}{I} \right) \\ &= \pm 0.02 \pm 2(0.03) \\ &= \pm 0.02 \pm 0.06 = 0.08 \text{ or } 8\% \end{aligned}$$

6. (b)

We know,  $\theta = \frac{GI}{K} = \frac{NBAI}{K}$

For

|           |                |                |
|-----------|----------------|----------------|
| 1°C rise  | 0.05% decrease | 0.03% decrease |
| 10°C rise | 0.5% decrease  | 0.3% decrease  |

So change in K.

$$\begin{aligned} K' &= K - 0.5\% \text{ of } K \\ &= K - \frac{0.5}{100} K = K - \frac{5}{1000} K \end{aligned}$$

$$K' = \frac{995 K}{1000}$$

$$B' = B - 0.3\% \text{ of } B = \frac{997 B}{1000}$$

$$\theta' = \frac{NB'A}{K'} I = \frac{(0.997) NBA}{(0.995) K} I$$

$$\theta' = 1.002 \theta$$

$$\begin{aligned} \therefore \text{Change in reading} &= \frac{\theta' - \theta}{\theta} \times 100 \\ &= \frac{0.002\theta}{\theta} \times 100 = 0.2\% \text{ increase} \end{aligned}$$

7. (b)

The multiplication factor,

$$m = \frac{I}{I_m} = \frac{200 \text{ mA}}{100 \mu\text{A}} = 2000$$

$\therefore$  The shunt resistance required,

$$R_s = \frac{R_m}{m-1} = \frac{500}{2000-1} = \frac{500}{1999} = 0.250 \Omega$$

8. (c)

We know

$$R_s = S_{dc} \times \text{Range}_{dc} - R_m$$

and

$$S_{dc} = \frac{1}{I_{fs}} = \frac{1}{1 \text{ mA}} = \frac{1 \text{ k}\Omega}{\text{V}}$$

$$R_s = \frac{1 \text{ k}\Omega}{\text{V}} \times \frac{0.45 E_{\text{rms}}}{1} - R_m$$

$$= \frac{1 \text{ k}\Omega}{\text{V}} \times \frac{0.45 \times 20 \text{ V}}{1} - 300$$

$$= 9000 - 300 = 8700 \Omega = 8.7 \text{ k}\Omega$$

9. (b)

As instrument calibrated to measure dc,

Current taken by meter with 120 V dc

$$= \frac{120}{240} = 0.5 \text{ A}$$

Current taken by meter at 120 V, 50 Hz supply,

$$I_1 = \frac{120}{251.56} = 0.477 \text{ A}$$

Deflection is proportional to operating current,

Hence reading in with 120 V 50 Hz ac

$$\text{AC reading} = \frac{120 \times 0.477}{0.50} = 114.5 \text{ V}$$

10. (a)

At 50 Hz supply, impedance of the instrument circuits,

$$Z = \frac{V_{ac}}{I_{ac}} = \frac{500}{0.1} = 5000 \Omega$$

$$R = \sqrt{Z^2 - X_L^2} = \sqrt{(5000)^2 - (2\pi \times 50 \times 0.8)^2} = 4993.7 \Omega$$

When connected to 300 V dc,

$$\text{Instrument current, } I_{dc} = \frac{V_{dc}}{R} = \frac{300}{4993.7} = 0.06008 \text{ A}$$

Reading of instrument when connected to 300 V dc,

$$= \frac{V_{dc}}{I_{ac}} \times I_{dc} = \frac{500}{0.1} \times 0.06008 = 300.4 \text{ V}$$

11. (c)

Phase angle error,

$$\theta = \frac{180}{\pi} \left[ \frac{I_m \cos \delta - I_e \sin \delta}{n I_s} \right]$$

12. (a)

At balance condition,  $Z_1 Z_4 = Z_2 Z_3$

$$\left( \frac{R_1}{1 + j\omega C_1 R_1} \right) R_4 = \left( R_2 - \frac{j}{\omega C_2} \right) R_3$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} + \frac{C_1}{C_2} + j \left( \omega C_1 R_2 - \frac{1}{\omega C_2 R_1} \right)$$

Equating the real and imaginary parts

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} + \frac{C_1}{C_2}$$

and  $\omega C_1 R_2 - \frac{1}{\omega C_2 R_1} = 0$

$$\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

As given in question,  $R_2 = R_1$

and  $C_2 = C_1$

$$\omega = \frac{1}{RC}$$

and  $f = \frac{1}{2\pi RC}$

Hence option (a) is correct.

13. (c)

Given, input signal  $x(t) = 10 \sin(20t)$

$$x_1(t) = \frac{d}{dt} x(t) = \frac{d}{dt} (10 \sin 20t) = 200 \cos 20t$$

$$x_2(t) = \frac{200 \cos 20t}{20} = 10 \cos 20t$$

$x_1(t)$  and  $x_2(t)$  are same signal but  $90^\circ$  displaced in time domain.

$$x_2(t) = 10 \sin(20t + 90^\circ)$$

Hence, in XY mode CRO shows circle as output.

Hence option (c) is correct.

14. (b)

We know, Deflection,  $D = \frac{L l_d E_d}{2d E_a}$

Voltage required at deflecting plates,

$$E_d = \frac{2d E_a D}{L l_d} = \frac{2 \times d \times E_a \times D}{L l_d}$$

$$= \frac{2 \times 5 \times 10^{-3} \times 4 \times 10^{-2} \times 1500}{50 \times 10^{-2} \times 1.5 \times 10^{-2}}$$

$$E_d = \frac{60000 \times 10^{-5}}{75 \times 10^{-4}} = 80 \text{ V}$$

Input voltage to amplifier = 2 V

We know input voltage required for a deflection of 4 cm

$$= \frac{E_d}{\text{Amplifier gain}}$$

So, amplifier gain =  $\frac{E_d}{2} = \frac{80}{2} = 40$

15. (c)

Given, Error : 0.4% of reading

i.e.,  $\frac{0.4}{100} \times 5 = 0.02 \text{ V}$

If 5 V is displayed on 10 V range as : 05.00

∴ Least count digit in the LSD has value : 0.01

∴ Total possible error : 0.01 + 0.02 = 0.03 V

16. (b)

We know for triangular wave form

$$\text{Average value} = \frac{V_m}{2}$$

$$\text{RMS value} = \frac{V_m}{\sqrt{3}}$$

$$\text{Comparing rms value } \frac{V_m}{\sqrt{3}} = \frac{40}{\sqrt{3}}$$

$$V_m = 40 \text{ V}$$

$$\text{Average value of triangular input} = \frac{40}{2} = 20 \text{ V}$$

17. (b)

For the meter,

Full scale deflection current = 2 mA

Internal resistance = 500 Ω

The voltage drop across voltmeter at full scale current

$$= 2 \text{ mA} \times 500 = 1 \text{ V}$$

The full scale deflection on required voltmeter

$$= 200 \text{ V}$$

Maximum possible voltage around meter

$$= 1 \text{ V}$$

$$\text{Extra potential drop} = 200 - 1 \text{ V} = 199 \text{ V}$$

Comparing voltage drop and resistances

$$\frac{199}{1} = \frac{x}{500}$$

$$x = 500 \times 199 = 99.5 \text{ k}\Omega$$

Alternatively:

$$V_m = 2 \times 10^{-3} \times 500 = 1 \text{ V}$$

$$m = \frac{V}{V_m} = \frac{200}{1} = 200$$

$$R_{se} = (m - 1) R_m$$

$$= (200 - 1) \times 500 = 99500 = 99.5 \text{ k}\Omega$$

18. (a)

Total power in the load circuit,

$$\begin{aligned} P &= W_1 + W_2 \\ &= 6000 - 1000 = 5000 \text{ W} \end{aligned}$$

$$\begin{aligned} \phi &= \tan^{-1} \left[ \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right] \\ &= \tan^{-1} \left[ \frac{\sqrt{3}[(6000 - (-1000))]}{6000 - 1000} \right] \\ &= \tan^{-1} \left[ \frac{\sqrt{3}(7000)}{5000} \right] = 67.58^\circ \end{aligned}$$

$$\cos \phi = 0.381$$

Load current per phase,

$$\begin{aligned} I_P &= \frac{5000}{\sqrt{3} \times 440 \times 0.381} \\ I_P &= 17.22 \text{ A} \end{aligned}$$

Load impedance per phase,

$$Z_P = \frac{V_P}{I_P} = \frac{440}{\left( \frac{17.22}{\sqrt{3}} \right)} = 44.25 \text{ }\Omega$$

Load resistance per phase,

$$\begin{aligned} R_P &= Z_P \cos \phi = 44.25 \cos (67.58) \\ &= 44.25 \times 0.381 \\ R_P &= 16.87 \text{ }\Omega \end{aligned}$$

Load reactance per phase,

$$\begin{aligned} X_P &= Z_P \sin \phi = 44.25 \sin (67.58) \\ X_P &= 40.9 \text{ }\Omega \end{aligned}$$

Reading of wattmeter B will be zero when power factor,

$$\begin{aligned} \cos \phi' &= 0.5 \\ \phi' &= 60^\circ \end{aligned}$$

Since there is no change in resistance, reactance in circuit per phase,

$$\begin{aligned} X_P' &= R_P \tan \phi' \\ X_P' &= 16.87 \times \tan 60^\circ = 29.22 \text{ }\Omega \end{aligned}$$

Values of capacitive reactance introduced in each phase,

$$\begin{aligned} X_C &= X_P - X_P' \\ &= 40.9 - 29.22 = 11.68 \text{ }\Omega \end{aligned}$$

$$\therefore C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 11.68}$$

$$C = 272.52 \text{ }\mu\text{F}$$

19. (c)

We know, figure of merit = sensitivity

$$\text{Sensitivity} = \frac{1}{I_{fsd}}$$


Full scale deflection current for meter 1

$$= \frac{1}{20 \text{ k}\Omega} \frac{V}{\text{V}} = 0.05 \text{ mA} = 50 \text{ }\mu\text{A}$$

Full scale deflection current for meter 2

$$= \frac{1}{40 \text{ k}\Omega} \frac{V}{\text{V}} = 0.025 \text{ mA} = 25 \text{ }\mu\text{A}$$

For series combination

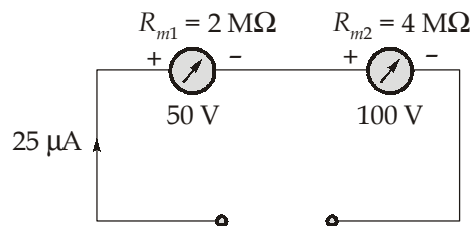Maximum allowable current = 25  $\mu\text{A}$ 

So maximum voltage measured from series combination

$$= 50 + 100 = 150 \text{ V}$$

20. (b)

We know ,

$$\omega = 2\pi f = 2\pi \times 1000 \text{ Hz} = 6283.19 \text{ Hz}$$

$$X_{L2} = \omega L_2 = 6283.19 \times 15.92 \times 10^{-3} = 100 \text{ }\Omega$$

$$X_{C3} = \frac{1}{\omega C_3} = \frac{1}{6283.19 \times 0.4 \times 10^{-6}} = 400 \text{ }\Omega$$

The impedance of the bridge arm

$$Z_1 = R_1 = 400 \angle 0^\circ \text{ }\Omega$$

$$Z_2 = R_2 + jX_{L2} = 200 + j100 \\ = 223.6 \angle 26.6^\circ \text{ }\Omega$$

$$Z_3 = R_3 - jX_{C3} \\ = 300 - j400 = 500 \angle -53.13^\circ \text{ }\Omega$$

$$\therefore Z_x = \frac{Z_2 Z_3}{Z_1} = \frac{(223.6 \angle 26.6^\circ)(500 \angle -53.13^\circ)}{400 \angle 0^\circ} \\ = 279.5 \angle -26.53^\circ \\ = (250.07 - j124.84) \text{ }\Omega$$

$$\text{we know } C = \frac{1}{\omega X_C} = \frac{1}{6283.19 \times 124.84} \approx 1.28 \text{ }\mu\text{F}$$

 $\therefore$  Z impedance is series combination of 250.35  $\Omega$  resistance and 1.28  $\mu\text{F}$  capacitance.

21. (d)

Current through current coil

$$= \frac{24}{6} = 4 \text{ A}$$

As pressure coil is supplied by ideal half wave rectifier

∴ Conduction happens for only half cycle

Reading of wattmeter = Average power over a cycle

$$\begin{aligned} &= \frac{1}{2\pi} \left[ \int_0^{2\pi} V_i d\theta \right] = \frac{1}{2\pi} \int_0^{\pi} \sqrt{2} \times 100 \sin \theta \times 4 d\theta \\ &= \frac{\sqrt{2} \times 4 \times 100}{2\pi} [-\cos \theta]_0^{\pi} \\ &= \frac{\sqrt{2} \times 4 \times 100}{2\pi} \times 2 = \frac{400\sqrt{2}}{\pi} \text{ W} \end{aligned}$$

22. (b)

PMMC always reads average value,

$$\begin{aligned} V_0 &= \frac{1}{T} \int_0^T v dt \\ &= \frac{1}{25} \left[ (10 \times 5) + (-5 \times 5) + \left( \frac{1}{2} \times 10 \times 10 \right) \right] \\ &= \frac{1}{25} [50 - 25 + 50] = 3 \text{ V} \end{aligned}$$

23. (d)

Given, temperature range  $(50^\circ - (-20^\circ)) = 70^\circ\text{C}$

Resolution =  $0.2^\circ\text{C}$

Resolution relative to range =  $\frac{0.2}{70} = 0.00286$

For  $N$  bit ADC

$$\begin{aligned} \text{Resolution} &= \frac{1}{2^N - 1} = 0.00286 \\ 2^N &= 350 \\ N &\simeq 9 \end{aligned}$$

24. (a)

We know,

$$\begin{aligned} \text{Self capacitance of coil, } C_d &= \frac{C_1 - 4C_2}{3} = \frac{490 - 4 \cdot (120)}{3} \\ &= \frac{490 - 480}{3} = \frac{10}{3} \text{ pF} \end{aligned}$$

25. (d)

At balance condition for schering bridge

$$R_x = \frac{R_3 C_4}{C_2} = \frac{(100 \times 10^3)(0.01 \times 10^{-6})}{(0.1 \times 10^{-6})} = 10 \text{ k}\Omega$$

$$C_x = \frac{C_2 R_4}{R_3} = \frac{(0.1 \times 10^{-6})(470 \times 10^3)}{100 \times 10^3}$$

$$= 0.47 \times 10^{-6} \text{ F} = 0.47 \text{ } \mu\text{F}$$

26. (b)

$$\text{Percentage error} = \frac{I^2 R_C}{VI \cos \phi}$$

$$= \frac{(12)^2 \times 0.1}{250 \times 12 \times 1} \times 100$$

$$= \frac{14.4}{3000} \times 100 = 0.48\%$$

27. (d)

$$\text{Percentage error} = \frac{\text{Energy recorded} - \text{Actual energy}}{\text{Actual energy}}$$

$$\text{Actual energy} = \frac{4 \text{ kW} \times 40}{3600} \text{ hr} = \frac{2}{45} \text{ kWhr}$$

$$\text{So,} \quad 0.08 = \frac{\text{Energy recorded} - \frac{2}{45}}{\frac{2}{45}}$$

$$\text{Energy recorded} = 0.048 \text{ kWhr}$$

$$\text{Meter constant} = \frac{\text{No. of revolution}}{\text{Energy recorded}} = \frac{40}{0.048} = 833.33 \text{ rev/kWhr}$$

28. (d)

$$C_x = \frac{R_4}{R_3} C_2$$

$$= \frac{318}{130} \times 106 \times 10^{-12} = 259.29 \text{ pF}$$

$$R_x = R_3 \times \frac{C_4}{C_2}$$

$$= 130 \times \frac{0.35 \times 10^{-6}}{106 \times 10^{-12}} = 429.25 \text{ k}\Omega$$

29. (d)

Given,

Frequency of signal at X plates,

$$f_x = 52 \text{ Hz}$$


Frequency of signal of Y plates,  $f_y$

$$\frac{f_y}{f_x} = \frac{\text{Number of horizontal tangencies}}{\text{Number of vertical tangencies}}$$

No. of horizontal tangencies : 3

No. of vertical tangencies : 2
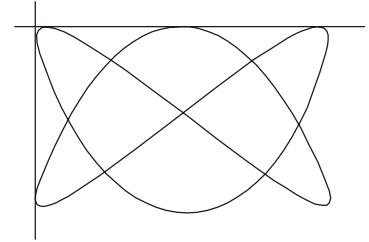
$$f_y = f_x \times \frac{3}{2} = \frac{52 \times 3}{2} = 78 \text{ Hz}$$



30. (b)

$$\begin{aligned} R_1 &= R_2(k - 1) \\ &= 1 \text{ M}\Omega (10 - 1) \\ &= 9 \text{ M}\Omega \end{aligned}$$

$$C_1 = \frac{C_2}{k - 1} = \frac{30 \text{ pF}}{10 - 1} = 3.33 \text{ pF}$$

■■■■