

**MADE EASY**

Leading Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

DIGITAL LOGIC

COMPUTER SCIENCE & IT

Date of Test : 17/09/2026

ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (d) | 7. (c) | 13. (a) | 19. (a) | 25. (d) |
| 2. (d) | 8. (d) | 14. (d) | 20. (b) | 26. (c) |
| 3. (d) | 9. (b) | 15. (b) | 21. (c) | 27. (d) |
| 4. (b) | 10. (c) | 16. (c) | 22. (b) | 28. (d) |
| 5. (a) | 11. (a) | 17. (c) | 23. (b) | 29. (c) |
| 6. (d) | 12. (a) | 18. (b) | 24. (d) | 30. (a) |

DETAILED EXPLANATIONS

1. (d)

$$\begin{aligned} Q &= AB + \overline{(B+C)(BC)} \\ &= AB + \overline{BC + BC} \\ &= AB + \overline{BC} \\ &= AB + \overline{B} + \overline{C} \\ Q &= A + \overline{B} + \overline{C} \end{aligned}$$

2. (d)

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

If any one of the input is zero, output is logic '1'. Otherwise output is logic '0', which represents the NAND gate.

3. (d)

Output of ExOR Gate = $b_i \oplus b_{i+1}$

Initially $Q = 0$ assume

So, After 1 clock, $Z = b_7 \oplus b_0$
 After 2 clock, $Z = b_7 \oplus b_6$
 After 3 clock, $Z = b_6 \oplus b_5$
 After 4 clock, $Z = b_5 \oplus b_4$
 After 5 clock, $Z = b_4 \oplus b_3$
 After 6 clock, $Z = b_3 \oplus b_2$
 After 7 clock, $Z = b_2 \oplus b_1$
 After 8 clock, $Z = b_1 \oplus b_0$

Which is same as Binary to gray code converter.

4. (b)

$$\begin{aligned} Y &= A\overline{B} + A \oplus C \\ &= A\overline{B} + A\overline{C} + \overline{A}C \\ \text{So, SOP} &= \sum m(1, 3, 4, 5, 6) \\ \text{POS} &= \prod M(0, 2, 7) \end{aligned}$$

5. (a)

Given, $(5456)_8$


$$\begin{array}{cccc}
 5 & 4 & 5 & 6 \\
 \downarrow & \downarrow & \downarrow & \downarrow \\
 101 & 100 & 101 & 110 \\
 (101100101110)_2
 \end{array}$$

For Hexadecimal number, grouping 4 binary bits

$$\begin{array}{ccc}
 1011 & 0010 & 1110 \\
 \downarrow & \downarrow & \downarrow \\
 B & 2 & E
 \end{array}$$

$$\therefore (5456)_8 \longrightarrow (B2E)_{16}$$

6. (d)

 

7. (c)

We know that for a stage change to ripple through n stages i.e. $T_C = n \times t_{pd}$.

$$f_c = \frac{1}{T_C}$$

$$f_c = \frac{1}{n \times t_{pd}}$$

So,

$$t_{pd} = \frac{1}{n \times f_c}$$

$$t_{pd}(\text{min}) = \frac{1}{10 \times 10 \times 10^6 \text{ Hz}} = 0.01 \times 10^{-6} \text{ sec} = 10 \times 10^{-9} \text{ sec} = 10 \text{ nsec}$$

8. (d)

S	R	T	Q	Q ⁺
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

SR \ TQ	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

$$Q^+ = TQ' + T'QS + T'QR' + T'SR' = TQ' + T'[Q(S + R') + SR']$$

9. (b)

(i) $x > y$


(ii) $x > 6$

$$x = 8, y = 7$$

$$(673)_8 + (54)_8 = (487)_{10}$$

$$(443)_{10} + (44)_{10} = (487)_{10}$$

10. (c)

 


$$Q_{n+1} = D = Q \oplus X$$

For $X = 0$, $Q_{n+1} = Q_n$ and for $X = 1$, $Q_{n+1} = \overline{Q_n}$.

Therefore, the given circuit acts as T flip-flop for $T = X$.

11. (a)

 

EPI = Essential Prime Implicant [which cover a minterm not covered by any other prime implicants]
 NEPI = Non Essential Prime Implicant. Number of EPI's = 2, number of NEPI's = 5.

12. (a)

$$Y = \bar{S}_1 \bar{S}_0 (I_0) + \bar{S}_1 S_0 (I_1) + S_1 \bar{S}_0 (I_2) + S_1 S_0 (I_3)$$

$$I_0 = I_3 = S_1$$

$$I_1 = I_2 = S_0$$

⇒

$$Y = \underbrace{\bar{S}_1 \bar{S}_0 (S_1)}_0 + \bar{S}_1 S_0 (S_0) + \underbrace{S_1 \bar{S}_0 (S_0)}_0 + S_1 S_0 (S_1)$$

$$Y = \bar{S}_1 S_0 + S_1 S_0$$

- $S_0 = B, S_1 = A$

$$Y = \bar{A}B + AB = (\bar{A} + A)B = B$$

- $S_0 = A, S_1 = \bar{B}$

$$Y = \bar{\bar{B}}A + \bar{B}A = BA + \bar{B}A = A(B + \bar{B}) = A$$

- $S_0 = \bar{A}, S_1 = B$

$$Y = \bar{B}\bar{A} + B\bar{A} = \bar{A}(B + \bar{B}) = \bar{A}$$

- $S_0 = \bar{A}, S_1 = \bar{B}$

$$Y = \bar{\bar{A}}\bar{\bar{B}} + \bar{B}\bar{A} = \bar{A}B + \bar{B}\bar{A} = \bar{A}(B + \bar{B}) = \bar{A}$$

Hence option (a) is the correct answer.

13. (a)

For every combination of x, y, z the function value remains same for input $\bar{x}, y, \bar{z}$.

x	y	z	$f(x, y, z) = f(\bar{x}, y, \bar{z})$
0	0	0	} either 0 or 1
1	0	1	
0	0	1	} either 0 or 1
1	0	0	
0	1	0	} either 0 or 1
1	1	1	
0	1	1	} either 0 or 1
1	1	0	

Effectively there are only four rows for the truth table of the function $f(x, y, z)$.

$\therefore$ Total Boolean expressions possible is $2^4 = 16$.

14. (d)

$$\begin{aligned}
 \text{(a)} \quad & \overline{(\bar{A}B + \bar{C})}(A + C) = (A + \bar{B})C \\
 & (A + \bar{B}) \cdot C \cdot (A + C) = (A + \bar{B})C \\
 & (AC + \bar{B}C)(A + C) = (A + \bar{B})C \\
 & AC + A\bar{B}C + \bar{B}C = (A + \bar{B})C \\
 & AC + \bar{B}C = (A + \bar{B})C \\
 & (A + \bar{B})C = (A + \bar{B})C \quad \therefore \text{True}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad & \overline{(A + \bar{B} + \bar{C})(A + \bar{B}C)} = \bar{A}(B + \bar{C}) \\
 & (\bar{A}BC) + \bar{A}(B + \bar{C}) = \bar{A}B + \bar{A}\bar{C} \\
 & \bar{A}BC + \bar{A}B + \bar{A}\bar{C} = \bar{A}B + \bar{A}\bar{C} \\
 & \bar{A}B(C + 1) + \bar{A}\bar{C} = \bar{A}B + \bar{A}\bar{C} \\
 & \bar{A}\bar{C} + \bar{A}B = \bar{A}B + \bar{A}\bar{C} \quad \therefore \text{True}
 \end{aligned}$$

$$\begin{aligned}
 \text{(c)} \quad & (A + \bar{A}\bar{B}\bar{C})B + \bar{A}B = BA + \bar{A}B \\
 & (A + \bar{B}\bar{C})B + \bar{A}B = (A + \bar{A})B \\
 & AB + \bar{A}B = B \\
 & B(A + \bar{A}) = B \\
 & B = B \quad \therefore \text{True}
 \end{aligned}$$

So, all the expression are correct.

15. (b)

$$I_1 = Q_1 \oplus Q_0$$

$$I_0 = Q_3 \odot Q_2$$

Clock	Q_3	Q_2	Q_1	Q_0	I_1	I_0	Y_2
	0	0	0	0	0	1	0
1	0	0	0	1	1	1	0
2	0	0	1	0	1	1	0
3	0	0	1	1	0	1	0
4	0	1	0	0	0	0	0
5	0	1	0	1	1	0	1
6	0	1	1	0	1	0	1
7	0	1	1	1	0	0	0
8	1	0	0	0	0	0	0
9	1	0	0	1	1	0	1
10	0	0	0	0	0	1	0

Since, in 10 clock cycle y_2 is 1 for 3 clock cycles.

16. (c)

Let the output of XNOR gate is Y

$$Y = (Q_3 \oplus Q_1 \oplus Q_0) \odot Q_5$$

CLK	Y	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
—		1	0	0	0	0	0
1	0	0	1	0	0	0	0
2	1	1	0	1	0	0	0
3	1	1	1	0	1	0	0
4	0	0	1	1	0	1	0
5	1	1	0	1	1	0	1

Minimum five clock pulses are required to get the sequence 101101

17. (c)

For MOD - 10 counter

$$X = \text{Johnson counter required} = 5 \text{ FF's}$$

$$Y = \text{ring counter required} = 10 \text{ FF's}$$

$$Z = \text{ripple counter required} = 4 \text{ FF's}$$

$$X + Y + Z = 5 + 10 + 4 = 19 \text{ FF's}$$

18. (b)

Essential prime implicant is a prime implicant which is having atleast one minterm which is not the part of any other prime implicant.

Using K-map for the given function

we get

CD \ AB	00	01	11	10
00	1			
01	1	1		
11		1	1	
10			1	1

The total number of prime implicants = 6 and the number of essential prime implicants = 2.

19. (a)

J-K flip-flop will change for every clock pulse. Mod-3 counter will change whenever Q is changing from 0 to 1 because it is ripple counter.

CLK	Q	A	B
	0	0	0
1	1	1	1
2	0	1	1
3	1	0	1
4	0	0	1
5	1	1	0

20. (b)

$$\left. \begin{array}{l} S_1 = C \\ S_0 = A \end{array} \right\}$$

$$E = C$$

$$I_0 = B \oplus D$$

$$I_1 = 1$$

$$I_2 = \bar{D}$$

$$I_3 = BD$$

Mux output is

$$Y = [\bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3] \bar{E}$$

Substituting the values

$$\begin{aligned} f(A, B, C, D) &= [\bar{C} \bar{A}(B \oplus D) + \bar{C} A(1) + C \bar{A}(\bar{D}) + CA(BD)] \bar{C} \\ &= \bar{C} \bar{A}(B \oplus D) + \bar{C} A + \underbrace{C \bar{C} \bar{A} \bar{D}}_0 + \underbrace{C \bar{C} A B D}_0 \\ &= \bar{C} \bar{A}(\bar{B} D + B \bar{D}) + \bar{C} A \\ &= \bar{A} \bar{B} \bar{C} D + \bar{A} B \bar{C} \bar{D} + A \bar{C} \\ &\quad \quad \quad 1 \quad \quad \quad 4 \quad (8, 9, 12, 13) \\ &= \sum m(1, 4, 8, 9, 12, 13) \end{aligned}$$


21. (c)

$$F = \bar{X}Z + \bar{X}W + \bar{Y}Z + \bar{Y}W$$

K-map

WZ \ XY	00	01	11	10
00	0	1	1	1
01	0	1	1	1
11	0	0	0	0
10	0	1	1	1

$$F = (\bar{X} + \bar{Y})(W + Z)$$

 

Total 5 NOR gates are required.

22. (b)

Given, Input frequency = 640 kHz

$$\text{Output frequency after 4-bit ring counter} = \frac{640}{4} = 160 \text{ kHz}$$

$$\text{Output frequency after 4-bit Johnson counter} = \frac{160}{8} = 20 \text{ kHz}$$

$$\text{Output frequency after decade counter} = \frac{20}{10} = 2 \text{ kHz}$$

23. (b)

Number of flip-flops for mod-8 ripple counter = 3

$$\text{Maximum clock frequency} = f = \frac{1}{T}$$

$$\Rightarrow 4 \text{ MHz} = \frac{1}{3 \times x \text{ ns}} \text{ Hz}$$

$$\Rightarrow 4 \times 10^6 \text{ Hz} = \frac{10^9}{3 \times x} \text{ Hz}$$

$$\Rightarrow x = \frac{10^9}{4 \times 10^6 \times 3} = \frac{10^3}{12} = 83.33$$

24. (d)
Let,

$$\begin{array}{r}
 A = \quad \quad \quad a_2 \quad \quad \quad a_1 \quad \quad \quad a_0 \\
 B = \quad \quad \quad \quad \quad \quad b_1 \quad \quad \quad b_0 \\
 \hline
 A \times B = \quad \quad \quad a_2b_0 \quad \quad a_1b_0 \quad \quad a_0b_0 \\
 \quad \quad \quad b_1a_2 \quad b_1a_1 \quad b_1a_0 \quad \quad \downarrow \\
 \hline
 \quad \quad \quad b_1a_2 \quad (a_2b_0 + a_1b_1) \quad (a_1b_0 + b_1a_0) \quad a_0b_0 \\
 \quad \quad \quad C_3 \quad \quad C_2 \quad \quad C_1 \quad \quad C_0
 \end{array}$$

Number of AND gates required $X = 6$

Number of one bit full adders required $Y = 3$

$$X + Y = 6 + 3 = 9$$

25. (d)


Present state (Q_n)	Input (Y)	Next state (Q_{n+1})
0	1	0
0	0	1
1	1	0
1	0	0

$$Q_{n+1} = \overline{Q_n + Y}$$

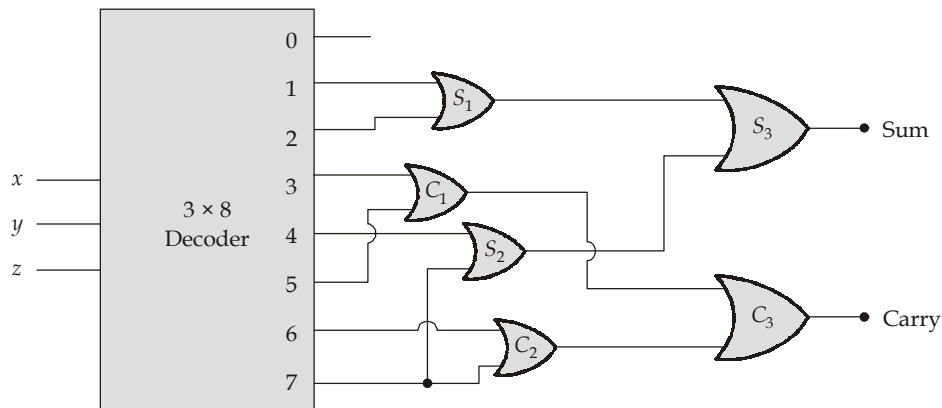26. (c)
To implement full adder using 3×8 decoder

$$\text{Sum } (x, y, z) = \Sigma(1, 2, 4, 7)$$

$$\text{Carry } (x, y, z) = \Sigma(3, 5, 6, 7)$$



Hence 3 OR-gate is required for sum and 3-OR-gate is required for carry.

So, total 6 OR-gates is needed.

27. (d)
Given that,

$$D_A = Q_{B'}$$

$$J_B = Q_{C'}$$

$$K_B = \bar{Q}_{C'}$$


$$D_C = Q_C \odot Q_A$$

So, the state table is

Clock	Present state			Next state			D_A	J_B	K_B	D_C
	Q_A	Q_B	Q_C	Q_A	Q_B	Q_C				
1	1	1	0	1	0	0	1	0	1	0
2	1	0	0	0	0	0	0	0	1	0
3	0	0	0	0	0	1	0	0	1	1
4	0	0	1	0	1	0	0	1	0	0
5	0	1	0	1	0	1	1	0	1	1
6	1	0	1	0	1	1	0	1	0	1

Hence 6 clock pulses are required.

 28. (d)
All the above statements are correct.
29. (c)



	J	K	Q	$\bar{Q}$
			0	1
1	1	1	1	0
2	0	1	0	1
3	1	1	1	0
4	0	1	0	1
5	1	1	1	0
6	0	1	0	1

The output Q will be 101010.

30. (a)
The total delay for synchronous series counter
- $$= t_{pd} \text{ (of FF)} + (n - 2) t_{pd} \text{ (of AND gate)}$$
- where n = Number of flip-flops
- As $M \leq 2^n$ (Where M = modulus)
- So, $256 \leq 2^n$
- $$n = 8$$

$$\begin{aligned} \text{Total delay} &= 25 + (8 - 2) 5 \\ &= 25 + 30 = 55 \text{ nsec} \end{aligned}$$

So, the maximum frequency of MOD-256 counter will be

$$= \frac{1}{55 \text{ nsec}} = 18.18 \text{ MHz}$$

