

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Lucknow | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

POWER SYSTEMS-2

ELECTRICAL ENGINEERING

Date of Test : 25/04/2022

ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (c) | 13. (b) | 19. (a) | 25. (a) |
| 2. (c) | 8. (c) | 14. (a) | 20. (b) | 26. (b) |
| 3. (b) | 9. (a) | 15. (a) | 21. (b) | 27. (c) |
| 4. (c) | 10. (c) | 16. (d) | 22. (c) | 28. (c) |
| 5. (b) | 11. (b) | 17. (a) | 23. (c) | 29. (a) |
| 6. (c) | 12. (b) | 18. (d) | 24. (d) | 30. (b) |

DETAILED EXPLANATIONS

1. (b)

3-φ fault current:

Let system is under no load condition before fault,

$$\therefore E = 1\angle 0^\circ \text{ p.u.}$$

$$\text{3-φ fault current, } I_f = \frac{E}{X_1}$$

$$\Rightarrow X_1 = \frac{1}{-j5} = j0.2 \text{ p.u.}$$

Line-line fault current:

$$I_f = \frac{\sqrt{3}E}{X_1 + X_2}$$

$$\Rightarrow X_1 + X_2 = \frac{\sqrt{3}}{-j2.5}$$

$$\Rightarrow j0.2 + X_2 = j0.69 \text{ p.u.}$$

$$\Rightarrow X_2 = j0.49 \text{ p.u.}$$

2. (c)

For a solid LG fault,

$$\text{Fault current is: } (I_F)_{LG} = \frac{3E}{(2X_1 + X_0 + 3X_n)} \quad (\text{Here, } X_1 \approx X_2 \text{ for synchronous generator})$$

Similarly, for a solid 3-φ fault

$$(I_F)_{3-\phi} = \frac{E}{X_1}$$

For LG fault current to be less than 3-φ fault current,

$$\frac{3E}{2X_1 + X_0 + 3X_n} < \frac{E}{X_1}$$


$$\text{or, } 2X_1 + X_0 + 3X_n > 3X_1$$

$$\text{or, } X_n > \frac{1}{3}(X_1 - X_0)$$

Hence, option (c) is correct.

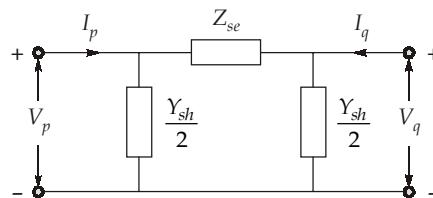3. (b)


Y -bus matrix for the π equivalent circuit.



$$Y_{\text{bus}} = \begin{bmatrix} \frac{1}{Z_{se}} + \frac{Y_{\text{sh}}}{2} & -\frac{1}{Z_{se}} \\ -\frac{1}{Z_{se}} & \frac{1}{Z_{se}} + \frac{Y_{\text{sh}}}{2} \end{bmatrix}$$

Here, $Z_{se} = jX; Y_{\text{sh}} = 0$

The above circuit diagram becomes,

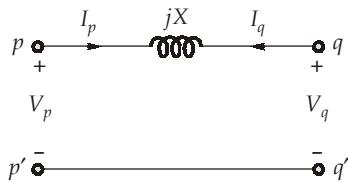

$$\therefore Y_{\text{bus}} = \begin{bmatrix} \frac{1}{jX} & -1 \\ -1 & \frac{1}{jX} \end{bmatrix}$$

4. (c)

In LLG fault,

$$I_{\text{positive}} + I_{\text{negative}} + I_{\text{zero}} = 0$$

Here, $j1.653 - j0.5 - j1.153 = 0$

Hence fault is double line to ground fault.

5. (b)

$$\text{Synchronizing power coefficient} = P_{\max} \cos \delta_0 = \frac{dP_e}{d\delta}$$

$$\text{Here, } P_{\max} = 2, \quad \delta = 30^\circ$$

$$\therefore S_p = 2 \cos 30^\circ \\ = 2 \times \frac{\sqrt{3}}{2} = \sqrt{3}$$

6. (c)

$$\text{SLG fault current } I_f = \frac{3E}{X_1 + X_2 + X_0 + 3X_n} = 1$$

$$\text{or, } 3X_n = 3 - (0.75) \\ \text{or, } X_n = 0.75 \text{ pu}$$

7. (c)

$$P_{m_0} = P_m \sin \delta_0 \\ \therefore \delta_0 = \sin^{-1}\left(\frac{1}{2}\right) = 30 \text{ degree or, } 0.5235 \text{ rad}$$

Critical clearing angle

$$\text{or, } \delta_{cr} = \cos^{-1}[(\pi - 2\delta_0) \sin \delta_0 - \cos \delta_0] \\ \text{or, } \delta_{cr} = \cos^{-1}[(\pi - 2(0.5235)) \sin(30^\circ) - \cos(30^\circ)]$$

$$\delta_{cr} = 79.55^\circ$$

8. (c)

$$\begin{aligned}
 Y_{11} &= y_{11} + y_{12} + y_{13} = -j 2.86 \\
 Y_{22} &= y_{12} + y_{22} + y_{23} = -j 6 \\
 Y_{33} &= y_{13} + y_{23} + y_{33} = -j 8.86 \\
 Y_{12} &= Y_{21} = -y_{12} = 0 \\
 Y_{13} &= Y_{31} = -y_{13} = j 2.86 \\
 Y_{23} &= Y_{32} = -y_{23} = j 2
 \end{aligned}$$

9. (a)

Total Kinetic energy of the two machines,

$$\begin{aligned}
 &= G_1 H_1 + G_2 H_2 \\
 &= 400 \times 4 + 1600 \times 2 \\
 &= 4800 \text{ MJ}
 \end{aligned}$$

The equivalent H on the base of 200 MVA,

$$\begin{aligned}
 &= \frac{4800 \text{ MJ}}{200 \text{ MVA}} \\
 &= 24 \text{ MJ/MVA}
 \end{aligned}$$

10. (c)

$$\begin{aligned}
 \text{Minimum number of equations} &= 2n - m - 2 \\
 &= 2(112) - 20 - 2 = 202
 \end{aligned}$$


11. (b)

$$\text{The reactance in p.u.} = Z_{\text{p.u.}} = Z_\Omega \times \frac{\text{MVA}_{(b)}}{(\text{kV})_b^2}$$


$$\begin{aligned}
 Z_\Omega &= Z_{\text{p.u.}} \times \frac{(kV_b)^2}{(\text{MVA})_b} \\
 &= 0.10 \times \frac{(33)^2}{10} = 10.89 \Omega
 \end{aligned}$$

So reactance per phase $= Z_{ph} = 10.89 \Omega$
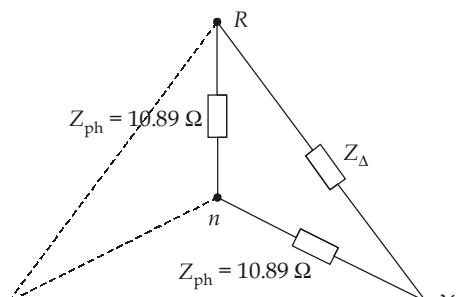
$$\begin{aligned}
 Z_\Delta &= 3 \times Z_{ph} = 3 \times 10.89 \\
 Z_\Delta &= 32.67 \Omega
 \end{aligned}$$



12. (b)

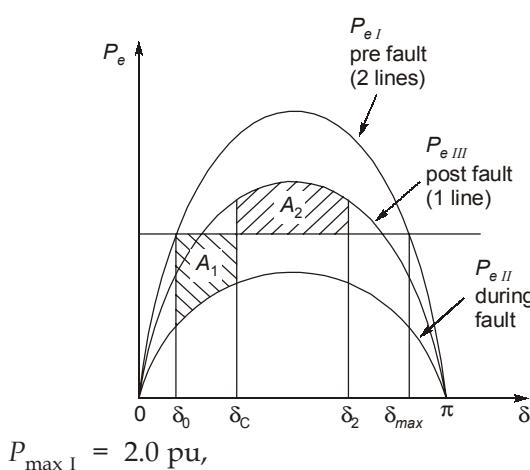

$$P_{\max II} = 0.5 \text{ pu},$$

and,

$$P_{\max III} = 1.5 \text{ pu}$$

Initial loading

$$P_m = 1.0 \text{ pu}$$

$$\delta_0 = \sin^{-1} \left(\frac{P_m}{P_{\max I}} \right) = \sin^{-1} \frac{1}{2} = 0.523 \text{ rad}$$

$$\delta_{\max} = \pi - \sin^{-1} \left(\frac{P_{\max}}{P_{\max III}} \right) = \pi - \sin^{-1} \left(\frac{1}{1.5} \right) = 2.41 \text{ rad}$$


$$\cos \delta_{cr} = \frac{P_m(\delta_{\max} - \delta_0) - P_{\max II} \cos \delta_0 + P_{\max III} \cos \delta_{\max}}{P_{\max III} - P_{\max II}}$$

$$\cos \delta_{cr} = \frac{1.0(2.41 - 0.523) - 0.5 \cos 0.523 + 1.5 \cos 2.41}{1.5 - 0.5}$$

$$\delta_{cr} = 70.3^\circ$$

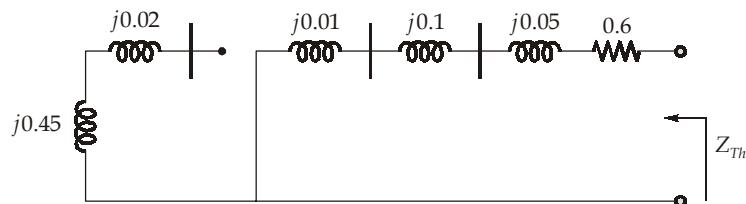13. (b)


The zero sequence impedance network from point P and ground



The Thevenin's equivalent zero sequence impedance

$$Z_{\text{Th}} = (0.6 + j 0.16) \text{ p.u.}$$

14. (a)

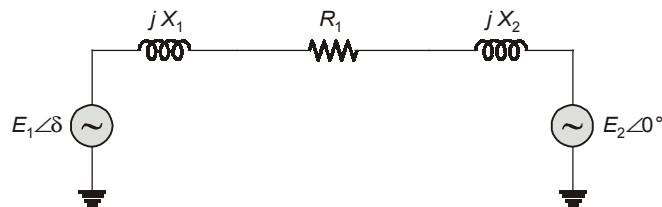

$$P_2 = E_2 I_2^*$$

$$P_2 = E_2 \left(\frac{E_1 \angle \delta - E_2 \angle 0^\circ}{R_1 + j(X_1 + X_2)} \right)^*$$

$$\text{Let } R_1 + j(X_1 + X_2) = Z$$

$$|Z| \angle \beta$$

$$P_2 = E_2 \left[\frac{E_1 \angle \delta - E_2}{|Z| \angle \beta} \right]^*$$

$$P_2 = E_2 \left[\frac{E_1}{|Z|} \angle (\beta - \delta) - \frac{E_2}{|Z|} \angle \beta \right]$$

$$P_2 = \frac{E_2 E_1}{|Z|} \cos(\beta - \delta) - \frac{E_2}{|Z|} \cos \beta$$

to obtain the maximum value of P_2 , differentiate it with respect to δ and equate it to zero.

$$\left(\frac{dP_2}{d\delta} \right) = 0$$

$$\frac{E_2 E_1}{|Z|} \sin(\beta - \delta) = 0$$

$$\sin(\beta - \delta) = 0$$

$$\beta = \delta$$

i.e.

$$\delta < 90^\circ$$

similarly

$$P_1 = E_1 I_1^* = E_1 \left(\frac{E_1 \angle \delta - E_2}{|Z| \beta} \right)^*$$


\therefore Both $P_{1 \max}$ and $P_{2 \max}$ occur at $\delta < 90^\circ$.

15. (a)

The earth fault is assumed to occur on the red phase. Taking red phase as the reference, its phase e.m.f.

$$E_R = \frac{11 \times 1000}{\sqrt{3}} = 6351 \text{ V}$$

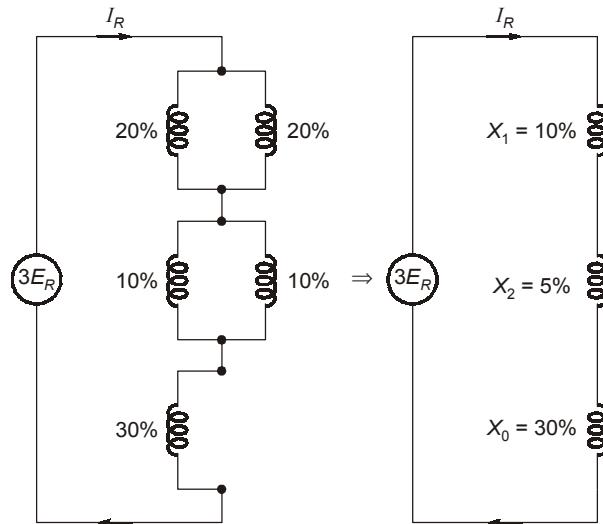For line to ground fault the equivalent circuit will be



The percentage reactances can be converted into ohmic values as under :

$$\% X = \frac{Z (MVA_b)}{(KV)^2} \times 100$$

$$Z = \frac{\% X \times (KV)^2}{(MVA_b) \times 100}$$

$$X_1 = \frac{10 \times (11)^2}{20 \times 100} = 0.605 \Omega$$

$$X_2 = \frac{5 \times 11^2}{20 \times 100} = 0.3025 \Omega$$

$$X_0 = \frac{30 \times 11^2}{20 \times 100} = 1.815 \Omega$$

Fault current

$$\vec{I}_R = \frac{3\vec{E}_R}{X_1 + X_2 + X_0} = \frac{3 \times 6351}{j0.605 + j0.3025 + j1.815}$$

$$\vec{I}_R = -j 6998 \text{ A}$$

$$|I_R| = 6998 \text{ A}$$

16. (d)

Let us choose a base of 15 MVA, 11 kV on LV side of transformer.

We know that:

$$Z_{(pu)\text{new}} = Z_{(pu)\text{old}} \times \frac{(MVA)_{b,\text{new}}}{(MVA)_{b,\text{old}}} \times \frac{(kV)^2_{b,\text{old}}}{(kV)^2_{b,\text{new}}}$$

∴

$$X_{g_1} = 0.2 \times \frac{15}{10} = 0.3 \text{ p.u.}$$

$$X_{g_2} = 0.2 \times \frac{15}{5} = 0.6 \text{ p.u.}$$

$$X_{Tr} = 0.1 \text{ p.u.}$$


∴

$$I_F'' = \frac{E_g}{Z_1} = \frac{1.0}{(j0.3 \parallel j0.6) + j0.1}$$

$$= -j 3.333 \text{ p.u.}$$

Thus,
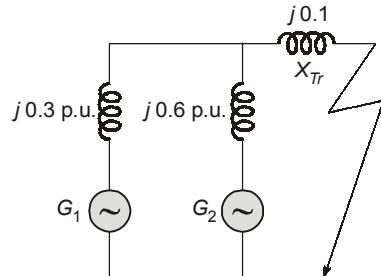
$$I_{G1}'' = \text{Subtransient current of generator-1} = -j 3.333 \text{ pu}$$



17. (a)

$$|I''| = \frac{E}{|X_d''|} = \frac{1}{0.22} = 4.54 \text{ p.u.}$$

$$I_{\text{base}} = \frac{\text{MVA}_b}{\sqrt{3}(kV_b)} = \frac{100 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 5248.6 \text{ A} = 5.248 \text{ kA}$$

The magnitude of initial symmetrical rms current

$$= 4.54 \times 5.248 = 23.82 \text{ kA}$$

18. (d)

Since the new branch is connected between bus-2 and reference bus, therefore

$$Z_{\text{bus, new}} = Z_{\text{bus, old}} - \frac{1}{(Z_{kk} + Z_s)} [2^{\text{nd}} \text{ column}] [2^{\text{nd}} \text{ row}]$$

or,

$$Z_{22, \text{ new}} = Z_{22, \text{ old}} - \frac{1}{(Z_{22} + Z_s)} (Z_{22})(Z_{22})$$

$$= 0.34 - \frac{1(0.34)(0.34)}{(0.34 + 0.1)}$$

$$= 0.0772 \text{ pu}$$

Also,

$$\begin{aligned} Z_{23, \text{ new}} &= Z_{23, \text{old}} - \frac{1}{(Z_{22} + Z_s)} (Z_{22})(Z_{23}) \\ &= 0.25 - \frac{1}{(0.34 + 0.1)} (0.34)(0.25) \\ &= 0.0568 \text{ pu} \end{aligned}$$

19. (a)

For three phase fault,

$$\begin{aligned} I_{f(3-\phi)} &= \frac{E}{X_1} \\ \Rightarrow 2000 &= \frac{\frac{11000}{\sqrt{3}}}{X_1} \\ X_1 &= \frac{11000}{\sqrt{3} \times 2000} = 3.175 \Omega \end{aligned}$$

For a line to line fault


$$\begin{aligned} I_{f(L-L)} &= \frac{\sqrt{3}E}{X_1 + X_2} \\ \Rightarrow 2600 &= \frac{\sqrt{3} \times \left(\frac{11000}{\sqrt{3}} \right)}{X_1 + X_2} \\ X_1 + X_2 &= 4.231 \Omega \\ X_2 &= 4.231 - 3.175 = 1.056 \Omega \end{aligned}$$

For SLG fault

$$\begin{aligned} I_{f(L-G)} &= \frac{3E}{X_1 + X_2 + X_0} \\ \Rightarrow 4200 &= \frac{3 \times \frac{11000}{\sqrt{3}}}{X_0 + X_1 + X_2} \\ X_0 + X_1 + X_2 &= 4.536 \Omega \\ X_0 + 4.231 &= 4.536 \\ X_0 &= 4.536 - 4.231 = 0.305 \Omega \end{aligned}$$

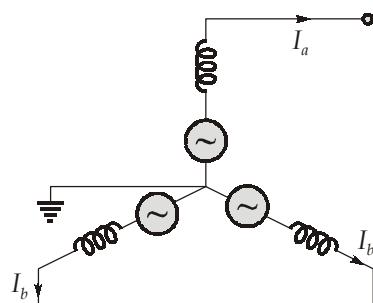20. (b)

Line-to line fault occurs on *b* and *c* phases of generator,




$$I_f = I_b = -I_c$$

and

$$I_a = 0$$

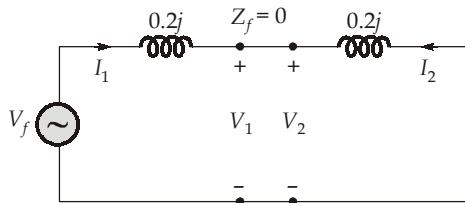The sequence network for line to line fault is



$$I_1 = \frac{V_f}{z_1 + z_2}$$

$$\Rightarrow I_f = I_b = (\alpha^2 - \alpha)I_1 = -j\sqrt{3}I_1 = \frac{-j\sqrt{3}V_f}{z_1 + z_2}$$

and

$$I_{f \text{ p.u.}} = \frac{-j\sqrt{3} \times 1}{j0.2 + j0.2}$$

$$|I_{f \text{ p.u.}}| = \frac{\sqrt{3}}{0.4} = 4.33 \text{ p.u.}$$

$$\text{Base current} = \frac{25 \times 10^3}{\sqrt{3} \times 11} = 1312.16 \text{ A}$$

$$\text{Fault current, } I_f = 4.33 \times 1312.16 = 5.68 \text{ kA}$$

21. (b)

Let the base kVA be 500 kVA and base voltage be 2.5 kV,


Per unit transient reactance of generator,

$$X_g' = \frac{j8}{100} = j0.08 \text{ p.u.}$$

Per unit subtransient reactance of each motor,

$$X_m'' = j0.2 \times \frac{500}{250} = j0.4 \text{ p.u.}$$

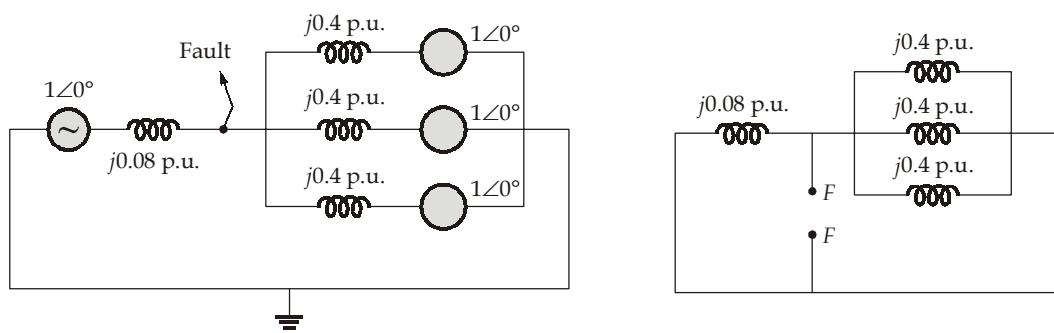Per unit reactance diagram is shown below,



Thevenin reactance when viewed from fault terminals,

$$X_{th} = \frac{\frac{j0.4}{3} \times j0.08}{\frac{j0.4}{3} + j0.08} = j0.05 \text{ p.u.}$$

At fault location V_{th} = rated voltage,

$$\text{Fault current at } F, I_f = \frac{1}{j0.05} = -j20 \text{ p.u.}$$

The generator contribution is,

$$I_g = -j20 \times \frac{j\frac{0.4}{3}}{j\frac{0.4}{3} + j0.08}$$

$$I_g = -j12.5 \text{ p.u.}$$

Contribution of motors,

$$3I_m = I_f - I_g = -j20 - (-j12.5)$$

$$3I_m = -j7.5$$

$$I_m = -j2.5 \text{ p.u.}$$

22. (c)

Only Y_{22} , Y_{24} , Y_{42} , Y_{44} will change because transmission line is connected between 2nd and 4th buses.

$$\begin{aligned} Y_{22} &= -j60 + \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} \\ &= -j60 + \frac{1}{j0.1} + j20 = -j60 - j10 + j20 = -j50 \end{aligned}$$

$$Y_{24} = Y_{42} = 0 - \frac{Y_{sh}}{2} = -j20$$

$$Y_{44} = -j25 + \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} = -j25 + \frac{1}{j0.1} + j20 = -j25 - j10 + j20$$

$$Y_{44} = -j15$$

23. (c)

Reactive power supplied by capacitor to bus-1,

$$Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_2||V_1|}{X} \cos \delta$$

Given that,

$$Q_{21} = 0$$

$$\frac{|V_2|^2}{X} = \frac{|V_2||V_1|}{X} \cos \delta$$

$$|V_2| = |V_1| \cos \delta$$

Given that,

$$|V_1| = 1 \text{ p.u.}$$

$$|V_2| = \cos \delta \quad \dots(i)$$

Since load demand at bus 2 is 1 p.u. (real power). This real power can be supplied by generator S_{G1} only. So this power should flow through transmission line from bus 1 to bus 2

$\therefore P_{12} = 1 \text{ p.u.}$
 $\therefore \text{real power flow from bus 1 to bus 2,}$

$$P_{12} = \frac{|V_1||V_2|}{X} \sin \delta$$

$$1 = \frac{1 \cdot \cos \delta}{0.5} \cdot \sin \delta$$

$$0.5 = \frac{\sin 2\delta}{2}$$

$$\sin 2\delta = 1$$

$$2\delta = 90^\circ$$

$$\delta = 45^\circ$$

\therefore from equation (i),

$$|V_2| = \cos \delta = \cos 45^\circ = \frac{1}{\sqrt{2}}$$

$$\text{Voltage at bus-2, } V_2 = \frac{1}{\sqrt{2}} \angle -45^\circ$$

24. (d)

$$\begin{aligned} \text{Inertia constant, } H &= 4 \text{ MW-sec/MVA} \\ &= 4 \text{ MJ/MVA} \end{aligned}$$

$$\text{No load voltage, } V_1 = 1.2 \text{ p.u.}$$

$$\text{Infinite bus voltage, } V_2 = 1 \text{ p.u.}$$

$$\begin{aligned} \text{Total reactance, } X &= X_G + X_L = 0.25 + 0.15 \\ X &= 0.4 \text{ p.u.} \end{aligned}$$

$$\text{Angular momentum, } M = \frac{GH}{\pi f} = \frac{1 \times 4}{\pi \times 50} = 0.0254 \text{ p.u.}$$


$$\text{For 80% loading, } \sin \delta_0 = \frac{80}{100} = 0.8$$

$$\cos \delta_0 = \sqrt{1 - \sin^2 \delta_0} = \sqrt{1 - 0.8^2} = 0.6$$

$$\therefore \frac{\partial P_e}{\partial \delta} = \frac{V_1 V_2}{X} \cos \delta_0 = \frac{1.2 \times 1}{0.4} \times 0.6 = 1.8$$

$$\begin{aligned} f_n &= \sqrt{\left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0}} = \sqrt{\frac{1.8}{0.0254}} = 8.41 \text{ rad/sec} \\ &= 1.34 \text{ Hz} \end{aligned}$$

25. (a)

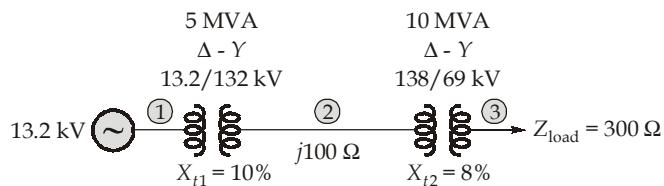

Let,

$$S_{\text{base}} = 10 \text{ MVA}$$

$$V_{\text{base}} = 13.8 \text{ kV}$$

Base impedance at section-3,

$$Z_{3 \text{ base}} = \frac{(69 \times 10^3)^2}{10 \times 10^6} = 476.1 \Omega$$

$$Z_{\text{load}} = \frac{300}{476.1} = 0.63 \text{ p.u.}$$

Base impedance at section-2,


$$Z_{2 \text{ base}} = \frac{(138 \times 10^3)^2}{10 \times 10^6} = 1904.4 \Omega$$

$$Z_{\text{line}} = \frac{j100}{1904.4} = j0.0525 \text{ p.u.}$$

$$X_{t1 \text{ (new)}} = 0.1 \times \left(\frac{132}{138} \right)^2 \times \frac{10}{5} = 0.183 \text{ p.u.}$$

$$X_{t2} = 0.08 \text{ p.u.}$$
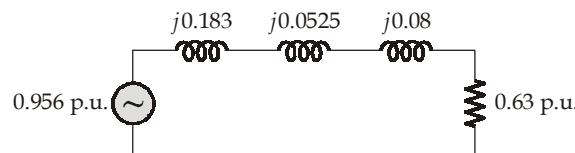
$$E_s = \frac{13.2}{13.8} = 0.956 \text{ p.u.}$$



$$V_L = 0.956 \times \frac{0.63}{j(0.183 + 0.0525 + 0.08) + 0.63}$$

$$V_L \text{ (p.u.)} = 0.956 \times \frac{0.63}{\sqrt{(0.3155)^2 + (0.63)^2}} = 0.854$$

$$\begin{aligned} \text{Voltage at load} &= V_L \text{ (p.u.)} \times V_L \text{ (base)} \\ &= 0.854 \times 69 \text{ kV} \\ &= 58.926 \text{ kV} \end{aligned}$$

26. (b)


Let base MVA = 10 MVA

Per unit reactance of each generator is 0.3 p.u.

Per unit reactance of each reactor is 0.1 p.u.

Per unit reactance of each transformer on the base MVA
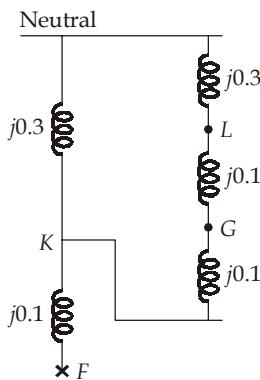
$$= \frac{5}{100} \times \frac{10}{5} = 0.1 \text{ p.u.}$$



Total per unit impedance from generator neutral upto fault point F

$$\begin{aligned} &= 0.1 + [(0.3) \parallel (0.5)] \\ &= 0.1 + \frac{(0.3)(0.5)}{(0.3) + (0.5)} = 0.2875 \text{ p.u.} \end{aligned}$$

$$\text{Short circuit MVA} = \frac{\text{Base MVA}}{\text{Per unit fault reactance}} = \frac{10}{0.2785} = 34.78 \text{ MVA}$$

27. (c)

The rating of the machine, G = 100 MVA

$$\begin{aligned} \text{Inertia constant, } H &= 5 \text{ kW-s/kVA} \\ &= 5 \text{ KJ/KVA} = 5 \text{ MJ/MVA} \end{aligned}$$

Kinetic energy stored in the rotating parts of generator and turbine at synchronous speed ($f = 50 \text{ Hz}$)
 $= HG = 5 \times 100 = 500 \text{ MJ}$

Excess power input to the generator shaft before the steam valve begins to close,
 $= 100 - 60 = 40 \text{ MW}$

Excess energy transferred to rotating parts in 0.5 sec
 $= 40 \times 0.5 = 20 \text{ MJ}$

Since, Kinetic energy, $K.E. \propto (\text{speed})^2 \propto f^2$

So, frequency at the end of 0.5 sec

$$\begin{aligned} f_2 &= f_1 \sqrt{\frac{\text{Total energy stored in 0.5 sec}}{\text{Energy stored at synchronous speed}}} \\ f_2 &= 50 \sqrt{\frac{500 + 20}{500}} = 50 \times 1.02 \approx 51 \text{ Hz} \end{aligned}$$


$$\begin{aligned} \text{Change in frequency} &= f_2 - f_1 \\ &= 51 - 50 \approx 1 \text{ Hz} \end{aligned}$$

28. (c)

By equalizing the station,

$$P_{G_1} = P_{G_2} = 20 \text{ p.u.}$$

$$\begin{aligned} \text{Now, } 5 &= \frac{|E||V|}{|X|} \sin\delta = \frac{1 \times 1}{0.05} \sin\delta \\ \delta &= 14.47^\circ \end{aligned}$$

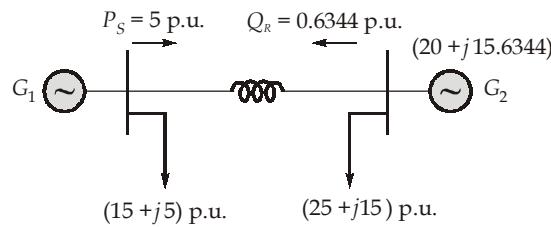

$$Q_R = \frac{|V_1| |V_2|}{X} \cos \delta - \frac{|V_1|^2}{X} = -0.6344 \text{ p.u.}$$

$$\begin{aligned}\text{Total load on station 2} &= (25 + j15) + (-5 + j0.6344) \\ &= (20 + j15.6344)\end{aligned}$$

$$\begin{aligned}\text{Power factor of station 2} &= \cos\left(\tan^{-1}\left(\frac{15.6344}{20}\right)\right) \\ &= 0.78 \text{ lagging}\end{aligned}$$

29. (a)


Base MVA = 2 MVA

The p.u. reactance of 2 MVA transformer is $j0.1$ p.u.

The p.u. reactance of 10 MVA transformer,

$$\begin{aligned}X_{\text{p.u. (new)}} &= X_{\text{p.u.(old)}} \times \frac{2}{10} \\ &= 0.1 \times \frac{2}{10} = 0.02 \text{ p.u.}\end{aligned}$$

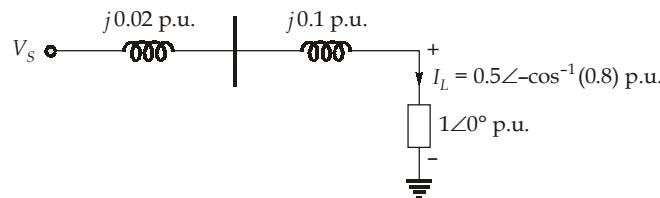The load current is 0.5 p.u. for 2 MVA base



KVL in the loop:

$$\begin{aligned}V_S &= I_L Z + V \angle 0^\circ \\ &= [(0.5 \angle -36.87^\circ)(j0.12)] + (1 \angle 0^\circ) \\ &= 1.037 \angle 2.65^\circ \text{ p.u.} \\ V_S &= 1.037 \times 33 = 34.22 \text{ kV}\end{aligned}$$

30. (b)

Sum of the line currents in a Δ is always zero

$$\begin{aligned}I_a + I_b + I_c &= 0 \\ I_b &= -I_a\end{aligned}$$

$$\begin{aligned}I_{a1} &= \frac{1}{3} [I_a + \alpha I_b + \alpha^2 I_c] = \frac{1}{3} [I_a - \alpha I_a] \\ &= \frac{I_a (1 - 1 \angle 120^\circ)}{3} = \frac{(10 \angle 0^\circ) (1 - 1 \angle 120^\circ)}{3} \\ I_{a1} &= 5.77 \angle -30^\circ \text{ A}\end{aligned}$$

