



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Noida | Bhopal | Hyderabad | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

CLASS TEST 2019-2020

ELECTRICAL ENGINEERING

Date of Test : 04/06/2019

ANSWER KEY > Digital Electronics

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (d) | 7. (c) | 13. (a) | 19. (a) | 25. (c) |
| 2. (b) | 8. (c) | 14. (d) | 20. (b) | 26. (c) |
| 3. (a) | 9. (c) | 15. (c) | 21. (c) | 27. (d) |
| 4. (c) | 10. (c) | 16. (b) | 22. (c) | 28. (d) |
| 5. (c) | 11. (c) | 17. (d) | 23. (a) | 29. (c) |
| 6. (b) | 12. (a) | 18. (c) | 24. (c) | 30. (b) |

DETAILED EXPLANATIONS

1. (d)

Since P is stuck at '1', output Y will be zero if $X = 1$.

Here,
$$X = (A + B) + (\bar{B}C) = A + (B + \bar{B})(B + C)$$

Thus,
$$X = A + B + C = 1$$

2. (b)



If the Present Count is $\rightarrow 1001100111$

then Next Count will be $\rightarrow 10011101000$


We observe that '4' flip-flops are complemented to reach next count.

  3. (a)

Applying alternate logic symbol for all the four gates and redrawing the circuit bubbled OR gate is NAND gate and $A \odot \bar{B} = A \oplus B$.



5. (c)

 

7. (c)

number of flip-flops required = 4

maximum delay = $4 \times 10 \text{ nsec} = 40 \text{ nsec}$

8. (c)

$$\begin{aligned} (AB + \bar{B}C + \bar{A}C)(A + C) &= AB + AB\bar{C} + ABC + \bar{A}C \\ &= AB + \bar{A}C \end{aligned}$$

9. (c)

Range of signed 1's complement number is $-2^{n-1} + 1$ to $2^{n-1} - 1$.

10. (a)

Numbers of 4×16 decoders required

$$\frac{256}{16} = 16$$


$$\frac{16}{16} = 1 = 16 + 1 = 17$$

11. (c)


	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
\bar{D}	0	2	4	6	8	10	12	14
D	1	3	5	7	9	11	13	15
D	0	0	0	1	D	1	\bar{D}	0

So, the function F is $\Sigma m(1, 6, 7, 9, 10, 11, 12)$.The number of minterms in F is 7 so number of maxterms will be 9.

12. (a)

 AND - OR Realization of the function Y is

Equivalent NAND-NAND realization

 

So, number of two input NAND gates required is '6'.

13. (a)

Let us consider active high input.

		YZ			
		00	01	11	10
X	0	0	1	1	0
	1	0	1	0	1

$$\begin{aligned}
 F &= \Sigma(1, 3, 5, 6) \\
 &= \bar{X}Z + \bar{Y}Z + XY\bar{Z} \\
 &= (Y+Z) \cdot (X+Z) \cdot (\bar{X} + \bar{Y} + \bar{Z})
 \end{aligned}$$

14. (d)

$$F = \overline{(XYZ) \oplus (XY) \oplus (YX) \oplus (XZ)}$$

X	Y	Z	XY	YZ	ZX	XYZ	F
0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	1
0	1	0	0	0	0	0	1
0	1	1	0	1	0	0	0
1	0	0	0	0	0	0	1
1	0	1	0	0	1	0	0
1	1	0	1	0	0	0	0
1	1	1	1	1	1	1	1

		YZ			
		00	01	11	10
X	0	1	1		
	1			1	

$$= \bar{X}\bar{Y} + \bar{Y}\bar{Z} + \bar{Z}\bar{X} + XYZ$$

15. (c)

		CD			
		00	01	11	10
AB	00			1	1
	01				
	11	1		1	1
	10	1		1	1

Number of essential prime implicants are 3.

16. (b)

Clock frequency $f = 100 \text{ KHz}$

$$\text{Time period of clock} = T_{\text{CLK}} = \frac{1}{f} = \frac{1}{100 \times 10^3}$$

$$T_{\text{CLK}} = 10^{-5} \text{ sec}$$

\therefore Number of bits = $n = 8$

\Rightarrow Maximum conversion time of an 8-bit digital ramp ADC = $(2^n - 1) T_{\text{CLK}}$

$$T_1 = (2^8 - 1) \times T_{\text{CLK}} = (2^8 - 1) \times 10^{-5} = 2550 \mu \text{ sec}$$

Maximum conversion time of successive approximation ADC = $n \cdot T_{\text{CLK}}$

$$T_2 = nT$$

$$T_2 = 8 \times 10^{-5} \text{ sec} = 80 \mu \text{ sec}$$

$$\frac{T_1}{T_2} = \frac{2550}{80} = 31.875 \approx 31.88$$

17. (d)

$$\text{Total count} \Rightarrow M = (16383)_{10}$$

as we know that,

$$\text{Number of required flip-flops } (n) \geq \log_2(M + 1)$$

$$n \geq \log_2(16383 + 1)$$

$$n \geq \log_2(16384)$$

$$\{\log_2 16384 = \frac{\log_{10} 16384}{\log_{10} 2}\}$$

$$n \geq 14$$

So, 14 flip-flops are required.

18. (c)

	Q_A	Q_B	Q_C	$Q_A \oplus Q_C$
	1	1	0	1
1	1	0	1	0
2	0	1	0	0
3	1	0	0	1
4	0	0	1	1
5	0	1	1	1

After 5 clock pulse $Q_A Q_B Q_C$ will be 011.

19. (a)

Analog voltage = resolution \times binary equivalent


$$= \frac{15}{2^5} \times [2^5 \times 0 + 2^4 \times 1 + 2^3 \times 1 + 2^2 \times 1 + 2^1 \times 0 + 2^0 \times 1] = 6.79 \text{ V}$$

21. (c)

Race around condition never occurs in dynamic or edge triggering.

Static shift registers are made up of flip-flops while dynamic shift registers are made up of CMOS.

22. (c)

 

$$Y = A\bar{C} + BC$$

$$f = Y\bar{D} + CD$$


$$f = (A\bar{C} + BC)\bar{D} + CD = A\bar{C}\bar{D} + BC\bar{D} + CD$$

$$f(A, B, C, D) = \Sigma m(3, 6, 7, 8, 11, 12, 14, 15)$$

		CD	
		C	D
AB	00		1
	01		1
	10	1	1
	11	1	

 23. (a)

$$\begin{aligned}
 I_{13} &\rightarrow A \ B \ C \ D \\
 &\quad 1 \ 1 \ 0 \ 1 \\
 A' &= A \oplus B = 1 \oplus 1 = 0 \\
 B' &= B \cdot D = 1 \cdot 1 = 1 \\
 C' &= \overline{\overline{D}} = D = 1 \\
 D' &= \overline{\overline{C}} = \overline{0} = 1 \\
 I_n &\rightarrow A' \ B' \ C' \ D' \\
 &\quad 0 \ 1 \ 1 \ 1 \\
 (A' \ B' \ C' \ D') &= 7 \\
 \Rightarrow n &= 7
 \end{aligned}$$



24. (c)

Let a number N is given to the system
 output after 1's compliment = $15 - N$
 output after 2's compliment = $16 - 15 + N = N + 1$
 3 such systems are connected in cascade.
 so final output = Input + $(3)_{10} = 1010 + 0011 = 1101$

25. (c)

Q_3	Q_2	Q_1
0	0	0
0	0	1
0	1	0
1	0	0
1	0	1
1	1	0
0	0	0

Total number of possible states = $2^3 = 8$
 used states = 6
 unused states = $8 - 6 = 2$

26. (c)

$$\begin{aligned}
 S_1 &= A \oplus B \\
 C_1 &= AB \\
 S &= (A \oplus B) \oplus AB = (A \oplus B) \cdot \overline{AB} + (\overline{A \oplus B}) \cdot AB \\
 &= (A\overline{B} + \overline{A}B) (\overline{A} + \overline{B}) + (AB + \overline{A}\overline{B}) (A, B) = A\overline{B} + \overline{A}B + AB = A + B \\
 C &= (A \oplus B) \cdot AB = (A\overline{B} + \overline{A}B) \cdot AB = 0
 \end{aligned}$$

27. (d)

Number of function using n variables is 2^{2^n} .

Since, here $n = 3$, so number of function is 256.

28. (d)

Let us assume initial outputs of both the flip flops to be 0.

Clock	D_1	D_2	Q_1	Q_2	\bar{Q}_1	\bar{Q}_2	Y
0	1	0	0	0	1	1	0
1	1	1	1	0	0	1	0
2	0	1	1	1	0	0	1
3	0	0	0	1	1	0	0
4	1	0	0	0	1	1	0
5	1	1	1	0	0	1	0
6	0	1	1	1	0	0	1

Thus, the output sequence is Y(0 0 1 0 0 0 1...)

Thus the period of output is four clock cycles. For one clock cycle output is high and for three cycles it is low. Thus,

$$\text{Duty cycle} = \frac{T_{ON}}{T_{ON} + T_{OFF}} \times 100 = \frac{1}{4} \times 100 = 25\%$$

29. (c)

Here

$$\begin{aligned} J_0 &= 1, \\ K_0 &= Q_2, \\ J_1 &= \bar{Q}_2 \odot Q_0, \\ K_1 &= 1, \\ J_2 &= Q_1, \\ K_2 &= 1 \end{aligned}$$

Clock	Present state $Q_2 Q_1 Q_0$	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$	Next state $Q_2 Q_1 Q_0$
0	0 0 0	0 1	0 1	1 0	0 0 1
1	0 0 1	0 1	1 1	1 0	0 1 1
2	0 1 1	1 1	1 1	1 0	1 0 1
3	1 0 1	0 1	0 1	1 1	0 0 0
4	0 0 0	0 1	0 1	1 0	0 0 1

Thus output will have four states (000, 001, 011, 101) and after 115 clock pulses output will be at 101.

30. (b)

$$(10)_{10}^3 = (1000)_{10} = (4096)_{10}$$

$$(64)_{10}^2 = (X)_{10}^2$$

\Rightarrow

$$X = 64$$

◆◆◆◆