

ANSWER KEY > Digital Electronics


1. (c)	7. (a)	13. (c)	19. (b)	25. (a)
2. (c)	8. (d)	14. (c)	20. (c)	26. (b)
3. (c)	9. (c)	15. (d)	21. (d)	27. (d)
4. (b)	10. (c)	16. (a)	22. (c)	28. (c)
5. (b)	11. (c)	17. (a)	23. (b)	29. (a)
6. (b)	12. (b)	18. (c)	24. (a)	30. (d)

DETAILED EXPLANATIONS

1. (c)

$$\begin{aligned}(AB + B\bar{C} + \bar{A}C)(A + C) &= AB + AB\bar{C} + ABC + \bar{A}C \\ &= AB + \bar{A}C\end{aligned}$$

2. (c)

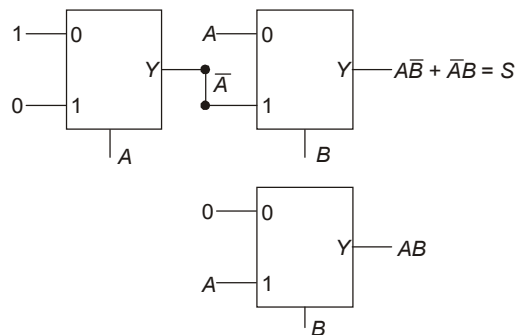

3. (c)
 number of flip-flops required = 4
 maximum delay = $4 \times 10 \text{ nsec} = 40 \text{ nsec}$
4. (b)
 Total number of states possible with 11 flip-flops = $2^{11} = 2048$
 Required states = 2014
 Number of states to be eliminated
 = $2048 - 2014 = 34$
5. (b)
 When MOD 5 and MOD 4 counters are cascaded, the combination becomes MOD 20 counter.
 So, output frequency,

$$f_o = \frac{f_i}{20} = \frac{20}{20} = 1 \text{ MHz}$$
6. (b)
 In 2's complement data representation, range with n-bit is: $-(2^{n-1})$ to $+(2^{n-1} - 1)$.
 So, 8-bit 2's complement can represent numbers between -128 to $+127$.
7. (a)
 In the given digital circuit each multiplexer is working as a NOT gate thus it is a ring oscillator with five NOT gates. The frequency of oscillation will be $f = \frac{1}{2Nt_{pd}}$.
- N = number of NOT gates in cascade
 t_{pd} = propagation delay of each NOT gate.
- \therefore
$$f = \frac{1}{2 \times 5 \times 25 \text{ ns}} = 4 \times 10^6 \text{ Hz} = 4 \text{ MHz.}$$
8. (d)
 From the figure $J = \bar{Q}, K = 1$.

Clock	J	K	Q	Q ⁺
–	1	1	0	–
1	1	1	0	1
2	0	1	1	0
3	1	1	0	1
4	0	1	1	0
5	1	1	0	1

Hence, sequence of Q is 010101.

9. (c)
 Divide by 78 counter can be realized by using cascade of MOD-13 and MOD-6 counter.
10. (c)

$$\begin{aligned}
 Q^+ &= \bar{X}\bar{Y} + X\bar{Y}Q + \bar{X}Y\bar{Q} = \bar{Y}[\bar{X} + XQ] + \bar{X}Y\bar{Q} \\
 &= \bar{Y}\bar{X} + \bar{Y}Q + \bar{X}Y\bar{Q} = \bar{Y}Q + \bar{X}[\bar{Y} + Y\bar{Q}] = \bar{Y}Q + \bar{X}\bar{Y} + \bar{X}\bar{Q} \\
 Q^+ &= \bar{Y}Q + \bar{X}\bar{Q} \quad \text{[using Consensus Law]}
 \end{aligned}$$

11. (c)

$$\begin{array}{r} \textcircled{1} \textcircled{1} \textcircled{1} \\ \text{G A T E} \\ + \text{E E E} \\ \hline \text{T 7 E A} \end{array}$$

13. (c)

$$\begin{aligned} S_1 &= A \oplus B \\ C_1 &= AB \\ S &= (A \oplus B) \oplus AB = (A \oplus B) \cdot \overline{AB} + (\overline{A \oplus B}) \cdot AB \\ &= (\overline{AB} + \overline{AB}) (\overline{A} + \overline{B}) + (AB + \overline{AB}) (A, B) = \overline{AB} + \overline{AB} + AB = A + B \\ C &= (A \oplus B) \cdot AB = (\overline{AB} + \overline{AB}) \cdot AB = 0 \end{aligned}$$

14. (c)

Q_3	Q_2	Q_1	
0	0	0	← Initial state
0	0	1	1 st clock pulse
0	1	1	2 nd clock pulse
1	0	1	3 rd clock pulse
0	0	0	4 th clock pulse

⇒ Modulus of the counter is 4, After 8 clock pulses $Q_3 Q_2 Q_1$ will be 101

15. (d)

From the figure we can see that

- 1st change at $t = 1$ ns is accepted, so 6th bit i.e. MSB is 1
- 2nd change at $t = 2$ ns is not accepted, so 5th bit is 0.
- 3rd change at $t = 3$ ns is not accepted, so 4th bit is 0.
- 4th change at $t = 4$ ns is accepted, so 3rd bit is 1.
- 5th change at $t = 5$ ns is not accepted, so 2nd bit is 0.
- 6th change at $t = 6$ ns is accepted, so 1st bit is 1.

So, digital output is $(100101)_2$.

16. (a)

The following table represent the output of the multiplexer.

Clock	Counter Output			MUX Input			Output
	A_2	A_1	A_0	S_1	S_0	Enable	
–	1	0	1	0	1	1	I_1
1	1	0	0	0	1	0	0
2	0	1	1	1	0	1	I_2
3	0	1	0	1	0	0	0

17. (a)

Since, % accuracy is 0.02 thus the maximum error will be

$$= \text{maximum output} \times \frac{(0.02)}{100} = 5 \times \frac{(0.02)}{100} = 1 \text{ mV}$$


18. (c)

The input D is $Q_0 \oplus Q_2 \oplus Q_3$.

Clock	D	Q_3	Q_2	Q_1	Q_0
–	–	1	0	0	0
1	1	1	1	0	0
2	0	0	1	1	0
3	1	1	0	1	1
4	0	0	1	0	1
5	0	0	0	1	0
6	0	0	0	0	1

Hence, the pattern 0001 appears at 6th pulse.

19. (b)

 

	A	B	C	Y
$t < 10$ ns	1	1	0	0
10 ns $< t < 20$ ns	1	0	0	1
20 ns $< t < 30$ ns	1	0	1	1
30 ns $< t < 40$ ns	1	0	0	0
40 ns $< t$	1	0	0	1

⇒ option (b) is correct.

20. (c)

$$Y = \overline{ABC} + \overline{A}B + BC$$

Dual of Y

$$\begin{aligned} Y_d &= \overline{(A+B+C) \cdot (\overline{A} + \overline{B}) \cdot (B+C)} \\ &= \overline{[(A+B+C) + (\overline{A} + \overline{B})] \cdot (B+C)} \end{aligned}$$


Compliment of Y

$$Y_c = \overline{\overline{(\overline{ABC} + \overline{A}B) + BC}} = \overline{\overline{(\overline{ABC} + \overline{A}B)} \cdot \overline{BC}} = (\overline{ABC} + \overline{A}B) \cdot \overline{BC}$$


21. (d)

State Table

A	B	Q_{n+1}	J	K
0	0	\overline{Q}_n	1	1
0	1	1	1	0
1	0	Q_n	0	0
1	1	0	0	1

 

22. (c)

 

By checking all the options option (c) correctly matches.

23. (b)

Initially $Q_0 = Q_1 = 0$
 $\Rightarrow Y_0 = 0$

\Rightarrow J - K flip-flop is cleared

$Q_A = 0$ $\bar{Q}_A = 1$

As clock pulse is applied counter starts up counting

As counter reaches $Q_1 = 1, Q_0 = 1$ after 3 clock pulses J - K flip flop is preset.

$\Rightarrow Q_A = 1$ $\bar{Q}_A = 0$

\Rightarrow Counter starts down counting until Y_0 is low and this repeats.

So, Output $Q_1 Q_0$ in decimal form is

0, 1, 2, 3, 2, 1, 0, 1....

24. (a)

$$\overline{\text{Chipselect}} = \overline{(A_2 \odot A_3) \cdot [(A_4 \odot A_5) + (A_6 \odot A_7)]}$$

$$\text{Chip select} = (A_2 \odot A_3) \cdot [(A_4 \odot A_5) + (A_6 \odot A_7)]$$

Chip select will be '1' when

$$[(A_2 = A_3) \text{ and } (A_4 \neq A_5) \text{ and } (A_6 \neq A_7)]$$

Since A_1, A_0 are not present in expression of chip select they can have any value.

So the address combination for chip select = 1 are

	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
1	0	1	1	0	0	0	x	x
2	1	0	1	0	0	0	x	x
3	1	0	0	1	0	0	x	x
4	0	1	0	1	0	0	x	x
5	0	1	1	0	1	1	x	x
6	1	0	1	0	1	1	x	x
7	1	0	0	1	1	1	x	x
8	0	1	0	0	1	1	x	x

We get 8 combinations only 1st combination match with option a

25. (a)

In the circuit, we have

$$D_0 = \overline{Q_1 \cdot Q_2} = \overline{Q_1} + \overline{Q_2}$$

$$D_1 = Q_0$$

$$D_2 = Q_1$$

The truth table for the circuit is obtained below.

CLK	Input			Output		
	D_2	D_1	D_0	Q_2	Q_1	Q_0
0	0	0	1	0	0	0
1	0	1	1	0	0	1
2	1	1	1	0	1	1
3	1	1	0	1	1	1
4	1	0	0	1	1	0
5	0	0	0	1	0	0

The D-flip flop transfer the data from input to output, if CLK pulse is given. After 4 clock pulses, output is

$$Q_2 Q_1 Q_0 = 110$$

26. (b)

Since clock is applied to ÷ 12 counter. The AND gates have open collector output so RST will be '1' if both the AND gates produce '1'. Thus RST will be 1 when output of top counter is '0110' and output of bottom counter is '1001'. From the circuit we can determine that after every twelve pulses of clock, one pulse of CLK reach to the top counter. So,

Clock	Output of bottom counter	Output of top counter	Z
0	0000	0000	0
.	.	.	.
.	.	.	.
11	1011	0000	0
12	0000	0001	0
.	.	.	.
.	.	.	.
23	1011	0001	0
24	0000	0010	0
.	.	.	.
.	.	.	.
35	1011	0010	0
36	0000	0011	0
.	.	.	.
.	.	.	.
47	1011	1011	0
48	0000	0100	1
.	.	.	.
.	.	.	.
59	1011	0100	1
60	0000	0101	1
.	.	.	.
.	.	.	.
71	1011	0101	1
72	0000	0110	1
.	.	.	.
.	.	.	.
81	1001	0110	0
82	0000	0000	0

So Z remain 1 for (12 + 12 + 9) clock cycles

$$\text{So duty cycle} = \frac{12 + 12 + 8}{12 + 12 + 12 + 12 + 12 + 12 + 8} \times 100 = 39.5\%$$

27. (d)

$$S_1 = \text{SUM} = A \oplus B \text{ and } S_0 = \text{CARRY} = A \cdot B$$

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

$$= (A \oplus B)' (AB)' C + (A \oplus B)' (AB) C + (A \oplus B) (AB)' C' + (A \oplus B) (AB) C'$$

$$Y = A \oplus B \oplus C$$

28. (c)

Given circuit is of 8 to 1 multiplexer. Multiplexer is used to select any one input out of all inputs at a time. Hence, output will be equal to I_5 for a particular combination of selection lines.

For $D = 1;$

$C = 0;$

$A = 1$

combination selects the I_5 . Also, we have the given logic function as

$$F = AC + ABD + ACD + BCD$$

So, by substituting $D = 1, C = 0,$ and $A = 1,$


We get

$$F = 0 + B + 0 + 0$$

$$F = B$$

Thus, input to I_5 must be equal to B .

29. (a)

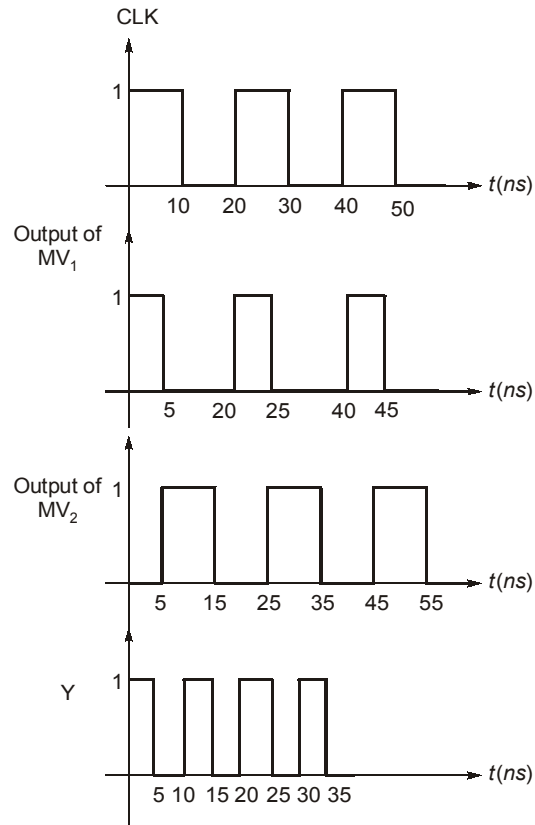

Since $Y = (\text{output of } MV_2) \oplus \text{CLK}$
So the time period of Y is 100 MHz

30. (d)

$$\begin{array}{r} A = 10\ 10\ 10\ 10 \\ B = 11\ 11\ 11\ 11 \\ \hline \text{Ex-NOR} : 10\ 10\ 10\ 10 \end{array}$$

Gray code of 10 10 10 10 is 11 11 11 11

Decimal equivalent of (11111111) = 255

