



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Lucknow | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ANALOG ELECTRONICS

ELECTRONICS ENGINEERING

Date of Test : 10/07/2022

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (d) | 7. (c) | 13. (a) | 19. (c) | 25. (d) |
| 2. (d) | 8. (b) | 14. (c) | 20. (b) | 26. (c) |
| 3. (b) | 9. (c) | 15. (c) | 21. (a) | 27. (d) |
| 4. (b) | 10. (c) | 16. (b) | 22. (c) | 28. (b) |
| 5. (b) | 11. (a) | 17. (c) | 23. (c) | 29. (c) |
| 6. (a) | 12. (b) | 18. (b) | 24. (b) | 30. (b) |

DETAILED EXPLANATIONS

1. (d)

When D_2 is ON then the value of V_0 will be


$$V_0 = 3 - 0.7 \text{ V} = 2.3 \text{ V}$$

Hence, D_1 will be OFF.

Thus, The current, $I = \frac{2.3 - (-3)}{5} \times 10^{-3} = \frac{5.3}{5} \times 10^{-3} = 1.06 \text{ mA}$

2. (d)

The circuit can be redrawn as,

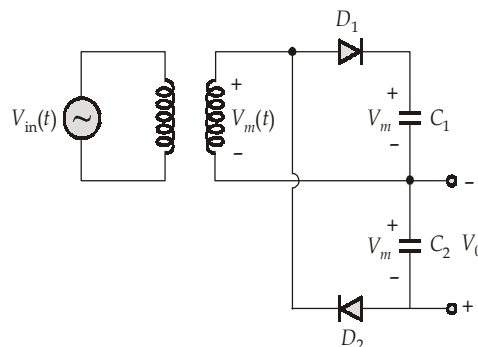

The circuit represents a voltage doubler circuit, if the voltage was taken by adding voltages of both the capacitors, but to calculate V_0 we have to find the voltage stored on a single capacitor. Thus, comparing from the above figure,

$$V_0 = -V_m$$

3. (b)

The early voltage V_A can be calculated as

$$V_A = r_0 I_C$$

where $r_0 = \text{output resistance} = \frac{1}{\text{slope of } I_C - V_{CB} \text{ curve}}$

$$r_0 = \frac{1}{3 \times 10^{-5}}$$

thus, $V_A = \frac{1}{3 \times 10^{-5}} \times 3 \times 10^{-3} = 100 \text{ V}$ ($\because I_C = 3 \times 10^{-3} \text{ A}$)

6. (a)


Since, the op-amp represents a closed loop unity gain amplifier.

Thus,

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}}$$

$$= \frac{999}{1 + 999} = 0.999$$


7. (c)
 In the given circuit

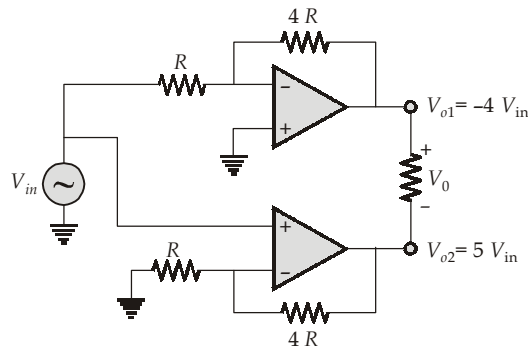

$$\begin{aligned} \therefore V_o &= V_{o1} - V_{o2} \\ &= -4 V_{in} - 5 V_{in} \\ &= -9 V_{in} \end{aligned}$$


$$\therefore \frac{V_o}{V_{in}} = -9$$

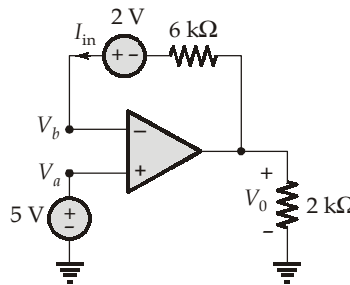8. (b)
 Since, negative feedback is applied to the op-amp, thus the concept of virtual ground is applicable.



Thus, $V_a = V_b$
 now, since the op-amp is ideal thus $I_{in} = 0$
 Hence
$$\begin{aligned} V_o &= V_b - 2 V \\ &= 5 V - 2 V \\ &= 3 V \end{aligned}$$

9. (c)

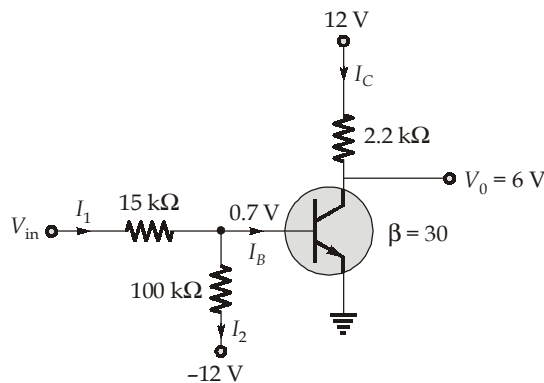

Now,
$$I_C = \frac{12 - 6}{2.2} \times 10^{-3} = 2.727 \text{ mA}$$

\therefore
$$I_B = \frac{I_C}{\beta} = \frac{2.727}{30} = \frac{1}{11} \text{ mA}$$


Now,
$$I_2 = \frac{0.7 - (-12)}{100 \text{ k}\Omega} = 0.127 \text{ mA}$$

\therefore
$$I_1 = I_2 + I_B = 0.218 \text{ mA}$$

thus,
$$V_{in} = I_1 \times 15 \times 10^3 \Omega + 0.7$$

$$V_{in} = 3.968 \text{ V} \approx 3.97 \text{ V}$$

10. (c)

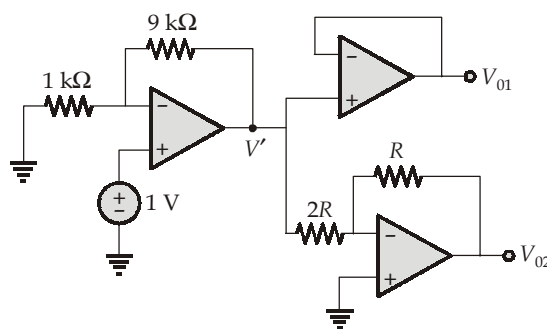

$$V' = \left(1 + \frac{9 \text{ k}\Omega}{1 \text{ k}\Omega} \right) \times 1 \text{ V} \quad (\because \text{non-inverting amplifier})$$

$$V' = 10 \text{ V}$$

now,
$$V_{01} = V' = 10 \text{ V} \quad (\because \text{it is a voltage buffer})$$

and
$$V_{02} = -\frac{R}{2R} V' \quad (\because \text{inverting amplifier})$$

$$V_{02} = -\frac{1}{2} V' = -\frac{10 \text{ V}}{2} = -5 \text{ V}$$

\therefore
$$V_{02} - V_{01} = -5 \text{ V} - 10 \text{ V} = -15 \text{ V}$$

11. (a)

The current of both the transistors are equal since they are perfectly matched.

Thus,
$$\frac{I}{2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS1} - V_t)^2$$


$$10 \times 10^{-3} = \frac{1}{2} \times 500 \times 10^{-6} \times 100 (V_{GS1} - 0.5)^2$$

\therefore
$$V_{GS1} = V_{GS2} = 1.132 \text{ V}$$

Thus,
$$V_S = V_{cm} - V_{GS1} = 3 - 1.132 = 1.868 \text{ V}$$

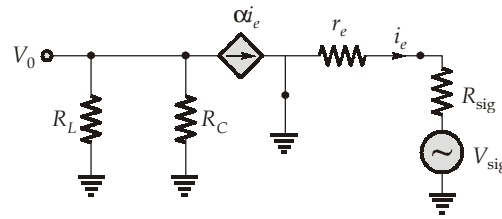12. (b)

The small signal r_e equivalent circuit can be drawn as



$$V_0 = -\alpha(R_C \parallel R_L)i_e \quad \dots(i)$$

and

$$i_e = \frac{-V_{sig}}{R_{sig} + r_e} \quad \dots(ii)$$

Combining equation (i) and (ii), we get,

$$V_0 = \frac{\alpha(R_C \parallel R_L)}{R_{sig} + r_e} \cdot V_{sig}$$

thus,

$$\frac{V_0}{V_{sig}} = \frac{\alpha(R_C \parallel R_L)}{R_{sig} + r_e}$$

13. (a)

$$\frac{V_0}{V_i} = -g_m R_C$$

now,


$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{2V_T} = \frac{1 \times 10^{-3}}{2 \times 25 \times 10^{-3}} = 20 \text{ mA/V}$$

∴

$$\frac{V_0}{V_{in}} = -20 \times 10^{-3} \times 1 \times 10^3 = -20 \text{ V/V}$$

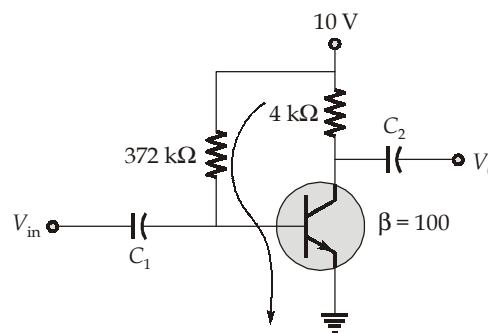
14. (c)

Applying KVL in base-emitter loop, we get,



$$I_B = \frac{10 - 0.7}{372 \text{ k}\Omega} = 25 \mu\text{A}$$

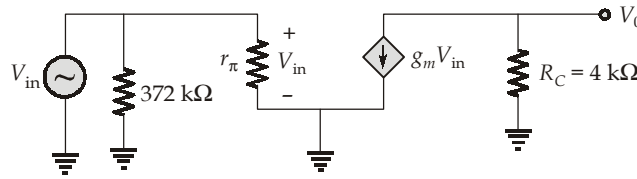To draw the small signal we need to calculate r_π



$$\therefore r_{\pi} = \frac{V_T}{I_{B_{DC}}} = \frac{25 \times 10^{-3}}{25 \times 10^{-6}} = 10^3 \Omega$$

now,


$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{10^3} = 0.1 \text{ A/V}$$

now,

$$A_v = \frac{V_0}{V_{in}} = -g_m R_C = -0.1 \times 4 \times 10^3 = -400$$

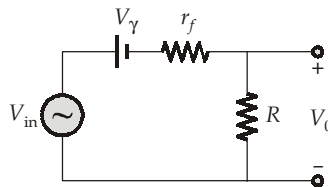15. (c)

The small signal equivalent model can be drawn as



\(\therefore\) The output can be expressed as,

$$V_0 = \frac{R}{R + r_f} V_{in} - \frac{R}{R + r_f} V_{\gamma} \quad \dots(i)$$

Thus, the slope of line in the graph of the input output curve can be written

$$\text{Slope} = \frac{R}{R + r_f} = \frac{1.2}{2 - 0.7} = \frac{1.2}{1.3} \quad \dots\text{from equation (i)}$$

Thus,

$$r_f = 83.33 \Omega$$

16. (b)

In the transistor $V_{GS} = V_{DS}$

Since, the gate and drain terminals are shorted, the transistor will always be in saturation mode.

thus,

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

now,


$$I_D = \frac{V_0}{R} = \frac{3}{3} \times 10^{-3} = 1 \text{ mA}$$

thus,

$$1 \times 10^{-3} = \frac{50 \times 10^{-3}}{2} \left(\frac{W}{L} \right) \times (2 - 1)^2$$

$$\left(\frac{W}{L} \right) = \frac{1}{25} = 0.04$$

17. (c)

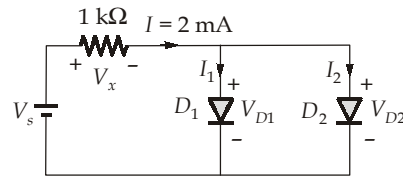

$$V_s = V_x + V_{D1} \quad (\because V_{D1} = V_{D2})$$

and

$$I = I_1 + I_2$$

thus

$$2 \times 10^{-3} = 10^{-12} \left[e^{\frac{V_{D1}}{26 \times 10^{-3}}} - 1 \right] + 10^{-10} \left[e^{\frac{V_{D1}}{26 \times 10^{-3}}} - 1 \right]$$

$$2 \times 10^{-3} \approx 10^{-10} (1.01) \cdot e^{\frac{V_{D1}}{26 \times 10^{-3}}}$$

$$\frac{V_{D1}}{26 \times 10^{-3}} = \ln(1.9801 \times 10^7) = 16.801$$

∴

$$V_{D1} = 0.437 \text{ V}$$


Now,

$$V_x = 2 \times 10^{-3} \times 1 \times 10^3 = 2 \text{ V}$$

$$V_s = V_x + V_{D1} = 2 + 0.437 = 2.437 \text{ V}$$

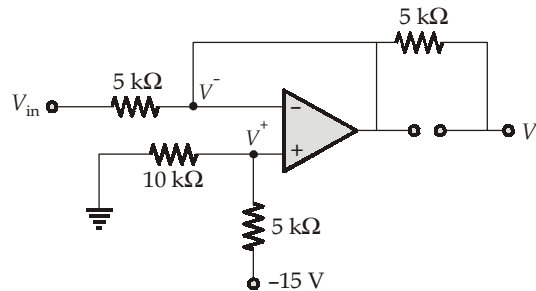18. (b)

Case -I : When $V_{in} > -10 \text{ V}$, then the voltage across diode D_1 is positive so diode D_1 is in ON state, and therefore the equivalent circuit can be drawn as



$$V^+ = -15 \times \frac{10}{15} = -10 \text{ V}$$

Due to virtual ground, $V^+ = V^- = -10 \text{ V}$


and $V_0 = V^- = -10 \text{ V}$

∴ $V_0 = -10 \text{ V}$

Case -II : When $V_{in} < -10 \text{ V}$

$$V_0 = +V_{sat}$$

Thus,

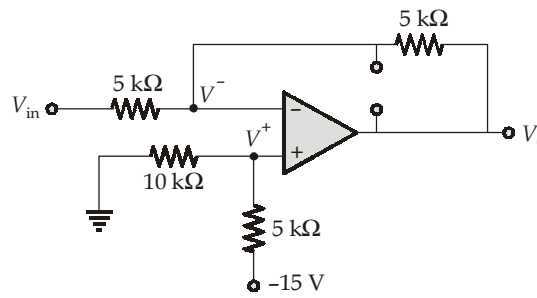

∴ $V_0 = -\frac{5}{5} \times V_{in} = -V_{in}$ (for $V_{in} < -10$ V)


Alternately, we can write the equation of the graph by applying KCL at node V-

∴ $V^- = V^+ = -10$ V

$$\frac{-10 - V_{in}}{5 \text{ k}\Omega} + \frac{-10 - V_0}{5 \text{ k}\Omega} = 0$$


$$-20 - V_{in} - V_0 = 0$$

$$V_0 = -V_{in} - 20$$

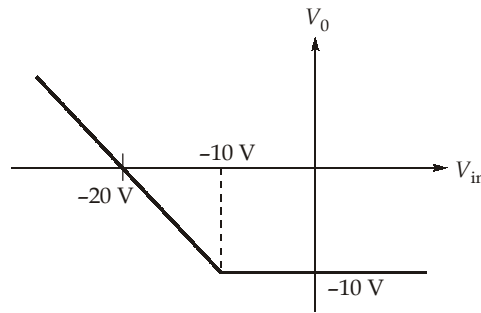

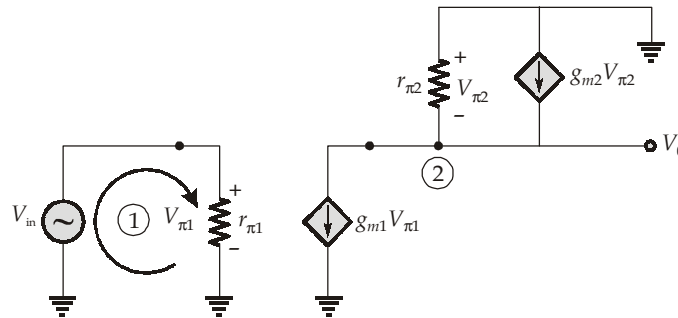19. (c)

Drawing the small signal equivalent model of the transistor, we get,



Now,

$$V_{in} = V_{\pi 1}$$

and

$$V_0 = -V_{\pi 2}$$

Applying KCL at node-2 we get

$$g_{m1} V_{\pi 1} + \frac{V_0}{r_{\pi 2}} = g_{m2} V_{\pi 2}$$

$$\Rightarrow g_{m1} V_{in} + \frac{V_0}{r_{\pi 2}} = -g_{m2} V_0$$

$$V_0 \left[\frac{1}{r_{\pi 2}} + g_{m2} \right] = -g_{m1} V_{in}$$

$$|A_v| = \left| \frac{V_0}{V_{in}} \right| = \frac{g_{m1} r_{\pi 2}}{1 + g_{m2} r_{\pi 2}}$$


Since $\beta \gg 1$ for both the transistors.

Thus, the above expression can be approximated as

$$|A_v| \approx \frac{g_{m1}}{g_{m2}}$$

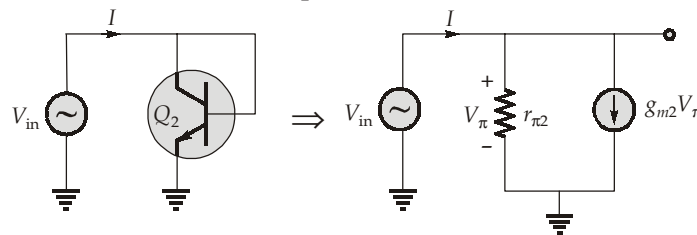20. (b)

For transistor Q_2 , we can calculate the equivalent resistance as



$$\therefore I = \frac{V_{\pi}}{r_{\pi 2}} + g_{m2} V_{\pi}$$

Now,


$$V_{in} = V_{\pi}$$

$$\therefore \frac{I}{V_{in}} = \frac{1}{r_{\pi 2}} + g_{m2}$$

or

$$R' = r_{\pi 2} \parallel \frac{1}{g_{m2}}$$

Now, the circuit can be redrawn as

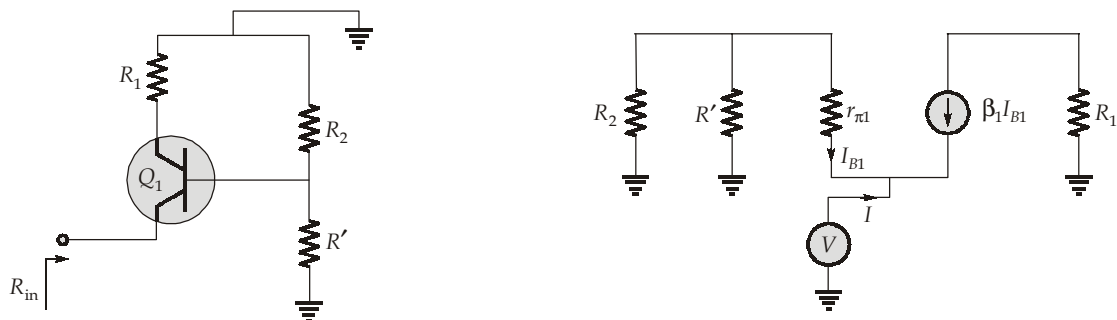

$$I = -I_{B1} - \beta_1 I_{B1}$$

$$I = -(1 + \beta_1) I_{B1}$$

Now,

$$I_{B1} = \frac{-V}{r_{\pi 1} + R' \parallel R_2}$$

$$\therefore \frac{V}{I} = \frac{r_{\pi 1} + R' \parallel R_2}{\beta_1 + 1}$$

$$\therefore R_{in} = \frac{1}{\beta_1 + 1} \left(r_{\pi 1} + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_2 \right)$$

$$\therefore \text{where, } \beta_1 = 99$$

$$\therefore R_{in} = \frac{1}{100} \left(r_{\pi 1} + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_2 \right)$$

21. (a)

In the circuit, the capacitor starts charging from 0 V (as the switch was initially closed) towards the steady state value of 20 V.


Now, when the switch is flipped open, the capacitor will charge upto 20 V.

$$\therefore V_c(t) = V_c(\infty) - [V_c(0) - V_c(\infty)]e^{-t/RC}$$

$$RC = 1 \times 10^3 \times 0.01 \times 10^{-6} = 10 \mu\text{sec}$$

$$\therefore V_c(t) = 20 (1 - e^{-t/RC})$$

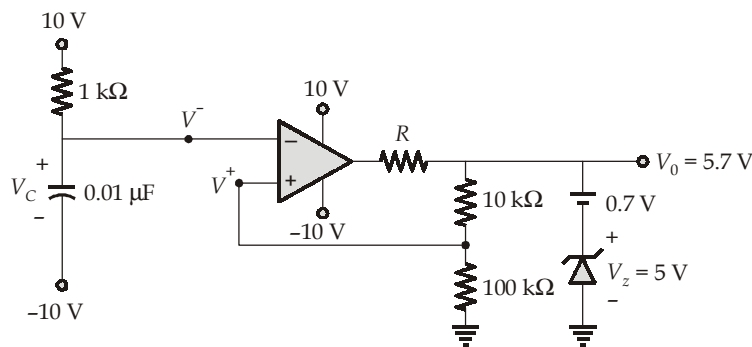Voltage at non-inverting amplifier is obtained as



$$V^+ = V_0 \times \frac{100 \text{ k}\Omega}{(10 + 100) \text{ k}\Omega}$$

$$V^+ = V_0 \times \frac{100}{110} = \frac{V_0 \times 10}{11}$$

\therefore Initially V^- was equal to -10 V, thus $V_0 = +5.7$ V.

Thus, now capacitor will start charging as soon as the switch is opened.

Thus, $V^- = V_C - 10$ V

or, $V_C = V^- + 10$ V

now, $V^- = V^+ = \frac{5.7 \text{ V} \times 10}{11}$ [\therefore the op-amp will switch]

thus, $V_C = \frac{10 \times 5.7}{11} + 10$

now, $V_C = 20(1 - e^{-t/RC})$

$$\therefore 20(1 - e^{-t/RC}) = 10 + \frac{57}{11}$$


$$1 - e^{-t/RC} = \frac{1}{2} + \frac{57}{220}$$

$$1 - e^{-t/RC} = 0.7590$$

$$e^{-t/RC} = 0.2409$$


$$T = 14.23 \mu\text{sec}$$

Hence, the output voltage wave will be,

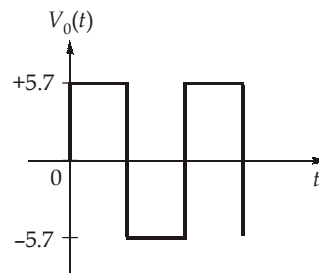

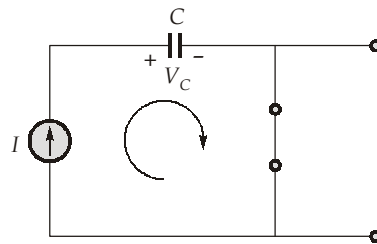22. (c)


For negative cycle $V_{in} < 3.2$ V always, thus the MOSFET M_1 will be OFF and diode D_1 will be ON



$$\therefore V_c = \frac{I}{C} \cdot t$$

$$\Rightarrow V_c = \frac{I}{C} \cdot T_{off} = \frac{I}{C} (1 - D)T$$

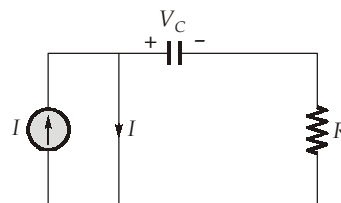Now, when $V_{in} > 3.2$ V, thus the MOSFET transistor will be switched ON and hence



Now, since R is very large, thus, V_c will not reduce substantially and thus, V_c will not change during the positive going pulse.

Hence, after 5 clock pulse value of V_c


$$V_c = \frac{5I}{C} (1 - D)T$$

23. (c)

Now,
$$g_{m1} = 2\sqrt{k_{n1}I_{D1}} = 2\sqrt{0.5 \times 0.2 \times 10^{-6}} = 0.632 \text{ mA/V}$$

and
$$g_{m2} = 2\sqrt{k_{n2}I_{D2}} = 2\sqrt{(0.2)(0.5) \times 10^{-6}} = 0.632 \text{ mA/V}$$

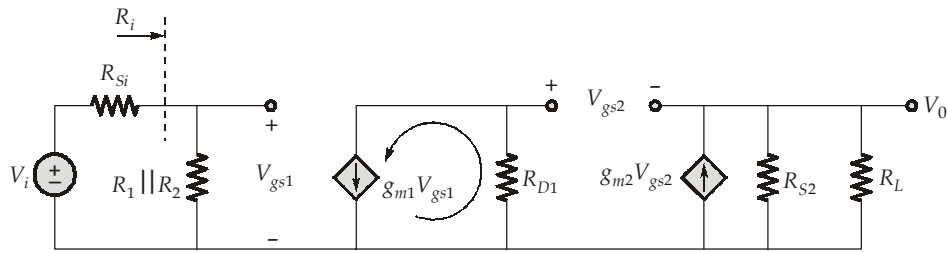Now, drawing the small signal equivalent circuit, we get,



Now, $V_0 = g_{m2}(R_{S2} || R_L) \cdot V_{gs2} \dots (i)$

Also, $V_{gs2} + V_0 = -g_{m1} V_{gs1} R_{D1} \dots (ii)$

and $V_{gs1} = \frac{R_1 || R_2}{R_1 || R_2 + R_{Si}} \times V_i \dots (iii)$

Putting values of V_{gs1} and V_{gs2} from equation (i) and (iii) in equation (ii), we get

$$\frac{V_0}{g_{m2}(R_{S2} || R_L)} + V_0 = -g_{m1} R_{D1} \left[\frac{R_1 || R_2}{R_1 || R_2 + R_{Si}} \right] \cdot V_i$$

$$\therefore A_V = \frac{V_0}{V_i} = \frac{-g_{m1} g_{m2} R_{D1} (R_{S2} || R_L)}{1 + g_{m2} (R_{S2} || R_L)} \times \left[\frac{R_1 || R_2}{R_1 || R_2 + R_{Si}} \right]$$

Now, $R_{S2} || R_L = \frac{8}{3} \text{ k}\Omega$

$R_1 || R_2 = 99.8 \text{ k}\Omega \approx 100 \text{ k}\Omega$

$$\therefore A_v = \frac{V_0}{V_i} = \frac{-(0.632)(0.632)(16.1)(8/3)}{1 + (0.632)(8/3)} \times \left[\frac{100}{104} \right] \approx -6.14$$

24. (b)

Applying KVL in the circuit shown below, we get,

$$2V_{BE1} = V_{BE3} + I_0 R_E$$

(\because both the transistor are matched with negligible base current thus $V_{BE1} = V_{BE2}$ for same I_{reff}).


Now, $V_{BE1} = V_T \ln \left(\frac{I_{\text{reff}}}{I_s} \right)$

$$V_{BE3} = V_T \ln \left(\frac{I_0}{I_s} \right)$$

$$2V_T \ln \left(\frac{I_{\text{reff}}}{I_s} \right) - V_T \ln \left(\frac{I_0}{I_s} \right) = I_0 R_E$$

$$V_T \ln \left(\frac{I_{\text{reff}}^2}{I_0 I_s} \right) = I_0 R_E$$
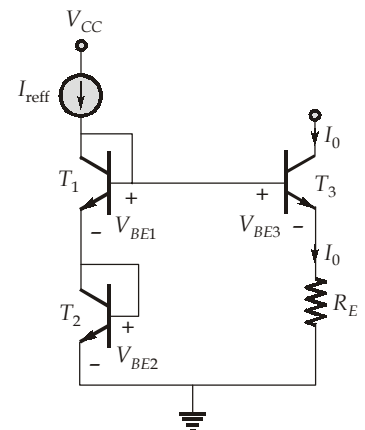
$$R_E = \frac{V_T}{I_0} \ln \left(\frac{I_{\text{reff}}^2}{I_0 I_s} \right) = 0.208 \ln \left(\frac{625}{10 \times 120 \times 10^{-3}} \right) = 15.638 \text{ k}\Omega$$



25. (d)

$$I_D = k_n(V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$$r_0 = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{1}{(\partial I_D / \partial V_{DS})}$$

$$\frac{\partial I_D}{\partial V_{DS}} = k_n(V_{GS} - V_{th})^2 \lambda$$

at $V_{GS} = 0.5, I_D = 1 \text{ mA}$
 so, $1 \text{ mA} = k_n(V_{GS} - V_{th})^2 (1 + 0.05)$

$$k_n(V_{GS} - V_{th})^2 = \frac{1}{1.05} \text{ m}\bar{U}$$

$$r_0 = \frac{1.05}{0.1} \text{ k}\Omega = 10.5 \text{ k}\Omega$$

26. (c)

Assuming all the diodes are forward biased,

$$V_B = -0.7 \text{ V}$$

$$V_A = 0 \text{ V}$$

$\therefore I_2 = \frac{10 - 0}{10 \text{ k}} = 1 \text{ mA}$

and $I_1 = \frac{-0.7 - (-10)}{10 \text{ k}} = 0.93 \text{ mA}$

$\therefore I_2 = I_{D1} + I_{D2}$

and $I_1 = I_{D2} + I_{D3}$

applying KVL in the outer loop, we get,

$$10 \text{ k}I_2 + 0.7 + 10 \text{ k}I_{D1} - 20 = 10$$

$$10 \text{ k}(I_{D1} + I_{D2}) + 10 \text{ k}I_{D1} = 30 - 0.7 = 29.3$$

$$20 \text{ k}I_{D1} + 10 \text{ k}I_{D2} = 29.3$$

$$2I_{D1} + I_{D2} = 2.93 \text{ mA} \tag{... (i)}$$

also, $I_{D1} + I_{D2} = I_2 = 1 \text{ mA} \tag{... (ii)}$

from (i) and (ii)

$$I_{D1} = 1.93 \text{ mA and } I_{D2} = -0.93 \text{ mA}$$

$\therefore I_{D2} + I_{D3} = 0.93 \text{ mA}$


$\Rightarrow I_{D3} = -I_{D2} + 0.93 \text{ mA} = 1.86 \text{ mA}$

Here I_{D2} is negative, Hence, our assumption is incorrect.

Therefore, D_2 is reverse biased

and $\therefore I_{D1}$ and I_{D3} are positive,

D_1, D_3 are forward biased.

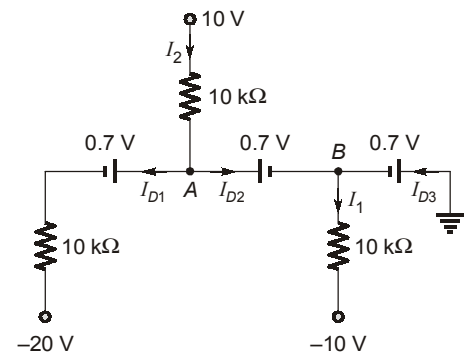

27. (d)

By applying superposition theorem, we get,
 When V_1 at non-inverting terminal is shorted

$$V_{01} = -\frac{40}{20}V_1 = -2V_1 \quad \dots(i)$$

When V_1 at inverting terminal is shorted, then

$$V_{02} = \left[1 + \frac{40}{20}\right] \times \left[\frac{30}{30+30}\right] V_1 = 3 \times \frac{3}{6} V_1 = 1.5 V_1 \quad \dots(ii)$$

Combining equation (i) and (ii), we get,

$$\begin{aligned} V_0 &= V_{01} + V_{02} = -2V_1 + 1.5V_1 \\ &= -\frac{V_1}{2} \end{aligned}$$

28. (b)

$$V_{P-P} = 8 \text{ V}$$

Thus, $v(t) = 4\sin(\omega t)$

$$V^- = 2 \text{ V}$$

$$\therefore \text{Duty cycle} = \frac{T_{\text{on}}}{T_{\text{total}}} = \frac{\theta_{\text{on}}}{\theta_{\text{total}}}$$

now, $\theta_1 = \sin^{-1}\left(\frac{2}{4}\right)$

$$\theta_1 = \frac{\pi}{6}$$


and

$$\theta_2 = \pi - \frac{\pi}{6} = \frac{5\pi}{6}$$


thus,

$$\theta_{\text{on}} = \frac{5\pi}{6} - \frac{\pi}{6} \text{ and } \theta_{\text{total}} = 2\pi$$
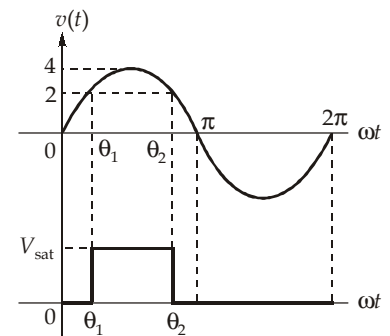
$$\therefore \text{Duty cycle} = \frac{\frac{5\pi}{6} - \frac{\pi}{6}}{2\pi} \times 100 = 33.33\%$$



29. (c)

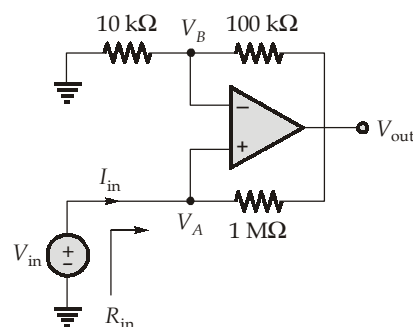

now, $I_{\text{in}} = \frac{V_A - V_0}{1 \text{ M}\Omega} \quad \dots(i)$

Applying KCL at inverting terminal, we get,

$$\frac{V_B - 0}{10 \text{ k}\Omega} + \frac{V_B - V_0}{100 \text{ k}\Omega} = 0$$

$$\frac{V_B}{10 \text{ k}\Omega} = \frac{V_0 - V_B}{100 \text{ k}\Omega} \quad \dots(ii)$$


now $V_B = V_A$ due to virtual ground

thus,
$$\frac{V_A}{10 \text{ k}\Omega} = - \left[\frac{V_A - V_0}{100 \text{ k}\Omega} \right]$$

$$\therefore \frac{V_A}{10 \text{ k}\Omega} = \frac{-I_{in} \times (1 \text{ M}\Omega)}{100 \text{ k}\Omega}$$

$$\frac{V_{in}}{I_{in}} = -100 \text{ k}\Omega \quad \{ \because V_A = V_{in} \}$$

30. (b)
 For the transistor

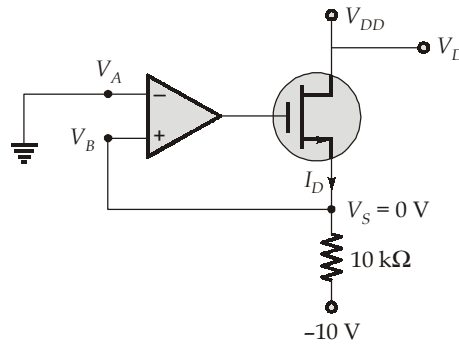

$$V_S = V_B = V_A$$

due to virtual ground,
 thus,

$$V_S = 0 \text{ V}$$

Hence,

$$I_D = \frac{0 - (-10)}{10 \times 10^3} = 1 \text{ mA}$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$\therefore V_{GS} - V_T = \sqrt{\frac{I_D}{\frac{\mu_n C_{ox} W}{2L}}}$$

$$V_{GS} - V_T = \sqrt{\frac{1 \times 10^{-3}}{\frac{0.5 \times 10^{-3}}{2}}}$$

$$V_{GS} - V_T = 2 \text{ V}$$

For the MOSFET to be in saturation region

$$V_{DS} \geq V_{GS} - V_T$$

\therefore at the edge of saturation

$$V_{DS} = V_{GS} - V_T = 2 \text{ V}$$

$\therefore V_S = 0$

$\therefore V_D = V_G - V_T$

$\Rightarrow V_{DD} = 2 \text{ V}$

