



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Lucknow | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ELECTRIC CIRCUITS

ELECTRICAL ENGINEERING


Date of Test : 20/07/2022

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (c) | 7. (a) | 13. (b) | 19. (a) | 25. (a) |
| 2. (d) | 8. (c) | 14. (c) | 20. (d) | 26. (c) |
| 3. (d) | 9. (b) | 15. (a) | 21. (c) | 27. (b) |
| 4. (d) | 10. (a) | 16. (a) | 22. (c) | 28. (c) |
| 5. (b) | 11. (b) | 17. (c) | 23. (b) | 29. (b) |
| 6. (b) | 12. (c) | 18. (a) | 24. (c) | 30. (c) |

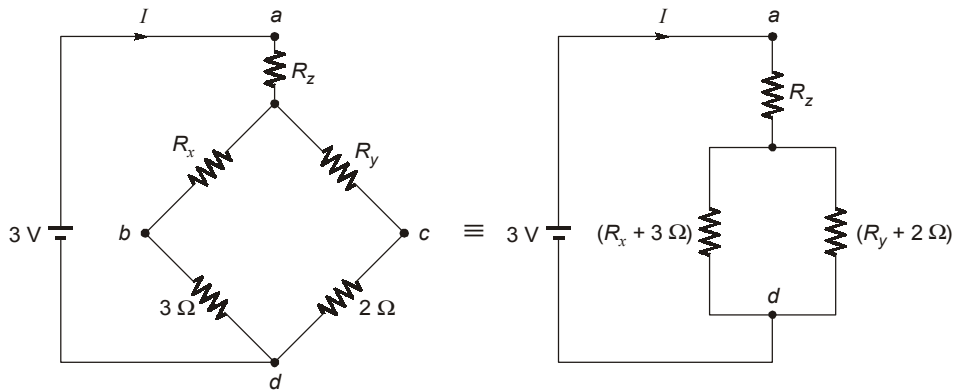1. (c)

Let us convert Δabc to $Y xyz$ where R_x , R_y and R_z are the component resistors. Thus, the given circuit can be redrawn as



$$\therefore R_{ad} = [(R_x + 3) \parallel (R_y + 2)] + R_z$$

Where, $R_x = R_y = R_z = \frac{5}{3} = 1.667 \Omega$

$$\begin{aligned} \therefore R_{ac} &= [(1.667 + 3) \parallel (1.667 + 2)] + 1.667 \\ &= [(4.667 \parallel 3.667) + 1.667] \Omega = 3.721 \Omega \end{aligned}$$

$$\therefore \text{Source current } I = \frac{3}{3.721} = 0.806 \text{ A}$$


2. (d)

Here 5 V and -5 V sources are in series

$$\therefore 5 - 5 = 0 \text{ V (short circuit)}$$

Also 4 A and 4 A sources are in series which is equivalent to a 4A source.

\therefore The circuit can be redrawn as

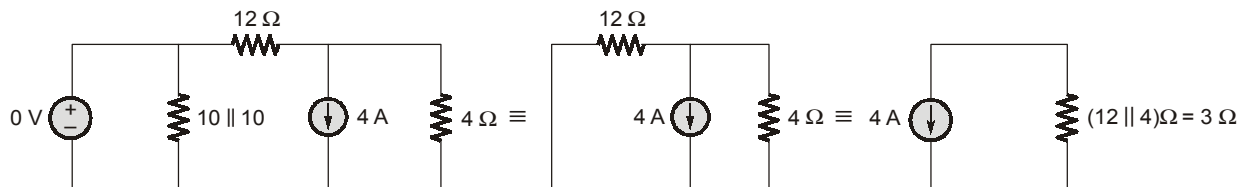

3. (d)

For maximum power to be transferred,

$$Z_L = Z_s^*$$

Here, $Z_s = (2 - j4) \Omega$

$$\therefore Z_s^* = (2 - j4)^* = (2 + j4) \Omega$$


4. (d)

When the switch was open, the current source drives the current through R - L circuit thus


$$i_L(0^-) = i_L(0^+) = 2 \text{ A}$$

and

$$v_c(0^-) = v_c(0^+) = 0 \text{ V}$$

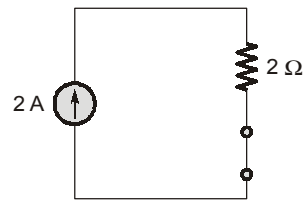

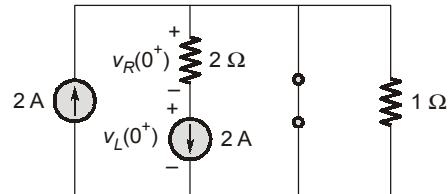After closing the switch, at $t = 0^+$ the capacitor acts as a short circuit.



However, the inductor current remains at 2 A.

$$\begin{aligned} \therefore v_R(0^+) + v_L(0^+) &= 0 \text{ V} \\ v_L(0^+) &= -v_R(0^+) = -i_L(0^+) \times R = -2 \times 2 = -4 \text{ V} \end{aligned}$$

5. (b)

$$v_2(t) = M \frac{di_1(t)}{dt} \quad (\because \text{secondary coil is open circuited})$$

$$M = k\sqrt{L_1 L_2} = 0.25\sqrt{0.6 \times 0.6} = 0.15 \text{ H}$$

$$\text{So, } v_2(t) = M \frac{di_1(t)}{dt} = 0.15 \frac{d}{dt} (6 \sin 100t) \text{ V}$$

$$\text{or, } v_2(t) = 0.15 \times 6 \times 100 \cos 100t \text{ V} = 90 \cos 100t \text{ V}$$

6. (b)

$$i(t) = \frac{V}{Z} = \frac{A \cos \omega t}{2 + j\omega}$$

$$\begin{aligned} \text{Now, } V_2 &= Z_2(j\omega)i(t) \\ V_1 &= Z_1(j\omega)i(t) \\ \frac{V_2}{V_1} &= \frac{1 + j\omega}{1} = 1 + j\omega \end{aligned}$$

$$\therefore \phi = \tan^{-1} \left(\frac{\omega}{1} \right) = \frac{\pi}{4}$$

$$\frac{\omega}{1} = 1$$

$$\omega = 1 \text{ rad/sec}$$

7. (a)

$$V_1 = 5I$$

Applying KVL around the loop we get

$$10 \angle 30^\circ - 1 \times I - 0.5(5I) - 5I = 0$$

$$V_{oc} = 5I = \frac{10 \angle 30^\circ}{8.5} \times 5 = \frac{10 \angle 30^\circ}{1.7}$$

$$I_{sc} = \frac{10 \angle 30^\circ}{1} = 10 \angle 30^\circ \text{ A}$$

$$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{1}{1.7} = 0.588 \Omega$$

8. (c)

For parallel resonant circuit

$$Q_0 = R\sqrt{\frac{C}{L}}$$

$$Q_0 = 2000\sqrt{\frac{54 \times 10^{-6}}{240 \times 10^{-3}}}$$

$$Q_0 = 2000\sqrt{\frac{9}{4} \times 10^{-4}} = \frac{2000}{100} \times \frac{3}{2} = 30$$

9. (b)

Since no independent source in the network, thus $V_{th} = 0$ V.


$$\therefore V = R_{eq} I_1$$

$$-I_1 + \frac{V-0}{4} + \frac{V-2I_1}{2} = 0$$

or
$$-I_1 + \frac{V}{4} + \frac{V-2I_1}{2} = 0$$


$$\frac{V}{4} + \frac{V}{2} = 2I_1$$

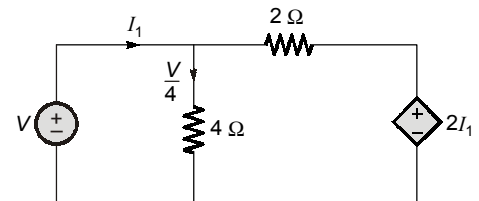or
$$\frac{V}{I_1} = R_{eq} = 2.667 \Omega$$



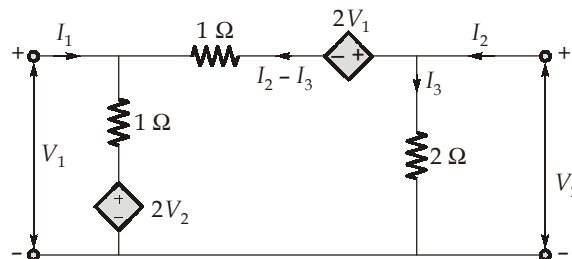10. (a)

Transforming the dependent current source in to voltage source, the network is shown as,



Let I_3 be the current through 2Ω

Apply KVL in outer loop,

$$-V_2 + 2V_1 + I_2 - I_3 + V_1 = 0$$

$$-V_2 + 3V_1 + I_2 - I_3 = 0$$

...(i)

Also,

$$-V_1 + I_1 + I_2 - I_3 + 2V_2 = 0$$

$$V_1 = I_1 + I_2 - I_3 + 2V_2$$

...(ii)

From equation (i) and (ii), we get

$$5V_2 + 3I_1 + 4I_2 - 4I_3 = 0$$

Where,
$$I_3 = \frac{V_2}{2}$$

$$V_2 = -I_1 - \frac{4}{3}I_2$$

Hence,
$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = -1 \Omega$$

11. (b)

$$\begin{aligned} Z_{Th} &= (40 - j30) \parallel j20 \\ &= \frac{j20(40 - j30)}{j20 + 40 - j30} = (9.412 + j22.35) \Omega \end{aligned}$$

By voltage division,

$$\begin{aligned} V_{th} &= \frac{j20}{j20 + 40 - j30} (150 \angle 30^\circ) \\ &= 72.76 \angle 134^\circ \text{ V} \end{aligned}$$

The value of R_L that will absorb the maximum average power is

$$R_L = |Z_{th}| = \sqrt{(9.412)^2 + (22.35)^2} = 24.25 \Omega$$


The current through the load is,

$$I = \frac{V_{th}}{Z_{th} + R_L} = \frac{72.76 \angle 134^\circ}{33.66 + j22.35} = 1.8 \angle 100.416^\circ$$


The maximum average power absorbed by R_L is

$$\begin{aligned} P_{\max} &= \frac{1}{2} |I|^2 R_L = \frac{1}{2} (1.8)^2 (24.25) \\ &= 39.285 \approx 39.29 \text{ W} \end{aligned}$$

12. (c)

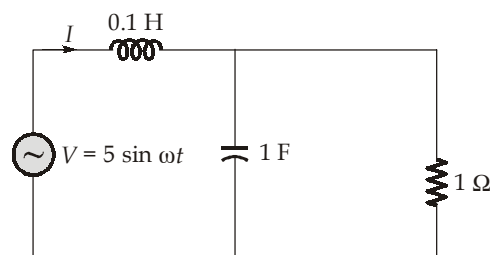

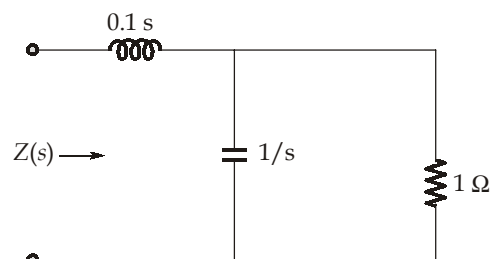For V and I in phase imaginary part of $Z(s)$, should be zero,



$$Z(s) = \frac{\frac{1}{s} \times 1}{\frac{1}{s} + 1} + 0.1s = \frac{1 + 0.1s + 0.1s^2}{s + 1}$$

multiplying numerator and denominator by $(s - 1)$

$$\begin{aligned} Z(s) &= \frac{(0.1s^2 + 0.1s + 1)(s - 1)}{(s + 1)(s - 1)} \\ &= \frac{0.1s^3 + 0.1s^2 + s - 0.1s^2 - 0.1s - 1}{s^2 - 1} \end{aligned}$$

Put $s = j\omega$

$$Z(j\omega) = \frac{0.1(j\omega)^3 + 0.9(j\omega) - 1}{(j\omega)^2 - 1} = \frac{j(0.9\omega - 0.1\omega^3) - 1}{-\omega^2 - 1}$$

Equating imaginary part to zero,


$$0.9\omega - 0.1\omega^3 = 0$$

$$\omega^2 = 9$$

$$\omega = \pm 3 \text{ rad/sec}$$

Alternative Solution:

In frequency domain,

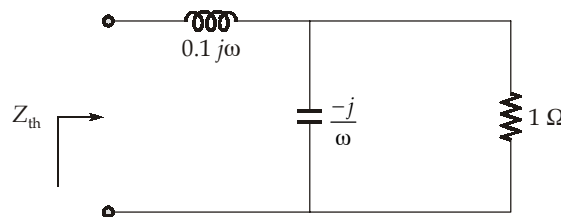

$$Z_{th} = \frac{(1)(-j/\omega)}{1 - j/\omega} + 0.1j\omega$$

$$\Rightarrow \frac{j}{j - \omega} + 0.1j\omega = 0$$

$$\Rightarrow \frac{j(j + \omega)}{(j - \omega)(j + \omega)} + 0.1j\omega = 0$$


$$\Rightarrow \frac{1 - j\omega}{1 + \omega^2} + 0.1j\omega = 0$$

For V and I in phase, imaginary term = 0

$$\text{Thus, } \frac{-\omega}{1 + \omega^2} + 0.1\omega = 0$$

$$\Rightarrow \omega = 3 \text{ rad/s}$$

13. (b)
Using de-coupled technique,

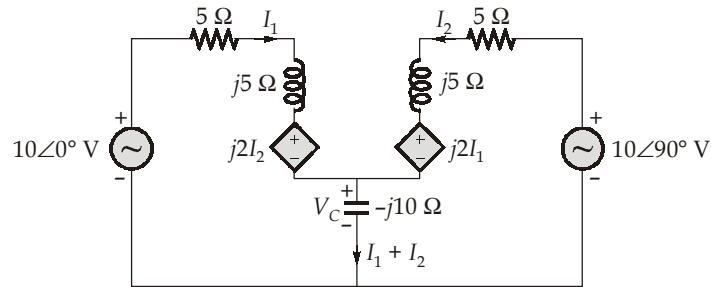

Applying KVL in loop-1,

$$\begin{aligned} 10\angle 0^\circ &= I_1(5 + j5 - j10) + I_2(j2 - j10) \\ &= (5 - j5)I_1 + (-j8)I_2 \end{aligned} \quad \dots(i)$$

Applying KVL in loop-2,

$$\begin{aligned} 10\angle 90^\circ &= I_2(5 + j5 - j10) + I_1(j2 - j10) \\ 10\angle 90^\circ &= I_2(5 - j5) + (-j8)I_1 \end{aligned} \quad \dots(ii)$$

Now adding equation (i) and (ii),


$$\begin{aligned} 10 + j10 &= I_1(5 - j13) + I_2(5 - j13) \\ I_1 + I_2 &= \frac{10 + j10}{5 - j13} \\ V_C &= -jX_C(I_1 + I_2) \\ &= -j10 \times \frac{10 + j10}{5 - j13} = 10.15\angle 24^\circ \text{ V} \end{aligned}$$

14. (c)
As we know that,

$$R_{th} = \frac{V_{OC}}{I_{SC}}$$

For V_{OC}

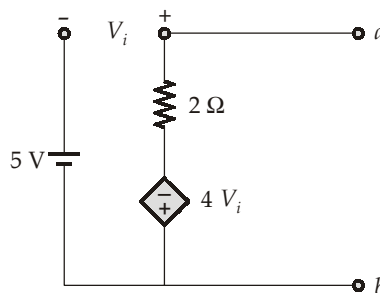From the circuit, there is open voltage at terminal ab




$$\begin{aligned} V_{OC} &= -4V_i \\ \text{Where, } V_i &= -4V_i - 5 \\ \therefore V_i &= -1 \\ \therefore V_{OC} &= -4 \times -1 = 4 \text{ V} \end{aligned}$$

For I_{SC}

Short circuit current is determined by shorting terminals a and b ,

Applying KVL,

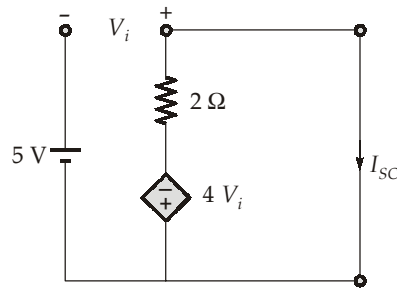


$$\begin{aligned}
 4V_i + 2 I_{SC} &= 0 \\
 2 I_{SC} &= -4 V_i \\
 I_{SC} &= -2 V_i \\
 5 + V_i - 4V_i + 4V_i &= 0 \\
 V_i &= -5 \text{ V} \\
 I_{SC} &= 10 \text{ A}
 \end{aligned}$$

$$\therefore R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{4}{10} = 0.4 \Omega$$

Alternative Solution:

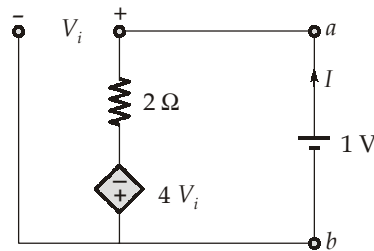Let, $V_{dc} = 1 \text{ V}$ applied across a - b terminals




Applying KVL:

$$\begin{aligned}
 -1 + V_i &= 0 \\
 \Rightarrow V_i &= 1 \\
 -1 + 2I - 4V_i &= 0 \\
 \Rightarrow -1 + 2I - 4 &= 0 \\
 \Rightarrow I &= \frac{5}{2} \text{ A}
 \end{aligned}$$

$$\text{Hence, } R_{th} = R_{ab} = \frac{1}{I} = \frac{2}{5} = 0.4 \Omega$$

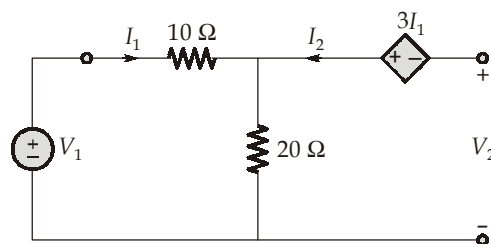15. (a)

To determine A and C , we leave the output port open as in figure. So that $I_2 = 0$ and place a voltage source V_1 at the input port.




$$\begin{aligned}
 V_1 &= (10 + 20)I_1 = 30I_1 \\
 V_2 &= 20I_1 - 3I_1 = 17I_1
 \end{aligned}$$

Thus,

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = 1.765$$

$$C = \frac{I_1}{V_2} = \frac{I_1}{17I_1} = 0.0588 \text{ S}$$

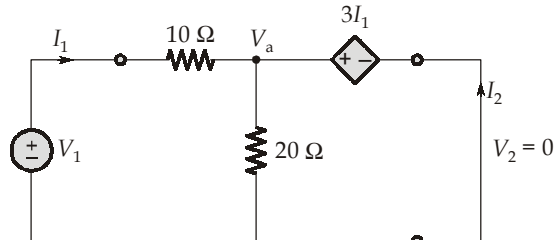To obtain B and D , we short circuit the output port so that,



But,

$$V_a = 3I_1$$

and

$$I_1 = \frac{(V_1 - V_a)}{10}$$

$$V_1 = 13I_1$$

Applying KCL at node a ,

$$I_1 - \frac{3I_1}{20} + I_2 = 0$$

$$\frac{17}{20}I_1 = -I_2$$

Therefore,


$$B = -\frac{V_1}{I_2} = \frac{-13I_1}{\left(-\frac{17}{20}\right)I_1} = 15.29 \Omega$$

$$D = \frac{20}{17} = 1.176$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1.765 & 15.29 \\ 0.0588 & 1.176 \end{bmatrix}$$

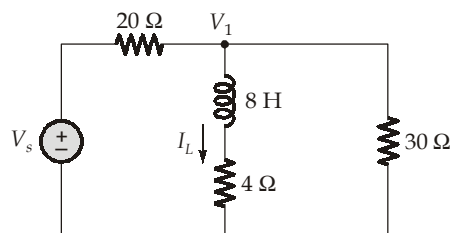16. (a)

$$V_s(s) = \frac{-5}{s} + \frac{12}{s} + 3 = \left(\frac{7}{s} + 3\right)$$



$$\frac{(V_1 - V_s)}{20} + \frac{V_1}{8s + 4} + \frac{V_1}{30} = 0$$

$$V_1 \left(\frac{1}{20} + \frac{1}{8s+4} + \frac{1}{30} \right) = \frac{1}{20} \left(\frac{7+3s}{s} \right)$$

$$V_1 \left(\frac{24s+12+60+16s+8}{60(8s+4)} \right) = \frac{1}{20s} (7+3s)$$

$$V_1 = \frac{7+3s}{20s} \times \frac{60(8s+4)}{(40s+80)}$$

$$= \frac{3(7+3s)(8s+4)}{s(40s+80)}$$

$$I_L = \frac{3(7+3s)(8s+4)}{s(40s+80)(8s+4)} = \frac{3}{s} \times \frac{(7+3s)}{40(s+2)}$$

$$I_L = \frac{3}{40} \left[\frac{7}{2s} + \frac{-1}{2(s+2)} \right]$$


$$i_L(t) = \frac{3}{40} \left(\frac{7}{2} - \frac{1e^{-2t}}{2} \right) u(t)$$

$$i_L(t) = \left(\frac{21}{80} - \frac{3}{80} e^{-2t} \right) u(t)$$

17. (c)

$$X_L = \omega L = 2$$

$$X_C = \frac{1}{1} = 1$$

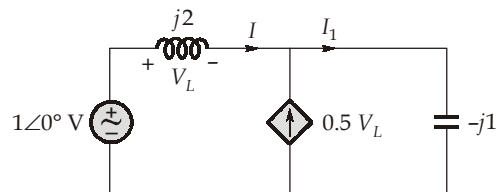

$$I = 0.5 V_L + I_1$$

$$= -0.5 \times (j2)I + I_1$$

$$I = -jI + I_1$$

$$I(1+j) = \frac{(1-j2I)}{-j1}$$

$$I(-j+1) = (1-j2I)$$


$$I(1+j) = 1$$

$$I = \left(\frac{1}{2} - \frac{j}{2} \right)$$

$$Y_{in} = I \times 1 = \left(\frac{1}{2} + \frac{1}{j2} \right) s$$



$$R = 2 \Omega, L = 2 \text{ H}$$

18. (a)
At $t < 0$,

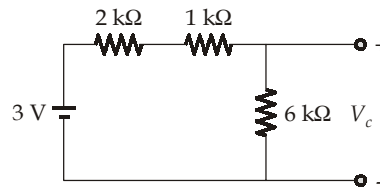

$$V_c(0^-) = 3 \times \frac{6}{(6+3)} = \frac{18}{9} = 2 \text{ V}$$

At $t > 0$,

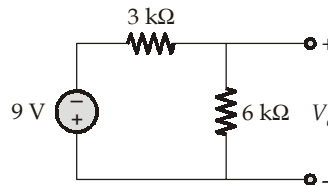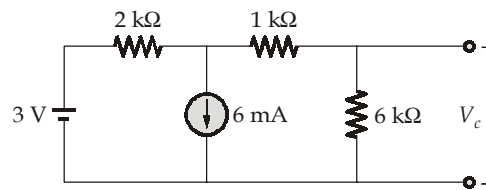

$$v_c(\infty) = \frac{6}{9} \times (-9) = -6 \text{ V}$$

$$v_c(t) = -6 + (2 + 6)e^{-t/\tau}$$

$$\tau = \frac{18}{9} \times 1 = 2 \mu\text{s}$$

$$V_c(t) = -6 + 8e^{-\frac{t}{2}}$$

$$V_c(2 \mu\text{s}) = -6 + 8e^{-1} = -3.06 \text{ V}$$


19. (a)

$$X_{L1} = j\omega L = j4 \times 5 = j20 \Omega$$

$$X_{L2} = j\omega L_2 = j4 \times 4 = j16 \Omega$$

$$X_C = \frac{1}{j\omega C} = \frac{16}{j4 \times 1} = -j4 \Omega$$
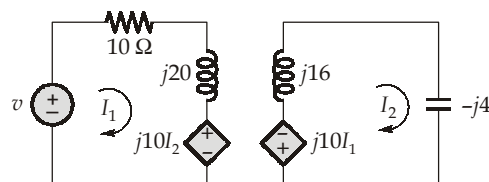
$$X_m = j\omega M = j \times 4 \times 2.5 = j10 \Omega$$



$$-60\angle 30^\circ + (10 + 20j)I_1 + j10I_2 = 0 \tag{i}$$

$$(j16 - j4)I_2 + j10I_1 = 0$$

$$I_1 = -1.2I_2 \tag{ii}$$

$$\begin{aligned}
 -(10 + j20) \times 1.2I_2 + j10I_2 &= 60\angle 30^\circ \\
 I_2 &= 3.25\angle 160.6^\circ \text{ A} \\
 I_2 &= 3.25 \cos(4t + 160.6^\circ) \\
 I_1 &= 3.9 \cos(4t - 19.4^\circ) \\
 \text{At } t = 1 \text{ sec,} \quad 4t &= 4 \text{ rad} = 229.18^\circ \\
 I_2 &= 2.82 \text{ A} \\
 I_1 &= -3.38 \text{ A}
 \end{aligned}$$


Total energy stored in the coupled inductor is

$$\begin{aligned}
 E &= \frac{1}{2}L_1I_1^2 + \frac{1}{2}L_2I_2^2 + MI_1I_2 \\
 E &= \frac{1}{2} \times 5 \times (-3.38)^2 + \frac{1}{2} \times 4 \times (2.82)^2 - 2.5 \times 3.38 \times 2.82 = 20.5 \text{ J}
 \end{aligned}$$

20. (d)

$$\begin{aligned}
 i(0) &= -1 \text{ A} \\
 V(0) &= 5 \text{ V}
 \end{aligned}$$

Apply node analysis

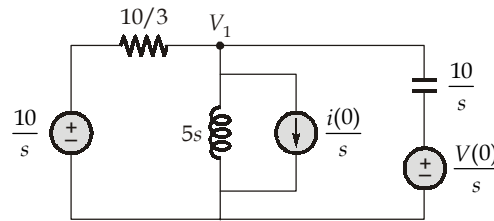

$$\frac{\left(V_1 - \frac{10}{s}\right)}{\frac{10}{3}} + \frac{V_1}{5s} - \frac{1}{s} + \frac{\left(V_1 - \frac{5}{s}\right)}{\left(\frac{10}{s}\right)} = 0$$

$$V_1 \left(\frac{3}{10} + \frac{1}{5s} + \frac{s}{10} \right) - \frac{10 \times 3}{s \times 10} - \frac{1}{s} - \frac{5}{s} \times \frac{s}{10} = 0$$

$$V_1 \left(\frac{3s + 2 + s^2}{10s} \right) = \left(\frac{3}{s} + \frac{1}{s} + \frac{0.5s}{s} \right)$$

$$V_1 = \frac{10s}{(s^2 + 3s + 2)} \times \frac{(0.5s + 4)}{s}$$

$$V_1 = \frac{(5s + 40)}{s^2 + 3s + 2} = \frac{5(s + 8)}{(s + 1)(s + 2)}$$

$$V_1 = 5 \left(\frac{7}{s + 1} - \frac{6}{s + 2} \right)$$

$$v_1(t) = (35e^{-t} - 30e^{-2t})u(t)$$

21. (c)

Let the instantaneous voltage across the capacitor at any time t is,

$$v = V_m \cos \omega_0 t$$

$$\therefore \text{Energy stored by the capacitor, } E_C = \frac{1}{2} C V_m^2 \cos^2 \omega_0 t \quad \dots(i)$$

Similarly, the instantaneous current through the inductor at any time t will be,

$$i = \frac{1}{L} \int_0^t v dt = \frac{V_m}{\omega_0 L} \sin \omega_0 t = I_m \sin \omega_0 t$$

Where,

$$I_m = \frac{V_m}{\omega_0 L} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$i = I_m \sin \omega_0 t$$

\therefore Energy stored by the inductor,

$$E_L = \frac{1}{2} L I_m^2 \sin^2 \omega_0 t = \frac{L}{2} \times \frac{V_m^2}{\frac{1}{LC} \times L^2} \sin^2 \omega_0 t = \frac{1}{2} C V_m^2 \sin^2 \omega_0 t$$

\therefore


$$\text{Total energy} = E = E_C + E_L$$

$$E = \frac{1}{2} C V_m^2 [\cos^2 \omega_0 t + \sin^2 \omega_0 t]$$

$$= \frac{1}{2} C V_m^2$$

22. (c)

Redrawing the given circuit, we get,

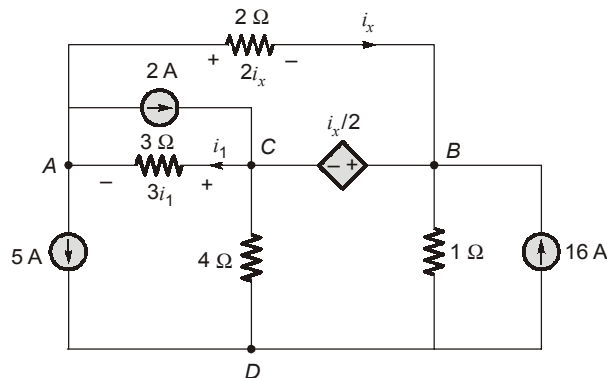

By KCL at node A, we get,

$$i_1 = 2 + 5 + i_x = 7 + i_x$$

By KVL in ABCA, we get,

$$2i_x + \frac{i_x}{2} + 3i_1 = 0$$

$$\frac{5i_x}{2} + 3(7 + i_x) = 0$$

$$\frac{5i_x}{2} + 21 + 3i_x = 0$$

$$\frac{11i_x}{2} = -21$$


$$i_x = -\frac{42}{11} = -3.818 \text{ A}$$

23. (b)

The equation for the input can be written as

$$V_{ab} = i R_{th} + V_{oc}$$

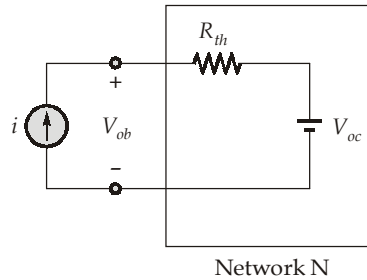Assume the equivalent network to be replaced by a Thevenin's equivalent.



Substituting the given values we get

$$6 = 10^{-3} R_{th} + V_{oc} \quad \dots(i)$$

and


$$10 = 2 \times 10^{-3} R_{th} + V_{oc} \quad \dots(ii)$$

solving the two equations we get


$$V_{oc} = 2 \text{ V}$$

$$R_{th} = 4 \text{ k}\Omega$$

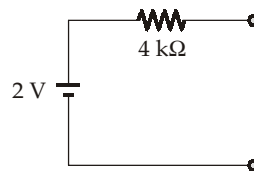
thus, the equivalent circuit can be drawn as



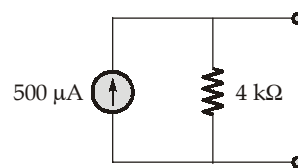The equivalent Norton circuit can be drawn as



24. (c)

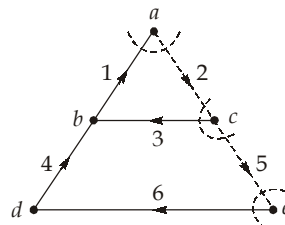

$C_1(1, 2)$: This separates the node-a and direction of both branch is opposite to each other.

$C_2(2, 3, 5)$: This separates node-C and direction of branch - 2 is opposite to branch - 3 and branch - 5.

25. (a)

$$[Z_a] = \begin{bmatrix} 25 & 20 \\ 5 & 10 \end{bmatrix}$$

$$\therefore \Delta Z_a = 250 - 100 = 150$$

$$[Z_b] = \begin{bmatrix} 50 & 25 \\ 25 & 30 \end{bmatrix}$$

$$\Delta Z_b = 1500 - 625 = 875$$

$$[g] = \begin{bmatrix} \frac{1}{Z_{11}} & \frac{-Z_{12}}{Z_{11}} \\ \frac{Z_{21}}{Z_{11}} & \frac{\Delta Z}{Z_{11}} \end{bmatrix}$$

$$[g_a] = \begin{bmatrix} 0.04 & -0.8 \\ 0.2 & 6 \end{bmatrix}$$

$$[g_b] = \begin{bmatrix} 0.02 & -0.5 \\ 0.5 & 17.5 \end{bmatrix}$$

$$\therefore [g] = [g_a] + [g_b]$$

$$= \begin{bmatrix} 60 \text{ mS} & -1.3 \\ 0.7 & 23.5 \Omega \end{bmatrix}$$

26. (c)

From Z-parameter model, we have

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_1 = Z_{21} I_1 + Z_{22} I_2$$

where,

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \dots(i)$$

Similarly from Y-parameter model, we have

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \dots(ii)$$

Considering the above two conditions for transmission parameter model, we get,

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

By keeping $I_2 = 0$,

$$A = \frac{V_1}{V_2} \quad \text{and} \quad C = \frac{I_1}{V_2}$$

or,

$$\frac{V_1}{I_1} = \frac{A}{C} = Z_{11} \quad \dots(iii)$$

and by keeping $V_2 = 0$,

$$B = -\frac{V_1}{I_2} \quad \text{and} \quad D = -\frac{I_1}{I_2}$$

or
$$\frac{I_1}{V_1} = \frac{D}{B} = Y_{11} \quad \dots(\text{iv})$$


$\therefore Z_{11} = \frac{1}{Y_{11}}$ (Given in the question)

From equations (iii) and (iv), we get,

$$\frac{A}{C} = \frac{B}{D}$$

or $AD - BC = 0$

27. (b)

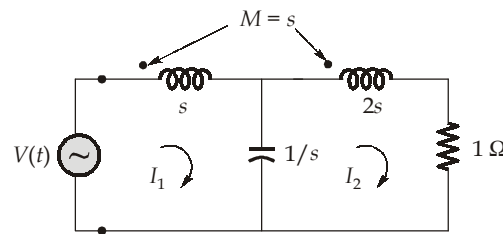

Applying laplace transform and KVL in loop 1.

$$V(s) = sI_1(s) + sI_2(s) + \frac{I_1(s) - I_2(s)}{s} \quad \dots(\text{i})$$

Applying KVL in loop 2.

$$0 = sI_1(s) + (2s + 1)I_2(s) + \frac{I_2(s) - I_1(s)}{s} \quad \dots(\text{ii})$$

$$\therefore \frac{I_1(s)}{s} - sI_1(s) = \left(2s + 1 + \frac{1}{s}\right)I_2(s)$$

$$\left(\frac{1}{s} - s\right)I_1(s) = \left(2s + 1 + \frac{1}{s}\right)I_2(s)$$

substituting the value of I_2 in eqn. (i) we get

$$Y_1(s) = \frac{I_1(s)}{V(s)} = \frac{2s^2 + s + 1}{s^3 + s^2 + 5s + 1}$$

substituting $\omega = 1$ rad we get

$$Y_1(j\omega) = \frac{1 + j}{4} = \frac{\sqrt{2} \angle 45^\circ}{4}$$

$$I_1(j\omega) = Y_1(j\omega) V_1(j\omega)$$


$\therefore i(t) = \cos(\omega t + 45^\circ) \text{ A}$

28. (c)

$$i_L(0^-) = i_L(0^+) = 0 \text{ A}$$

$$v_c(0^-) = v_c(0^+) = 100 \text{ V}$$

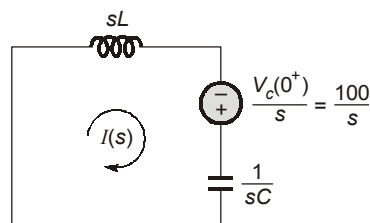The circuit can be redrawn in s-domain as,



or

$$I(s) = \frac{\left(\frac{100}{s}\right)}{\left(sL + \frac{1}{sC}\right)} = \frac{100}{L} \left(\frac{1}{s^2 + \frac{1}{LC}} \right)$$

$$= 100 \sqrt{\frac{C}{L}} \left(\frac{\frac{1}{\sqrt{LC}}}{s^2 + \left(\frac{1}{\sqrt{LC}}\right)^2} \right)$$

Taking inverse Laplace transform of the above equation, we get,

$$i(t) = 100 \sqrt{\frac{C}{L}} \sin \frac{1}{\sqrt{LC}} t$$

Now by putting the values of L and C , we get,

$$i(t) = 100 \sqrt{\frac{10 \times 10^{-6}}{1 \times 10^{-3}}} \sin \frac{t}{\sqrt{10 \times 1 \times 10^{-9}}} = (10 \sin 10^4 t) \text{ A}$$

29. (b)

From transmission parameter model,

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$\therefore C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

From h -parameter model,

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

By keeping $I_2 = 0$,

$$\frac{I_1}{V_2} = \frac{-h_{22}}{h_{21}} = C$$

From Z-parameter model,

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

By keeping $I_2 = 0$,

$$\frac{I_1}{V_2} = \frac{1}{Z_{21}} = C$$

From Y-parameter model,

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

By keeping $I_2 = 0$,

$$V_1 = \frac{-Y_{22}}{Y_{21}} V_2$$

and

$$I_1 = \left[\frac{-Y_{22} Y_{11}}{Y_{21}} + Y_{12} \right] V_2$$


or

$$\frac{I_1}{V_2} = \left(Y_{12} - \frac{Y_{11} Y_{22}}{Y_{21}} \right) = C$$

Thus, only option (b) satisfies the condition.

30. (c)

By redrawing the circuit, we get,

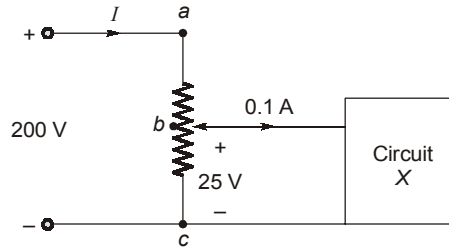

Let us assume the tap position at 'b'

$$\therefore R_{ac} = 500 \Omega \quad (\text{given})$$

$$\text{Let, } R_{bc} = x \Omega$$

$$\therefore R_{ab} = (500 - x)\Omega$$

$$\text{Also, } V_{ab} = 200 - 25 = 175 \text{ V}$$

$$\text{The circuit current, } I = \frac{25}{x} + 0.1$$

$$\text{We can also write, } V_{ab} = I \times (500 - x) = \left(\frac{25}{x} + 0.1 \right) (500 - x)$$

$$\text{or } 0.1x^2 + 150x - 12500 = 0$$

By solving, we get,

$$x = 79.16 \Omega \quad \text{and} \quad -1579.16 \Omega$$

By considering $x = 79.16 \Omega$,

$$I = \frac{25}{x} + 0.1 \text{ A} = 0.416 \text{ A}$$

$$\text{Total power supplied} = 200 \text{ V} \times I = 200 \text{ V} \times 0.416 \text{ A} = 83.2 \text{ W}$$

