

**MADE EASY**

India's Best Institute for IES, GATE &amp; PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Lucknow | Pune | Bhubaneswar | Kolkata | Patna

Web: [www.madeeasy.in](http://www.madeeasy.in) | E-mail: [info@madeeasy.in](mailto:info@madeeasy.in) | Ph: 011-45124612

# ELECTRICAL & ELECTRONICS MEASUREMENTS

**EC+EE****Date of Test: 06/08/2022****ANSWER KEY ➤**

- |        |         |         |         |         |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (b)  | 13. (c) | 19. (c) | 25. (d) |
| 2. (d) | 8. (c)  | 14. (b) | 20. (b) | 26. (b) |
| 3. (a) | 9. (c)  | 15. (a) | 21. (b) | 27. (c) |
| 4. (b) | 10. (a) | 16. (b) | 22. (b) | 28. (d) |
| 5. (c) | 11. (c) | 17. (b) | 23. (d) | 29. (c) |
| 6. (b) | 12. (a) | 18. (a) | 24. (d) | 30. (b) |

**1. (b)**

Given, meter constant = 450 rev per kWhr

Load current = 12 A at 0.8 p.f. lag

Voltage rating = 230 V

Total power consumed by load,

$$230 \times 12 \times 0.8 = 2208 \text{ W or } 2.208 \text{ kW}$$

In one hour no. of revolution =  $2.208 \times 450 = 993.60$  rev per hour


$$\text{No. of revolutions in a minute} = \frac{993.60}{60} = 16.56 \text{ rpm}$$

**2. (d)**

We know,

$$\frac{f_y}{f_x} = \frac{\text{No. of Horizontal tangencies}}{\text{No. of Vertical tangencies}}$$

$$\frac{4200}{700} = \frac{6}{1}$$

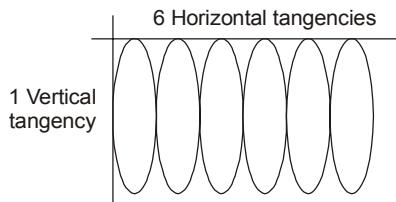

Hence option (d) is correct.

**3. (a)**

As the ammeters are connected in parallel, so voltage is same

$$R_A = \frac{V}{I_{fsd-A}} = \frac{V}{15 \text{ mA}}$$

$$R_B = \frac{V}{I_{fsd-B}} = \frac{V}{50 \text{ mA}}$$

$$\frac{R_A}{R_B} = \frac{50 \text{ mA}}{15 \text{ mA}} = \frac{10}{3} = 10 : 3$$

**4. (b)**

Value of resistor,  $R_1 = 2 \times 10^4 \pm 7\%$

i.e.

$$R_1 = 20000 \pm \frac{7}{100} \times 20000$$

$$= (20000 \pm 1400) \Omega$$

Value of resistor,  $R_2 = 6 \times 10^3 \pm 4\%$

$$= 6000 \pm \frac{6000 \times 4}{100} = (6000 \pm 240) \Omega$$

Series network =  $(26000 \pm 1640) \Omega$

$$\text{The tolerance limit} = \frac{1640}{26000} \times 100 = 6.307 \approx 6.31\%$$

## 5. (c)

Limiting error can be calculated using

$$P = I^2 R$$

Taking log on both sides

$$\ln P = 2 \ln I + \ln R$$

$$\frac{\partial R}{R} = \frac{\partial P}{P} - \frac{2\partial I}{I}$$

$$\begin{aligned}\text{So limiting error, } \frac{\partial R}{R} &= \pm \left( \frac{\partial P}{P} + \frac{2\partial I}{I} \right) \\ &= \pm 0.02 \pm 2(0.03) \\ &= \pm 0.02 \pm 0.06 = 0.08 \text{ or } 8\%\end{aligned}$$

## 6. (b)

We know,

$$\theta = \frac{GI}{K} = \frac{NBAI}{K}$$

For

	$K$	$B$
1°C rise	0.05% decrease	0.03% decrease
10°C rise	0.5% decrease	0.3% decrease

So change in  $K$ .

$$K' = K - 0.5\% \text{ of } K$$

$$= K - \frac{0.5}{100} K = K - \frac{5}{1000} K$$

$$K' = \frac{995}{1000} K$$

$$B' = B - 0.3\% \text{ of } B = \frac{997}{1000} B$$

$$\theta' = \frac{NB'A}{K'} I = \frac{(0.997)}{(0.995)} \frac{NBA}{K} I$$

$$\theta' = 1.002 \theta$$

$$\therefore \text{Change in reading} = \frac{\theta' - \theta}{\theta} \times 100$$

$$= \frac{0.002\theta}{\theta} \times 100 = 0.2 \% \text{ increase}$$

## 7. (b)

The multiplication factor,

$$m = \frac{I}{I_m} = \frac{200 \text{ mA}}{100 \mu\text{A}} = 2000$$

∴ The shunt resistance required,

$$R_s = \frac{R_m}{m-1} = \frac{500}{2000-1} = \frac{500}{1999} = 0.250 \Omega$$

## 8. (c)

We know

$$R_s = S_{dc} \times \text{Range}_{dc} - R_m$$

and

$$\begin{aligned} S_{dc} &= \frac{1}{I_{fs}} = \frac{1}{1 \text{ mA}} = \frac{1 \text{ k}\Omega}{V} \\ R_s &= \frac{1 \text{ k}\Omega}{V} \times \frac{0.45E_{rms}}{1} - R_m \\ &= \frac{1 \text{ k}\Omega}{V} \times \frac{0.45 \times 20 \text{ V}}{1} - 300 \\ &= 9000 - 300 = 8700 \Omega = 8.7 \text{ k}\Omega \end{aligned}$$

9. (c)

We know

$$f \propto \frac{1}{\sqrt{C}}$$

$$\text{So, } \frac{f_1}{f_2} = \sqrt{\frac{C_2 + C_d}{C_1 + C_d}}$$

where  $C_d$  is self capacitance of the coil.

$$\frac{3}{1} = \frac{\sqrt{C_d + 360}}{\sqrt{C_d + 12}}$$

Squaring both sides, we get,

$$\begin{aligned} 9 &= \frac{C_d + 360}{C_d + 12} \\ 108 + 9C_d &= C_d + 360 \\ 8C_d &= 252 \\ \Rightarrow C_d &= \frac{252}{8} = 31.5 \text{ pF} \end{aligned}$$

10. (a)

At 50 Hz supply, impedance of the instrument circuits,

$$\begin{aligned} Z &= \frac{V_{ac}}{I_{ac}} = \frac{500}{0.1} = 5000 \Omega \\ R &= \sqrt{Z^2 - X_L^2} = \sqrt{(5000)^2 - (2\pi \times 50 \times 0.8)^2} = 4993.7 \Omega \end{aligned}$$

When connected to 300 V dc,

$$\text{Instrument current, } I_{dc} = \frac{V_{dc}}{R} = \frac{300}{4993.7} = 0.06008 \text{ A}$$

Reading of instrument when connected to 300 V dc,

$$= \frac{V_{dc}}{I_{ac}} \times I_{dc} = \frac{500}{0.1} \times 0.06008 = 300.4 \text{ V}$$

11. (c)

Given,

Secondary winding impedance,

$$\begin{aligned} &= (0.583 + j 0.25) \Omega \\ &= 0.6343 \angle 23.21^\circ \Omega \end{aligned}$$

Secondary load angle,  $\delta = 23.21^\circ$ 

Magnetizing current at primary,

$$I_\mu = 10.6 \text{ A}$$

Core loss component current,

$$I_c = 5.28 \text{ A}$$

$$\text{Turn ratio, } n = \frac{400}{4} = 100$$

$$\beta = \frac{180}{\pi} \times \frac{I_\mu \cos \delta - I_c \sin \delta}{n I_2}$$

$$= \frac{180}{\pi} \times \frac{(10.6 \cos 23.21^\circ - 5.28 \sin 23.21^\circ)}{100 \times 5} = 0.878^\circ \approx 0.88^\circ$$

12. (a)

At balance condition,  $Z_1 Z_4 = Z_2 Z_3$ 

$$\begin{aligned} \left( \frac{R_1}{1 + j\omega C_1 R_1} \right) R_4 &= \left( R_2 - \frac{j}{\omega C_2} \right) R_3 \\ \frac{R_4}{R_3} &= \frac{R_2}{R_1} + \frac{C_1}{C_2} + j \left( \omega C_1 R_2 - \frac{1}{\omega C_2 R_1} \right) \end{aligned}$$

Equating the real and imaginary parts

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} + \frac{C_1}{C_2}$$

$$\text{and } \omega C_1 R_2 - \frac{1}{\omega C_2 R_1} = 0$$

$$\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

As given in question,  $R_2 = R_1$ and  $C_2 = C_1$ 

$$\omega = \frac{1}{RC}$$

$$\text{and } f = \frac{1}{2\pi RC}$$

Hence option (a) is correct.

13. (c)

Given, input signal  $x(t) = 10 \sin(20t)$ 

$$x_1(t) = \frac{d}{dt} x(t) = \frac{d}{dt}(10 \sin 20t) = 200 \cos 20t$$

$$x_2(t) = \frac{200 \cos 20t}{20} = 10 \cos 20t$$

$x_1(t)$  and  $x_2(t)$  are same signal but  $90^\circ$  displaced in time domain.

$$x_2(t) = 10 \sin(20t + 90^\circ)$$

Hence, in XY mode CRO shows circle as output.

Hence option (c) is correct.

**14. (b)**

$$\text{We know, Deflection, } D = \frac{Ll_d E_d}{2d E_a}$$

Voltage required at deflecting plates,

$$\begin{aligned} E_d &= \frac{2d E_a D}{Ll_d} = \frac{2 \times d \times E_a \times D}{Ll_d} \\ &= \frac{2 \times 5 \times 10^{-3} \times 4 \times 10^{-2} \times 1500}{50 \times 10^{-2} \times 1.5 \times 10^{-2}} \\ E_d &= \frac{60000 \times 10^{-5}}{75 \times 10^{-4}} = 80 \text{ V} \end{aligned}$$

Input voltage to amplifier = 2 V

We know input voltage required for a deflection of 4 cm

$$= \frac{E_d}{\text{Amplifier gain}}$$

$$\text{So, } \text{amplifier gain} = \frac{E_d}{2} = \frac{80}{2} = 40$$

**15. (a)**

Given,

Output of SAR type ADC = 01110110

$$\begin{aligned} \text{Decimal equivalent of output} &= 2^6 \times 1 + 2^5 \times 1 + 2^4 \times 1 + 2^2 \times 1 + 2^1 \times 1 \\ &= 64 + 32 + 16 + 4 + 2 \\ &= 118 \end{aligned}$$

Input to ADC is analog voltage with amplitude,  $A = 3.24 \text{ V}$

$$\begin{aligned} \text{The resolution can be} &= \frac{\text{Amplitude of analog signal}}{\text{Number of divisions}} \\ &= \frac{3.24}{118} = 0.02745 \\ &= 27.458 \text{ mV} \approx 27.46 \text{ mV} \end{aligned}$$

**16. (b)**

We know for triangular wave form

$$\text{Average value} = \frac{V_m}{2}$$

$$\text{RMS value} = \frac{V_m}{\sqrt{3}}$$

$$\text{Comparing rms value } \frac{V_m}{\sqrt{3}} = \frac{40}{\sqrt{3}}$$

$$V_m = 40 \text{ V}$$

$$\text{Average value of triangular input} = \frac{40}{2} = 20 \text{ V}$$

17. (b)

For the meter,

Full scale deflection current = 2 mA

Internal resistance = 500 Ω

The voltage drop across voltmeter at full scale current  
= 2 mA × 500 = 1 VThe full scale deflection on required voltmeter  
= 200 VMaximum possible voltage around meter  
= 1 V

Extra potential drop = 200 - 1 V = 199 V

Comparing voltage drop and resistances

$$\frac{199}{1} = \frac{x}{500}$$

$$x = 500 \times 199 = 99.5 \text{ k}\Omega$$

**Alternatively:**

$$V_m = 2 \times 10^{-3} \times 500 = 1 \text{ V}$$

$$m = \frac{V}{V_m} = \frac{200}{1} = 200$$

$$R_{se} = (m - 1) R_m$$

$$= (200 - 1) \times 500 = 99500 = 99.5 \text{ k}\Omega$$

18. (a)

Total power in the load circuit,

$$P = W_1 + W_2$$

$$= 6000 - 1000 = 5000 \text{ W}$$

$$\phi = \tan^{-1} \left[ \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right]$$

$$= \tan^{-1} \left[ \frac{\sqrt{3}[(6000 - (-1000))]}{6000 - 1000} \right]$$

$$= \tan^{-1} \left[ \frac{\sqrt{3}(7000)}{5000} \right] = 67.58^\circ$$

$$\cos \phi = 0.381$$

Load current per phase,

$$I_P = \frac{5000}{\sqrt{3} \times 440 \times 0.381}$$

$$I_P = 17.22 \text{ A}$$

Load impedance per phase,

$$Z_p = \frac{V_p}{I_p} = \frac{440}{\left(\frac{17.22}{\sqrt{3}}\right)} = 44.25 \Omega$$

Load resistance per phase,

$$\begin{aligned} R_p &= Z_p \cos \phi = 44.25 \cos (67.58) \\ &= 44.25 \times 0.381 \\ R_p &= 16.87 \Omega \end{aligned}$$

Load reactance per phase,

$$\begin{aligned} X_p &= Z_p \sin \phi = 44.25 \sin (67.58) \\ X_p &= 40.9 \Omega \end{aligned}$$

Reading of wattmeter *B* will be zero when power factor,

$$\begin{aligned} \cos \phi' &= 0.5 \\ \phi' &= 60^\circ \end{aligned}$$

Since there is no change in resistance, reactance in circuit per phase,

$$\begin{aligned} X_p' &= R_p \tan \phi' \\ X_p' &= 16.87 \times \tan 60^\circ = 29.22 \Omega \end{aligned}$$

Values of capacitive reactance introduced in each phase,

$$\begin{aligned} X_C &= X_p - X_p' \\ &= 40.9 - 29.22 = 11.68 \Omega \end{aligned}$$

$$\begin{aligned} \therefore C &= \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 11.68} \\ C &= 272.52 \mu F \end{aligned}$$

### 19. (c)

We know, figure of merit = sensitivity

$$\text{Sensitivity} = \frac{1}{I_{fsd}}$$


Full scale deflection current for meter 1

$$= \frac{1}{20 \text{ k}\Omega} V = 0.05 \text{ mA} = 50 \mu A$$

Full scale deflection current for meter 2

$$= \frac{1}{40 \text{ k}\Omega} V = 0.025 \text{ mA} = 25 \mu A$$

For series combination

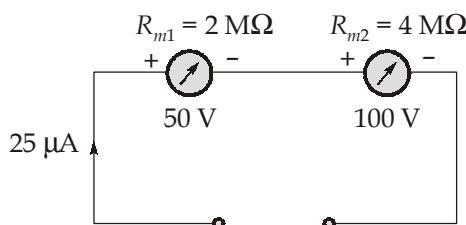

Maximum allowable current = 25  $\mu A$

So maximum voltage measured from series combination

$$= 50 + 100 = 150 \text{ V}$$

20. (b)

We know ,

$$\omega = 2\pi f = 2\pi \times 1000 \text{ Hz} = 6283.19 \text{ Hz}$$

$$X_{L2} = \omega L_2 = 6283.19 \times 15.92 \times 10^{-3} = 100 \Omega$$

$$X_{C3} = \frac{1}{\omega C_3} = \frac{1}{6283.19 \times 0.4 \times 10^{-6}} = 400 \Omega$$

The impedance of the bridge arm

$$\begin{aligned} Z_1 &= R_1 = 400 \angle 0^\circ \Omega \\ Z_2 &= R_2 + jX_{L2} = 200 + j100 \\ &= 223.6 \angle 26.6^\circ \Omega \\ Z_3 &= R_3 - jX_{C3} \\ &= 300 - j400 = 500 \angle -53.13^\circ \Omega \\ \therefore Z_x &= \frac{Z_2 Z_3}{Z_1} = \frac{(223.6 \angle 26.6^\circ)(500 \angle -53.13^\circ)}{400 \angle 0^\circ} \\ &= 279.5 \angle -26.53^\circ \\ &= (250.07 - j124.84) \Omega \end{aligned}$$

$$\text{we know } C = \frac{1}{\omega X_C} = \frac{1}{6283.19 \times 124.84} \approx 1.28 \mu\text{F}$$

$\therefore$  Z impedance is series combination of  $250.35 \Omega$  resistance and  $1.28 \mu\text{F}$  capacitance.

21. (b)

Let the reading of first wattmeter be  $P_1$  and second wattmeter be  $P_2$ 

$$P_1 = 3P_2$$

$$\text{Using expression, } \tan\phi = \frac{\sqrt{3}(P_1 - P_2)}{P_1 + P_2}$$

$$\tan\phi = \frac{\sqrt{3}(3P_2 - P_2)}{3P_2 + P_2}$$

$$\tan\phi = \sqrt{3} \frac{2P_2}{4P_2} = \frac{\sqrt{3}}{2}$$

$$\phi = \tan^{-1} \frac{\sqrt{3}}{2} = 40.893^\circ$$

As

$$180^\circ - \pi \text{ radians}$$

$$\text{So, } 40.893^\circ - \frac{\pi}{180^\circ} \times 40.893^\circ$$

So load impedance angle =  $0.227 \pi$ 

22. (b)

PMMC always reads average value,

$$V_0 = \frac{1}{T} \int_0^T v dt$$

$$\begin{aligned}
 &= \frac{1}{25} \left[ (10 \times 5) + (-5 \times 5) + \left( \frac{1}{2} \times 10 \times 10 \right) \right] \\
 &= \frac{1}{25} [50 - 25 + 50] = 3 \text{ V}
 \end{aligned}$$

23. (d)

Given, temperature range  $(50^\circ - (-20^\circ)) = 70^\circ\text{C}$

Resolution =  $0.2^\circ\text{C}$

$$\text{Resolution relative to range} = \frac{0.2}{70} = 0.00286$$

For  $N$  bit ADC

$$\text{Resolution} = \frac{1}{2^N - 1} = 0.00286$$

$$2^N = 350$$

$$N \simeq 9$$

24. (d)

For limiting error in  $V_0$

$$\text{Let } x = \frac{C_2}{C_1}$$

$$\Rightarrow x = \frac{9}{1} = 9$$

$$\ln x = \ln C_2 - \ln C_1$$

$$\frac{dx}{x} = \frac{dC_2}{C_2} - \frac{dC_1}{C_1}$$

Limiting error in  $x$

$$\begin{aligned}
 \frac{\Delta x}{x} &= \pm \left( \frac{\Delta C_2}{C_2} + \frac{\Delta C_1}{C_1} \right) \\
 &= \pm 0.05 \pm 0.05 = \pm 0.1 = \pm 10\%
 \end{aligned}$$

So,  $x = 9 \pm 10\%$

$$\Delta x = \pm 10\% \text{ of } x = 10\% \text{ of } 9 = \pm 0.9$$

$$V_0 = \frac{V_i}{1+x}$$

$$\frac{dV_0}{dx} = \frac{-V_i}{(1+x)^2}$$

$$dV_0 = -V_i \frac{dx}{(1+x)^2}$$

Limiting error in  $V_0$

$$\Delta V_0 = -V_i \frac{\Delta x}{(1+x)^2} = \frac{-200 \times (0.9)}{(1+9)^2}$$

$$= \pm 1.8 = \pm 1.8 \text{ kV}$$

Nominal value,  $V_0 = \frac{V_i}{1+x} = \frac{200}{1+9} = 20 \text{ kV}$

So,  $V_0 = 20 \text{ kV} \pm 1.8 \text{ kV}$   
 $\therefore V_{0 \text{ max}} = 21.8 \text{ kV}$

25. (d)

At balance condition for schering bridge

$$\begin{aligned} R_x &= \frac{R_3 C_4}{C_2} = \frac{(100 \times 10^3)(0.01 \times 10^{-6})}{(0.1 \times 10^{-6})} = 10 \text{ k}\Omega \\ C_x &= \frac{C_2 R_4}{R_3} = \frac{(0.1 \times 10^{-6})(470 \times 10^3)}{100 \times 10^3} \\ &= 0.47 \times 10^{-6} \text{ F} = 0.47 \mu\text{F} \end{aligned}$$

26. (b)

$$\begin{aligned} \text{Percentage error} &= \frac{I^2 R_C}{VI \cos \phi} \\ &= \frac{(12)^2 \times 0.1}{250 \times 12 \times 1} \times 100 \\ &= \frac{14.4}{3000} \times 100 = 0.48\% \end{aligned}$$

27. (c)

$$L = (10 + 50 - 20^2) \mu\text{H}$$

$$\frac{dL}{d\theta} = (5 - 4\theta) \mu\text{H}/\text{radian}$$

and also,  $\frac{dL}{d\theta} = \frac{2k\theta}{I^2}$

$$\therefore (5 - 4\theta) \times 10^{-6} = \frac{2k\theta}{I^2} \quad \dots(i)$$

Substituting,  $\theta = \frac{\pi}{4}$  and  $I = 5 \text{ A}$  in above expression, we get

$$\left[ 5 - 4\left(\frac{\pi}{4}\right) \right] \times 10^{-6} = \frac{2k \times \frac{\pi}{4}}{(5)^2}$$

$$[5 - \pi] \times 10^{-6} = \frac{\pi}{2 \times 25} k$$

$$\frac{50}{\pi} [5 - \pi] \times 10^{-6} = k$$

$$k = 2.95 \times 10^{-5} \text{ Nm/radian}$$

Substituting,  $I = 10 \text{ A}$  and  $k = 2.95 \times 10^{-5}$  in equation (i), we get

$$(5 - 4\theta) \times 10^{-6} = \frac{2 \times 2.95 \times 10^{-5} \times \theta}{10^2}$$

$$\begin{aligned}
 (5 - 4\theta) \times 10^{-6} &= 5.9 \times 10^{-7} \theta \\
 5 - 4\theta &= 0.59 \theta \\
 5 &= 4.59 \theta \\
 \theta &= \frac{5}{4.59} = 1.089 \text{ radian (or)} 62.41^\circ
 \end{aligned}$$

28. (d)

$$\begin{aligned}
 C_x &= \frac{R_4}{R_3} C_2 \\
 &= \frac{318}{130} \times 106 \times 10^{-12} = 259.29 \text{ pF} \\
 R_x &= R_3 \times \frac{C_4}{C_2} \\
 &= 130 \times \frac{0.35 \times 10^{-6}}{106 \times 10^{-12}} = 429.25 \text{ k}\Omega
 \end{aligned}$$

29. (c)

$$\begin{aligned}
 \frac{f_y}{f_x} &= \frac{2\frac{1}{2}}{1} \\
 f_y &= 2.5 \times f_x \\
 \therefore \text{frequency of vertical voltage signal} \\
 &= 2.5 \times 3 \\
 &= 7.5 \text{ kHz}
 \end{aligned}$$

30. (b)

$$\begin{aligned}
 R_1 &= R_2(k - 1) \\
 &= 1 \text{ M}\Omega (10 - 1) \\
 &= 9 \text{ M}\Omega \\
 C_1 &= \frac{C_2}{k - 1} = \frac{30 \text{ pF}}{10 - 1} = 3.33 \text{ pF}
 \end{aligned}$$

