



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Lucknow | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

POWER SYSTEMS-2

ELECTRICAL ENGINEERING

Date of Test : 09/08/2022


ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (b) | 13. (c) | 19. (a) | 25. (d) |
| 2. (b) | 8. (b) | 14. (b) | 20. (b) | 26. (b) |
| 3. (b) | 9. (a) | 15. (b) | 21. (d) | 27. (a) |
| 4. (a) | 10. (d) | 16. (b) | 22. (b) | 28. (c) |
| 5. (c) | 11. (b) | 17. (a) | 23. (b) | 29. (d) |
| 6. (d) | 12. (c) | 18. (a) | 24. (b) | 30. (a) |

DETAILED EXPLANATIONS

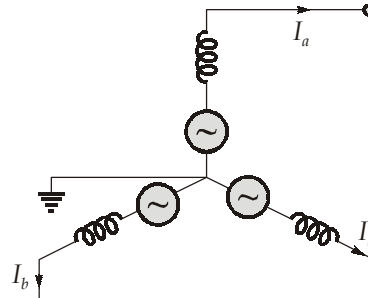1. (b)

Line-to-line fault occurs on *b* and *c* phases of generator,




$$I_f = I_b = -I_c$$

$$I_a = 0$$

and

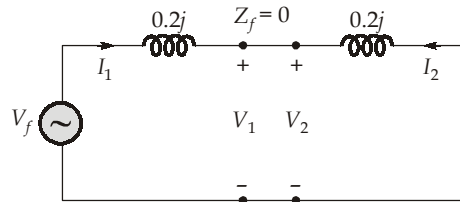The sequence network for line to line fault is



$$I_1 = \frac{V_f}{z_1 + z_2}$$

⇒

$$I_f = I_b = (\alpha^2 - \alpha)I_1 = -j\sqrt{3}I_1 = \frac{-j\sqrt{3}V_f}{z_1 + z_2}$$

and

$$I_{f \text{ p.u.}} = \frac{-j\sqrt{3} \times 1}{j0.2 + j0.2}$$

$$|I_{f \text{ p.u.}}| = \frac{\sqrt{3}}{0.4} = 4.33 \text{ p.u.}$$

$$\text{Base current} = \frac{25 \times 10^3}{\sqrt{3} \times 11} = 1312.16 \text{ A}$$

$$\text{Fault current, } I_f = 4.33 \times 1312.16 = 5.68 \text{ kA}$$

2. (b)

For the fully transposed transmission line,

$$\text{Positive sequence impedance } Z_1 = Z_s - Z_m$$

$$\text{Negative sequence impedance } Z_2 = Z_s - Z_m$$

$$\text{Zero sequence impedance, } Z_0 = Z_s + 2Z_m + 3Z_n$$

Where,

$$Z_s = \text{Self impedance/ph}$$

$$Z_m = \text{Mutual impedance/ph}$$


If the system voltages are unbalanced, we have a neutral current, I_n flowing through the neutral (ground) having impedance Z_n .

From above equations, we can say

1. Positive and negative sequence impedance are equal.
 2. Zero sequence impedance is much larger than the positive or negative sequence impedance.
- ∴ Statement (I) is true and statement (II) is false.

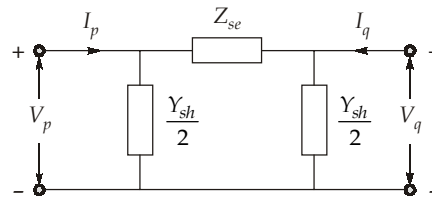3. (b)


Y-bus matrix for the π equivalent circuit.



$$Y_{\text{bus}} = \begin{bmatrix} \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} & -\frac{1}{Z_{se}} \\ -\frac{1}{Z_{se}} & \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} \end{bmatrix}$$

Here, $Z_{se} = jX; Y_{sh} = 0$

The above circuit diagram becomes,

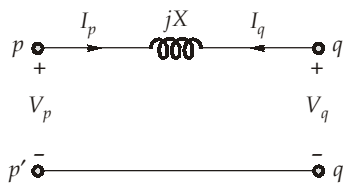

∴

$$Y_{\text{bus}} = \begin{bmatrix} \frac{1}{jX} & \frac{-1}{jX} \\ \frac{-1}{jX} & \frac{1}{jX} \end{bmatrix}$$

4. (a)

Total Kinetic energy of the two machines,

$$\begin{aligned} &= G_1 H_1 + G_2 H_2 \\ &= 400 \times 4 + 1600 \times 2 \\ &= 4800 \text{ MJ} \end{aligned}$$

The equivalent H on the base of 200 MVA,

$$\begin{aligned} &= \frac{4800 \text{ MJ}}{200 \text{ MVA}} \\ &= 24 \text{ MJ/MVA} \end{aligned}$$

5. (c)

Minimum number of equations = $2n - m - 2$

$$\begin{aligned} &= 2(112) - 20 - 2 \\ &= 202 \end{aligned}$$

6. (d)

We know that,
$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \times \frac{(MVA)_{new}}{(MVA)_{old}} \times \frac{(kV)_{old}^2}{(kV)_{new}^2}$$


For G_1 and M_1 :

$$(X_{p.u.})_{new} = 0.05 \times \frac{80}{40} \times \left(\frac{11}{11}\right)^2 = j 0.1 \text{ p.u.}$$

For line:

$$(X_{\Omega})_{base} = \frac{(kV)^2}{MVA} = \frac{33^2}{80} = 13.6125 \Omega$$
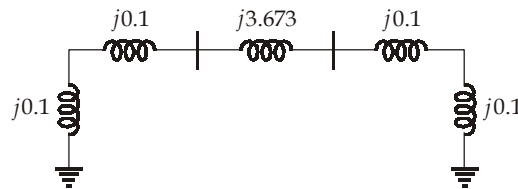
$$(X_{p.u.})_{line} = \frac{\text{Actual value}}{\text{Base value}} = \frac{50}{13.6125} = j 3.673 \text{ p.u.}$$



7. (b)

3- ϕ fault current:

Let system is under no load condition before fault,

$$\therefore E = 1 \angle 0^\circ \text{ p.u.}$$

$$3\text{-}\phi \text{ fault current, } I_f = \frac{E}{X_1}$$

$$\Rightarrow X_1 = \frac{1}{-j5} = j0.2 \text{ p.u.}$$

Line-line fault current:

$$I_f = \frac{\sqrt{3}E}{X_1 + X_2}$$


$$\Rightarrow X_1 + X_2 = \frac{\sqrt{3}}{-j2.5}$$

$$\Rightarrow j 0.2 + X_2 = j 0.69 \text{ p.u.}$$

$$\Rightarrow X_2 = j 0.49 \text{ p.u.}$$

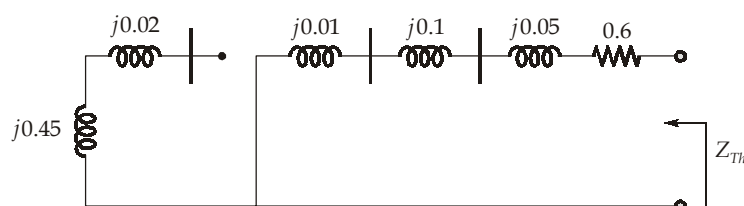8. (b)


The zero sequence impedance network from point P and ground




The Thevenin's equivalent zero sequence impedance

$$Z_{Th} = (0.6 + j 0.16) \text{ p.u.}$$

9. (a)

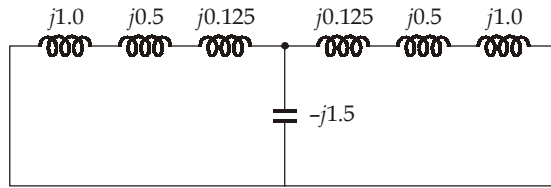

Converting star into delta:

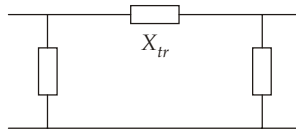

The transfer reactance,
$$X_{tr} = j1.625 + j1.625 + \frac{j1.625 \times j1.625}{-j1.5}$$

$$= 1.48 \text{ p.u.}$$

10. (d)

$$Z_{Bus (new)} = \begin{bmatrix} 0.3 & 0.3 \\ 0.3 & 0.3 + 0.5 \end{bmatrix} = \begin{bmatrix} 0.3 & 0.3 \\ 0.3 & 0.8 \end{bmatrix}$$

11. (b)

Let the base kVA be 500 kVA and base voltage be 2.5 kV,


Per unit transient reactance of generator,

$$X_g' = \frac{j8}{100} = j0.08 \text{ p.u.}$$

Per unit subtransient reactance of each motor,

$$X_m'' = j0.2 \times \frac{500}{250} = j0.4 \text{ p.u.}$$

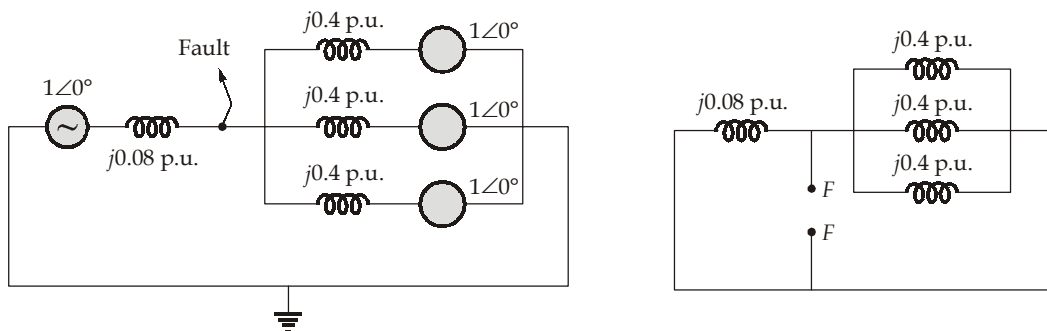Per unit reactance diagram is shown below,



Thevenin reactance when viewed from fault terminals,

$$X_{th} = \frac{\frac{j0.4}{3} \times j0.08}{\frac{j0.4}{3} + j0.08} = j0.05 \text{ p.u.}$$

At fault location V_{th} = rated voltage,

$$\text{Fault current at } F, I_f = \frac{1}{j0.05} = -j20 \text{ p.u.}$$

The generator contribution is,

$$I_g = -j20 \times \frac{j\frac{0.4}{3}}{j\frac{0.4}{3} + j0.08}$$

$$I_g = -j12.5 \text{ p.u.}$$

Contribution of motors,

$$3I_m = I_f - I_g = -j20 - (-j12.5)$$

$$3I_m = -j7.5$$

$$I_m = -j2.5 \text{ p.u.}$$

12. (c)

Only $Y_{22}, Y_{24}, Y_{42}, Y_{44}$ will change because transmission line is connected between 2nd and 4th buses.

$$\begin{aligned} Y_{22} &= -j60 + \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} \\ &= -j60 + \frac{1}{j0.1} + j20 = -j60 - j10 + j20 = -j50 \end{aligned}$$

$$Y_{24} = Y_{42} = 0 - \frac{Y_{sh}}{2} = -j20$$

$$Y_{44} = -j25 + \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} = -j25 + \frac{1}{j0.1} + j20 = -j25 - j10 + j20$$

$$Y_{44} = -j15$$

13. (c)

Reactive power supplied by capacitor to bus-1,

$$Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_2||V_1|}{X} \cos \delta$$

Given that,

$$Q_{21} = 0$$

$$\frac{|V_2|^2}{X} = \frac{|V_2||V_1|}{X} \cos \delta$$

$$|V_2| = |V_1| \cos \delta$$

Given that,

$$|V_1| = 1 \text{ p.u.}$$

$$|V_2| = \cos \delta \quad \dots(i)$$

Since load demand at bus 2 is 1 p.u. (real power). This real power can be supplied by generator S_{G1} only. So this power should flow through transmission line from bus 1 to bus 2

$$\therefore P_{12} = 1 \text{ p.u.}$$

\therefore real power flow from bus 1 to bus 2,

$$P_{12} = \frac{|V_1||V_2|}{X} \sin \delta$$

$$1 = \frac{1 \cdot \cos \delta}{0.5} \cdot \sin \delta$$

$$0.5 = \frac{\sin 2\delta}{2}$$

$$\sin 2\delta = 1$$

$$2\delta = 90^\circ$$

$$\delta = 45^\circ$$

∴ from equation (i),

$$|V_2| = \cos \delta = \cos 45^\circ = \frac{1}{\sqrt{2}}$$

Voltage at bus-2, $V_2 = \frac{1}{\sqrt{2}} \angle -45^\circ$

14. (b)

Given, before fault,

$$0.6 P_{m1} = P_{m1} \sin \delta_0$$

$$\therefore \delta_0 = 36.86^\circ \text{ (or) } 0.643 \text{ radian}$$

During fault,

$$P_{m2} = 0.25 P_{m1} \text{ as } X_2 = 4X_1$$

After fault,

$$P_{m3} = 0.75 P_{m1} \text{ (given)}$$

$$\therefore \delta_{\max} = 180 - \sin^{-1} \left(\frac{0.6 P_{m1}}{0.75 P_{m1}} \right)$$

$$= 126.86^\circ \text{ (or) } 2.214 \text{ radian}$$

Since, $\cos \delta_{cr} = \frac{P_s(\delta_{\max} - \delta_0) + P_{m3} \cos \delta_m - P_{m2} \cos \delta_0}{P_{m3} - P_{m2}}$

$$\cos \delta_{cr} = \frac{0.6 P_{m1} [2.214 - 0.643] + 0.75 P_{m1} \cos(126.86) - 0.25 P_{m1} \cos(36.86)}{0.75 P_{m1} - 0.25 P_{m1}}$$

$$= \frac{0.6(2.214 - 0.643) + 0.75 \cos(126.86) - 0.25 \cos(36.86)}{0.75 - 0.25}$$

$$\cos \delta_{cr} = 0.585$$

$$\delta_{cr} = 54.2^\circ$$

15. (b)


The reactance in p.u. = $Z_{p.u.} = Z_\Omega \times \frac{\text{MVA}_b}{(\text{kV}_b)^2}$

$$\begin{aligned} Z_\Omega &= Z_{p.u.} \times \frac{(\text{kV}_b)^2}{(\text{MVA}_b)} \\ &= 0.10 \times \frac{(33)^2}{10} = 10.89 \Omega \end{aligned}$$

So reactance per phase = $Z_{ph} = 10.89 \Omega$

$$Z_\Delta = 3 \times Z_{ph} = 3 \times 10.89$$

$$Z_\Delta = 32.67 \Omega$$

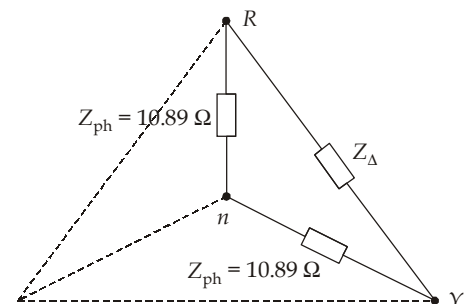

16. (b)

$$S_{D2} = (0.8 + j0) \text{ p.u.}$$

This 0.8 p.u. active power is supplied by the generator G_1

$$\therefore 0.8 = \frac{1 \times 1}{0.5} \sin \delta$$

$$\delta = \sin^{-1} \left(\frac{0.8}{2} \right) = 23.58^\circ$$

$$Q_R = \frac{|V_1| \times |V_2|}{X} \cos \delta - \frac{|V_1|^2}{X}$$


$$= \frac{1}{0.5} \cos(23.58^\circ) - \frac{1}{0.5}$$

$$Q_R = -0.167 \text{ p.u.}$$

The VAR rating of the capacitor = 0.167 p.u.

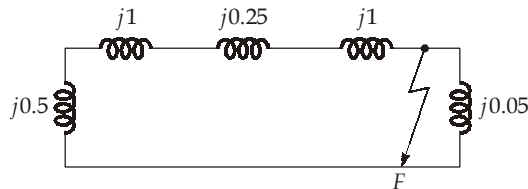17. (a)


Positive and negative sequence reactance diagram:



$$Z_1 = Z_2$$

$$= j 2.75 \parallel j 0.5 = j 0.423 \text{ p.u.}$$

Zero sequence reactance diagram:

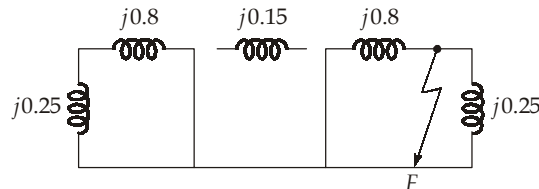

$$Z_0 = j 0.8 \parallel j 0.25 = j 0.19 \text{ p.u.}$$

Considering system at no load before fault

i.e.

$$E = 1.0 \angle 0^\circ \text{ p.u.}$$

$$(I_F) = 3 \left(\frac{E}{Z_1 + Z_2 + Z_0} \right) = 3 \left(\frac{1}{j0.423 + j0.423 + j0.19} \right)$$

$$I_f = -j2.896 \text{ p.u.}$$

18. (a)

$$|I''| = \frac{E}{|X_d''|} = \frac{1}{0.22} = 4.54 \text{ p.u.}$$

$$I_{\text{base}} = \frac{\text{MVA}_b}{\sqrt{3}(\text{kV}_b)} = \frac{100 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 5248.6 \text{ A} = 5.248 \text{ kA}$$

The magnitude of initial symmetrical rms current

$$= 4.54 \times 5.248 = 23.82 \text{ kA}$$

19. (a)

$$\vec{I}_R = 100\angle 0^\circ \text{ A} \quad ; \quad \vec{I}_Y = 100\angle -120^\circ \text{ A} \quad ; \quad \vec{I}_B = 100\angle -240^\circ \text{ A}$$

$$I_{R0} = \frac{1}{3}(\vec{I}_R + \vec{I}_Y + \vec{I}_B)$$

$$\vec{I}_{R0} = \frac{1}{3}[100\angle 0^\circ + 100\angle 240^\circ + 100\angle 120^\circ] = 0 \text{ A}$$

$$\begin{aligned} \vec{I}_{R1} &= \frac{1}{3}[\vec{I}_R + a\vec{I}_Y + a^2\vec{I}_B] \\ &= \frac{1}{3}(100\angle 0^\circ + (1\angle 120^\circ)(100\angle -120^\circ) + (1\angle 240^\circ)(100\angle -240^\circ)) \\ &= 100 \text{ A} \end{aligned}$$

$$\begin{aligned} \vec{I}_{R2} &= \frac{1}{3}[\vec{I}_R + a^2\vec{I}_Y + a\vec{I}_B] \\ &= \frac{1}{3}(100\angle 0^\circ + (1\angle 240^\circ)(100\angle -120^\circ) + (1\angle 120^\circ)(100\angle -240^\circ)) = 0 \text{ A} \end{aligned}$$

20. (b)

$$\delta_0 = \sin^{-1}\left(\frac{P_e}{P_m}\right) = \sin^{-1}(0.5) = 30^\circ$$

$$P_e = \frac{EV}{X} \sin \delta_0$$

$$\begin{aligned} \frac{dP_e}{d\delta} &= \frac{EV}{X} \cos \delta_0 = \frac{1.2 \times 1}{1.8} \cos 30^\circ \\ &= 0.577 \text{ MW (p.u.) / elec. rad} \end{aligned}$$

$$M = \frac{GH}{\pi f} = \frac{1 \times 4}{\pi \times 50} = 0.025 \text{ s}^2 / \text{elec. rad}$$


$$\omega = \left(\frac{\left(\frac{dP_e}{d\delta_0} \right)}{M} \right)^{1/2} = \left(\frac{0.577}{0.025} \right)^{1/2} = 4.8 \text{ rad/sec}$$

Frequency of natural oscillation,

$$f = \frac{\omega}{2\pi} = 0.764 \text{ Hz}$$

21. (d)

Existing system and bus matrix is

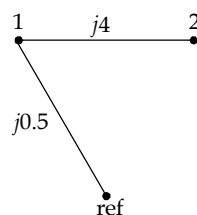

$$Z_{\text{Bus}} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix}$$

Modifying line with reactance $j2$ is equivalent to adding a line in parallel with impedance $j4$. Thus it is type-4 modification.

$$[Z_{\text{new}}] = [Z_{\text{old}}] - \frac{1}{Z_{11} + Z_{22} - 2Z_{12} + Z_s} \begin{bmatrix} \text{subtract} \\ 2^{\text{old}} \text{ column} \\ \text{to first column} \end{bmatrix} [\text{Transpose}]$$

$$[Z_{\text{Bus}}]_{\text{new}} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix} - \frac{1}{j0.5 + j4.5 - 2(j0.5) + j4} \begin{bmatrix} j0 \\ -j4 \end{bmatrix} \begin{bmatrix} j0 & -j4 \end{bmatrix}$$


$$= \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix} - \frac{1}{j8} \begin{bmatrix} 0 & 0 \\ 0 & -16 \end{bmatrix}$$

$$= \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 \end{bmatrix} - \begin{bmatrix} 0 & 0 \\ 0 & -\frac{16}{j8} \end{bmatrix}$$


$$= \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j4.5 - \frac{j16}{8} \end{bmatrix} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j2.5 \end{bmatrix}$$

Alternative :

New system will

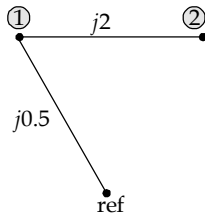


First branch :

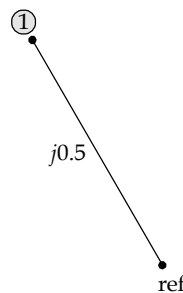

$$Z = [j0.5]$$

Type - 2 modification

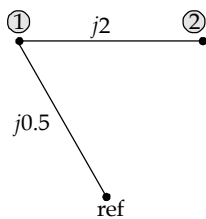

$$Z = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j0.5 + j2 \end{bmatrix} = \begin{bmatrix} j0.5 & j0.5 \\ j0.5 & j2.5 \end{bmatrix}$$

22. (b)

For single line to ground fault, fault current is

$$I_f = 3I_a^{(0)}$$

and

$$I_a^{(0)} = \frac{-V_a^{(0)}}{Z_{g0}}$$

$$V_a^{(0)} = \frac{1}{3}[V_a + V_b + V_c] = \frac{1}{3}[0 + 1.013\angle -102.25^\circ + 1.013\angle 102.25^\circ]$$

$$= -0.1433 \text{ p.u.}$$


$$I_a^{(0)} = -\left(\frac{-0.1433}{j0.1}\right) = -j1.43 \text{ p.u.}$$

$$I_f = 3 \times (-j1.43) = -j4.29 \text{ p.u.}$$

$$I_f = -j4.29 \times \left(\frac{20000}{\sqrt{3} \times 13.8}\right) = -j3.59 \text{ kA}$$

23. (b)

Reactance diagram of the system is

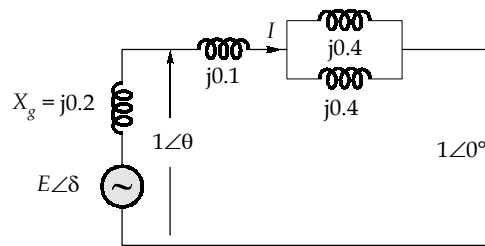Terminal voltage $V_t = 1\angle\theta$

$$\text{Power supplied} = \frac{|1||1|}{X} \sin\theta$$

$$X = j0.1 + \left(\frac{j0.4}{2}\right) = j(0.1 + 0.2) = j0.3$$

$$1.0 = \frac{1}{0.3} \sin\theta$$

$$\theta = \sin^{-1}(0.3) = 17.46^\circ$$

$$\text{Current, } \vec{I} = \frac{1\angle\theta - 1\angle 0^\circ}{j0.3}$$

$$\vec{I} = \frac{1\angle 17.46^\circ - 1\angle 0^\circ}{j0.3} = 1.0118\angle 8.73^\circ \text{ p.u.}$$

$$\text{Excitation emf, } \vec{E} = \vec{V} + jX\vec{I} = 1\angle 17.46^\circ + (j1.0118\angle 8.73^\circ)(0.2)$$

$$\vec{E} = 1.05\angle 28.44^\circ \text{ p.u.}$$

$$\text{Power angle equation} = \frac{EV}{X} \sin\delta = \frac{(1.05)(1)}{0.5} \sin\delta = 2.1 \sin\delta$$

24. (b)

We know that,
$$f_n = \sqrt{\frac{\left(\frac{\partial P_e}{\partial \delta}\right)_{\delta_0}}{M}}$$

$$\left(\frac{\partial P_e}{\partial \delta}\right)_{\delta=\delta_0} = P_{\max} \cos \delta_0 = \frac{|E||V|}{|X|} \cos \delta_0$$

$$0.5 P_{\max} = P_{\max} \sin \delta_0$$

$$\delta_0 = 30^\circ$$

$$\left.\frac{\partial P_e}{\partial \delta}\right|_{\delta=\delta_0} = \frac{1.05 \times 1}{0.8} \cos 30^\circ = 1.1366 \text{ p.u.}$$

$$M = \frac{GH}{\pi f} = \frac{1 \times 5}{\pi \times 50} = 0.0318$$

Natural frequency of Oscillations

$$f_n = \sqrt{\frac{1.1366}{0.0318}} = 5.9787 \text{ rad}$$

$$f_n = 0.9515 \text{ Hz}$$

25. (d)

$$M = \frac{GH}{\pi f} = \frac{100 \times 8}{50 \times 180} = \frac{4}{45} \text{ MJ-s/elec. degree}$$

$$\frac{Md^2\delta}{dt^2} = (P_m - P_e)$$

$$\frac{d^2\delta}{dt^2} = 30 \times \frac{45}{4}$$

$$\frac{d^2\delta}{dt^2} = 337.5 \text{ elec deg/s}^2$$

$$\frac{d\delta}{dt} = 337.5t$$

$$\frac{d\delta}{dt} = 337.5 \times \frac{10}{50} \times \frac{60}{360} \times \left(\frac{2}{4}\right) = 5.625 \text{ rpm}$$

$$\omega_m = \omega_{m0} + \frac{d\delta}{dt}$$

$$N_m = \frac{120 \times 50}{4} + 5.625 = 1505.625 \text{ rpm}$$

26. (b)

$$X_{1 \text{ eq}} = \frac{j0.18}{2} = j0.09 \text{ p.u.}$$

$$X_{2 \text{ eq}} = \frac{j0.15}{2} = j0.075 \text{ p.u.}$$

$$Z_{0\text{eq}} = j0.1 + \frac{3 \times 2}{11^2} \times 20 = (0.9917 + j0.1) \text{ p.u.}$$

$$\begin{aligned} \text{Fault current, } I_f &= \frac{3E_f}{j(X_1) + jX_2 + Z_{0\text{eq}}} \\ &= \frac{3 \times 1 \angle 0^\circ}{1.0265 \angle 14.96^\circ} = 2.922 \angle -14.96^\circ \text{ A} \end{aligned}$$

Current in grounding resistor,

$$I_f = 2.922 \times \frac{20}{11\sqrt{3}} = 3.07 \text{ kA}$$


27. (a)

Let the base MVA be 45 MVA.

$$\% \text{ Reactance of alternator } A \text{ at the base MVA } (\%X_A) = \frac{45}{25} \times 40 = 72\%$$

$$\% X_B = 60\%$$

% reactance of alternator B,

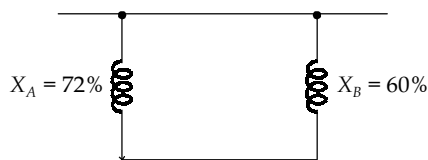

$$I_{\text{base}} = \frac{\text{MVA}}{\sqrt{3} \text{ kV}} = \frac{45 \times 10^6}{\sqrt{3} \times 15 \times 10^3} = 1732.05 \text{ A}$$

Total % reactance from generator neutral to fault point is

$$\% X = X_A \parallel X_B = \frac{60 \times 72}{60 + 72} = 32.72\%$$

P.u. short circuit current,

$$I_{\text{SC}} = \frac{1}{0.3272} = 3.0562 \text{ p.u.}$$

$$I_{\text{SC actual}} = I_{\text{SC p.u.}} \times I_{\text{base}} = 5293 \text{ A} = 5.29 \text{ kA}$$

28. (c)

For a line to ground fault,


Positive sequence current,

$$I_{a1} = \frac{E_a}{Z_1 + Z_2 + Z_0}$$


$$I_{a1} = \frac{1}{j0.25 + j0.35 + j0.1} = -j1.428$$

$$\text{Base current, } I_B = \frac{25 \times 1000 \times 10^3}{\sqrt{3} \times 13.2 \times 10^3} = 1093.46 \text{ A}$$
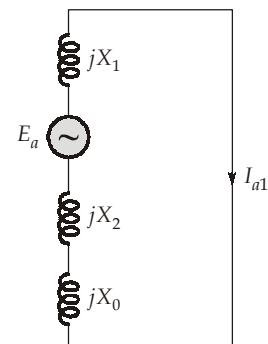
$$\begin{aligned} \text{Fault current, } I_f &= 3I_{a1} \times I_b \\ &= 3 \times 1.428 \times 1093.46 \\ &= 4684.38 \text{ A} \end{aligned}$$



29. (d)

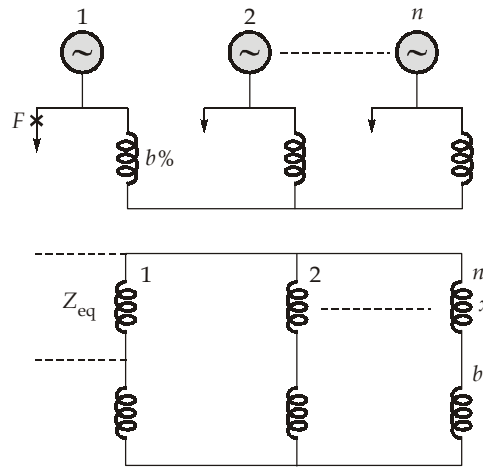

Equivalent impedance Z_{eq} between the zero potential bus and the fault point is

$$\left(\frac{b+x}{n-1} + b\right) \parallel x = \left(\frac{bn+x}{n-1}\right) \parallel x$$

$$\frac{1}{Z_{eq}} = \frac{1}{x} + \frac{n-1}{bn+x}$$

$$\begin{aligned} \text{SC kVA} &= \frac{8}{Z_{eq}} \times 100 \\ &= 8 \left[\frac{1}{x} + \frac{n-1}{bn+x} \right] \times 100 \end{aligned}$$

If n is very large.

$$\text{Short circuit kVA} = 8 \left[\frac{1}{x} + \frac{1}{b} \right]$$

30. (a)

$$\begin{aligned} \delta_0 &= \sin^{-1}(0.25) \\ &= 14.48^\circ \end{aligned}$$

$$\begin{aligned} \delta_c &= \sin^{-1}(0.5) \\ &= 30^\circ \end{aligned}$$

$$\int_{\delta_0}^{\delta_c} (0.5 - \sin \delta) d\delta = \int_{\delta_c}^{\delta_m} (\sin \delta - 0.5) d\delta$$

$$\Rightarrow 0.5(\delta_c - \delta_0) + \cos \delta_c - \cos \delta_0 = \cos \delta_c - \cos \delta_m - 0.5(\delta_m - \delta_c)$$

$$0.5(\delta_m - \delta_0) = \cos 14.48^\circ - \cos \delta_m$$

$$0.5 \delta_m + \cos \delta_m = 1.0945$$

$$\delta_m = 46.41^\circ$$

