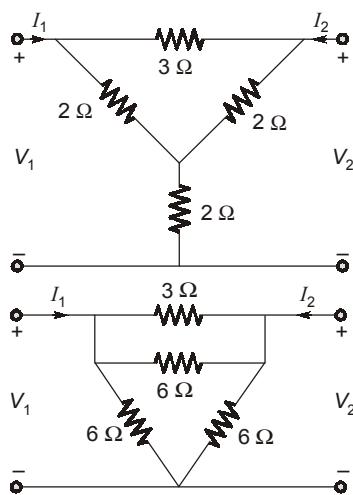



### ANSWER KEY > Network Theory

- |        |         |         |         |         |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (d)  | 13. (a) | 19. (b) | 25. (d) |
| 2. (c) | 8. (c)  | 14. (c) | 20. (b) | 26. (a) |
| 3. (b) | 9. (a)  | 15. (b) | 21. (b) | 27. (b) |
| 4. (b) | 10. (b) | 16. (c) | 22. (c) | 28. (b) |
| 5. (a) | 11. (c) | 17. (a) | 23. (d) | 29. (b) |
| 6. (b) | 12. (d) | 18. (c) | 24. (b) | 30. (d) |


### DETAILED EXPLANATIONS

1.(b)



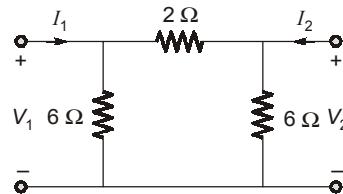

for  $\Pi$ -network

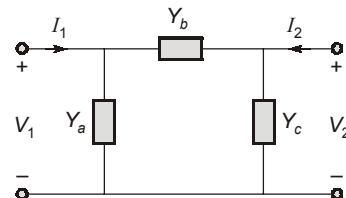

$$\therefore [Y] = \begin{bmatrix} Y_a + Y_b & -Y_b \\ -Y_b & Y_b + Y_c \end{bmatrix}$$

$$\text{for the given problem, } Y_a = \frac{1}{6} \text{ S}$$

$$Y_b = \frac{1}{2} \text{ S}$$

$$Y_c = \frac{1}{6} \text{ S}$$

$$\therefore [Y] = \begin{bmatrix} \frac{2}{3} \text{ S} & -\frac{1}{2} \text{ S} \\ -\frac{1}{2} \text{ S} & \frac{2}{3} \text{ S} \end{bmatrix}$$

### 2.(c)

$$\text{Time period } (T) = \frac{2\pi}{\omega}$$

where

$$\omega = \frac{1}{\sqrt{LC}}$$

thus,

$$T = 2\pi\sqrt{LC}$$


In figure

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} + 2M_{23} - 2M_{13}$$

$$= 4 + 5 + 6 - 2(2) + 2(2) - 2(3) = 9 \text{ H}$$


$$C = 1 \text{ F}$$

$$T = 2\pi\sqrt{9} = 6\pi \text{ sec}$$

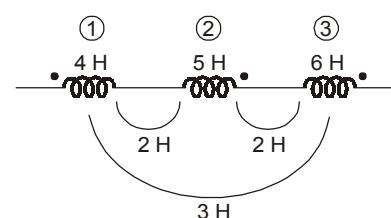
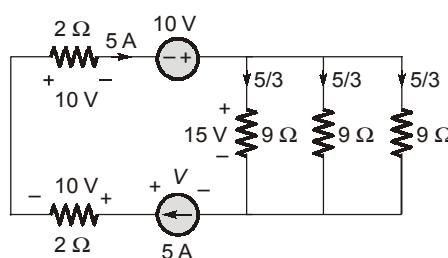
### 3.(b)

The circuit can be redrawn by short circuiting inductor and open circuiting capacitor as DC sources are used.



Applying KVL

$$V - 10 - 10 + 10 - 15 = 0 \\ V = 25 \text{ V}$$

4.(b)

$$\frac{R}{2} \sqrt{\frac{L}{C}} \Rightarrow \frac{R}{2} \sqrt{\frac{L\omega}{C\omega}} = \frac{R}{2} \sqrt{X_L X_C}$$

Unit of  $R_1$  is  $\Omega$

Unit of ' $X_L$ ' and ' $X_C$ ' is  $\Omega$

$$\text{Unit of } \frac{R}{2} \sqrt{\frac{L}{C}} \text{ is } \Omega \times \sqrt{\Omega \times \Omega} \Rightarrow (\Omega)^2$$

5.(a)

The average value of periodic signal can be calculated by considering one time period


$$= \frac{\text{Total area under the graph for one period}}{T_0}$$

Total area under the graph for one period = Area 1 + Area 2 + Area 3 + Area 4

here Area 1 = Area 2 = Area 3 = Area 4 = 4

and  $T_0 = 8 \text{ sec}$
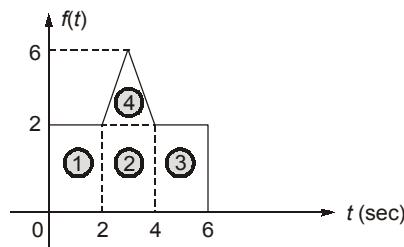
$$\text{Average value} = \frac{4 + 4 + 4 + 4}{8} = \frac{16}{8} = 2$$




6.(b)

Before closing the switch, the circuit was not energized, therefore, current through inductor and voltage across capacitor are zero.

After closing the switch, at  $t = 0^+$  inductor acts as open-circuit and capacitor acts as short-circuit.

Equivalent circuit at  $t = 0^+$

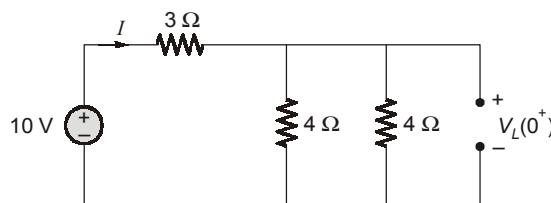

$$I = \frac{10}{3 + 4 \parallel 4} = 2 \text{ A}$$

$$V_L(0^+) = I \times (4 \parallel 4) \\ = 2 \times 2 = 4 \text{ V}$$

**7.(d)**

Applying KVL in both the loops we get


$$V_1 = (j\omega L_1)I_1 + (j\omega M)I_2$$

$$V_2 = (j\omega L_2)I_2 + (j\omega M)I_1$$

$$\frac{V_2}{V_1} = \frac{L_2 I_2 + M I_1}{L_1 I_1 + M I_2}$$

$$\text{also, } M = K\sqrt{L_1 L_2} = \sqrt{L_1 L_2};$$

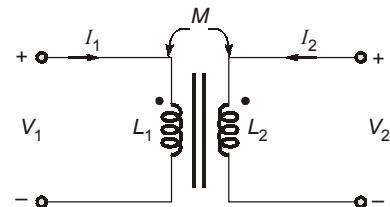$\therefore K = 1$  for ideal transformer



$$\frac{V_2}{V_1} = \frac{L_2 I_2 + \sqrt{L_1 L_2} I_1}{L_1 I_1 + \sqrt{L_1 L_2} I_2}$$

$$\therefore \frac{V_2}{V_1} = \frac{\sqrt{L_2}}{\sqrt{L_1}}$$

$$\Rightarrow \frac{V_2}{V_1} = \sqrt{\frac{5}{25}} = \frac{1}{\sqrt{5}}$$

**8.(c)**

As we know,

$$\text{Real power} = V_{\text{rms}} \cdot I_{\text{rms}} \cos \phi \quad \dots(i)$$

$$\text{Reactive power} = V_{\text{rms}} \cdot I_{\text{rms}} \sin \phi \quad \dots(ii)$$

$$\text{Apparent power} = V_{\text{rms}} \cdot I_{\text{rms}} \quad \dots(iii)$$

$$\text{Given that } v(t) = 10\cos(2t + 75^\circ) \\ i(t) = 2\cos(2t + 15^\circ)$$

from equation (i)


$$\text{Real power} = \frac{10}{\sqrt{2}} \times \frac{2}{\sqrt{2}} \times \frac{1}{2} = 5 \text{ Watts}$$

from equation (ii)

$$\text{Reactive power} = \frac{10}{\sqrt{2}} \times \frac{2}{\sqrt{2}} \times \frac{\sqrt{3}}{2} = 5\sqrt{3} = 8.66 \text{ VAR}$$

from equation (iii)


$$\text{Apparent power} = \frac{10}{\sqrt{2}} \times \frac{2}{\sqrt{2}} = 10 \text{ VA}$$

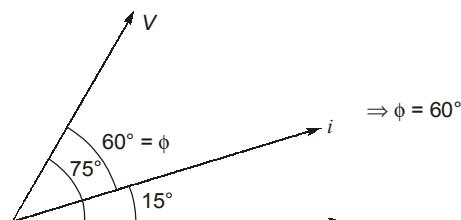**9.(a)**

$$Y = Y_1 + Y_2$$

$$Y = \frac{1}{R + jX_L} + \frac{1}{R - jX_C}$$
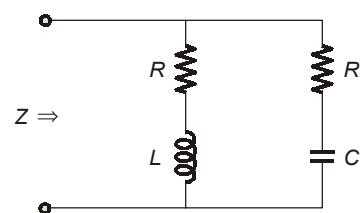
$$Y = \frac{R - jX_L}{(R^2 + X_L^2)} + \frac{(R + jX_C)}{(R^2 + X_C^2)}$$



$$\text{Im}(Y) = \frac{-X_L(R^2 + X_C^2) + X_C(R^2 + X_L^2)}{(R^2 + X_L^2)(R^2 + X_C^2)}$$

For 'Z' to purely resistive

also  $\text{Im}(Y) = 0$

$$\begin{aligned} \Rightarrow X_L(R^2 + X_C^2) &= X_C(R^2 + X_L^2) \\ R^2 X_L + X_C^2 X_L &= R^2 X_C + X_L^2 X_C \\ R^2(X_L - X_C) &= X_L X_C (X_L - X_C) \end{aligned}$$

$$R^2 = X_L X_C = \omega L \times \frac{1}{\omega C} = \frac{L}{C}$$

### 10.(b)

For parallel resonant circuit

$$Q_0 = R \sqrt{\frac{C}{L}}$$

$$Q_0 = 2000 \sqrt{\frac{54 \times 10^{-6}}{240 \times 10^{-3}}}$$

$$Q_0 = 2000 \sqrt{\frac{9}{4} \times 10^{-4}}$$

$$Q_0 = \frac{2000}{100} \times \frac{3}{2}$$

$$Q_0 = 30$$

### 11.(c)

Also

$$L_{\text{eq}} = (L + L - 2M) \parallel L$$


$$M = k \sqrt{L_1 L_2} = M = k \sqrt{L^2} = kL$$

$$L_{\text{eq}} = (L + L - 2kL) \parallel L$$

$$\frac{L}{3} = \frac{(2L - 2kL) \times L}{2L - 2kL + L}$$

on solving, we get

$$k = 0.75$$

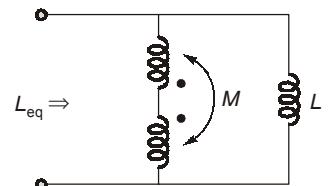


### 12.(d)

$$V_C(s) = I(s) \times \frac{1}{1 + \frac{1}{s}} \times \frac{1}{s} = I(s) \times \frac{1}{s+1}$$

$$I(s) = \frac{2(s+1)}{(s+1)^2 + 1}$$

$$V_C(s) = \frac{2(s+1)}{(s+1)^2 + 1} \times \frac{1}{1+s} = \frac{2}{(s+1)^2 + 1}$$

$$v_C(t) = 2e^{-t} \sin t u(t) V$$

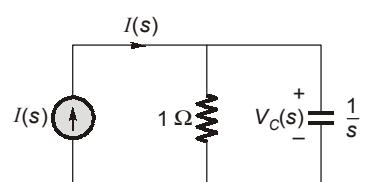

## 13.(a)


to determine  $V_{th}$ :

$$I_1 = \frac{10 - 5V_2}{3} = \frac{10 - 5V_{th}}{3}$$

$$V_{th} = -\frac{I_1}{2} = \frac{5V_{th} - 10}{6}$$

$$6V_{th} = 5V_{th} - 10$$

$$V_{th} = -10 \text{ V}$$

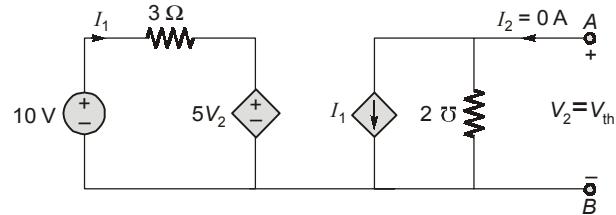to determine  $R_{th}$ :

$$I_2 = 2V_2 + I_1$$

$$1 \text{ A} = 2V_2 + I_1$$


$$0 = 3I_1 + 5V_2$$

$$I_1 = -\frac{5}{3}V_2$$

$$1 \text{ A} = 2V_2 - \frac{5}{3}V_2$$


$$V_2 = 3 \text{ V}$$
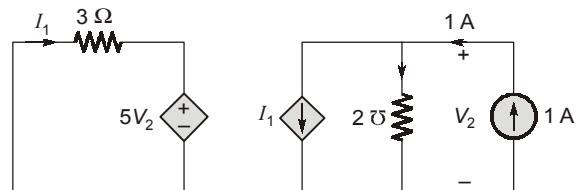
$$R_{th} = \frac{V_2}{1 \text{ A}} = 3 \Omega$$




$$P_{L_{max}} = \frac{V_{th}^2}{4R_{th}} = \frac{100}{12} \text{ W} = 8.33 \text{ W}$$

## 14.(c)

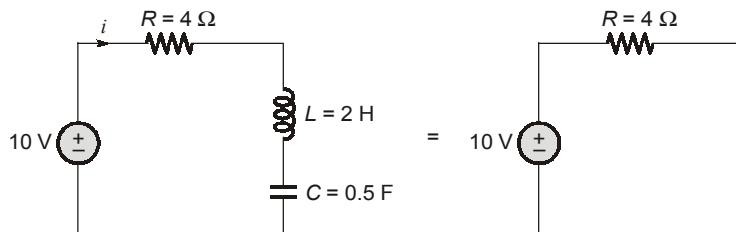At ( $t = 0^-$ )

$$V_C(0^-) = 10 \text{ V}$$

$$i_L(0^-) = 0 \text{ A}$$

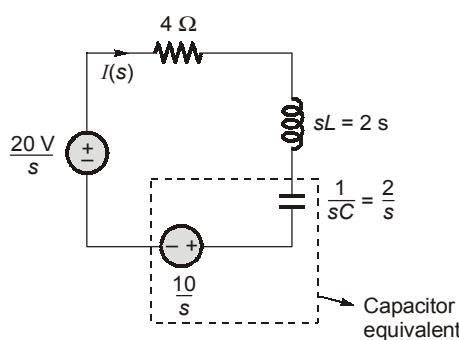At ( $t = 0^+$ )

$$I(s) = \frac{10/s}{4+2s+\frac{2}{s}} = \frac{10/s}{\frac{4s+2s^2+2}{s}} = \frac{10}{2(s^2+2s+1)}$$

$$I(s) = \frac{5}{(s+1)^2}$$

$$i(t) = 5te^{-t} u(t) \text{ A}$$

### 15.(b)

For a series  $RL$  circuit with DC excitation,

$$i(t) = \frac{V_s}{R} \left( 1 - e^{-\frac{Rt}{L}} \right) u(t) \text{ A}$$

$$v(t) = V_s \left( e^{-\frac{Rt}{L}} \right) u(t) \text{ A}$$

$$A = \frac{V_s}{R}$$

$$B = \frac{R}{L}$$

$$C = V_s$$

$$\frac{AB}{C} = \frac{\frac{V_s}{R} \times \frac{R}{L}}{V_s} = \frac{1}{L}$$

$$= \frac{1}{5 \times 10^{-3}} = 200$$

### 16.(c)

Applying Millman's Theorem

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{30} + \frac{1}{90} + \dots$$


$$\frac{1}{R_{eq}} = \frac{1}{10} \left( 1 + \frac{1}{3} + \frac{1}{9} + \dots \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{10} \left( \frac{1}{1 - \frac{1}{3}} \right) = \frac{3}{10 \times 2} = \frac{3}{20}$$

$$R_{eq} = \frac{20}{3} \Omega$$

$$V_{eq} = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3} + \dots}{\frac{1}{R_{eq}}}$$

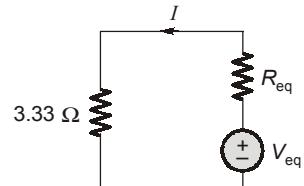
$$= \frac{1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots}{\frac{3}{20}} = \frac{\frac{1}{1 - \frac{1}{2}}}{\frac{3}{20}} = \frac{20}{3} \times 2$$



$$V_{\text{eq}} = \frac{40}{3} \text{ V}$$

$$I = \frac{\frac{40}{3}}{\frac{20}{3} + \frac{10}{3}} = \frac{\frac{40}{3}}{\frac{30}{3}} = \frac{4}{3} \text{ A}$$

$$I = 1.33 \text{ A}$$

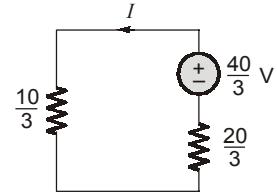
**17.(a)**

At ( $t = 0^-$ ), both the switches are opened.

$L$  is initially uncharged  $i_L(0^-) = 0$


At ( $t = 0^+$ )

$$i(t) = i(\infty) + (i(0^+) - i(\infty)) e^{-\frac{R_{\text{eq}} t}{L_{\text{eq}}}}$$

$$R_{\text{eq}} = 5 \Omega$$

$$L_{\text{eq}} = 1 \text{ H}$$

$$i(0^+) = 0 \text{ A}$$

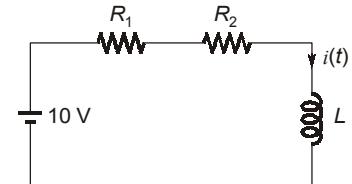

$$i(t) = 2 + (0 - 2)e^{-\frac{5t}{1}} \text{ A} ; \text{ for } t > 0$$

At ( $t = 2^-$ )

$$i(2^-) = 2 - 2e^{-\frac{10}{1}} \text{ A}$$

$$i(2^-) \approx 2 \text{ A}$$


At ( $t = 2^+$ )

$$i(2^-) = i(2^+) = 2 \text{ A}$$

for  $t > 2$  sec

$$i(t) = i(\infty) + (i(2^+) - i(\infty)) e^{-\frac{R_1(t-2)}{L}} ; \text{ for } t > 2$$

$$i(t)|_{t=3s} = 5 + (2 - 5)e^{-\frac{2}{1}(3-2)} = 5 - 3e^{-2} \\ = 4.594 \text{ A}$$

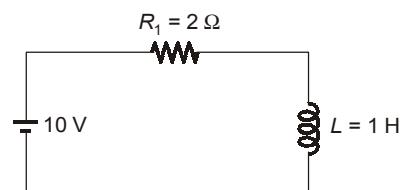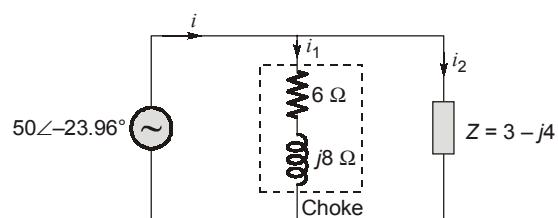

**18.(c)**

Here, applying KCL


$$i(t) = i_1(t) + i_2(t) \\ = \frac{V_1}{6+j8} + \frac{V_1}{3-j4}$$

$$\Rightarrow V_1 \left( \frac{3-j4+6+j8}{2(3+j4)(3-j4)} \right) = \frac{V_1(9+j4)}{2 \times 25}$$

$$\Rightarrow \frac{50 \angle -23.96^\circ \times \sqrt{97} \angle 23.96^\circ}{50} \text{ A} = \sqrt{97} \text{ A} \\ = 9.85 \text{ A}$$




19.(b)

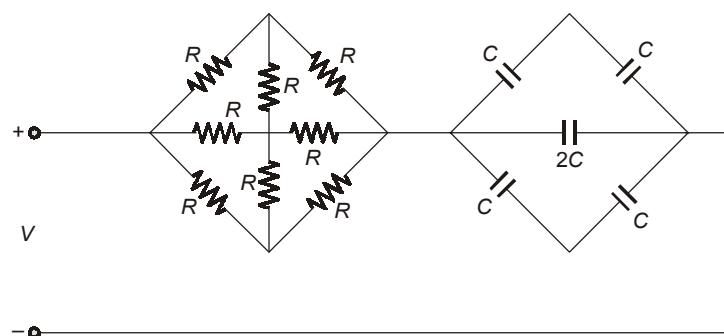


The time constant of an  $RC$  circuit is  $\tau = R_{eq} C_{eq}$


Calculation of  $C_{eq}$

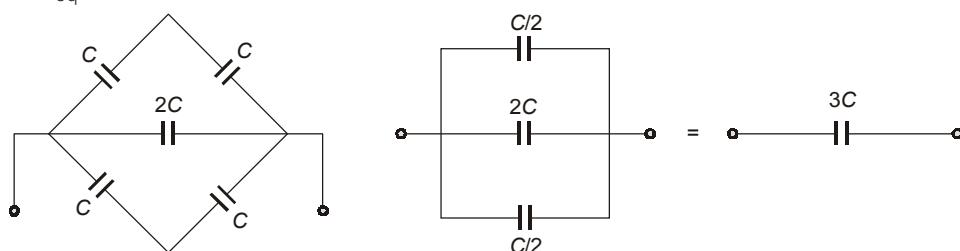

Calculation of  $R_{eq}$

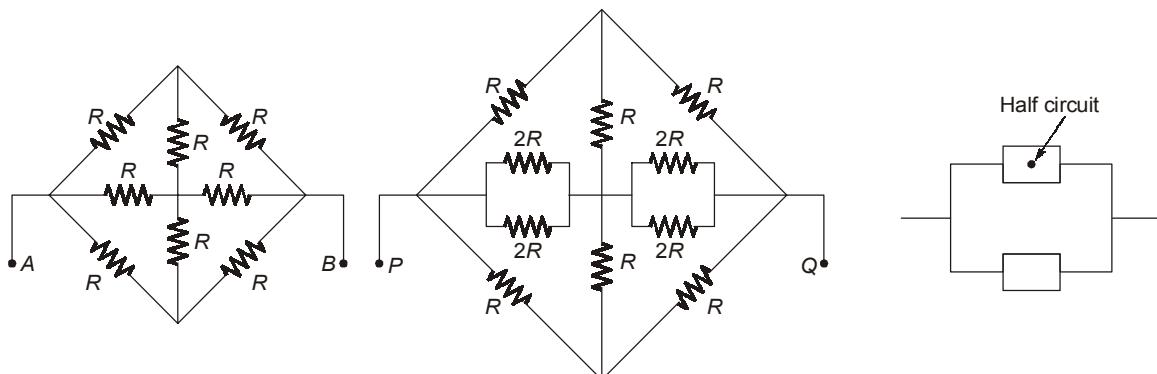

It is Wheatstone bridge.

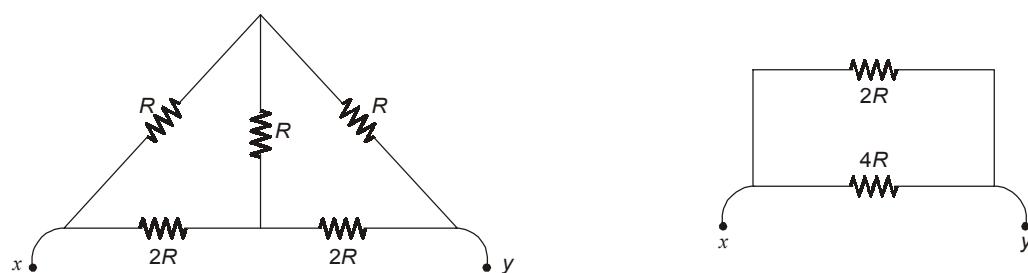

$$(R_{eq})_{\text{Half circuit}} = \frac{4R \times 2R}{6R} = \frac{4R}{3}$$

$$R_{eq} = (R_{eq})_{\text{Half circuit}} \parallel (R_{eq})_{\text{Half circuit}}$$


$$= \left(\frac{4R}{3}\right) \parallel \left(\frac{4R}{3}\right) = \left(\frac{2R}{3}\right)$$

$$\therefore \tau = R_{eq} C_{eq}$$

$$= \frac{2R}{3} \times 3C = 2RC$$

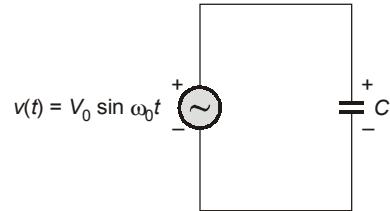20.(b)


$$\begin{aligned} W(t) &= \frac{1}{2} Cv^2(t) \\ &= \frac{1}{2} CV_0^2 \sin^2 \omega_0 t \\ &= \frac{1}{4} CV_0^2 (1 - \cos 2\omega_0 t) \end{aligned}$$



thus only option (b) satisfies this condition.

21.(b)

Network 'N' can be replaced as

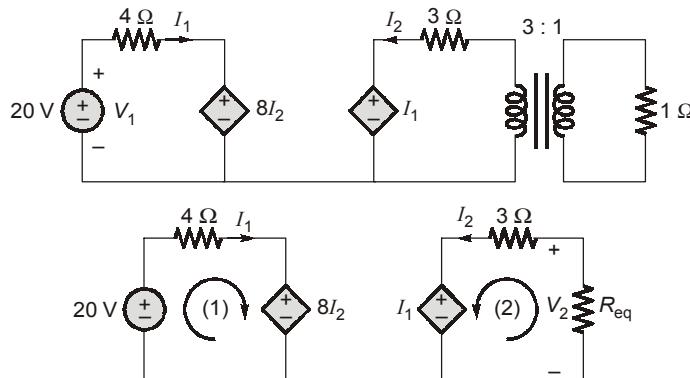


$$R_{eq} = (1) \times \left(\frac{3}{1}\right)^2 = 9 \Omega$$

Applying KVL at loop (1)

$$\begin{aligned} 20 &= 4I_1 + 8I_2 \\ \text{also } V_2 &= -9I_2 = I_1 + 3I_2 \\ \Rightarrow I_1 &= -12I_2 \\ 20 &= 4(-12I_2) + 8I_2 \\ 20 &= -40I_2 \\ \Rightarrow I_2 &= -0.5 \text{ A} \\ I_1 &= -12(-0.5) = 6 \text{ A} \end{aligned}$$


Now,
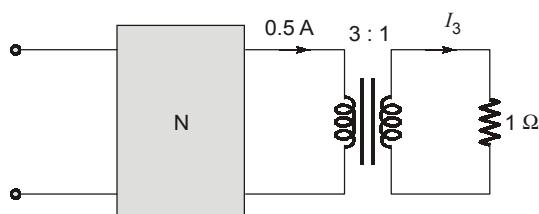
$$\begin{aligned} \frac{I_{\text{primary}}}{I_{\text{secondary}}} &= \frac{1}{3} \\ \Rightarrow 3I_{\text{primary}} &= I_{\text{secondary}} \\ 3(-I_2) &= I_3 \\ \Rightarrow I_3 &= 1.5 \text{ A} \\ \text{Power delivered to } 1 \Omega &= (I_3)^2 \times R_L = (1.5)^2 \times 1 \\ &= 2.25 \text{ Watts} \end{aligned}$$



22.(c)

Calculating  $R_{th}$

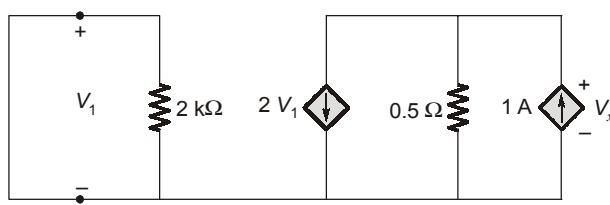


$$1 \text{ A} = \frac{V_x}{0.5} + 2V_1$$

$$\therefore V_1 = 0 \quad (\text{As independent voltage source is short circuited})$$

$$\Rightarrow V_x = 0.5 \text{ V}$$

$$R_{th} = 0.5 \Omega = 500 \text{ m}\Omega$$

Calculating  $V_{th}$

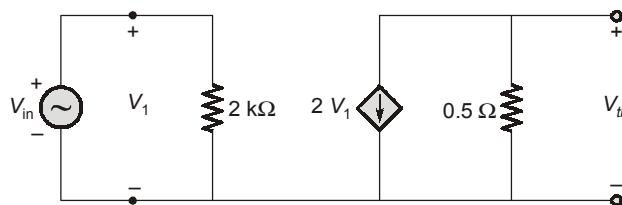


$$V_{th} = -2V_1 \times 0.5$$

$$V_1 = V_{in} = 5\angle 0^\circ \text{ V}$$

$$V_{th} = -2 \times 5 \times 0.5 = -5\angle 0^\circ$$

$$= 5\angle 180^\circ \text{ V}$$

23.(d)

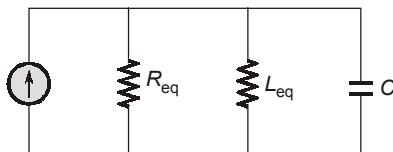


For a parallel resonant circuit

the damping ratio

$$\xi = \frac{1}{2Q} = \frac{1}{2R_{eq}} \sqrt{\frac{L_{eq}}{C}} = \frac{1}{\sqrt{2}}$$

... (i)

given

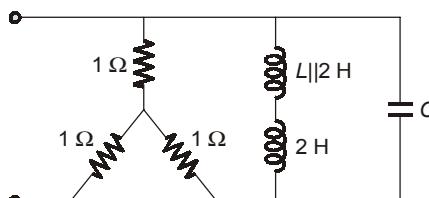

$$R_{eq} = 1 \parallel 1 + 1 = 1.5 \Omega$$

$$L_{eq} = 2 + \frac{2L}{L+2}$$

$$C_{eq} = \frac{4}{9}$$

From equation (i)

$$\frac{L_{eq}}{C} = \frac{4R_{eq}^2}{2} = 2R_{eq}^2$$


or  $L_{eq} = 2R_{eq}^2 C = 2 \times (1.5)^2 \times \frac{4}{9} = 2 \text{ H}$

$$\therefore L_{eq} = 2H + \frac{2L}{L+2}$$

$$2 + \frac{2L}{L+2} = 2 \text{ H}$$

$$\Rightarrow L = 0 \text{ H}$$

24.(b)

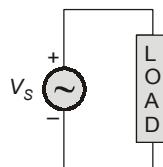


$$pf = 0.50 \text{ lagging}$$

$$\cos\phi = 0.5$$



$$\phi = 60^\circ$$

$$\Rightarrow Q = P \tan 60^\circ = 10\sqrt{3} \text{ kVAR}$$
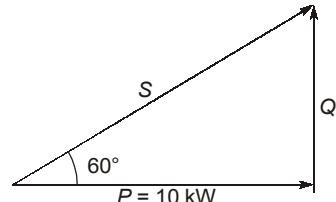
$$S = \sqrt{P^2 + Q^2} = 20 \text{ kVA}$$



Now,

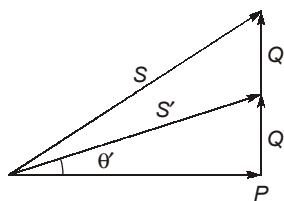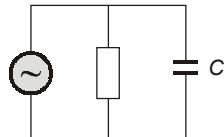

As per question

$$S' = 14.14 = 10\sqrt{2} \text{ kVA}$$

$$P' = 10 \text{ kW}$$

$$\cos\theta' = \frac{P}{S} = \frac{10}{10\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$\theta' = 45^\circ$$

$$Q' = 10 \text{ kVAR}$$

Reduction in reactive power

$$= (10\sqrt{3} - 10) \text{ kVAR}$$

$$= 10(\sqrt{3} - 1) = 10(0.732)$$

$$= 7.32 \text{ kVAR}$$

25. (d)

Let  $v_{in}(t)$  be the input voltage while  $v_{out}(t)$  be the output voltage

$$h(t) = (e^{-2t} + e^{-3t}) u(t) \text{ V}$$

$$\therefore H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{s+2} + \frac{1}{s+3} = \frac{2s+5}{(s+2)(s+3)}$$

if

$$v_{out}(t) = te^{-2t} u(t) \text{ V}$$

$$V_{out}(s) = \frac{1}{(s+2)^2}$$

However,

$$H(s) = \frac{2s+5}{(s+2)(s+3)} = \frac{V_{out}(s)}{V_{in}(s)}$$

$\therefore$

$$V_{in}(s) = \frac{V_{out}(s)}{H(s)}$$

or


$$V_{in}(s) = \frac{1}{(s+2)^2} \times \frac{(s+2)(s+3)}{(2s+5)} = \frac{1}{2} \left[ \frac{2}{s+2} - \frac{1}{s+2.5} \right]$$

Taking inverse of Laplace

$$v_{in}(t) = \left( e^{-2t} - \frac{1}{2} e^{-2.5t} \right) u(t) \text{ volts}$$

26.(a)

For the circuit

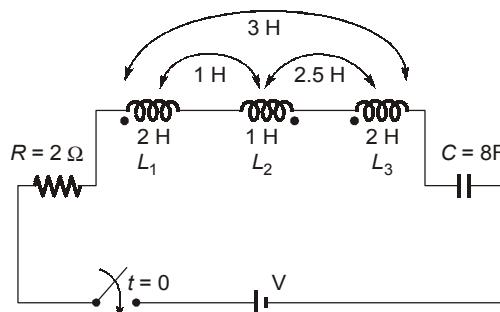

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$$

$$L_1 = 2 \text{ H}$$

$$L_2 = 1 \text{ H}$$

$$L_3 = 2 \text{ H}$$

$$M_{12} = 1 \text{ H}$$

$$M_{23} = 2.5 \text{ H}$$

$$M_{13} = 3 \text{ H}$$

$$L_{eq} = 2 + 1 + 2 - 2 - 5 + 6$$

$$= 11 - 7$$

$$= 4 \text{ H}$$

$$C = 8 \text{ F}$$

$$R = 2 \Omega$$

Note :  $M_{12}$ ,  $M_{23}$  is negative, because both  $L_1$ ,  $L_2$  and  $L_2$ ,  $L_3$  opposes the flux of respective loops.


$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{2}{2} \sqrt{\frac{8}{4}} = \sqrt{2} = 1.414$$

Thus, the given circuit is overdamped.

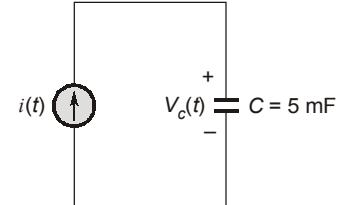27.(b)

$$i = C \frac{dv}{dt}$$

$$V_C = \frac{1}{C} \int_{-\infty}^t i dt$$




For  $0 < t < 5$  ; Unit step current is applied ; voltage will increase linearly.

For  $5 < t < 10$  ; No current is applied, hence open circuit, the capacitor will hold the charge.

For  $10 < t < 15$  ; again capacitor's voltage increases linearly.

From above analysis,

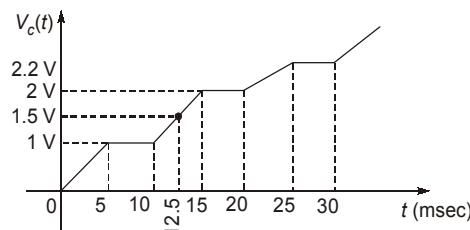

$$V_C(t)|_{12.5 \text{ msec}} = 1.5 \text{ V}$$


28.(b)

Applying KVL,

$$V_{in} - i_1(1 + 1) - 50 i_1(-jX_C) = 0$$

$$\Rightarrow V_{in} = i_1[2 - j50 X_C]$$
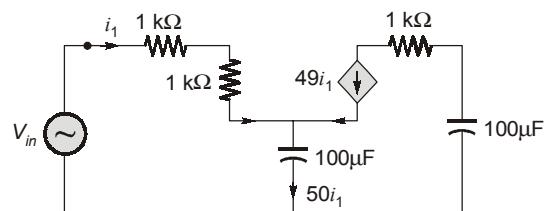
$$\text{Input impedance} = \frac{V_{in}}{i_1} = 2 - j50X_C$$



As imaginary part is negative, input impedance has equivalent capacitive reactance  $X_{Ceq}$ .

$$X_{Ceq} = 50 X_C$$


$$\frac{1}{\omega C_{eq}} = \frac{50}{\omega C}$$

$$C_{eq} = \frac{C}{50} = \frac{100}{50} \mu F$$

$$C_{eq} = 2 \mu F$$

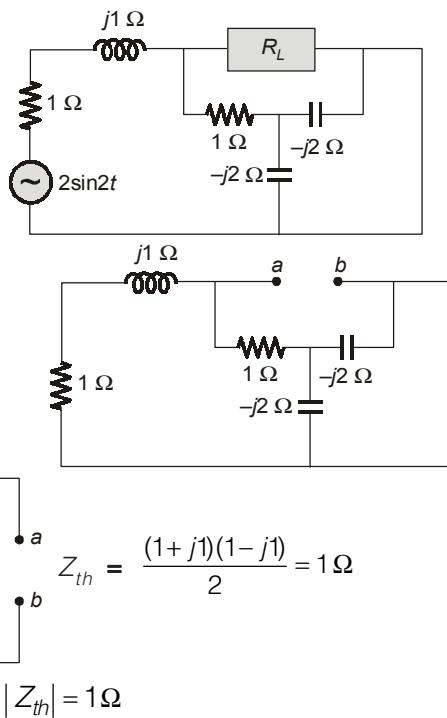29.(b)

Since  $(\omega) = 2 \text{ rad/sec}$ , the network is drawn as




Hence, for maximum power to  $R_L$ , it should be  $1\Omega$ .

30. (d)

$$\begin{aligned} v(t) &= 2\cos(500t + 60^\circ) \text{ V} \\ &= 2\angle 60^\circ \text{ V} \end{aligned}$$

Using AC phasor
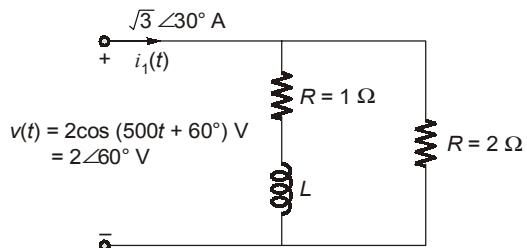
$$\begin{aligned} i(t) &= -\sqrt{3}\cos(500t + 30^\circ) \text{ A} \\ v(t) &= 2\angle 60^\circ \text{ V} \\ i_1(t) = -i(t) &= \sqrt{3}\angle 30^\circ \text{ A} \\ \sqrt{3}\angle 30^\circ &= \frac{2\angle 60^\circ}{1+jX_L} + \frac{2\angle 60^\circ}{2} \\ \sqrt{3}\angle 30^\circ &= \frac{2\left(\frac{1}{2} + j\frac{\sqrt{3}}{2}\right)}{(1+jX_L)} + \frac{1}{2} + j\frac{\sqrt{3}}{2} \end{aligned}$$



By equating real parts on both sides,

$$\begin{aligned} \frac{3}{2} &= \frac{1}{1+X_L^2} + \frac{1}{2} + \frac{X_L\sqrt{3}}{1+X_L^2} \\ &= \frac{1+X_L\sqrt{3}}{1+X_L^2} = \frac{3}{2} - \frac{1}{2} = 1 = 1+X_L\sqrt{3} = 1+X_L^2 \end{aligned}$$

$$X_L = \omega L = \sqrt{3} \Omega$$

$$\text{or } L = \frac{\sqrt{3}}{500} = 3.46 \text{ mH}$$

