

CLASS TEST

S.No. : 02 LS1_EC_B_140519

Networks Theory



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Noida | Bhopal | Hyderabad | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

CLASS TEST 2019-2020

ELECTRONICS ENGINEERING

Networks Theory


Date of Test : 14/05/2019

Answer Key

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (a) | 7. (c) | 13. (a) | 19. (a) | 25. (d) |
| 2. (c) | 8. (a) | 14. (d) | 20. (b) | 26. (d) |
| 3. (b) | 9. (b) | 15. (d) | 21. (a) | 27. (a) |
| 4. (b) | 10. (a) | 16. (b) | 22. (a) | 28. (a) |
| 5. (a) | 11. (c) | 17. (a) | 23. (d) | 29. (b) |
| 6. (b) | 12. (a) | 18. (a) | 24. (b) | 30. (c) |

DETAILED EXPLANATIONS

1. (a)

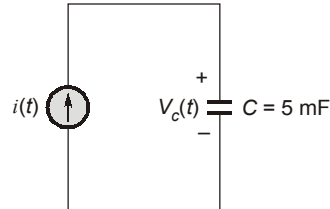

$$i = C \frac{dv}{dt}$$


$$V_C = \frac{1}{C} \int_{-\infty}^t i dt$$

For $0 < t < 5$; Unit step current is applied ; voltage will increase linearly.

For $5 < t < 10$; No current is applied, hence open circuit, the capacitor will hold the charge.

For $10 < t < 15$; again capacitor's voltage increases linearly.


From above analysis,

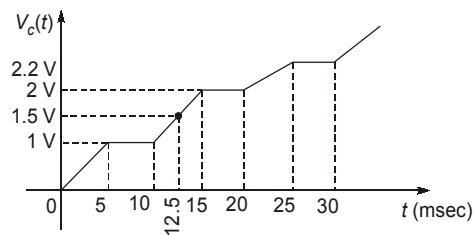

$$V_C(t)|_{12.5 \text{ msec}} = 1.5 \text{ V}$$

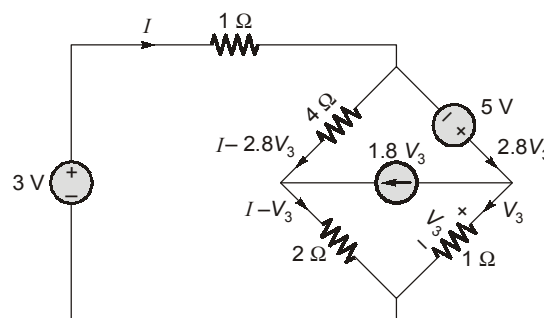3. (b)

Showing the corresponding currents in all the branches, the circuit is shown as below



Now we apply KVL in outer loop


$$\begin{aligned} -3 + I(1) - 5 + V_3 &= 0 \\ I + V_3 &= 8 \end{aligned} \quad \dots(i)$$

Applying KVL in bridge,

$$\begin{aligned} -5 + V_3 - 2(I - V_3) - 4(I - 2.8V_3) &= 0 \\ 14.2 V_3 - 6I &= 5 \\ I &= 5.37 \text{ A} \\ V_3 &= 2.62 \text{ V} \end{aligned}$$

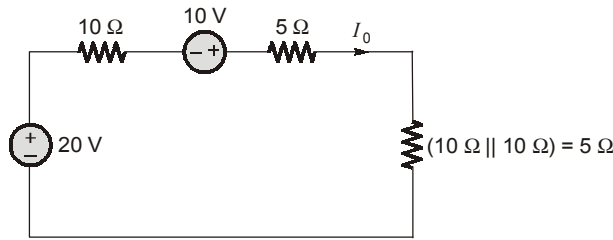4. (b)

Using the source transformation technique, the given circuit can be reduced as shown below:




$$I_0 = \frac{20V + 10V}{10\Omega + 5\Omega + 5\Omega} = 1.5 \text{ A}$$

$$I_x = \frac{I_0}{2} = 0.75 \text{ A}$$

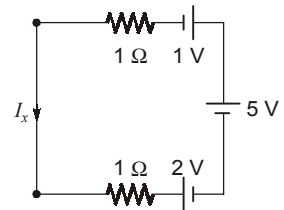5. (a)

Using the source transformation technique, the given circuit can be reduced as shown:

$$I_x = \frac{-1V + 5V - 2V}{1\Omega + 1\Omega} = \frac{2V}{2\Omega} = 1 \text{ A}$$



6. (b)

Resonance frequency, $f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(10 \times 10^{-3})(10^{-6})}} \text{ Hz} = \frac{10}{2\pi} \text{ kHz} = 1.6 \text{ kHz}$

7. (c)

Since total power absorbed or delivered in the circuit

$$\Rightarrow \Sigma P = 0;$$


then $-30 \times 6 + 6 \times 12 + 3 V_0 + 28 + 28 \times 2 - 3 \times 10 = 0$

$$72 + 84 + 3 V_0 = 210;$$

or $3 V_0 = 54$

$$\Rightarrow V_0 = 18 \text{ V}$$

8. (a)

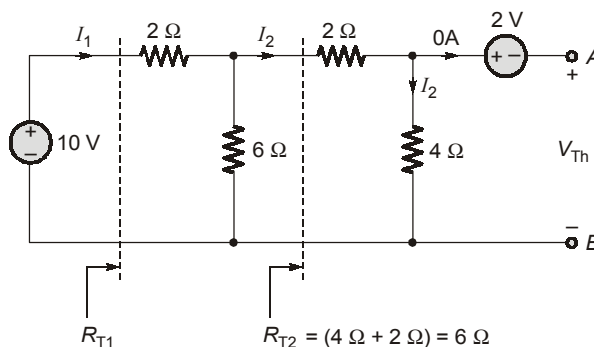

$$R_{T1} = 2\Omega + (6\Omega \parallel R_{T2}) = 5\Omega$$

$$I_1 = \frac{10}{R_{T1}} = 2 \text{ A}$$


$$I_2 = I_1 \times \frac{6\Omega}{R_{T2} + 6\Omega} = \frac{I_1}{2} = 1 \text{ A}$$

$$V_{Th} = (4\Omega) I_2 - 2V = 4V - 2V = 2V$$

9. (b)

Maximum power will be transferred to R_L in the given circuit, when $R_L = R_{Th}$.


To determine R_{Th} :

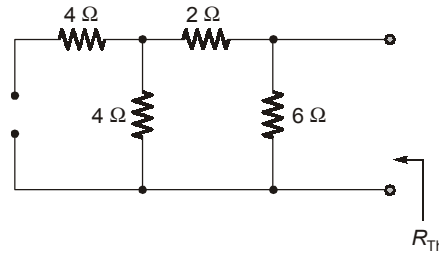

$$R_{Th} = (4 \Omega + 2 \Omega) \parallel 6 \Omega = 6 \Omega + 6 \Omega = 3 \Omega$$

10. (a)

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0 \Rightarrow \text{port - 1 is open circuited}}$$

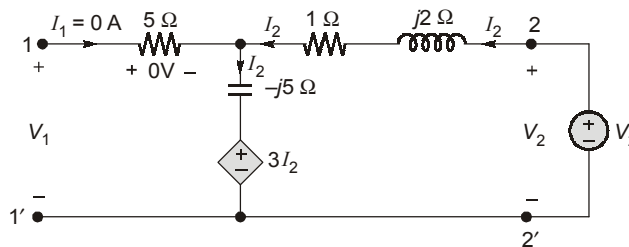

When port-1 is open circuited, i.e. $I_1 = 0$,

$$V_1 = (-j5 \Omega)I_2 + 3I_2 = (3 - j5)I_2$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = (3 - j5)\Omega$$

11. (c)

$$R_{AB} = \frac{V_0}{I_0}$$

By applying KCL at node C, we get,


$$I_0 = \frac{4V_x}{8\Omega} + \frac{V_x}{6\Omega} = \frac{4V_x}{6\Omega} \quad \dots(i)$$

Also, $4V_x$ can be written as, $4V_x = V_0 - I_0(6\Omega) \quad \dots(ii)$


From the equation (i) and (ii), $I_0 = \frac{V_0 - I_0(6\Omega)}{6\Omega}$

$$2I_0 = \frac{V_0}{6\Omega}$$

$$R_{AB} = \frac{V_0}{I_0} = 12 \Omega$$

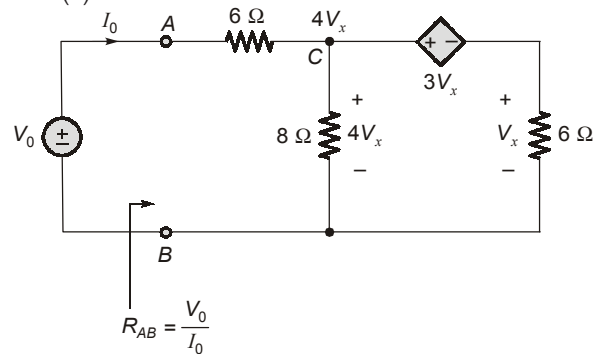


12 (a)

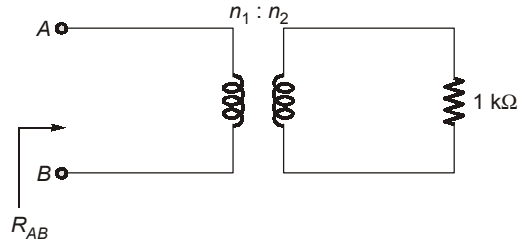

$$R_{AB} = \left(\frac{n_1}{n_2}\right)^2 (1 \text{ k}\Omega) = \left(\frac{1}{5}\right)^2 (1000)\Omega = 40 \Omega$$

13. (a)

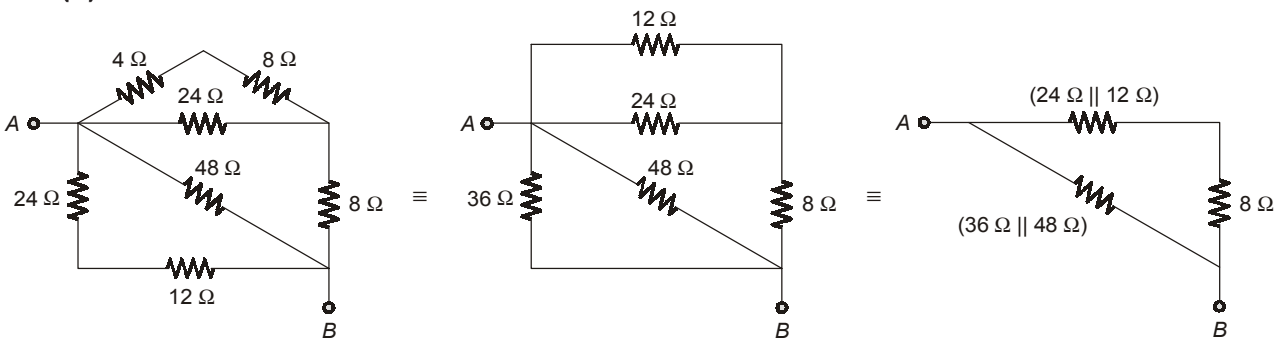

$$\begin{aligned} R_{AB} &= [(24 \Omega \parallel 12 \Omega) + 8 \Omega] \parallel (36 \Omega \parallel 48 \Omega) \\ &= (8 \Omega + 8 \Omega) \parallel (36 \Omega \parallel 48 \Omega) \\ &= 16 \Omega \parallel 36 \Omega \parallel 48 \Omega = 12 \Omega \parallel 36 \Omega = 9 \Omega \end{aligned}$$

14. (d)

Let the current be shown in the figure

$$i = 0.6 V_0 + 12$$

$$i = i_1 + i_2$$

Since branches *ab* and *ac* have identical resistance,

Hence,

$$i_1 = i_2$$

and

$$i = 12 + 0.6 V_0 = 2i_1 = 2i_2$$

$$V_0 = (i_1 \times 2) \text{ V}$$

$$i = 2i_1, \text{ we write}$$

$$i_1 = \frac{i}{2} = \frac{1}{2}(12 + 0.6V_0)$$

and

$$V_0 = i_1 \times 2 = i_1 + 0.6 V_0$$

$$V_0 = i_1 \times 2 = 12 + 0.6 V_0$$

Equation resistance across *xe* node is:

$$R_{xe} = (5 \parallel 5) + 4 + 1 = 7.5 \Omega$$

$$\begin{aligned} V_{xe} &= 0.6 V_0 \times 7.5 + 12 \times 7.5 \\ &= 18 \times 7.5 + 12 \times 7.5 \\ &= 225 \text{ V} \end{aligned}$$

15. (d)

$$I_0 = \frac{I_m}{\sqrt{2}}$$

$$I_m = \frac{V_0}{\omega_0 L}$$

When,

$$v(t) = -V_0 \sin(\omega_0 t) + 4V_0 \sin(4\omega_0 t)$$


$$i(t) = -\frac{V_0 \sin(\omega_0 t)}{j\omega_0 L} + \frac{4V_0 \sin(4\omega_0 t)}{j4\omega_0 L} = j[I_m \sin(\omega_0 t) - I_m \sin(4\omega_0 t)]$$

Reading of meter = overall RMS value of $i(t)$

$$= \sqrt{\left(\frac{I_m}{\sqrt{2}}\right)^2 + \left(\frac{I_m}{\sqrt{2}}\right)^2} = I_m = \sqrt{2} I_0$$

16. (b)

Network 'N' can be replaced as

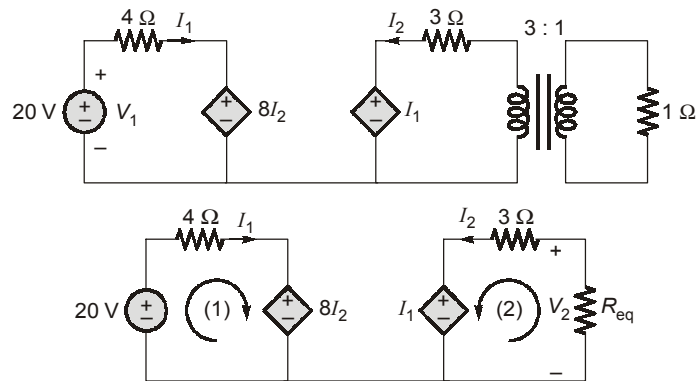

$$R_{eq} = (1) \times \left(\frac{3}{1}\right)^2 = 9 \Omega$$

Applying KVL at loop (1)

$$20 = 4I_1 + 8I_2$$

also

$$V_2 = -9I_2 = I_1 + 3I_2$$

⇒

$$I_1 = -12I_2$$

$$20 = 4(-12I_2) + 8I_2$$


$$20 = -40I_2$$

⇒

$$I_2 = -0.5 \text{ A}$$

$$I_1 = -12(-0.5) = 6 \text{ A}$$

Now,

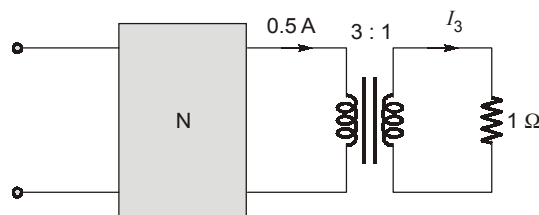

$$\frac{I_{\text{primary}}}{I_{\text{secondary}}} = \frac{1}{3}$$


⇒

$$3I_{\text{primary}} = I_{\text{secondary}}$$

$$\begin{aligned} 3(-I_2) &= I_3 \\ \Rightarrow I_3 &= 1.5 \text{ A} \\ \text{Power delivered to } 1 \Omega &= (I_3)^2 \times R_L = (1.5)^2 \times 1 \\ &= 2.25 \text{ Watts} \end{aligned}$$

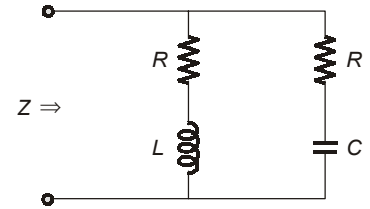17. (a)

$$\begin{aligned} Y &= Y_1 + Y_2 \\ Y &= \frac{1}{R + jX_L} + \frac{1}{R - jX_C} \\ Y &= \frac{R - jX_L}{(R^2 + X_L^2)} + \frac{(R + jX_C)}{(R^2 + X_C^2)} \\ \text{Im}(Y) &= \frac{-X_L(R^2 + X_C^2) + X_C(R^2 + X_L^2)}{(R^2 + X_L^2)(R^2 + X_C^2)} \end{aligned}$$




For 'Z' to be purely resistive
also $\text{Im}(Y) = 0$

$$\begin{aligned} \Rightarrow X_L(R^2 + X_C^2) &= X_C(R^2 + X_L^2) \\ R^2 X_L + X_C^2 X_L &= R^2 X_C + X_L^2 X_C \\ R^2(X_L - X_C) &= X_L X_C(X_L - X_C) \\ R^2 &= X_L X_C = \omega L \times \frac{1}{\omega C} = \frac{L}{C} \end{aligned}$$

18. (a)

Maximum power will be delivered to R_L , when $R_L = R_{Th}$.


To determine R_{Th} :

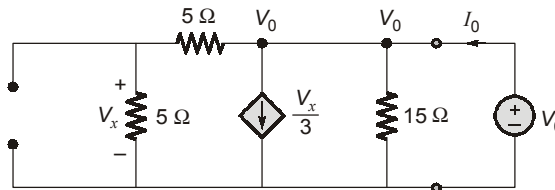


$$\begin{aligned} I_0 &= \frac{V_0}{15\Omega} + \frac{V_x}{3} + \frac{V_0}{10\Omega} \\ V_x &= \frac{V_0}{2} \\ \text{So, } I_0 &= \frac{V_0}{15\Omega} + \frac{V_0}{6\Omega} + \frac{V_0}{10\Omega} \\ R_{Th} &= \frac{V_0}{I_0} = (15 \Omega \parallel 6 \Omega \parallel 10 \Omega) = 3 \Omega \end{aligned}$$

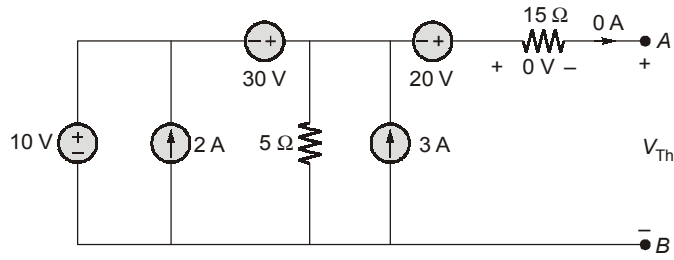19. (a)

It is very easy to calculate Thevenin's equivalent rather than Norton's equivalent for the given circuit.


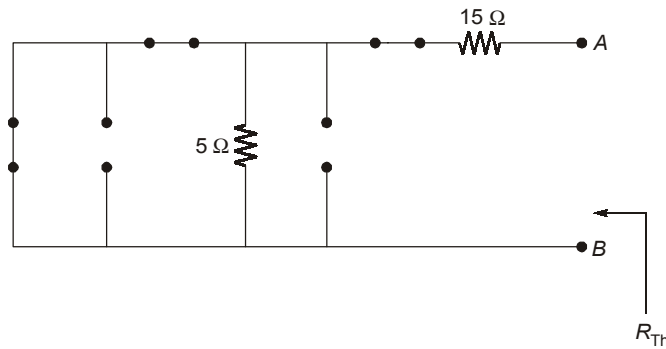
$$V_{Th} = 0\text{ V} + 20\text{ V} + 30\text{ V} + 10\text{ V} = 60\text{ V}$$



$$R_{Th} = 15\ \Omega + (5\ \Omega \parallel 0\ \Omega) = 15\ \Omega$$


So,

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{60\text{ V}}{15\ \Omega} = 4\text{ A}$$

$$R_N = R_{Th} = 15\ \Omega$$

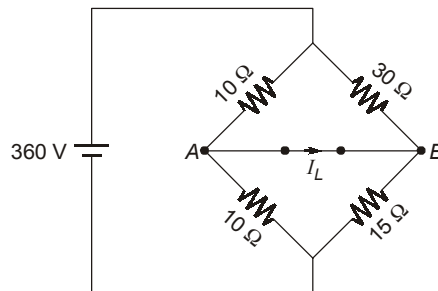
20. (b)

In the steady state condition, for DC excitation, Inductor acts as short circuit.



It is easy to calculate I_L by calculating Thevening equivalent across the terminals A and B.

To determine V_{Th} :

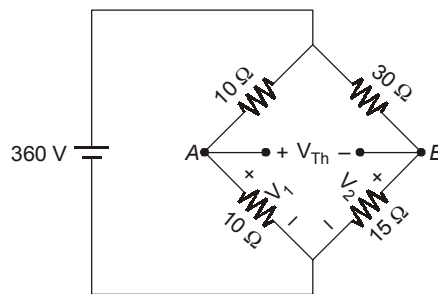

$$V_{Th} = V_1 - V_2$$


$$V_1 = \frac{10}{10+10} \times 360 \text{ V} = 180 \text{ V}$$

$$V_2 = \frac{15}{15+30} \times 360 \text{ V} = 120 \text{ V}$$

So,

$$V_{Th} = 180 \text{ V} - 120 \text{ V} = 60 \text{ V}$$

To determine R_{Th} :

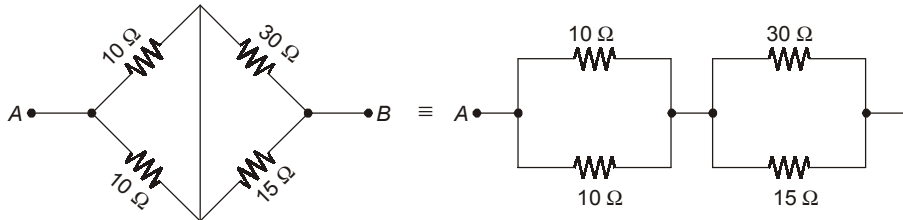

$$R_{Th} = (10 \Omega \parallel 10 \Omega) + (30 \Omega \parallel 15 \Omega) = 15 \Omega$$


So,

$$I_L = \frac{V_{Th}}{R_{Th}} = 4 \text{ A}$$

Steady state energy stored in the inductor is,

$$W_L = \frac{1}{2} L I_L^2 = \frac{1}{2} (2) (4)^2 \text{ J} = 16 \text{ J}$$

21. (a)

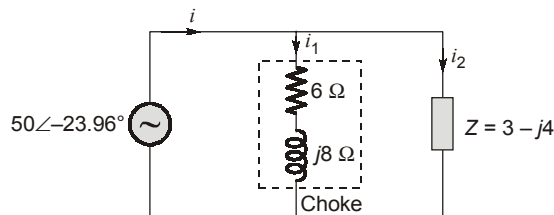

Here, applying KCL

$$i(t) = i_1(t) + i_2(t)$$

$$= \frac{V_1}{6 + j8} + \frac{V_1}{3 - j4} \Rightarrow V_1 \left(\frac{3 - j4 + 6 + j8}{2(3 + j4)(3 - j4)} \right)$$

$$= \frac{V_1(9 + j4)}{2 \times 25} \Rightarrow \frac{50 \angle -23.96^\circ \times \sqrt{97} \angle 23.96^\circ}{50} \text{ A}$$


$$= \sqrt{97} \text{ A}$$

$$= 9.85 \text{ A}$$

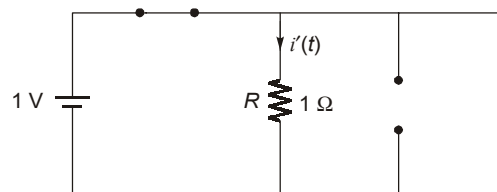22. (a)


The given circuit has two sources with different frequencies, hence we have to use superposition theorem.

When 1 V DC source is acting alone (in steady state):



$$i'(t) = \frac{1\text{V}}{1\Omega} = 1\text{A}$$

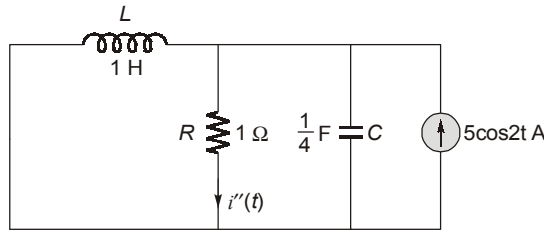When $5\cos 2t$ A AC source is acting alone (in steady state):



The circuit looking like a parallel RLC circuit.

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2 \text{ rad/sec}$$

And the source is also working with 2 rad/sec. So, the circuit will be in resonance.

When the parallel RLC circuit is in resonance, the total source current flows through the resistor.

So, $i''(t) = 5\cos 2t$ A

When both the sources are acting simultaneously,

$$i(t) = i'(t) + i''(t) = (1 + 5\cos 2t) \text{ A}$$

23. (d)

It is clear from the given circuit that, the current flowing through 1Ω resistor due to either 5 V source alone or 30 A source alone is in the same direction.

So,
$$I_{1\Omega} = I'_{1\Omega} + I''_{1\Omega}$$

$$I'_{1\Omega} = \sqrt{\frac{1\text{W}}{1\Omega}} = 1\text{A}$$


$$I''_{1\Omega} = \sqrt{\frac{576\text{W}}{1\Omega}} = 24\text{A}$$

$$I_{1\Omega} = 24 \text{ A} + 1 \text{ A} = 25 \text{ A}$$

$$P_{1\Omega} = (25 \text{ A})^2 (1 \Omega) = 625 \text{ W}$$

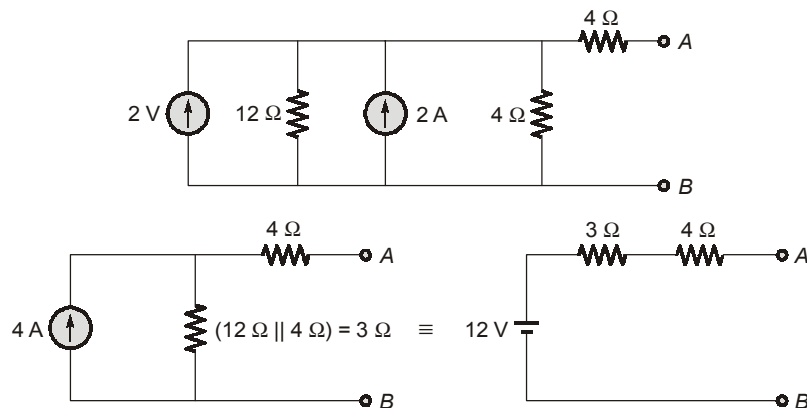24. (b)

By applying source transformation technique, we get,



So,
and

$$V_x = 12 \text{ V}$$

$$R_x = 7 \Omega$$

25. (d)

The voltage across inductor is,

$$V_L = L \frac{di_L}{dt} = L \frac{di_s(t)}{dt}$$

Current across capacitor is given by,


$$i_c = C \frac{dv_c}{dt}$$

$$v_c = 3v_L$$


$$\Rightarrow i_c = 3C \frac{dv_L}{dt} = 3C.L \frac{d^2 i_s(t)}{dt^2} = -9.6 \sin 4t \text{ A}$$

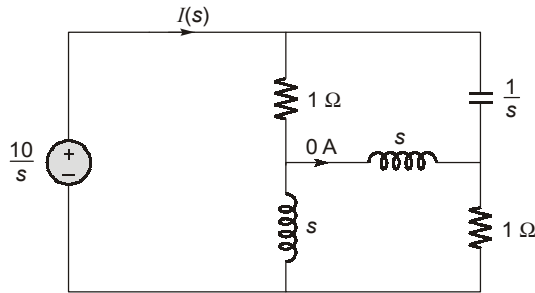26. (d)

By considering the given circuit in Laplace domain, we get,



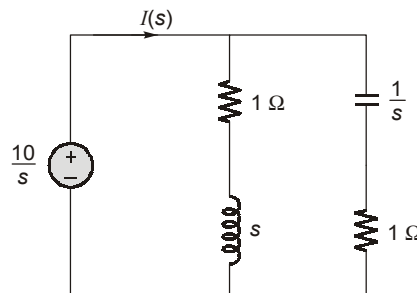Bridge is balanced, hence the circuit can be reduced as,



$$Z(s) = (1+s) \parallel \left(1 + \frac{1}{s} \right) = \frac{(1+s) \left(1 + \frac{1}{s} \right)}{1+s+1+\frac{1}{s}} = \frac{(s+1)^2}{s^2+2s+1} = 1$$

So,
$$I(s) = \frac{10/s}{Z(s)} = \frac{10}{s}$$

By taking inverse Laplace transform, we get,

$$i(t) = 10 u(t) \text{ A}$$

27. (a)

Applying KVL,

$$V_{xy} - j\omega L_2 i_2 - j\omega M i_1 = 0$$

as
$$i_2 = 0$$

then,
$$V_{xy} - j\omega M i_1 = 0$$

...(i)

applying KVL in loop 1


$$V_1 = j\omega L_1 i_1$$

...(ii)

Using value of i_1 from equation (ii) in equation (i)

$$V_{xy} = j\omega M \left[\frac{V_1}{j\omega L_1} \right] = \frac{M V_1}{L_1}$$

28. (a)
For the circuit

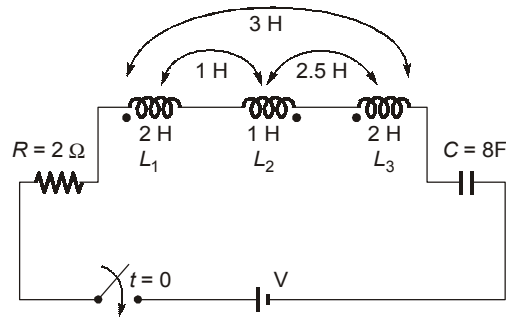

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$$

$$L_1 = 2 \text{ H}$$

$$L_2 = 1 \text{ H}$$

$$L_3 = 2 \text{ H}$$

$$M_{12} = 1 \text{ H}$$

$$M_{23} = 2.5 \text{ H}$$

$$M_{13} = 3 \text{ H}$$

$$L_{eq} = 2 + 1 + 2 - 2 - 5 + 6$$

$$= 11 - 7$$

$$= 4 \text{ H}$$

$$C = 8 \text{ F}$$

$$R = 2 \Omega$$

Note : M_{12} , M_{23} is negative, because both L_1 , L_2 and L_2 , L_3 opposes the flux of respective loops.

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{2}{2} \sqrt{\frac{8}{4}} = \sqrt{2} = 1.414$$

Thus, the given circuit is overdamped.

29. (b)
For $t > 0$, the given circuit acts like a series RLC circuit,

$$L = 40 \text{ H}$$

and $C = 10 \mu\text{F}$

Damping ratio,
$$\zeta = \frac{1}{2Q}$$

Quality factor,
$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (\text{for series RLC circuit})$$

So,
$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$\zeta \geq 1$ for oscillation free response.

So,
$$\frac{R}{2} \sqrt{\frac{C}{L}} \geq 1$$

$$R \geq 2 \sqrt{\frac{L}{C}} = 2 \sqrt{\frac{40}{10} \times 10^6}$$

$$R \geq 4 \text{ k}\Omega$$
$$R_{\min} \geq 4 \text{ k}\Omega$$

30. (c)

In a series RL circuit,

$$v_L(t) = V_s e^{-t/\tau} u(t)$$
$$v_R(t) = V_s (1 - e^{-t/\tau}) u(t)$$

$$\tau = \frac{L}{R} = \frac{7\text{H}}{2\Omega} = 3.5 \text{ sec}$$

$$V_s e^{-t/\tau} = V_s (1 - e^{-t/\tau})$$
$$2e^{-t/\tau} = 1$$

$$-\frac{t}{\tau} = \ln(1/2)$$

$$t = \tau \ln(2) = 2.426 \text{ sec}$$

■■■■