

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Noida | Bhopal | Hyderabad | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

CLASS TEST 2019-2020

ELECTRONICS ENGINEERING

Date of Test : 29/07/2019**ANSWER KEY ➤ Measurement**

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (d) | 7. (b) | 13. (b) | 19. (a) | 25. (c) |
| 2. (a) | 8. (d) | 14. (c) | 20. (b) | 26. (b) |
| 3. (b) | 9. (a) | 15. (d) | 21. (b) | 27. (b) |
| 4. (b) | 10. (b) | 16. (d) | 22. (a) | 28. (a) |
| 5. (c) | 11. (a) | 17. (d) | 23. (c) | 29. (c) |
| 6. (d) | 12. (a) | 18. (d) | 24. (b) | 30. (b) |

Detailed Explanations

1. (d)

Moving-iron voltmeter reads RMS value,

$$V = \sqrt{V_{1\text{rms}}^2 + V_{2\text{rms}}^2}$$

$$V_{1\text{rms}} = 5 \text{ V}$$

and

$$V_{2\text{rms}} = \frac{10}{\sqrt{2}} \text{ V}$$

$$\therefore V = \sqrt{5^2 + \left(\frac{10}{\sqrt{2}}\right)^2} = \sqrt{75} \text{ V}$$

2. (a)

At balanced condition,

$$\frac{1000}{R_x + j\omega L_x} = \frac{R_s}{(j\omega R_s C_s + 1) 1000}$$

or

$$10^6 (j\omega R_s C_s + 1) = R_s (R_x + j\omega L_x)$$

Equating real and imaginary terms,

$$10^6 = R_s R_x$$

$$\Rightarrow R_x = \frac{10^6}{R_s} = 1000 \Omega$$

and

$$10^6 C_s = L_x$$

$$\Rightarrow L_x = 10^6 \times 0.5 \times 10^{-6} = 0.5 \text{ H}$$

3. (b)

Because of over voltage there are chances of insulation breakdown.

4. (b)

$$S_E = \frac{l \cdot L}{2dV_a} = \frac{2 \times 20}{2 \times 0.2 \times 2000} = 0.05 \text{ cm/V}$$

5. (c)

$$f \propto \frac{1}{\sqrt{C}}$$

$$\Rightarrow \frac{f_1}{f_2} = \sqrt{\frac{C_2 + C_d}{C_1 + C_d}}$$

Where, C_d = self capacitance of the coil

$$\frac{1 \times 10^6}{500 \times 10^3} = \sqrt{\frac{250 + C_d}{40 + C_d}} = 2$$

$$\Rightarrow \frac{250 + C_d}{40 + C_d} = 4$$

$$\Rightarrow 250 + C_d = 160 + 4 C_d$$

$$\Rightarrow 3 C_d = 90$$

$$\Rightarrow C_d = 30 \text{ pF}$$

6. (d)

Probable error,

$$\sigma = \sqrt{\left(\frac{\partial I}{\partial I_1}\right)^2 \sigma_1^2 + \left(\frac{\partial I}{\partial I_2}\right)^2 \sigma_2^2}$$

Here,

$$I = I_1 + I_2$$

So,

$$\frac{\partial I}{\partial I_1} = \frac{\partial I}{\partial I_2} = 1$$

and

$$\sigma = \sqrt{(1)^2(1)^2 + (1)^2(2)^2} = 2.24 \text{ A}$$

Therefore,

$$I = 300 \pm 2.24 \text{ A}$$

7. (b)

Deflecting torque in PMMC ;

$$T_d \propto BI$$

Given,

$$B_2 = 2B_1$$

and

$$I_2 = \frac{I_1}{2}$$

∴

$$T_{d2} \propto B_2 I_2 \propto (2B_1) \left(\frac{I_1}{2}\right) \propto B_1 I_1$$

Thus,

$$T_{d2} = T_{d1}$$

So, same deflection (90°) is produced.

8. (d)

Wien bridge is balanced only for pure sinusoidal input supply and no harmonics in supply. So, no null indication is possible.

9. (a)

Heaviside Campbell bridge method is commonly used for finding mutual inductance.

10. (b)

For the d.c. potentiometer, we have:

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

or, emf of the test cell,

$$E_2 = E_1 \cdot \frac{l_2}{l_1} = (1.18) \times \frac{680}{600} \approx 1.34 \text{ V}$$

11. (a)**Method-1**

Given that,

$$V = 230 \text{ Volt},$$

$$I = 5 \text{ A}, \cos \phi = 0.1$$

$$R_P = 10 \text{ k}\Omega, L_P = 100 \text{ mH} = 0.1 \text{ H}$$

$$\therefore \beta = \tan^{-1} \left(\frac{\omega L_P}{R_P} \right) \approx 0.18^\circ$$

$$\text{And, } \phi = \cos^{-1}[0.1] = 84.26^\circ$$

$$\text{Now, True power} = P_T = VI \cos \phi = 115 \text{ watt}$$

Reading of wattmeter for lagging p.f.,

$$P_{\text{Read}} = VI \cos(\phi - \beta) \cos \beta = 118.6 \text{ watt}$$

$$\therefore \% \text{ error} = \frac{118.6 - 115.0}{115.0} \times 100 = 3.13\%$$

Method-2

Solution can be given directly from the equation given below after finding “ β ” as,

$$\% \text{ error} = \tan \phi \cdot \tan \beta \times 100 = \tan(84.26^\circ) \cdot \tan(0.18^\circ) \times 100 = 3.13\%$$

12. (a)

$$S_{dc} = \frac{1}{I_{fs}} = \frac{1}{1 \times 10^{-3}} = 1000 \Omega/V$$

$$R_m = S_{dc} V = 1000 \times 1 = 1000 \Omega$$

$$\therefore R_s = 0.45 \times 1000 \times 10 - 1000$$

$$R_s = 3.5 \text{ k}\Omega$$

13. (b)

$$\text{The limiting error to } 80 \text{ V} = \frac{0.02 \times 100}{80} \times 100 = 2.5\%$$

$$\text{The limiting error at } 80 \text{ mA} = \frac{0.02 \times 150}{80} \times 100 = 3.75\%$$

The limiting error for power calculation

$$= 2.5\% + 3.75\% = 6.25\%$$

14. (c)

Effective value of input wave (thermocouple based instrument reads rms value)

$$= \sqrt{I_1^2 + I_H^2} = \sqrt{I_1^2 + \left(\frac{I_1}{5}\right)^2} = \sqrt{\frac{26}{25} I_1^2} = \sqrt{1.04 I_1^2} = 1.0198 I_1$$

$$\approx 1.02 I_1 = I_1 + 0.02 I_1$$

Hence, error = 2%

15. (d)

At balance condition,

$$Z_1 Z_x = Z_2 Z_3$$

i.e., $R_1 \left(R_x - \frac{j}{\omega C_x} \right) = R_2 \left(R_3 - \frac{j}{\omega C_3} \right)$

$$\therefore R_1 R_x - \frac{j R_1}{\omega C_x} = R_2 R_3 - \frac{j R_2}{\omega C_3}$$

Equating the real and the imaginary parts,

$$R_1 R_x = R_2 R_3$$

$$\Rightarrow R_x = \frac{R_2 R_3}{R_1} = \frac{30 \times 25}{20} = 37.5 \Omega$$

and $\frac{R_1}{\omega C_x} = \frac{R_2}{\omega C_3}$

$$\Rightarrow C_x = \frac{C_3 R_1}{R_2} = \frac{10 \times 20}{30} = 20/3 \text{ pF}$$

16. (d)

Total power in the circuit

$$P = W_1 + W_2 = 500 \text{ W} + (-100) \text{ W} = 400 \text{ W}$$

Power factor of the circuit,

$$\begin{aligned}\cos \phi &= \cos \left[\tan^{-1} \left\{ \left(\frac{W_1 - W_2}{W_1 + W_2} \right) \cdot \sqrt{3} \right\} \right] = \cos \left(\tan^{-1} \left[\frac{0.5 - (-0.1)}{0.5 + (-0.1)} \right] \cdot \sqrt{3} \right) \\ &= \cos (\tan^{-1} (1.5 \times \sqrt{3})) = 0.359\end{aligned}$$

17. (d)

Rate of change of inductance with deflection is,

$$\frac{dL}{d\theta} = \frac{d}{d\theta} (10 + 5\theta - \theta^2) = (5 - 2\theta) \mu\text{H}/\text{rad}$$

The deflection is,

$$\theta = \frac{1}{2} \frac{I^2}{K} \frac{dL}{d\theta}$$

or,

$$\theta = \frac{1}{2} \times \frac{(5)^2}{12 \times 10^{-6}} \times (5 - 2\theta) \times 10^{-6}$$

On solving, we get:

$$\theta = 1.69 \text{ rad} = 1.69 \times 180/\pi \text{ degree} = 96.8^\circ$$

18. (d)

$$v = V_1 \sin \omega t + V_2 \sin(2\omega t + \theta_1) + V_3 \sin(3\omega t + \theta_2) + \dots$$

$$i = I_1 \sin \omega t + I_2 \sin 2\omega t + I_3 \sin 3\omega t + \dots$$

So,

$$P = v \cdot i = \frac{1}{2} V_1 I_1 + \frac{1}{2} V_2 I_2 \cos \theta_1 + \frac{1}{2} V_3 I_3 \cos \theta_2 + \dots$$

Here,

$$v = 100 \sin \omega t + 60 \cos(3\omega t - 30^\circ) + 40 \sin(5\omega t + 45^\circ) \text{ V}$$

$$i = 8 \sin \omega t + 6 \sin(5\omega t + 120^\circ) \text{ A}$$

So, power

$$P_T = \frac{1}{2} \times 100 \times 8 + \frac{1}{2} \times 60 \times 0 + \frac{1}{2} \times 40 \times 6 \cos(120^\circ - 45^\circ) \text{ W} = 431 \text{ Watt}$$

19. (a)

$$V_{\text{true}} = 400 \times \frac{200}{400} = 200 \text{ V} = V_t$$

$$\text{Resistance of voltmeter} = 20 \frac{\text{k}\Omega}{\text{V}} \times 10 \text{ V} = 200 \text{ k}\Omega$$

$$\therefore V_{\text{measured}} = 400 \times \frac{100}{300} = 133.33 \text{ V} = V_m$$

$$\text{Thus, } \% \text{ error} = \frac{V_m - V_t}{V_t} \times 100 = -33.335\% \approx -33.33\%$$

20. (b)

The magnitude of limiting error for the voltmeter

$$\epsilon_V = 0.01 \times 150 = 1.5 \text{ V}$$

$$\text{the limiting error at } 100 \text{ V} = \frac{1.5}{100} \times 100 = 1.5\%$$

The magnitude of the limiting error for the ammeter

$$\epsilon_A = 0.01 \times 100 = 1 \text{ mA}$$

$$\text{The limiting error at } 55 \text{ mA} = \frac{1}{55} \times 100 = 1.8\%$$

The limiting error for the power, $P = VI$

$$= \text{sum of the individual limiting error} = (1.5 + 1.8)\% = 3.3\%$$

21. (b)

When op-amps are used as comparators in ADC, this means ADC is flash type ADC.

So, number of comparators required for n -bit ADC is $2^n - 1$.


$$= 2^5 - 1 = 31 \text{ comparators}$$

22. (a)

The overall uncertainty

$$\omega_x = \sqrt{\omega_{x1}^2 + \omega_{x2}^2 + \omega_{x3}^2} = \sqrt{1^2 + 1^2 + 3^2} = \sqrt{11}\%$$

23. (c)

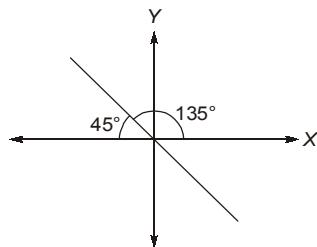

It means voltages are 180° in phase.

$$\therefore V_y = 2 \sin(\omega t + 180^\circ) \\ V_y = -2 \sin \omega t$$

24. (b)

$$P = \frac{1}{2} (V_1 I_1 \cos \phi_1 + V_3 I_3 \cos \phi_3) = \frac{1}{2} (40 \times 5 \cos 75^\circ + 60 \times 3 \cos 15^\circ) \\ = 112.8 \text{ W}$$

25. (c)

$$\text{Resolution} = 0.01\% = \frac{0.01}{100} = \frac{1}{10000}$$

$$\frac{1}{2^n} = \frac{1}{10000}$$

\therefore Minimum number of bits, $n = 14$ as $2^{14} = 16384$

(we cannot choose $n = 13$ as $2^{13} = 8192$. Which is less than 10000)

$$\text{Analog value of LSB} = \frac{1}{2^n} \times 10 = \frac{1}{2^{14}} \times 10 = \frac{1}{16384} \times 10 \text{ V} = 610.4 \mu\text{V}$$

26. (b)

$$\sin \theta = \frac{K}{K_g} \cdot V$$

$$\begin{aligned} \theta_1 &= 90^\circ, V = 200 \text{ V} \\ \Rightarrow \frac{K}{K_g} &= \frac{1}{200} \\ \sin \theta_2 &= \frac{1}{200} \times 100 = \frac{1}{2} \\ \Rightarrow \theta_2 &= 30^\circ \end{aligned}$$

27. (b)

instantaneous value of voltage across 1 mH inductor is

$$\begin{aligned} V_L &= L \frac{dI}{dt} = 1 \times 10^{-3} \frac{d}{dt} (0.5 + 0.3 \sin \omega t - 0.2 \sin 2\omega t) \\ &= 1 \times 10^{-3} \times \omega (0.3 \cos \omega t - 0.4 \cos 2\omega t) \end{aligned}$$

Put, $\omega = 10^6$ rad/sec then,

$$V_L = 300 \cos \omega t - 400 \cos 2\omega t$$

Hence, reading of electrostatic voltmeter across 1 mH inductor is

$$\begin{aligned} V_L &= \sqrt{\left(\frac{300}{\sqrt{2}}\right)^2 + \left(\frac{400}{\sqrt{2}}\right)^2} \\ V_L &= 354 \text{ V} \end{aligned}$$

28. (a)

$$\begin{aligned} \sin \phi &= \frac{Y_1}{Y_2} = \frac{2}{4} = \frac{1}{2} \\ \phi &= 30^\circ \end{aligned}$$

29. (c)

from the modified De-Sauty bridge

$$\begin{aligned} \frac{R_2}{R_3} &= \frac{r_1}{R_4 + r_4} = \frac{C_4}{C_1} \\ r_1 &= \frac{R_2(R_4 + r_4)}{R_3} = \frac{2000 \times (4.8 + 0.4)}{2850} = 3.65 \Omega \end{aligned}$$

$$\text{and, } C_1 = \frac{R_3 C_4}{R_2} = \frac{2850 \times 0.5 \times 10^{-6}}{2000} = 0.7125 \mu\text{F}$$

$$\begin{aligned} \text{and } \tan \delta_1 &= \omega C_1 r_1 = 2\pi \times 450 \times 0.7125 \times 10^{-6} \times 3.65 = 7353.1 \times 10^{-6} = 0.007351 \\ \delta_1 &= \tan^{-1}(0.007351) = 0.42^\circ \end{aligned}$$

30. (b)

In parallel voltage is same.

If R_1 is resistance of 1st ammeter and R_2 is resistance of 2nd ammeter.

Hence,

$$R_1 = \frac{V}{I_{fsd_1}} = \frac{V}{1 \text{ mA}}$$

$$R_2 = \frac{V}{I_{fsd_2}} = \frac{V}{10 \text{ mA}}$$

$$\therefore \frac{R_1}{R_2} = \frac{10}{1}$$

