

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Lucknow | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

NETWORK THEORY


EC+EE**Date of Test : 14/02/2023****ANSWER KEY ➤**

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (c) | 7. (c) | 13. (a) | 19. (b) | 25. (c) |
| 2. (b) | 8. (a) | 14. (b) | 20. (c) | 26. (a) |
| 3. (a) | 9. (b) | 15. (b) | 21. (c) | 27. (b) |
| 4. (a) | 10. (c) | 16. (b) | 22. (a) | 28. (c) |
| 5. (c) | 11. (b) | 17. (a) | 23. (d) | 29. (d) |
| 6. (a) | 12. (d) | 18. (b) | 24. (b) | 30. (a) |

DETAILED EXPLANATIONS

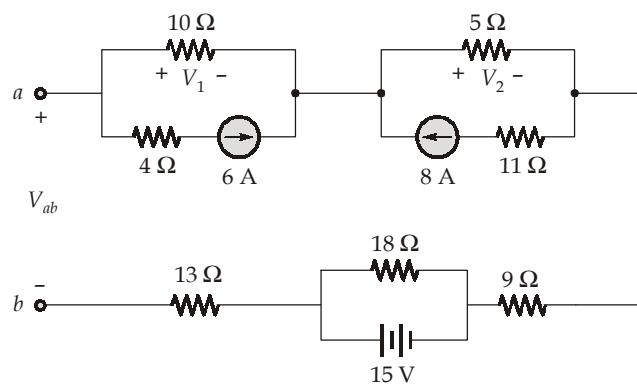1. (c)

Since terminal a and b forms is open circuit thus, no current flows through circuit is zero, thus the current only flows into the loops.




$$V_{ab} = V_1 + V_2 - 15 \text{ V}$$

$$\therefore V_{ab} = (-6 \text{ A}) (10 \Omega) + (8 \text{ A} \times 5 \Omega) - 15$$

$$V_{ab} = -35 \text{ V}$$

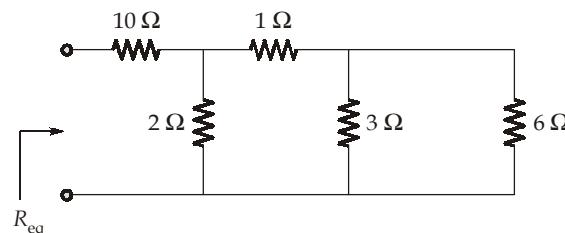2. (b)

The resistance $6 \Omega \parallel 3 \Omega$ and $12 \Omega \parallel 4 \Omega$ also 1Ω is in series with 5Ω , thus, the circuit can be redrawn as



$$\therefore R_{eq} = 10 \Omega + 2 \Omega \parallel (1 + 3 \Omega \parallel 6 \Omega)$$

$$R_{eq} = 11.2 \Omega$$

3. (a)

$$Z_L = j\omega L = j\Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(1)(0.05)} = -j20 \Omega$$

$$\therefore Z_{eq} = j + 2 \parallel (-j20) = 1.98 + j0.802 \Omega$$

and $Z_L(5j) = 5j \Omega$

$$Z_C(5j) = -j4 \Omega$$


$$\therefore Z_{eq}(j5) = j5 + 2 \parallel (-j4) = 1.6 + j4.2 \Omega$$

Now,

$$I(j\omega) \propto \frac{1}{Z(j\omega)}$$

$$\therefore \left| \frac{I_o(j)}{I_o(j5)} \right| = \frac{|Z(j5)|}{|Z(j)|} = \frac{|1.6 + j4.2|}{|1.98 + j0.802|} = 2.104$$

4. (a)

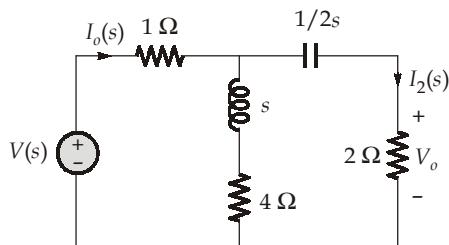

Now, applying current division rule, we get,

$$I_2(s) = \frac{(s+4)I_o(s)}{s+4+2+\frac{1}{2s}}$$

$$I_2(s) = \frac{2s(s+4)}{2s^2+12s+1} \cdot I_o(s)$$

$$V_o(s) = 2I_2(s) = \frac{4s(s+4)}{2s^2+12s+1} I_o(s)$$

$$\frac{V_o(s)}{I_o(s)} = \frac{4s(s+4)}{2s^2+12s+1}$$

5. (c)


$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)] e^{-t/\tau}$$

where, $\tau = RC = 4 \times 2 = 8$, $v(0) = 4$ V and $v_c(\infty) = 20$ V

$$\therefore v_c(t) = 20 + (4 - 20)e^{-t/8}$$

$$v_c(t) = 20 - 16 e^{-t/8} \text{ V}$$

6. (a)

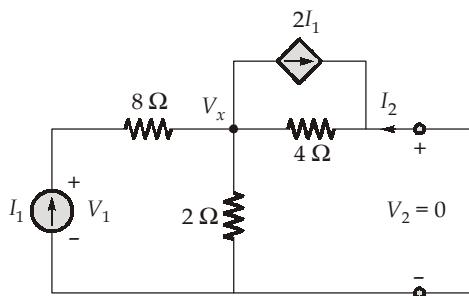

$$I_1 = \frac{V_x}{2} + \frac{V_x}{4} + 2I_1$$

$$-I_1 = 0.75V_x \quad \dots (i)$$

$$I_2 = -\frac{V_x}{4} - 2I_1 = -\frac{V_x}{4} + 1.5V_x = 1.25V_x$$

Now,

$$V_1 = 8I_1 + V_1$$


$$V_1 = -6V_x + V_x = -5V_x$$

$$\therefore \frac{I_2}{V_1} = -\frac{1.25}{5} = -0.25 \text{ S}$$

7. (c)

$$R_L = |Z_s^*| = |5 - j10| = \sqrt{5^2 + 10^2} = 11.18 \Omega$$

8. (a)

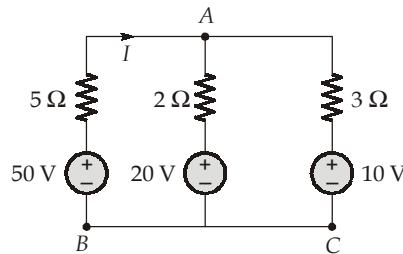

Using nodal analysis,
KCL at node 'A'

$$\frac{50 - V_A}{5} = \frac{V_A - 20}{2} + \frac{V_A - 10}{3}$$


$$V_A = 22.580 \text{ V}$$

$$\text{So, } I = \frac{50 - 22.580}{5} = 5.483 \text{ A}$$

So, power delivered by 50 V is,

$$50 \times I = 50 \times 5.483 = 274.2 \text{ Watts}$$

9. (b)

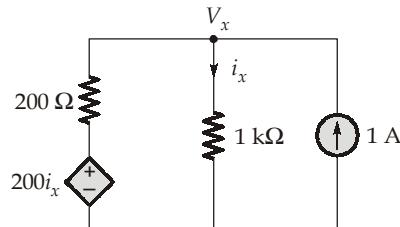

Since,

$$i_x = \frac{V_x}{1 \text{ k}\Omega} = \frac{V_x}{1000}$$

$$200i_x = 0.2V_x$$

$$\text{and } \frac{V_x}{1000} + \frac{V_x - 0.2V_x}{200} = 1 \text{ A}$$

$$V_x = 200 \text{ V}$$

$$R_{\text{eq}} = \frac{V_x}{1 \text{ A}} = 200 \Omega$$

10. (c)

Voltage across capacitor

$$\begin{aligned} v_c(t) &= V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}})e^{-t/RC} \\ &= 0 + (5 - 0)e^{-t/RC} \end{aligned}$$

But given,

$$v_c(t) = \frac{5}{e} = 5e^{-t/RC}$$

$$\frac{5}{e} = 5e^{-(0.1/40 \text{ k}\Omega \times C)}$$


$$\frac{0.1}{40 \text{ k}\Omega \times C} = 1$$

$$\therefore C = 2.5 \mu\text{F} \quad (\text{or}) \quad 2.5 \times 10^{-6} \text{ F}$$

11. (b)

$$R_{ab} = \frac{V_{OC}}{I_{SC}}$$

To find open circuit voltage

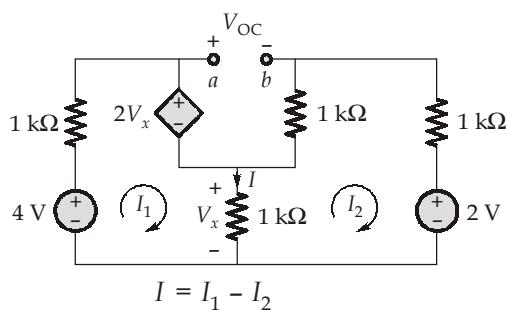

$$I = I_1 - I_2$$

Applying KVL in loop 1, we get,

$$(1 \text{ k}\Omega)I_1 + 2V_x + I(1 \text{ k}\Omega) = 4$$

$$V_x = I(1 \text{ k}\Omega)$$

$$\therefore (4 \text{ k}\Omega)I_1 - 3 \text{ k}\Omega I_2 = 4 \quad \dots(i)$$

Applying KVL in loop 2, we get,

$$(1 \text{ k}\Omega)I_2 + (1 \text{ k}\Omega)I_1 - (1 \text{ k}\Omega)I = -2$$

$$-(1 \text{ k}\Omega)I_1 + (3 \text{ k}\Omega)I_2 = -2 \quad \dots(ii)$$

Solving equations (i) and (ii), we get,


$$I_1 = 0.667 \text{ mA}$$

$$I_2 = -0.444 \text{ mA}$$

$$\therefore V_{OC} = 2V_x + (1 \text{ k}\Omega)I_2$$

$$V_{OC} = 1.78 \text{ V}$$

Finding short circuit current

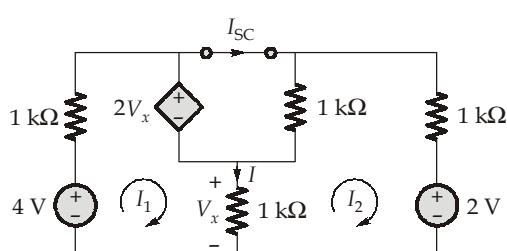

$$I_{SC} = I' + I_2$$

$$I' = I_{SC} - I_2$$

$$I + I_2 = I_1$$

$$I = I_1 - I_2$$

Applying KVL in loop (1)

$$(4 \text{ k}\Omega)I_1 + 2V_x - (3 \text{ k}\Omega)I_2 = 4 \quad \dots(i)$$

Applying KVL in loop (ii)

$$(-1 \text{ k}\Omega)I_{SC} - (1 \text{ k}\Omega)I_1 + (3 \text{ k}\Omega)I_2 = -2 \quad \dots(\text{ii})$$

$$V_x = (1 \text{ k}\Omega)I = (1 \text{ k}\Omega)(I_1 - I_2)$$

Thus,

$$I_1 = 1.43 \text{ mA}$$


$$I_2 = 0.57 \text{ mA}$$

$$\therefore I_{SC} = \frac{(-1 \text{ k}\Omega)I_1 + (3 \text{ k}\Omega)I_2 + 2}{1 \text{ k}\Omega} = 2.29 \text{ mA}$$

$$\therefore R_{Th} = \frac{1.78}{2.29} \times 10^3 \Omega = 777 \Omega$$

12. (d)

Applying KCL on supernode

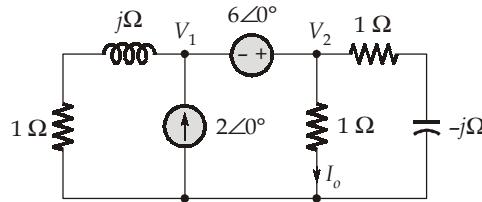

$$\frac{V_1}{1+j} - 2 + \frac{V_2}{1} + \frac{V_2}{1-j} = 0$$

and

$$V_1 + 6 = V_2$$

$$\therefore \begin{bmatrix} 0.5 - 0.5j & 1.5 + 0.5j \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$\therefore V_2 = \frac{\begin{bmatrix} 0.5 - 0.5j & 2 \\ 1 & -6 \end{bmatrix}}{\begin{bmatrix} 0.5 - 0.5j & j0.5 + 0.5j \\ 1 & -1 \end{bmatrix}}$$

$$V_2 = \frac{5.83095 \angle 149.036}{2 \angle 180^\circ}$$

$$V_2 \approx 2.915 \angle -30.96^\circ$$

Thus,

$$I_o = \frac{V_2}{1 \Omega} = 2.915 \angle -30.96^\circ$$

13. (a)

$$V_c(t) = \frac{-1}{10 \times 10^{-6}} \left[\int_0^t 0.2e^{-800\tau} d\tau - \int_0^t 0.04e^{-200\tau} d\tau \right] + 5$$

$$= 25e^{-800t} - 20e^{-200t}$$

$$V_L(t) = 150 \times 10^{-3} \frac{dI_o}{dt} = 150(-160e^{-800t} + 8e^{-200t}) \times 10^{-3}$$

$$= -24e^{-800t} + 1.2e^{-200t}$$

$$V_o(t) = V_c(t) - V_L(t)$$

$$= (25e^{-800t} - 20e^{-200t}) - (-24e^{-800t} + 1.2e^{-200t})$$

$$V_o(t) = (49e^{-800t} - 21.2e^{-200t}) \text{ V}$$

14. (b)

The 20Ω impedance can be reflected to the primary side as

$$\begin{aligned} Z_R &= \frac{20}{n^2} = \frac{20}{4} = 5 \Omega \\ \therefore Z_i &= 4 - 6j + 5 \\ &= 9 - 6j = 10.82 \angle -33.69^\circ \Omega \\ I_1 &= \frac{120 \angle 0^\circ}{Z_{in}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \\ \therefore I_2 &= -\frac{1}{n} I_1 = -5.545 \angle 33.69^\circ \text{ A} \\ V_o &= 20I_2 = 110.9 \angle 213.69^\circ \text{ V} \end{aligned}$$

15. (b)

The transfer function, $H(s) = \frac{v_o}{v_i} = \frac{R \parallel 1/sC}{sL + R \parallel 1/sC}$

$$\begin{aligned} H(s) &= \frac{R}{\frac{1+sRC}{sL+\frac{R}{1+sRC}}} = \frac{R}{s^2RLC + sL + R} \\ H(j\omega) &= \frac{R}{-\omega^2RLC + j\omega L + R} \end{aligned}$$

At corner frequency, $|H(j\omega)| = \frac{1}{\sqrt{2}} |H(j\omega)|_{\max}$

$$\begin{aligned} \text{Now, } |H(j\omega)| &= \frac{R}{\sqrt{(R - \omega^2 RLC)^2 + \omega^2 L^2}} \\ |H(j\omega)|^2 &= \frac{1}{2} = \frac{R^2}{(R - \omega^2 RLC)^2 + \omega^2 L^2} \\ 2 &= (1 - \omega_o^2 LC)^2 + \left(\frac{\omega_o L}{R}\right)^2 \\ 2 &= (1 - \omega_o^2 4 \times 10^{-6})^2 + (\omega_o \times 10^{-3})^2 \\ 16\omega_o^4 - 7\omega_o^2 - 1 &= 0 \text{ (where } \omega_o \text{ is in Krad/s)} \\ \therefore \omega_o &= 0.742 \text{ K rad/sec} = 742 \text{ rad/sec} \end{aligned}$$

16. (b)

$$\begin{aligned} Z_{AB} &= \left(\frac{23}{6}\right) + [(3+j4)\parallel(3-j4)] \\ &= \frac{23}{6} + \frac{(3+j4)(3-j4)}{6} = \frac{23+25}{6} = \frac{48}{6} \Omega = 8 \Omega \\ \therefore Z_{AB} &= 8 \Omega \end{aligned}$$

17. (a)

$$L_{\text{eq}} = L_1 + L_2 - 2M = 4 + 4 - 2 \times 2 = 4 \text{ mH}$$

$$\text{Resonant frequency, } f_o = \frac{1}{2\pi\sqrt{L_{\text{eq}}C}}$$

$$f_o = \frac{1}{2\pi\sqrt{4 \times 0.1 \times 10^{-9}}} = 7.96 \text{ kHz}$$

18. (b)

$$\text{Impedance matrix for 'N' } = \frac{1}{[Y]} = \frac{1}{5} \begin{bmatrix} 3 & -2 \\ -2 & 3 \end{bmatrix} = \begin{bmatrix} 3/5 & -2/5 \\ -2/5 & 3/5 \end{bmatrix}$$

In series connection: individual impedance parameters are added

$$\therefore \text{For individual network } = \frac{1}{2} \begin{bmatrix} 3/5 & -2/5 \\ -2/5 & 3/5 \end{bmatrix} = \begin{bmatrix} 0.3 & -0.2 \\ -0.2 & 0.3 \end{bmatrix}$$

19. (b)

We know that, for a transformer

$$R_s = \left(\frac{n_1}{n_2} \right)^2 R_L$$

$$100 \text{ k}\Omega = \left(\frac{n_1}{n_2} \right)^2 10$$

$$\left(\frac{n_1}{n_2} \right)^2 = 10^4$$

$$\therefore \frac{n_1}{n_2} = 100$$

20. (c)

$$v(t) = 2[u(t) - u(t-2)] \text{ V}$$

$$i(t) = [r(t) - r(t-2)] \text{ A}$$

$$v(t) = 2 \frac{di(t)}{dt}$$


$$\text{For inductor, } v(t) = L \frac{di(t)}{dt}$$

\therefore The element is inductor of 2 H

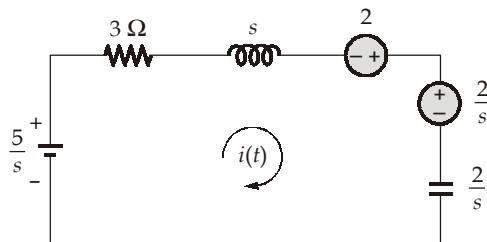21. (c)

At $t = 0$, switch is closed

For $t > 0$, the circuit in s -domain becomes,



Applying KVL, we get,


$$\frac{5}{s} - \frac{2}{s} + 2 = \left(3 + s + \frac{2}{s}\right) I(s)$$

$$I(s) = \frac{2s+3}{(s+1)(s+2)}$$

$$\text{Using partial fractions, } I(s) = \frac{1}{(s+1)} + \frac{1}{(s+2)}$$

$$\text{or } i(t) = L^{-1}[I(s)] = (e^{-t} + e^{-2t}) \text{ A ; for } t > 0$$

22. (a)

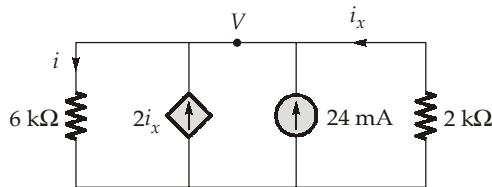

$$\text{Applying KCL, } i = 2i_x + 24 \text{ mA} + i_x \dots (\text{i})$$

$$\text{where, } i = \frac{V}{6000} \text{ and } i_x = \frac{-V}{2000} \dots (\text{ii})$$

Therefore, from equations (i) and (ii)

$$\frac{V}{6000} + \frac{V}{2000} - 2\left(-\frac{V}{2000}\right) = 24 \text{ mA}$$

$$\Rightarrow V = (600)(24 \times 10^{-3}) = 14.4 \text{ V}$$

Hence, power supplied by independent current source

$$P = V \times 24 \text{ mA} = 14.4 \times 24 \times 10^{-3} = 345.6 \text{ mW}$$

23. (d)

Given,

$$f = 1.5 \text{ MHz}$$

$$C = 150 \text{ pF}$$

$$\text{BW} = 10 \text{ kHz}$$

$$\text{For series RLC circuit, } Q = \frac{f_o}{\text{BW}} = \frac{1.5 \times 10^6}{10 \times 10^3} = 150$$

$$Q = \frac{1}{\omega RC}$$

$$\frac{1}{150} = 2\pi \times 1.5 \times 10^6 \times 150 \times 10^{-12} \times R$$

$$R = \frac{10^6}{2\pi \times 1.5 \times 150} = 4.71 \Omega$$

24. (b)

For $t < 0$, source 2 $u(t) = 0$

$$\text{Therefore, } i_L(0^-) = i_L(0^+) = 0 \text{ A}$$

$$v_c(0^-) = v_c(0^+) = 0 \text{ V}$$

$$\text{For } t > 0, \quad i_c(0^+) = 2 \text{ mA}$$

$$i_c(0^+) = c \frac{dv_c(0^+)}{dt}$$

$$\frac{dv_c(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{2 \times 10^{-3}}{4 \times 10^{-3}} = 0.5 \text{ V/sec}$$

25. (c)


For a capacitor

$$i(t) = \frac{cdv(t)}{dt} = 10 \times 10^{-6} \frac{dv(t)}{dt} \times 10^3 \text{ A}$$

$$= 10^{-2} \frac{dv(t)}{dt} \text{ A} = 10 \frac{dv(t)}{dt} \text{ mA}$$

26. (a)

For the circuit

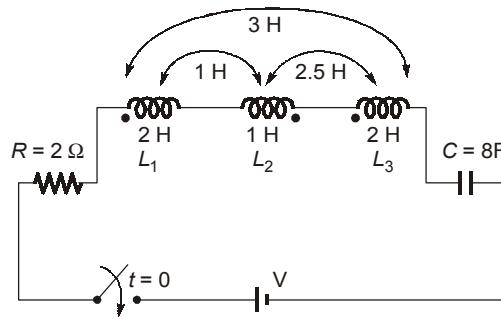

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$$

$$L_1 = 2 \text{ H}$$

$$L_2 = 1 \text{ H}$$

$$L_3 = 2 \text{ H}$$

$$M_{12} = 1 \text{ H}$$

$$M_{23} = 2.5 \text{ H}$$

$$M_{13} = 3 \text{ H}$$

$$L_{eq} = 2 + 1 + 2 - 2 - 5 + 6$$

$$= 11 - 7$$

$$= 4 \text{ H}$$

$$C = 8 \text{ F}$$

$$R = 2 \Omega$$

$$\therefore \omega_n = \frac{1}{\sqrt{L_{eq}C}} = \frac{1}{\sqrt{8 \times 4}} = 0.176 \text{ rad/sec} \approx 0.18 \text{ rad/sec}$$

Note : M_{12}, M_{23} is negative, because both L_1, L_2 and L_2, L_3 opposes the flux of respective loops.

27. (b)

$\because p(t)$ varies with time, thus it can be concluded that the network is not purely resistive circuit.

$$\therefore \text{let, } v(t) = \sqrt{2} V_{rms} \cos(\omega t + \theta_v)$$

$$i(t) = \sqrt{2} I_{rms} \cos(\omega t + \theta_I)$$

then, the instantaneous power into the network N is given as,

$$p(t) = v(t) i(t) = 2V_{rms} I_{rms} \cos(\omega t + \theta_v) \cos(\omega t + \theta_I)$$

$$= V_{\text{rms}} I_{\text{rms}} \left[\underbrace{\cos(\theta_v - \theta_I)}_{\text{constant}} + \underbrace{\cos(2\omega t + \theta_v + \theta_I)}_{\text{time varying}} \right]$$

thus, for minimum power delivered,

$$\cos(2\omega t + \theta_v + \theta_I) = -1$$

and for maximum power delivered

$$\cos(2\omega t + \theta_v + \theta_I) = 1$$

$$p(t)_{\max} = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_I) + V_{\text{rms}} I_{\text{rms}} \quad \dots(i)$$

$$p(t)_{\min} = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_I) - V_{\text{rms}} I_{\text{rms}} \quad \dots(ii)$$

Thus, from equation (i) and (ii), we get,

thus, $2V_{\text{rms}} I_{\text{rms}} = 2500$

$$V_{\text{rms}} I_{\text{rms}} = 1250$$

$$I_{\text{rms}} = \frac{1250}{V_{\text{rms}}} = \frac{1250}{100} = 12.5 \text{ A}$$

28. (c)

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}} = 50 \text{ krad/sec}$$

$$Q = \frac{\omega_0 L}{R} = \frac{50 \times 10^3 \times 10^{-3}}{2} = 25$$

$$B = \frac{\omega_0}{Q} = \frac{50 \times 10^3}{25} = 2 \text{ krad/sec}$$

$$\text{now, } \omega_1 = \omega_0 - \frac{B}{2} = 50 - 1 = 49 \text{ krad/sec}$$

$$\text{now, } \omega_2 = \omega_0 + \frac{B}{2} = 50 + 1 = 51 \text{ krad/sec}$$

Hence, option (c) is incorrect.

29. (d)

Now, applying KCL at node A, we get,

$$\begin{aligned} I_1 &= V_1 + (V_1' - V_1) \\ &= 2V_1 - V_1' \end{aligned}$$


$$I_1 = 2V_1 - \frac{1}{a}V_2$$

For I_2 , we can write

$$I_2 = -\frac{1}{a}I_1' = -\frac{1}{a}[-V_1' + (V_1 - V_1')]$$

$$= -\frac{1}{a}V_1 + \frac{2}{a^2}V_2$$
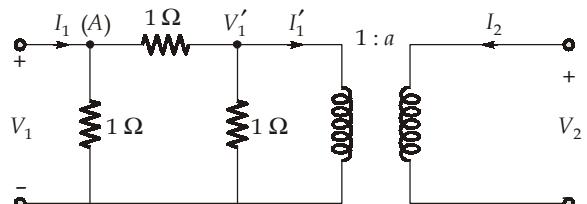
$$\therefore \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 2 & -\frac{1}{a} \\ -\frac{1}{a} & \frac{2}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



For the Z-parameter to not exist.

$$\begin{aligned} |Y| &= 0 \\ \therefore |Y| &= \frac{4}{a^2} - \frac{1}{a^2} = \frac{3}{a^2} \\ \therefore |Y| &\neq 0 \end{aligned}$$

Thus, no such value exist for which $|Y| = 0$.

30. (a)

From phasor, we can write

$$\begin{aligned} \tan 30^\circ &= \frac{X_C}{R_2} \\ \Rightarrow R_2 &= X_C \sqrt{3} = \frac{\sqrt{3}}{\omega C} \\ \tan 45^\circ &= \frac{X_L}{R_1} \\ \Rightarrow R_1 &= X_L = \omega L \\ R_1 R_2 &= \frac{\sqrt{3}}{\omega C} \times \omega L = \frac{L}{C} \sqrt{3} \\ R_1 R_2 &= \sqrt{3} = 1.732 \end{aligned}$$

we know

$$\frac{R_1 + R_2}{2} \geq \sqrt{R_1 R_2}$$

as arithmetic mean \geq geometric mean ; (for non-negative real numbers)

$$R_1 + R_2 \geq 2\sqrt{3}$$

$$R_1 + R_2 \geq 2(3)^{1/4}$$

Minimum value of $R_1 + R_2 = 2.63 \Omega$

