



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ANALOG ELECTRONICS

ELECTRICAL ENGINEERING

Date of Test : 02/05/2023

ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (d) | 7. (b) | 13. (c) | 19. (d) | 25. (d) |
| 2. (b) | 8. (d) | 14. (d) | 20. (d) | 26. (b) |
| 3. (c) | 9. (d) | 15. (c) | 21. (b) | 27. (b) |
| 4. (c) | 10. (d) | 16. (c) | 22. (a) | 28. (b) |
| 5. (c) | 11. (a) | 17. (d) | 23. (a) | 29. (a) |
| 6. (a) | 12. (d) | 18. (b) | 24. (d) | 30. (c) |

DETAILED EXPLANATIONS

1. (d)

Applying KVL we get,

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{3 - 0.2}{1k} = 2.8 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{2.8 \text{ mA}}{50} = 56 \mu\text{A}$$

2. (b)

$$V_{EC(\text{sat})} = 0.2 \text{ V}$$

$$V_{EB} = 0.7 \text{ V}$$

Assume that BJT is in saturation region

KVL in outer most loop:

$$\begin{aligned} -10 + 1k (I_E) + V_{EC(\text{sat})} + 1k I_C &= 0 \\ 1k (I_B + I_C) + 1k I_C &= 10 - 0.2 = 9.8 \\ 1k I_B + 2k I_C &= 9.8 \end{aligned} \quad \dots(i)$$

KVL in emitter base loop:

$$\begin{aligned} -10 + 1k (I_E) + 0.7 + 270k (I_B) &= 0 \\ (271k)I_B + 1k I_C &= 9.3 \end{aligned} \quad \dots(ii)$$

From (i) and (ii),

$$I_B = 0.0162 \text{ mA};$$

$$I_C = 4.892 \text{ mA}$$


$$I_{B \text{ min}} = \frac{I_{C(\text{sat})}}{\beta} = 0.04892 \text{ mA}$$

$$I_B < I_{B \text{ min}}$$

∴ transistor is in linear or active region.

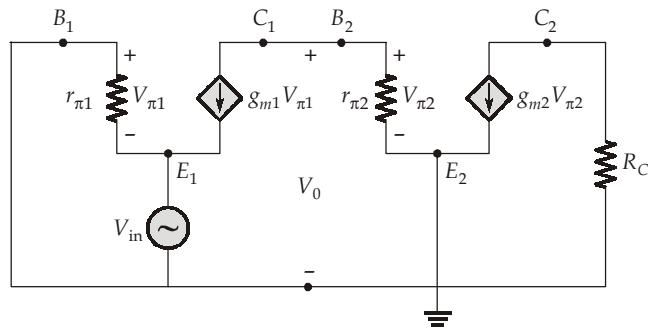3. (c)

The small signal equivalent of the above circuit can be given as



$$-V_{in} - V_{\pi 1} = 0$$

$$V_{in} = -V_{\pi 1} \quad \dots(i)$$

$$V_0 = -g_{m1} V_{\pi 1} r_{\pi 2} \quad \dots(ii)$$

$$A_V = \frac{g_{m1} V_{\pi 1} r_{\pi 2}}{V_{\pi 1}}$$

$$A_V = g_{m1} r_{\pi 2}$$


As we know,

$$r_{\pi} = \frac{\beta}{g_m}$$

$$A_V = \beta_2 \left(\frac{g_{m1}}{g_{m2}} \right)$$

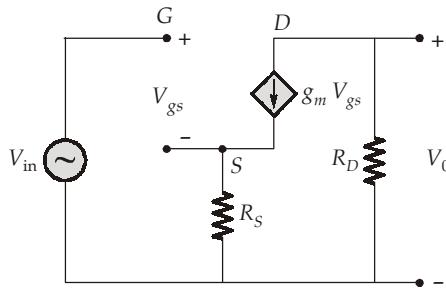4. (c)

For common source amplifier the ac small signal circuit is,



$$V_0 = -g_m V_{gs} R_D$$

KVL in gate source loop,

$$-V_i + V_{gs} + g_m V_{gs} R_s = 0$$

$$V_i = V_{gs} (1 + g_m R_s)$$

$$A_V = \frac{-g_m R_D}{1 + g_m R_s}$$

$$|A_V| = 1 = \frac{g_m R_D}{1 + g_m R_s}$$

If $g_m R_s \gg 1$

$$1 = \frac{g_m R_D}{g_m R_s}$$

$$R_D = R_s$$

5. (c)

Dynamic resistance of diode,

$$r_d = \frac{\eta V_T}{I_0 e^{v/\eta V_T}} \quad \text{P} \quad \frac{r_{d2}}{r_{d1}} = \frac{e^{v_1/\eta V_T}}{e^{v_2/\eta V_T}}$$

$$\therefore 1000 = e^{|v_1 - v_2|/\eta V_T}$$


$$\therefore \ln 10^3 = |v_1 - v_2| / \eta V_T$$

$$\Rightarrow \text{for } \eta = 1, \quad |v_1 - v_2| = V_T (\ln 10^3)$$

6. (a)

\because The feedback is voltage-series feedback, so the amplifier will be a voltage amplifier.

7. (b)

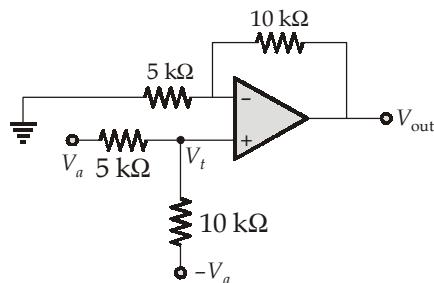

Since, the amplifier is an non-inverting amplifier thus,

$$V_{\text{out}} = \left(1 + \frac{R_2}{R_1}\right)V_t$$

$$V_t = V_a \times \frac{10 \text{ k}}{15 \text{ k}} - \frac{V_a \times 5 \text{ k}}{15 \text{ k}}$$

$$V_t = \frac{V_a}{3}$$

$$V_{\text{out}} = \left(1 + \frac{10 \text{ k}}{5 \text{ k}}\right) \cdot V_t = 3 \times \frac{V_a}{3} = V_a$$

8. (d)

For amplifier to have a valid

$$V_{\text{out}} = A(V_1 - V_2)$$

$$V_1 - V_2 = \frac{V_{\text{out}}}{A}$$

now, for virtual ground $A \rightarrow \infty$.

But if $A \neq \infty$, then

$$V_t = \frac{\pm V_{\text{out}}}{A} = \frac{\pm 10}{1000} = \pm 10 \text{ mV}$$

9. (d)

The value of input capacitance is equal to

$$C_{\text{in}} = C(1 - A_v) \quad (\text{Miller's theorem})$$

\therefore The op-amp is ideal and inverting.

$$C_{\text{in}} \approx \infty$$

10. (d)

The equation of output voltage for steady state can be given as


$$V_0 = V_i - 7.5$$

\therefore For $V_i = 10$, $V_0 = 2.5 \text{ V}$

and for $V_i = -10 \text{ V}$, $V_0 = -17.5 \text{ V}$

11. (a)

Assume both the diode to be ON.

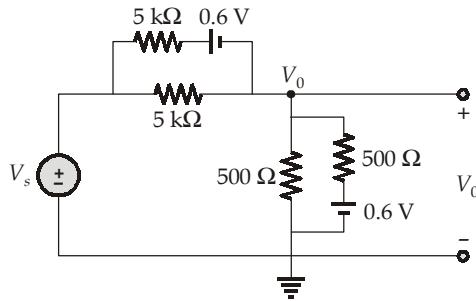

Applying the KCL at node V_0 , we get,

$$\frac{V_0 + 0.6 - V_s}{5 \text{ k}} + \frac{V_0 - V_s}{5 \text{ k}} + \frac{V_0}{500} + \frac{V_0 - 0.6}{500} = 0$$

$$\therefore V_0 = \frac{2}{22} V_s + \frac{5.4}{22}$$

$$V_0 = \frac{1}{11} V_s + \frac{54}{220}$$

For diode D_1 to be ON.

$$V_s - V_0 > 0.6$$

$$V_s - \frac{2V_s + 5.4}{22} > 0.6$$

$$V_s > 0.93 \text{ V}$$

For diode D_2 to be ON.

$$V_0 > 0.6 \text{ V}$$

$$\frac{2V_s + 5.4}{22} > 0.6$$

$$V_s > 3.9 \text{ V}$$

12. (d)

To find maximum power dissipated across the resistance, we have to find the maximum current flowing in the load resistance R_L

$$\begin{aligned} i_{\text{Load (max)}} &= i_{\text{in}} - i_{z(\min)} \\ &= \frac{6.3 - 4.8}{12} - 5 \times 10^{-3} = (125 - 5) \times 10^{-3} = 120 \text{ mA} \end{aligned}$$

$$\therefore P_{(\max)} = (120 \times 10^{-3}) \times 4.8 = 0.576 \text{ W}$$

For maximum value of resistance R_L , we have to find $i_{L(\min)}$

$$\begin{aligned} i_{\text{Load (min)}} &= i_{\text{in}} - i_{z(\max)} \\ &= 125 \times 10^{-3} - \frac{0.48}{4.8} = 125 \times 10^{-3} - 100 \times 10^{-3} = 25 \text{ mA} \end{aligned}$$

$$\therefore R_{L(\max)} = \frac{4.8}{25} \times 10^3 = 192 \Omega$$

13. (c)

$$S_v = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{\beta, I_{CO} \text{ are constant}}$$

$$= \frac{-\beta}{R_B + R_E(1+\beta)} = \frac{-\frac{\beta}{R_E}}{1+\beta + \frac{R_B}{R_E}}$$


$$S_v \approx -\frac{1}{R_E} \quad \because \frac{R_B}{R_E} \ll 1 + \beta \text{ and } 1 + \beta \equiv \beta$$

14. (d)

If the bypass capacitor is removed, then the mid band voltage gain will decrease and the input resistance will increase. This happens because of the negative feedback introduced by R_E .

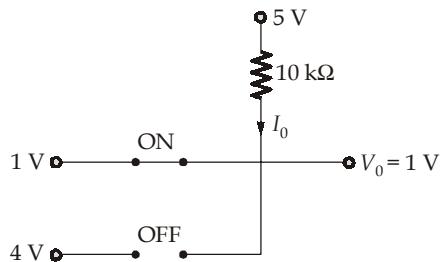15. (c)

From the circuit, we can conclude that diode D_1 will conduct and diode D_2 will be switched off.



$$I_0 = \frac{5V - V_0}{10 \text{ k}\Omega} = \frac{5V - 1V}{10 \text{ k}\Omega} = 0.4 \text{ mA}$$

Thus, $V_0 = 1 \text{ V}$ and $I_0 = 0.4 \text{ mA}$.

16. (c)

For astable multivibrator

$$f = \frac{1.44}{(R_A + 2R_B)C} \text{ Hz}$$

therefore, $2 \times 10^3 = \frac{1.44}{(R_A + 2R_B)C}$

$$(R_A + 2R_B)C = 7.2 \times 10^{-4}$$

$$R_A + 2R_B = 7.2 \times 10^3$$

($\because C = 0.1 \mu\text{F}$) ... (i)

now, Duty cycle D

$$D = 0.75 = \frac{R_A + R_B}{R_A + 2R_B}$$


$$R_B = 0.5R_A \quad \dots \text{(ii)}$$

From equation (i) and (ii), we get,

$$R_B = 1.8 \text{ k}\Omega$$

$$R_A = 3.6 \text{ k}\Omega$$

17. (d)

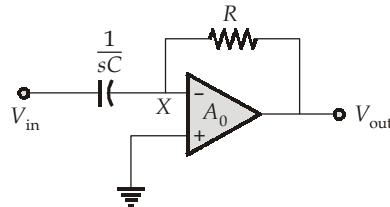

Applying KCL at node 'X', we get,

$$\frac{V_{in} - V_x}{1/sC} = \frac{V_x - V_{out}}{R_1}$$

now,

$$\frac{-V_{out}}{A_0} = V_x$$

∴

$$\frac{-V_{out}}{V_{in}} = \frac{-RCs}{1 + \frac{1}{A_0} + \frac{sRC}{A_0}}$$

$$\frac{s_p RC}{A_0} + \frac{1}{A_0} + 1 = 0$$

$$\frac{s_p RC}{A_0} = -1 - \frac{1}{A_0}$$

$$\text{Pole, } s_p = \frac{-(1 + A_0)}{RC}$$

Hence option (d) is correct.

18. (b)

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} = \frac{\frac{A_0}{(1 + j\omega/\omega_0)}}{1 + \frac{A_0}{\left(1 + \frac{j\omega}{\omega_0}\right)} \cdot \beta} = \frac{A_0}{1 + j\frac{\omega}{\omega_0} + A_0\beta}$$

$$= \frac{\frac{A_0}{1 + A_0\beta}}{1 + j\frac{\omega}{\omega_0(1 + A_0\beta)}} = \frac{A'_{CL}}{1 + j\frac{\omega'}{\omega_0}}$$

∴

$$\omega' = \omega_0(1 + A_0\beta)$$

19. (d)

Applying KVL we get,

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{3 - 0.2}{1k} = 2.8 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{2.8 \text{ mA}}{50} = 56 \mu\text{A}$$

20. (d)

If transistor is in normal active region, base current can be calculated as
At input loop,

$$10 - I_E (1 \times 10^3) - 0.7 - 270 \times 10^3 I_B = 0$$

$$9.3 = 10^3 (1 + \beta) I_B + 270 \times 10^3 I_B$$

$$I_B = \frac{9.3 \text{ mA}}{270 + 101} = 25 \mu\text{A}$$

In saturation, base current is

$$10 - I_C(1 \text{ k}) - V_{CE \text{ sat}} - I_E(1 \text{ k}) = 0$$


$$I_{C \text{ sat}} = \frac{10}{2 \text{k}} = 5 \text{ mA} \quad (\because I_E \approx I_C)$$

$$I_{B \text{ sat}} = \frac{I_{C \text{ sat}}}{\beta} = \frac{5 \text{ mA}}{100} = 50 \mu\text{A}$$

$$I_B < (I_B)_{\text{sat}}$$

So transistor is in forward active region.

21. (b)

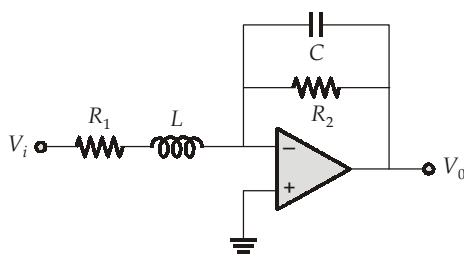

$$\frac{V_i - 0}{R_1 + sL} = \frac{(0 - V_0)(1 + R_2 C s)}{R_2}$$

$$\left| \frac{V_0}{V_i} \right| = \frac{R_2}{(R_1 + sL)(1 + R_2 C s)}$$

This is a low pass filter.

22. (a)

$$\text{Output voltage, } V_0 = V_Z - V_{BE}$$

$$= 8.3 - 0.7 = 7.6 \text{ V}$$

$$\text{Current through, } R = \frac{V_i - V_z}{R} = \frac{15 - 8.3}{1.8} \text{ mA} = 3.72 \text{ mA}$$

$$I_L = \frac{V_0}{R_L} = \frac{7.6}{2} = 3.8 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{I_L}{\beta} = \frac{3.8}{100} \text{ mA} = 0.038 \text{ mA}$$

$$I_Z = I_R - I_B$$

$$= 3.72 - 0.038 = 3.684 \text{ mA}$$

23. (a)

The PIV rating of full-wave rectifier with centre tap is $2 V_m = 2 \times 100 = 200$ V

24. (d)

Miller effect increase input capacitance and there by decreases the higher cut-off frequency.

25. (d)

$$V_G = \frac{47\text{k}\Omega(16\text{V})}{47\text{k}\Omega + 91\text{k}\Omega} = 5.44 \text{ V}$$

$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{16 - 12}{1.8\text{k}\Omega} = 2.22 \text{ mA}$$

$$\begin{aligned} V_{GS} &= V_G - I_D R_S \\ -2 &= 5.44 - (2.22 \text{ mA}) R_s \end{aligned}$$

$$R_s = \frac{7.44}{2.22 \text{ mA}} = 3.35 \text{ k}\Omega$$

26. (b)

$$\begin{aligned} I &= \frac{V_2 - V_{BE}}{R_E} = \frac{6.2 - 0.7}{1.8\text{k}\Omega} \\ &= 3.06 \text{ mA} \approx 3 \text{ mA} \end{aligned}$$

27. (b)

$$\text{Feedback factor, } \beta = \frac{V_f}{V_0} = \frac{-R_E}{R_C}$$

28. (b)

Transistor will enter to saturation region for $V_{CE(\text{sat})} = 0$ V

Applying KVL in collector emitter loop,

$$-20 + (I_C \times 10 \text{ k}) + V_{CE\text{ sat}} = 0$$

$$I_C = \frac{20 - V_{CE(\text{sat})}}{10\text{k}} = 2 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{2 \times 10^{-3}}{50} = 40 \mu\text{A}$$

Applying KVL in base emitter loop

$$-10 + I_B R_B + 0.7 = 0$$

$$R_B = \frac{10 - 0.7}{40 \times 10^{-6}} = 232.5 \text{ k}\Omega$$

\therefore For all values of $R_B > 232.5 \text{ k}\Omega$ the transistor will not operate in saturation region.

29. (a)

The output voltage of differential amplifier is given as,

$$V_0 = A_d V_d + A_c V_c$$

Where,

A_d = Differential gain

A_c = Common mode gain

V_d = Differential input voltage = $V_1 - V_2$

V_c = Common mode input voltage = $\frac{V_1 + V_2}{2}$

$$V_0 = A_d V_d \left[1 + \frac{A_c V_c}{A_d V_d} \right] = A_d V_d \left[1 + \frac{1}{\rho} \cdot \frac{V_c}{V_d} \right]$$

Where,

$\rho = \frac{A_d}{A_c}$ = common mode rejection ratio

Set of signal 1,

$$V_d = 50 \mu V - (-50 \mu V) = 100 \mu V$$

$$V_c = \frac{50 \mu V + 50 \mu V}{2} = 0$$

$$V_{01} = 100 \mu V A_d [1 + 0] = 100 A_d \mu V$$

$$V_c = \frac{1050 \mu V + 950 \mu V}{2} = 1000 \mu V$$

$$V_d = 1050 \mu V - 950 \mu V = 100 \mu V$$

$$\therefore V_{02} = A_d 100 \mu V \left[1 + \frac{1}{100} \times \frac{1000 \mu V}{100 \mu V} \right] = 110 A_d \mu V$$

$$\% \text{ difference} = \frac{V_{02} - V_{01}}{V_{01}} \times 100 = \frac{110 - 100}{100} \times 100 = 10\%$$

30. (c)

The given circuit is voltage series feedback,

$$\begin{aligned} \therefore Z_{if} &= Z_i (1 + \beta A) \\ &= 10 \text{ k}\Omega (1 + 10) = 110 \text{ k}\Omega \end{aligned}$$

$$Z_{0f} = \frac{Z_0}{1 + \beta A} = \frac{20 \times 10^3}{11} = 1.82 \text{ k}\Omega$$

