

CLASS TEST

S.No. : 05 LS1_EC_E+F_100819

Topic Name



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Noida | Bhopal | Hyderabad | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

CLASS TEST 2019-2020

ELECTRONICS ENGINEERING


Date of Test : 10/08/2019

ANSWER KEY > Network Theory

1. (c)	7. (d)	13. (d)	19. (c)	25. (b)
2. (d)	8. (d)	14. (c)	20. (c)	26. (c)
3. (b)	9. (c)	15. (d)	21. (d)	27. (a)
4. (b)	10. (c)	16. (c)	22. (c)	28. (b)
5. (b)	11. (a)	17. (b)	23. (a)	29. (c)
6. (c)	12. (b)	18. (b)	24. (a)	30. (b)

DETAILED EXPLANATIONS

1. (c)
using source transformation

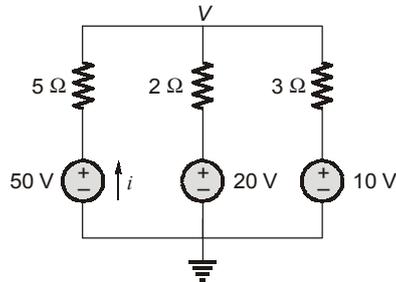

applying KCL at V

$$\frac{V - 50}{5} + \frac{V - 20}{2} + \frac{V - 10}{3} = 0$$

$$\frac{6V - 300 + 15V - 300 + 10V - 100}{30} = 0$$


$$31V - 700 = 0$$

or
$$V = \frac{700}{31} = 22.58 \text{ V}$$

$$i = \frac{50 - V}{5}$$

$$= \frac{50 - 22.58}{5} = 5.48 \text{ A}$$

2. (d)

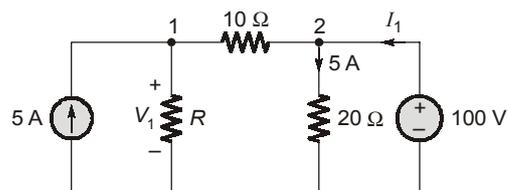

At node 1, using KCL, we have:

$$5 = \frac{V_1}{R} + \frac{V_1 - 100}{10} \quad \dots(i)$$

At node 2, using KCL, we have:

$$\frac{V_1 - 100}{10} + I_1 = \frac{100}{20} = 5$$

or,
$$\frac{V_1 - 100}{10} + I_1 = 5 \quad \dots(ii)$$

For equal power; $100 I_1 = 5 V_1 \quad \dots(iii)$

From equation (i) we obtain,

$$\frac{V_1}{R} + \frac{V_1}{10} = 15 \quad \dots(\text{iv})$$

From equation (ii) we obtain,

$$I_1 + \frac{V_1}{10} = 15 \quad \dots(\text{v})$$

Equating equation (iv) and (v) we can write,


$$I_1 = \frac{V_1}{R} \quad \dots(\text{vi})$$

Finally equation (iii) and (vi) yield,

$$\frac{100V_1}{R} = 5V_1$$

or, $R = 20 \Omega$

3. (b)

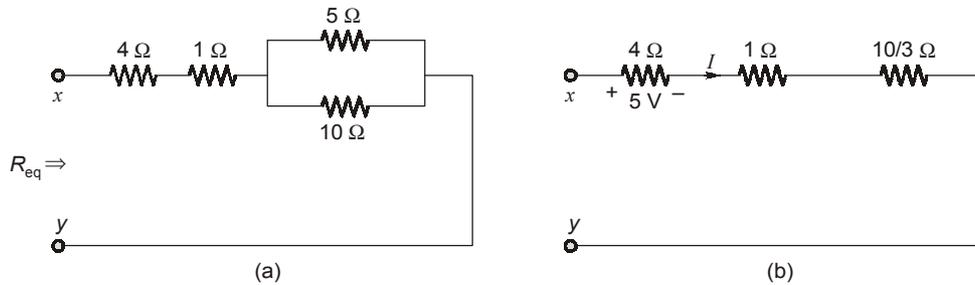

$$\begin{aligned} R_{\text{eq}} &= 4 \Omega + 1 \Omega + (5 \parallel 10) \Omega \\ &= 5 \Omega + \left(\frac{5 \times 10}{15} \right) \Omega \\ &= 5 + \frac{10}{3} = \frac{25}{3} \Omega \end{aligned}$$

Also from (b) $I = \frac{5}{4} \text{ A}$ (in series circuit current remains same)

$\therefore V_{xy} = \frac{5}{4} \times \frac{25}{3} = 10.417 \text{ V}$

4. (b)

$$R = \frac{V^2}{P} = \frac{110^2}{10} = 1210 \Omega$$


Also $I_R = \frac{V}{R} = \frac{110 \angle 0^\circ}{1210 \angle 0^\circ} = 0.091 \text{ A}$

$$I = \sqrt{I_R^2 + I_C^2}$$

$\therefore I_C = \sqrt{I^2 - I_R^2} = \sqrt{0.5^2 - 0.091^2} = 0.492 \text{ A}$

5. (b)

At $t = 0^+$

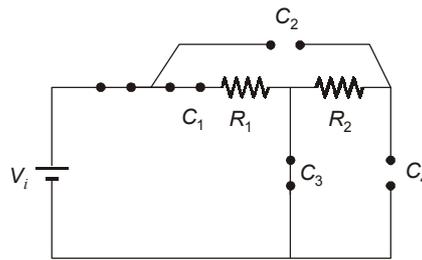

Series combination of C_2 and C_4 is connected across V_i directly. So C_2 and C_4 will charge instantly.

6. (c)

For the given circuit the transient free condition can be obtained as

$$\omega t_0 = \tan^{-1}\left(\frac{1}{\omega RC}\right) + \frac{\pi}{2}$$

$$\therefore \omega = 2 \text{ rad/sec}, \quad R = 1 \Omega \text{ and } C = \frac{1}{2} F$$

$$2t_0 = \tan^{-1}\left(\frac{1}{2 \times 1 \times \frac{1}{2}}\right) + \frac{\pi}{2} = \frac{\pi}{4} + \frac{\pi}{2}$$

or
$$t_0 = \frac{3\pi}{2 \times 4} = 1.178 \text{ sec.}$$

7. (d)

$$V_L = L \frac{di}{dt}$$

$$V_L(s) = L[sI_L(s) - i_L(0^+)]$$

where

$$i_L(0^+) = \lim_{s \rightarrow \infty} sI_L(s)$$

$$= \lim_{s \rightarrow \infty} s \cdot \frac{10}{s(s+2)} = 0$$

and

$$V_L(s) = s \times L \times I_L(s)$$


$$= s \times 4 \times \frac{10}{s(s+2)} = \frac{40}{(s+2)}$$

\therefore Initial voltage across the inductor is

$$\lim_{s \rightarrow \infty} sV_L(s) = \lim_{s \rightarrow \infty} \frac{s \times 40}{(s+2)} = 40 \text{ V}$$

8. (d)

Converting the network into s-domain

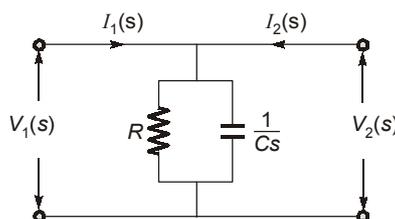

$$V_2(s) = I_1(s) \left(\frac{R \times \frac{1}{Cs}}{R + \frac{1}{Cs}} \right)$$

or
$$\frac{V_2(s)}{I_1(s)} = \frac{R}{RCs + 1} = \frac{1}{\left(s + \frac{1}{RC}\right)}$$

∴
$$Z_{21}(s) = \frac{V_2(s)}{I_1(s)} = \frac{1}{\left(s + \frac{1}{RC}\right)} = \frac{1}{1(s + 1)}$$

$$Z_{21}(s) = \frac{1}{(s + 1)}$$

9. (c)

At node-1

$$i + 49i = \frac{V_1}{25}$$

$$50i = \frac{V_1}{25}$$

$$50 \left(\frac{10 - V_1}{100 \times 10^3} \right) = \frac{V_1}{25}$$

$$V_1 = 0.123$$

at node-2

$$49i = \frac{10 - V_2}{1 \times 10^3}$$

$$49 \left(\frac{10 - V_1}{100 \times 10^3} \right) = \frac{10 - V_2}{1 \times 10^3}$$

$$49 \left(\frac{10 - 0.123}{100 \times 10^3} \right) = \frac{10 - V_2}{1 \times 10^3}$$

$$V_2 = 5.16 \text{ V}$$

10. (c)

$$P = P_0 + P_1 + P_2$$

$$= 4^2 \times 20 + \left(\frac{5}{\sqrt{2}} \right)^2 \times 20 + \left(\frac{3}{\sqrt{2}} \right)^2 \times 20$$

$$= (16 + 12.5 + 4.5) \times 20 = 660 \text{ W}$$

$$\left[\because I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} \right]$$

11. (a)

The impedance Z will be

$$Z = 4j + \frac{4j \times 4}{4j + 4} - \frac{j}{\omega C}$$

$$= -\frac{j}{\omega C} + 4j + \frac{j16(4 - 4j)}{32}$$



$$= -\frac{j}{\omega C} + 4j + 2j + 2 = -\frac{j}{\omega C} + 6j + 2$$

For the power factor to be unity, reactive part of impedance must be zero

$$\frac{1}{\omega C} = 6$$

$$C = \frac{1}{6\omega} = \frac{1}{6 \times 314} = 530.78 \mu\text{F}$$

12. (b)

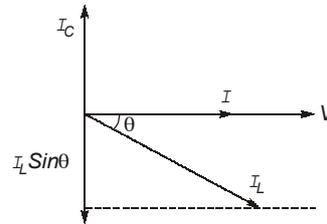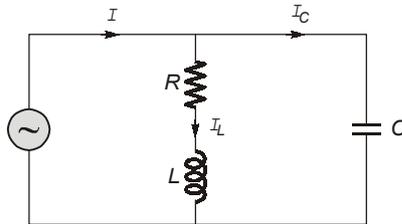

$$\text{where } \theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$I_C = \omega C \cdot V$$

$$I_L = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + \omega L^2}}$$


For power factor to be unity

$$I_C = I_L \sin \theta$$

$$\omega C V = \frac{V}{\sqrt{R^2 + (\omega L)^2}} \times \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}}$$

$$C = \frac{L}{R^2 + (\omega L)^2}$$

13. (d)

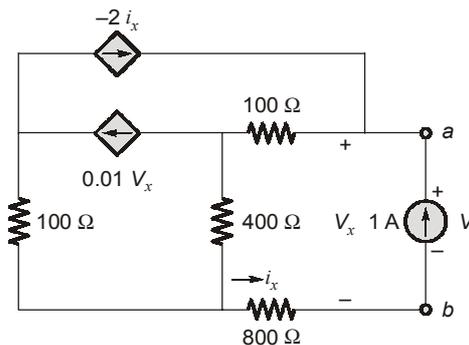

$$V = 100(1 - 2i_x) + 400(1 - 2i_x - 0.01V_x) + 800i_x$$

$$i_x = 1 \text{ A and } V_x = V$$


$$5V = 1300 - 1000 = 300$$

\therefore
and

$$V = 60 \text{ V}$$

$$R_{\text{TH}} = 60 \Omega$$

14. (c)

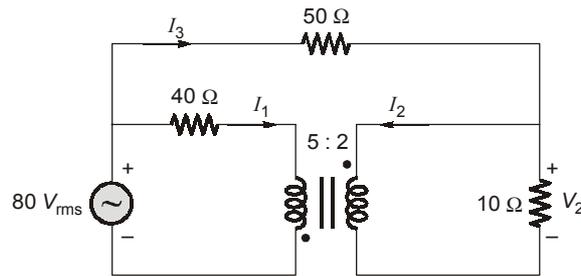

$$V_1 = 2.5 V_2$$

$$I_1 = 0.4 I_2, \quad I_3 = I_2 + \frac{V_2}{10}$$

$$80 = 40 (0.4 I_2) - 2.5 V_2 \quad \dots (i)$$

$$80 = 50 I_3 + V_2$$

$$80 = 50 (I_2 + 0.1 V_2) + V_2 \quad \dots (ii)$$

⇒

From (i) and (ii)

$$V_2 = -12.31 \text{ V}$$

15. (d)

The h -parameter

$$V_1 = 2I_1 + 4V_2$$

$$I_2 = -5I_1 + 2V_2$$

Power dissipated in R_L

$$P_L = \frac{V_2^2}{R_L} = 25 \text{ W}$$

$$\therefore V_2 = \sqrt{25 \times 4} = 10 \text{ V}$$

$$\therefore V_2 = -I_2 R_L$$

$$\therefore I_2 = -2.5 \text{ A}$$

substituting the values

we get

$$V_1 = 2I_1 + 40$$

$$-2.5 = -5I_1 + 20$$

$$\therefore I_1 = 4.5 \text{ A} \quad \text{and} \quad V_1 = 49 \text{ V}$$

$$\therefore I_1 = \frac{V_s - V_1}{2} = 4.5$$

$$\Rightarrow V_s = 58 \text{ V}$$

16. (c)

$$P_x = \frac{1}{T} \int_{\langle T \rangle} |x(t)|^2 dt$$

$$= \frac{1}{T} \int_0^{\alpha T} \left(\frac{3}{\alpha T} t \right)^2 dt$$

$$= \frac{1}{T} \int_0^{\alpha T} \frac{9t^2}{\alpha^2 T^2} dt$$

$$= \frac{9}{\alpha^2 T^3} \left(\frac{t^3}{3} \right)_0^{\alpha T} = \frac{3}{\alpha^2 T^3} (\alpha^3 \cdot T^3)$$

$$P_x = 3\alpha = 3\left(\frac{2}{3}\right) = 2 \text{ Watt}$$

17. (b)

Given,

$$\begin{aligned} f_0 &= 5 \text{ kHz} \\ Z &= Z_{\text{source}} + Z_{\text{load}} \\ &= 2 + j4 + 10 - jX_C \\ &= [12 + j(4 - X_C)] \Omega \end{aligned}$$

at resonance, imaginary part of Z is zero.


$$\therefore X_L = X_C$$

$$\therefore X_C = \frac{1}{\omega_0 C} = 4$$

$$\text{or } C = 7.95 \mu\text{F}$$

As at resonance current is maximum and thus, maximum power transferred to R .

18. (b)

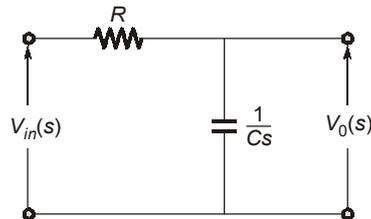

$$\frac{V_0}{V_i} = \frac{1}{1 + j\omega CR}$$

$$\tan\theta = \omega RC$$

$$\tan(30^\circ) = \omega RC$$

$$R = \frac{1}{\sqrt{3}\omega C}$$

$$\frac{1}{\omega C} = \sqrt{3}R$$

$$Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

$$Z = \sqrt{R^2 + (\sqrt{3}R)^2} = 2R$$

$$R = \frac{Z}{2} = \frac{250}{2} = 125 \Omega$$

$$C = \frac{1}{\sqrt{3}\omega R} = 14.7 \mu\text{F}$$

19. (c)


When switch is at position 'A'

$$i_1(t) = \frac{10}{10k} = 1 \text{ mA}$$

when switch is at position 'B'

$$i_2(t) = \frac{10}{20} = 0.5 \text{ mA}$$


∴

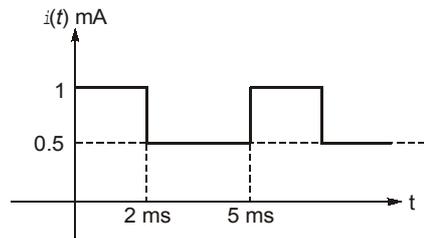

Average value

$$\begin{aligned} i_{av}(t) &= \frac{1}{5} \int_0^5 i(t) dt = \frac{1}{5} \left\{ \int_0^2 1 dt + \int_2^5 0.5 dt \right\} \\ &= \frac{1}{5} (1 \times 2 + 0.5 \times 3) = 0.7 \text{ mA} \end{aligned}$$

20. (c)

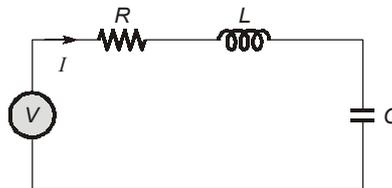

For series RLC circuit,

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

The circuit current

$$I = \frac{V}{Z}$$

∴ The drop across the capacitor C

$$V_C = IX_C = \frac{V}{Z} X_C$$

i.e.

$$V_C^2 = \frac{V^2 X_C^2}{Z^2} = \frac{V^2}{(\omega C)^2 \left[R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right]}$$

For maximum voltage drop

$$\begin{aligned} V_{C_{\max}} &= \frac{dV_C}{d\omega} = 0 \\ &= \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}} \text{ rad/sec} \end{aligned}$$

21. (d)

$$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned}$$

For Lattice network

$$Z_{11} = \frac{Z_1 + Z_2}{2} = Z_{22}$$

and
$$Z_{21} = Z_{12} = \frac{Z_1 - Z_2}{2}$$

from h parameters

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$\therefore h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

from Z -parameter model

$$h_{12} = \frac{V_1}{V_2} = \frac{Z_{12}}{Z_{22}} = \frac{Z_1 - Z_2}{Z_1 + Z_2}$$

Hence option (d) is the correct answer.

22. (c)

Condition for Transient free response is given by

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta + \frac{\pi}{2}$$

here,
$$\omega = \frac{1}{2}, \quad \theta = 45^\circ$$

$$\frac{t_0}{2} = \tan^{-1}\left(\frac{\frac{1}{2} \times 2}{1}\right) - \frac{\pi}{4} + \frac{\pi}{2}$$

$$\frac{t_0}{2} = \frac{\pi}{2}$$

$$t_0 = \pi = 3.1416 \text{ sec}$$

23. (a)

Using KCL

$$100 = R \frac{dQ}{dt} + \frac{Q}{C}$$

$$100 C = RC \frac{dQ}{dt} + Q$$

$$\int_{Q_0}^Q \frac{dQ}{100C - Q} = \frac{1}{RC} \int_0^t dt$$

$$(-\ln(100C - Q))_{Q_0}^Q = \frac{t}{RC}$$

$$\ln \frac{(100C - Q)}{(100C - Q_0)} = -\frac{t}{RC}$$

$$100C - Q = (100C - Q_0)e^{-t/RC}$$


$$i = \frac{dQ}{dt} = \left(\frac{100C - Q_0}{RC}\right)e^{-t/RC} = \left(\frac{50 - 10}{1}\right)e^{-t/RC}$$

$$i = 40 e^{-t/RC}$$

at $t = 2 \text{ sec}$

$$i = 40 e^{-2} = 5.413 \text{ A}$$

24. (a)

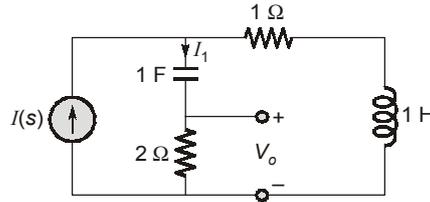


$$I_1(s) = \frac{I(s)(1+s)}{\frac{1}{s} + 2 + 1 + s} = \frac{I(s)(s+1)s}{s^2 + 3s + 1}$$

$$V_o(s) = 2I_1(s) = \frac{I(s)2s(s+1)}{s^2 + 3s + 1}$$

$$\frac{V_o(s)}{I(s)} = \frac{2s(s+1)}{s^2 + 3s + 1}$$

25. (b)

Redrawing the circuit

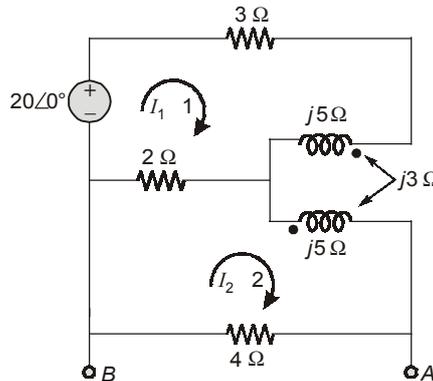

Applying Mesh Law

Mesh I

$$3I_1 + j5I_1 + j3I_2 + 2I_1 - 2I_2 = 20\angle 0^\circ$$

$$(5 + j5)I_1 + (-2 + j3)I_2 = 20\angle 0^\circ \quad \dots(i)$$

Mesh II

$$2I_2 + j5I_2 + j3I_1 + 4I_2 - 2I_1 = 0$$


$$(6 + j5)I_2 + (-2 + 3j)I_1 = 0 \quad \dots(ii)$$

From equations (i) and (ii)

$$I_1 = 2.30\angle -41.70^\circ \quad I_2 = 1.064\angle -137.8^\circ$$

$$V_{Th} = V_{AB} = I_2 \times (4) = 4.256\angle -137.8^\circ$$

26. (c)

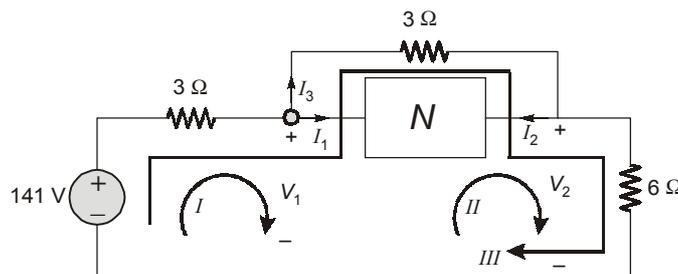

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 & 1 \\ 1 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow \begin{aligned} V_1 &= 2I_1 + I_2 \\ V_2 &= I_1 + 4I_2 \end{aligned}$$

Applying KVL

Loop I

$$\begin{aligned} 3(I_1 + I_3) + V_1 &= 141 \\ 3I_1 + 3I_3 + 2I_1 + I_2 &= 141 \\ 5I_1 + I_2 + 3I_3 &= 141 \end{aligned} \quad \dots(i)$$

Loop II

$$\begin{aligned} V_2 &= (I_3 - I_2) \cdot 6 \\ V_2 &= I_1 + 4I_2 \\ I_1 + 4I_2 &= 6I_3 - 6I_2 \\ I_1 + 10I_2 - 6I_3 &= 0 \end{aligned} \quad \dots(ii)$$


Loop III

$$\begin{aligned} 3(I_1 + I_3) + 3I_3 + 6(I_3 - I_2) &= 141 \\ 3I_1 - 6I_2 + 12I_3 &= 141 \end{aligned} \quad \dots(iii)$$

By equation (i), (ii) and (iii)


$$I_1 = 24 \text{ A} \quad I_2 = 1.5 \text{ A} \quad I_3 = 6.5 \text{ A}$$

27. (a)
 Z_{Th} :

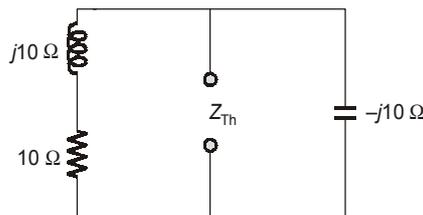

$$Z_{Th} = \frac{(10 + j10)(-j10)}{10 + j10 - j10} = 10 - j10$$

V_{Th} :

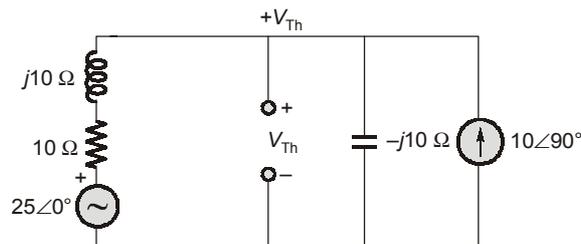

$$\frac{V_{Th} - 25}{10 + j10} + \frac{V_{Th}}{-j10} = 10 \angle 90^\circ$$

$$\frac{V_{Th}}{10 + j10} - \frac{25}{10 + j10} - \frac{V_{Th}}{j10} = 10j$$

$$(V_{Th})j10 - 25j - 10V_{Th} - 10jV_{Th} = -100(10 + 10j)$$

$$j10V_{Th} - 25j - 10V_{Th} - 10jV_{Th} = -1000(1 + j)$$

$$-10V_{Th} = -1000 - 1000j + 25j$$

$$-10V_{Th} = -1000 - 750j$$


$$V_{Th} = 100 + j75$$

$$Z_L = Z_{Th}^* = 10 + j10$$

$$P_{\max} = \frac{|V_{Th}|^2}{4\text{Re}\{Z_{Th}\}} = \frac{(\sqrt{100^2 + 75^2})^2}{4 \times 10} = 390.625 \text{ W}$$


28. (b)
at $t = 0^-$

$$v_C = I \times R_2$$

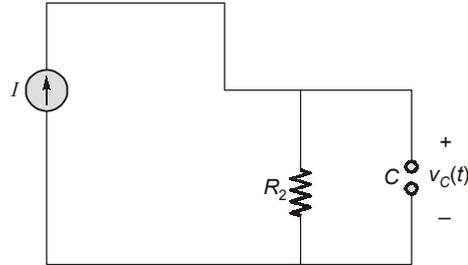

at $t = 0^+$

$$v_C(0^-) = v_C(0^+) = IR_2$$

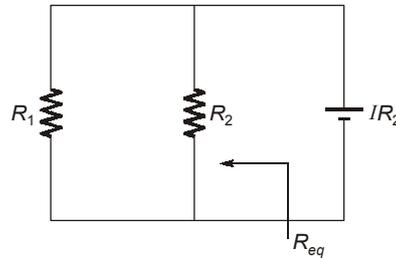

$$v_C(\infty) = 0$$

(\because capacitor will discharge fully)

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$v_C(t) = [v_C(0) - v_C(\infty)] e^{-\frac{t}{\tau}} + v_C(\infty)$$

$$v_C(t) = IR_2 \cdot e^{-\frac{t(R_1 + R_2)}{R_1 R_2 C}} \text{ Volts}$$

29. (c)

$$Y_L = \frac{1}{R_L + jX_L} = \frac{1}{10 + j10} \text{ mho}$$

$$= \frac{10 - j10}{1 + j10} = \frac{10}{200} - j\frac{10}{200}$$

and $Y_C = \frac{1}{R_C - j2} = \frac{R_C + j2}{R_C^2 + 4} \text{ mho}$

at resonance, imaginary part of Y_L must be equal to Y_C

i.e. $-j \times \frac{10}{200} + j \frac{2}{R_C^2 + 4} = 0$


$$\Rightarrow \frac{10}{200} = \frac{2}{R_C^2 + 4}$$

$$10R_C^2 + 40 = 400$$


$$R_C^2 = \frac{360}{10}$$

$$R_C = \sqrt{\frac{360}{10}} = 6 \Omega$$

30. (b)

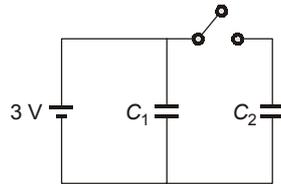At $t = 0^-$ S_1 is closed. S_2 is open C_1 gets charged upto 3 V charge stored in C_1

$$Q_0 = C_1 V = 1 \times 3 = 3 C$$

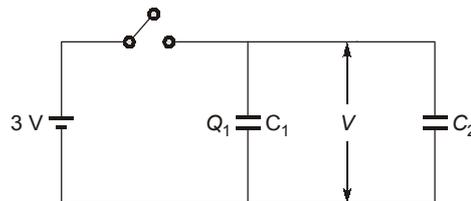Voltage across C_2 is zero at $t = 0^-$, so no charge stored in C_2 .At $t > 0$, S_1 is open and S_2 is closed.charge stored (Q_0) initially in C_1 gets redistributed between C_1 and C_2 Let Charge stored in $C_1 = Q_1$ Charge stored in $C_2 = Q_2$

According to conservation of charge

$$Q_1 + Q_2 = Q_0 = 3 \quad \dots(1)$$

Voltage across $C_1 =$ Voltage across C_2

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \Rightarrow \frac{Q_1}{1} = \frac{Q_2}{2}$$

$$Q_2 = 2Q_1 \quad \dots(2)$$

from (1) and (2)

$$Q_1 = 1 C$$

and

$$Q_2 = 2 C$$

$$\therefore \text{Voltage across the combination} = \frac{Q_1}{C_1} = \frac{1}{1} = 1V$$

