

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ANALOG ELECTRONICS

ELECTRONICS ENGINEERING

Date of Test : 22/06/2023

ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (d) | 7. (b) | 13. (c) | 19. (b) | 25. (a) |
| 2. (b) | 8. (d) | 14. (d) | 20. (a) | 26. (c) |
| 3. (d) | 9. (a) | 15. (a) | 21. (c) | 27. (c) |
| 4. (b) | 10. (c) | 16. (b) | 22. (c) | 28. (a) |
| 5. (c) | 11. (c) | 17. (a) | 23. (b) | 29. (a) |
| 6. (b) | 12. (b) | 18. (b) | 24. (b) | 30. (a) |

DETAILED EXPLANATIONS

1. (d)

When D_2 is ON then the value of V_0 will be


$$V_0 = 3 - 0.7 \text{ V} = 2.3 \text{ V}$$

Hence, D_1 will be OFF.

Thus, The current, $I = \frac{2.3 - (-3)}{5} \times 10^{-3} = \frac{5.3}{5} \times 10^{-3} = 1.06 \text{ mA}$

3. (d)

The circuit can be redrawn as,

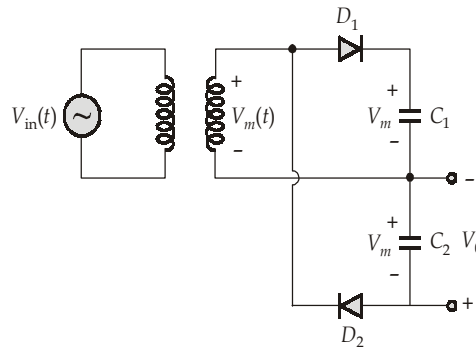

The circuit represents a voltage doubler circuit, if the voltage was taken by adding voltages of both the capacitors, but to calculate V_0 we have to find the voltage stored on a single capacitor.

Thus, comparing from the above figure,

$$V_0 = -V_m$$

4. (b)

$$V_{GS} - V_t = 2 - 1.5 = 0.5 \text{ V}$$

and

$$V_{DS} = 1 \text{ V}$$

$$\therefore V_{DS} > V_{GS} - V_t$$

Hence, MOSFET is in saturation region.

5. (c)

For a fixed biased circuit,

$$I_C = \beta I_B + (\beta + 1) I_{co}$$

$$\therefore \frac{\partial I_C}{\partial I_{co}} = (\beta + 1) \quad \left[\because I_B = \frac{V_{CC} - V_{BE}}{R_B} = \text{constant} \right]$$

$$\therefore S = \frac{\partial I_C}{\partial I_{co}} = 100 + 1 = 101$$

6. (b)

The early voltage V_A can be calculated as

$$V_A = r_0 I_C$$


where r_0 = output resistance = $\frac{1}{\text{slope of } I_C - V_{CB} \text{ curve}}$

$$r_0 = \frac{1}{3 \times 10^{-5}}$$

thus, $V_A = \frac{1}{3 \times 10^{-5}} \times 3 \times 10^{-3} = 100 \text{ V} \quad (\because I_C = 3 \times 10^{-3} \text{ A})$

8. (d)

The circuit can be redrawn as,

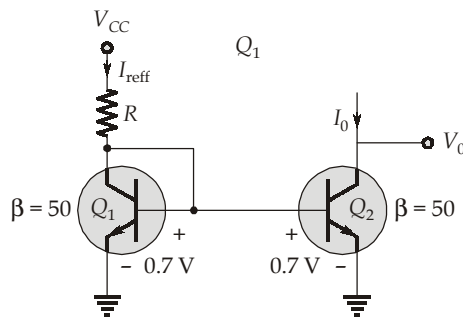

For current mirror circuit,

$$I_{\text{ref}} = \frac{V_{CC} - V_{BE}}{R} = \frac{10 - 0.7}{37 \times 10^3} = 0.251 \text{ mA}$$

now,

$$I_0 = \frac{I_{\text{ref}}}{\left(1 + \frac{2}{\beta}\right)} = \frac{0.251}{\left(1 + \frac{2}{50}\right)} = 0.241 \text{ mA}$$

9. (a)

Since, the op-amp represents a closed loop unity gain amplifier.


Thus,

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}}$$

$$= \frac{999}{1 + 999} = 0.999$$

10. (c)

In the given circuit

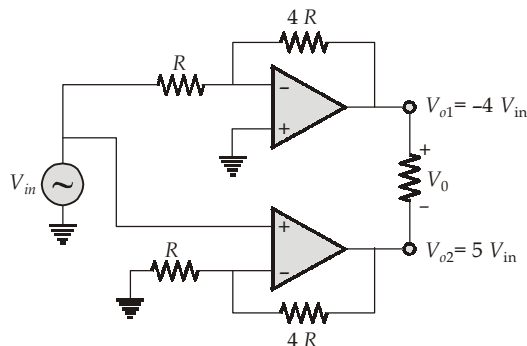


$$\begin{aligned} \therefore V_o &= V_{o1} - V_{o2} \\ &= -4 V_{in} - 5 V_{in} \\ &= -9 V_{in} \end{aligned}$$

$$\therefore \frac{V_o}{V_{in}} = -9$$

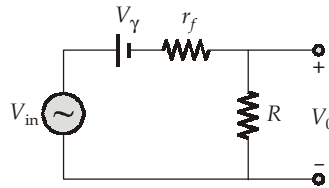11. (c)

The small signal equivalent model can be drawn as



∴ The output can be expressed as,

$$V_0 = \frac{R}{R + r_f} V_{in} - \frac{R}{R + r_f} V_\gamma \quad \dots(i)$$

Thus, the slope of line in the graph of the input output curve can be written

$$\text{Slope} = \frac{R}{R + r_f} = \frac{1.2}{2 - 0.7} = \frac{1.2}{1.3} \quad \dots \text{from equation (i)}$$

Thus,

$$r_f = 83.33 \, \Omega$$

12. (b)

In the transistor $V_{GS} = V_{DS}$


Since, the gate and drain terminals are shorted, the transistor will always be in saturation mode.

$$\text{thus,} \quad I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$\text{now,} \quad I_D = \frac{V_0}{R} = \frac{3}{3} \times 10^{-3} = 1 \text{ mA}$$

$$\begin{aligned} \text{thus,} \quad 1 \times 10^{-3} &= \frac{50 \times 10^{-3}}{2} \left(\frac{W}{L} \right) \times (2 - 1)^2 \\ \left(\frac{W}{L} \right) &= \frac{1}{25} = 0.04 \end{aligned}$$

13. (c)

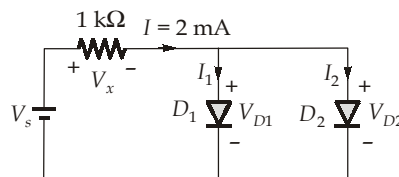

$$V_s = V_x + V_{D1} \quad (\because V_{D1} = V_{D2})$$

and

$$I = I_1 + I_2$$

thus

$$2 \times 10^{-3} = 10^{-12} \left[e^{\frac{V_{D1}}{26 \times 10^{-3}}} - 1 \right] + 10^{-10} \left[e^{\frac{V_{D1}}{26 \times 10^{-3}}} - 1 \right]$$

$$2 \times 10^{-3} \approx 10^{-10} (1.01) \cdot e^{\frac{V_{D1}}{26 \times 10^{-3}}}$$

$$\frac{V_{D1}}{26 \times 10^{-3}} = \ln(1.9801 \times 10^7) = 16.801$$

∴

$$V_{D1} = 0.437 \text{ V}$$

Now,

$$V_x = 2 \times 10^{-3} \times 1 \times 10^3 = 2 \text{ V}$$

$$V_s = V_x + V_{D1} = 2 + 0.437$$

$$= 2.437 \text{ V}$$

14. (d)

Assuming the transistor to be in active region, we get,

$$I_C = \alpha I_E = \frac{\beta}{1+\beta} \cdot I_E = \frac{60}{61} \times 0.61 \times 10^{-3}$$

$$= 0.6 \text{ mA}$$

Now, the voltage at $V_C = -10 + 4.7 \times 0.6 = -7.18 \text{ V}$

$$\text{Value of } I_B = \frac{I_C}{\beta} = \frac{0.6}{60} \times 10^{-3} = 1 \times 10^{-5} \text{ A} = 10 \mu\text{A},$$

now,

$$V_B = I_B R_B$$

$$= 10 \times 10^{-6} \times 50 \times 10^3 = 0.5 \text{ V}$$

$$\therefore V_E = V_B + V_{EB} = 0.5 + 0.7 = 1.2 \text{ V}$$

$$V_{EC} = 1.2 - (-7.18) = 8.38 \text{ V}$$

$$\therefore \text{Power dissipated} = V_{EC} \times I_C = 8.38 \times 0.6 \times 10^{-3} \approx 5.028 \text{ mW}$$

15. (a)

The current of both the transistors are equal since they are perfectly matched.

Thus,

$$\frac{I}{2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS1} - V_t)^2$$

$$10 \times 10^{-3} = \frac{1}{2} \times 500 \times 10^{-6} \times 100 (V_{GS1} - 0.5)^2$$


$$\therefore V_{GS1} = V_{GS2} = 1.132 \text{ V}$$

Thus,

$$V_S = V_{cm} - V_{GS1} = 3 - 1.132 = 1.868 \text{ V}$$

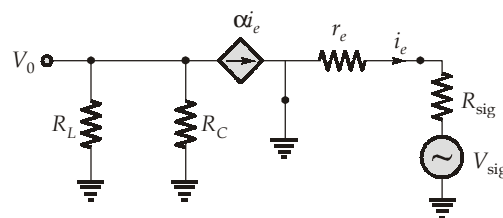16. (b)

The small signal r_e equivalent circuit can be drawn as



$$V_0 = -\alpha (R_C \parallel R_L) i_e \quad \dots(i)$$

and

$$i_e = \frac{-V_{sig}}{R_{sig} + r_e} \quad \dots(ii)$$

Combining equation (i) and (ii), we get,

$$V_0 = \frac{\alpha (R_C \parallel R_L)}{R_{sig} + r_e} \cdot V_{sig}$$

thus,

$$\frac{V_0}{V_{sig}} = \frac{\alpha (R_C \parallel R_L)}{R_{sig} + r_e}$$

17. (a)


From the figure it can be seen that,

$$I_C = I_E = 0.5 \text{ mA} \quad (\because \beta \text{ is very large})$$

now,

$$g_m = \frac{I_C}{V_T} \approx \frac{I_E}{V_T} = \frac{0.5 \times 10^{-3}}{25 \times 10^{-3}} \text{ A/V} = 20 \text{ mA/V}$$

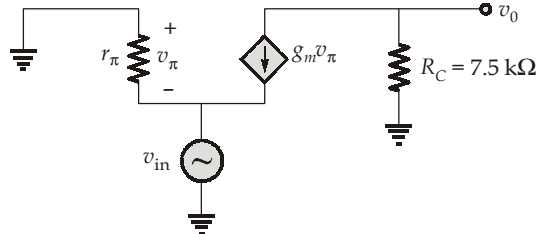Drawing the equivalent small signal circuit, we get,



Now, applying KVL, we get

$$v_{in} + v_{\pi} = 0$$

$$v_{in} = -v_{\pi}$$

and


$$v_0 = -g_m v_{\pi} \times R_C$$

$$v_0 = g_m R_C v_{in}$$

$$\frac{v_0}{v_{in}} = g_m R_C = 20 \times 10^{-3} \times 7.5 \times 10^3 = 150$$

18. (b)

Base emitter loop

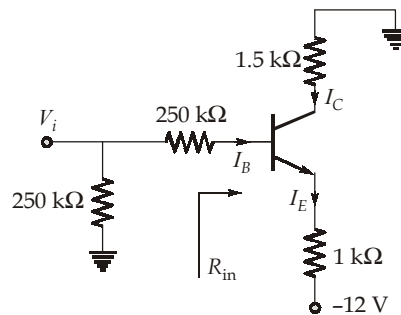

$$500k I_B + 0.7 + 1k(I_B + I_C) = 12$$

$$I_C = 100 I_B$$

$$I_E = 101 I_B$$

from here

$$I_B = 18.80 \mu\text{A}$$

$$r_{\pi} = \beta \times \frac{V_T}{I_C} = \frac{V_T}{I_B} = \frac{26}{18.8} \text{ k}\Omega = 1.383 \text{ k}\Omega$$

$$R_{in} = r_{\pi} + (1 + \beta)R_E$$

$$= 1.383k + 101 \times 1k = 102.383 \text{ k}\Omega$$

19. (b)

For the transistor

$$V_S = V_B = V_A$$

due to virtual ground,

thus,

$$V_S = 0 \text{ V}$$

Hence,

$$I_D = \frac{0 - (-10)}{10 \times 10^3} = 1 \text{ mA}$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$\therefore V_{GS} - V_T = \sqrt{\frac{I_D}{\frac{\mu_n C_{ox} W}{2L}}}$$

$$V_{GS} - V_T = \sqrt{\frac{1 \times 10^{-3}}{\frac{0.5 \times 10^{-3}}{2}}}$$

$$V_{GS} - V_T = 2 \text{ V}$$

For the MOSFET to be in saturation region

$$V_{DS} \geq V_{GS} - V_T$$

 \therefore at the edge of saturation


$$V_{DS} = V_{GS} - V_T = 2 \text{ V}$$

$$\therefore V_S = 0$$

$$\therefore V_D = V_G - V_T$$

$$\Rightarrow V_{DD} = 2 \text{ V}$$


20. (a)

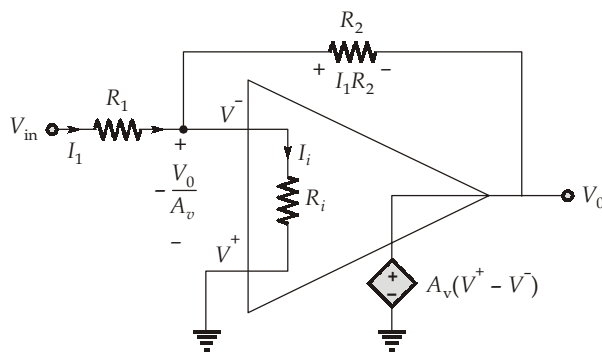 $\therefore R_i \neq \infty$ thus concept of virtual ground is not applicable for this circuit.

$$V_0 = -\frac{R_2}{R_1} \left[V_{in} + \frac{V_0}{A_v} \right] - \frac{V_0}{A_v}$$

$$V_0 = -\frac{R_2}{R_1} V_{in} - \frac{1}{A_v} \left[1 + \frac{R_2}{R_1} \right] V_0$$
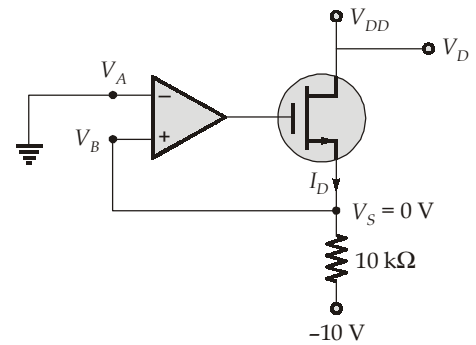
$$\therefore \frac{V_0}{V_{in}} = \frac{-\frac{R_2}{R_1}}{1 + \frac{1}{A_v} \left(1 + \frac{R_2}{R_1} \right)}$$



Thus,
$$\frac{V_0}{V_{in}} = \frac{-100/1}{1 + \frac{1}{10^3} \left(1 + \frac{100}{1} \right)} = \frac{-100}{1.1} = -90.83 \text{ V/V}$$

21. (c)

$$\text{Slew rate} = \left. \frac{dV_0}{dt} \right|_{\max}$$

$$\therefore \text{Slew rate} = A \cdot \frac{dV_0}{dt} = A \cdot \frac{d}{dt} A_m \sin(\omega t)$$

$$\text{Slew rate} = A A_m \omega$$


now,
$$A = 10^{\frac{66.0206}{20}} \approx 2000$$

$$\therefore 10 \times 10^6 = 2 \times 10^3 \times A_m \times 2\pi \times 10 \times 10^3$$

$$\therefore A_m = 79.57 \text{ mV}$$

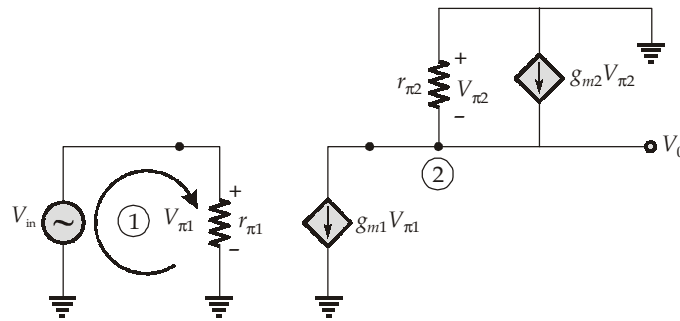22. (c)

Drawing the small signal equivalent model of the transistor, we get,



Now,

$$V_{in} = V_{\pi 1}$$

and

$$V_0 = -V_{\pi 2}$$

Applying KCL at node-2 we get

$$g_{m1} V_{\pi 1} + \frac{V_0}{r_{\pi 2}} = g_{m2} V_{\pi 2}$$

$$\Rightarrow g_{m1} V_{in} + \frac{V_0}{r_{\pi 2}} = -g_{m2} V_0$$

$$V_0 \left[\frac{1}{r_{\pi 2}} + g_{m2} \right] = -g_{m1} V_{in}$$

$$|A_v| = \left| \frac{V_0}{V_{in}} \right| = \frac{g_{m1} r_{\pi 2}}{1 + g_{m2} r_{\pi 2}}$$


Since $\beta \gg 1$ for both the transistors.

Thus, the above expression can be approximated as

$$|A_v| \approx \frac{g_{m1}}{g_{m2}}$$

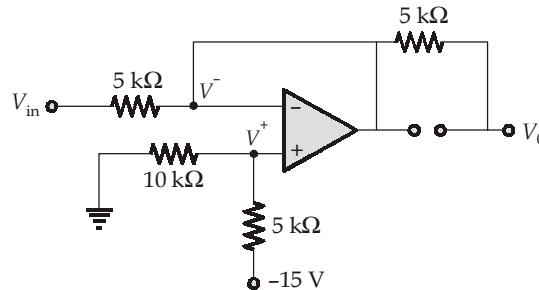23. (b)

Case -I : When $V_{in} > -10$ V, then the voltage across diode D_1 is positive so diode D_1 is in ON state, and therefore the equivalent circuit can be drawn as



$$V^+ = -15 \times \frac{10}{15} = -10 \text{ V}$$

Due to virtual ground, $V^+ = V^- = -10$ V


and $V_0 = V^- = -10$ V

$\therefore V_0 = -10$ V

Case -II : When $V_{in} < -10$ V

$$V_0 = +V_{sat}$$

Thus,

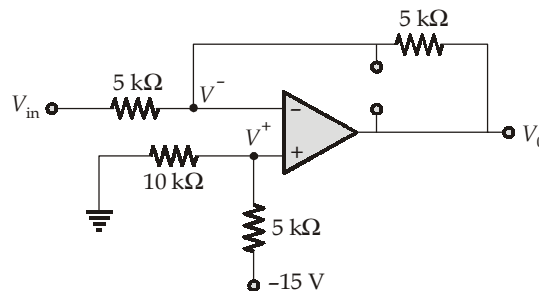

$$\therefore V_0 = -\frac{5}{5} \times V_{in} = -V_{in} \text{ (for } V_{in} < -10 \text{ V)}$$


Alternately, we can write the equation of the graph by applying KCL at node V^-

$$\therefore V^- = V^+ = -10 \text{ V}$$

$$\frac{-10 - V_{in}}{5 \text{ k}\Omega} + \frac{-10 - V_0}{5 \text{ k}\Omega} = 0$$


$$-20 - V_{in} - V_0 = 0$$

$$V_0 = -V_{in} - 20$$

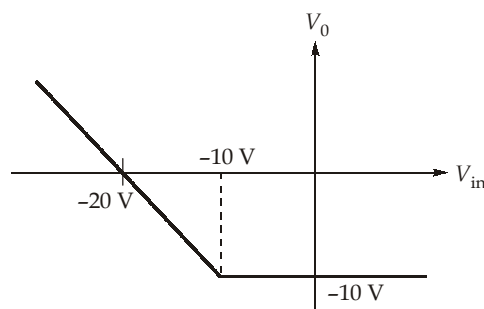

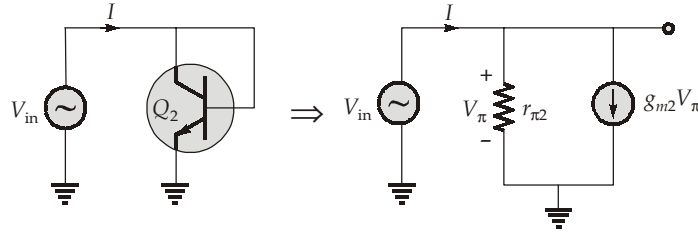24. (b)

For transistor Q_2 , we can calculate the equivalent resistance as




$$\therefore I = \frac{V_\pi}{r_{\pi 2}} + g_{m2} V_\pi$$

Now, $V_{in} = V_\pi$

$$\therefore \frac{I}{V_{in}} = \frac{1}{r_{\pi 2}} + g_{m2}$$

or $R' = r_{\pi 2} \parallel \frac{1}{g_{m2}}$

Now, the circuit can be redrawn as

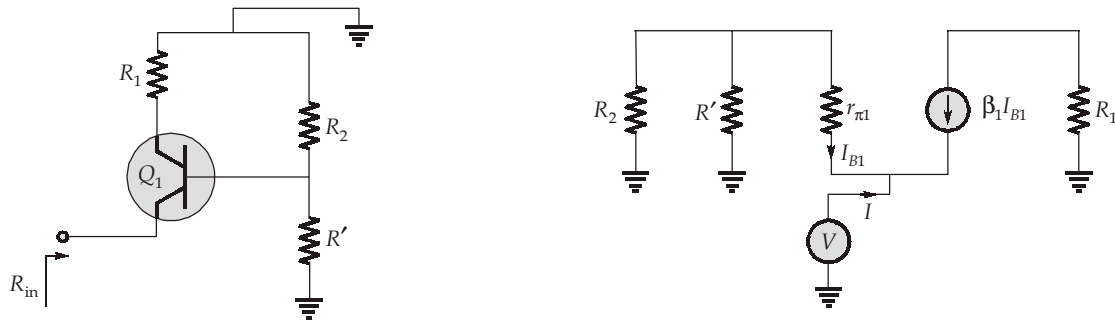

$$I = -I_{B1} - \beta_1 I_{B1}$$

$$I = -(1 + \beta_1) I_{B1}$$

Now, $I_{B1} = \frac{-V}{r_{\pi 1} + R' \parallel R_2}$

$$\therefore \frac{V}{I} = \frac{r_{\pi 1} + R' \parallel R_2}{\beta_1 + 1}$$

$$\therefore R_{in} = \frac{1}{\beta_1 + 1} \left(r_{\pi 1} + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_2 \right)$$

\therefore where, $\beta_1 = 99$

$$\therefore R_{in} = \frac{1}{100} \left(r_{\pi 1} + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_2 \right)$$

25. (a)

In the circuit, the capacitor starts charging from 0 V (as the switch was initially closed) towards the steady state value of 20 V.


Now, when the switch is flipped open, the capacitor will charge upto 20 V.

$$\therefore V_c(t) = V_c(\infty) - [V_c(0) - V_c(\infty)]e^{-t/RC}$$

$$RC = 1 \times 10^3 \times 0.01 \times 10^{-6} = 10 \mu\text{sec}$$

$$\therefore V_c(t) = 20(1 - e^{-t/RC})$$

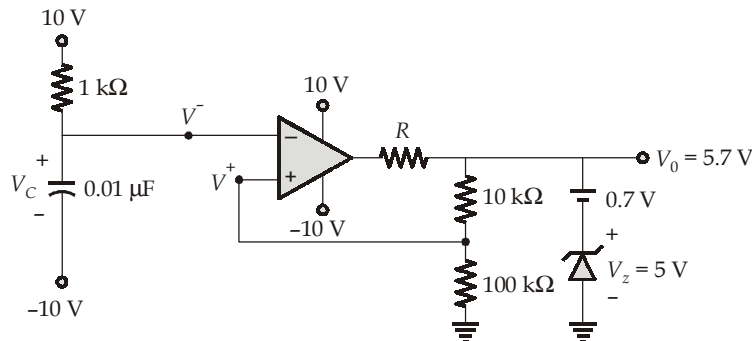Voltage at non-inverting amplifier is obtained as



$$V^+ = V_0 \times \frac{100 \text{ k}\Omega}{(10 + 100) \text{ k}\Omega}$$

$$V^+ = V_0 \times \frac{100}{110} = \frac{V_0 \times 10}{11}$$

\therefore Initially V^- was equal to -10 V , thus $V_0 = +5.7 \text{ V}$.

Thus, now capacitor will start charging as soon as the switch is opened.

$$\text{Thus, } V^- = V_c - 10 \text{ V}$$

$$\text{or, } V_c = V^- + 10 \text{ V}$$

$$\text{now, } V^- = V^+ = \frac{5.7 \text{ V} \times 10}{11} \quad [\because \text{the op-amp will switch}]$$

$$\text{thus, } V_c = \frac{10 \times 5.7}{11} + 10$$

$$\text{now, } V_c = 20(1 - e^{-t/RC})$$

$$\therefore 20(1 - e^{-t/RC}) = 10 + \frac{57}{11}$$


$$1 - e^{-t/RC} = \frac{1}{2} + \frac{57}{220}$$

$$1 - e^{-t/RC} = 0.7590$$

$$e^{-t/RC} = 0.2409$$

$$T = 14.23 \mu\text{sec}$$

Hence, the output voltage wave will be,

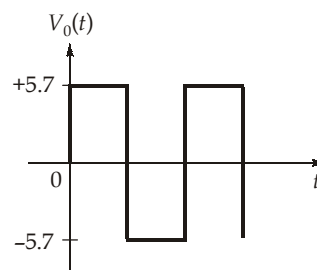


26. (c)

$$\text{Now, } g_{m1} = 2\sqrt{k_{n1}I_{D1}} = 2\sqrt{0.5 \times 0.2 \times 10^{-6}} = 0.632 \text{ mA/V}$$

$$\text{and } g_{m2} = 2\sqrt{k_{n2}I_{D2}} = 2\sqrt{(0.2)(0.5) \times 10^{-6}} = 0.632 \text{ mA/V}$$

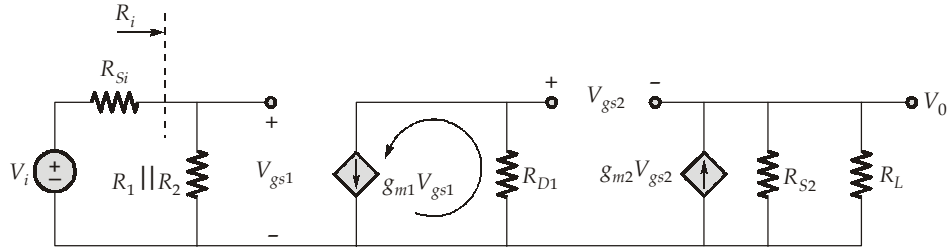Now, drawing the small signal equivalent circuit, we get,



$$\text{Now,} \quad V_0 = g_{m2}(R_{S2} \parallel R_L) \cdot V_{gs2} \quad \dots (i)$$

$$\text{Also,} \quad V_{gs2} + V_0 = -g_{m1}V_{gs1}R_{D1} \quad \dots (ii)$$

$$\text{and} \quad V_{gs1} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \times V_i \quad \dots (iii)$$

Putting values of V_{gs1} and V_{gs2} from equation (i) and (iii) in equation (ii), we get

$$\frac{V_0}{g_{m2}(R_{S2} \parallel R_L)} + V_0 = -g_{m1}R_{D1} \left[\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \right] \cdot V_i$$

$$\therefore \quad A_V = \frac{V_0}{V_i} = \frac{-g_{m1}g_{m2}R_{D1}(R_{S2} \parallel R_L)}{1 + g_{m2}(R_{S2} \parallel R_L)} \times \left[\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \right]$$

$$\text{Now,} \quad R_{S2} \parallel R_L = \frac{8}{3} \text{ k}\Omega$$

$$R_1 \parallel R_2 = 99.8 \text{ k}\Omega \approx 100 \text{ k}\Omega$$

$$\therefore \quad A_v = \frac{V_0}{V_i} = \frac{-(0.632)(0.632)(16.1)(8/3)}{1 + (0.632)(8/3)} \times \left[\frac{100}{104} \right] \approx -6.14$$

27. (c)

Assuming all the diodes are forward biased,

$$V_B = -0.7 \text{ V}$$

$$V_A = 0 \text{ V}$$

$$\therefore \quad I_2 = \frac{10 - 0}{10 \text{ k}} = 1 \text{ mA}$$

$$\text{and} \quad I_1 = \frac{-0.7 - (-10)}{10 \text{ k}} = 0.93 \text{ mA}$$

$$\therefore \quad I_2 = I_{D1} + I_{D2}$$


$$\text{and} \quad I_1 = I_{D2} + I_{D3}$$

applying KVL in the outer loop, we get,

$$10 \text{ k}I_2 + 0.7 + 10 \text{ k}I_{D1} - 20 = 10$$

$$10 \text{ k}(I_{D1} + I_{D2}) + 10 \text{ k}I_{D1} = 30 - 0.7 = 29.3$$
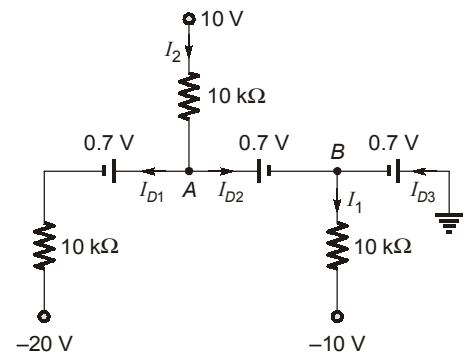
$$20 \text{ k}I_{D1} + 10 \text{ k}I_{D2} = 29.3$$



$$2I_{D_1} + I_{D_2} = 2.93 \text{ mA} \quad \dots(i)$$

$$\text{also, } I_{D_1} + I_{D_2} = I_2 = 1 \text{ mA} \quad \dots(ii)$$

from (i) and (ii)

$$I_{D_1} = 1.93 \text{ mA and } I_{D_2} = -0.93 \text{ mA}$$

$$\therefore I_{D_2} + I_{D_3} = 0.93 \text{ mA}$$

$$\Rightarrow I_{D_3} = -I_{D_2} + 0.93 \text{ mA} = 1.86 \text{ mA}$$

Here I_{D_2} is negative, Hence, our assumption is incorrect.


Therefore, D_2 is reverse biased

and $\therefore I_{D_1}$ and I_{D_3} are positive,

D_1, D_3 are forward biased.

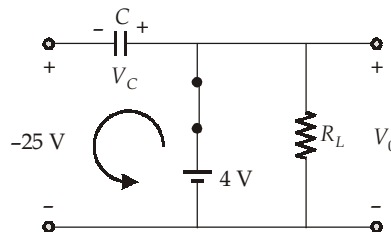28. (a)

The diode will get forward biased when the negative value of input wave will be applied at the input terminal.



Applying KVL, we get,


$$-4 \text{ V} + V_C - 25 \text{ V} = 0$$

$$V_C = 29 \text{ V}$$

and

$$V_0 = 4 \text{ V}$$

For positive cycle

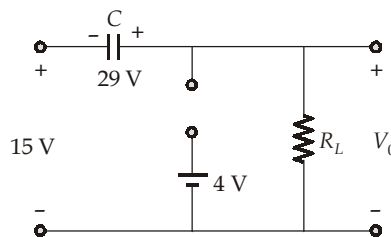

$$\therefore V_0 = 29 + 15 = 44 \text{ V}$$

29. (a)

$$I_z + I_B = I_1$$

$$I_z = I_1 - I_B$$

$$V_0 = V_Z - V_{BE}$$


$$= 10 - 0.7 = 9.3 \text{ V}$$

and

$$I_E = \frac{V_0}{1 \text{ k}\Omega} = \frac{9.3 \text{ V}}{1 \text{ k}\Omega} = 9.3 \text{ mA}$$

now,
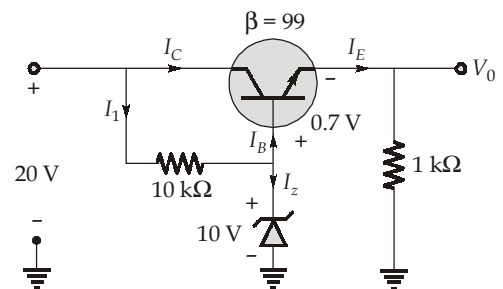
$$I_B = \frac{I_E}{\beta + 1} = \frac{9.3}{100} = 93 \mu\text{A}$$




$$I_1 = \frac{20 - 10}{10 \text{ k}} = 1 \text{ mA}$$

∴

$$I_z = (1000 - 93) \mu\text{A}$$

$$I_z = 907 \mu\text{A}$$

30. (a)

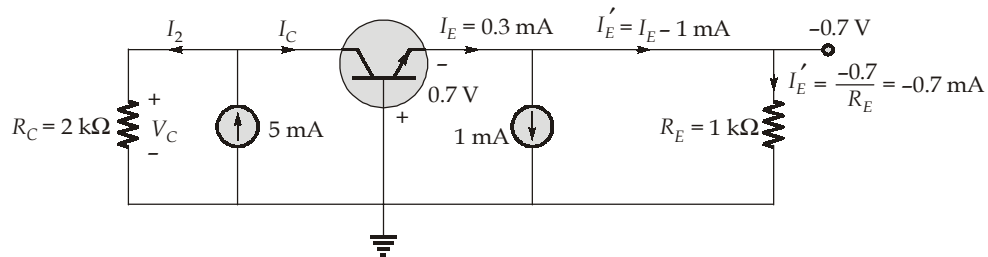

now,

$$I_E = I'_E + 1 \text{ mA}$$

$$I_E = 1 \text{ mA} - 0.7 \text{ mA} = 0.3 \text{ mA}$$

now,

$$I_C = \alpha I_E$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{99}{1 + 99} = 0.99$$

∴

$$I_C = 0.99 \times 0.3 = 0.297 \text{ mA}$$

∴

$$I_2 + I_C = 5 \text{ mA}$$

$$\begin{aligned} I_2 &= 5 \text{ mA} - I_C \\ &= 4.703 \text{ mA} \end{aligned}$$

∴

$$V_C = I_2 \cdot R_C = 4.703 \times 2$$

$$V_C = 9.406$$

∴

$$V_{CE} = 9.406 + 0.7 = 10.1 \text{ V}$$

