

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ELECTRICAL ENGINEERING

NETWORK THEORY

Duration : 1:00 hr.**Maximum Marks : 50**


Read the following instructions carefully

1. This question paper contains **30** objective questions. **Q.1-10** carry one mark each and **Q.11-30** carry two marks each.
2. Answer all the questions.
3. Questions must be answered on Objective Response Sheet (**ORS**) by darkening the appropriate bubble (marked **A, B, C, D**) using HB pencil against the question number. Each question has only one correct answer. In case you wish to change an answer, erase the old answer completely using a good soft eraser.
4. There will be **NEGATIVE** marking. For each wrong answer **1/3rd** of the full marks of the question will be deducted. More than one answer marked against a question will be deemed as an incorrect response and will be negatively marked.
5. Write your name & Roll No. at the specified locations on the right half of the **ORS**.
6. No charts or tables will be provided in the examination hall.
7. Choose the **Closest** numerical answer among the choices given.
8. If a candidate gives more than one answer, it will be treated as a **wrong answer** even if one of the given answers happens to be correct and there will be same penalty as above to that questions.
9. If a question is left blank, i.e., no answer is given by the candidate, there will be **no penalty** for that question.

DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO

Q.No. 1 to Q.No. 10 carry 1 mark each

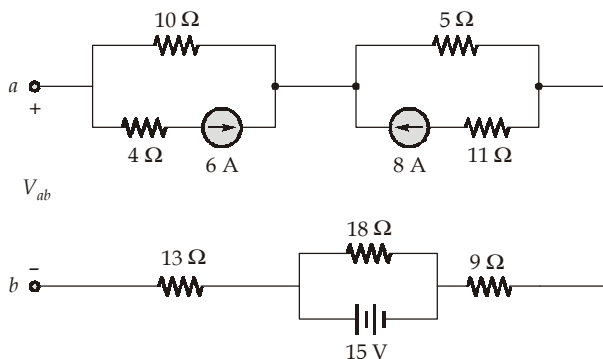
Q.1 Consider the circuit shown in the figure below:



the value of voltage V_{ab} is equal to

- (a) $V_{ab} = 25 \text{ V}$ (b) $V_{ab} = -85 \text{ V}$
 (c) $V_{ab} = -35 \text{ V}$ (d) $V_{ab} = 105 \text{ V}$

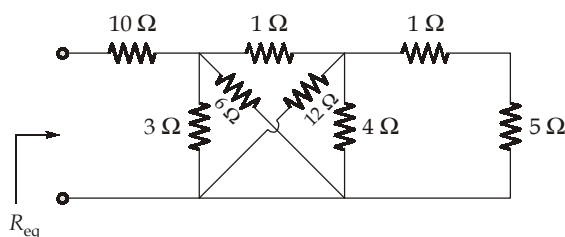
Q.2 Consider the circuit shown in the figure below:



the equivalent resistance (R_{eq}) is

- (a) 10.5Ω (b) 11.2Ω
 (c) 22.4Ω (d) 36.5Ω

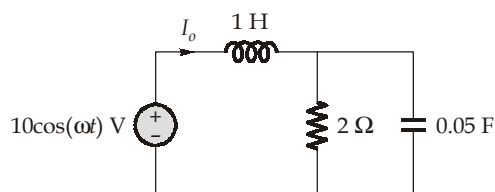Q.3 Consider the circuit shown in the figure below:




If the $I_o(j\omega)$ is current flowing in the circuit for particular value of angular frequency ω ,

then the value of $\left| \frac{I_o(j)}{I_o(5j)} \right|$ is equal to

- (a) 2.1 (b) 3.6
 (c) 4.2 (d) 8.8

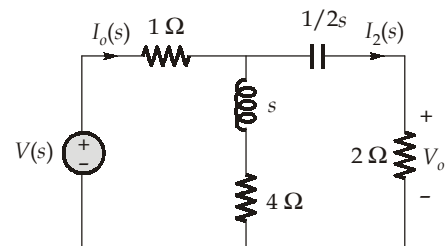
Q.4 Consider the circuit shown in the figure below:



The transfer function $H(s) = \frac{V_o(s)}{I_o(s)}$ is equal to

- (a) $\frac{4s(s+4)}{2s^2+12s+1}$ (b) $\frac{4(s+2)}{2s^2+12s+3}$
 (c) $\frac{4(s+4)}{s^2+12s+2}$ (d) $\frac{4s(s+4)}{2s^2+2s+1}$

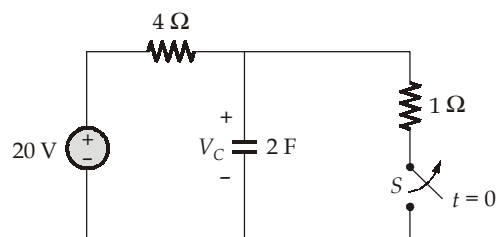
Q.5 Consider the circuit shown in the figure below:



The switch 'S' was closed for long time and then it was opened at $t = 0$, then the value of voltage V_C across the capacitor for $t > 0$ is equal to

- (a) $16 - 20 e^{-t/8} \text{ V}$ (b) $4 - 6 e^{-t/8} \text{ V}$
 (c) $20 - 16 e^{-t/8} \text{ V}$ (d) $16 - 16 e^{-t/8} \text{ V}$

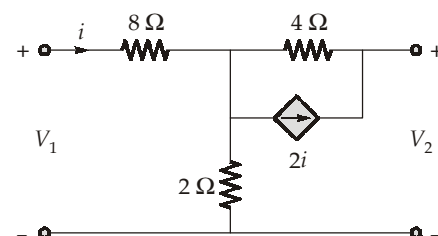Q.6 Consider the circuit shown in the figure below:




the value of Y_{21} is equal to

- (a) -0.25 s (b) -0.5 s
 (c) -0.75 s (d) -1 s


- Q.7** If the combined generator and line impedance is $(5 + j10) \Omega$, then for the maximum power transfer to a resistive load from a generator of constant generated voltage, the load resistance is given by which one of the following
- (a) 10Ω (b) 15Ω
(c) 11.18Ω (d) 5Ω

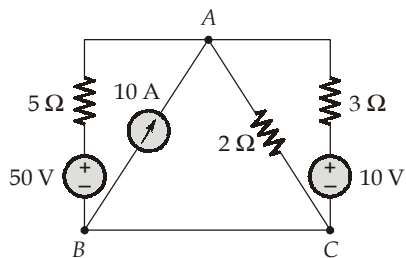- Q.8** The power delivered by the 50 V voltage source in the circuit shown below is




- (a) 274.2 W (b) 100 W
(c) 125.5 W (d) 375.5 W

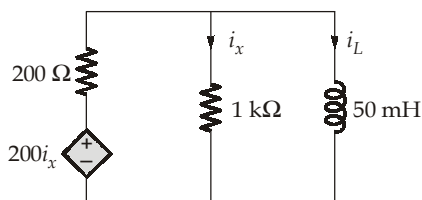- Q.9** In the circuit given below, the equivalent resistance seen by the inductor is



- (a) 100Ω (b) 200Ω
(c) 400Ω (d) 600Ω

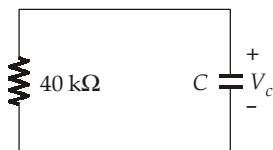- Q.10** Consider the circuit shown in figure below:




Assume $V_c(0^-) = 5 \text{ V}$. If $v_c(t) = \frac{5}{e} \text{ V}$ at $t = 0.1$

sec, then the value of C is

- (a) $1.2 \mu\text{F}$ (b) $1.5 \mu\text{F}$
(c) $2.5 \mu\text{F}$ (d) $5 \mu\text{F}$

Q. No. 11 to Q. No. 30 carry 2 marks each

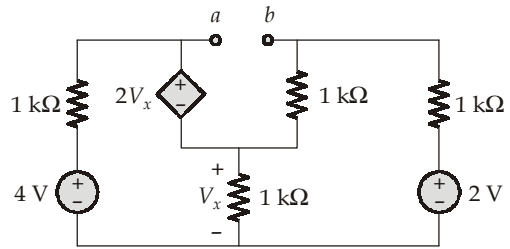
- Q.11** Consider the circuit shown in the figure below:



The value of resistance as seen from terminal ab i.e. R_{ab} is equal to

- (a) $R_{ab} = 555 \Omega$ (b) $R_{ab} = 777 \Omega$
(c) $R_{ab} = 252 \Omega$ (d) $R_{ab} = 111 \Omega$

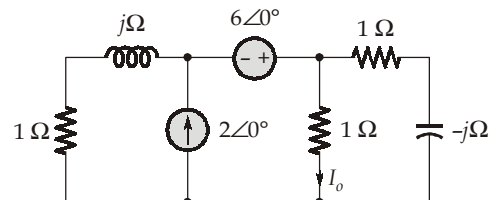
- Q.12** Consider the circuit shown in the figure below:



The value of I_o is equal to

- (a) $5.831 \angle 149.03^\circ$ (b) $2 \angle 180^\circ$
(c) $6.913 \angle 132.1^\circ$ (d) $2.915 \angle -30.96^\circ$

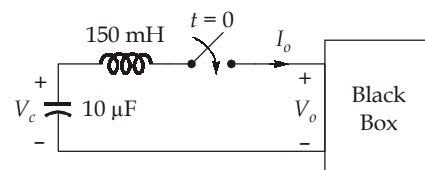
- Q.13** At $t = 0$, a series-connected capacitor and inductor are placed across the terminal of a black box as shown in the figure below:



For $t > 0$, $I_o = (200e^{-800t} - 40e^{-200t}) \text{ mA}$. If $V_c(0) = 5 \text{ V}$, then the value of V_o for $t > 0$ is equal to

- (a) $49e^{-800t} - 21.2e^{-200t}$
(b) $21.2e^{-800t} + 49e^{-200t}$
(c) $21.2e^{-800t} - 21.2e^{-200t}$
(d) $49e^{-200t} - 21.2e^{-800t}$

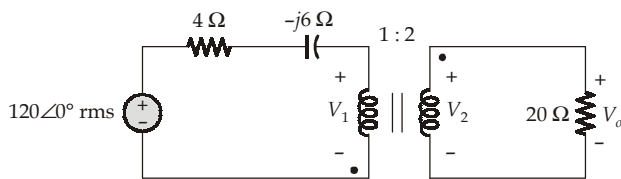
Q.14 Consider the circuit shown in the figure below:



The value of output voltage $|V_o|$ is equal to
(Assume the transformer to be ideal)

- (a) 100.2 (b) 110.9
(c) 211.4 (d) 92.6

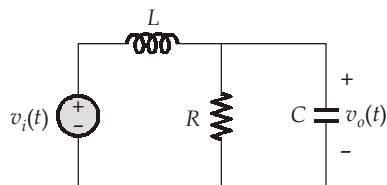
Q.15 Consider the circuit shown in the figure below:



If $R = 2 \text{ k}\Omega$, $L = 2 \text{ H}$ and $C = 2 \text{ }\mu\text{F}$, then the corner cut-off frequency for the circuit is equal to


- (a) 638 rad/s (b) 742 rad/s
(c) 845 rad/s (d) 931 rad/s

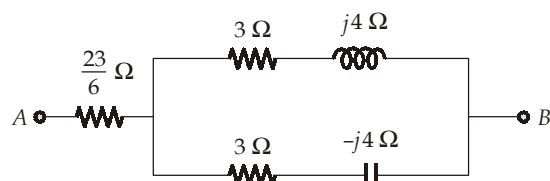Q.16 For the circuit shown below the equivalent impedance seen across the terminals A and B is



- (a) $5 \text{ }\Omega$ (b) $8 \text{ }\Omega$
(c) $j8\Omega$ (d) $(7 + j10) \text{ }\Omega$

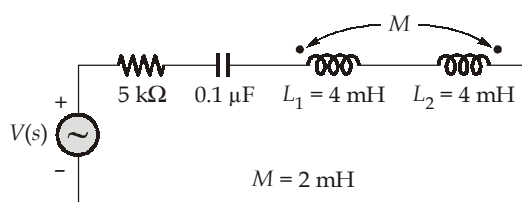Q.17 The resonant frequency of the circuit shown in the figure below is



- (a) 7.96 kHz (b) 11.58 kHz
(c) 14.76 kHz (d) 17.86 kHz


Q.18 Two identical two port networks are connected in series to form a composite network 'N'. The admittance parameter of

'N' is given by $\begin{bmatrix} 3 & 2 \\ 2 & 3 \end{bmatrix}$. The impedance

matrix for individual network is

- (a) $\begin{bmatrix} 1.5 & -1 \\ -1 & 1.5 \end{bmatrix}$
(b) $\begin{bmatrix} 0.3 & -0.2 \\ -0.2 & 0.3 \end{bmatrix}$
(c) $\begin{bmatrix} 0.2 & 0.3 \\ 0.3 & 0.2 \end{bmatrix}$
(d) $\begin{bmatrix} 3/5 & -2/5 \\ -2/5 & 3/5 \end{bmatrix}$

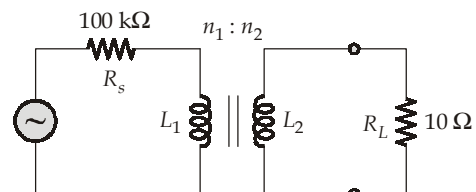Q.19 Consider the circuit shown in figure below:




For maximum power delivered to load, the

required transformer turns ratio $\left(\frac{n_1}{n_2}\right)$ is

- (a) 10 (b) 100
(c) 120 (d) 10000

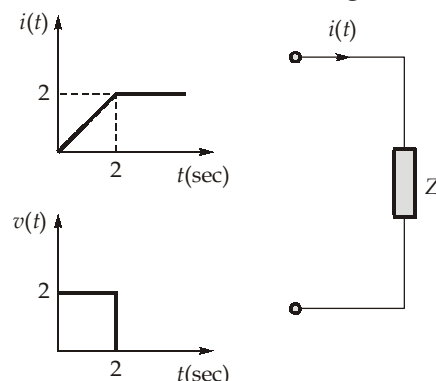
Q.20 The voltage and current waveforms for an element are shown in the figure below:



The circuit element and its values are


- (a) capacitor and 2F
(b) inductor and 1 H
(c) inductor and 2 H
(d) capacitor and 1 F

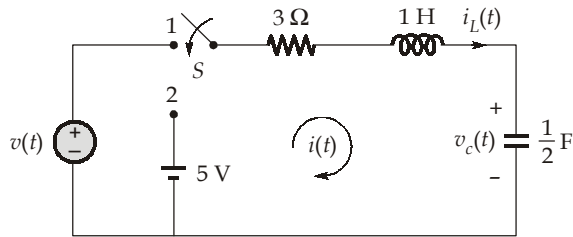- Q.21** In the figure shown below, the switch S is moved from position 1 to 2 at time $t = 0$. Just before the switch is thrown, the initial conditions are $i_L(0^-) = 2$ A and $V_c(0^-) = 2$ V. Then the current $i(t)$ for $t > 0$ is



- (a) $(e^t - e^{-2t})$ A (b) $(e^{-t} - e^{-2t})$ A
(c) $(e^{-t} + e^{-2t})$ A (d) $(e^t + e^{2t})$ A

- Q.22** In the circuit shown below:

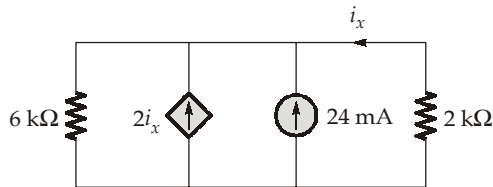


The power supplied by independent current source is

- (a) 345.6 mW (b) 425.9 mW
(c) 520.6 mW (d) 700 mW

- Q.23** The resonant frequency of a series RLC circuit is 1.5 MHz with the resonating capacitor set at 150 pF. If the bandwidth is 10 kHz, then the effective resistance of the circuit would be (approximately)
- (a) 1.25 Ω (b) 2.25 Ω
(c) 3.25 Ω (d) 4.71 Ω




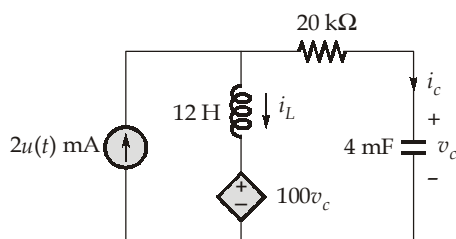
- Q.24** Consider the circuit shown below:



Then the value of $\frac{dv_c(0^+)}{dt}$ will be


- (a) 0.25 V/sec (b) 0.5 V/sec
(c) 1 V/sec (d) 2 V/sec

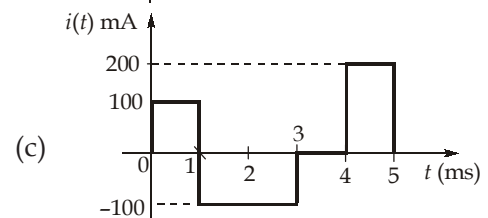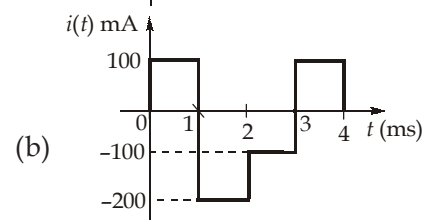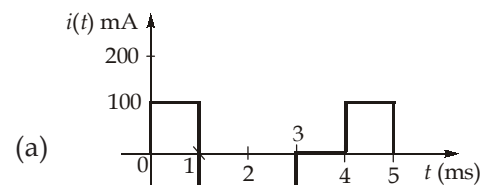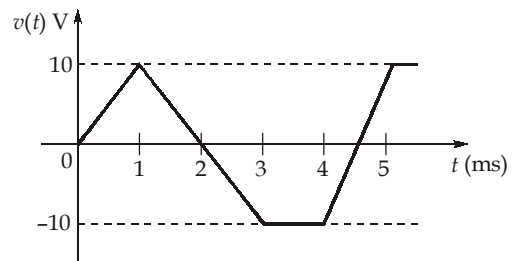- Q.25** A voltage signal $v(t)$ is applied to a capacitor with capacitance equal to 10 μ F. The voltage wave is shown in the figure below. Which of the following plot is correct for the current $i(t)$ through the capacitor?



- (d) None of these

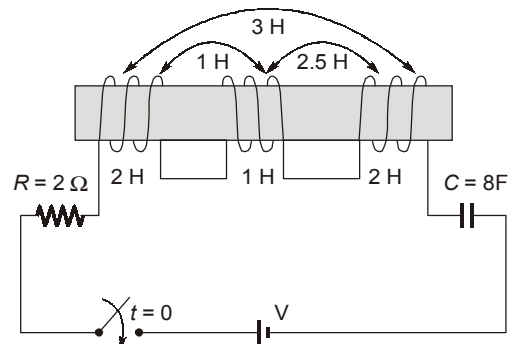
- Q.26** Consider the circuit shown in the figure below,



The value of natural frequency ω_n for the circuit is equal to


- (a) 0.18 rad/sec (b) 0.018 rad/sec
(c) 0.25 rad/sec (d) 0.025 rad/sec

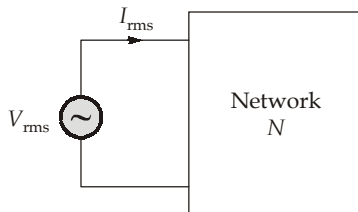- Q.27** For the circuit shown in the figure below, $V_{\text{rms}} = 100 \text{ V}$, the instantaneous power $p(t)$ dissipated by the network N has a maximum value of 1500 W and minimum value of -1000 W .



The RMS value of current I_{rms} flowing in the circuit is equal to

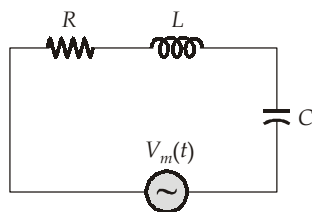
- (a) 1.25 A (b) 12.5 A
(c) 1.625 A (d) 16.25 A
- Q.28** Consider the circuit shown in the figure below:



The value of resistance $R = 2 \Omega$, $L = 1 \text{ mH}$ and capacitance $C = 0.4 \mu\text{F}$, then which of the following statement is not correct?

- (a) The resonant frequency ω_0 for the circuit is equal to 50 krad/sec .
(b) The lower half-power frequency ω_1 is equal to 49 krad/sec .
(c) The upper half-power frequency ω_2 is equal to 59 krad/sec .
(d) The quality factor ' Q ' for the circuit is equal to 25.

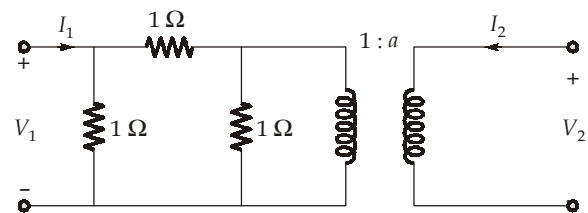- Q.29** Consider the circuit shown in the figure below:



Assuming ' a ' to be a positive non zero number, then which of the following statement is correct?

- (a) Z-parameter does not exists for all values of ' a '
(b) Z-parameter does not exists for ' a ' = 3
(c) Z-parameter does not exists for ' a ' = 8
(d) Z-parameter exists for all positive value of ' a '

- Q.30** An RLC circuit along with its phase diagram is shown in figure below,

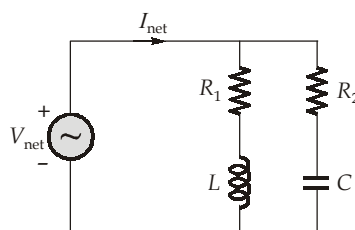


Figure -1

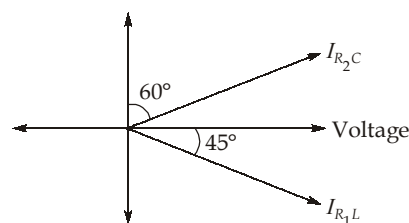


Figure -2

If $L = C$, then the minimum value of $R_1 + R_2$ is

- (a) 2.63Ω (b) 6.33Ω
(c) 21.4Ω (d) 19Ω



**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata**Web:** www.madeeasy.in | **E-mail:** info@madeeasy.in | **Ph:** 011-45124612

NETWORK THEORY

ELECTRICAL ENGINEERING

Date of Test : 02/07/2023


ANSWER KEY ➤

1. (c)	7. (c)	13. (a)	19. (b)	25. (c)
2. (b)	8. (a)	14. (b)	20. (c)	26. (a)
3. (a)	9. (b)	15. (b)	21. (c)	27. (b)
4. (a)	10. (c)	16. (b)	22. (a)	28. (c)
5. (c)	11. (b)	17. (a)	23. (d)	29. (d)
6. (a)	12. (d)	18. (b)	24. (b)	30. (a)

DETAILED EXPLANATIONS

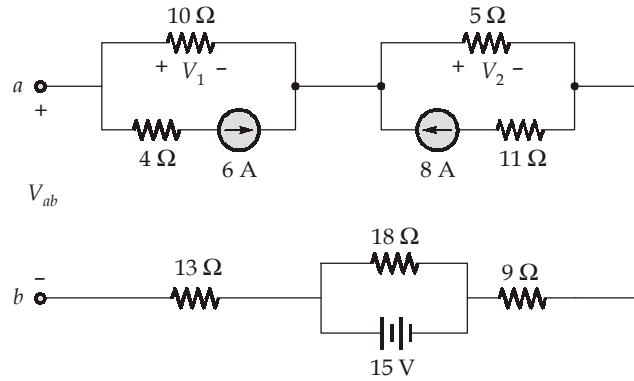1. (c)


Since terminal a and b forms is open circuit thus, no current flows through circuit is zero, thus the current only flows into the loops.



$$\begin{aligned}
 V_{ab} &= V_1 + V_2 - 15 \text{ V} \\
 \therefore V_{ab} &= (-6 \text{ A})(10 \Omega) + (8 \text{ A} \times 5 \Omega) - 15 \\
 V_{ab} &= -35 \text{ V}
 \end{aligned}$$

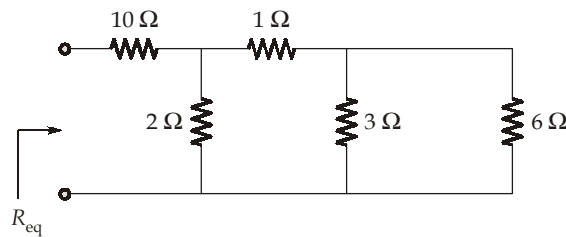2. (b)

The resistance $6 \Omega \parallel 3 \Omega$ and $12 \Omega \parallel 4 \Omega$ also 1Ω is in series with 5Ω , thus, the circuit can be redrawn as



$$\begin{aligned}
 \therefore R_{eq} &= 10 \Omega + 2 \Omega \parallel (1 + 3 \Omega \parallel 6 \Omega) \\
 R_{eq} &= 11.2 \Omega
 \end{aligned}$$

3. (a)

$$Z_L = j\omega L = j\Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(1)(0.05)} = -j20 \Omega$$

$$\therefore Z_{eq} = j + 2 \parallel (-j20) = 1.98 + j0.802 \Omega$$


$$\begin{aligned}
 \text{and } Z_L(5j) &= 5j\Omega \\
 Z_C(5j) &= -j4 \Omega
 \end{aligned}$$

$$\therefore Z_{eq}(j5) = j5 + 2 \parallel (-j4) = 1.6 + j4.2 \Omega$$

$$\text{Now, } I(j\omega) \propto \frac{1}{Z(j\omega)}$$

$$\therefore \left| \frac{I_o(j)}{I_o(j5)} \right| = \frac{Z(j5)}{Z(j)} = \left| \frac{1.6 + j4.2}{1.98 + j0.802} \right| = 2.104$$

4. (a)

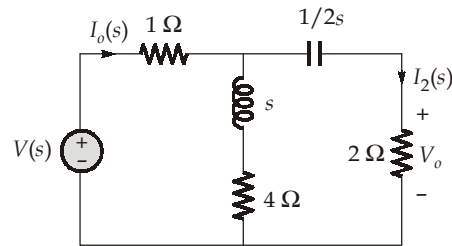

Now, applying current division rule, we get,

$$I_2(s) = \frac{(s+4)I_o(s)}{s+4+2+\frac{1}{2s}}$$

$$I_2(s) = \frac{2s(s+4)}{2s^2+12s+1} \cdot I_o(s)$$

$$V_o(s) = 2I_2(s) = \frac{4s(s+4)}{2s^2+12s+1} I_o(s)$$

$$\frac{V_o(s)}{I_o(s)} = \frac{4s(s+4)}{2s^2+12s+1}$$

5. (c)


$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)] e^{-t/\tau}$$

where, $\tau = RC = 4 \times 2 = 8$, $v(0) = 4$ V and $v_c(\infty) = 20$ V

$$\therefore v_c(t) = 20 + (4 - 20)e^{-t/8}$$

$$v_c(t) = 20 - 16 e^{-t/8} \text{ V}$$

6. (a)

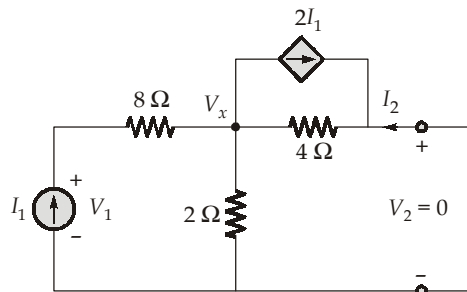

$$I_1 = \frac{V_x}{2} + \frac{V_x}{4} + 2I_1$$

$$-I_1 = 0.75V_x \quad \dots(i)$$

$$I_2 = -\frac{V_x}{4} - 2I_1 = -\frac{V_x}{4} + 1.5V_x = 1.25 V_x$$

Now,

$$V_1 = 8I_1 + V_x$$


$$V_1 = -6V_x + V_x = -5 V_x$$

$$\therefore \frac{I_2}{V_1} = \frac{-1.25}{5} = -0.25 \text{ S}$$

7. (c)

$$R_L = |Z_s^*| = |5 - j10| = \sqrt{5^2 + 10^2} = 11.18 \Omega$$

8. (a)

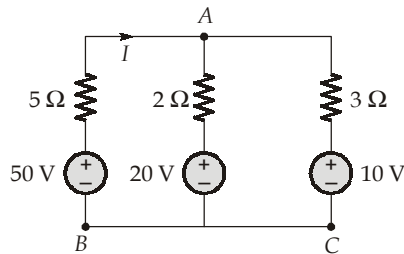

Using nodal analysis,
KCL at node 'A'

$$\frac{50 - V_A}{5} = \frac{V_A - 20}{2} + \frac{V_A - 10}{3}$$


$$V_A = 22.580 \text{ V}$$

So,
$$I = \frac{50 - 22.580}{5} = 5.483 \text{ A}$$

So, power delivered by 50 V is,

$$50 \times I = 50 \times 5.483 = 274.2 \text{ Watts}$$

9. (b)

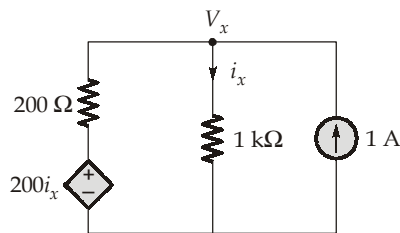

Since,
$$i_x = \frac{V_x}{1 \text{ k}\Omega} = \frac{V_x}{1000}$$

$$200i_x = 0.2V_x$$

and
$$\frac{V_x}{1000} + \frac{V_x - 0.2V_x}{200} = 1 \text{ A}$$

$$V_x = 200 \text{ V}$$

$$R_{eq} = \frac{V_x}{1 \text{ A}} = 200 \Omega$$

10. (c)

Voltage across capacitor

$$\begin{aligned} v_c(t) &= V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}})e^{-t/RC} \\ &= 0 + (5 - 0)e^{-t/RC} \end{aligned}$$

But given,
$$v_c(t) = \frac{5}{e} = 5e^{-t/RC}$$

$$\frac{5}{e} = 5e^{-(0.1/40 \text{ k}\Omega \times C)}$$


$$\frac{0.1}{40 \text{ k}\Omega \times C} = 1$$

$$\therefore C = 2.5 \text{ }\mu\text{F} \quad (\text{or}) \quad 2.5 \times 10^{-6} \text{ F}$$

11. (b)

$$R_{ab} = \frac{V_{OC}}{I_{SC}}$$

To find open circuit voltage

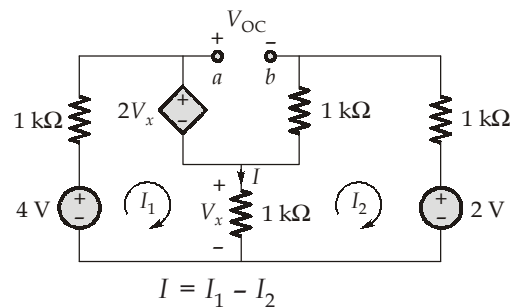

Applying KVL in loop 1, we get,

$$(1 \text{ k}\Omega)I_1 + 2V_x + I(1 \text{ k}\Omega) = 4$$

$$V_x = I(1 \text{ k}\Omega)$$

$$\therefore (4 \text{ k}\Omega)I_1 - 3 \text{ k}\Omega I_2 = 4 \quad \dots(i)$$

Applying KVL in loop 2, we get,

$$(1 \text{ k}\Omega)I_2 + (1 \text{ k}\Omega)I_2 - (1 \text{ k}\Omega)I = -2$$

$$-(1 \text{ k}\Omega)I_1 + (3 \text{ k}\Omega)I_2 = -2 \quad \dots(ii)$$

Solving equations (i) and (ii), we get,


$$I_1 = 0.667 \text{ mA}$$

$$I_2 = -0.444 \text{ mA}$$

$$\therefore V_{OC} = 2V_x + (1 \text{ k}\Omega)I_2$$

$$V_{OC} = 1.78 \text{ V}$$

Finding short circuit current

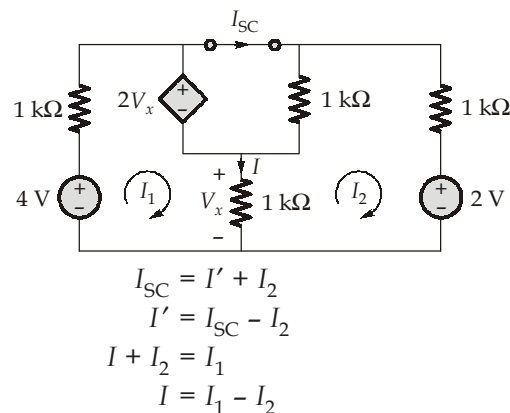

Applying KVL in loop (1)

$$(4 \text{ k}\Omega)I_1 + 2V_x - (3 \text{ k}\Omega)I_2 = 4 \quad \dots(i)$$

Applying KVL in loop (ii)

$$(-1 \text{ k}\Omega)I_{\text{SC}} - (1 \text{ k}\Omega)I_1 + (3 \text{ k}\Omega)I_2 = -2 \quad \dots(\text{ii})$$

Thus,

$$V_x = (1 \text{ k}\Omega)I = (1 \text{ k}\Omega)(I_1 - I_2)$$

$$I_1 = 1.43 \text{ mA}$$


$$I_2 = 0.57 \text{ mA}$$

$$\therefore I_{\text{SC}} = \frac{(-1 \text{ k}\Omega)I_1 + (3 \text{ k}\Omega)I_2 + 2}{1 \text{ k}\Omega} = 2.29 \text{ mA}$$

$$\therefore R_{\text{Th}} = \frac{1.78}{2.29} \times 10^3 \Omega = 777 \Omega$$

12. (d)

Applying KCL on supernode

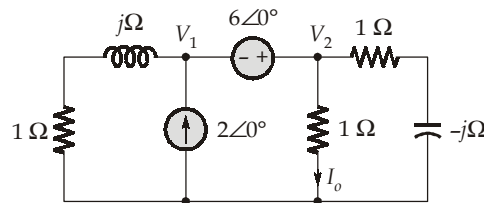

$$\frac{V_1}{1+j} - 2 + \frac{V_2}{1} + \frac{V_2}{1-j} = 0$$

and

$$V_1 + 6 = V_2$$

$$\therefore \begin{bmatrix} 0.5-0.5j & 1.5+0.5j \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$\therefore V_2 = \frac{\begin{bmatrix} 0.5-0.5j & 2 \\ 1 & -6 \end{bmatrix}}{\begin{bmatrix} 0.5-0.5j & j0.5+0.5j \\ 1 & -1 \end{bmatrix}}$$

$$V_2 = \frac{5.83095 \angle 149.036^\circ}{2 \angle 180^\circ}$$

$$V_2 \approx 2.915 \angle -30.96^\circ$$

Thus,

$$I_o = \frac{V_2}{1 \Omega} = 2.915 \angle -30.96^\circ$$

13. (a)

$$V_c(t) = \frac{-1}{10 \times 10^{-6}} \left[\int_0^t 0.2e^{-800\tau} d\tau - \int_0^t 0.04e^{-200\tau} d\tau \right] + 5$$

$$= 25e^{-800t} - 20e^{-200t}$$

$$V_L(t) = 150 \times 10^{-3} \frac{dI_o}{dt} = 150(-160e^{-800t} + 8e^{-200t}) \times 10^{-3}$$

$$= -24e^{-800t} + 1.2e^{-200t}$$

$$V_o(t) = V_c(t) - V_L(t)$$

$$= (25e^{-800t} - 20e^{-200t}) - (-24e^{-800t} + 1.2e^{-200t})$$

$$V_o(t) = (49e^{-800t} - 21.2e^{-200t}) \text{ V}$$

14. (b)

The 20 Ω impedance can be reflected to the primary side as

$$Z_R = \frac{20}{n^2} = \frac{20}{4} = 5 \Omega$$

$$\therefore \begin{aligned} Z_i &= 4 - 6j + 5 \\ &= 9 - 6j = 10.82 \angle -33.69^\circ \Omega \end{aligned}$$

$$I_1 = \frac{120 \angle 0^\circ}{Z_{in}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ$$

$$\therefore I_2 = -\frac{1}{n} I_1 = -5.545 \angle 33.69^\circ \text{ A}$$

$$V_o = 20I_2 = 110.9 \angle 213.69^\circ \text{ V}$$

15. (b)

The transfer function, $H(s) = \frac{v_o}{v_i} = \frac{R \parallel 1/sC}{sL + R \parallel 1/sC}$

$$H(s) = \frac{\frac{R}{1+sRC}}{sL + \frac{R}{1+sRC}} = \frac{R}{s^2RLC + sL + R}$$

$$H(j\omega) = \frac{R}{-\omega^2RLC + j\omega L + R}$$

At corner frequency, $|H(j\omega)| = \frac{1}{\sqrt{2}} |H(j\omega)|_{\max}$

Now, $|H(j\omega)| = \frac{R}{\sqrt{(R - \omega^2RLC)^2 + \omega^2L^2}}$

$$|H(j\omega)|^2 = \frac{1}{2} = \frac{R^2}{(R - \omega^2RLC)^2 + \omega^2L^2}$$

$$2 = (1 - \omega_o^2LC)^2 + \left(\frac{\omega_o L}{R}\right)^2$$

$$2 = (1 - \omega_o^2 4 \times 10^{-6})^2 + (\omega_o \times 10^{-3})^2$$

$$16\omega_o^4 - 7\omega_o^2 - 1 = 0 \text{ (where } \omega_o \text{ is in Krad/s)}$$

$$\therefore \omega_o = 0.742 \text{ K rad/sec} = 742 \text{ rad/sec}$$

16. (b)

$$\begin{aligned} Z_{AB} &= \left(\frac{23}{6}\right) + [(3+j4) \parallel (3-j4)] \\ &= \frac{23}{6} + \frac{(3+j4)(3-j4)}{6} = \frac{23+25}{6} = \frac{48}{6} \Omega = 8 \Omega \end{aligned}$$

$$\therefore Z_{AB} = 8 \Omega$$

17. (a)

$$L_{\text{eq}} = L_1 + L_2 - 2M = 4 + 4 - 2 \times 2 = 4 \text{ mH}$$

$$\text{Resonant frequency, } f_o = \frac{1}{2\pi\sqrt{L_{\text{eq}}C}}$$

$$f_o = \frac{1}{2\pi\sqrt{4 \times 0.1 \times 10^{-9}}} = 7.96 \text{ kHz}$$

18. (b)

$$\text{Impedance matrix for 'N'} = \frac{1}{[Y]} = \frac{1}{5} \begin{bmatrix} 3 & -2 \\ -2 & 3 \end{bmatrix} = \begin{bmatrix} 3/5 & -2/5 \\ -2/5 & 3/5 \end{bmatrix}$$

In series connection: individual impedance parameters are added

$$\therefore \text{For individual network} = \frac{1}{2} \begin{bmatrix} 3/5 & -2/5 \\ -2/5 & 3/5 \end{bmatrix} = \begin{bmatrix} 0.3 & -0.2 \\ -0.2 & 0.3 \end{bmatrix}$$

19. (b)

We know that, for a transformer

$$R_s = \left(\frac{n_1}{n_2} \right)^2 R_L$$

$$100 \text{ k}\Omega = \left(\frac{n_1}{n_2} \right)^2 10$$

$$\left(\frac{n_1}{n_2} \right)^2 = 10^4$$

$$\therefore \frac{n_1}{n_2} = 100$$

20. (c)

$$v(t) = 2[u(t) - u(t-2)] \text{ V}$$

$$i(t) = [r(t) - r(t-2)] \text{ A}$$

$$v(t) = 2 \frac{di(t)}{dt}$$


$$\text{For inductor, } v(t) = L \frac{di(t)}{dt}$$

\therefore The element is inductor of 2 H

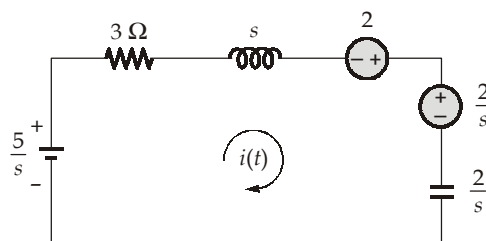21. (c)

At $t = 0$, switch is closed

For $t > 0$, the circuit in s-domain becomes,



Applying KVL, we get,


$$\frac{5}{s} - \frac{2}{s} + 2 = \left(3 + s + \frac{2}{s}\right)I(s)$$

$$I(s) = \frac{2s+3}{(s+1)(s+2)}$$

Using partial fractions, $I(s) = \frac{1}{(s+1)} + \frac{1}{(s+2)}$

or $i(t) = L^{-1}[I(s)] = (e^{-t} + e^{-2t}) \text{ A ; for } t > 0$

22. (a)

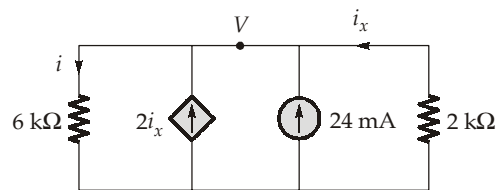

Applying KCL, $i = 2i_x + 24 \text{ mA} + i_x \dots (i)$

where, $i = \frac{V}{6000}$ and $i_x = \frac{-V}{2000} \dots (ii)$

Therefore, from equations (i) and (ii)

$$\frac{V}{6000} + \frac{V}{2000} - 2\left(-\frac{V}{2000}\right) = 24 \text{ mA}$$

$$\Rightarrow V = (600) (24 \times 10^{-3}) = 14.4 \text{ V}$$

Hence, power supplied by independent current source

$$P = V \times 24 \text{ mA} = 14.4 \times 24 \times 10^{-3} = 345.6 \text{ mW}$$

23. (d)

Given,

$$f = 1.5 \text{ MHz}$$

$$C = 150 \text{ pF}$$

$$\text{BW} = 10 \text{ kHz}$$

$$\text{For series RLC circuit, } Q = \frac{f_o}{\text{BW}} = \frac{1.5 \times 10^6}{10 \times 10^3} = 150$$

$$Q = \frac{1}{\omega RC}$$

$$\frac{1}{150} = 2\pi \times 1.5 \times 10^6 \times 150 \times 10^{-12} \times R$$

$$R = \frac{10^6}{2\pi \times 1.5 \times 150 \times 150} = 4.71 \Omega$$

24. (b)

For $t < 0$, source $2u(t) = 0$

Therefore, $i_L(0^-) = i_L(0^+) = 0 \text{ A}$

$v_c(0^-) = v_c(0^+) = 0 \text{ V}$

For $t > 0$, $i_c(0^+) = 2 \text{ mA}$

$$i_c(0^+) = c \frac{dv_c(0^+)}{dt}$$

$$\frac{dv_c(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{2 \times 10^{-3}}{4 \times 10^{-3}} = 0.5 \text{ V/sec}$$

25. (c)


For a capacitor

$$i(t) = \frac{cdv(t)}{dt} = 10 \times 10^{-6} \frac{dv(t)}{dt} \times 10^3 \text{ A}$$

$$= 10^{-2} \frac{dv(t)}{dt} \text{ A} = 10 \frac{dv(t)}{dt} \text{ mA}$$

26. (a)

For the circuit

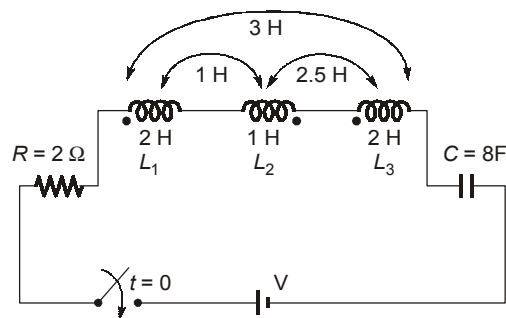

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$$

$$L_1 = 2 \text{ H}$$

$$L_2 = 1 \text{ H}$$

$$L_3 = 2 \text{ H}$$

$$M_{12} = 1 \text{ H}$$

$$M_{23} = 2.5 \text{ H}$$

$$M_{13} = 3 \text{ H}$$

$$L_{eq} = 2 + 1 + 2 - 2 - 5 + 6$$

$$= 11 - 7$$

$$= 4 \text{ H}$$

$$C = 8 \text{ F}$$

$$R = 2 \Omega$$

$$\therefore \omega_n = \frac{1}{\sqrt{L_{eq}C}} = \frac{1}{\sqrt{8 \times 4}} = 0.176 \text{ rad/sec} \approx 0.18 \text{ rad/sec}$$

Note : M_{12} , M_{23} is negative, because both L_1 , L_2 and L_2 , L_3 opposes the flux of respective loops.

27. (b)

$\therefore p(t)$ varies with time, thus it can be concluded that the network is not purely resistive circuit.

$$\therefore \text{let, } v(t) = \sqrt{2} V_{\text{rms}} \cos(\omega t + \theta_v)$$

$$i(t) = \sqrt{2} I_{\text{rms}} \cos(\omega t + \theta_I)$$

then, the instantaneous power into the network N is given as,

$$p(t) = v(t) i(t) = 2V_{\text{rms}} I_{\text{rms}} \cos(\omega t + \theta_v) \cos(\omega t + \theta_I)$$

$$= V_{\text{rms}} I_{\text{rms}} \left[\underbrace{\cos(\theta_v - \theta_I)}_{\text{constant}} + \underbrace{\cos(2\omega t + \theta_v + \theta_I)}_{\text{time varying}} \right]$$

thus, for minimum power delivered,

$$\cos(2\omega t + \theta_v + \theta_I) = -1$$

and for maximum power delivered

$$\cos(2\omega t + \theta_v + \theta_I) = 1$$

$$p(t)_{\text{max}} = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_I) + V_{\text{rms}} I_{\text{rms}} \quad \dots(i)$$

$$p(t)_{\text{min}} = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_I) - V_{\text{rms}} I_{\text{rms}} \quad \dots(ii)$$

Thus, from equation (i) and (ii), we get,

thus,

$$2V_{\text{rms}} I_{\text{rms}} = 2500$$

$$V_{\text{rms}} I_{\text{rms}} = 1250$$

$$I_{\text{rms}} = \frac{1250}{V_{\text{rms}}} = \frac{1250}{100} = 12.5 \text{ A}$$

28. (c)

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}} = 50 \text{ krad/sec}$$

$$Q = \frac{\omega_0 L}{R} = \frac{50 \times 10^3 \times 10^{-3}}{2} = 25$$

$$B = \frac{\omega_0}{Q} = \frac{50 \times 10^3}{25} = 2 \text{ krad/sec}$$

$$\text{now, } \omega_1 = \omega_0 - \frac{B}{2} = 50 - 1 = 49 \text{ krad/sec}$$

$$\text{now, } \omega_2 = \omega_0 + \frac{B}{2} = 50 + 1 = 51 \text{ krad/sec}$$

Hence, option (c) is incorrect.

29. (d)

Now, applying KCL at node A, we get,

$$I_1 = V_1 + (V_1 - V_1')$$

$$= 2V_1 - V_1'$$

$$I_1 = 2V_1 - \frac{1}{a}V_2$$


For I_2 , we can write

$$I_2 = -\frac{1}{a}I_1' = -\frac{1}{a}[-V_1' + (V_1 - V_1')]$$

$$= -\frac{1}{a}V_1 + \frac{2}{a^2}V_2$$

$$\therefore \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 2 & -\frac{1}{a} \\ -\frac{1}{a} & \frac{2}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

For the Z-parameter to not exist.

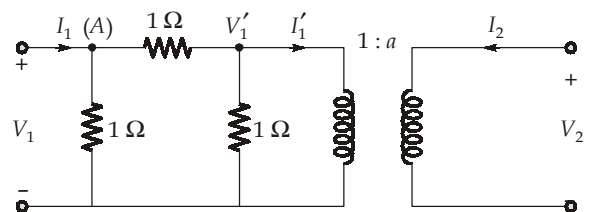

$$|Y| = 0$$

$$\therefore |Y| = \frac{4}{a^2} - \frac{1}{a^2} = \frac{3}{a^2}$$

$$\therefore |Y| \neq 0$$

Thus, no such value exist for which $|Y| = 0$.

30. (a)

From phasor, we can write

$$\tan 30^\circ = \frac{X_C}{R_2}$$

$$\Rightarrow R_2 = X_C \sqrt{3} = \frac{\sqrt{3}}{\omega C}$$

$$\tan 45^\circ = \frac{X_L}{R_1}$$

$$\Rightarrow R_1 = X_L = \omega L$$

$$R_1 R_2 = \frac{\sqrt{3}}{\omega C} \times \omega L = \frac{L}{C} \sqrt{3}$$

$$R_1 R_2 = \sqrt{3} = 1.732$$

we know

$$\frac{R_1 + R_2}{2} \geq \sqrt{R_1 R_2}$$

as arithmetic mean \geq geometric mean ; (for non-negative real numbers)

$$R_1 + R_2 \geq 2\sqrt{\sqrt{3}}$$

$$R_1 + R_2 \geq 2(3)^{1/4}$$

Minimum value of $R_1 + R_2 = 2.63 \Omega$

