

**MADE EASY**

India's Best Institute for IES, GATE &amp; PSUs

**Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata****Web:** [www.madeeasy.in](http://www.madeeasy.in) | **E-mail:** [info@madeeasy.in](mailto:info@madeeasy.in) | **Ph:** 011-45124612

# ELECTRIC CIRCUITS

## ELECTRICAL ENGINEERING


**Date of Test : 23/07/2023**

### ANSWER KEY ➤

- |        |         |         |         |         |
|--------|---------|---------|---------|---------|
| 1. (c) | 7. (a)  | 13. (d) | 19. (a) | 25. (b) |
| 2. (a) | 8. (a)  | 14. (a) | 20. (a) | 26. (b) |
| 3. (b) | 9. (d)  | 15. (b) | 21. (b) | 27. (b) |
| 4. (d) | 10. (b) | 16. (a) | 22. (c) | 28. (b) |
| 5. (a) | 11. (a) | 17. (c) | 23. (b) | 29. (c) |
| 6. (b) | 12. (a) | 18. (a) | 24. (a) | 30. (b) |

## DETAILED EXPLANATIONS

1. (c)

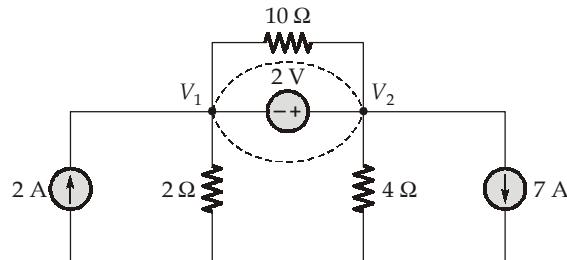

Using supernode method,

$$-2 + \frac{V_1}{2} + \frac{V_2}{4} + 7 = 0$$


$$2V_1 + V_2 = -20$$

$$V_1 - V_2 = -2$$

$$V_1 = -7.33 \text{ V}$$

$$V_2 = -5.33 \text{ V}$$

2. (a)

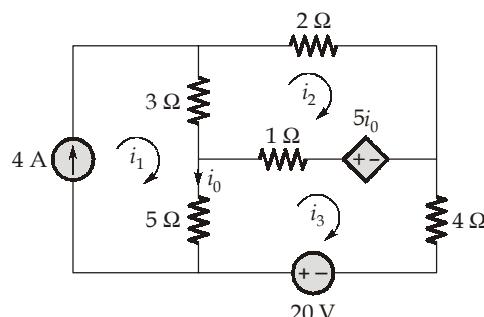

Apply mesh analysis,

$$i_1 = 4$$

$$i_0 = (i_1 - i_3) = 4 - i_3$$

$$3(i_2 - i_1) + 2i_2 - 5i_0 + (i_2 - i_3) = 0$$

$$6i_2 + 4i_3 = 32 \quad \dots(i)$$

$$1(i_3 - i_2) + 5i_0 + 4i_3 - 20 - 5i_0 = 0$$

$$5i_3 - i_2 = 20 \quad \dots(ii)$$


From equation (i) and (ii), we get

$$i_2 = 2.35 \text{ A};$$

$$i_3 = 4.4705 \text{ A}$$

$$i_0 = 4 - i_3 = -0.4705 \text{ A}$$

3. (b)

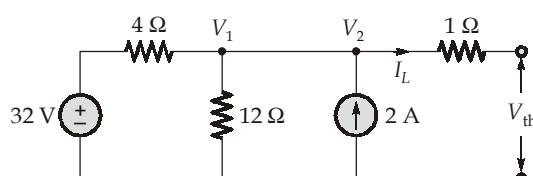

Apply node analysis,

$$\begin{aligned}\frac{V_1 - 32}{4} + \frac{V_1}{12} - 2 &= 0 \\ V_1 \left( \frac{1}{4} + \frac{1}{12} \right) &= 10 \\ V_1 \left( \frac{4}{12} \right) &= 10 \\ V_1 &= \frac{120}{4} = 30 \text{ V}\end{aligned}$$

The thevenin across  $a, b$  it is open circuited,

$$\therefore V_{\text{th}} = V_1 = 30 \text{ V}$$

4. (d)

$$\begin{aligned}i(t) &= 10t e^{-5t} \\ \text{Energy stored, } E &= \frac{1}{2} L i^2 = \frac{1}{2} \times 0.1 \times (10t e^{-5t})^2 \\ &= \frac{0.1}{2} \times 100t^2 e^{-10t} = 5t^2 e^{-10t} \\ \text{At } t = 1 \text{ sec, } E_{1 \text{ sec}} &= 5 \times 1 \times e^{-10} \\ &= \frac{5}{e^{10}} = 227 \times 10^{-6} = 227 \mu\text{J}\end{aligned}$$

5. (a)

$$\begin{aligned}Z_{\Delta} &= (8 + 4j) \Omega \\ Z_Y &= \frac{Z_{\Delta}}{3} = \left( \frac{8}{3} + \frac{4j}{3} \right) \Omega \\ V_{an} &= 100 \angle 10^\circ \text{ V} \\ V_{cn} &= 100 \angle 130^\circ \text{ V} \\ \text{In star; } I_c \text{ line} &= I_c \text{ phase} = \frac{100 \angle 130^\circ}{(8 + 4j)/3} \\ &= 33.54 \angle 103.43^\circ \text{ A}\end{aligned}$$

6. (b)

$y$ -parameters of  $1 \Omega$  resistor network are  $\begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$

New  $y$ -parameter,

$$\begin{aligned}&= \begin{bmatrix} 5 & 3 \\ 1 & 2 \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \\ &= \begin{bmatrix} 6 & 2 \\ 0 & 3 \end{bmatrix} S\end{aligned}$$

7. (a)

$$\begin{aligned}\text{Let, } i_x &= i_{xA} + i_{xB} + i_{xC} \\ i_{xA} + i_{xB} &= 20\end{aligned}$$


$$\begin{aligned}
 i_{xA} + i_{xC} &= -5 \\
 i_{xA} + i_{xB} + i_{xC} &= 12 \\
 i_{xA} &= 3 \text{ A;} \\
 i_{xB} &= 17 \text{ A;} \\
 i_{xC} &= -8 \text{ A}
 \end{aligned}$$

∴ if only source  $V_B$  is operating,

then

$$i_x = i_{xB} = 17 \text{ A}$$

8. (a)

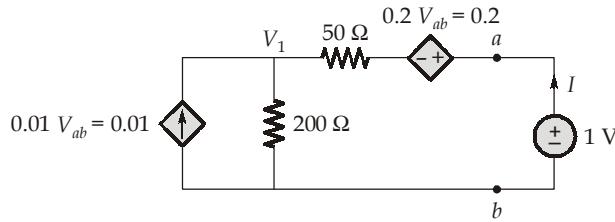

$$0.01 = \frac{V_1}{200} + \frac{V_1 - 1 + 0.2}{50}$$

$$0.01 = \frac{V_1}{200} + \frac{V_1}{50} - 0.016$$

$$V_1 = 0.026 \times 40 = 1.04 \text{ V}$$

$$I = \frac{1 - 0.2 - 1.04}{50} = -0.0048 \text{ A}$$

$$R_{\text{th}} = \frac{V}{I} = \frac{1}{-0.0048} = -208.33 \Omega$$


9. (d)

$$C_{\text{eq}} = 1 \parallel 4 = \frac{4}{5} = 0.8 \mu\text{F}$$

$$\begin{aligned}
 i &= C_{\text{eq}} \frac{dv}{dt} = 0.8 \frac{d}{dt}(100e^{-80t}) \times 10^{-6} \\
 &= 0.8 \times 100 \times (-80)e^{-80t} \times 10^{-6} \\
 &= -6.4 e^{-80t} \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 v_1(t) &= \frac{1}{C_1} \int_0^t i dt + V_1(0) \\
 &= \frac{1}{1 \times 10^{-6}} \int_0^t -6.4 e^{-80t} dt \times 10^{-3} + 20 \\
 &= \frac{-6.4}{10^{-3}} \times \frac{e^{-80t}}{-80} \Big|_0^t + 20 \\
 v_1(t) &= 80(e^{-80t} - 1) + 20 \\
 &= (80e^{-80t} - 60) \text{ V}
 \end{aligned}$$

10. (b)

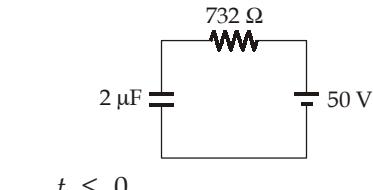

$$t \leq 0 \\ v(0^-) = 50 \text{ V}$$



$$t \geq 0$$

$$i = \frac{50/s}{\left(R + \frac{1}{CS}\right)}$$

$$i = \frac{50C}{(1+RCS)}$$

$$i(t) = \frac{50}{R} e^{-t/RC} A$$

$$v = iR = 50e^{-t/RC}$$

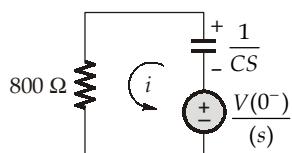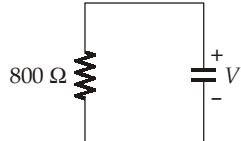


$$v(t=2 \text{ ms}) = 50 e^{\frac{-2 \times 10^{-3}}{800 \times 2 \times 10^{-6}}} = 14.33 \text{ V}$$

11. (a)

$$\text{Energy stored maximum} = \frac{1}{2} L_{eq} i^2 = \frac{1}{2} \times 9 \times 2^2 = 18 \text{ J}$$

12. (a)

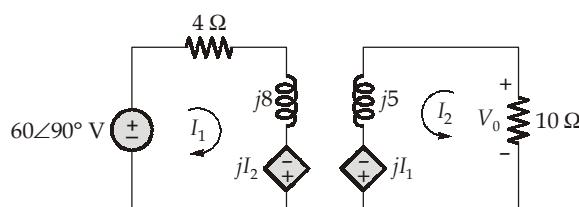

Apply KVL,

$$(10 + j5)I_2 - jI_1 = 0$$

$$I_1 = \frac{(10 + j5)}{j} I_2 = (5 - 10j)I_2$$

$$-60j + (4 + 8j)I_1 - jI_2 = 0$$

$$(4 + 8j)(5 - 10j)I_2 - jI_2 = 60j$$

$$I_2 = 0.6 \angle 90^\circ$$


$$V_0 = -10 \times I_2 \\ = -10 \times 0.6j = -6j$$

13. (d)

$$i(0) = -1 \text{ A}$$

$$V(0) = 5 \text{ V}$$

Apply node analysis

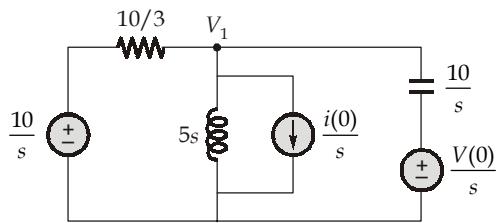

$$\frac{\left(V_1 - \frac{10}{s}\right)}{\frac{10}{3}} + \frac{V_1}{5s} - \frac{1}{s} + \frac{\left(V_1 - \frac{5}{s}\right)}{\left(\frac{10}{s}\right)} = 0$$

$$V_1 \left( \frac{3}{10} + \frac{1}{5s} + \frac{s}{10} \right) - \frac{10 \times 3}{s \times 10} - \frac{1}{s} - \frac{5}{s} \times \frac{s}{10} = 0$$

$$V_1 \left( \frac{3s + 2 + s^2}{10s} \right) = \left( \frac{3}{s} + \frac{1}{s} + \frac{0.5s}{s} \right)$$

$$V_1 = \frac{10s}{(s^2 + 3s + 2)} \times \frac{(0.5s + 4)}{s}$$

$$V_1 = \frac{(5s + 40)}{s^2 + 3s + 2} = \frac{5(s + 8)}{(s + 1)(s + 2)}$$

$$V_1 = 5 \left( \frac{7}{s+1} - \frac{6}{s+2} \right)$$

$$v_1(t) = (35e^{-t} - 30e^{-2t})u(t)$$


14. (a)

$$X_{L1} = j\omega L = j4 \times 5 = j20 \Omega$$

$$X_{L2} = j\omega L_2 = j4 \times 4 = j16 \Omega$$

$$X_C = \frac{1}{j\omega C} = \frac{16}{j4 \times 1} = -j4 \Omega$$
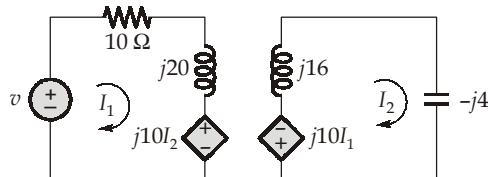
$$X_m = j\omega M = j \times 4 \times 2.5 = j10 \Omega$$



$$-60\angle 30^\circ + (10 + 20j)I_1 + j10I_2 = 0 \quad \dots(i)$$

$$(j16 - j4)I_2 + j10I_1 = 0$$

$$I_1 = -1.2I_2 \quad \dots(ii)$$

$$-(10 + j20) \times 1.2I_2 + j10I_2 = 60\angle 30^\circ$$

$$I_2 = 3.25\angle 160.6^\circ \text{ A}$$

$$I_2 = 3.25 \cos(4t + 160.6^\circ)$$

$$I_1 = 3.9 \cos(4t - 19.4^\circ)$$

At  $t = 1$  sec,

$$4t = 4 \text{ rad} = 229.18^\circ$$

$$I_2 = 2.82 \text{ A}$$

$$I_1 = -3.38 \text{ A}$$

Total energy stored in the coupled inductor is

$$E = \frac{1}{2}L_i I_i^2 + \frac{1}{2}L_2 I_2^2 + M I_1 I_2$$

$$E = \frac{1}{2} \times 5 \times (-3.38)^2 + \frac{1}{2} \times 4 \times (2.82)^2 - 2.5 \times 3.38 \times 2.82 = 20.5 \text{ J}$$

15. (b)

$$\text{T.F.} = \frac{s}{(s+50)^2 + (1000)^2} = \frac{s}{s^2 + 100s + 100.25 \times 10^4}$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$


$$\frac{1}{RC} = 100;$$

$$\frac{1}{LC} = 100.25 \times 10^4 = \frac{1}{L \times 1 \times 10^{-6}}$$

$$L = 0.9975 \text{ H}$$

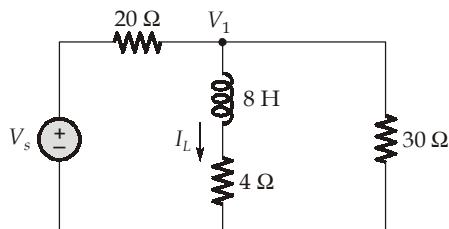16. (a)

$$V_S(s) = \frac{-5}{s} + \frac{12}{s} + 3 = \left( \frac{7}{s} + 3 \right)$$



$$\frac{(V_1 - V_s)}{20} + \frac{V_1}{8s + 4} + \frac{V_1}{30} = 0$$

$$V_1 \left( \frac{1}{20} + \frac{1}{8s + 4} + \frac{1}{30} \right) = \frac{1}{20} \left( \frac{7 + 3s}{s} \right)$$

$$V_1 \left( \frac{24s + 12 + 60 + 16s + 8}{60(8s + 4)} \right) = \frac{1}{20s} (7 + 3s)$$

$$V_1 = \frac{7 + 3s}{20s} \times \frac{60(8s + 4)}{(40s + 80)}$$

$$= \frac{3}{s} \frac{(7 + 3s)(8s + 4)}{(40s + 80)}$$

$$I_L = \frac{3}{s} \frac{(7+3s)(8s+4)}{(40s+80)(8s+4)} = \frac{3}{s} \times \frac{(7+3s)}{40(s+2)}$$

$$I_L = \frac{3}{40} \left[ \frac{7}{2s} + \frac{-1}{2(s+2)} \right]$$


$$i_L(t) = \frac{3}{40} \left( \frac{7}{2} - \frac{1e^{-2t}}{2} \right) u(t)$$

$$i_L(t) = \left( \frac{21}{80} - \frac{3}{80} e^{-2t} \right) u(t)$$

17. (c)

$$X_L = \omega L = 2$$

$$X_C = \frac{1}{1} = 1$$

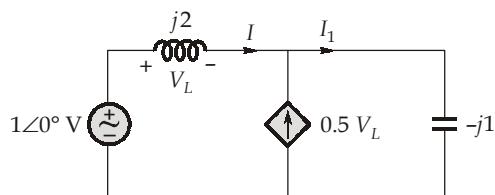

$$I = 0.5 V_L + I_1 = -0.5 \times (j2)I + I_1$$

$$I = -jI + I_1$$

$$I(1+j) = \frac{(1-j2I)}{-j1}$$

$$I(-j+1) = (1-j2I)$$

$$I(1+j) = 1$$


$$I = \left( \frac{1}{2} - \frac{j}{2} \right)$$

$$Y_{\text{in}} = I \times 1 = \left( \frac{1}{2} + \frac{1}{j2} \right) s$$

$$R = 2, L = 2$$


18. (a)

At  $t < 0$ ,

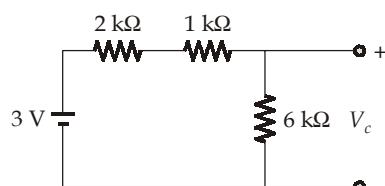

$$V_c(0^-) = 3 \times \frac{6}{(6+3)} = \frac{18}{9} = 2 \text{ V}$$

At  $t > 0$ ,

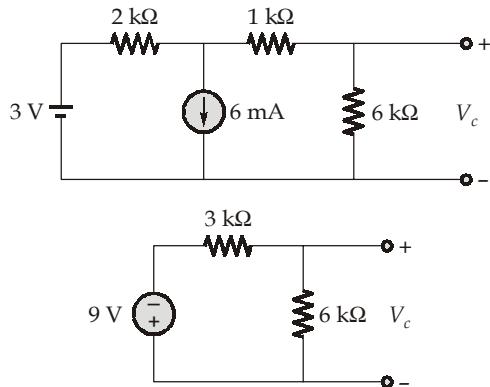

$$v_c(\infty) = \frac{6}{9} \times (-9) = -6 \text{ V}$$

$$v_c(t) = -6 + (2 + 6)e^{-t/\tau}$$

$$\tau = \frac{18}{9} \times 1 = 2 \mu\text{s}$$

$$V_c(t) = -6 + 8e^{-\frac{t}{2}}$$

$$V_c(2 \mu\text{s}) = -6 + 8e^{-1} = -3.06 \text{ V}$$

19. (a)

The equivalent resistance across  $x-y$  is

$$R_{x-y} = \frac{mr}{2} + \frac{r}{m} = \frac{m^2 r + 2r}{2m}$$

It may be noted that  $I$  will be maximum when  $R_{x-y}$  will be minimum,

$$\frac{\delta R_{x-y}}{\delta m} = 0$$

$$\text{i.e., } 2m(2mr) - 2(m^2r + 2r) = 0$$

$$\text{i.e., } m = \sqrt{2}$$

20. (a)

$$(V_{\text{rms}})^2 = \frac{1}{T} \left[ \int_0^{t_1} v^2 dt + \int_{t_1}^T v^2 dt \right]$$


$$= \frac{1}{2} \left[ \int_0^1 10^4 (1 - 2e^{-10t} + e^{-20t}) dt + \int_1^2 10^4 e^{-20t} dt \right]$$

$$= (5000) \left[ [(t + 0.2e^{-10t} - 0.05e^{-20t})]_0^1 - \left( \frac{1}{20} \right) e^{-20t}]_1^2 \right]$$

$$= (5000) [1 + 0.2e^{-10} - 0.2 + 0.05 - 0.05e^{-40}]$$

$$\therefore V_{\text{rms}} = 65.25 \text{ V}$$

21. (b)

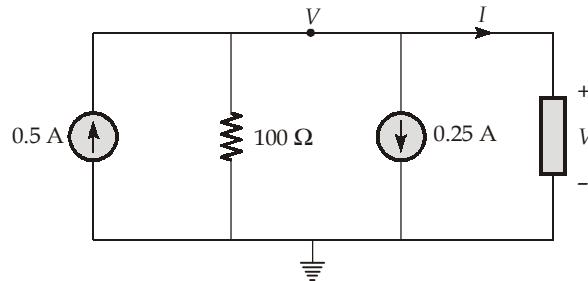

Voltage across 0.5 A current source is

$$V = \frac{\text{Power}}{\text{Current}} = \frac{1 \text{ W}}{0.5 \text{ A}} = 2 \text{ V}$$

Applying nodal analysis at node

$$0.5 = \frac{V}{100} + 0.25 + I$$


$$0.5 = \frac{2}{100} + 0.25 + I$$

$$I = 0.23 \text{ A}$$

Power absorbed by unknown element =  $0.23 \times 2 = 0.46 \text{ W}$

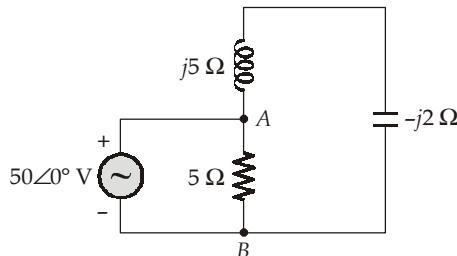
22. (c)

**Step-I:** When the  $50\angle 0^\circ \text{ V}$  source is acting alone.



$$V'_{AB} = 50\angle 0^\circ + 0 \text{ V} = 50\angle 0^\circ \text{ V}$$

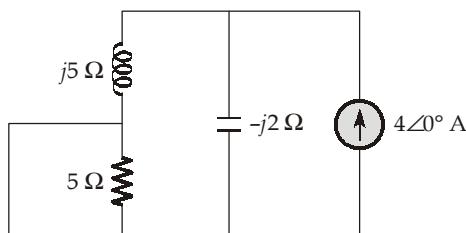**Step-II:** When the  $4\angle 0^\circ \text{ A}$  source is acting alone.



$$V''_{AB} = 0 \text{ V}$$

$$\begin{aligned} \text{By superposition theorem, } V_{AB} &= V'_{AB} + V''_{AB} \\ &= 50\angle 0^\circ = 50\angle 0^\circ \text{ V} \end{aligned}$$

23. (b)

$$X_{L1} = 2\pi \times 50 \times 0.01 = 3.14 \Omega$$

$$X_{L2} = 2\pi \times 50 \times 0.02 = 6.28 \Omega$$

$$X_C = \frac{1}{2\pi \times 50 \times 200 \times 10^{-6}} = 15.92 \Omega$$

$$\bar{Z}_1 = 6 + j3.14 \Omega$$

$$\bar{Z}_2 = 4 + j6.28 \Omega$$

$$\bar{Z}_3 = 2 - j15.92 \Omega$$

$$\bar{Z} = \bar{Z}_1 + \frac{\bar{Z}_2 \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3}$$

$$= (6 + j3.14) + \frac{(4 + j6.28)(2 - j15.92)}{(4 + j6.28) + (2 - j15.92)} = 17.27 \angle 30.75^\circ \Omega$$

Power factor =  $\cos\phi = \cos(30.75^\circ) = 0.86$  (lagging)

24. (a)

RMS value of the rectangular wave =  $I_m$


RMS value of sinusoidal current wave =  $\frac{I_m}{\sqrt{2}}$

Heating effect due to rectangular current wave =  $I_m^2 RT$

Heating effect due to sinusoidal current wave =  $\left(\frac{I_m}{\sqrt{2}}\right)^2 RT$

Relative heating effects =  $\left(\frac{I_m}{\sqrt{2}}\right)^2 RT : I_m^2 RT = 1 : 2$

25. (b)

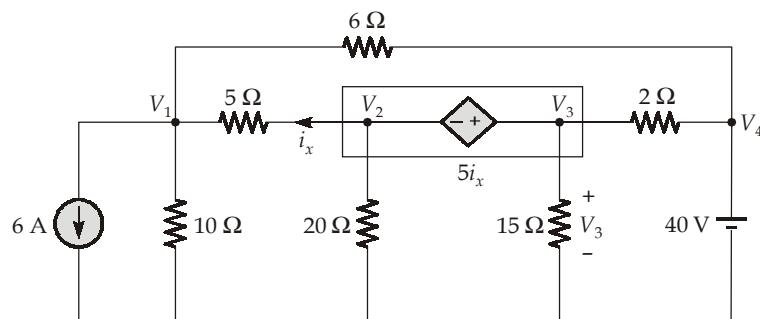

Nodes 2 and 3 form a super node:

$$\begin{aligned} V_3 &= 5i_x + V_2 \\ &= 5 \left[ \left( \frac{V_2 - V_1}{5} \right) \right] + V_2 = 2V_2 - V_1 \end{aligned}$$

Applying KCL at node 1,

$$6 + \frac{V_1}{10} + \frac{V_1 - V_2}{5} + \frac{V_1 - V_4}{6} = 0$$

$$6 + \frac{V_1}{10} + \frac{V_1}{5} - \frac{V_2}{5} + \frac{V_1 - 40}{6} = 0$$

$$\frac{7}{15}V_1 - \frac{1}{5}V_2 = \frac{2}{3} \quad \dots(3)$$

Applying KCL for the super node:

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{V_3}{15} + \frac{V_3 - V_4}{2} = 0$$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{(2V_2 - V_1)}{15} + \frac{(2V_2 - V_1) - 40}{2} = 0$$

$$-\frac{23}{30}V_1 + \frac{83}{60}V_2 = 20 \quad \dots(4)$$

Solving equation (3) and (4),

$$V_1 = 10 \text{ V}$$


$$V_2 = 20 \text{ V}$$

$$V_3 = 2V_2 - V_1$$

$$= 40 - 10 = 30 \text{ V}$$
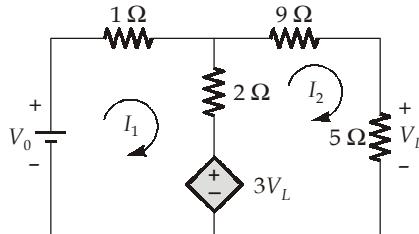
## 26. (b)

Let us apply a voltage source  $V_0$  at the input terminals such that the current in the loops be  $I_1$  and  $I_2$ .



Obviously,

$$V_L = R_L I_2 = 5I_2$$

$\therefore$  The dependent voltage source is  $3V_L = 15I_2$

Again applying KVL in loop-1,

$$V_0 = 3I_1 + 15I_2 - 2I_2$$

$$= 3I_1 + 13I_2 \quad \dots(1)$$

In loop-2,

$$0 = -2I_1 + (2 + 9 + 5) I_2 - 3V_L$$

$$0 = -2I_1 + 16I_2 - 15I_2 \quad \dots(2)$$

$$I_2 = 2I_1$$

$$V_0 = 3I_1 + 13 \times 2I_1$$

$$V_0 = 29I_1$$

$$\frac{V_0}{I_1} = R_{\text{input}} = 29 \Omega$$

## 27. (b)

$$Z_{ph} \text{ (Phase impedance)} = \frac{V_{ph}}{I_{ph}} = \frac{400}{75\sqrt{3}} = 3 \Omega$$

$$\left[ \text{In star connection } I_{ph} = I_{\text{line}}, V_{ph} = \frac{V_L}{\sqrt{3}} \right]$$

$$\frac{\text{Power}}{\text{Phase}} = I_{ph}^2 R_{ph}$$

$$\frac{10 \times 10^3}{3} = (75)^2 R_{ph}$$

$$\therefore R_{ph} = \frac{10 \times 1000}{3 \times 75 \times 75} = 0.6 \Omega$$

$$\therefore X_{ph} = \sqrt{Z_{ph}^2 - R_{ph}^2} = \sqrt{3^2 - (0.6)^2} = 2.94 \Omega$$

As the current is leading,  $X_{ph}$  must be capacitive.

$$\therefore X_c = 2.94 \Omega$$

$$\text{or, } \frac{1}{\omega C} = 2.94 \Omega$$

$$\therefore C = \frac{1}{2.94 \times 2\pi f} = \frac{1}{2.94 \times 2 \times \pi \times 50} = 1083 \mu\text{F}$$

28. (b)

For a series RLC circuit operating at resonance,

$$V_R = V = 200 \text{ V}$$

$$P_R = \frac{V^2}{R}$$

$$15.3 = \frac{(200)^2}{R}$$

$$R = \frac{200 \times 200}{15.3} = 2.61 \text{ k}\Omega$$

$$Q = \frac{f_0}{\Delta f} = \frac{10}{1} = 10$$

$$\text{Now, } Q = \frac{\omega_0 L}{R}$$

$$10 = \frac{2\pi(10^4)(L)}{2.61 \times 10^3}$$

$$\therefore L = 416 \text{ mH}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$10^4 = \frac{1}{2\pi\sqrt{416 \times 10^{-3}C}}$$

$$C = 610 \text{ pF}$$

29. (c)

$$V_1 = 5I_1 + 2I_2 \quad \dots(1)$$

$$V_2 = 2I_1 + I_2 \quad \dots(2)$$

and

$$V_2 = -I_2 R_L = -3I_2 \quad \dots(3)$$

From equation (2) and (3),

$$-3I_2 = 2I_1 + I_2$$

or,


$$-4I_2 = 2I_1$$

$$I_2 = -\frac{I_1}{2} \text{ put this value in equation (1)}$$

$$V_1 = 5I_1 + 2\left(-\frac{I_1}{2}\right) = 4I_1$$

$$\therefore Z_{in} = \frac{V_1}{I_1} = 4 \Omega$$


30. (b)

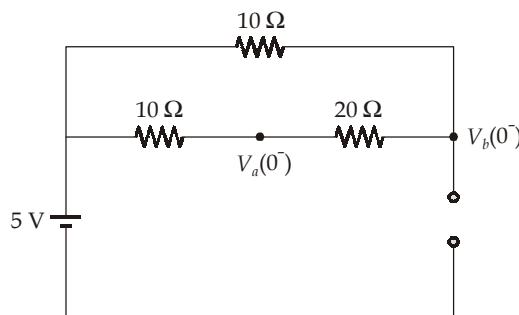At  $t = 0^-$ , the network attains steady state condition. Hence, the capacitor acts as an open-circuit.

$$V_b(0^-) = 5 \text{ V}$$

At  $t = 0^+$ , the capacitor acts as a voltage source of 5 V,

$$V_b(0^+) = 5 \text{ V}$$

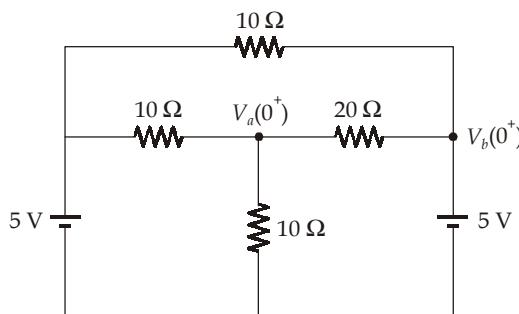Writing KCL equation at  $t = 0^+$ 

$$\frac{V_a(0^+) - 5}{10} + \frac{V_a(0^+)}{10} + \frac{V_a(0^+) - 5}{20} = 0$$

$$0.25 V_a(0^+) = 0.75$$

$$V_a(0^+) = 3 \text{ V}$$

