

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | **E-mail:** info@madeeasy.in | **Ph:** 011-45124612

DIGITAL LOGIC

COMPUTER SCIENCE & IT

Date of Test : 20/07/2023

ANSWER KEY ➤

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (b) | 7. (a) | 13. (d) | 19. (c) | 25. (b) |
| 2. (c) | 8. (b) | 14. (c) | 20. (b) | 26. (c) |
| 3. (a) | 9. (c) | 15. (b) | 21. (b) | 27. (d) |
| 4. (c) | 10. (c) | 16. (a) | 22. (b) | 28. (d) |
| 5. (b) | 11. (b) | 17. (a) | 23. (b) | 29. (a) |
| 6. (d) | 12. (c) | 18. (c) | 24. (b) | 30. (a) |

DETAILED EXPLANATIONS

1. (b)

Converting into decimal,

$$(2)_3 = 2 \times 3^0 = 2$$

$$(3)_4 = 3 \times 4^0 = 3$$

$$(14)_5 = 1 \times 5^1 + 4 \times 5^0 = 9$$

$$(15)_6 = 1 \times 6^1 + 5 \times 6^0 = 11$$

2. (c)

The characteristics table with J , K , Q_n , Q_{n+1} and the excitation table for S and R is shown below –

J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	×
0	0	1	1	×	0
0	1	0	0	0	×
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	×	0
1	1	0	1	1	0
1	1	1	0	0	1

The K-map for S and R is shown as –

For S ,

$$S(J, K, Q_n) = \Sigma m(4, 6) + d(1, 5) = J\bar{Q}_n$$

		KQ_n			
J		00	01	11	10
	0		×		
	1	1	×		1

$$S = J\bar{Q}_n$$


For R ,

$$R(J, K, Q_n) = \Sigma m(3, 7) + d(0, 2) = KQ_n$$

		KQ_n			
J		00	01	11	10
	0	×		1	×
	1			1	

$$R = KQ_n$$


3. (a)

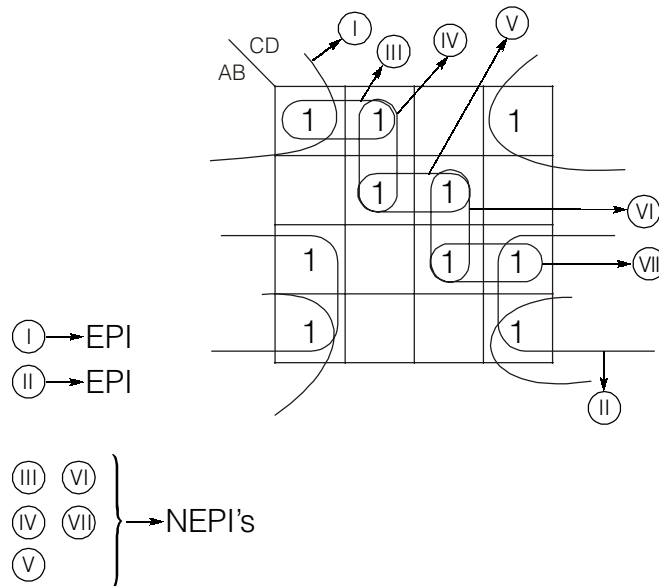

EPI = Essential Prime Implicant [which cover a minterm not covered by any other prime implicants]
NEPI = Non Essential Prime Implicant. Number of EPI's = 2, number of NEPI's = 5.

4. (c)


For one full Adder :

 

The propagation delay of AND / OR gate $t_{pd} = 1.2 \mu \text{ sec}$.

The propagation delay of EX-OR gate $2t_{pd} = 2.4 \mu \text{ sec}$.

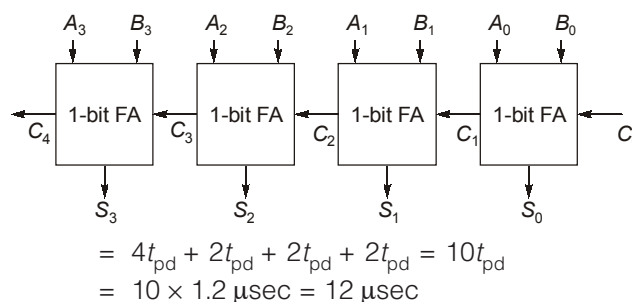- Binary Adder external inputs are available to all HA1's simultaneously.
- First HA1 output of all full adders are available simultaneously with delay of $2.4 \mu \text{ sec}$ (i.e., $2t_{pd}$).
- Carry generate from previous Full adder is passing only through HA2 of next full adder.
- The delay of LSB full adder = $4t_{pd}$.
- The 4 bit ripple carry binary delay:



5. (b)

For MOD - 10 counter –


 $X =$ Johnson counter required = 5 FF's $Y =$ ring counter required = 10 FF's $Z =$ ripple counter required = 4 FF's

$$X + Y + Z = 5 + 10 + 4$$

$$= 19 \text{ FF's.}$$

6. (d)

Clk	Q_1	Q_0	FF1		FF0	
			$J_1 = Q_0$	$K_1 = \bar{Q}_0$	$J_0 = \bar{Q}_1$	$K_0 = Q_1$
	0	0	0	1	1	0
1	0	1	1	0	1	0
2	1	1	1	0	0	1
3	1	0	0	1	0	1
4	0	0				

 

$$N = 4$$

$$K = 334$$

$$K \% N = 2 = (11)_2$$

7. (a)

Prime implicants are:

Cells(0, 2, 8, 10) : This is an EPI because it covers minterm 2 uniquely.

Cells(0, 1, 8, 9) : This is an EPI because it covers minterm 1 uniquely.

Cells (10, 14) : This is an EPI because it covers minterm 14 uniquely.

So, 3 PI, 3 EPI.

$$\text{So, PI + EPI} = 3 + 3 = 6$$

8. (b)

$$M = 1000 \ 1111; N = 0110 \ 0010; O = 0100 \ 1001; P = 0111 \ 0010$$

Now, program execution begins:

$$1. \ M \leftarrow M \oplus N :: //M = 1110 \ 1101$$

$$2. \ M \leftarrow \text{CSL } M :: //M = 1101 \ 1011$$

$$3. \ N \leftarrow M + N :: //N = 0011 \ 1101$$

$$4. \ O \leftarrow O \wedge N :: //O = 0000 \ 1001$$

$$5. \ O \leftarrow \text{CSR } O :: //O = 1000 \ 0100$$

$$6. \ P \leftarrow P + 1 :: //P = 0111 \ 0011$$

$$7. \ P \leftarrow P + O :: //P = 1111 \ 0111$$

Hence, answer is option (b).

9. (c)

$$Y = \overline{ABC} + \overline{A}\bar{B} + BC$$

Dual of Y

$$Y_d = \overline{(A+B+C)} \cdot \overline{(\bar{A}+\bar{B})} \cdot (B+C) = \left[\overline{(A+B+C)} + \overline{(\bar{A}+\bar{B})} \right] \cdot (B+C)$$

Compliment of Y

$$\begin{aligned} Y_c &= \overline{(\overline{ABC} + \overline{A}\bar{B}) + BC} = \overline{(\overline{ABC} + \overline{A}\bar{B})} \cdot \overline{BC} \\ &= (ABC + \bar{A}\bar{B}) \cdot \overline{BC} \end{aligned}$$

10. (c)

Output of the 4 : 1 MUX circuit in Figure A is

$$Y = I_0 \bar{A} \bar{B} + I_1 \bar{A} B + I_2 A \bar{B} + I_3 A B$$

Output of the circuit in Figure B is

$$Y = A \oplus B \oplus C = \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B C$$

On comparison

$$I_0 = C$$

$$I_1 = \bar{C}$$

$$I_2 = \bar{C}$$

$$I_3 = C$$

11. (b)

$$Y_1 = \bar{c}$$

$$F = Y_2 = \bar{d} Y_1 + dc$$

$$= \bar{d} \bar{c} + dc$$

$$= c \odot d$$

12. (c)

A	B	J	K	Q_{n+1}
0	0	1	0	1
0	1	1	1	\bar{Q}_n
1	0	1	0	1
1	1	0	1	0

$$Q_{n+1} = \bar{A} \bar{B} + A \bar{B} + \bar{A} B \bar{Q}_n$$

$$Q_{n+1} = \bar{B} + \bar{A} B \bar{Q}_n$$

$$= \bar{B} + \bar{A} \bar{Q}_n$$

13. (d)

14. (c)

Number of flip-flops for mod-16 ripple counter = 4

$$\text{Maximum clock frequency} = \frac{10^9}{4\rho} \text{ Hz} = 5 \text{ MHz}$$

$$\rho = \frac{10^9}{4 \times 5 \times 10^6} = \frac{1000}{20}$$

$$\rho = 50$$

15. (b)

Let the base be x , then

$$\begin{aligned} 292_{10} &= 1204_x \\ &= 1 \times x^3 + 2 \times x^2 + 0 \times x^1 + 4 \times x^0 \\ &= 292_{10} \\ &= x^3 + 2x^2 + 4 \\ &= 6 \text{ (By substitution)} \end{aligned}$$

16. (a)

For the given 4×1 MUX, 'A' and 'B' are select lines and 'C' be the input

	I_0	I_1	I_2	I_3
\bar{C}	0	2	4	6
C	1	3	5	7
	1	0	1	0

So,

$$I_0 = 1 = a$$

$$I_1 = 0 = b$$

$$I_2 = 1 = c$$

$$I_3 = 0 = d$$


So,

$$a \oplus d = b \oplus c = 1$$

So, output of NAND gate is 0 i.e. MUX 'E' connected to '0'.

The MUX is in disable state. MUX is having active high enable, but $E = 0$, so that MUX is in disable state. Hence MUX output Z is equal to '0'.


17. (a)

 

$$= (A + B)(\bar{A} + \bar{B})$$


$$= A\bar{B} + \bar{A}B$$

$$= A \oplus B$$

 


18. (c)

An Ex-OR gate can be represented as

 


 So, for EX-OR gate, it will take 30 nsec to get the output.



So, to get the output Y, it will take 50 nsec.


19. (c)

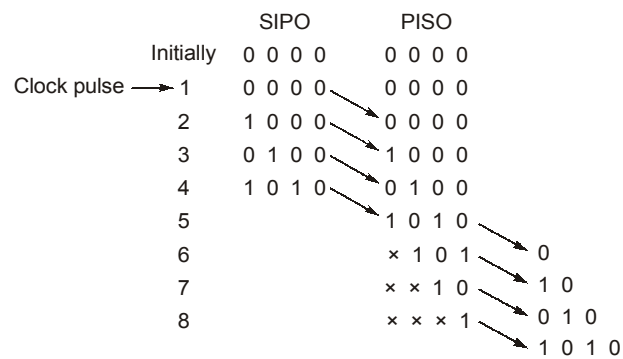

So, after 8 pulses, the output from PISO will be same as input in SIPO.


20. (b)

CLK	FFO				FFI	
	Q_1	Q_0	$J_0 = \bar{Q}_1$	$K_0 = 1$	$J_1 = Q_0$	$K_1 = \bar{Q}_0$
	0	0	1	1	0	1
1	0	1	1	1	1	0
2	1	0	0	1	0	1
3	0	0				

 

21. (b)

The k-map has to be rearranged as

 

$$F = \bar{A}\bar{B}\bar{C} + \bar{B}\bar{D} + AC$$

22. (b)

Simplifying boolean expression:

$$\begin{aligned}
 F &= C(B + C)(A + B + C) \\
 &= (CB + CC)(A + B + C) \\
 &= (CB + C)(A + B + C) \\
 &= C(1 + B)(A + B + C) \\
 &= C(A + B + C) \\
 &= AC + BC + C \\
 &= C(1 + A + B) \\
 &= C
 \end{aligned}$$

23. (b)

Let the base be x , then

$$\begin{aligned}
 292_{10} &= 1204_x \\
 &= 1 \times x^3 + 2 \times x^2 + 0 \times x^1 + 4 \times x^0 \\
 &= 292_{10} \\
 &= x^3 + 2x^2 + 4 \\
 &= 6 \text{ (By substitution)}
 \end{aligned}$$

24. (b)

Gray codes are less error-prone for mechanical devices that involve making and breaking electrical circuits because they only change in one bit position at a time.

So, they are considered as the minimum error code.

25. (b)

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

$$I_0 = I_3 = S_1 \text{ and } I_1 = I_2 = S_0$$

So,

$$\begin{aligned}
 Y &= \bar{S}_1 \bar{S}_0 S_1 + \bar{S}_1 S_0 S_0 + S_1 \bar{S}_0 S_0 + S_1 S_0 S_1 \\
 &= \bar{S}_1 S_0 + S_1 S_0 = S_0
 \end{aligned}$$

So, whenever $S_0 = B$, output (Y) = B

So, option (b) is correct.

26. (c)

All the statements are correct.

27. (d)

- S_1 is incorrect, as mentioned in question would required five 4X1 MUX instead of three.
- S_2 is incorrect, as it is not always the case. For example, the function $f(x, y, z) = \sum_m(2, 4, 5, 6)$ can have different PI when group differently in K-map.

28. (d)

Let $x = y \odot z$

So, $x \odot y \odot z$

$$\frac{y \odot z}{P} \odot \frac{y \odot z}{P}$$

and $P \odot P = 1$. So option (d) is correct.

29. (a)

Truth table for BCD to excess-3 code output:

Decimal Value	Input				Output				Decimal Value
	P	Q	R	S	P	Q	R	S	
0	0	0	0	0	0	0	1	1	3
1	0	0	0	1	0	1	0	0	4
2	0	0	1	0	0	1	0	1	5
3	0	0	1	1	0	1	1	0	6
4	0	1	0	0	0	1	1	1	7
5	0	1	0	1	1	0	0	0	8
6	0	1	1	0	1	0	0	1	9
7	0	1	1	1	1	0	1	0	10
8	1	0	0	0	1	0	1	1	11
9	1	0	0	1	1	1	0	0	12

K-map for P: $f(P, Q, R, S) = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$

PQ \ RS		RS			
		00	01	11	10
00	PQ				
01	PQ		1	1	1
11	PQ	X	X	X	X
10	PQ	1	1	X	X

$$= P + QS + QR$$

$$= P + Q(S + R)$$

30. (a)

In the given digital circuit each multiplexer is working as a NOT gate thus it is a ring oscillator with five NOT gates.

The frequency of oscillation will be $f = \frac{1}{2Nt_{pd}}$.

N = number of NOT gates in cascade

t_{pd} = propagation delay of each NOT gate.

$$\therefore f = \frac{1}{2 \times 5 \times 25ns} = 4 \times 10^6 \text{ Hz} = 4 \text{ MHz.}$$

