

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612**EC + EE****DIGITAL ELECTRONICS****Duration : 1:00 hr.****Maximum Marks : 50**

Read the following instructions carefully

1. This question paper contains **30** objective questions. **Q.1-10** carry one mark each and **Q.11-30** carry two marks each.
2. Answer all the questions.
3. Questions must be answered on Objective Response Sheet (**ORS**) by darkening the appropriate bubble (marked **A, B, C, D**) using HB pencil against the question number. Each question has only one correct answer. In case you wish to change an answer, erase the old answer completely using a good soft eraser.
4. There will be **NEGATIVE** marking. For each wrong answer **1/3rd** of the full marks of the question will be deducted. More than one answer marked against a question will be deemed as an incorrect response and will be negatively marked.
5. Write your name & Roll No. at the specified locations on the right half of the **ORS**.
6. No charts or tables will be provided in the examination hall.
7. Choose the **Closest** numerical answer among the choices given.
8. If a candidate gives more than one answer, it will be treated as a **wrong answer** even if one of the given answers happens to be correct and there will be same penalty as above to that questions.
9. If a question is left blank, i.e., no answer is given by the candidate, there will be **no penalty** for that question.

DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO


Q.No. 1 to Q.No. 10 carry 1 mark each

Q.1 The value of X and Y is

$$(1110011.0011)_2 = (X)_8 = (Y)_{10}$$


- (a) $X = 163.14$ $Y = 110.3$
 (b) $X = 163.14$ $Y = 115.1875$
 (c) $X = 155.30$ $Y = 110.3$
 (d) $X = 155.3$ $Y = 115.1875$

 Q.2 The output of the 4-bit comparator is




- (a) $X = 1, Y = 0, Z = 0$
 (b) $X = 0, Y = 1, Z = 0$
 (c) $X = 1, Y = 0, Z = 1$
 (d) $X = 0, Y = 0, Z = 1$

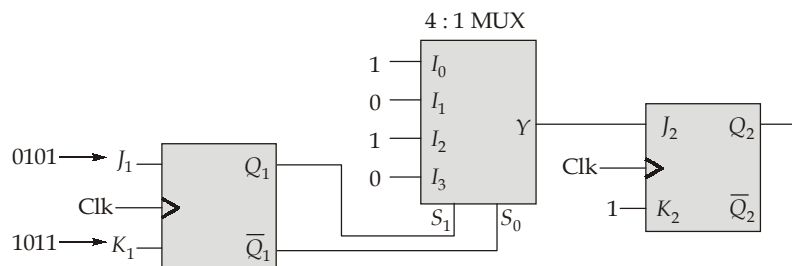Q.3 Identify the state of the flip-flops Q_2Q_1 after 3 clock cycles if the initial state, $Q_1Q_2 = 01$.



- (a) 10
 (b) 11
 (c) 01
 (d) 00

 Q.4 The final expression Y at the output of the MUX is




- (a) $A + B$
 (b) A
 (c) $A + \bar{B}$
 (d) \bar{B}

Q.5 The input clock frequency to an 8-bit successive approximation ADC is 5 MHz. The time required to convert 16 V analog input into equivalent digital output is

- (a) $0.5 \mu\text{sec}$
 (b) $1 \mu\text{sec}$
 (c) $1.6 \mu\text{sec}$
 (d) $2.5 \mu\text{sec}$

 Q.6 The circuit shown below is used to implement the function $Z = f(A, B) = \bar{A} + B$. The values of P and Q are:




- (a) $P = A, Q = B$ (b) $P = B, Q = \bar{A}$
 (c) $P = \bar{B}, Q = 0$ (d) $P = 0, Q = \bar{B}$

Q.7 A 4-bit ripple counter and 4-bit synchronous counter are made by flip-flops having propagation delay of 10 ns each. If the worst case delay in the ripple counter and the synchronous counter be R and S respectively then,


- (a) $R = 10 \text{ ns}, S = 40 \text{ ns}$
 (b) $R = 40 \text{ ns}, S = 10 \text{ ns}$
 (c) $R = 10 \text{ ns}, S = 30 \text{ ns}$
 (d) $R = 30 \text{ ns}, S = 10 \text{ ns}$

 Q.8 The MUX shown below is 4×1 multiplexer. The output for an input of A, B, C will be




- (a) ABC (b) $A \oplus B \oplus C$
 (c) $A \odot B \odot C$ (d) $A + B + C$

 Q.9 The circuit shown below represents a Boolean expression. Number of minterms present in the Boolean expression are



- (a) 4 (b) 6
 (c) 8 (d) 12

 Q.10 In the given counter, each flip-flop has a propagation delay of 8 ns.




The worst-case (longest) delay time from a clock pulse to the arrival of the counter in a given state is

- (a) 10 nsec (b) 12 nsec
 (c) 15 nsec (d) 24 nsec

Q.No. 11 to Q.No. 30 carry 2 marks each

 Q.11 Which of the following represents the correct state diagram for circuit given with input X and output Y ?



- (a)
- (b)
- (c)
- (d)


Q.12 Consider the Boolean expression given below

$$Y = A\bar{B}C + \overline{\overline{A}B(C+D)} + B\bar{C}$$

The simplified Boolean expression for Y is


- (a) $\bar{A}\bar{B} + BC$
- (b) $A\bar{B} + \bar{B}C$
- (c) $\bar{A}B + \bar{B}\bar{C}$
- (d) $\bar{A}B + B\bar{C}$

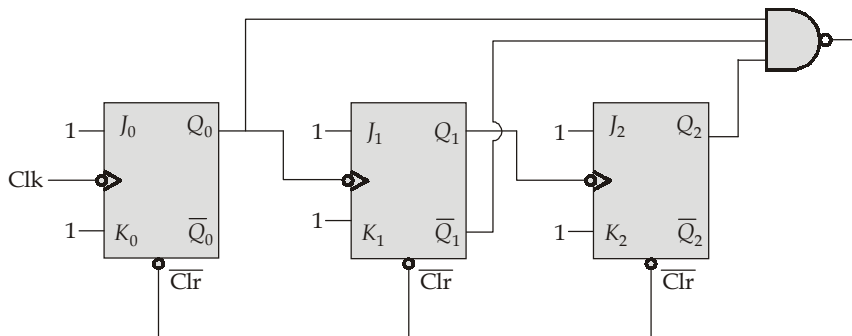Q.13 Identify the type of asynchronous counter and the MOD number. Assume initial state $Q_2Q_1Q_0$ to be 000.




- (a) Up-counter, MOD-3
- (b) Down-counter, MOD-5
- (c) Up-counter, MOD-5
- (d) Down-counter, MOD-3

Q.14 The output Y can be represented by

 


- (a) $B(A+B)(\bar{A}+\bar{B})$
- (b) $(A+B)(\bar{A}+\bar{B})A$
- (c) $(A+\bar{B})(\bar{A}+B)$
- (d) $(\bar{A}+\bar{B})(\bar{A}+B)$

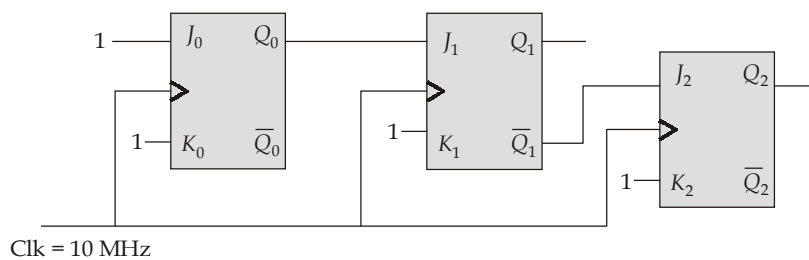Q.15 In the circuit given below, initial state $Q_0Q_1Q_2 = 000$. The time taken by state $Q_2Q_1Q_0$ to become 110 is



- (a) 0.1 μ sec
- (b) 0.2 μ sec
- (c) 0.3 μ sec
- (d) 0.4 μ sec

 
Q.16 If the input to the ladder DAC is 1000. What is the value of output voltage V_0 if $R = 5\text{ k}\Omega$ and $R_f = 10\text{ k}\Omega$?



- (a) -2.5 V
- (b) 2.5 V
- (c) -5 V
- (d) 5 V


Q.17 In the given circuit, V_0 is the output, A and B are the inputs. The output can take the values 0, 1 and high impedance state (Z).

The output of the given circuit is

 


- (a) $V_0 = 0$ if $AB = 00$
- (b) $V_0 = 1$ if $AB = 11$
- (c) $V_0 = 1$ if $AB = 10$
- (d) $V_0 = Z$ if $AB = 10$

 Q.18 What is the state Q_1Q_0 of the counter after 3 clock cycles, given initial state of the counter $Q_0Q_1 = 10$?




- (a) 11
- (b) 10
- (c) 01
- (d) 00

 Q.19 The minimum number of 2-input NAND gates required to realise the minimized output expression Y of the given 4×1 MUX is



- (a) 1
- (b) 2
- (c) 3
- (d) 4

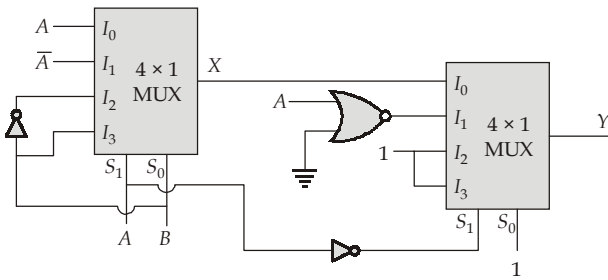Q.20 The propagation delay of 4×1 MUX is 8 ns and delay of NOR and NOT gates is 2ns. For $A = 1, B = 0$ the output Y will be stable in




- (a) 10 nsec
- (b) 5 nsec
- (c) 15 nsec
- (d) 20 nsec

Q.21 Assume $Y = f(A, B, C, D)$ the Boolean expression $Y = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$ in its simplified form is given as,


- (a) $CD + AB$
- (b) $CD + \bar{A}\bar{B}$
- (c) $AC + \bar{B}\bar{D}$
- (d) $AC + BD$

Q.22 The network shown below implements:

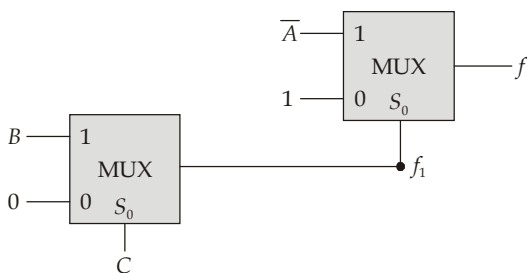

- (a) NOR gate
- (b) NAND gate
- (c) XOR gate
- (d) XNOR gate

 Q.23 The JK flip-flop shown below is initially cleared and then 5 clock pulses are applied, the sequence at the Q output will be



- (a) 010000
- (b) 011001
- (c) 010010
- (d) 010101


Q.24 A full adder is realized using only 2 input NOR gates. The minimum number of NOR gates required to realize Sum and Carry out is

- (a) 8
- (b) 9
- (c) 10
- (d) 12

Q.25 A 1-bit full-adder takes 20 ns to generate carry-out bit and 40 ns for the sum bit. The maximum rate of addition per second, when four 1-bit full adders are cascaded is

- (a) 10×10^6
- (b) 10×10^4
- (c) 5×10^6
- (d) 5×10^4

 Q.26 The three stage Johnson counter as shown in figure below is clocked at a constant frequency of 15 MHz from the starting state of $Q_2 Q_1 Q_0 = 101$. The frequency of output $Q_2 Q_1 Q_0$ will be



- (a) 5 MHz
- (b) 4.5 MHz
- (c) 6 MHz
- (d) 7.5 MHz

Q.27 If $(7.FD6)_{16} = (7.7726)_x$ and $(7864)_{10} = (1EB8)_y$. Then the values of x and y are respectively


- (a) 4 and 8
- (b) 10 and 16
- (c) 8 and 16
- (d) 8 and 8

Q.28 The minimized expression for the Boolean function

$$f(A, B, C, D) = \sum m(0, 2, 3, 4, 6, 8, 10, 11)$$


- (a) $\bar{A}\bar{D} + \bar{B}D + \bar{B}C$ (b) $\bar{A}\bar{D} + B\bar{D} + B\bar{C}$
 (c) $\bar{A}\bar{D} + \bar{B}\bar{D} + BC$ (d) $\bar{A}\bar{D} + \bar{B}\bar{D} + \bar{B}C$

 Q.29 The majority function is a Boolean function $f(x, y, z)$, that takes the value 1 whenever a majority of variables x, y, z are 1. In the circuit diagram for the majority function shown below. The logic gates for the boxes labeled P and Q are, respectively



- (a) AND, OR (b) OR, AND
 (c) EXOR, OR (d) EXOR, AND

 Q.30 The circuit shown in figure below is,



Initially both flip-flops are at 00. After two clock pulses, the content at $Q_A Q_B$ is

- (a) 00 (b) 01
 (c) 10 (d) 11

