



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Bhubaneswar | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

POWER SYSTEMS-2

ELECTRICAL ENGINEERING

Date of Test : 07/08/2023

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (c) | 7. (b) | 13. (c) | 19. (b) | 25. (c) |
| 2. (c) | 8. (a) | 14. (b) | 20. (a) | 26. (b) |
| 3. (d) | 9. (d) | 15. (d) | 21. (b) | 27. (b) |
| 4. (b) | 10. (c) | 16. (a) | 22. (c) | 28. (b) |
| 5. (a) | 11. (d) | 17. (a) | 23. (b) | 29. (b) |
| 6. (b) | 12. (b) | 18. (b) | 24. (c) | 30. (b) |

DETAILED EXPLANATIONS

1. (c)

We know,
$$Z_{pu} = \frac{Z_{act}}{Z_{base}}$$

also,
$$Z_{base} = \frac{kV_{base}^2}{MVA_{base}}$$

$$\therefore Z_{pu} = Z_{act} \times \frac{MVA_{base}}{kV_{base}^2} = x \quad \dots(1)$$

After capacity is tripled and voltage is halved,


$$Z'_{pu} = (Z_{act}) \times \frac{3MVA_{base}}{\left(\frac{kV_{base}}{2}\right)^2} = Z_{act} \times \frac{12MVA_{base}}{kV_{base}^2} \quad \dots(2)$$

Dividing equation (1) and (2),

$$\frac{x}{Z'_{pu}} = \frac{1}{12} \text{ or } Z'_{pu} = 12x$$

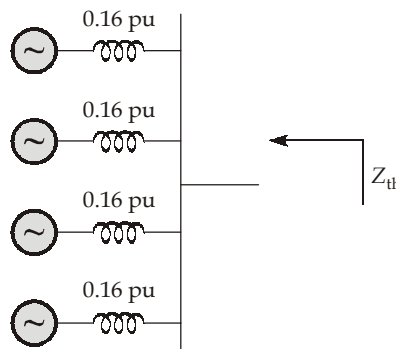2. (c)

For given power system four alternators are connected in parallel,



Thevenin's impedance,
$$Z_{th} = \frac{0.16}{4} = 0.04 \text{ pu}$$

Also, fault current in pu,
$$I_f = \frac{1}{Z_{th}} = \frac{1}{0.04} = 25 \text{ pu}$$

per unit short-circuit of system,

$$MVA_{sc} = 25 \text{ pu}$$

$$\therefore \text{short-circuit MVA, } MVA_{sc} = 25 \times \text{base MVA} \\ = 25 \times 5 = 125 \text{ MVA}$$

3. (d)

During fault, the current value increases the voltage drops, power factor decreases reactive power drawn increases generally due to reactance of line.

\therefore fault current is high having 90° lagging nature in a transmission line for phasor diagram.

The phasor of \vec{I}_2 is having largest magnitude and lags voltage V_1 by almost 90° .

So quantities \vec{V}_1 and \vec{I}_2 resembles faulty condition.

\therefore location B is most feasible fault position according to phasor diagram.

4. (b)

We know for transposed transmission line,

$$X_2 = X_s - X_m = X_1$$

$$X_0 = X_s + 2 X_m$$

Given, $X_s = 0.8 \Omega/\text{km}$ and $X_m = 0.2 \Omega/\text{km}$

where, $X_1 = +\text{ve}$ sequence reactance

$X_2 = -\text{ve}$ sequence reactance

$X_0 =$ zero sequence reactance

\therefore Negative sequence reactance,

$$X_2 = 0.8 - 0.2 = 0.6 \Omega/\text{km}$$

Zero sequence reactance,

$$X_0 = 0.8 + 2(0.2) = 1.2 \Omega/\text{km}$$

5. (a)

We know for coherently swinging generators,

$$\begin{aligned} G_{eq} \cdot H_{eq} &= G_1 H_1 + G_2 H_2 \\ &= 300 \times 1.8 + 450 \times 1 \end{aligned}$$

Also given, $G_{eq} =$ common MVA = 200 MVA

$$\therefore H_{eq} = \frac{300 \times 1.8 + 450 \times 1}{200} = 4.95 \text{ pu}$$

6. (b)

Kinetic energy \propto frequency²

$$W \propto f^2$$

$$\frac{W_1}{W_2} = \frac{f_1^2}{f_2^2}$$

$$\begin{aligned} f_2 &= f_1 \sqrt{\frac{W_2}{W_1}} = 50 \times \sqrt{\frac{500 - (0.5 \times 50)}{500}} \quad [\because W = GH = 100 \times 5 \text{ MJ}] \\ &= 48.734 \text{ Hz} \end{aligned}$$

Percentage deviation in frequency,

$$= \frac{50 - 48.734}{50} \times 100 = 2.532\%$$

Thus we can say that I_1 and I_3 currents are going into bus thus they are PQ bus and I_2 is going away from bus

\therefore Bus-2 is generator bus (PV bus).

7. (b)

This method is not directly applicable to multi-machine system.

8. (a)

Fault current at bus 3 is,

$$I_{f3} = \frac{V_3(0)}{Z_{33} + Z_f} = \frac{1}{j0.2780 + j0.15}$$

$$I_{f3} = -j 2.336 \text{ p.u.}$$

$$|I_{f3}| = 2.336 \text{ p.u.}$$

9. (d)

Zero sequence current in R line is

$$\vec{I}_{R0} = \frac{1}{3} \times \text{Current in neutral wire}$$

$$= \frac{1}{3} \times 300 \angle 300^\circ = 100 \angle 300^\circ \text{ A}$$


$$\text{Current in Y-line} = \vec{I}_Y = \vec{I}_{R0} + a^2 \vec{I}_{R1} + a \vec{I}_{R2}$$

$$= (100 \angle 300^\circ) + (1 \angle 120^\circ)^2 (200 \angle 0^\circ) + (1 \angle 120^\circ) (100 \angle 60^\circ)$$

$$= (100 \angle 300^\circ) + (200 \angle -120^\circ) + (100 \angle 180^\circ)$$

$$\vec{I}_Y = (300 \angle -120^\circ) \text{ A}$$

10. (c)

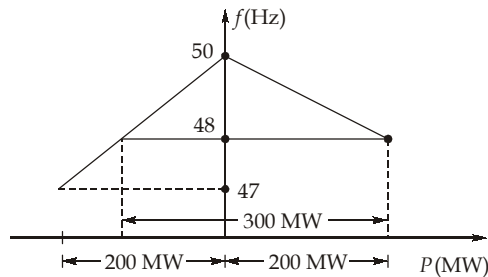

New frequency of operation of 200 MW alternator,

$$f_1 = 50 - \frac{2}{200} P_1$$

and,

$$f_2 = 50 - \frac{3}{200} P_2$$

$$\text{Total load, } P_1 + P_2 = 300 \text{ MW}$$

...(i)

Units operated in parallel so,

$$f_1 = f_2 = f$$

$$50 - \frac{2}{200} P_1 = 50 - \frac{3}{200} P_2$$

$$2P_1 - 3P_2 = 0$$

...(ii)

From equations (i) and (ii), we get

$$P_1 = 180 \text{ MW}$$

$$P_2 = 120 \text{ MW}$$

Machine (1) which has better speed regulation will be loaded first to its full load rating, so it will operate on maximum load of 200 MW.

$$2P_1 - 3P_2 = 0$$

$$2 \times 200 - 3P_2 = 0$$

...(iii)

$$P_2 = \frac{400}{3} = 133.33 \text{ MW}$$

Total power delivered by two machine without overloading

$$\therefore P_1 + P_2 = 200 + 133.33 = 333.33 \text{ MW}$$

11. (d)

We know,
$$Z_{\text{pu}} = Z_{\text{act}} \times \frac{\text{MVA}_{\text{base}}}{\text{kV}_{\text{base}}^2}$$

For generators G_1 and G_2 , base voltage remains same but MVA doubled to 40 MVA and $Z_{\text{pu}} = 0.05 \text{ pu}$.

$$\begin{aligned} \therefore Z_{\text{pu new}} &= Z_{\text{pu old}} \times \frac{\text{MVA}_{\text{new}}}{\text{MVA}_{\text{old}}} \times \left(\frac{\text{kV}_{\text{old}}}{\text{kV}_{\text{new}}} \right)^2 \\ &= 0.05 \times \frac{40}{20} (1)^2 = 0.10 \text{ or } 10\% \end{aligned}$$

For transformers base voltage is same and per unit value is given as 10% or 0.10 pu.

$$\therefore X_{\text{pu base}} = 0.10 \text{ pu} \times \frac{40}{18} = 0.22 \text{ pu}$$

For transmission line, hv side voltage will be base value,

$$Z_{\text{pu}} = Z_{\text{act}} \times \frac{\text{MVA}_{\text{base}}}{(\text{kV}_{\text{base}})^2} = 90 \times \frac{40}{(100)^2} = 0.36 \text{ pu}$$

12. (b)

Given, balanced system bus phase sequence RYB,

$$\vec{I}_R = I_R \angle 0^\circ = 10 \text{ A}$$

$$\vec{I}_Y = I_R \angle 240^\circ = a^2 10$$

$$\vec{I}_B = I_R \angle 120^\circ = a 10$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10 \\ a^2 10 \\ a 10 \end{bmatrix}$$

$$\therefore I_{R1} = \frac{1}{3} (10 + a^3 10 + a^3 10) = \frac{30}{3} = 10 \text{ A}$$

After fuses were blown,

$$I'_{R0} = I'_{R1} = I'_{R2} = \frac{10}{3} \text{ A}$$

As,
$$I_R = 10 \text{ A} \text{ and } I_Y = I_B = 0$$

$$\therefore \text{Ratio} = \frac{I_{R1}}{I'_{R1}} = \frac{10}{10/3} = 3$$

13. (c)

We know,
$$\delta = \delta_0 + \frac{P_a t^2}{M 2} \quad \dots(1)$$

Also, 5 cycles of 50 Hz frequency

$$= 20 \text{ ms} \times 5 = 100 \text{ msec} = 0.1 \text{ sec}$$

$$M = \frac{GH}{180f} = \frac{840}{180 \times 50} \text{ (MJ sec/elec. degree)} \quad \dots(\text{data in electrical degree})$$

According power,

$$P_a = P_M - P_E$$

Using equation (1) as load in removed,

$$P_a = P_M$$

$$\delta = 10^\circ + \frac{50 \times 180 \times 50 \times (0.1)^2}{2 \times 840} = 12.679^\circ \text{ electrical degree}$$

14. (b)

The short-circuit current, $I_{sc} = 6 \text{ pu}$

$$I_{sc} = \frac{100}{\% X} \times I = 6I$$

or
$$\% X = \frac{100}{6} = \frac{50}{3} = 16.67\%$$

$$\% \text{ internal reactance} = 5\%$$

$$\therefore \text{ Required extra reactance} = (16.67 - 5)\% = 11.67\%$$

Also,
$$\% X = 100 \times x \text{ pu} = 100 \times \frac{I_x}{V}$$

$$\Rightarrow x = \frac{\% x}{100} \times \frac{V}{I}$$

$$\therefore \text{ The reactance per phase, } x = \frac{11.67}{100 \times I} \times \frac{(10 \times 10^3)}{\sqrt{3}}$$

where I , full load current

$$\therefore I = I_L = \frac{VA}{\sqrt{3} V_L} = \frac{20 \times 10^6}{\sqrt{3} \times 10 \times 10^3} = 1154.7 \text{ A}$$

Using above value,
$$x = \frac{11.67 \times 10^4}{\sqrt{3} \times 100 \times 1154.7} = 0.584 \Omega$$

15. (d)

Voltage drop in each phase of generator is

$$\begin{bmatrix} \Delta V_a \\ \Delta V_b \\ \Delta V_c \end{bmatrix} = \begin{bmatrix} j2 & j1 & j1 \\ j1 & j2 & j1 \\ j1 & j1 & j2 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

or we can write in sequence components,

$$\begin{bmatrix} \Delta V_{a0} \\ \Delta V_{b0} \\ \Delta V_{c0} \end{bmatrix} = \begin{bmatrix} X_0 & 0 & 0 \\ 0 & X_1 & 0 \\ 0 & 0 & X_2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

$$X_0 = X_s + 2X_m = j2 + 2(j1) = j4 \text{ p.u.}$$

$$X_1 = X_s - X_m = j2 - j1 = j1 \text{ p.u.}$$

$$X_2 = X_s - X_m = j2 - j1 = j1 \text{ p.u.}$$

$$I_f = I_a = \frac{3E_a}{X_1 + X_2 + X_0} = \frac{3 \times 1}{j(4 + 1 + 1)} = -j0.5 \text{ p.u.}$$

$$\begin{bmatrix} \Delta V_a \\ \Delta V_b \\ \Delta V_c \end{bmatrix} = \begin{bmatrix} j2 & j1 & j1 \\ j1 & j2 & j1 \\ j1 & j1 & j2 \end{bmatrix} \begin{bmatrix} -j0.5 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 0.5 \\ 0.5 \end{bmatrix}$$

$$\begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \begin{bmatrix} E_{an} \\ E_{bn} \\ E_{cn} \end{bmatrix} - \begin{bmatrix} \Delta V_a \\ \Delta V_b \\ \Delta V_c \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} - \begin{bmatrix} 1 \\ 0.5 \\ 0.5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0.5 \\ 0.5 \end{bmatrix}$$

16. (a)

From coordination equation,

$$\frac{dF_n}{dP_{Gn}} \cdot \frac{1}{1 - \frac{\partial P_L}{\partial P_{Gn}}} = \lambda$$

Given, $P_L = 0.5P_{G1}^2$

So, $\frac{dF_1}{dP_{G1}} \cdot \frac{1}{1 - P_{G1}} = \frac{dF_2}{dP_{G2}} \cdot \frac{1}{1 - 0}$

$$\Rightarrow 10000 \times \frac{1}{1 - P_{G1}} = 12500$$

$$P_{G1} = \frac{1}{5} \text{ p.u.}$$

as the base value of 100 MVA

$$P_{G1} = \frac{1}{5} \times 100 = 20 \text{ MVA}$$

$$P_L = 0.5P_{G1}^2 = 0.5 \times \left(\frac{1}{5}\right)^2 = 0.02 \text{ p.u.}$$

$$= 0.02 \times 100 = 2 \text{ MVA}$$

$$P_D = P_{G1} + P_{G2} - P_L$$

$$40 = 20 + P_{G2} - 2$$

$$\Rightarrow P_{G2} = 22 \text{ MVA}$$

17. (a)

Given, $P_e = 50 \text{ MW}$

$$\text{K.E.} = 800 \text{ MJ}$$

$$f = 50 \text{ Hz;}$$

$$\delta_0 = 10^\circ$$

$$\text{Time for 8 cycles} = \frac{8}{50} = 0.16 \text{ sec}$$

$$\text{Time for 4 cycles} = 0.08 \text{ sec}$$

$$P_a = 50 \text{ MW}$$

$$M = \frac{K.E.}{180f} = \frac{GH}{180 \times f}$$

$$M = \frac{800}{180 \times 50} = 0.088$$

We know that, $M \frac{d^2\delta}{dt^2} = P_a$

$$\frac{d^2\delta}{dt^2} = \frac{P_a}{M}$$


Integrating twice we have,

$$\delta = \frac{P_a}{M} \left[\frac{t^2}{2} \right] + \delta_0 = \frac{50}{0.088} \left[\frac{0.08^2}{2} \right] + 10^\circ$$

New value of power angle = $1.81^\circ + 10^\circ = 11.81^\circ$

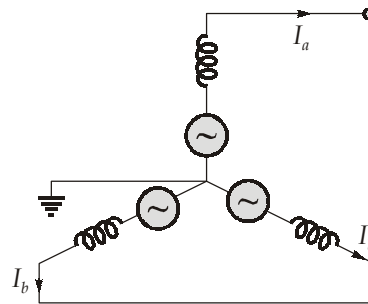18. (b)

Line-to line fault occurs on *b* and *c* phases of generator,




$$I_f = I_b = -I_c$$

$$I_a = 0$$

and

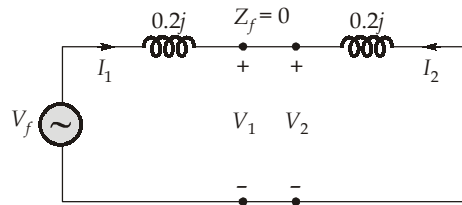The sequence network for line to line fault is



$$I_1 = \frac{V_f}{z_1 + z_2}$$

$$\Rightarrow I_f = I_b = (\alpha^2 - \alpha)I_1 = -j\sqrt{3}I_1 = \frac{-j\sqrt{3}V_f}{z_1 + z_2}$$

and

$$I_{f \text{ p.u.}} = \frac{-j\sqrt{3} \times 1}{j0.2 + j0.2}$$

$$|I_{f \text{ p.u.}}| = \frac{\sqrt{3}}{0.4} = 4.33 \text{ p.u.}$$

$$\text{Base current} = \frac{25 \times 10^3}{\sqrt{3} \times 11} = 1312.16 \text{ A}$$

$$\text{Fault current, } I_f = 4.33 \times 1312.16 = 5.68 \text{ kA}$$

19. (b)

For the fully transposed transmission line,

Positive sequence impedance $Z_1 = Z_s - Z_m$

Negative sequence impedance $Z_2 = Z_s - Z_m$

Zero sequence impedance, $Z_0 = Z_s + 2Z_m + 3Z_n$

Where, $Z_s =$ Self impedance/ph

$Z_m =$ Mutual impedance/ph

If the system voltages are unbalanced, we have a neutral current, I_n flowing through the neutral (ground) having impedance Z_n .

From above equations, we can say

1. Positive and negative sequence impedance are equal.
 2. Zero sequence impedance is much larger than the positive or negative sequence impedance.
- ∴ Statement (I) is true and statement (II) is false.

20. (a)

Total Kinetic energy of the two machines,


$$\begin{aligned} &= G_1 H_1 + G_2 H_2 \\ &= 400 \times 4 + 1600 \times 2 \\ &= 4800 \text{ MJ} \end{aligned}$$

The equivalent H on the base of 200 MVA,

$$\begin{aligned} &= \frac{4800 \text{ MJ}}{200 \text{ MVA}} \\ &= 24 \text{ MJ/MVA} \end{aligned}$$

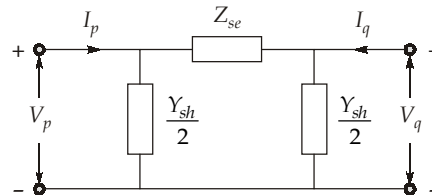21. (b)


Y-bus matrix for the π equivalent circuit.



$$Y_{\text{bus}} = \begin{bmatrix} \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} & -\frac{1}{Z_{se}} \\ -\frac{1}{Z_{se}} & \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} \end{bmatrix}$$

Here, $Z_{se} = jX; Y_{sh} = 0$

The above circuit diagram becomes,

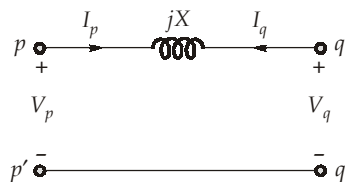

∴
$$Y_{\text{bus}} = \begin{bmatrix} \frac{1}{jX} & -\frac{1}{jX} \\ -\frac{1}{jX} & \frac{1}{jX} \end{bmatrix}$$

22. (c)

$$\begin{aligned} \text{Minimum number of equations} &= 2n - m - 2 \\ &= 2(112) - 20 - 2 \\ &= 202 \end{aligned}$$

23. (b)


Let the base kVA be 500 kVA and base voltage be 2.5 kV,
Per unit transient reactance of generator,

$$X_g' = \frac{j8}{100} = j0.08 \text{ p.u.}$$

Per unit subtransient reactance of each motor,

$$X_m'' = j0.2 \times \frac{500}{250} = j0.4 \text{ p.u.}$$

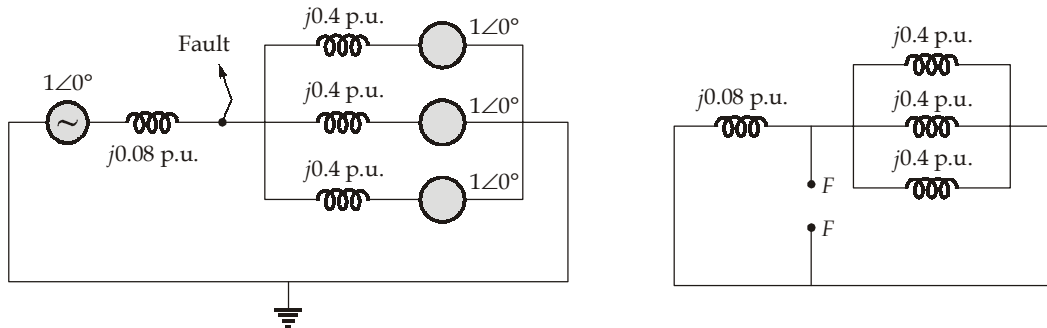Per unit reactance diagram is shown below,



Thevenin reactance when viewed from fault terminals,

$$X_{th} = \frac{\frac{j0.4}{3} \times j0.08}{\frac{j0.4}{3} + j0.08} = j0.05 \text{ p.u.}$$

At fault location $V_{th} = \text{rated voltage}$,

$$\text{Fault current at } F, I_f = \frac{1}{j0.05} = -j20 \text{ p.u.}$$

The generator contribution is,

$$I_g = -j20 \times \frac{j \frac{0.4}{3}}{j \frac{0.4}{3} + j0.08}$$

$$I_g = -j12.5 \text{ p.u.}$$

Contribution of motors,

$$3I_m = I_f - I_g = -j20 - (-j12.5)$$

$$3I_m = -j7.5$$

$$I_m = -j2.5 \text{ p.u.}$$

24. (c)

Only $Y_{22}, Y_{24}, Y_{42}, Y_{44}$ will change because transmission line is connected between 2nd and 4th buses.

$$Y_{22} = -j60 + \frac{1}{Z_{se}} + \frac{Y_{sh}}{2}$$

$$= -j60 + \frac{1}{j0.1} + j20 = -j60 - j10 + j20 = -j50$$

$$Y_{24} = Y_{42} = 0 - \frac{Y_{sh}}{2} = -j20$$

$$Y_{44} = -j25 + \frac{1}{Z_{se}} + \frac{Y_{sh}}{2} = -j25 + \frac{1}{j0.1} + j20 = -j25 - j10 + j20$$

$$Y_{44} = -j15$$

25. (c)

Reactive power supplied by capacitor to bus-1,

$$Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_2||V_1|}{X} \cos \delta$$

Given that,

$$Q_{21} = 0$$

$$\frac{|V_2|^2}{X} = \frac{|V_2||V_1|}{X} \cos \delta$$

$$|V_2| = |V_1| \cos \delta$$

Given that,

$$|V_1| = 1 \text{ p.u.}$$

$$|V_2| = \cos \delta \quad \dots(i)$$

Since load demand at bus 2 is 1 p.u. (real power). This real power can be supplied by generator S_{G1} only. So this power should flow through transmission line from bus 1 to bus 2

$$\therefore P_{12} = 1 \text{ p.u.}$$

\(\therefore\) real power flow from bus 1 to bus 2,

$$P_{12} = \frac{|V_1||V_2|}{X} \sin \delta$$

$$1 = \frac{1 \cdot \cos \delta}{0.5} \cdot \sin \delta$$

$$0.5 = \frac{\sin 2\delta}{2}$$

$$\sin 2\delta = 1$$

$$2\delta = 90^\circ$$

$$\delta = 45^\circ$$

\(\therefore\) from equation (i),

$$|V_2| = \cos \delta = \cos 45^\circ = \frac{1}{\sqrt{2}}$$

$$\text{Voltage at bus-2, } V_2 = \frac{1}{\sqrt{2}} \angle -45^\circ$$

26. (b)

Given, before fault,

$$0.6 P_{m1} = P_{m1} \sin \delta_0$$

$$\therefore \delta_0 = 36.86^\circ \text{ (or) } 0.643 \text{ radian}$$

During fault,

$$P_{m2} = 0.25 P_{m1} \text{ as } X_2 = 4X_1$$

After fault,

$$P_{m3} = 0.75 P_{m1} \text{ (given)}$$

$$\begin{aligned} \therefore \delta_{\max} &= 180 - \sin^{-1} \left(\frac{0.6 P_{m1}}{0.75 P_{m1}} \right) \\ &= 126.86^\circ \text{ (or) } 2.214 \text{ radian} \end{aligned}$$

Since,


$$\begin{aligned} \cos \delta_{cr} &= \frac{P_s(\delta_{\max} - \delta_0) + P_{m3} \cos \delta_m - P_{m2} \cos \delta_0}{P_{m3} - P_{m2}} \\ \cos \delta_{cr} &= \frac{0.6 P_{m1} [2.214 - 0.643] + 0.75 P_{m1} \cos(126.86) - 0.25 P_{m1} \cos(36.86)}{0.75 P_{m1} - 0.25 P_{m1}} \\ &= \frac{0.6(2.214 - 0.643) + 0.75 \cos(126.86) - 0.25 \cos(36.86)}{0.75 - 0.25} \\ \cos \delta_{cr} &= 0.585 \\ \delta_{cr} &= 54.2^\circ \end{aligned}$$

27. (b)

The reactance in p.u. = $Z_{p.u.} = Z_{\Omega} \times \frac{\text{MVA}_b}{(\text{kV}_b)^2}$

$$\begin{aligned} Z_{\Omega} &= Z_{p.u.} \times \frac{(\text{kV}_b)^2}{(\text{MVA}_b)} \\ &= 0.10 \times \frac{(33)^2}{10} = 10.89 \Omega \end{aligned}$$

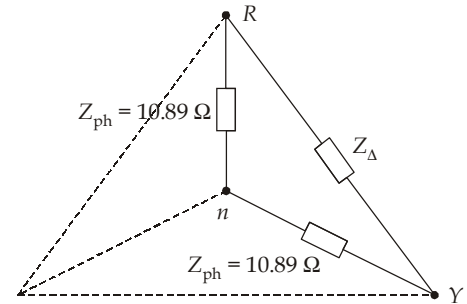So reactance per phase = $Z_{ph} = 10.89 \Omega$
 $Z_{\Delta} = 3 \times Z_{ph} = 3 \times 10.89$
 $Z_{\Delta} = 32.67 \Omega$



28. (b)

$$S_{D2} = (0.8 + j0) \text{ p.u.}$$

This 0.8 p.u. active power is supplied by the generator G_1


$$\begin{aligned} \therefore 0.8 &= \frac{1 \times 1}{0.5} \sin \delta \\ \delta &= \sin^{-1} \left(\frac{0.8}{2} \right) = 23.58^\circ \end{aligned}$$

$$\begin{aligned} Q_R &= \frac{|V_1| \times |V_2|}{X} \cos \delta - \frac{|V_1|^2}{X} \\ &= \frac{1}{0.5} \cos(23.58^\circ) - \frac{1}{0.5} \end{aligned}$$

$$Q_R = -0.167 \text{ p.u.}$$

The VAR rating of the capacitor = 0.167 p.u.

29. (b)

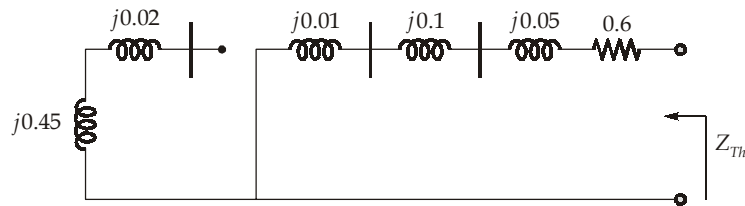The zero sequence impedance network from point P and ground

The Thevenin's equivalent zero sequence impedance

$$Z_{Th} = (0.6 + j 0.16) \text{ p.u.}$$

30. (b)

3- ϕ fault current:

Let system is under no load condition before fault,

$$\therefore E = 1 \angle 0^\circ \text{ p.u.}$$

$$\text{3-}\phi \text{ fault current, } I_f = \frac{E}{X_1}$$

$$\Rightarrow X_1 = \frac{1}{-j5} = j0.2 \text{ p.u.}$$

Line-line fault current:

$$I_f = \frac{\sqrt{3}E}{X_1 + X_2}$$

$$\Rightarrow X_1 + X_2 = \frac{\sqrt{3}}{-j2.5}$$

$$\Rightarrow j 0.2 + X_2 = j 0.69 \text{ p.u.}$$

$$\Rightarrow X_2 = j 0.49 \text{ p.u.}$$

