

Electronics Engineering

Network Theory

Comprehensive Theory

with Solved Examples and Practice Questions



MADE EASY
Publications



MADE EASY Publications

Corporate Office: 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016

E-mail: infomep@madeeasy.in

Contact: 011-45124660, 8860378007

Visit us at: www.madeeasypublications.org

Network Theory

Copyright © by MADE EASY Publications.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

First Edition : 2015

Second Edition : 2016

Third Edition : 2017

Fourth Edition : 2018

Fifth Edition : 2019

Sixth Edition : 2020

Contents

Network Theory

Chapter 1

Basic and Electric Circuits 1

1.1 Introduction.....	1
1.2 Charge.....	1
1.3 Current.....	2
1.4 Voltage.....	3
1.5 Power.....	4
1.6 Energy.....	5
1.7 Circuit Elements.....	5
1.8 Sources.....	8
<i>Student's Assignments</i>	11

Chapter 2

Basic Laws 15

2.1 Introduction.....	15
2.2 Ohm's Law and Resistance.....	15
2.3 Nodes, Paths, Loops and Branches.....	17
2.4 Kirchhoff's Current Law (KCL).....	18
2.5 Kirchhoff's Voltage Law (KVL).....	19
2.6 Series Resistances and Voltage Division.....	19
2.7 Parallel Resistances and Current Division.....	20
2.8 Source Transformation.....	21
2.9 Sources in Series or Parallel.....	22
2.10 Wye-Delta Transformations.....	24
2.11 Network Manipulations for Easy Analysis.....	25
<i>Student's Assignments</i>	32

Chapter 3

Basic Nodal and Mesh Analysis 38

3.1 Introduction.....	38
3.2 Nodal Analysis.....	38
3.3 Nodal Analysis with Voltage Source.....	40
3.4 Mesh Analysis.....	41
3.5 Mesh Analysis with Current Sources.....	43
3.6 Comparison Between Nodal Analysis and Mesh Analysis.....	44
<i>Student's Assignments</i>	49

Chapter 4

Circuit Theorems..... 53

4.1 Introduction.....	53
4.2 Linearity and Superposition.....	53
4.3 Source Transformation.....	55
4.4 Thevenin's Theorem.....	56
4.5 Norton's Theorem.....	58
4.6 Maximum Power Transfer.....	59
<i>Student's Assignments</i>	69

Chapter 5

Capacitors and Inductors..... 73

5.1 Introduction.....	73
5.2 Voltage, Current and Energy Relationship of a Capacitor.....	74
5.3 Capacitance Combinations.....	76
5.4 Inductors.....	77
5.5 Voltage, Current and Energy Relationship of an Inductor.....	77
5.6 Inductor Combinations.....	78
<i>Student's Assignments</i>	83

Chapter 6

First Order RL and RC Circuits 86

6.1 Introduction.....	86
6.2 Definition of the Laplace Transform.....	87
6.3 Circuit Elements in the s-domain.....	90
6.4 Source-Free or Zero-Input Response.....	93
6.5 Step Response of First Order Circuit.....	99
<i>Student's Assignments</i>	112

Chapter 7

Second Order RLC Circuits 117

7.1 Introduction.....	117
7.2 Finding Initial and Final Values.....	117
7.3 The Source-Free Series RLC Circuit.....	119

7.4	Source-Free Parallel RLC Circuit	122
7.5	Step By Step Approach of Solving Second Order Circuits	125
7.6	Step Response of Series RLC Circuit	125
7.7	Step Response of Parallel RLC Circuit.....	126
7.8	Circuit Analysis in the s-Domain	128
	<i>Student's Assignments</i>	139

Chapter 8

Sinusoidal Steady-State Analysis 143

8.1	Introduction	143
8.2	Sinusoids	143
8.3	Phasors.....	145
8.4	Phasor Relationship for Circuit Elements	146
8.5	Impedance and Admittance	148
8.6	Kirchhoff's Laws in the Frequency Domain	149
8.7	Impedance Combinations	150
8.8	Circuit Analysis in Phasor Domain	152
8.9	Phasor Diagrams	158
	<i>Student's Assignments</i>	170

Chapter 9

AC Power Analysis 176

9.1	Introduction	176
9.2	Instantaneous Power	176
9.3	Average Power	177
9.4	Effective Values of Current and Voltage	178
9.5	Average Value of Periodic Waveform	180
9.6	Apparent Power and Complex Power	181
	<i>Student's Assignments</i>	190

Chapter 10

Magnetically Coupled Circuits..... 195

10.1	Introduction	195
10.2	Self Inductance	195
10.3	Mutual Inductance	196
10.4	The Ideal Transformer	202
	<i>Student's Assignments</i>	210

Chapter 11

Frequency Response & Resonance.....213

11.1	Introduction	213
11.2	Transfer Functions.....	213
11.3	Resonant Circuit	214
	<i>Student's Assignments</i>	231

Chapter 12

Two Port Network 233

12.1	Introduction	233
12.2	Z-parameters	233
12.3	Y-parameters.....	235
12.4	h-parameters or Hybrid Parameters.....	236
12.5	g-parameters or Inverse Hybrid Parameters	237
12.6	Transmission Parameters (ABCD)	238
12.7	Inverse Transmission Parameters	239
12.8	Inter Relations in Network Parameters.....	240
12.9	Interconnection of Two-port Networks	241
12.10	Network Components	243
12.11	Barletts Bisection Theorem	244
12.12	Open Circuited and Short Circuited Impedances....	244
	<i>Student's Assignments</i>	254

Chapter 13

Network Topology 260

13.1	Introduction	260
13.2	Network Graph.....	260
13.3	Tree and Co-Tree.....	262
13.4	Incidence Matrix.....	263
13.5	Tie-Set	265
13.6	Cut-Set	266
13.7	Duality	268
	<i>Student's Assignments</i>	273



Second Order RLC Circuits

7.1 Introduction

In the previous chapter we studied circuits which contained only one energy storage element, combined with a passive network which partly determined how long it took either the capacitor or the inductor to charge/discharge. The differential equations which resulted from analysis were always first-order. In this chapter we will consider circuits containing two storage elements. These are known as second-order circuits because their responses are described by differential equations that contain second derivatives.

Our analysis of second-order circuits will be similar to that used for first-order. We will first consider circuits that are excited by the initial conditions of the storage elements. Although these circuits may contain dependent sources, they are free of independent sources. These source-free circuits, will give natural responses as expected. Later we will consider circuits that are excited by independent sources. These circuits will give both the transient response and the steady-state response.

7.2 Finding Initial and Final Values

A circuit is given and we need to find the initial and final conditions $i(0^+)$, $v(0^+)$, $\frac{dv(0^+)}{dt}$, $\frac{di(0^+)}{dt}$, $i(\infty)$ and $v(\infty)$ here $i(t)$ and $v(t)$ are the inductor current and capacitor voltage respectively.

To determine $i(0^+)$, $v(0^+)$ keep in mind that the capacitor voltage is always continuous so that

$$v(0^+) = v(0^-) \quad \dots(7.1)$$

and the inductor current is always continuous so that


$$i(0^+) = i(0^-) \quad \dots(7.2)$$

where $t = 0^-$ denotes the time just before a switching event and $t = 0^+$ is the time just after the switching event, assuming that the switching event takes place at $t = 0$.


To determine $\frac{dv(0^+)}{dt}$, $\frac{di(0^+)}{dt}$ draw the circuit at $t = 0^+$ (the circuit obtained after switching) and then try to

write the KVL or KCL equation, employing either the nodal equation or loop equation which give you required quantity more directly, then simply put condition $t = 0^+$, and find the required quantity.

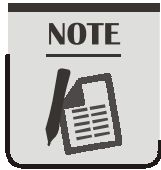To determine $i(\infty)$, $v(\infty)$ that is value of current and voltage at steady state (since at steady state the capacitor is open circuit and inductor is short circuit) so $i(\infty)$, $v(\infty)$ are the short circuit inductor current and open circuit capacitor voltage respectively. The examples at the end of the chapter illustrate these ideas.




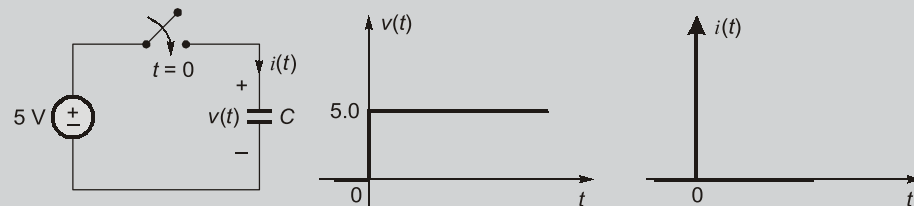- Till now we have considered that the voltage across capacitor will not change abruptly i.e. $v(0^-) = v(0^+)$ but there is an exception case as shown in the figure.




Initially the capacitor was not charged and $v(0^-) = 0$. Now the battery is connected to the circuit at $t = 0$, since the battery is ideal with $R_{Th} = 0$, so time constant of circuit $\tau = RC = 0$. So capacitor charges to 5 V instantaneously i.e. $v(0^-) \neq v(0^+)$ and current will be an impulse function in this case.

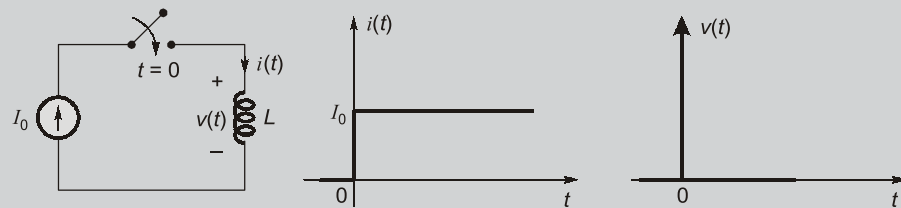- Till now we have considered that the current through inductor will not change abruptly i.e. $i(0^-) = i(0^+)$ but there is an exception case as shown in the figure.



Initially the inductor was not charged and $i(0^-) = 0$. Now the current source is connected to the circuit at $t = 0$, since the current source is ideal with $R_{Th} = \infty$, so time constant of circuit $\tau = L/R = 0$. So inductor charges to I_0 instantaneously i.e. $i(0^-) \neq i(0^+)$ and voltage will be an impulse function in this case.

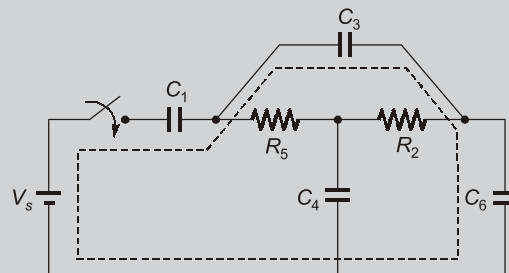- Consider the circuit given in the figure below, the switch is turn on at $t = 0$ and initial charge on each capacitor is 0 i.e. $v_c(0^-) = 0$.



All capacitors are initially uncharged and so circuit at $t = 0^+$, will have all the capacitors acting as short-circuit if we consider the path shown in the above circuit we can see that the current at $t = 0^+$ will be ∞ . Thus, $v_c(0^+) \neq v_c(0^-)$ for C_1 , C_6 , C_3 and $v_c(0^+)$ for these capacitors can be found using voltage division rule.

7.3 The Source-Free Series RLC Circuit

Consider the series RLC circuit shown in Figure (7.1). The circuit is being excited by the energy initially stored in the capacitor and inductor. The energy is represented by the initial capacitor voltage V_0 and initial inductor current I_0 . Thus, at $t = 0$,

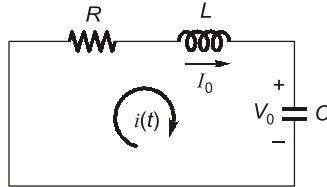


Figure-7.1 : A source-free series RLC circuit

$$v(0) = \frac{1}{C} \int_{-\infty}^0 i(t) dt = V_0 \quad \dots(7.3)$$

$$i(0) = I_0 \quad \dots(7.4)$$

Applying KVL around the loop in Figure (7.1)

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^t i(t) dt = 0 \quad \dots(7.5)$$

With the help of Laplace transform

$$i(t) \xrightarrow{\mathcal{L}} I(s)$$

$$\frac{di(t)}{dt} \xrightarrow{\mathcal{L}} sI(s) - i(0^-)$$

$$\int_{-\infty}^t i(t) dt \xrightarrow{\mathcal{L}} \frac{I(s)}{s} + \frac{\int_{-\infty}^0 i(t) dt}{s}$$

The equation (7.5) changes to, $RI(s) + L[sI(s) - I_0] + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{V_0}{s} \right] = 0$

$$I(s) = \left\{ \frac{I_0s - \frac{V_0}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} \right\} \quad \dots(7.6)$$

The denominator of the above equation is known as characteristic equation of the circuit. Roots of denominator of the above equation are

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad \dots(7.7)$$

$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad \dots(7.8)$$

A more compact way of expressing the roots is

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \dots(7.9)$$

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

The roots s_1 and s_2 are called natural frequencies, measured in nepers per second (Np/s), because they are associated with the natural response of the circuit; ω_0 is known as the resonant frequency or strictly as the undamped natural frequency, expressed in radians per second (rad/s); and α is the neper frequency or the damping factor, expressed in nepers per second. In terms of α and ω_0 , the denominator of the equation (7.6) can be written as

$$s^2 + 2\alpha s + \omega_0^2 = 0 \quad \dots(7.10)$$

The solution of equation (7.10) depends on α and ω_0 . The ratio $\frac{\alpha}{\omega_0}$ is known as the damping ratio ξ . Thus, the natural response of series RLC circuit is

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

where the constants A_1 and A_2 are determined from the initial values $i(0)$ and $\frac{di(0)}{dt}$.

From equation (7.9), we can infer that there are three types of solutions:

1. If $\alpha > \omega_0$, both the roots will be real and unequal, the response is said to be over-damped.
2. If $\alpha = \omega_0$, both the roots are real and equal, the response is said to be critically damped.
3. If $\alpha < \omega_0$, both the roots will be complex and conjugates of each other, the response is said to be under-damped.

We will consider each of these cases separately.

Overdamped Case ($\alpha > \omega_0$)

From equations (7.8) and (7.9), $\alpha > \omega_0$ implies $C > 4L/R^2$. When this happens, both roots s_1 and s_2 are negative and real. The response is

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Where A_1 and A_2 are found from the initial conditions. This shows that the natural response is the sum of two decaying exponential. For the over-damped response, damping ratio $\xi > 1$. Figure (7.2) illustrates a typical overdamped case.


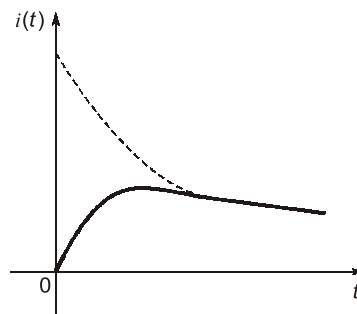


Figure-7.2: Overdamped response

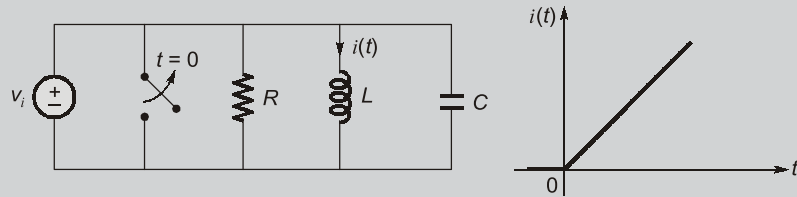- We considered the step response of the parallel RLC circuit where the input was current and response was the voltage across inductor. If we consider the response of parallel RLC circuit with voltage as input and current across the inductor as output then current across the inductor $i(t)$ will rise linearly as shown in the figure. The circuit in this case is an unstable circuit.



7.8 Circuit Analysis in the s-Domain

All the circuit analysis techniques that we have studied for pure resistive networks may be used in s-domain analysis. The node voltage method, mesh current method, source transformations, and Thevenin-Norton equivalents are all valid techniques in the s-domain. These can be applied using same methodologies as we discussed for resistive networks. The step-by-step procedure of circuit analysis in the s-domain is given below.

- **Step-1:** Draw the circuit into s-domain substituting an s-domain equivalent for each circuit element. The inductors and capacitors are replaced by their equivalent discussed in previous chapter (For inductor and capacitor we first need to determine the initial capacitor voltage and inductor current and then replace them with their s-domain equivalent).
- **Step-2:** Apply any circuit analysis technique to obtain the desired voltage or current in the s-domain.
- **Step-3:** Take inverse Laplace transform to convert the voltages and/or currents back to the time domain.

Using Laplace Transform to find which element get charged at steady-state

A circuit with inductor and capacitor is given and we need to determine that which element get charged at steady-state. For this we follow these steps:

- Convert the circuit from time domain into s-domain.
- Apply nodal analysis at the node connecting the inductor and capacitor.
- Now apply final value theorem to find value of voltage at node at $t = \infty$ and find which element get charged.

Now we shall illustrate these steps with the help of two examples.

Example-1: Consider the circuit given in the Figure 7.8, our motive is to determine which element get charged at steady-state.


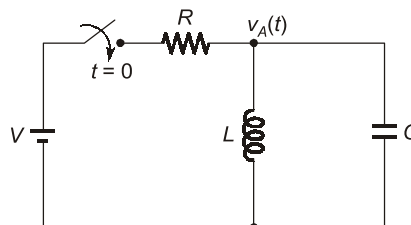


Figure-7.8

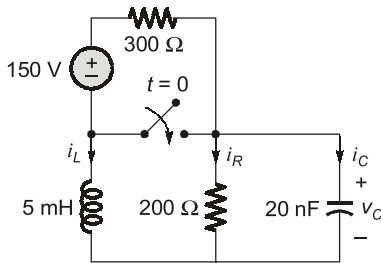


Student's Assignments 1


Q.1 Find an expression for $v_C(t)$ valid for $t > 0$ in the circuit of figure.



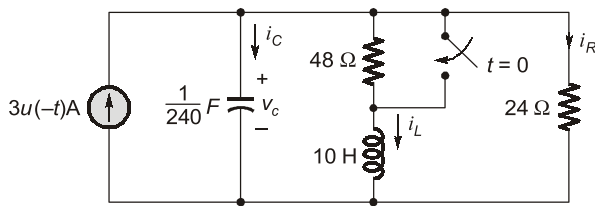
Q.2 After being open for a long time, the switch in figure, closes at $t = 0$. Find (a) $i_L(0^-)$; (b) $v_C(0^-)$; (c) $i_R(0^+)$; (d) $i_C(0^+)$; (e) $v_C(0.2)$.



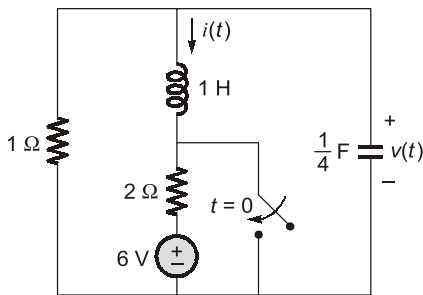
Q.3 Given the circuit in figure, find $i(t)$ and $v(t)$ for $t > 0$.



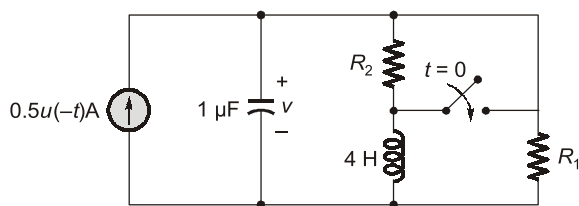
Q.4 (a) Choose R_1 in the circuit of figure, so that the response after $t = 0$ will be critically damped.
(b) Now find R_2 to obtain $v(0) = 100$ V.
(c) Find $v(t)$ at $t = 1$ ms.



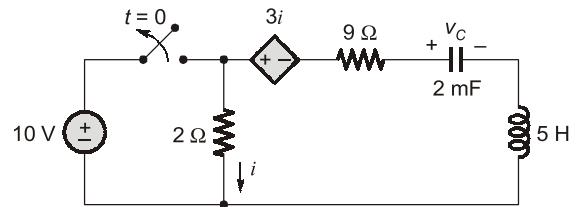
Q.5 Find an expression for $v_C(t)$ in the circuit of figure, valid for $t > 0$.



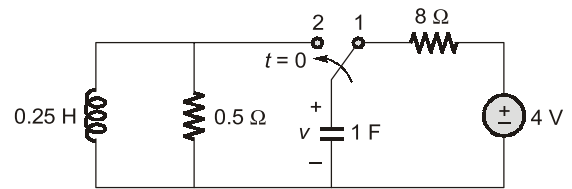
Q.6 In the circuit of figure, the switch has been in position 1 for a long time but moved to position 2 at $t = 0$. find
(a) $v(0^+)$, $dv(0^+)/dt$ (b) $v(t)$ and $t \geq 0$.



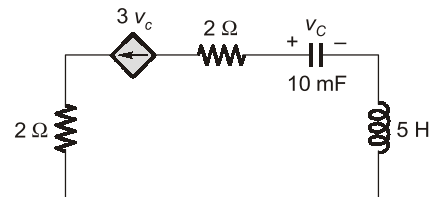
Q.7 Find an expression for $i_L(t)$ in the circuit of figure, valid for $t > 0$, if $v_C(0^-) = 10$ V and $i_L(0^-) = 0$.



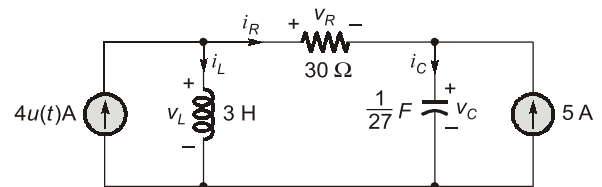
Q.8 Complete the determination of the initial conditions in the circuit of figure and determine the value of first derivative of all three voltage and current variable at $t = 0^+$.



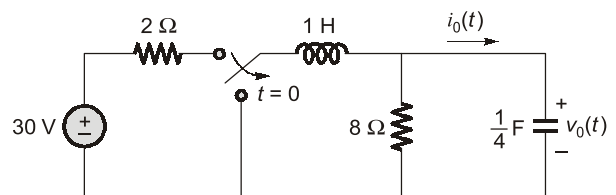
Q.9 In the circuit of figure, calculate $i_0(t)$ and $v_0(t)$ for $t > 0$.



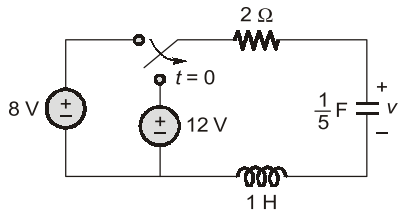
Q.10 Determine $v(t)$ for $t > 0$ in the circuit of figure.



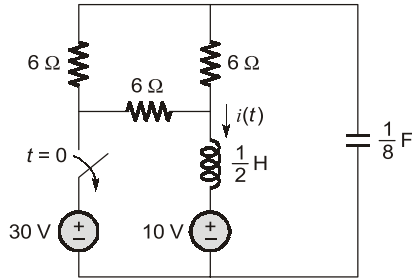
Q.11 For the network in figure, solve for $i(t)$ for $t > 0$.



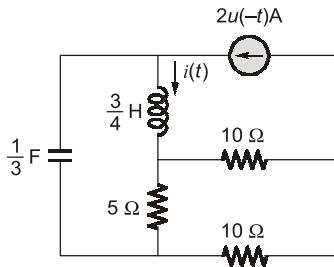
Q.12 Refer to the circuit in figure. Calculate $i(t)$ for $t > 0$.



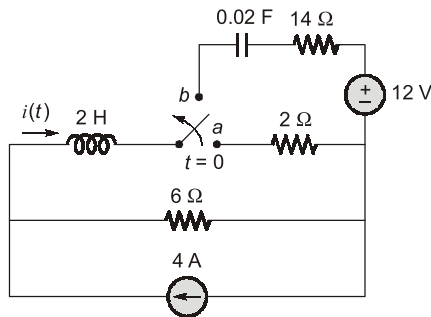Q.13 The switch in the circuit of figure is moved from position a to b at $t = 0$. Determine $i(t)$ for $t > 0$.



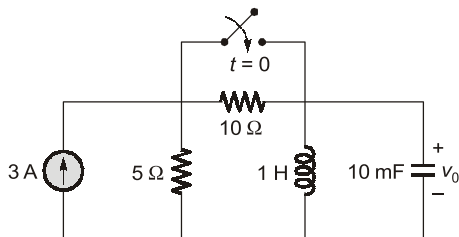Q.14 Find the output voltage $v_o(t)$ in the circuit of figure.



Answer:


1. $(80e^{-50000t} - 20e^{-200000t})$ V
2. (a) 1 A (b) 48 V (c) 2 A (d) -3 A (e) -17.54 V
3. $i(t) = (-2 - 2t)e^{-2t}$ A, $v(t) = (2 + 4t)e^{-2t}$ V
4. $(R_1 = 1 \text{ k}\Omega, R_2 = 250 \Omega, v(1 \text{ ms}) = -212 \text{ V})$
5. $-e^{-0.8t} (5 \cos 9.89t + 0.413 \sin 9.89t)$ V
6. (a) 4 V, -8 V/s (b) $e^{-t}(4 \cos 1.73t - 2.30 \sin 1.73t)$ V
7. $(-30e^{-300t})$ A
8. $V_L(0^+) = 120 \text{ V}, V_C(0^+) = 150 \text{ V}, V_R(0^+) = -30 \text{ V}$
 $\frac{dV_L(0^+)}{dt} = -1092 \text{ V/s}, \frac{dV_C(0^+)}{dt} = 108 \text{ V/s},$
 $\frac{dV_R(0^+)}{dt} = -1200 \text{ V/s}, \frac{di_R(0^+)}{dt} = -40 \text{ A/sec}$
 $\frac{di_C(0^+)}{dt} = -40 \text{ A/sec}$
9. $v_o(t) = e^{-t/4} (24 \cos 1.98t + 3.02 \sin 1.98t)$ V
 $i_o(t) = e^{-t/4} (0.00013 \cos 1.98t - 12.09 \sin 1.98t)$ A
10. $12 - e^{-t}(4 \cos 2t + 2 \sin 2t)$ V
11. $(5 e^{-4t})$ A 12. $(e^{-4.4t} + e^{-0.903t})$ A
13. $(3 - 9t)e^{-5t}$ A 14. $(200t e^{-10t})$ V



Student's Assignments

2

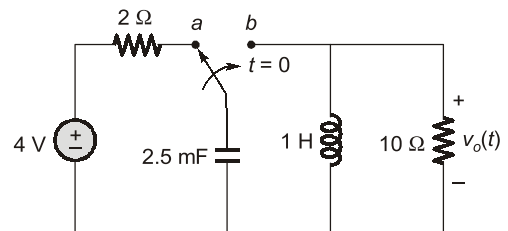Q.1 The switch in the circuit of figure below has been in position 'a' for a long time. At $t = 0$, the switch moves instantaneously to position 'b'.




If $v(t) = (Ae^{-20t} - Bte^{-20t})$ V, for $t > 0$, then the values of A and B respectively are

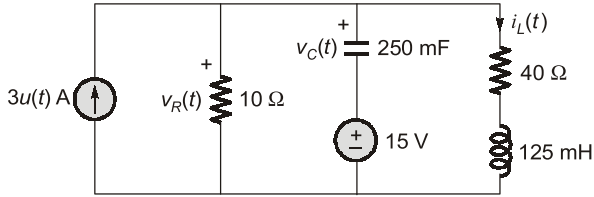- (a) 0, 80
- (b) 4, 240
- (c) 4, 80
- (d) 4, 0

Common Data Questions (9 to 10):

Consider the circuit shown in the figure, where $u(t)$ is given as unit step function.



Q.9 What are the values of $v_C(t)$ and $v_R(t)$, at $t = 0^+$ respectively?


- (a) 0, 0
- (b) -15 V, -30 V
- (c) 0, 30 V
- (d) -15 V, 0

Q.10 Which of the following sets of values is correct for the circuit at $t = 0^+$?

$\frac{di_L(0^+)}{dt}$	$\frac{dv_C(0^+)}{dt}$	$\frac{dv_R(0^+)}{dt}$
(a) 30 V/s	12 V/s	0
(b) 0	12 V/s	0
(c) 0	0	0
(d) 0	12 V/s	12 V/s

Q.11 The switch in the figure has been closed for a long time and is opened at $t = 0$. The inductor current and the capacitor voltage are zero at $t = 0$. For $t \geq 0$, $v(t)$ is given by

(Given $\omega_0 = \frac{1}{\sqrt{LC}}$)

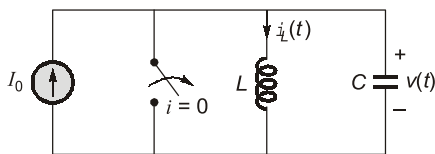


(a) $v(t) = \left(\frac{I_0}{\omega_0 C}\right) \sin \omega_0 t$

(b) $v(t) = (I_0 \omega_0 L) \cos \omega_0 t$

(c) $v(t) = \left(\frac{I_0}{\omega_0 L}\right) \sin \omega_0 t$

(d) $v(t) = (I_0 \omega_0 C) \cos \omega_0 t$

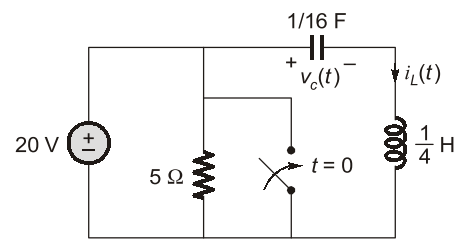Q.12 In the circuit shown below the switch is closed at $t = 0$ after long time. The current $i_L(t)$ for $t > 0$ is



- (a) $-10 \sin 8t$ A
- (b) $10 \sin 8t$ A
- (c) $-10 \cos 8t$ A
- (d) $10 \cos 8t$ A

Answer Key:

- 1. (c) 2. (c) 3. (a) 4. (b) 5. (c)
- 6. (a) 7. (d) 8. (b) 9. (d) 10. (d)
- 11. (a) 12. (a)

