

Electrical Engineering

Power Electronics

Comprehensive Theory

with Solved Examples and Practice Questions



MADE EASY
Publications



MADE EASY Publications

Corporate Office: 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016

E-mail: infomep@madeeasy.in

Contact: 011-45124660, 8860378007

Visit us at: www.madeeasypublications.org

Power Electronics

© Copyright by MADE EASY Publications.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

First Edition : 2015

Second Edition : 2016

Third Edition : 2017

Fourth Edition : 2018

Fifth Edition : 2019

Sixth Edition : 2020

Contents

Power Electronics

Chapter 1

Introduction 1

- 1.1 Block Diagram of Power Electronic Systems 1
- 1.2 Classification of The Power Semiconductors 4

Chapter 2

Power Semi-conductor Diode & Transistor 8

- 2.1 Basic Semiconductor Physics 8
- 2.2 Basic Structure and I-V Characteristics 8
- 2.3 Power Bipolar Junction Transistor: (Power BJT) 14
- 2.4 Power MOSFET 21
- 2.5 Insulated Gate Bipolar Transistor : (IGBT) 26

Chapter 3

Diode Rectifiers30

- 3.1 Single-Phase Halfwave Rectifier30
- 3.2 Single-Phase Halfwave Diode Rectifier with L-Load....32
- 3.3 Single-Phase Halfwave Diode Rectifier with C-Load....35
- 3.4 Single-Phase Halfwave Rectifier with RL-Load 36
- 3.5 Single-Phase Halfwave Diode Rectifier with RL-Load and Freewheeling Diode.....40
- 3.6 Single-Phase Halfwave Diode Rectifier with RE-Load..43
- 3.7 Single-Phase Fullwave Diode Rectifier47
- 3.8 Single-Phase Fullwave Diode Bridge Rectifier.....49
- 3.9 Performance Parameters52
- 3.10 Three-Phase Rectifier56
- 3.11 Three-Phase Halfwave Diode Rectifier56
- 3.12 Three-Phase Midpoint 6-Pulse Diode Rectifier 61
- 3.13 Three-Phase Halfwave Diode Rectifier with Common Anode Arrangement.....63
- 3.14 Three-Phase Diode Bridge Rectifier64

Chapter 4

Thyristors70

- 4.1 Thyristor.....70
- 4.2 Silicon Controlled Rectifier (SCR).....70

- 4.3 Structural Modification of the Device.....82
- 4.4 Heating and Cooling of SCR.....83
- 4.5 Series and Parallel Operation of SCR.....83
- 4.6 Firing Circuits for Thyristors.....90
- 4.7 Other Members of Thyristor Family.....95
- Student Assignments-1* 108

Chapter 5

Thyristor Commutation Techniques... 111

- 5.1 Introduction 111
- Class-A, Class-B, Class-C, Class-D, Class-E and Class-F
- Student Assignments-1* 125

Chapter 6

Phase Controlled Rectifiers..... 126

- 6.1 Introduction 126
- 6.2 Firing Angle 126
- 6.3 1- ϕ Halfwave Rectifier with R-Load..... 126
- 6.4 1- ϕ Halfwave Rectifier with RL-Load..... 131
- 6.5 1- ϕ Halfwave Rectifier with R-L Load and Free-wheeling Diode 133
- 6.6 Single Phase (1- ϕ) Halfwave Rectifier with RLE Load 136
- 6.7 1- ϕ Fullwave Mid-Point Type Rectifier 140
- 6.8 1- ϕ Fullwave Bridge Type Rectifier with R-Load 142
- 6.9 1- ϕ Fullwave Bridge Type Rectifier with RL-Load 143
- 6.10 1- ϕ Fullwave Bridge Type Rectifier with RLE Load 145
- 6.11 Inverter Mode of Operation 150
- 6.12 1- ϕ Fullwave Semi-converter with RLE Load (or) 1- ϕ Full wave Half Controlled Rectifier with Free Wheeling Diode 153
- 6.13 3- ϕ Controlled Half Wave Rectifier 163
- 6.14 3- ϕ Halfwave Rectifier with R-L Load 167

6.15 3- ϕ Full Converter (or) 3- ϕ Full wave Rectifier with R Load	168
6.16 3- ϕ Full Converter (or) 3- ϕ Full wave Bridge Rectifier with RLE Load	171
6.17 3- ϕ Fullwave Semi-converter with RLE Load and Freewheeling Diode.....	174
6.18 Effect of Source Inductance in 1- ϕ Rectifier	175
6.19 Dual Converter	182
<i>Student Assignments-1</i>	184

Chapter 7

Choppers..... 187

7.1 Definition	187
7.2 Principle of Operation of Step Down Chopper.....	187
7.3 Principle of Operation of Step-up Choppers.....	191
7.4 Step up/Step down Choppers.....	195
7.5 Switching Mode Regulators	197
7.6 First-Quadrant or Type-A Chopper	206
7.7 Second-Quadrant or Type-B Chopper	207
7.8 Type-D Chopper (or) Two Quadrant Type-B Chopper.....	208
7.9 Four Quadrant Chopper or Type-E Chopper	208
7.10 Steady State Analysis of Type A Chopper	211
7.11 Forced Commutation is of Two Types.....	215
<i>Student Assignments-1</i>	228

Chapter 8

Inverters 230

8.1 1-Phase Half Bridge Inverters.....	230
8.2 1-Phase Full Bridge Inverter	232
8.3 Fourier Analysis of 1-f Inverter Output Voltage.....	237
8.4 3-Phase Bridge Inverter	250
8.5 3-Phase 120° Mode VSI.....	257
8.6 Current Source Inverter (CSI)	263
<i>Student Assignments-1</i>	265

Chapter 9

Resonant Converters..... 268

9.1 Introduction	268
9.2 Zero-Current-Switching Resonant Converters	270
9.3 L-Type ZCS Resonant Converter.....	270
9.4 M-Type ZCS Resonance Converter (DC-DC).....	272
9.5 Zero-Voltage Switching Resonant Converters	274
9.6 Comparisons between ZCS and ZVS Resonant Converters	276

Chapter 10

Power Semiconductor Drives 277

10.1 DC Drives.....	277
10.2 AC Drives	288
10.3 Static Kramer Drive	290
10.4 Static Scherbius Drive.....	291

Chapter 11

High Frequency Inductors and Transformers 293

11.1 Design of Magnetic Components for Power Electronics	293
11.2 Magnetic Material and Cores	293
11.3 Hysteresis Loss	294
11.4 Skin Effect Limitations	294
11.5 Eddy Current Loss in Laminated Cores.....	295
11.6 Copper Windings	295
11.7 Winding Loss Due to DC Resistance of Windings.....	296
11.8 Skin Effect in Copper Windings.....	296
11.9 Thermal Considerations.....	297

Chapter 12

Switched Mode Power Supply (SMPS) 298

12.1 Switched Mode Power Supply (SMPS)	298
--	-----



Power Semiconductor Drives

10.1 DC Drives

- DC Drive consists of a DC Motor, Power Electronic Converter. i.e. Rectifier (or) chopper. Speed Sensing Mechanism – Tachometer, Feedback circuit and intelligent device (Micro controller)
- The following dc motors are suitable for speed control applications.
 1. Series motor
 2. Separately excited dc motor

In the speed control applications, load remains same i.e., output current is continuous and assumed to be constant.

$$E_a = \frac{Z\phi NP}{60A} = Z\phi n \left(\frac{P}{A} \right)$$

$$\omega_m = 2\pi n$$

$$E_a = Z\phi \left(\frac{\omega_m}{2\pi} \right) \left(\frac{P}{A} \right) = \left(\frac{Z}{2\pi} \cdot \frac{P}{A} \right) \phi \omega_m$$

$$E_a = K_a \phi \omega_m$$

where,

$$K_a = \frac{Z}{2\pi} \left(\frac{P}{A} \right)$$

$$E_a \cdot I_a \text{ (Electrical power)} = \tau_e \omega_m \text{ (Mechanical power)}$$

$$\tau_e = \frac{E_a I_a}{\omega_m}$$

$$\tau_e = K_a \phi I_a$$

Separately Excited DC Motor

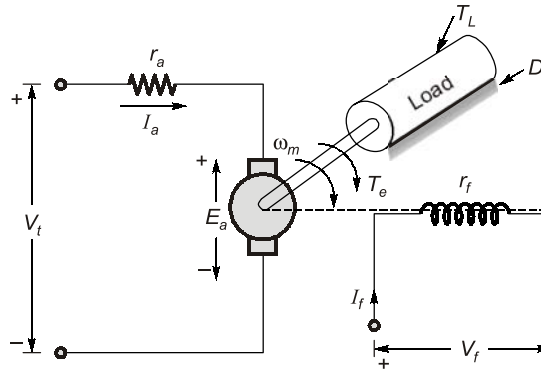


Figure-10.1

$$E_a = K_a \phi \omega_m = (K_a \phi) \omega_m \Rightarrow \boxed{E_a = K_m \omega_m}$$

where, $K_m = K_a \phi$ (V-s/rad)

$$T_e = K_a \phi I_a \Rightarrow \boxed{T_e = K_m I_a}$$

where, units of K_m are N-m/A

Example - 10.1

A 250 V separately excited DC motor has armature resistance of 2.5 ohms.

When driving a load at 600 r.p.m. with constant torque, the armature takes 20 A. The motor is controlled by a DC chopper operating with a frequency of 400 Hz and an input voltage of 250 V DC. What should be the value of duty ratio, if it is desired to reduce the speed from 600 r.p.m. to 400 rpm? Also find the motor speed at rated current and a duty ratio of 0.5, if the motor is regenerating.

Solution:

For separately excited dc motor,

Armature Resistance = 2.5 Ω

∴ back emf $E_\phi = k_n \phi N$

where $E = V_t - I_a R_a = 250 - 20 \times 2.5 = 200$ V

∴ $k_n \phi = \frac{200}{600} = \frac{1}{3}$

Let (δ) be the duty ratio, then, $V_t = \delta V_i$ [where V_i = input voltage]

$$[\delta V_i - I_a R_a] = k_n \phi \times N'$$

Since torque remains constant,

∴ 'T' should be constant

$$[\delta \times 250 - 20 \times 2.5] = \frac{1}{3} \times 400$$

$$\delta = 0.733$$

At (δ = 0.5), and given, motor is regenerating working as a generator, then

$$N' = \frac{[\delta V_i + I_a R_a]}{k_n \phi} = 3 \times [125 + 20 \times 2.5] = 525 \text{ rpm}$$

DC Series Motor

$$E_a = K_a \phi \omega_m$$

$$\phi \propto I_a$$

$$\phi = c I_a$$

$$E_a = K_a c I_a \omega_m \Rightarrow \boxed{E_a = K_1 I_a \omega_m}$$

$$T_e = K_a \phi I_a = K_a c I_a \cdot I_a \Rightarrow \boxed{T_e = K_1 I_a^2}$$

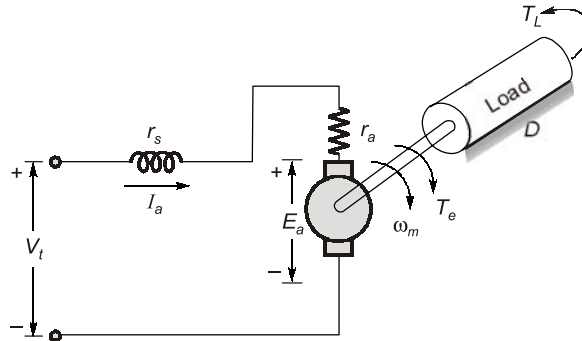


Figure-10.2

K_1 units are [N-m/A²]

1- ϕ Half wave Rectifier Drive

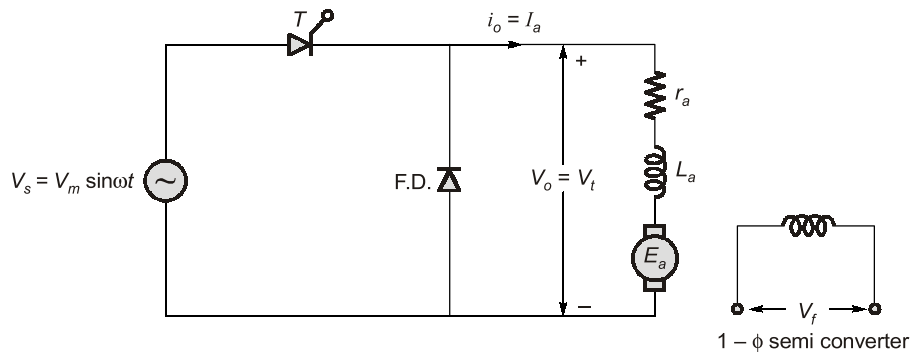


Figure-10.3

$$V_o = V_t = \frac{V_m}{2\pi} (1 + \cos \alpha_1)$$

$$V_f = \frac{V_m}{\pi} (1 + \cos \alpha_2)$$

Rms source current, $I_{sr} = I_{Tr} = I_a \sqrt{\left(\frac{\pi - \alpha_1}{2\pi}\right)}$

$$\text{Input power factor} = \frac{E_a I_a + I_a^2 r_a}{V_s I_{sr}} = \frac{I_a (E_a + I_a r_a)}{V_s \cdot I_{sr}}$$

$$\boxed{\text{Input power factor} = \frac{V_t \cdot I_a}{V_s \cdot I_{sr}}}$$

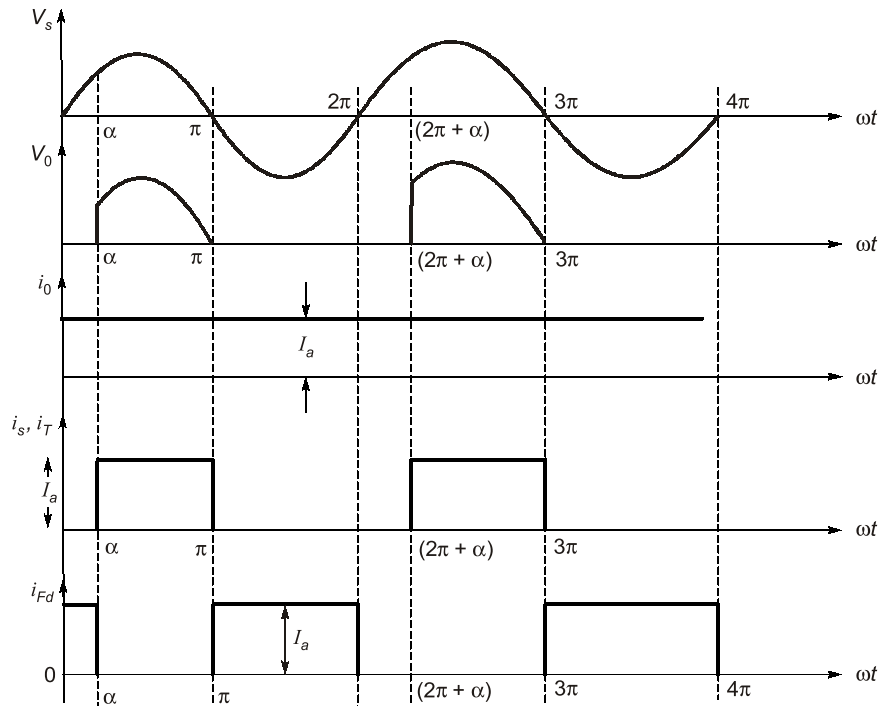


Figure-10.4

1-φ Semi Converter Drive

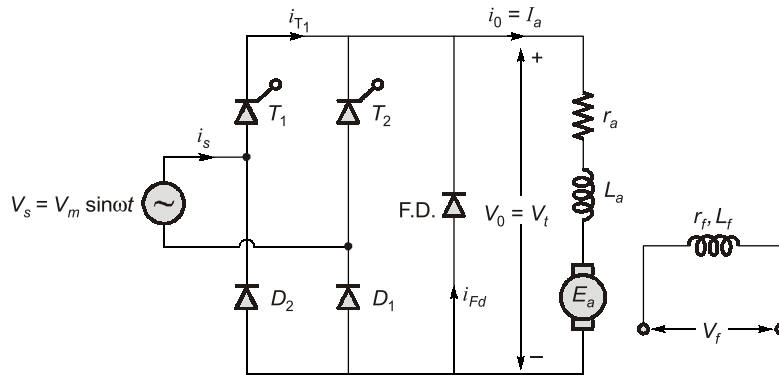


Figure-10.5

For a 1-φ semiconverter, average output voltage

$$V_0 = V_t = \frac{V_m}{\pi} (1 + \cos \alpha)$$

For field circuit,

$$V_f = \frac{V_m}{\pi} (1 + \cos \alpha_1)$$

Rms value of source current,

$$I_{s\text{ rms}} = I_a \sqrt{\left(\frac{\pi - \alpha}{\pi}\right)}$$

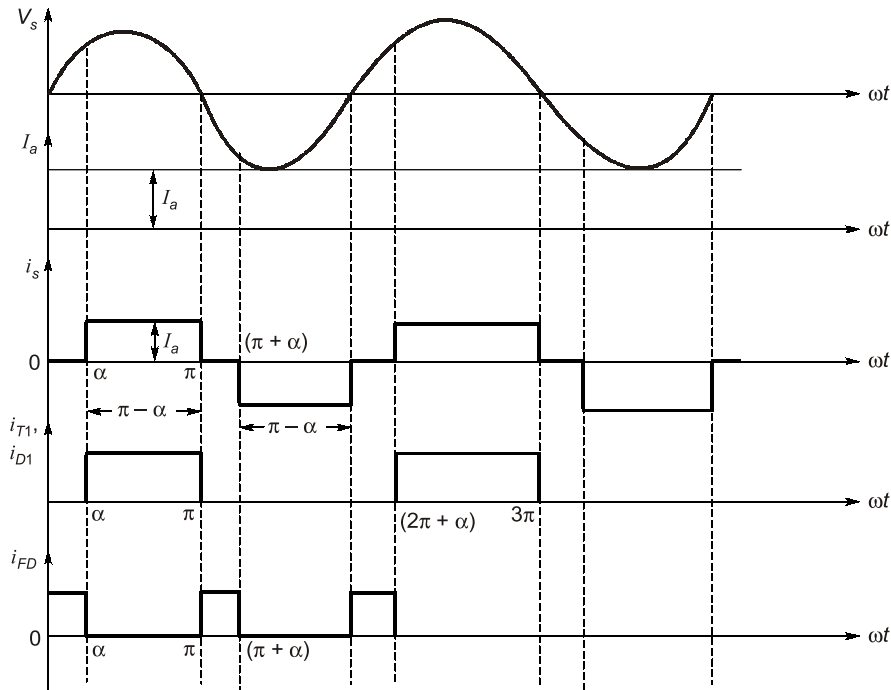


Figure-10.6

Rms value of freewheeling diode current,

$$I_{FD\text{ rms}} = I_a \sqrt{\left[\frac{\alpha}{\pi} \right]}$$

Rms value of thyristor current,

$$I_{T\text{ rms}} = I_a \sqrt{\left[\frac{\pi - \alpha}{2\pi} \right]}$$

$$\text{Input power factor} = \frac{V_t \cdot I_a}{V_s \cdot I_{sr}} = \frac{\sqrt{2} V_s \cdot (1 + \cos \alpha) \cdot I_a \sqrt{\pi}}{\pi \cdot V_s I_a \sqrt{\pi - \alpha}}$$

$$\text{Input pf} = (1 + \cos \alpha) \sqrt{\left[\frac{2}{\pi(\pi - \alpha)} \right]}$$

A 1- ϕ semiconverter is also called 1- ϕ half controlled bridge converter.

Example - 10.2

A single-phase half-controlled rectifier is driving a separately excited dc motor. The dc motor has a back emf constant of 0.25 V/rpm. The armature current is 5 A without any ripple. The armature resistance is 2 Ω . The converter is working from a 230 V, single phase ac source with a firing angle of 30°. Under this operating condition, the speed of the motor will be

- (a) 339 rpm
- (b) 346 rpm
- (c) 366 rpm
- (d) 386 rpm

Solution : (b)

$$\text{Back emf} = E_a = k\phi N$$

$$\text{or } E_a = k_b N$$

where, $k_b = \text{Back-emf constant} = 0.25 \text{ V/rpm}$

Average output voltage of 1- ϕ half controlled rectifier = V


$$V = \frac{V_m}{2\pi}(1 + \cos\alpha) = \frac{230\sqrt{2}}{2\pi}(1 + \cos 30^\circ)$$

$$\Rightarrow V = 96.6 \text{ V}$$

$$E_a = V - I_a R_a = 96.6 - 5 \times 2 = 86.6 \text{ V}$$

$$\text{Speed} = N = \frac{E_a}{k_b} = \frac{86.6}{0.25} = 346.4 \text{ V}$$

So, option (a) is closer to 346.4 V.

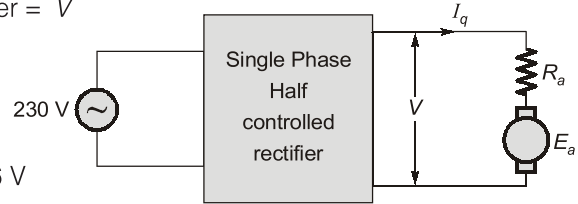**Example - 10.3**

A separately-excited dc motor is supplied from 230 V, 50 Hz source through a single-phase half-wave controlled converter. Its field is fed through 1-phase semiconverter with zero degree firing-angle delay. Motor resistance $r_a = 0.7 \Omega$ and motor constant = 0.5 V-sec/rad. For rated load torque of 15 Nm at 1000 rpm and for continuous ripple free currents, determine.

- Firing angle delay of the armature converter
- rms value of thyristor and freewheeling diode currents
- input power factor of the armature converter.

Solution:

$$(a) \quad \text{Motor constant} = 0.5 \text{ V-sec/rad} = 0.5 \text{ Nm/A} = K_m$$

$$\text{But motor torque, } T_e = K_m I_a$$

$$\therefore \text{Armature current} = \frac{15}{0.5} = 30 \text{ A}$$

$$\text{Motor emf, } E_a = K_m \omega_m = 0.5 \times \frac{2\pi \times 1000}{60} = 52.36 \text{ V}$$

For 1-phase half-wave converter feeding a dc motor.

$$V_t = \frac{V_m}{2\pi}(1 + \cos\alpha) = E_a + I_a r_a$$

$$\text{or } V_t = \frac{\sqrt{2} \times 230}{2\pi}(1 + \cos\alpha) = 52.36 + 30 \times 0.7 = 73.36 \text{ V}$$

$$\therefore \alpha = \cos^{-1} \left[\frac{73.36 \times 2\pi}{\sqrt{2} \times 230} - 1 \right] = 65.349^\circ$$

Thus, firing angle delay of converter 1 is 65.336°

(b) Rms value of thyristor current, is

$$\begin{aligned} I_{Tr} &= I_a \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2} = 30 \left(\frac{180 - 65.349^\circ}{360} \right)^{1/2} \\ &= 16.930 \text{ A} = I_{Sr} \end{aligned}$$

Rms value of freewheeling diode current,

$$I_{fd,r} = I_a \left(\frac{\pi + \alpha}{2\pi} \right)^{1/2} = 30 \left(\frac{180 + 65.349^\circ}{360} \right)^{1/2} = 24.766 \text{ A}$$

(c) Input power factor of armature converter = $\frac{V_t \cdot I_a}{V_s \cdot I_{sr}} = \frac{73.36 \times 30}{230 \times 16.931} = 0.5651 \text{ lag.}$

Also, input power factor of armature converter

$$= \frac{1 + \cos \alpha}{\sqrt{\pi(\pi - \alpha)}} = \frac{1 + \cos 65.349^\circ}{\left[\pi(180 - 65.336^\circ) \frac{\pi}{180} \right]^{1/2}} = 0.56518 \text{ lag.}$$

1-φ Fullwave Rectifier Drive

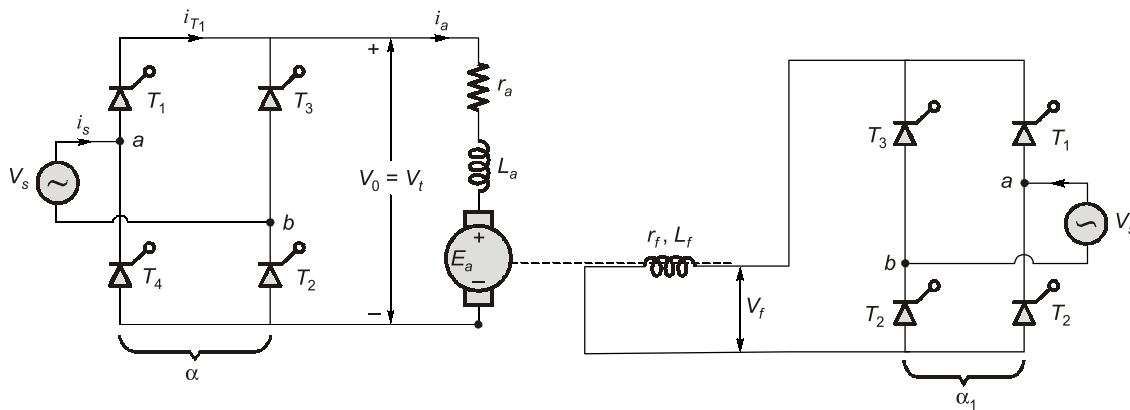


Figure-10.7

- For the armature converter 1,

$$V_0 = V_t = \frac{2V_m}{\pi} \cos \alpha \quad \text{for } 0 < \alpha < \pi.$$

- For the field converter 2, $V_f = \frac{2V_m}{\pi} \cos \alpha_1 \quad \text{for } 0 < \alpha_1 < \pi$

- Rms value of source current, $I_{s,rms} = \sqrt{\left(I_a^2 \cdot \frac{\pi}{\pi} \right)} = I_a$

- Rms value of thyristor current, $I_{T,rms} = \sqrt{\left(I_a^2 \cdot \frac{\pi}{2\pi} \right)} = \frac{I_a}{\sqrt{2}}$

- Input supply p.f. = $\frac{V_t \cdot I_a}{V_s \cdot I_{sr}} = \frac{2V_m}{\pi} \cos \alpha \frac{I_a \sqrt{2}}{V_m \cdot I_a}$

$$\text{Input p.f.} = \frac{2\sqrt{2}}{\pi} \cos \alpha$$


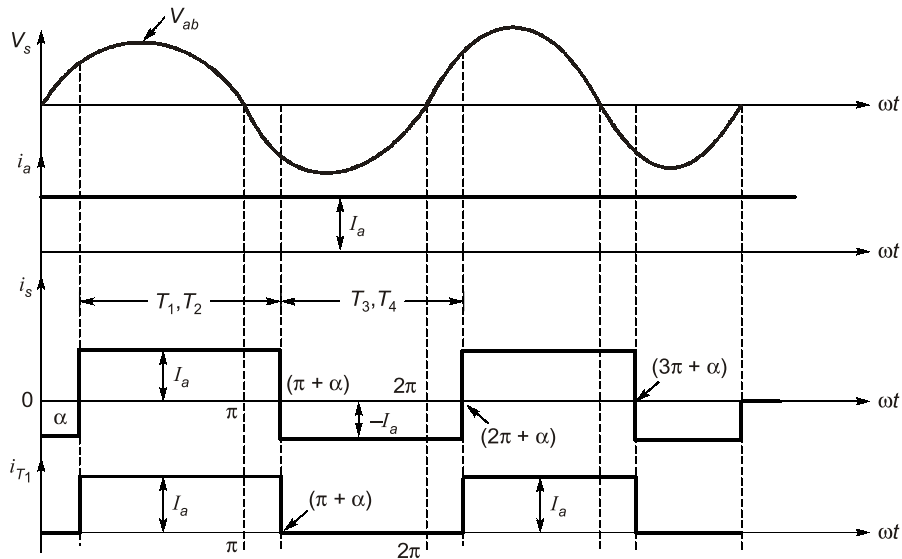


Figure-10.8

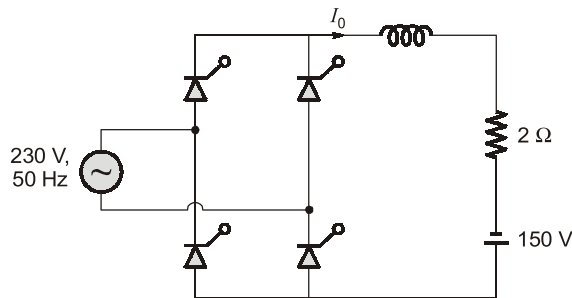Example - 10.4

A single phase fully controlled converter bridge is used for electrical braking of a separately excited dc motor. The dc motor load is represented by an equivalent circuit as shown in the figure.



Assume that the load inductance is sufficient to ensure continuous and ripple free load current.

The firing angle of the bridge for a load current of $I_0 = 10$ A will be

- (a) 44°
- (b) 51°
- (c) 129°
- (d) 136°

Solution : (c)

Average output voltage of the converter,

$$V_0 = \frac{2V_m}{\pi} \cos \alpha$$

Load current = $I_0 = 10$ A

Back emf = $E_b = 150$ V


Armature resistance = $R_a = 2 \Omega$

Applying KVL,

$$V_0 - 2I_0 + 150 = 0$$

$$\Rightarrow V_0 = -150 + 2 \times 10 = -130$$

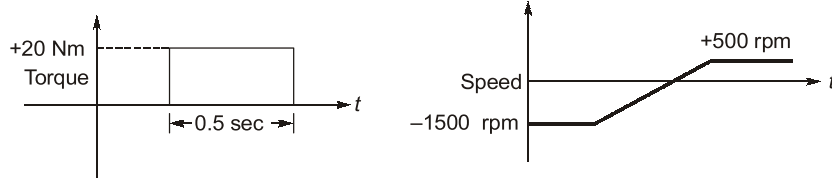Example - 10.11 A variable speed drive rated for 1500 rpm, 40 Nm is reversing under no load. Figure shows the reversing torque and the speed during the transient. The moment of inertia of the drive is



- (a) 0.048 kg m²
(c) 0.096 kg m²

- (b) 0.064 kg m²
(d) 0.128 kg m²

Solution : (a)

Speed changes from -1500 rpm to 500 rpm in 0.5 sec.
So angular acceleration,

$$\alpha = \frac{500 - (-1500)}{0.5} \times \frac{2\pi}{60} \text{ rad/sec}^2 = 418.88 \text{ rad/sec}^2$$

$$\text{Torque} = T = 20 \text{ N-m}$$

$$T = I\alpha$$

$$\text{Moment of inertia, } I = \frac{T}{\alpha} = \frac{20}{418.88} = 0.048 \text{ kgm}^2$$

Example - 10.12 An electric motor, developing a starting torque of 15 Nm, starts with a load torque of 7 Nm on its shaft. If the acceleration at start is 2 rad/sec², the moment of inertia of the systems must be (neglecting viscous and Coulomb friction)

- (a) 0.25 kg m²
(c) 4 kg m²

- (b) 0.25 Nm²
(d) 4 Nm²

Solution : (c)

$$T_S = \text{Starting torque developed by the motor} = 15 \text{ N-m}$$

$$T_L = \text{Load torque} = 7 \text{ N-m}$$

$$T_a = \text{Accelerating torque}$$

$$= T_S - T_L = 15 - 7 = 8 \text{ N-m}$$

$$\alpha = \text{Acceleration} = 2 \text{ rad/sec}^2$$

$$T_a = I\alpha$$

$$I = \text{Moment of inertia} = \frac{T_a}{\alpha} = \frac{8}{2} = 4 \text{ kg m}^2$$

