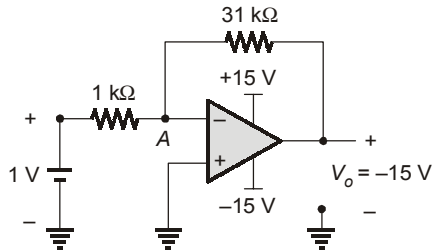


$$\therefore V_o = -\frac{31\text{k}\Omega}{1\text{k}\Omega} \times 1\text{V}$$

$$V_o = -31\text{V} < -15\text{V}$$

which is not possible

Hence, the output voltage of the op-amp is equal to -15V .



Now applying KCL of node 'A', we get,


$$\frac{V_A - (-15)}{31\text{k}\Omega} + \frac{V_A - 1}{1\text{k}\Omega} = 0$$

$$\frac{V_A}{31\text{k}\Omega} + \frac{V_A}{1\text{k}\Omega} = \frac{-15}{31\text{k}\Omega} + \frac{1}{1\text{k}\Omega}$$

$$V_A \left[\frac{1}{31} + \frac{1}{1} \right] = \frac{-15}{31} + 1$$

$$V_A = 0.5\text{V}$$

T4. (b)

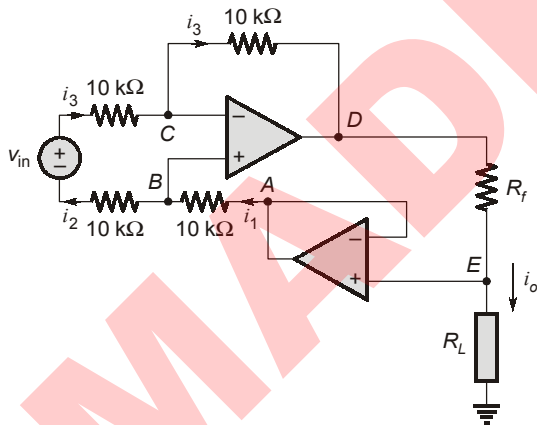

From the circuit,

$$V_E = i_o R_L$$

$$V_E = V_A \text{ (Virtual short concept)}$$

$$i_1 = i_2 = i_3$$

If we apply KVL between node B and C,

$$\therefore V_B = V_C \text{ (Virtual short concept)}$$

$$i_1 = i_2 = i_3 = \frac{V_{in}}{20\text{k}\Omega}$$

$$V_C - V_D = i_3 \times 10\text{k}\Omega = \frac{V_{in}}{2}$$

$$\text{and } V_A - V_B = i_1 \times 10\text{k}\Omega = \frac{V_{in}}{2}$$


$$\therefore V_B = V_C$$

$$\Rightarrow V_D - V_E = -V_{in}$$

$$\therefore i_o = \frac{-V_{in}}{R_f}$$

T5. (b)

From the given figure

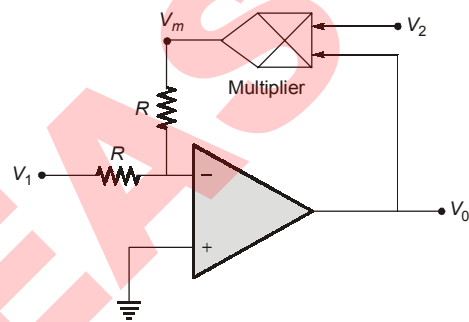


$$V_m = V_2 \times V_o$$

$$\text{and } V_m = -V_1 \left(\frac{R}{R} \right) = -V_1$$

$$\text{Thus, } -V_1 = V_2 \times V_o$$

$$V_o = -\frac{V_1}{V_2} = \frac{-15}{3} = -5\text{ Volts}$$

T6. (15)

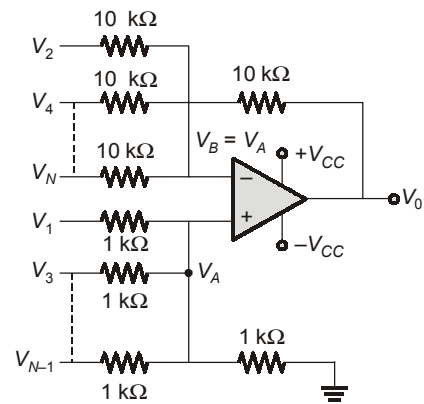

Node A:

$$\frac{V_A - V_1}{1\text{K}} + \frac{V_A - V_3}{1\text{K}} + \dots + \frac{V_A - V_{N-1}}{1\text{K}} + \frac{V_A}{1\text{K}} = 0$$

$$V_A \left(\frac{N}{2} + 1 \right) = V_1 + V_3 + \dots + V_{N-1}$$

$$V_B = V_A \quad \therefore \text{Virtual short}$$

Node B:

$$\frac{V_A - V_2}{10K} + \frac{V_A - V_4}{10K} + \dots + \frac{V_A - V_N}{10K} + \frac{V_A - V_0}{10K} = 0$$

$$V_0 = V_A \left(\frac{N}{2} + 1 \right) - (V_2 + V_4 + V_6 + \dots + V_N)$$

$$= \left(\frac{N}{2} + 1 \right) \cdot \frac{(V_1 + V_3 + \dots + V_{N-1})}{\left(\frac{N}{2} + 1 \right)} - (V_2 + V_4 + \dots + V_N)$$

$$= V_1 - V_2 + V_3 - V_4 + \dots$$

$$= 1 + \frac{1}{2} + \frac{1}{3} + \frac{1}{4} \dots$$

$$= \sum \frac{1}{N} = \infty$$

⇒ Output of op-amp goes to saturation
 $V_0 = V_{\text{sat}} = V_{CC} = 15 \text{ V}$


T7. (0.798)

Initially switch is closed and $V_B = 10 \text{ V}$

$$\Rightarrow V_{01} = -10 \text{ V}$$

$$\Rightarrow V_0 = -V_2 = -5 \text{ V}$$
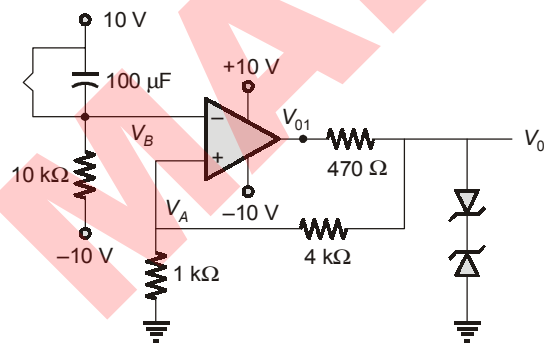
$$\Rightarrow V_A = \frac{V_0}{4k + 1k} \times 1k = -1 \text{ V}$$



At $t = 0$;
 The switch is opened and as $t \rightarrow \infty$, V_B approaches -10 V .
 Let at $t = T_1$,

V_B exceeds V_A (-1 V) so that V_{01} changes from -10 V to 10 V

$$\Rightarrow V_0 \text{ charges from } -5 \text{ V to } 5 \text{ V}$$

$$V_B = V_f + (V_i - V_f)e^{-t/\tau}$$

$$= -10 + [10 - (-10)] e^{-t/RC}$$

At $t = T_1$ $V_B = -1$

$$-1 \text{ V} = -10 + 20 e^{-T_1/RC}$$

$$\Rightarrow T_1 = RC \ln \frac{20}{9}$$


$$= 10 \times 10^3 \times 100 \times 10^{-6} \times 0.798$$

$$= 0.798 \text{ sec}$$

T8. (44.4)

• In the given circuit,

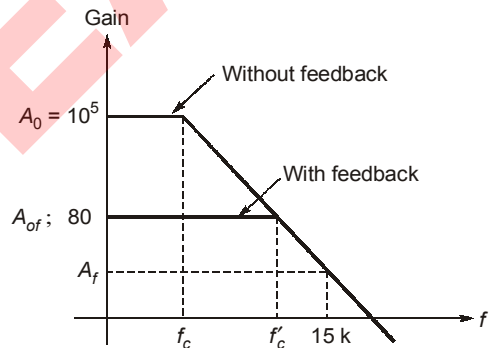Feedback factor, $\beta = \frac{R_1}{R_1 + R_2} = \frac{1}{80}$




- $A_{of} = \frac{A_o}{1 + A_o\beta} \approx 80$
- $f'_c = f_c(1 + A_o\beta) = 8 \left(1 + \frac{10^5}{80} \right) \text{ Hz} = 10,008 \text{ Hz}$
- Gain at $f = 15 \text{ kHz} = 15000 \text{ Hz}$ is,

$$A_f = \frac{A_{of}}{\sqrt{1 + \left(\frac{f}{f'_c} \right)^2}}$$

$$= \frac{80}{\sqrt{1 + \left(\frac{15000}{10008} \right)^2}} \approx 44.4$$

T9. (c)

For $t > 0$,

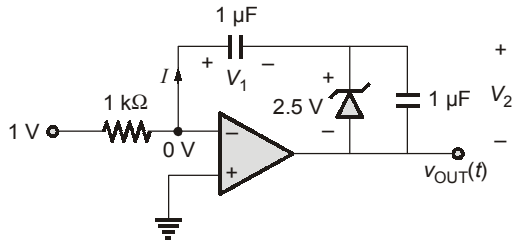

$$I = \frac{1V}{1k\Omega} = 1mA$$

The capacitor charges with constant current I and both V_1 and V_2 will increase till V_2 reaches 2.5 V. Thereafter, $V_2 = 2.5 V$ and V_1 increases with time.

When $v_{out}(t) = -10 V$,
 $V_1 = 7.5 V$

So,

$$\frac{1}{1\mu F} \int_0^t (1mA) dt = 7.5 V$$

$$10^3 t = 7.5$$

$$t = 7.5 \text{ msec}$$

■■■■

12 Negative Feedback Amplifiers & Oscillators

 **Detailed Explanation**
of
Try Yourself Questions

T1. (a)


The overall forward gain is 1000 and close loop gain is 100. Thus, $\beta = 0.009$.
Now, when gain of each stage increase by 10% then overall forward gain will be 1331 and using the previous value of β the close loop will be 102.55.
 \Rightarrow Close loop Voltage gain increase by 2.55%.

T2. (b)


The feedback element is R_f it samples voltage and mix current so shunt-shunt feedback.

T3. (a)

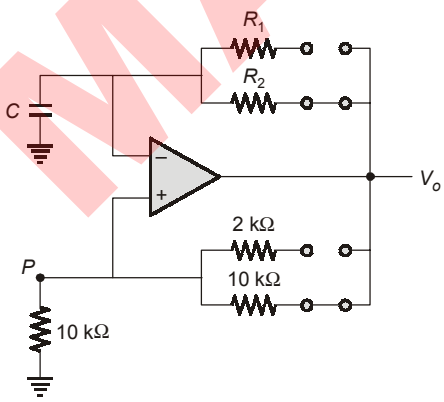The output can be ± 12 V only, when output is 12 V then



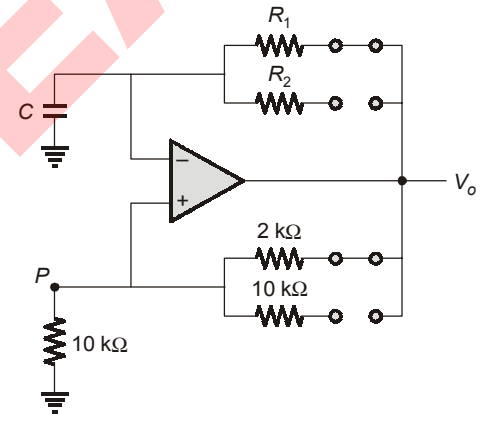So, $V_p = 6$ V
when output is -12 V then



So, $V_p = -10$ V

T4. (d)

Since there are 3 capacitors the maximum phase shift that can be provided will be 270° but due to the presence of the RC circuit the phase shift is equal to 60° for the individual RC circuit, making the phase shift of the feedback network equal to 180° . Thus the amplifier should be an inverting amplifier so that it can be a positive feedback circuit and because the amplifier is a practical amplifier thus $|A\beta| > 1$ for the circuit to work.



14

Bipolar Junction Transistor



Detailed Explanation of Try Yourself Questions

T1. (c)

$$\therefore (\beta + 1) = \frac{I_{CEO}}{I_{CBO}} = \frac{0.6 \times 10^{-3}}{3 \times 10^{-6}} = 200$$

$$\therefore \beta = 199$$

T2. (d)

$$\therefore I_B = 0$$



then only emitter to collector current will flow

$$\therefore I_{CEO} = (\beta + 1)I_{CBO}$$

$$= 101 \times 15 \times 10^{-6}$$

$$= 1515 \mu\text{A} = 1.515 \text{ mA}$$

T3. (c)

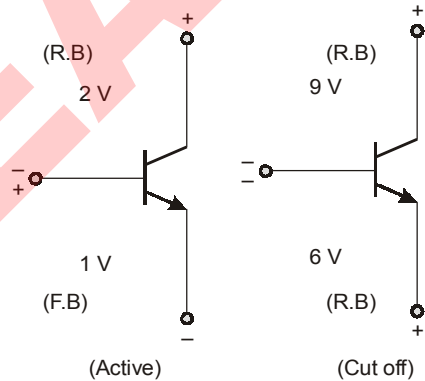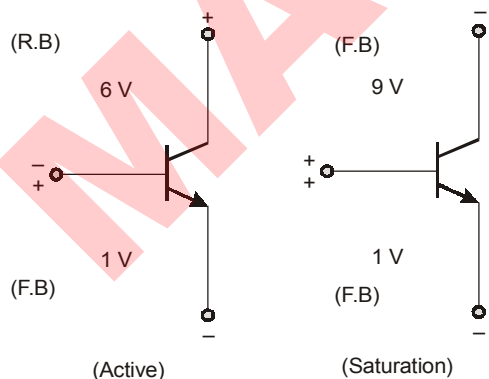

T4. (c)

If base length > length of diffusion then the carriers will not enter the collector.

T5. Sol.

$$I_C = \beta I_C + (\beta + 1)I_{CO}$$

Now,

$$\beta + 1 = \frac{I_{CEO}}{I_{CBO}} = \frac{0.6 \times 10^{-3}}{3 \times 10^{-6}} = 200$$

$$\therefore \beta = 199$$

$$\therefore I_C = 199(10 \mu\text{A}) + (1 + 199) \times 3 \times 10^{-6}$$

$$= 2.59 \times 10^{-3} \text{ Amp}$$

