

GATE

MADE EASY **WORKBOOK** 2024



**Detailed Explanations of
Try Yourself Questions**

Instrumentation Engineering Measurements



MADE EASY
Publications

1

Error Analysis



Detailed Explanation of Try Yourself Questions

T1. Sol.

Probable error,

$$\delta I = \sqrt{\left(\frac{\partial I}{\partial I_1}\right)^2 \delta I_1^2 + \left(\frac{\partial I}{\partial I_2}\right)^2 \delta I_2^2}$$

Here,

$$I = I_1 + I_2$$

So,

$$\frac{\partial I}{\partial I_1} = \frac{\partial I}{\partial I_2} = 1$$

$$\delta I = \sqrt{(1)^2 (1)^2 + (1)^2 (2)^2} = 2.24 \text{ A}$$

therefore,

$$I = 300 \pm 2.24 \text{ A}$$

■■■■

2

Indicating Meters



Detailed Explanation of Try Yourself Questions

T1. (d)

Average value of rectangular current wave = $\sqrt{\frac{1}{2T} [(12^2 \times T) + (5^2 \times T)]} \simeq 9.2$

Average volts = $9.2 \times 10 = 92 \text{ V}$

The MI meter will read 92 V.

■■■■

4

Instrument Transformers



Detailed Explanation of Try Yourself Questions

T1. (c)

Phase angle error for CT is = $\frac{180}{\pi} \left(\frac{I_m \cos \delta - I_e \sin \delta}{K_t I_s} \right)$ degree

Here,

$$K_t = \frac{1000}{5} = 200, I_s = 5 \text{ A}$$

$$I_m = 11 \text{ A}$$

$$I_e = 6.5 \text{ A}$$

$$\delta = 30^\circ$$

$$\text{So, phase angle error} = \frac{180}{\pi} \left(\frac{11 \cos 30^\circ - 6.5 \sin 30^\circ}{200 \times 5} \right) = 0.359^\circ$$

T2. (b)

Secondary circuit phase angle, $\delta = \tan^{-1} \left(\frac{1}{1.5} \right) = 33.69^\circ$

or,

$$\cos \delta = \cos 33.69^\circ = 0.835$$

$$\sin \delta = \sin 33.69^\circ = 0.555$$

Turn ratio,

$$K_t = \frac{N_s}{N_p} = \frac{300}{1} = 300$$

Magnetizing current,

$$I_m = \frac{\text{Magnetising mmf}}{N_p} = \frac{100}{1} = 90 \text{ A}$$

$$\text{Secondary circuit burden impedance} = \sqrt{(1.5)^2 + (1.0)^2} = 1.8 \Omega$$

$$\text{Secondary induced voltage, } E_s = 5 \times 1.8 = 9 \text{ V}$$

Primary induced voltage, $E_p = \frac{E_s}{300} = \frac{9 \text{ V}}{300}$

Loss component, $I_w = \frac{\text{iron loss}}{E_p} = \frac{1.2}{(9 / 300)} = 40 \text{ A}$

Phase angle,
$$\theta = \frac{180}{\pi} \left(\frac{I_m \cos \delta - I_w \sin \delta}{K_t I_s} \right)$$
$$= \frac{180}{\pi} \left(\frac{100 \times 0.835 - 40 \times 0.555}{300 \times 5} \right) = 2.34^\circ$$

■■■■

5

Measurement of R, L and C/Bridges



Detailed Explanation of Try Yourself Questions

T1. Sol.

$$\begin{aligned} R_3 &= 5 \, \Omega, \\ C &= 1 \, \text{mF}, \\ R_1 &= 160 \, \Omega, \\ R_2 &= 20 \, \Omega \end{aligned}$$

By using balance equation,

$$R = \frac{R_2 R_1}{R_3}$$

$$L = R_2 R_1 C$$

and

$$\text{quality factor} = Q = \frac{\omega L}{R}$$

So,

$$R = \frac{20 \times 160}{5} = 640 \, \Omega$$

$$L = 20 \times 160 \times 1 \times 10^{-3} = 3.2 \, \text{H}$$

$$Q = \frac{2\pi \times 50 \times 3.2}{640} = 1.57$$

T2. (b)

At balance,

$$Z_1 Z_4 = Z_2 Z_3$$

$$\frac{10 \times 10^3 \times X_C}{10 \times 10^3 + X_C} \times Z = 500 \times 10^3$$

as,

$$X_C = \frac{1}{j\omega C} = \frac{1}{j \times 100\pi \times 100 \times 10^{-9}} = -j \frac{10^5}{\pi}$$

$$\therefore \frac{-j10^4 \times 10^5}{\pi \left(10^4 - \frac{j \times 10^5}{\pi} \right)} \times 2 = 5 \times 10^5$$

$$\Rightarrow \frac{-j10^3}{1000\pi - j10^4} (R + jX) = 5$$

$$\Rightarrow -jR + X = 5\pi - j5 \times 10$$

$$\Rightarrow R = 50 \, \Omega$$

$$\text{and } L = \frac{5}{2 \times 50} = 50 \, \text{mH}$$

■■■■



Detailed Explanation of Try Yourself Questions

T1. Sol.

Using the equation,

$$V_{p-p} = \left(\frac{\text{volts}}{\text{div}} \right) \times \left(\frac{\text{no. of div}}{1} \right)$$

$$V_{p-p} = 0.5 \text{ V} \times 3 = 1.5 \text{ V}$$

T2. Sol.

The period of the signal is calculate using the equation

$$T = \left(\frac{\text{time}}{\text{div}} \right) \times \left(\frac{\text{no. of div}}{\text{cycle}} \right)$$

$$T = 2 \mu\text{s} \times 4 = 8 \mu\text{s}$$

Hence, frequency is

$$f = \frac{1}{T} = \frac{1}{8 \mu\text{s}} = 125 \text{ kHz}$$

■■■■