

Write all steps in detail.



**MADE EASY**

India's Best Institute for IES, GATE & PSUs

## ESE 2023 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

### Electrical Engineering

#### Test-1 : Electrical Circuits + Control Systems [All Topics]

Name : .....

Roll No :

#### Test Centres

Delhi ☒ Bhopal ☐ Jaipur ☐ Pune ☐  
Kolkata ☐ Bhubaneswar ☐ Hyderabad ☐

#### Student's Signature

#### Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. Answer must be written in English only.
3. Use only black/blue pen.
4. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
5. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
6. Last two pages of this booklet are provided for rough work. Strike off these two pages after completion of the examination.

#### FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	46
Q.2	30
Q.3	54
Q.4	
Section-B	
Q.5	55
Q.6	
Q.7	20
Q.8	
<b>Total Marks Obtained</b>	<b>205</b>

Signature of Evaluator

Cross Checked by

Sourabh Kumar .....

Corp. office : 44 - A/1, Kalu Sarai, New Delhi-16

Ph: 9021300500 | Web: www.madeeasy.in

Try to avoid calculation mistake

Improve presentation

## **IMPORTANT INSTRUCTIONS**

**CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.**

### **DONT'S**


1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

### **DO'S**


1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

## Section A : Electrical Circuits

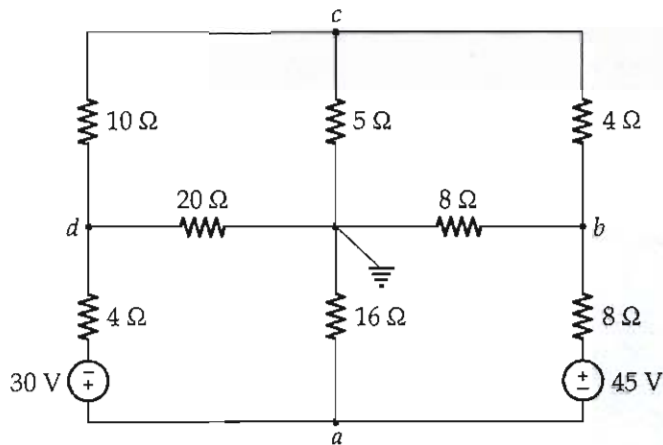Q.1 (a) Find the voltages at nodes  $a$ ,  $b$ ,  $c$  and  $d$  in the circuit shown.



[12 marks]

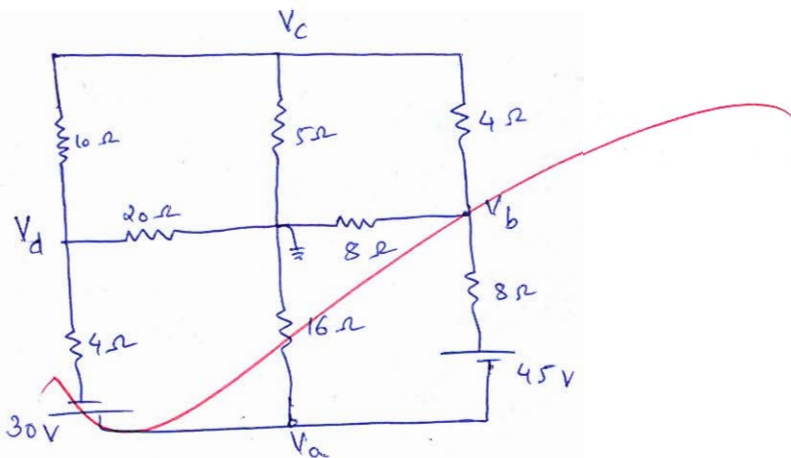

Applying Nodal analysis in the above circuit, we get

$$\text{at node A} \quad \frac{V_a - 30 - V_d}{4} + \frac{V_a}{16} + \frac{V_a + 45 - V_b}{8} = 0$$

$$\text{or} \quad \frac{7}{16} V_a - \frac{1}{8} V_b + 0 V_c - \frac{1}{4} V_d = \frac{15}{8} \quad \text{--- (i)}$$

$$\text{at node B} \quad \frac{V_b - 45}{8} + \frac{V_b}{8} + \frac{V_b - V_c}{4} = 0$$

$$\text{or} \quad 0 V_a + \frac{1}{2} V_b - \frac{1}{4} V_c + 0 V_d = \frac{45}{8} \quad \text{--- (ii)}$$

$$\text{at node C} \quad \frac{V_c - V_b}{4} + \frac{V_c}{5} + \frac{V_c - V_d}{10} = 0$$

$$\text{or} \quad 0 V_a - \frac{1}{4} V_b + \frac{11}{20} V_c - \frac{1}{10} V_d = 0 \quad \text{--- (iii)}$$

at node D  $\frac{V_d - V_c}{10} + \frac{V_d}{20} + \frac{V_d + 30 - V_a}{4} = 0$

$$\cancel{0V_a} + \cancel{0V_b} - \frac{1}{4} V_a + 0V_b - \frac{V_c}{10} + \frac{2}{5} V_d = -\frac{15}{2} \quad \text{--- (iv)}$$

from eq<sup>n</sup> (iii), we have

$$V_c = \frac{20}{11} \left[ \frac{V_b}{4} + \frac{V_d}{10} \right]$$

substituting in eq (i) (ii) & (iv) we get

$$\frac{7}{16} V_a - \frac{1}{8} V_b - \frac{1}{4} V_d = \frac{15}{8}$$

$$\frac{V_b}{2} - \frac{5}{11} \left[ \frac{V_b}{4} + \frac{V_d}{10} \right] = \frac{45}{8} \Rightarrow 0V_a + \frac{17}{44} V_b - \frac{1}{22} V_d = \frac{45}{8}$$

$$-\frac{1}{4} V_a - \frac{2}{11} \left[ \frac{V_b}{4} + \frac{V_d}{10} \right] + \frac{2}{5} V_d = -\frac{15}{2} \Rightarrow -\frac{1}{4} V_a - \frac{2}{44} V_b + \frac{21}{55} V_d = -\frac{15}{2}$$

or

$$\begin{bmatrix} \frac{7}{16} & -\frac{1}{8} & -\frac{1}{4} \\ 0 & \frac{17}{44} & -\frac{1}{22} \\ -\frac{1}{4} & -\frac{2}{44} & \frac{21}{55} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_d \end{bmatrix} = \begin{bmatrix} \frac{15}{8} \\ \frac{45}{8} \\ -\frac{15}{2} \end{bmatrix}$$

2

Calculation  
mistake

$$V_a = -4.25 \text{ V}$$


$$V_b = 12.09 \text{ V}$$

$$V_d = -20.99 \text{ V}$$

$$\Rightarrow V_c = \frac{20}{11} \left[ \frac{V_b}{4} + \frac{V_d}{10} \right] = 1.68 \text{ V}$$




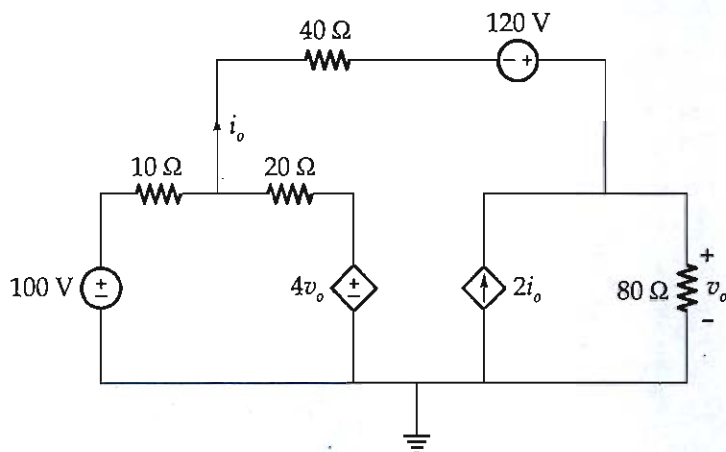Q.1 (b) Using nodal analysis, find  $v_o$  and  $i_o$  in the circuit shown in figure.



The circuit can be redrawn as

[12 marks]

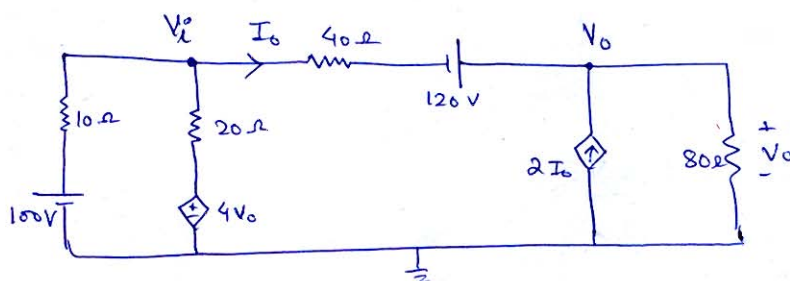

using nodal analysis

at node  $V_i$ , 
$$\frac{V_i - 100}{10} + \frac{V_i - 4v_o}{20} + \frac{V_i + 120 - V_o}{40} = 0$$

$$\frac{7}{40} V_i - \frac{9}{40} V_o = 7 \quad \text{--- (i)}$$

at node  $V_o$ , 
$$\frac{V_o - 120 - V_i}{40} + \frac{V_o}{80} = 2I_o$$

$$-\frac{1}{40} V_i + \frac{3}{80} V_o = 2I_o + 3 \quad \text{--- (ii)}$$

also

$$I_o = \frac{V_i + 120 - V_o}{40} \quad \text{--- (iii)}$$

$\therefore$  eq (ii) becomes

$$-\frac{1}{40} V_i + \frac{3}{80} V_o = \frac{2}{40} (V_i + 120 - V_o) + 3$$

$$-\frac{1}{40} V_i + \frac{3}{80} V_o = \frac{1}{20} V_i + 6 - \frac{1}{20} V_o + 3$$

$$-\frac{3}{40} V_i + \frac{7}{80} V_o = 9 \quad \text{--- (iv)}$$

Solving eq (i) & (iv)

$$\begin{bmatrix} \frac{7}{40} & -\frac{9}{40} \\ -\frac{3}{40} & \frac{7}{80} \end{bmatrix} \begin{bmatrix} V_i \\ V_o \end{bmatrix} = \begin{bmatrix} 7 \\ 9 \end{bmatrix}$$

$$\Rightarrow V_i = -1688 \text{ V}$$

$$V_o = -1344 \text{ V}$$

Improve  
presentation

$$\therefore I_o = \frac{V_i + 120 - V_o}{40}$$


$$= -5.6$$

$$\therefore V_o = -1344 \text{ V}$$

$$I_o = -5.6 \text{ A}$$


Good  
Approach

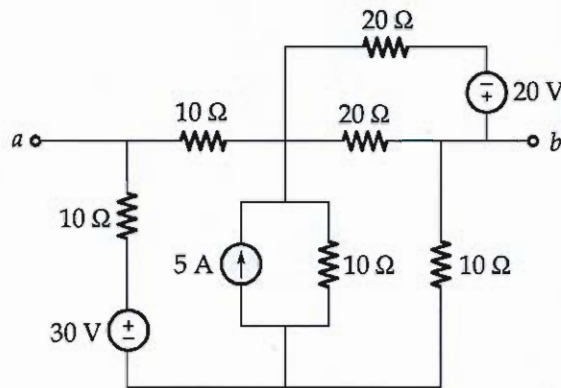- Q.1 (c) For the circuit shown, find the Thevenin's equivalent network between terminals  $a$  and  $b$ .




[12 marks]

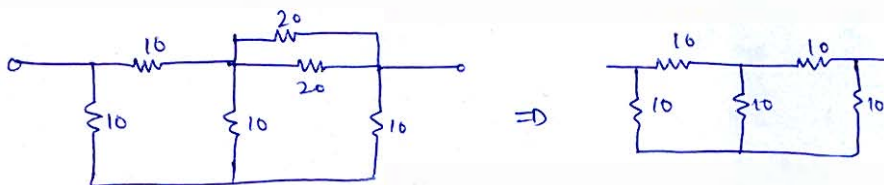To obtain  $Z_{th}$ , sources are deactivated




converting the  $10\Omega$  Y into delta

$$R_{\Delta} = 3 R_Y = 30\Omega$$

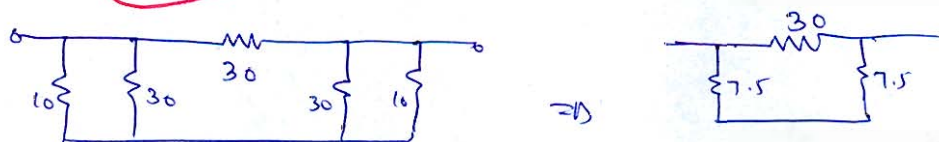

$$\Rightarrow R_{eq} = (7.5 + 7.5) \parallel 30 = 10\Omega$$

To obtain  $V_{oc}$

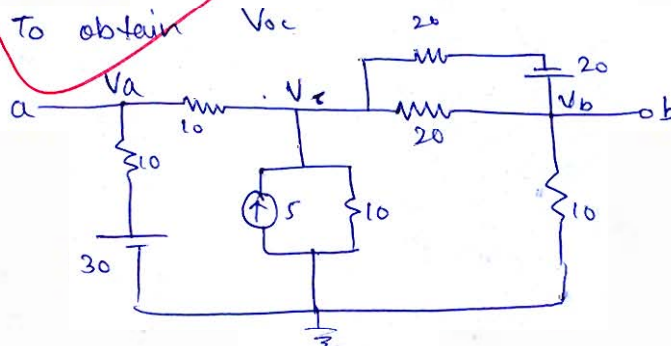

node a  $\frac{V_a - 30}{10} + \frac{V_a - V_c}{20} = 0$

$$2V_a - V_c = 30 \quad \text{--- (i)}$$

node c  $\frac{V_c - V_a}{10} + \frac{V_c - V_b}{20} + \frac{V_c + 20 - V_b}{20} + \frac{V_c}{10} = 5$

$$-\frac{V_a}{10} - \frac{V_b}{10} + \frac{3V_c}{10} = 4 \quad \text{--- (ii)}$$

node b

$$\frac{V_b}{10} + \frac{V_b - V_c}{20} + \frac{V_b - 20 - V_c}{20} = 0$$

$$\frac{V_b}{5} - \frac{V_c}{10} = 1 \quad \text{--- (iii)}$$

Solving (i), (ii), (iii), we get


$$V_a = 30V$$

$$V_b = 20V$$

$$V_c = 30V$$

$$V_{th} = V_a - V_b = 10V$$

∴ Thevenin equivalent is

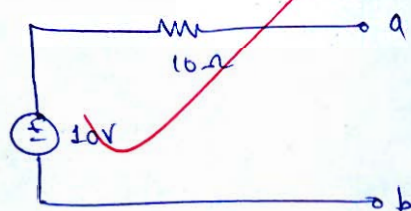


Good  
Approach



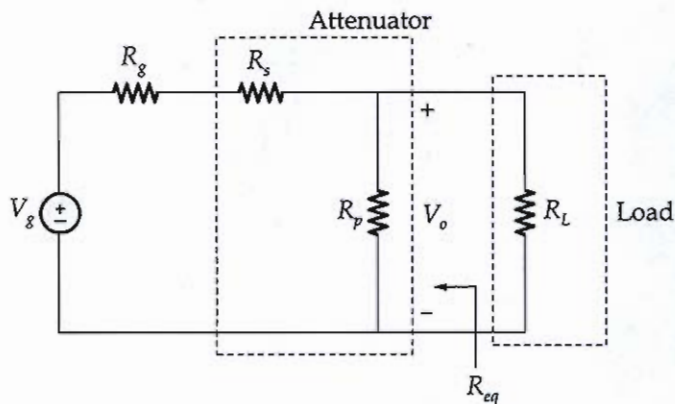- Q.1 (d) An attenuator is an interface circuit that reduces the voltage level without changing the output resistance. By specifying  $R_s$  and  $R_p$  of the interface circuit shown in figure, design an attenuator that will meet the following requirements :


$$\frac{V_o}{V_g} = 0.125, R_{eq} = R_{th} = R_g = 100 \Omega$$

Using the interface designed, also calculate the current through a load of  $R_L = 50 \Omega$  when  $V_g = 12 \text{ V}$ .



[12 marks]

For the attenuator circuit

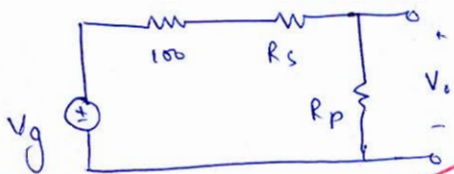

Write all  
steps in detail

$$V_o = V_g \times \frac{R_p}{R_s + R_p + 100} \Rightarrow \frac{V_o}{V_g} = \frac{R_p}{R_s + R_p + 100} = 0.125$$

$$\therefore 8R_p = R_s + R_p + 100 \quad \text{or} \quad \boxed{7R_p = R_s + 100} \quad \text{--- (1)}$$

now for  $R_{eq}$ ,  $V_g = 0$

$$\therefore R_{eq} = (R_g + R_s) \parallel R_p = 100$$

$$\Rightarrow \frac{(100 + R_s) R_p}{100 + R_s + R_p} = 100$$

$$\Rightarrow \frac{7R_p \cdot R_p}{8R_p} = 100$$

$$R_p = \frac{800}{7} \Omega$$


$$R_s = 700 \Omega$$

given  $V_g = 12 \text{ V}$



$Z_{th}$  to left of load  $= 100 \Omega$
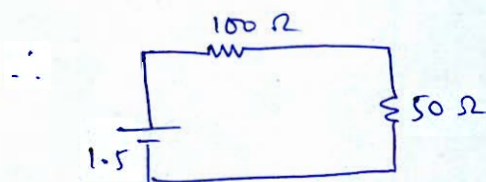
$$V_{th} = 0.125 \times V_g = 1.5 \text{ V}$$




Thevenin equivalent

$$\begin{aligned} \therefore I_L &= \frac{1.5}{100 + 50} \\ &= 0.01 \text{ A} \\ &= 10 \text{ mA} \end{aligned}$$



Good  
Approach

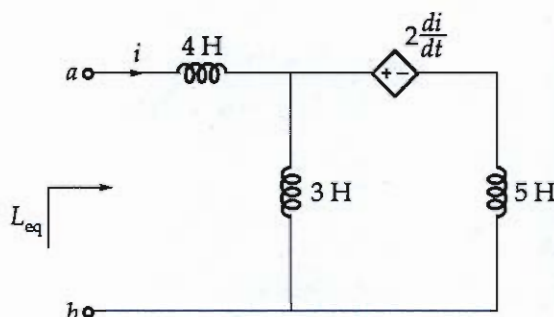- Q.1 (e) Determine the equivalent inductance,  $L_{eq}$  that can be used to represent the inductive network shown in figure.




[12 marks]

To compute  $L_{eq}$ , let us consider the circuit shown below

then  $V = L_{eq} \frac{di}{dt}$

we conclude  $i = I_1$

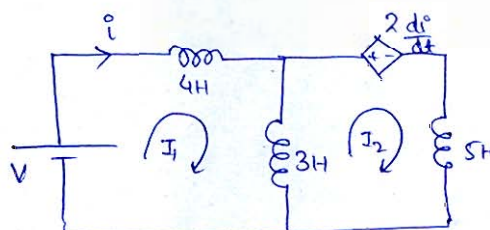

using mesh analysis

loop 1  $-V + 4 \frac{dI_1}{dt} + 3 \frac{d(I_1 - I_2)}{dt} = 0$

$$7 \frac{dI_1}{dt} - 3 \frac{dI_2}{dt} = V \quad \text{--- (1)}$$

Write all  
steps in  
detail

loop 2

$$2 \frac{dI_1}{dt} + 5 \frac{dI_2}{dt} + 3 \frac{d(I_2 - I_1)}{dt} = 0$$

$$- \frac{dI_1}{dt} + 8 \frac{dI_2}{dt} = 0$$

$$\text{or } \frac{1}{8} \frac{dI_1}{dt} = \frac{dI_2}{dt}$$

Substituting this in eq (1)

$$7 \frac{dI_1}{dt} - \frac{3}{8} \frac{dI_1}{dt} = V$$

$$\text{or } V = \frac{53}{8} \frac{dI_1}{dt}$$

$$\therefore V = \frac{53}{8} \frac{d\theta}{dt}$$

$$\text{Hence } L_{eq} = \frac{53}{8} H$$


$$\text{or } 6.625 H$$

11

Good  
Approach




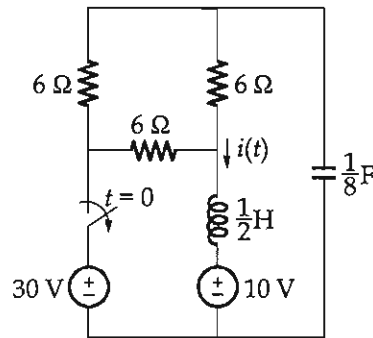Q.2 (a) For the network shown in figure, find the current  $i(t)$  for  $t > 0$ .




[20 marks]

At  $t = 0^-$

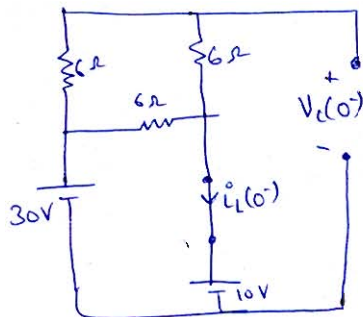

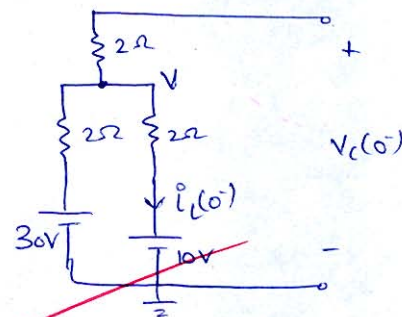converting delta  $6\Omega$  to star  $2\Omega$



Write  
all steps  
in detail

using nodal analysis


$$\frac{V-30}{2} + \frac{V-10}{2} = 0 \Rightarrow V = \frac{40}{2} = 20V$$

$$\therefore i_L(0^-) = \frac{20-10}{2} = 5A \quad \& \quad V_C(0^-) = V = 20V$$


$$= 5A$$

$$\Rightarrow i_L(0^+) = i_L(0^-) = 5A, \quad V_C(0^+) = V_C(0^-) = 20V$$

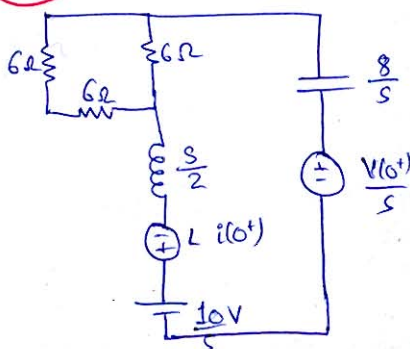Now for  $t > 0$ , circuit becomes (in Laplace domain)



on simplification

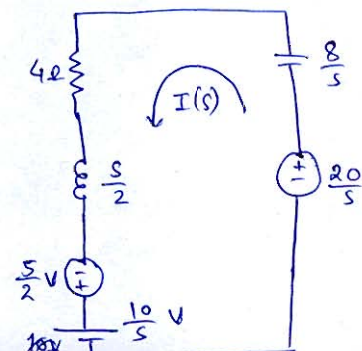

$$\therefore I(s) = \frac{\frac{20}{s} + 2.5 - \frac{10}{s}}{\frac{8}{s} + \frac{s}{2} + 4} = \frac{\frac{10}{s} + 2.5}{4 + \frac{8}{s} + \frac{s}{2}}$$

$$= \frac{10 + 2.5s}{4s + 8 + \frac{s^2}{2}} = \frac{20 + 5s}{s^2 + 8s + 16}$$


$$= \frac{5(s+4)}{(s+4)^2} = \frac{5}{s+4}$$

$$i(t) = L^{-1}\{I(s)\} = 5e^{-4t}, \quad t > 0$$


Good  
Approach

11

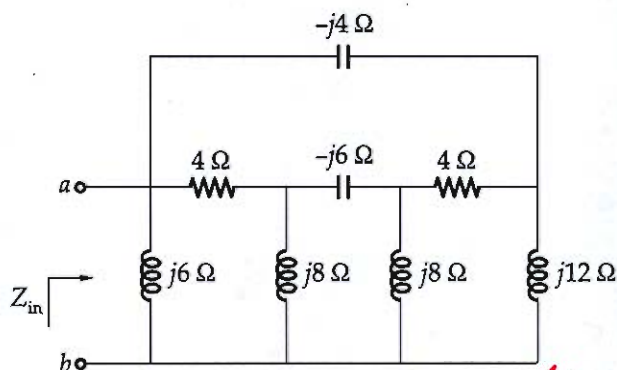Q.2(b) Determine the equivalent impedance of the circuit shown



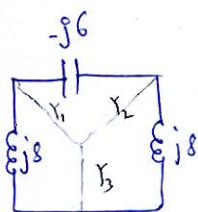*you can use figure given in question.* [20 marks]




converting this  $\Delta$ -network into  $Y$ , we get


$$Y_1 = \frac{j8 \times (-j6)}{j8 + j8 - j6} = -4.8j \, \Omega$$

$$Y_2 = Y_1 = -4.8j \, \Omega$$
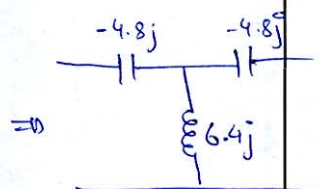
$$Y_3 = \frac{j8 \times j8}{j8 + j8 - j6} = 6.4j \, \Omega$$




Now consider 4 ohm resistances as well

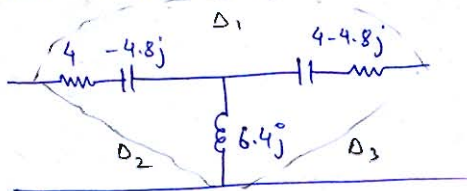

converting  $Y$  to  $\Delta$

$$\Delta_1 = 39.04 \angle -100.39^\circ \, \Omega$$

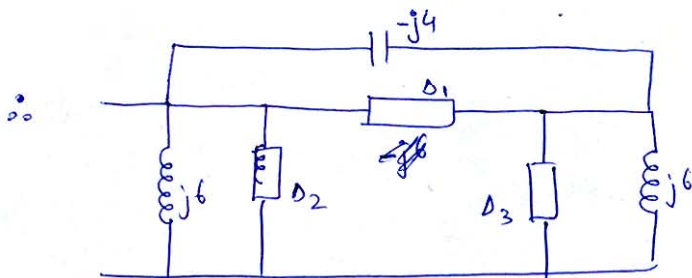
$$\Delta_2 = \Delta_3 = 39.99 \angle 39.81^\circ \, \Omega$$




$$\Delta_2 \parallel j6 = \Delta_3 \parallel j6 = 5.44 \angle 84^\circ \, \Omega$$
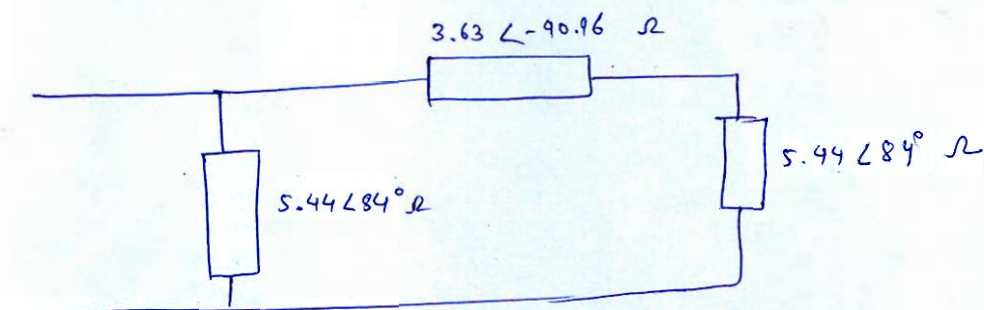
$$\Delta_1 \parallel (-j4) = 3.63 \angle -90.96^\circ \, \Omega$$




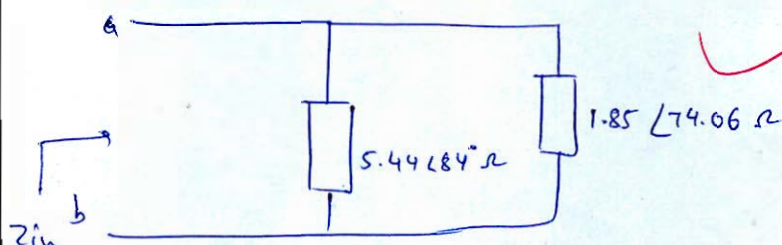
$$3.63 \angle -90.96 + 5.44 \angle 84^\circ = 1.85 \angle 74.06^\circ \Omega$$



$$\therefore Z_{in} = 5.44 \angle 84^\circ \parallel 1.85 \angle 74.06^\circ$$

$$Z_{in} = 1.38 \angle 76.58^\circ \Omega$$

$$\therefore Z_{in} = 1.38 \angle 76.58^\circ \Omega$$

$$\text{or } = (0.32 + j1.35) \Omega$$

$$Z_{in} = (0.66 + j1.48) \Omega$$


Calculation  
mistake

5





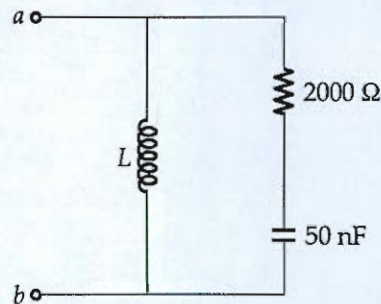
- Q.2 (c) (i) An industrial load is modelled as a series combination of a capacitance and a resistance as shown in figure. Calculate the value of an inductance  $L$  across the series combination so that net impedance is resistive at a frequency of 50 kHz.



- (ii) An industrial coil is modelled as a series combination of an inductance  $L$  and resistance  $R$ , as shown in figure. Since an AC voltmeter measures only the magnitude of a sinusoid, the following measurements are taken at 60 Hz. When the circuit operates in steady state :

$$|V_s| = 145 \text{ V}, |V_1| = 50 \text{ V}, |V_o| = 110 \text{ V}$$

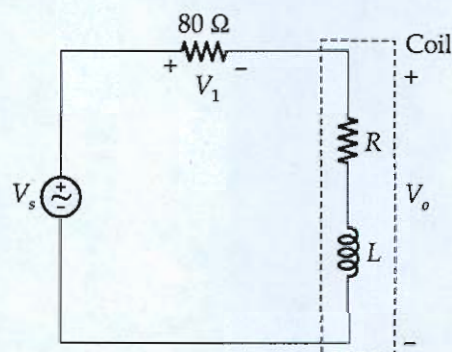Use these measurements to determine the values of  $L$  and  $R$ .




[10 + 10 marks]

①

For net impedance to be resistive at 50 kHz

⇒ circuit must be at resonance at 50 kHz

redrawing we get

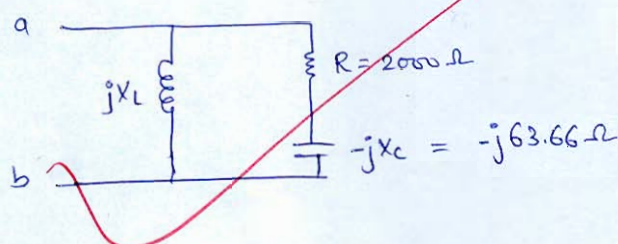

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC} = 63.66 \Omega$$

$$Y_{ab} = \frac{1}{jX_L} + \frac{1}{2000 - j63.66}$$

$$= \frac{-j}{X_L} + \frac{2000 + j63.66}{4004052.596}$$

$$\text{Im}(Y_{ab}) = \frac{-1}{X_L} + \frac{63.66}{4004052.596} = 0 \quad (\text{for resonance})$$

$$\therefore \frac{1}{X_L} = 1.5899 \times 10^{-5}$$

$$X_L = 62897.46$$

$$2\pi fL = 62897.46$$

$$\therefore L = 0.2 \text{ H}$$

9

Good  
Approach

ii

Let  $V_s = 145 \angle 0^\circ$  be the reference for phasors


$$\tilde{V}_s = \tilde{V}_r + \tilde{V}_o \quad \& \quad \tilde{I}_s = \tilde{I}_{\text{ser}} = \tilde{I}$$

as the coil is in

Try to avoid

Since the elements are connected in series, the current flowing through each element will be same.

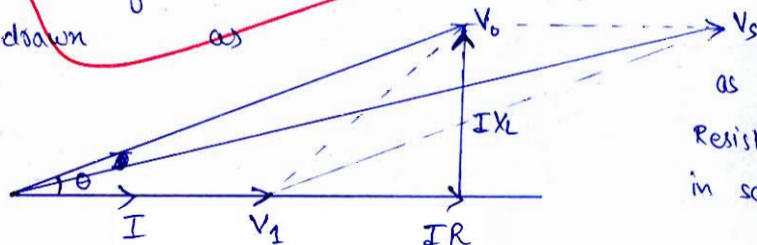Taking current  $\tilde{I}$  as reference, the phasors can be drawn as



as  $V_r$  is drop across Resistance,  $\therefore$  it will be in same phase with  $I$

and coil is inductive

$\therefore I$  lags  $V_o$  by  $\theta$

$$\text{where } \theta = \tan^{-1} \frac{X_L}{R}$$



as per vector addition

$$V_s^2 = V_1^2 + V_2^2 + 2V_1V_2 \cos \theta$$

$$145^2 = 50^2 + 110^2 + 2 \times 50 \times 110 \times \cos \theta$$

$$\therefore \cos \theta = 0.584$$

$$\therefore \theta = 54.26^\circ$$


also  $|I| = \frac{|V_1|}{80 \Omega}$

$$\therefore |I| = \frac{50}{80} = 0.625 \text{ A}$$

and  $|V_s| = |I| |Z|$

$$145 = 0.625 |80 + R + jX_L|$$

$$(80 + R)^2 + (X_L)^2 = 60712.96$$

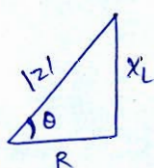

from impedance triangle

$$R = Z \cos \theta, \quad X_L = Z \sin \theta$$

$$= 0.584Z, \quad = 0.812Z$$

$$\therefore (80 + 0.584Z)^2 + (0.812Z)^2 = 60712.96$$

$$\Rightarrow Z = 190.99 \Omega$$

$$\therefore \boxed{R = 111.51 \Omega}$$

$$X_L = 155.04 \Omega$$


$$\therefore \boxed{L = \frac{X_L}{2\pi \times 60} = 0.41 \text{ H}}$$

5

Correct value  
 $R = 102.8 \Omega$   
 $L = 0.3789 \text{ H}$



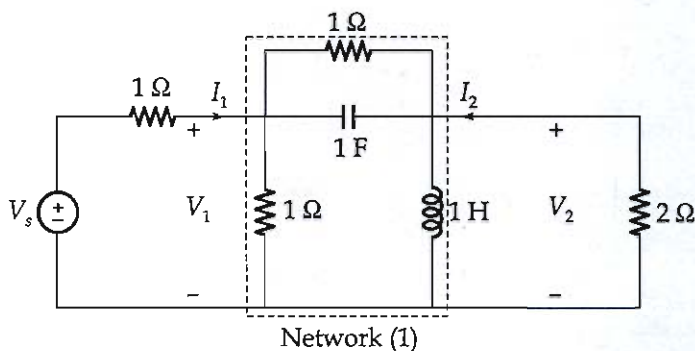- Q.3 (a) Determine the  $y$ -parameters of two port network (1). Also determine  $V_2(s)$  for  $V_s = 2u(t)$  V.




[10 + 10 marks]

we know 
$$\begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned}$$

write all steps  
in detail

N/w ① is drawn as

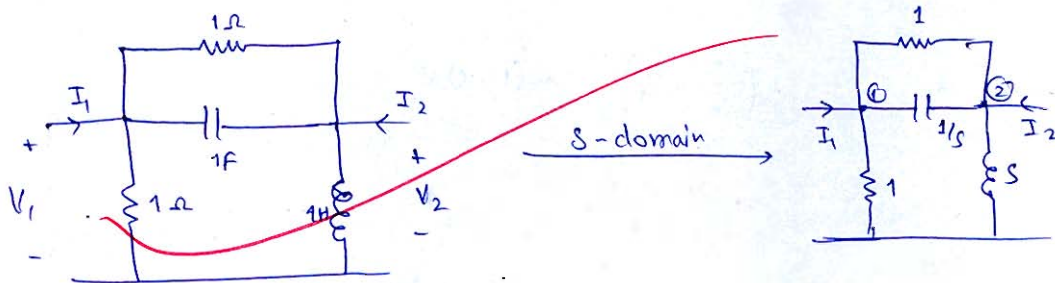

Applying nodal technique

at node ① 
$$I_1 = \frac{V_1}{1} + \frac{V_1 - V_2}{1/s} + \frac{V_1 - V_2}{1}$$

$$I_1 = (2 + s) V_1 + (-1 - s) V_2 \quad \text{--- ①}$$


at node ②

$$I_2 = \frac{V_2}{s} + \frac{V_2 - V_1}{1/s} + \frac{V_2 - V_1}{1}$$

$$I_2 = (-1 - s) V_1 + \left(1 + s + \frac{1}{s}\right) V_2 \quad \text{--- ②}$$

$$\therefore Y = \begin{bmatrix} 2 + s & -(1 + s) \\ -(1 + s) & \left(1 + s + \frac{1}{s}\right) \end{bmatrix}$$

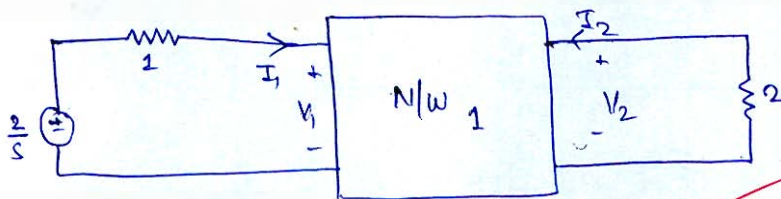Now  $V_s = 2u(t) \Rightarrow V_s(s) = \frac{2}{s}$



From the above circuit

$$\frac{2}{s} - I_1(1) = V_1 \Rightarrow V_1 = \frac{2}{s} - I_1$$

$$\& V_2 = -2I_2$$

Substituting these values in eq<sup>n</sup> (i) & (ii)

$$I_1 = (2+s) \left( \frac{2}{s} - I_1 \right) - (1+s)V_2 \quad \text{--- (iii)}$$

$$-\frac{V_2}{2} = (-1-s) \left( \frac{2}{s} - I_1 \right) + \left( 1+s + \frac{1}{s} \right) V_2 \quad \text{--- (iv)}$$

$$\text{or } I_1 = (2+s) \frac{2}{s} - I_1(2+s) - (1+s)V_2 \quad \left\{ \text{from (iii)} \right\}$$

$$\Rightarrow I_1(3+s) = \frac{4}{s} + 2 - (1+s)V_2$$

$$\Rightarrow I_1 = \frac{\frac{4}{s} + 2 - (1+s)V_2}{3+s}$$

Substituting in eq (iv)

$$V_2 \left( 1+s + \frac{1}{s} + \frac{1}{2} \right) = (1+s) \left[ \frac{2}{s} - \left[ \frac{\frac{4}{s} + 2 - (1+s)V_2}{3+s} \right] \right]$$

$$V_2 \left( \frac{3}{2} + s + \frac{1}{s} \right) = (1+s) \left[ \frac{6+2s-4-2s+s(1+s)V_2}{s(s+3)} \right]$$

$$V_2 \left( \frac{3}{2} + s + \frac{1}{s} \right) = (1+s) \left[ \frac{2 + s(1+s)V_2}{s(s+3)} \right]$$

$$V_2 \left[ \frac{3}{2} + s + \frac{1}{s} \right] = \frac{2(s+1)}{s(s+3)} + \frac{s(s+1)^2}{s(s+3)} V_2$$

$$V_2 \left[ \frac{3}{2} + s + \frac{1}{s} - \frac{(s+1)^2}{(s+3)} \right] = \frac{2(s+1)}{s(s+3)}$$

$$V_2 \left[ \frac{3s + 2s^2 + 2}{2s} - \frac{(s^2 + 2s + 1)}{s+3} \right] = \frac{2(s+1)}{s(s+3)}$$

$$V_2 \left[ \frac{(2s^2 + 3s + 2)(s+3) - (s^2 + 2s + 1)(2s)}{2s(s+3)} \right] = \frac{2(s+1)}{s(s+3)}$$

$$V_2 \left[ \frac{2s^3 + 6s^2 + 3s^2 + 9s + 2s + 6}{- (2s^3 + 4s^2 + 2s)} \right] = \frac{2(s+1)}{s(s+3)} \cdot 2s(s+3)$$

$$V_2 [5s^2 + 9s + 6] = 4(s+1)$$

$$V_2(s) = \frac{4(s+1)}{5s^2 + 9s + 6}$$


$$\therefore V_2(s) = \frac{4(s+1)}{5s^2 + 9s + 6}$$

18


Good  
Approach



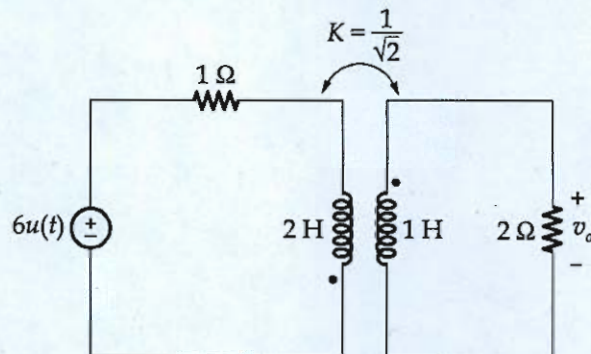Q.3 (b) For the circuit shown in figure, find  $V_o(t)$  for  $t > 0$ .



[20 marks]

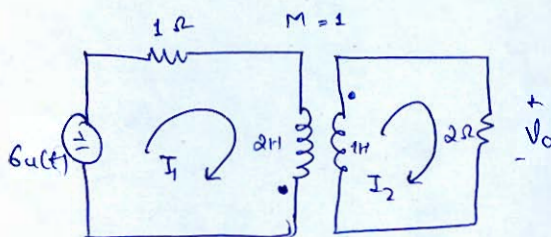

given  $K = \frac{1}{\sqrt{2}}$

$$\therefore \frac{M}{\sqrt{L_1 L_2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow M = 1$$

using mesh technique

$$6u(t) = I_1(1) + 2 \frac{dI_1}{dt} + 1 \frac{dI_2}{dt} \quad \text{--- (i) } \left[ \begin{array}{l} \text{both currents are} \\ \text{leaving the dot} \end{array} \right]$$

$$1 \frac{dI_2}{dt} + 1 \frac{dI_1}{dt} + 2I_2 = 0 \quad \text{--- (ii)}$$

Taking Laplace on both sides on eq (i) & eq (ii)

$$\frac{6}{s} = I_1(s) + 2sI_1(s) + sI_2(s)$$

$$\text{or } (1+2s)I_1(s) + sI_2(s) = \frac{6}{s} \quad \text{--- (iii)}$$

$$\& \quad sI_2(s) + sI_1(s) + 2I_2(s) = 0$$

$$\text{or } sI_1(s) + (2+s)I_2(s) = 0 \quad \text{--- (iv)}$$

$$\Rightarrow I_1(s) = \frac{-(2+s)I_2(s)}{s}$$



Substituting in eq<sup>n</sup> (11), we get

$$-(1+2s)\left(\frac{2+s}{s}\right) I_2(s) + s I_2(s) = \frac{6}{s}$$

$$\Rightarrow I_2(s) \left[ s - \frac{1}{s}(2+s+4s+2s^2) \right] = \frac{6}{s}$$

$$I_2(s) \left[ s^2 - (2+5s+2s^2) \right] = 6$$

$$I_2(s) [s^2 - 2 - 5s - 2s^2] = 6$$

$$I_2(s) = \frac{6}{-s^2 - 5s - 2}$$

$$= \frac{-6}{s^2 + 5s + 2} \quad \text{A}$$

$$\therefore V_o(s) = I_2(s) \cdot 2$$

$$= \frac{-12}{s^2 + 5s + 2} = \frac{-12}{(s+0.438)(s+4.562)}$$

$$= \frac{-2.91}{(s+0.438)} + \frac{2.91}{(s+4.562)} \quad \text{V}$$

18


Good:  
Approach

$$V_o(t) = \mathcal{L}^{-1}[V_o(s)] = -2.91e^{-0.438t} + 2.91e^{-4.562t}$$

$$\therefore V_o(t) = 2.91 \left[ e^{-4.562t} - e^{-0.438t} \right] \quad t \geq 0$$

Q.3 (c) Find the Thevenin's equivalent of circuit shown in figure as seen from :


- (i) terminals a-b  
(ii) terminals c-d

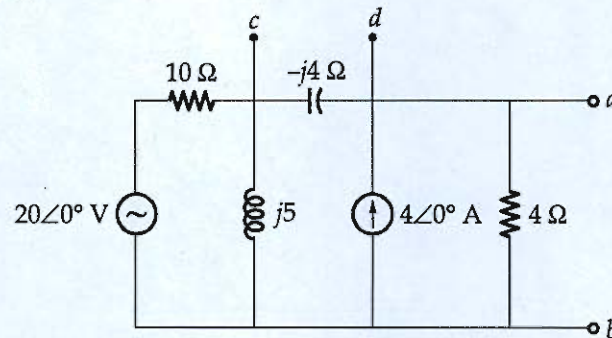

[20 marks]

①

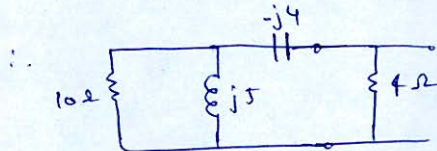To find  $Z_{th}$ , sources needs to be deactivated




$$Z_{eq} = \left\{ (10 \parallel j5) - j4 \right\} \parallel 4$$

$$= \frac{4}{3} \Omega$$

Write steps  
in detail

To find  $V_{oc}$ , we have

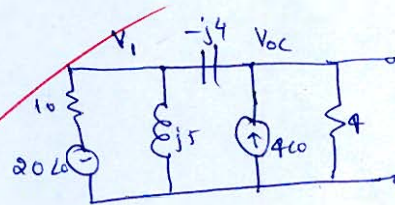

$$\frac{V_1 - 20}{10} + \frac{V_1}{j5} + \frac{V_1 - V_{oc}}{-j4} = 0$$

$$V_1 \left( \frac{1}{10} + \frac{1}{j5} \right) + V_{oc} \left( \frac{1}{j4} \right) = 2 \quad \text{--- (i)}$$

$$\frac{V_{oc}}{4} + \frac{V_{oc} - V_1}{-j4} = 4$$


$$V_{oc} \left( \frac{1}{4} + \frac{1}{j4} \right) + V_1 \left( \frac{1}{j4} \right) = 4 \quad \text{--- (ii)}$$

Solving (i) & (ii) we get


$$V_{oc} = 8 + \frac{16}{3}j = 9.61 \angle 33.69^\circ \text{ V}$$

∴ Thevenin's equivalent is

**Circuit**

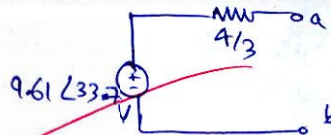

To find  $Z_{th}$

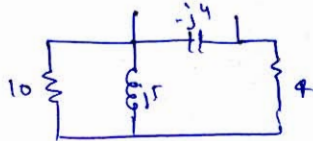

$$Z_{eq} = \left\{ (10 \parallel j5) + 4 \right\} \parallel (-j4) = \frac{8}{3} - 4j = 4.81 \angle -56.31^\circ \Omega$$

To find  $V_{oc}$

From part (i) calculations, we have

$$V_{oc(i)} = 9.61 \angle 33.69^\circ \text{ V}$$


$$\& V_1 = 18.85 \angle 45.02^\circ \text{ V}$$

Hence from the circuit we can conclude that

$$V_{oc(ii)} = V_1 - V_{oc(i)}$$

$$\therefore V_{oc(ii)} = 9.62 \angle 56.34^\circ \text{ V}$$


∴ Thevenin's equivalent circuit is

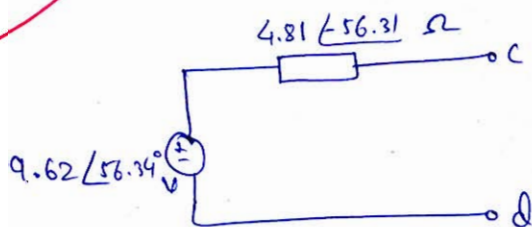

**Good Approach**

18

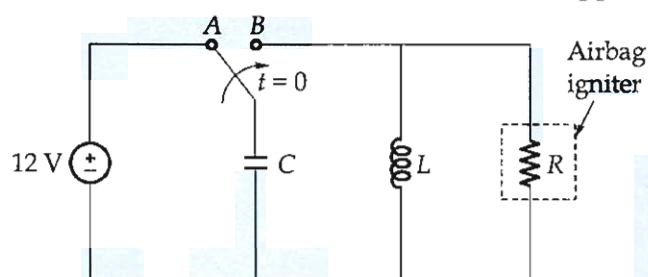- Q.4 (a) An automobile airbag igniter is modelled by the circuit shown in figure. Determine the time, it takes the voltage across the igniter to reach its first extreme (minimum or maximum) after switching from A to B. Let  $R = 3 \Omega$ ,  $C = \frac{1}{30} F$  and  $L = 60 \text{ mH}$ .



[20 marks]








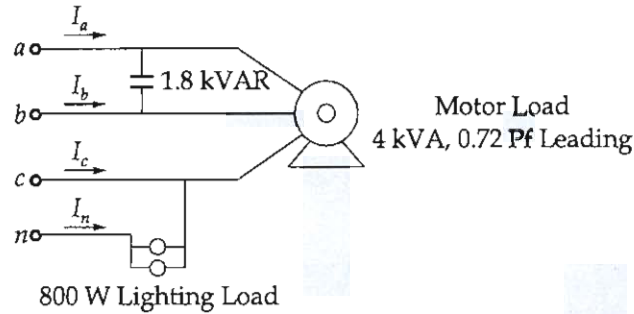Q.4 (b)

In the figure shown, a 3-phase delta connected motor load which is connected to a line of 440 V, draws 4 kVA at a power factor of 0.72 leading. In addition, a single 1.8 kVAR capacitor is connected between line  $a$  and  $b$ , while 800 W lighting load is connected between line  $C$  and neutral. Assuming  $abc$  phase sequence and taking  $V_{an} = V_p \angle 0^\circ$ , find the magnitude and phase angle of currents  $I_a$ ,  $I_b$ ,  $I_c$  and  $I_n$ .




[20 marks]





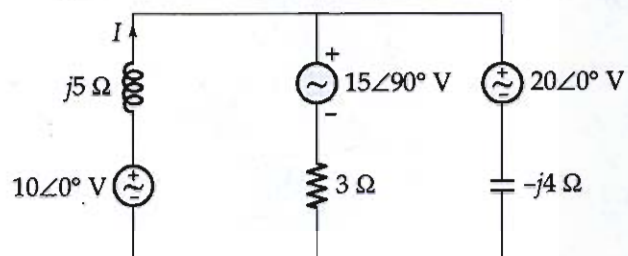Q.4 (c) Find current  $I$  through  $j5\ \Omega$  branch using superposition theorem for the network shown.




[20 marks]






## Section B : Control Systems

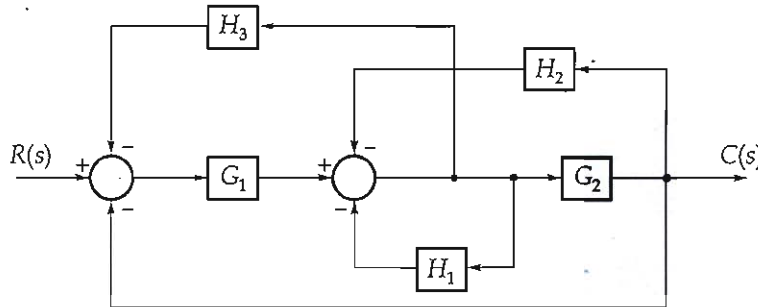Q.5 (a) Using block-diagram reduction technique, find the transfer function  $\frac{C(s)}{R(s)}$ .




[12 marks]

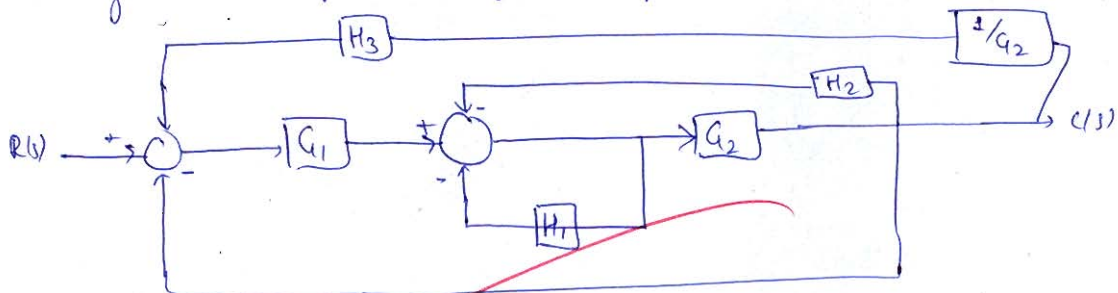
Moving the take off point of  $H_3$  after  $G_2$



on simplifying we get

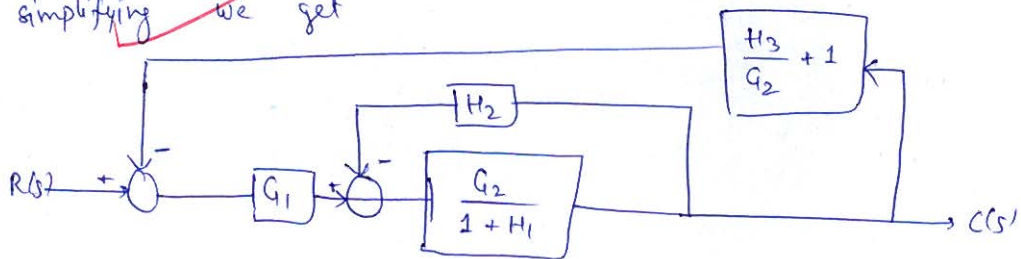

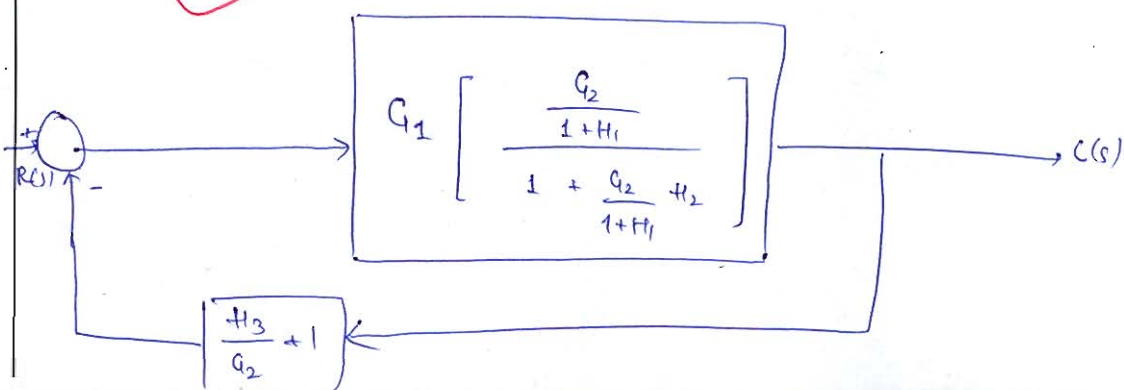
again simplifying  $H_2$  as -ve feedback  
&  $\frac{H_3}{G_2} + 1$  as forward gain after  $H_2$  feedback



On simplification


Forward path  $\Rightarrow \frac{G_1 G_2}{1 + H_1 + G_2 H_2}$

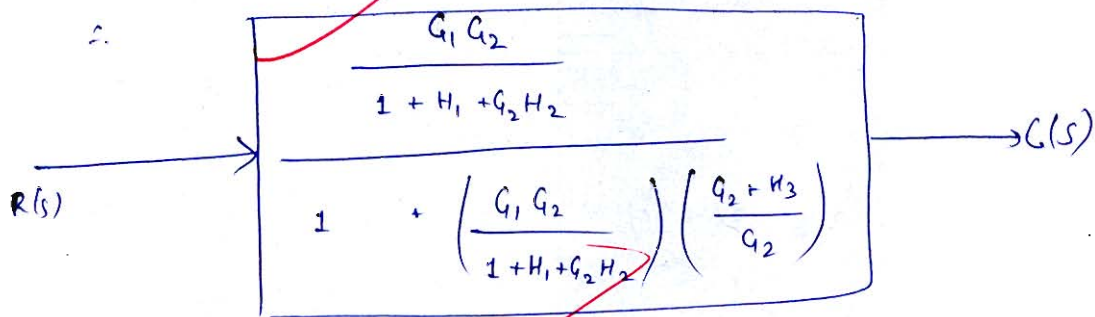Feedback path  $\Rightarrow \frac{G_2 + H_3}{G_2}$



on simplification
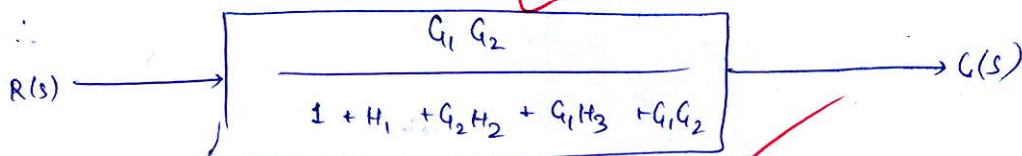
$$\frac{C(s)}{R(s)} = TF(s) = \frac{G_1 G_2}{1 + H_1 + G_2 H_2 + G_1 G_2 + G_1 H_3}$$



Good  
Approach

Q.5 (b) The closed loop transfer function of a system is

$$\frac{C(s)}{R(s)} = \frac{100}{s^6 + 3s^5 + 8s^4 + 18s^3 + 20s^2 + 24s + 16}$$

Determine the number of poles on the RHP, LHP and on the  $j\omega$ -axis and comment on the stability of the system.

[12 marks]

Using RH criteria to find location of poles

$$s^6 + 3s^5 + 8s^4 + 18s^3 + 20s^2 + 24s + 16 = 0$$

$s^6$	1	8	20	16
$s^5$	3	18	24	
$s^4$	2	12	16	
$s^3$	0	0		

as we got all terms in  $s^3$  row as zero

$\Rightarrow$  there are 4 poles symmetric to the origin

forming auxiliary eq<sup>n</sup> from  $s^4$  row

$$A(s) = 2s^4 + 12s^2$$

$$\frac{d}{ds} A(s) = 8s^3 + 24s$$

roots of this polynomial are ( $A(s)=0$ )  
 $0, 0, \pm j\sqrt{6}$

$\therefore$  RH table becomes

$s^3$	8	24
$s^2$	6	16
$s^1$	$\frac{8}{3}$	0
$s^0$	16	

∴ the complete table with 1<sup>st</sup> column is

$s^6$	1
$s^5$	3
$s^4$	2
$s^3$	8
$s^2$	6
$s^1$	$\frac{8}{3}$
$s^0$	16

Before the zero row, there is no sign change

⇒ 2 poles in LHP

After the zero row, there is no sign change

⇒ 4 poles symmetric to origin

& none of them are in RHP

⇒ none of them in LHP

⇒ all 4 are on  $j\omega$  axis

& two of them are at origin as

evident from auxiliary eq<sup>n</sup>.  $A(s) = 0$ .

∴ Out of 6 poles

2 poles — LHP

0 poles — RHP

4 poles —  $j\omega$ -axis

↳ at  $j\sqrt{6}$ ,  $-j\sqrt{6}$  & repeated at origin

∴ System is unstable due to repeated poles at the origin.

11  
Good Approach



Q.5 (c) The open-loop transfer function of a unity feedback system is

$$G(s) = \frac{K(s + \alpha)}{s(s^2 + 12s + 32)}$$

Find the value of  $K$  and  $\alpha$  so that the velocity error constant is 6.25 and the second-order response has a natural frequency of 5 rad/s. Assume that the system is stable.

[12 marks]

given  $\omega_n = 5 \text{ rad/s}$

&  $K_v = 6.25$

we know  $K_v = \lim_{s \rightarrow 0} s G(s)$

$$6.25 = \lim_{s \rightarrow 0} \frac{K(s + \alpha)}{(s^2 + 12s + 32)}$$

$$6.25 = \frac{K\alpha}{32}$$

$$\therefore K\alpha = 200 \quad \text{--- (i)}$$

Now  $q(s) = s^3 + 12s^2 + 32s + Ks + K\alpha$   
 $= s^3 + 12s^2 + (32 + K)s + 200$  --- (ii)

a third order system will have the characteristic eq<sup>n</sup> of the form

$$(s + p)(s^2 + 2\zeta\omega_n s + \omega_n^2) = 0$$

where the 2<sup>nd</sup> order term will be dominant

$$s^3 + (2\zeta\omega_n + p)s^2 + (\omega_n^2 + 2\zeta\omega_n p)s + p\omega_n^2 = 0 \quad \text{--- (iii)}$$

comparing eq (ii) & eq (iii) we get

$$2\zeta\omega_n + p = 12$$

$$32 + K = \omega_n^2 + 2\zeta\omega_n p$$

$$200 = p\omega_n^2$$

$$\text{given } \omega_n = 5 \Rightarrow \omega_n^2 = 25$$

$$\therefore 10\gamma + p = 12$$

$$25 + 10\gamma p = 32 + K$$

$$25p = 200$$

$$\Rightarrow p = 8$$

$$\gamma = 0.4$$

~~$$K = 17$$~~

$$K = 25$$

$$\therefore \alpha = \frac{200}{K} = 8$$

Hence


$$K = 25$$

$$\alpha = 8$$

Good  
Approach

11

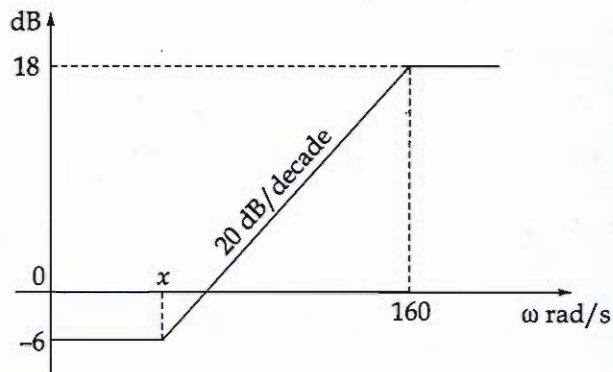Q.5 (d) An asymptotic bode magnitude plot is shown in figure.



Find the transfer function and gain cross-over frequency.

[12 marks]

initial slope is 0  
 $\Rightarrow$  no pole or zero at origin

at  $\omega = x$ , slope = 20 dB/dec

$\Rightarrow$  zero at  $\omega = x$

at  $\omega = 160$  slope = 0 again

$\Rightarrow$  pole at  $\omega = 160$

$$\therefore \text{TF} = \frac{K \left( \frac{s}{x} + 1 \right)}{\left( \frac{s}{160} + 1 \right)}$$

at  $\omega = x$ , gain = -6 dB

at  $\omega = 160$  gain = 18 dB

& slope = 20 dB/decade

$$\therefore \frac{18 - (-6)}{\log 160 - \log x} = 20 \quad \Rightarrow \quad \log \frac{160}{x} = \frac{6}{5}$$

$$\Rightarrow x = 48.19 \text{ rad/sec}$$

$$\Rightarrow x = 10.095$$

we know  $-20 + 20 \log K = \text{gain dB}$

$$x=0$$

$$\Rightarrow 20 \log K = -6 \quad (\text{at } \omega = x)$$

$$\Rightarrow K = 0.5$$

$$\therefore \text{TF}(s) = \frac{0.5 \left( 1 + \frac{s}{10.095} \right)}{\left( 1 + \frac{s}{160} \right)}$$

at  $\omega_{gc}$ , gain = 0 dB or  $|gain| = 1$

from the graph

$$\frac{18 - 0}{\log 160 - \log \omega_{gc}} = 20$$

$$\log \frac{160}{\omega_{gc}} = \frac{18}{20}$$

$$\omega_{gc} = 20.14 \text{ rad/sec}$$

11

Good  
APPROACH



- Q.5 (e) A system is represented by the state model,  $\dot{X} = \begin{bmatrix} 0 & 0 \\ 3 & -3 \end{bmatrix} X + \begin{bmatrix} 1 \\ 0 \end{bmatrix} r(t)$  and  $y = [1 \ 2]X$ . If the initial state vector is  $\begin{bmatrix} 1 \\ 2 \end{bmatrix}$ , find zero input response of the system.

[12 marks]

To obtain ZIR *Zero input response*

$$i/p = 0$$

$$\therefore r(t) = 0$$

$$\therefore \dot{X} = \begin{bmatrix} 0 & 0 \\ +3 & -3 \end{bmatrix} X$$

$$\Rightarrow \dot{X} = AX$$

$$y = [1 \ 2] X$$

$$\Rightarrow y = CX$$

applying Laplace, we get

$$sX(s) - x(0) = AX(s), \quad Y(s) = CX(s)$$

$$(sI - A)X(s) = x(0)$$

$$X(s) = (sI - A)^{-1} x(0)$$

$$\Rightarrow Y(s) = C \left\{ (sI - A)^{-1} x(0) \right\}$$

$$= [1 \ 2] \left[ \begin{bmatrix} s & 0 \\ -3 & s+3 \end{bmatrix}^{-1} \begin{bmatrix} 1 \\ 2 \end{bmatrix} \right]$$

$$= \frac{[1 \ 2] \begin{bmatrix} s+3 & 0 \\ 3 & s \end{bmatrix} \begin{bmatrix} 1 \\ 2 \end{bmatrix}}{s(s+3)}$$

$$= \frac{\begin{bmatrix} 1 & 2 \end{bmatrix} \begin{bmatrix} s+3 \\ 3+2s \end{bmatrix}}{s(s+3)}$$

$$= \frac{s+3 + 6+4s}{s(s+3)}$$

$$= \frac{5s+9}{s(s+3)}$$

$$= \frac{3}{s} + \frac{2}{s+3}$$

$$Y(s) = \frac{3}{s} + \frac{2}{s+3}$$

$$\therefore y(t) = \frac{3 + 2e^{-3t}}{(3 + 2e^{-3t})} u(t)$$

$$\therefore \text{ZIR} = (3 + 2e^{-3t}) u(t)$$

Good  
Approach

11

- Q.6 (a) The forward path gain of a first-order unity negative feedback system is  $G(s) = \frac{K}{s + a}$ . The unit step response reveals that the time constant is  $1/6$  sec. When the location of the pole is moved toward the origin by half its distance, the new time constant is found to be  $1/4$  sec. Find the value of  $a$  and  $K$ . For the time constant to be  $1/8$  sec, find the location of the closed-loop pole.

[20 marks]





Q.6 (b) A unity feedback system has open-loop transfer function

$$G(s) = \frac{3(2-s)}{(s+1)(s+5)}$$

Using Nyquist stability criterion, check whether the closed-loop system is stable or not. If the system is stable, find the gain margin and phase margin.

[20 marks]





Q.6 (c) A feedback system has open-loop transfer function

$$G(s)H(s) = \frac{K(s+5)}{(s+1)^2}$$

Sketch the root locus.


[20 marks]





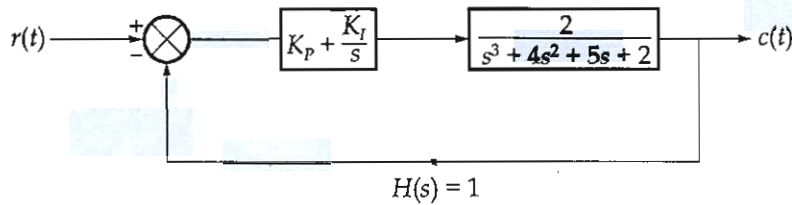Q.7 (a)

The stability of overall system shown in figure is controlled by tuning the PI parameters  $K_p$  and  $K_I$ . Find the maximum value of  $K_I$  that can be selected so as to keep overall system stable or in worst case, marginally stable.



[20 marks]

$$G(s) = \frac{2(K_I + sK_p)}{s(s^3 + 4s^2 + 5s + 2)}$$

Write all  
steps

$$\begin{aligned} TF(s) &= \frac{s^4 + 4s^3 + 5s^2 + 2s + 2K_p s + 2K_I}{s^4 + 4s^3 + 5s^2 + (2 + 2K_p)s + 2K_I} \\ &= \frac{s^4 + 4s^3 + 5s^2 + (2 + 2K_p)s + 2K_I}{s^4 + 4s^3 + 5s^2 + (2 + 2K_p)s + 2K_I} \end{aligned}$$

applying RH criteria

$$2 + 2K_p > 0$$

$$\Rightarrow K_p > -1$$

$$2K_I > 0$$

$$\Rightarrow K_I > 0$$

forming RH table

$$s^4 \quad 1 \quad 5 \quad 2K_I$$

$$s^3 \quad 4 \quad 2 + 2K_p$$

$$s^2 \quad \frac{20 - 2 - 2K_p}{4} \quad 2K_I$$

$$s^1 \quad 2 \rightarrow (2 + 2K_p) - \frac{8K_I}{(20 - 2 - 2K_p)}$$

$$s^0 \quad 2K_I$$

~~at marginally~~

for stability all coefficients of first column  $> 0$

$$20 - 2 - 2K_p > 0$$

$$18 > 2K_p$$

$$K_p < 9$$

$$2 + 2K_p > \frac{32 K_I}{20 - 2 - 2K_p}$$

$$(2 + 2K_p) (18 - 2K_p) > 32 K_I$$

$$(2 + 2K_p) (18 - 2K_p) > 32 K_I$$

$$\therefore -1 < K_p < 9$$

$$K_I > 0$$

for stability

$$K_{I \max} = \frac{25}{8} \text{ (for marginally stable system)}$$

at  $K_p = 4$

- Q.7 (b) The open loop transfer function of a unity feedback system is  $G_p(s) = \frac{K}{s(s+2)}$ . Design a lead compensator to have a velocity-error constant of  $20s^{-1}$  and phase margin of at least  $50^\circ$ . Indicate each step that you are using.

[20 marks]







- Q.7 (c) A negative unity feedback control system is expected to meet the following specifications : damping ratio is 0.5, natural frequency is  $\sqrt{10}$  rad/sec and the steady-state error is 10%. The open-loop transfer function is  $G(s) = \frac{K(s+\alpha)}{(s+\beta)^2}$ . Find the values of  $K$ ,  $\alpha$  and  $\beta$ .

[20 marks]

$$G(s) = \frac{K(s+\alpha)}{(s+\beta)^2}$$

$$TF(s) = \frac{K(s+\alpha)}{s^2 + 2s\beta + \beta^2 + Ks + K\alpha}$$

$$q(s) = s^2 + (2\beta + K)s + (\beta^2 + K\alpha)$$

given  $\gamma = 0.5$ ,  $\omega_n = \sqrt{10}$

$$\Rightarrow q(s) = s^2 + 2\gamma\omega_n s + \omega_n^2$$

$$= s^2 + \sqrt{10}s + 10$$

~~also since the system is type 0~~

~~$\therefore E_{ss} = 0$~~

Try to  
avoid

$$\Rightarrow \boxed{2\beta + K = \sqrt{10}}, \quad \boxed{\beta^2 + K\alpha = 10}$$

as the system is type 0 system

$$\Rightarrow K_p \neq 0$$

$$E_{ss} = \frac{1}{1+K_p} = 0.1$$

$$\Rightarrow K_p = 9$$

$$\Rightarrow \frac{K\alpha}{\beta^2} = 9$$

$$\Rightarrow \boxed{K\alpha = 9\beta^2}$$

Hence  $K\alpha = 9\beta^2$  — (i)

$\beta^2 + K\alpha = 10$  — (ii)

$2\beta + K = \sqrt{10}$  — (iii)

$\therefore$  from (i) & (ii)

$\beta^2 + 9\beta^2 = 10$

$\beta = \pm 1$

$\beta = -1$  is not possible

Case I

$\beta = 1$

$K\alpha = 9$

$2 + K = \sqrt{10}$

$K = 1.16$

$\alpha = 7.74$

$\beta = 1$

Case II

$\beta = -1$

$K\alpha = 9$

$-2 + K = \sqrt{10}$

$K = 5.16$

$\alpha = 1.74$

$\beta = -1$

17

$\therefore$  By setting the open loop pole to either  $+1$  or  $-1$  we may get two set of values.

In order to follow open loop stability, we may go for  $\beta = -1$



Q.8 (a) Draw the log-magnitude asymptotic plot for the transfer function.

$$G(s)H(s) = \frac{1000s}{(s+10)(s+100)}$$

Also find the gain cross-over frequency and the frequencies at 3 dB attenuation.

[20 marks]



Q.8 (b) Consider the system with state equation

$$\dot{X}(t) = AX(t) + BU(t)$$

where

$$A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -5 & -6 \end{bmatrix}, B = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$

By using the state feedback control  $u = -KX$ , it is desired to have the closed-loop poles at

$$u_1 = -2 + j4, u_2 = -2 - j4, u_3 = -10$$

Determine the state feedback gain matrix  $K$ . Also check the validity of arbitrary pole placement.


[20 marks]







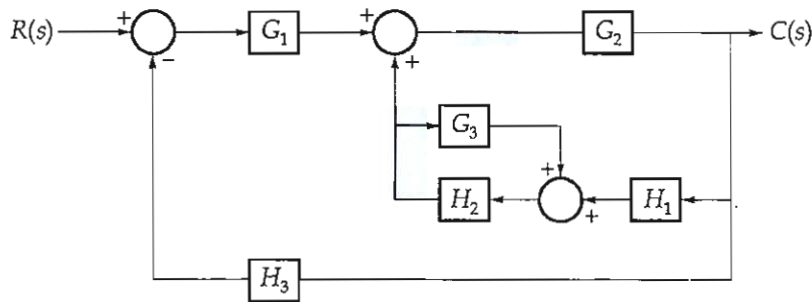
Q.8 (c) (i) For the block-diagram representation for a system shown below :



Draw the signal flow graph and determine the overall transfer function using Mason's gain formula.

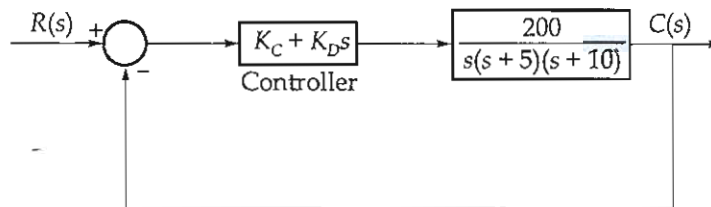(ii) A unity feedback system has plant transfer function  $G_C(s) = \frac{200}{s(s+5)(s+10)}$ .

The plant is controlled by a PD controller. Find the ranges of controller gains ( $K_C$ ,  $K_D$ ) for the system shown below to be stable. Also draw the region of stability.




[12 + 8 marks]



**Space for Rough Work**

---

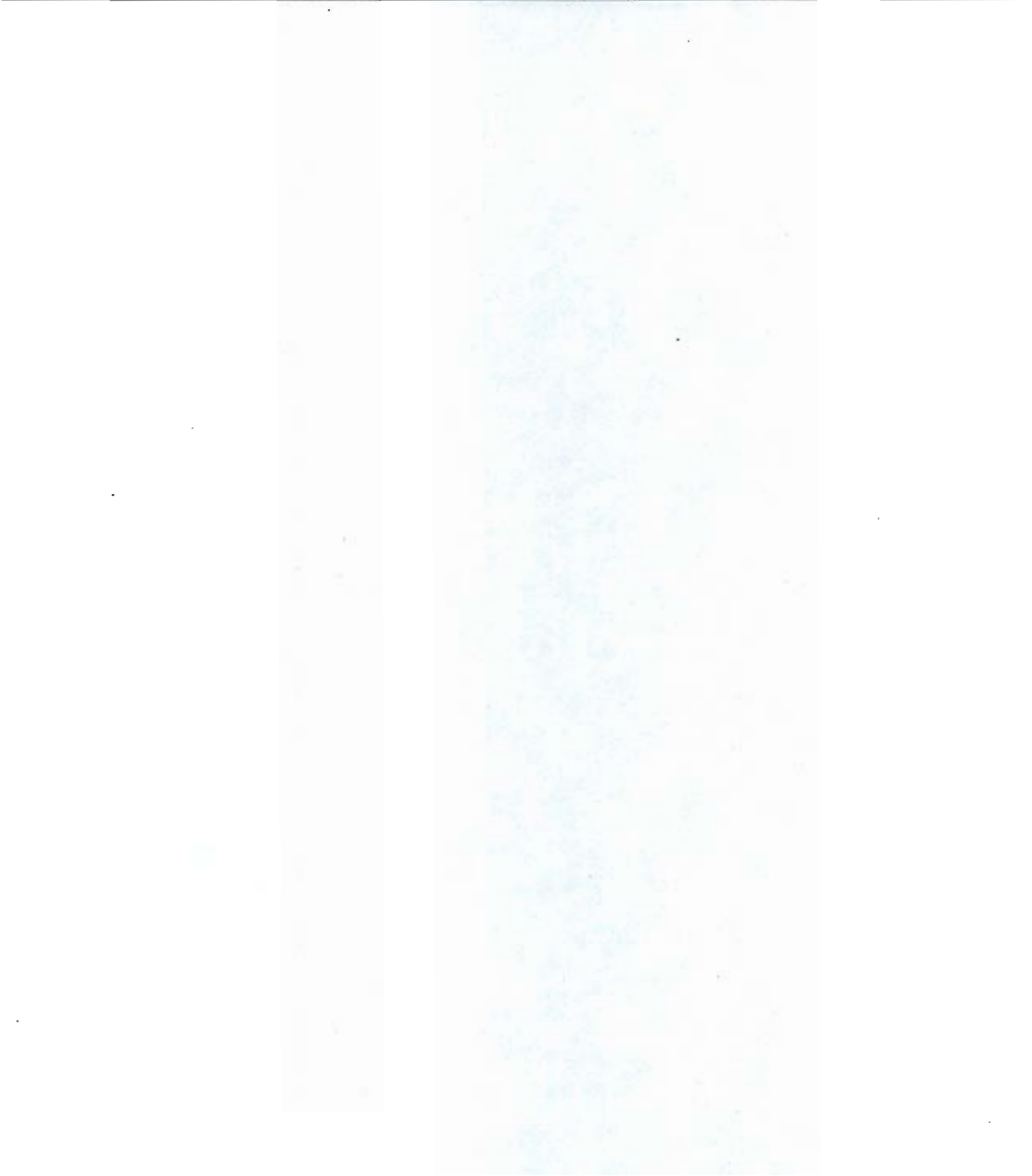

## Space for Rough Work

---

$$i = C \frac{dv}{dt}$$

$$i = C V(0)$$

$$V = \frac{C V(0)}{sL}$$

$$\frac{1}{1-j}$$

$$245.76 - 45.056j^\circ$$

$$\frac{4 - V_{oc} \left[ \frac{1}{4} + \frac{1}{4}j \right]}{\text{scribble}} \times \frac{-4}{j}$$

$$\left[ 16j + (1-j)V_{oc} \right] \left[ \frac{1}{10} + \frac{j}{20} \right] + V_{oc} \left( -\frac{j}{4} \right) = 2$$

$$\left( \frac{-4}{5} + \frac{8j}{5} \right) + \left( \frac{3}{20} - \frac{j}{20} \right) V_{oc} + V_{oc} \left( -\frac{j}{4} \right) = 2$$