

Write answer  
in detail.



**MADE EASY**

India's Best Institute for IES, GATE & PSUs

## ESE 2023 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

### Electrical Engineering

**Test-5 : Basic Electronics Engineering + Analog Electronics +  
Electrical Materials + Electrical Machines-1 + Power Systems-2**

Name : .....

Roll No :

#### Test Centres

Delhi ☒ Bhopal ☐ Jaipur ☐  
Pune ☐ Kolkata ☐ Bhubaneswar ☐ Hyderabad ☐

#### Student's Signature

#### Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

#### FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	38
Q.2	49
Q.3	
Q.4	38
Section-B	
Q.5	24
Q.6	
Q.7	41
Q.8	
<b>Total Marks Obtained</b>	<b>190</b>

Signature of Evaluator

Cross Checked by

*Sourabh Kumar*

Write answer  
in detail.



# MADE EASY

India's Best Institute for IES, GATE & PSUs

## ESE 2023 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

### Electrical Engineering

Saket

Test-5 : Basic Electronics Engineering + Analog Electronics +  
Electrical Materials + Electrical Machines-1 + Power Systems-2

Name : NIKHIL KUMAR

Roll No : EE23MTDLA007

#### Test Centres

Delhi ☒ Bhopal ☐ Jaipur ☐  
Pune ☐ Kolkata ☐ Bhubaneswar ☐ Hyderabad ☐

#### Student's Signature

#### Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

#### FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	38
Q.2	49
Q.3	
Q.4	38
Section-B	
Q.5	24
Q.6	
Q.7	41
Q.8	
<b>Total Marks Obtained</b>	<b>190</b>

Signature of Evaluator

Cross Checked by

Sourabh Kumar

## IMPORTANT INSTRUCTIONS

**CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.**

### DONT'S


1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

### DO'S

1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

**Section A : Basic Electronics Engineering + Analog Electronics + Electrical Materials**

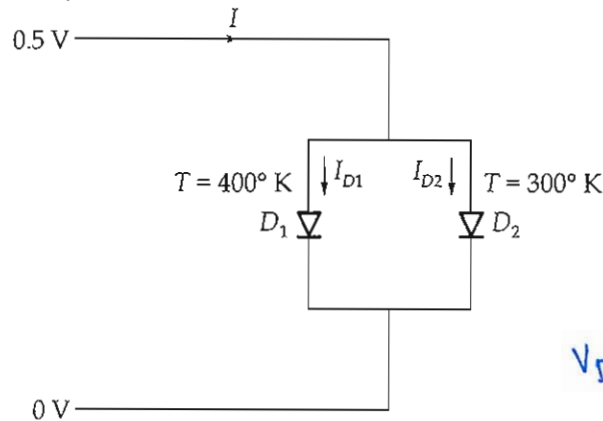- Q.1 (a) For the circuit shown in figure below, the two identical Si PN junction diodes are connected in parallel and a 0.5 V of forward bias is applied. Diode  $D_1$  is heated to  $400^\circ\text{K}$  temperature and diode  $D_2$  was kept at  $300^\circ\text{K}$  temperature. Calculate the ratio between the current flowing through diode  $D_1$  and diode  $D_2$ . (Ideality factor of Si = 2).



$$V_D = 0.5$$

[12 marks]

$$I_{D1} = I_s e^{V_D / n V_{T1}}$$

$$I_{D2} = I_s e^{V_D / n V_{T2}}$$

$$T_1 = 400\text{K}$$

$$T_2 = 300\text{K}$$

$$n = 2$$

$$\Rightarrow \frac{I_{D1}}{I_{D2}} = e^{\frac{0.5}{2} \left( \frac{1}{V_{T1}} - \frac{1}{V_{T2}} \right)}$$

$$V_{T1} = \frac{400}{11600} = 34.48\text{ mV}$$

$$V_{T2} = \frac{300}{11600} = 25.86\text{ mV}$$

$$\Rightarrow \frac{I_{D1}}{I_{D2}} = e^{\frac{0.5}{2} (-9.66)} = 0.0892$$

$$0.0868$$

Write in  
detail





- Q.1 (b) The average magnetic moment along the field direction per spin in Bohr magneton when a paramagnetic spin system is subjected to a uniform magnetic field is  $3.2 \times 10^{-4}$  Bohr magneton. Calculate the uniform magnetic field applied if the temperature is  $27^\circ\text{C}$ . (1 Bohr magneton =  $9.27 \times 10^{-24}$  A/m<sup>2</sup>).

[12 marks]

$$M = \frac{N \mu_B^2 B}{4kT} = N \frac{\mu_B^2 B}{4kT} \quad \text{--- (1)}$$

$$\Rightarrow \frac{3.2 \times 10^{-4} \times 9.27 \times 10^{-24}}{4 \times 10^{-24}} = \frac{1.6 \times 10^{-19} \times B}{4 \times 9.1 \times 10^{-31}}$$


$$M = N \mu_B$$

$$\Rightarrow \frac{\mu_B B}{4kT} = 1$$

$$\Rightarrow B = \frac{4kT}{\mu_B} = 5.2638 \text{ Tesla}$$



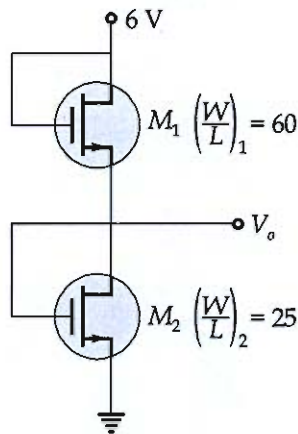Q.1 (c) Consider the circuit shown in figure below :



If both transistor have parameters  $\mu_n C_{ox} = 40 \mu\text{A}/\text{V}^2$  and  $V_{Th} = 0.9 \text{ V}$  then calculate the output voltage  $V_o$ .

[12 marks]

$$V_{GS1} = 6 - V_o$$

$$V_{GS2} = V_o$$

$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{Th})^2$$

$$= \frac{1}{2} \times 40 \times 60 (6 - V_o - 0.9)^2 \quad \text{--- (1)}$$

$$I_2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{Th})^2$$

$$= \frac{1}{2} \times 40 \times 25 (V_o - 0.9)^2 \quad \text{--- (2)}$$

$$I_1 = I_2$$

$$\Rightarrow 1200 (5.1 - V_o)^2 = 500 (V_o - 0.9)^2$$

$$\Rightarrow \frac{V_o - 0.9}{5.1 - V_o} = \pm 1.55$$

$$V_o = 3.452, 12.736 \text{ V (X)}$$

$V_o = 3.452$  (Because both (1) & (2) are in saturation)

Good  
Approach





Q.1(d) Write a short note on Top-down technique and bottom-up technique used in nano-material synthesis.

[12 marks]

Top Down approach method breaking of layers from top to bottom. for formation of nanomaterials. Nano particles are created.



Bottom up Approach → layer by layer deposition of nano particles material. formed by vapour deposition of nano particles

8





Q.1 (e) The Hall coefficient of a certain silicon specimen was found to be  $-8.25 \times 10^{-5} \text{ m}^3/\text{C}$  at  $300^\circ \text{K}$ . If the conductivity is  $2.50 \text{ } \Omega/\text{cm}$ , then find :

- (i) type of semiconductor
- (ii) density of charge carrier
- (iii) mobility of charge carrier

[12 marks]

i)  $R_H = -ve$

$\Rightarrow$  is  $n$ -type semiconductor

ii)  $|R_H| = \frac{1}{ne}$

$$\Rightarrow n = \frac{1}{R_H e} = \frac{1}{8.25 \times 10^{-5} \times 1.6 \times 10^{-19}}$$

$$= 7.575 \times 10^{20} / \text{m}^3$$

iii)  $\sigma = ne\mu_n = 2.5 \times 10^2 \text{ } \Omega/\text{m}$

$$\Rightarrow \mu_n = \frac{2.5 \times 10^2}{ne} = \frac{2.5 \times 10^2}{7.575 \times 10^{20} \times 1.6 \times 10^{-19}}$$

$$= 0.020625 \text{ } \Omega\text{-m}^2$$


(8)

Write answer in  
detail





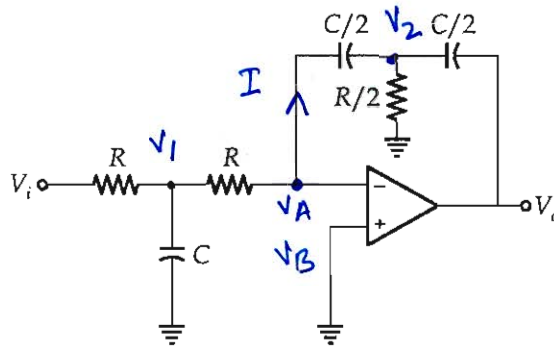Q.2 (a) Consider the circuit shown in figure



Find the relation between input  $V_i$  and output  $V_o$ . (Assume the op-amp is ideal).

[20 marks]

KU at  $V_1$

$$\Rightarrow \frac{V_1 - V_i}{R} + (V_1) \left( \delta + \frac{V_1 - 0}{R} \right) = 0$$

$$\Rightarrow V_1 - V_i + V_1 R(\delta + \frac{1}{R}) = 0 \quad \left( \text{as } V_A = V_B = 0 \right. \\ \left. \text{By V.C} \right)$$

$$V_1 = \frac{V_i}{2 + R\delta}$$

$$I = \frac{V_1 - 0}{R} = \frac{V_i}{R(2 + R\delta)}$$

$$V_2 = 0 - I \times \frac{2}{\delta} = -\frac{V_i}{R(2 + R\delta)} \times \frac{2}{\delta} \quad - (1)$$

KU at  $V_2$

$$\frac{(V_2 - 0) \left( \frac{\delta}{2} \right) + (V_2 - V_o) \left( \frac{\delta}{2} \right) + \frac{2V_2}{R} = 0$$

$$\Rightarrow V_2 \left( \delta + \frac{2}{R} \right) = V_o \frac{\delta}{2}$$

Substituting  $V_2$  from (1).

$$\Rightarrow \frac{-V_i}{R(2 + R\delta)} \times \frac{2}{\delta} \times \left( \frac{2 + R\delta}{R} \right) = V_o \frac{\delta}{2}$$

$$V_o = \frac{-4}{R^2 \delta^2} V_i$$

$$\Rightarrow V_o = \frac{-4}{R^2 \delta^2} \int \int V_i(t) dt^2$$

Write  
answer  
in detail

18



Q.2 (b) Zirconium has an HCP crystal structure and a density of  $6.51 \text{ g/cm}^3$ .

(i) Calculate the volume of its unit cell in cubic meters if the atomic weight of Zirconium is  $91.2 \text{ g/mol}$ .

(ii) If  $c/a$  ratio is  $1.593$ , then compute the values of  $c$  and  $a$ .

[20 marks]

$$(i) - \text{Density} = \frac{ZM}{N_A (a^3)} \quad \begin{array}{l} a^3 = \text{volume of} \\ \text{unit cell.} \\ Z = 6 \text{ (HCP)} \end{array}$$

$\Rightarrow$  from given data.

$$\begin{aligned} \text{Volume} &= \frac{6 \times 91.2}{6.51 \times 6.023 \times 10^{23}} \text{ cm}^3 \\ &= 1.395 \times 10^{-22} \text{ cm}^3 \\ &= 1.395 \times 10^{-28} \text{ m}^3 \end{aligned}$$

13

ii

$$c = 1.593a$$

$$\frac{c+a}{2} = \frac{\sqrt{3}}{2} a \Rightarrow \frac{a}{2} = \frac{2.593a}{2} = 1.2965a$$

$$\text{Volume} = 1.395 \times 10^{-28} = 24\sqrt{2} a^3$$

$$a = 1.601 \times 10^{-10} = 1.601 \text{ \AA}$$

$$\Rightarrow a = 1.2348 \text{ \AA}$$

$$c = 1.9671 \text{ \AA}$$


$$\begin{aligned} a &= 3.23 \times 10^{-10} \text{ m} \\ &= 0.323 \text{ nm} \end{aligned}$$

$$c = 0.5145 \text{ nm}$$





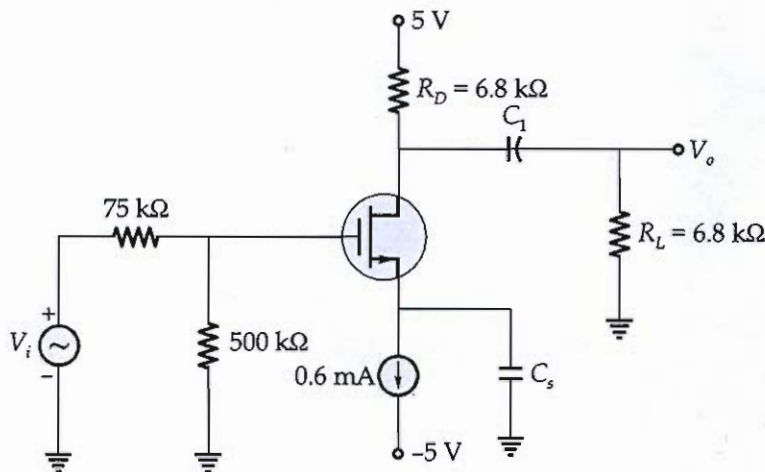- Q.2 (c) Determine the small signal voltage gain of the circuit shown in below figure having parameters  $V_T = 0.8 \text{ V}$ ,  $k = \frac{\mu_n C_{ox} W}{2L} = 1.2 \text{ mA/V}^2$ ,  $\lambda = 0$ . Also calculation gate-to-source voltage ( $V_{GSQ}$ ).



[20 marks]

Dc analysis

$$I_D = 0.6 \text{ mA}$$

$$I_D = k (V_{GS} - V_T)^2$$


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = 2k (V_{GS} - V_T)$$

$$\Rightarrow 0.6 \text{ mA} = 1.2 (V_{GS} - 0.8)^2$$

$$\Rightarrow V_{GSQ} = 1.507 \text{ V}$$

$$g_m = 2 \times 1.2 \times (1.507 - 0.8) = 1.6968 \text{ mA/V}$$

Ac analysis

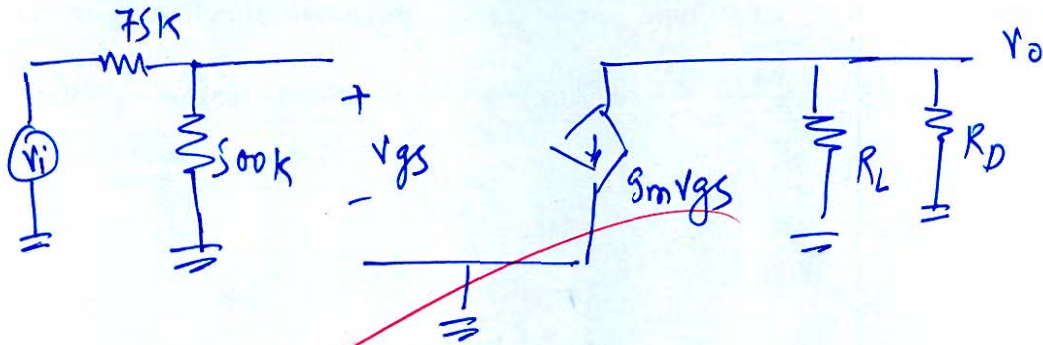

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$V_{gs} = \frac{500k}{500k + 75k} V_i = 0.8695 V_i$$

$$z) \quad V_o = -1.6968 \times 0.8695 V_i \times 3.4$$

$$A_v = \frac{V_o}{V_i} = -5.0162$$

18

Write answer  
in detail

- Q.3 (a)** The electron mobility of Indium (In) is measured to be  $7.5 \text{ cm}^2/\text{V-s}$  and the resistivity of In is  $9.43 \times 10^{-6} \Omega\text{-m}$  at room temperature ( $27^\circ\text{C}$ ).
- (i) Calculate the number of free electrons donated by each In atom in crystal.
  - (ii) If the mean free path of electrons in In is  $8.2 \text{ nm}$  then calculate the mean speed of electrons in In.
  - (iii) Calculate the thermal conductivity of In at room temperature.
- (Assume atomic mass of In =  $115 \text{ g/mol}$  and density =  $7.3 \text{ g/cm}^3$ )


**[20 marks]**







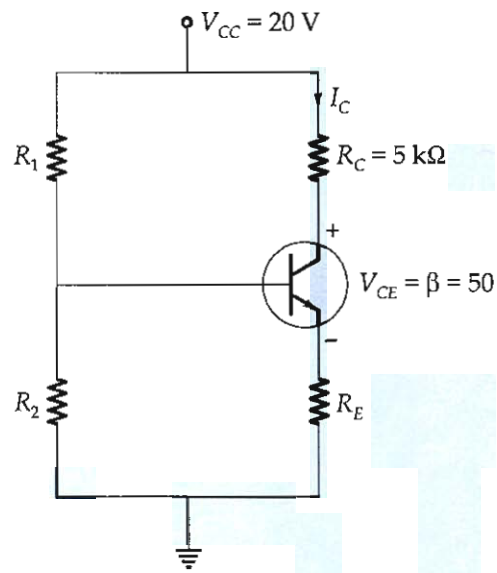Q.3 (b) A silicon transistor with  $\beta = 50$  is used in a self bias circuit as shown in figure below.



The operating point is  $Q(11.5 \text{ V}, 1.5 \text{ mA})$ . For stability factor  $S \leq 2$ , determine the values of  $R_1$ ,  $R_2$  and  $R_E$ .

[20 marks]







- Q.3 (c)
- (i) An amplifier has a mid-frequency gain of 800. Its upper and lower cut-off frequency  $f_U$  and  $f_L$  are 16 kHz and 40 Hz respectively. Determine the bandwidth of the amplifier. What will be the bandwidth if 2% of the output signal is given as a negative feedback?
- (ii) Define superconductivity. What are the condition required for superconductor? Also briefly discuss the properties of superconductor.

[10 + 10 marks]





- Q.4 (a) (i) A crystal oscillator has the following parameters :
- $L_s = 0.33 \text{ H}$ ,  $C_s = 0.065 \text{ pF}$ ,  $C_p = 1 \text{ pF}$ ,  $R_s = 5.5 \text{ k}\Omega$
- (a) Calculate the series-resonant frequency.
- (b) By what percentage does the parallel-resonant frequency exceed the series resonant frequency?
- (c) Calculate the quality factor  $Q$  of the crystal at series and parallel resonant frequencies.
- (ii) A solid specimen of dielectric has  $\epsilon_r = 4.1$  and  $\tan \delta = 0.001$  at a frequency of  $60 \text{ Hz}$ . If it is subjected to an alternating field of  $45 \text{ kV/cm}$  then calculate the heat generated in the specimen due to the dielectric loss.

[15 + 5 marks]

Ans. series ( $\omega_s$ ) =  $\frac{1}{\sqrt{L_s C_s}}$

$$= \frac{1}{\sqrt{0.33 \times 0.065 \times 10^{-12}}} = 6.827 \text{ Mrad/s.}$$

Parallel ( $\omega_p$ ) =  $\frac{1}{\sqrt{L_s \left( \frac{C_s C_p}{C_s + C_p} \right)}}$  =  $7.0463 \text{ Mrad/s.}$

(2)

ii.  $\% = \frac{\omega_p - \omega_s}{\omega_s} \times 100$

$$= \frac{7.0463 - 6.827}{6.827} \times 100 = 32.122\%$$

① At series resonance.  $Q_s = \frac{\omega_s L_s}{R_s} = 409.62$

$Q_p = \frac{1}{\omega_p R_s C_p} = 25.8037$




ii)  $\epsilon'_L = 4.1$      $\tan \delta = 0.001$      $f = 60 \text{ Hz}$   
 $E = 45 \text{ kV/cm}$      $\tan \delta = \frac{\epsilon''_L}{\epsilon'_L} \Rightarrow \epsilon''_L = 4.1 \times 10^{-3}$

$$\begin{aligned}
 E &= \omega \epsilon_0 \epsilon''_L E^2 \\
 \text{(energy loss)} &= (120\pi) \times 8.85 \times 10^{-12} \times 4.1 \times 10^{-3} \times (45 \times 10^5)^2 \\
 &= 297.27 \text{ J}
 \end{aligned}$$



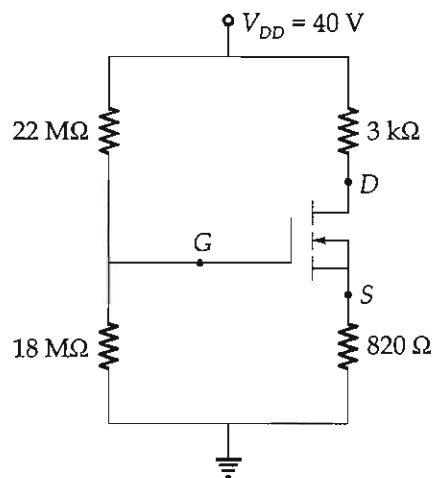Q.4 (b) Consider the circuit shown below :



If  $V_{GS(TH)} = 5\text{ V}$ ,  $I_{D(ON)} = 3\text{ mA}$  at  $V_{GS(ON)} = 10\text{ V}$ , then determine  $I_{DQ}$ ,  $V_{GSQ}$  and  $V_{DS}$ .

[20 marks]

$$I_{DQ} = k_n (V_{GS} - V_{TH})^2$$

from given data.

$$\Rightarrow 3 = k_n (10 - 5)^2 \Rightarrow k_n = \frac{3}{25} \text{ mA/V}^2$$

from the figure.

$$V_G = \frac{18 \times 40}{18 + 22} = 18\text{ V}$$

$$V_S = 0.82 I_D$$

$$I_D = \frac{3}{25} (18 - 0.82 I_D - 5)^2$$

$$\Rightarrow \frac{25 I_D}{3} = (13 - 0.82 I_D)^2$$

$$I_D = 37.37, 6.724\text{ mA}$$

$$I_{DQ} = 6.724\text{ mA} \quad (\text{As } V_{GS} > V_T \text{ is satisfied})$$

$$V_{GSQ} = 18 - 0.82 I_D = 12.486\text{ V}$$

$$V_{DS} = 40 - (3 + 0.82) \times 6.724 = 14.314\text{ V}$$

18


Write  
answer  
in detail







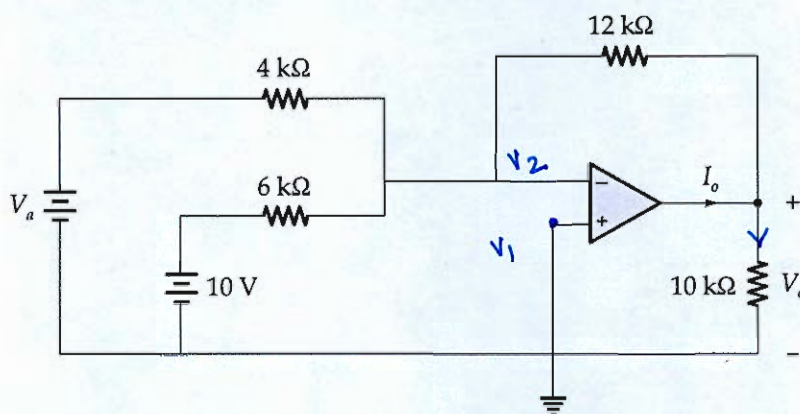Q.4 (c) For the circuit shown below, the op-amp is considered to be ideal.



- (i) For an input voltage  $V_a = 4$  V, find the output voltage  $V_o$  and current  $I_o$ .  
 (ii) Determine the range of input voltage  $V_a$  for linear operation if the saturation voltage of op-amp is  $\pm 12$  V.

[20 marks]

$$V_1 = V_2 = 0 \quad (\text{By virtual short})$$

KCL at  $V_2$

$$\Rightarrow \frac{V_2 - 4}{4} + \frac{V_2 - 10}{6} + \frac{V_2 - V_o}{12} = 0$$

$$\text{As } V_2 = 0 \Rightarrow \boxed{V_o = -32 \text{ V}}$$

$$I_o + \frac{0 - (-32)}{12} = \frac{-32}{10}$$

$$\Rightarrow I_o = -5.867 \text{ mA}$$

ii) KCL at  $v_2$

$$\frac{0 - v_a}{4} + \frac{0 - 10}{6} + \frac{0 - v_o}{12} = 0$$

$$\Rightarrow v_a = -4 \left( \frac{v_o}{12} + 10/6 \right) = -\frac{v_o}{3} - \frac{20}{3}$$

for  $v_o = +V_{sat} = 12$

$$v_{a1} = -10.67 \text{ V}$$

for  $v_o = -V_{sat} = -12$

$$v_{a2} = -2.667 \text{ V}$$


Range for  $v_a$  , linear operation  
 $-10.67 < v_a < -2.667 \text{ V}$

18



## Section B : Electrical Machine-1 + Power Systems-2

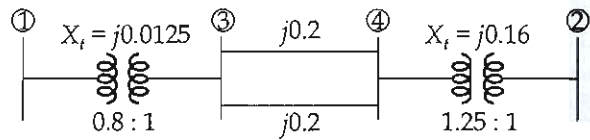- Q.5 (a) The single line diagram of a 4-bus power system is shown in figure. Reactances are given in per unit on a common MVA base. The transformer  $T_1$  and  $T_2$  have tap settings of 0.8 : 1 and 1.25 : 1 respectively. Obtain the bus admittance matrix of the system.




[12 marks]





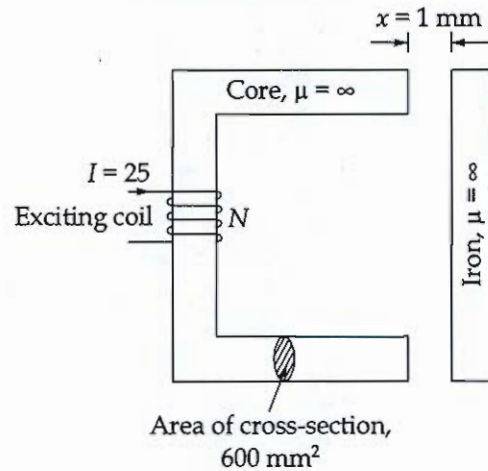- Q.5 (b) An electromagnet, shown in figure, is required to exert a 500 N force on the iron at an airgap of 1 mm, while the exciting coil is carrying 25 A dc. The cross-section at the air gap is 600 mm<sup>2</sup> in area. Calculate the required number of turns in the exciting coil.



[12 marks]

$$R = \frac{2x}{\mu A}$$

$$\phi = \frac{NI}{R}$$

$$E = \frac{1}{2} \phi^2 R$$

$$F = -\frac{1}{2} \phi^2 \frac{dR}{dx}$$

$$= -\frac{1}{2} \times \frac{N^2 i^2}{4x^2} \times 4x^2 \times \frac{2}{\mu A} = -\frac{1}{4} \frac{N^2 i^2}{x^2} \mu A$$

$$F = 500 \text{ N}$$

$$\Rightarrow \frac{1}{4} \times \frac{N^2 \times (25)^2}{(10^{-3})^2} \times 4\pi \times 10^{-7} \times 600 \times 10^{-6} = 500$$

$$N = 65.147$$

$$\boxed{N \sim 66}$$

11



- Q.5 (c) A 3- $\phi$ , squirrel cage induction motor is designed to restrict the maximum starting line current drawn from 400 V, 3- $\phi$  supply to 120 A. If starting current of motor is six times the full load current. What is the maximum permissible full KVA rating of motor when
- it is directly connected to the supply mains?
  - it is connected through an auto-transformer with a tapping of 60%?
  - it is designed for the use with star-delta starter?

[12 marks]

$$(i) I_{st} = 6 I_{fl} = 6 \text{ pu}$$

$$I_{st} = 120 \text{ A}$$

$$\Rightarrow I_{fl} = 120/6 = 20 \text{ A}$$

$$\text{Maximum kVA} = \sqrt{3} \times 400 \times 20 = 13.856 \text{ kVA}$$

$$(ii) \text{ for } x = 0.6$$

$$\text{for } I_L = 120 \text{ A}$$

$$\text{Motor line current (Max)} = \frac{120}{0.6} = 200 \text{ A} \quad I_{fl} = \frac{200}{6}$$

$$\text{rating} = \sqrt{3} \times 400 \times \frac{200}{6} = \frac{138.56}{6} \text{ kVA} = 23.093 \text{ kVA}$$

$$(iii) x = 1/\sqrt{3}$$

$$\text{Motor line current max} = 120\sqrt{3} \quad I_{fl} = 34.641$$

$$\text{rating} = \sqrt{3} \times 400 \times 34.641 = 24 \text{ kVA}$$

Incomplete  
solution





Q.5 (d)

A 230 V, 20 hp, 60 Hz, 6 pole, 3- $\phi$  induction motor driving a constant torque load of rated frequency, rated voltage and rated hp, has a speed of 1175 rpm and an efficiency of 92.10%. Determine the new operating speed if a system disturbance causes 10% drop in voltage and 6% drop in frequency. Assuming the friction, windage and stray power loss remain constant.

[12 marks]

$$N_1 = 1175 \text{ rpm} \quad \eta_1 = 92.10\%$$

$$N_s = \frac{120 \times 60}{6} = 1200 \text{ rpm}$$

$$s_1 = \frac{1200 - 1175}{1200} = 0.020833$$

$$T = \frac{3}{\omega_s} \frac{V^2}{(R_2/s)^2 + X_2^2} \times R_2/s \quad (\text{as low slip})$$

$$\text{for } \frac{R_2}{s} \gg X_2 \Rightarrow T \propto \frac{V^2}{R_2 f} = \text{const.}$$

$$\text{for } V_2 = 0.9 V_1 \quad \downarrow \quad f_2 = 0.94 f_1$$

$$\Rightarrow \frac{0.020833 \times V_1^2}{R_2 \times f_1} = \frac{s_2 \times (0.9 V_1)^2}{0.94 f_1 \times R_2}$$

$$\Rightarrow s_2 = 0.02417$$

$$N_2 = 1170.987 \text{ rpm}$$

2






Q.5 (e) Consider the  $Y_{bus}$  of a 4-bus power system,

$$Y_{bus} = \begin{bmatrix} -6 & 2 & 2.5 & 0 \\ 2 & -10 & 2.5 & 4 \\ 2.5 & 2.5 & -9 & 4 \\ 0 & 4 & 4 & -8 \end{bmatrix}$$

where first, second, third and fourth row refers to bus 1, 2, 3 and 4 respectively and all the given entries in matrix are in per unit. Draw the reactance diagram of given power system.

[12 marks]

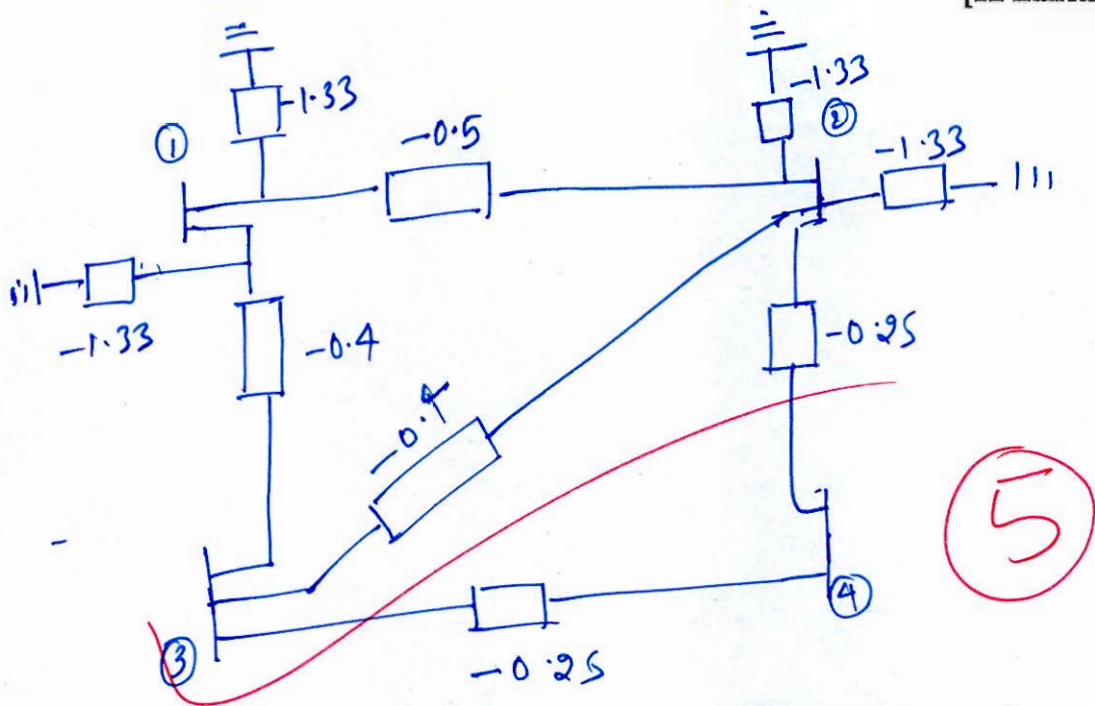


Sum of Row gives Admittance to ground on bus.

Do not write  
answer directly



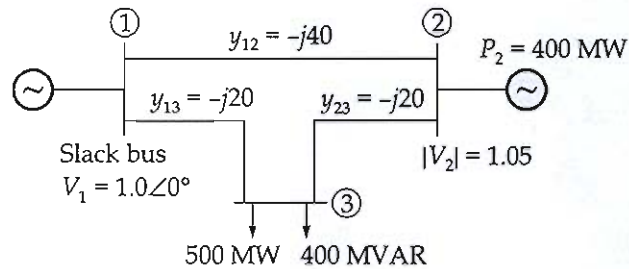Q.6 (a)

The figure shows the single line diagram of a simple three-bus power system with generation at bus-(1) and bus-(2). The voltage at bus-(1) is  $V = 1.0 \angle 0^\circ$  pu. The voltage magnitude at bus-(2) is fixed at 1.05 pu with real power generation of 400 MW. A load consisting of 500 MW and 400 MVAR is taken from bus-(3). Line admittances are marked in per unit on a 100 MVA base. The line resistances and line charging susceptances are neglected.



Using Newton-Raphson method, start with the initial guess of  $V_2^{(0)} = 1.05 + j0$  and  $V_3^{(0)} = 1.0 + j0$  and keeping  $|V_2| = 1.05$  pu, determine the phasor values of  $V_2$  and  $V_3$  after one iteration.

[20 marks]







Q.6 (b) (i) The fuel inputs for two plants are given as :

$$F_1 = 0.005P_1^2 + 2P_1 + 10 \text{ Rs/hr}$$

$$F_2 = 0.005P_2^2 + 0.75P_2 + 15 \text{ Rs/hr}$$

The loss coefficients are  $B_{11} = 0.0015$ ,  $B_{22} = 0.0025$  and  $B_{12} = -0.0005$ . The cost of power received by each plant is 2.6 Rs/MWhr, then calculate the generating schedule and the load received by the system.

(ii) A generating station having a capacity of 200 MW and it is supplying  $600 \times 10^6$  units in a year, the load factor of the unit is 0.60. Find plant utilization factor, plant capacity factor and reserve capacity of the plant.

[14 + 6 marks]





Q.6 (c) The following test data were taken as a 7.5 hp, 4-pole, 208 V, 60 Hz, Y-connected induction motor having a rated current of 28 A.

DC test :  $V_{dc} = 9.07 \text{ V}, I_{dc} = 28.0 \text{ A}$

No-load test :  $V_t = 208 \text{ V}; f = 60 \text{ Hz}; P_{in} = 420 \text{ W}$

$I_a = 8.12 \text{ A}; I_b = 8.20 \text{ A}$  and  $I_c = 8.18 \text{ A}$

Blocked rotor test :

$V_t = 25 \text{ V}, f = 15 \text{ Hz}, P_{in} = 920 \text{ W}$

$I_a = 28.1 \text{ A}, I_b = 28.0 \text{ A}, I_c = 27.6 \text{ A}$

(i) Draw the equivalent circuit of motor and find its parameters. Assume the stator and rotor are equal reactances.

(ii) Find the slip at the pull-out torque and find the value of the pull-out torque.

(Consider AC resistance to be 1.5 times of DC resistance)

[20 marks]












- Q.7 (a) A single machine is connected to a load centre through a transmission line as shown in figure. The load centre is represented by a reactance connected to an infinite bus. The generator is initially operating with  $P_e = 1.0$  pu and the magnitudes of voltages  $V_1$  and  $V_2$  are 1.0 pu. Assume  $X_g = 0.3$  pu,  $X_t = 0.1$  pu,  $X = 0.4$  pu and  $X_2 = 0.1$  pu.

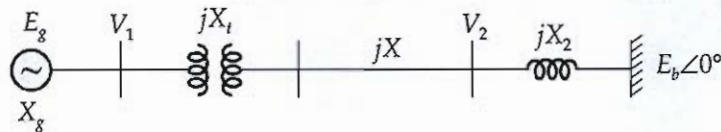
- (i) Find the maximum step increase in mechanical power that will not cause transient instability.
- (ii) Find the critical clearing angle and time for a three phase fault at the generator terminal. Generator is initially supplying power of 1.0 pu. Assume that post-fault system is identical to the prefault system. ( $H = 4.0$  sec,  $f_b = 50$  Hz).



[10 + 10 marks]

$$P_e = 1 \text{ pu}$$
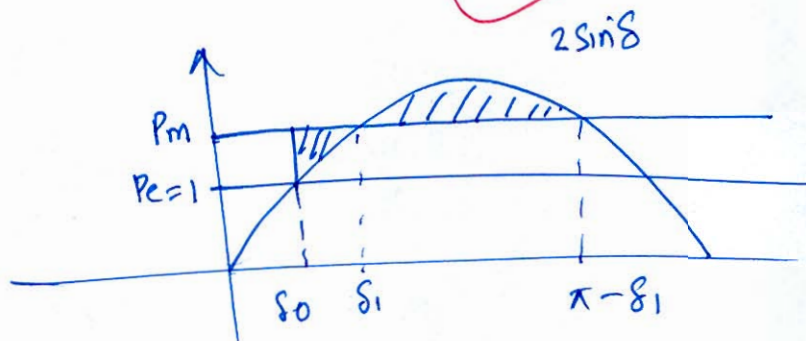
$$P = \frac{V_1 V_2}{X_t + X} \sin \delta = \frac{1}{0.5} \sin \delta = 2 \sin \delta$$



$$\delta_0 = \sin^{-1}(1/2) = \pi/6$$

Let mechanical

power increase to  $P_m$ .

⇒ equal area criteria

$$\int_{\delta_0}^{\delta_1} (P_m - 2 \sin \delta) d\delta = \int_{\delta_1}^{\pi - \delta_1} (2 \sin \delta - P_m) d\delta$$

$$\Rightarrow P_m(\delta_1 - \delta_0) - 2(\cos \delta_0 - \cos \delta_1) = 2(2 \cos \delta_1) - P_m(\pi - 2\delta_1)$$

$$P_m(\delta_1 - \delta_0 + \pi - 2\delta_1) = 2 \cos \delta_0 + 2 \cos \delta_1$$


$$\delta_1 = \sin^{-1}\left(\frac{P_m}{2}\right)$$

4

Solving

$$\delta P_m = 1.739 \text{ pu}$$

$$\text{maximum increase} = 1.739 - 1 = 0.739 \text{ pu}$$

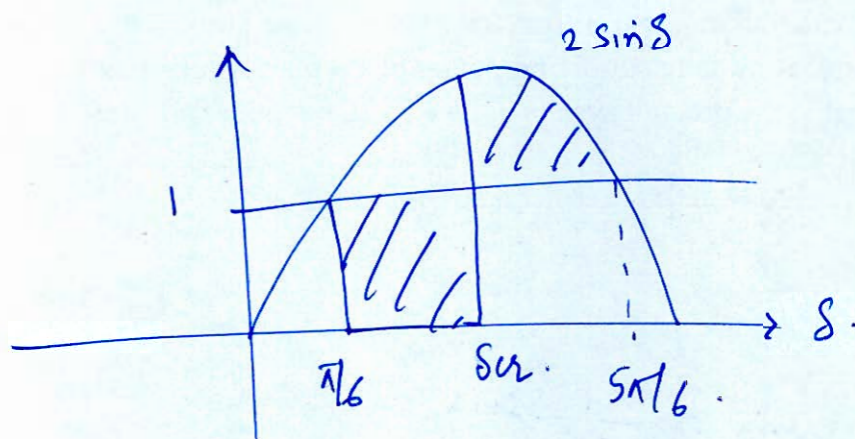ii)

By equal area criteria for stability.

$$1 \times (\delta_u - \pi/6) = \int_{\delta_u}^{5\pi/6} (2 \sin \delta - 1) d\delta$$

$$\Rightarrow \delta_u - \pi/6 = 2 (\cos \delta_u + 0.866) - (5\pi/6 - \delta_u)$$

$$\frac{4\pi}{6} = 2 (\cos \delta_u + 0.866)$$

$$\boxed{\delta_u = 79.56^\circ}$$

$$\therefore M = H \omega_f = \frac{4}{50\pi}$$

$$\Rightarrow M \frac{d^2 \delta}{dt^2} = 1$$

$$\Rightarrow \frac{d^2 \delta}{dt^2} = \frac{50\pi}{4} \text{ rad/s}^2$$



$$\frac{1}{2} \left( \frac{50\pi}{4} \right) t^2 = (79.56 - 30) \times \frac{100\pi}{180}$$

$$\Rightarrow \boxed{t = 0.2098 \text{ s.}}$$



- Q.7 (b) (i) An 11500/2300 V transformer is rated at 100 kVA as a 2-winding transformer. If the windings are connected in series to form an auto-transformer, what will be the possible voltage ratios and output? Also calculate the power transferred through conduction and induction and percentage saving in conductor material.


- (ii) Write any four applications of auto-transformers.

[16 + 4 marks]

$$I_{F1} = \frac{100 \times 10^3}{11500} = 8.695 \text{ A}$$

$$I_{F2} = \frac{100 \times 10^3}{2300} = 43.478 \text{ A}$$

Possible connections

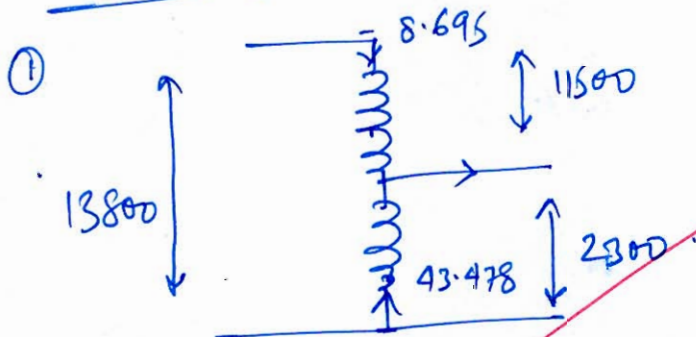

$$\text{kVA} = 13800 \times 8.695 = 120 \text{ kVA}$$

$$\frac{N_2}{N_1} = \frac{2300}{13800} = 0.167$$


$$\% \text{ Saving} = (1 - \frac{N_2}{N_1}) \times 100 = 83.3\%$$

(Induction)  $P_{\text{transformed}} = 11500 \times 8.695 = 100 \text{ kVA}$

②  $P_{\text{in}} = 120 \text{ kVA}$

$P_{\text{cond}} = 20 \text{ kVA}$

②

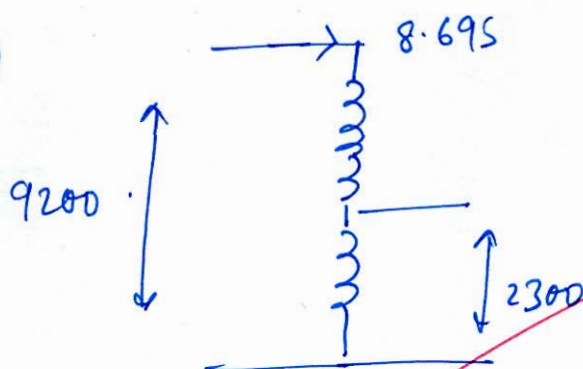

(Subtractive connection.)

$$\text{kVA} = 9200 \times 8.695 = 80 \text{ kVA}$$

$$\frac{N_2}{N_1} = \frac{2300}{9200} = 0.25$$


$$\% \text{ S} = (1 - 0.25) \times 100 = 75\%$$

$P_{\text{induction}} = 11500 \times 8.695 = 100 \text{ kVA}$

$P_{\text{cond}} = 80 - 100 = -20 \text{ kVA}$



③ (Additive)

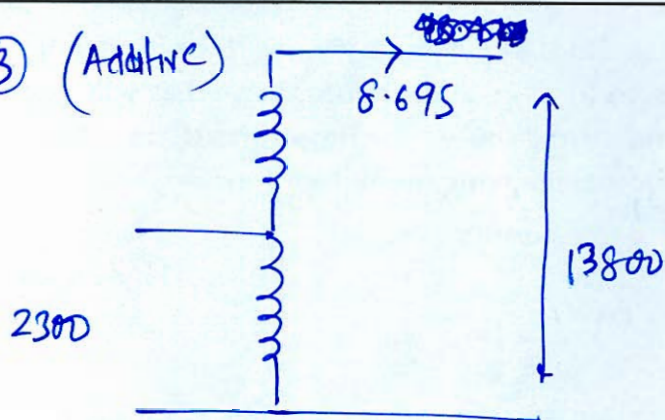

$$\text{kVA} = 13800 \times 8.695$$

$$= 120 \text{ kVA}$$

$$\frac{N_1}{N_2} = \frac{2300}{13800}$$

$$= 0.167 \quad (9 < 1)$$

$$\gamma.s = (1 - 0.167) \times 100$$


$$= 83.33\%$$

$$P_{\text{induction}} = 11500 \times 8.695$$

$$= 100 \text{ kVA}$$

$$P_{\text{cond.}} = 120 - 100 = 20 \text{ kVA}$$

④ (Opposing)

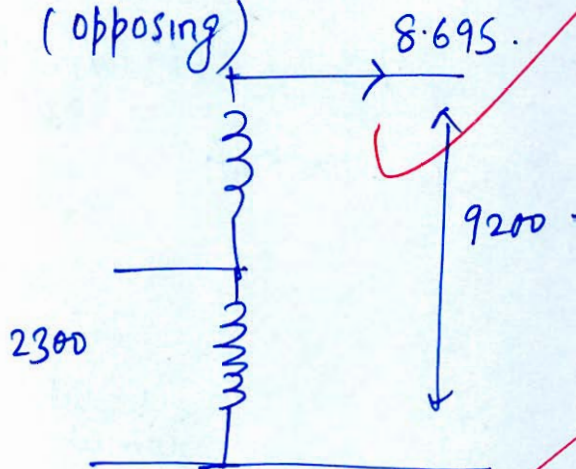

$$\text{kVA} = 9200 \times 8.695$$

$$= 80 \text{ kVA}$$

$$\frac{N_1}{N_2} = \frac{1}{4}$$

$$\gamma.s = (1 - 1/4) \times 100$$

$$= 75\%$$

$$P_{\text{ind}} = 11500 \times 8.695$$

$$= 100 \text{ kVA}$$

$$P_{\text{cond.}} = -20 \text{ kVA}$$

15

ii. Auto transformer uses

- ① used in Induction motor starting to provide low starting current & good torque
- ② used in to save material & space for an equivalent transformer
- ③ used in welding works, to provide high current
- ④ used for smooth variation of voltages with movable tapping.

4



- Q.7 (c) (i) For a 3- $\phi$ , induction motor, maximum torque is twice the full load torque and starting torque is 1.6 times the full load torque. In order to get a full load slip of 5%, determine the percentage reduction in rotor resistance. Neglect the stator impedance.
- (ii) Two generating units rated 300 MW and 400 MW have governor speed regulation of 6% and 4% respectively from no load to full load. Both the generating units are operating in parallel to share a load of 600 MW. Assuming free governor action, determine the load shared by both units and frequency of operation. (Assume no-load frequency to be 50 Hz).

[10 + 10 marks]

(i)  $T_{\max} = 2 T_{fl}$   $s_{fl} = 0.05$

"  $T_{st} = 1.6 T_{fl}$

$$\frac{T_{fl}}{T_{\max}} = \frac{1}{2} \quad \frac{T_{st}}{T_{\max}} = \frac{1.6}{2} \quad - (1)$$

using  $\frac{T}{T_{\max}} = \frac{2}{\frac{s}{s_{\max}} + \frac{s_{\max}}{s}}$

$$\Rightarrow \frac{1}{2} = \frac{2}{\frac{s_{\max}}{0.05} + \frac{0.05}{s_{\max}}}$$

from (1)

$$\Rightarrow \frac{1.6}{2} = \frac{2}{s_{\max 1} + \frac{1}{s_{\max 1}}}$$

$$s_{\max 1} = 0.5$$

$$\Rightarrow \frac{R_2}{X_2} = 0.5 \quad \Rightarrow R_2 = 0.5 X_2$$

When  $s_{fl} = 0.05$ , let  $s_{\max 2}$  (with new resistance  $R_2'$ )

$$\Rightarrow \frac{T_{fl}}{T_{\max}} = \frac{1}{2} = \frac{2}{\frac{0.05}{s_{\max 2}} + \frac{s_{\max 2}}{0.05}}$$

$$\Rightarrow \frac{20 s_{\max 2} + 1}{20 s_{\max 2}} = 4$$

$$\Rightarrow s_{\max 2} = 0.1866, 0.0134$$

$$\frac{\lambda_2'}{x_2} = 0.1866$$

$$\lambda_2' = 0.1866 x_2$$

$$\% \text{ reduction} = \frac{\lambda_2 - \lambda_2'}{\lambda_2} \times 100 = \frac{0.5 - 0.1866}{0.5} \times 100 = 62.68\%$$

$$(i) R_1 = \frac{0.6}{100} \times 50 = 0.01 \text{ Hz/MW}$$

$$R_2 = \frac{4}{100} \times 50 = 0.005 \text{ Hz/MW}$$

$$\text{Let } P_{\text{base}} = 600 \text{ MW} \Rightarrow R_1, R_2$$

$$R_1 = 0.12 \text{ pu}$$

$$R_2 = 0.06 \text{ pu}$$

$$P_L = 1 \text{ pu}$$

$$\frac{\Delta f}{f_r} = \frac{-P_L}{\frac{P}{R_1} + \frac{1}{R_2}} = \frac{-1}{\frac{1}{0.12} + \frac{1}{0.06}} = -0.04 \text{ pu}$$

$$\Delta f = -2 \text{ Hz} \Rightarrow \text{operation freq} = 50 - 2 = 48 \text{ Hz}$$

$$P_1 = \frac{-\Delta f (P)}{R_1} = \frac{0.04}{0.12} \text{ pu} = 0.333 \text{ pu} = 200 \text{ MW}$$

$$P_2 = \frac{-\Delta f}{R_2} = \frac{0.04}{0.06} = 0.667 = 400 \text{ MW}$$

18  
Good  
Approach





- Q.8 (a) A 600 kVA, 1- $\phi$  transformer with 0.012 pu resistance and 0.06 pu reactance is connected in parallel with a 300 kVA transformer with 0.014 pu resistance and 0.045 pu reactance to share a load of 800 kVA at 0.8 pf lagging. Find the load shared by each transformer when :
- (i) both the secondary voltages are 440 V.
  - (ii) the open circuit voltages are respectively 445 V and 455 V. (Also comment on the results).

[20 marks]







Q.8 (b)

(i) Explain the advantages of HVDC power transmission in detail.

(ii) A d.c. link has a loop resistance of  $10\ \Omega$  and is connected to transformer giving secondary voltage of 120 kV at each end.

The bridge connected converters operates as follows :

Rectifier :  $\alpha = 15^\circ$ ,  $X = 15\ \Omega$

Inverter :  $\delta_o = 10^\circ$ ,  $\gamma = 15^\circ$ ,  $X = 15\ \Omega$ . Allow  $5^\circ$  margin on  $\delta_o$  for  $\delta$ .


Calculate the direct current delivered if inverter operates on constant  $\beta$  control.

[14 + 6 marks]





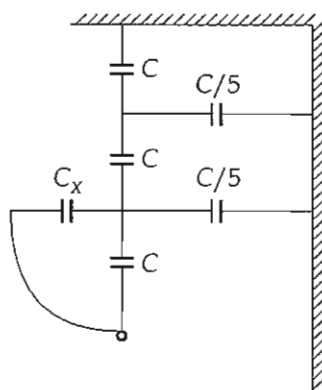- Q.8 (c) (i) A 250 MVA, 60 Hz, two-pole synchronous generator with inertia constant  $H$  of 5.4 MJ/MVA. Assume the machine is running steadily at synchronous speed with a shaft input of 331, 100 hp. The electrical power developed suddenly changes from its normal value to a value of 200 MW. Determine the acceleration or deceleration of rotor. If acceleration computed for the generator is constant for a period of 9 cycles, determine the change in the power angle in that period, frequency of system and speed of generator at the end of 9 cycles.
- (ii) In a transmission line each conductor is at 20 kV and supported by a string of 3 suspension insulators. The air capacitance between each cap-pin junction and tower is one fifth of the capacitance  $C$  of each insulation unit. A guard ring, effective only over the line-end insulator unit is fitted so that the voltages on two units nearest to line-end are equal.



Calculate the voltage on line-end unit and the value of capacitance  $C_x$ .

[10 + 10 marks]







## Space for Rough Work

---

## Space for Rough Work

---

## Space for Rough Work


---


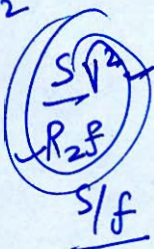
## Space for Rough Work

---

$$T = \frac{1}{\omega} \frac{V_{TM}}{R_2^2 + X_2^2} \times \frac{R_2}{S}$$



$$\propto \frac{SV^2}{R_2 f}$$