

# **GATE**

## **Electronics Engineering**

---

**(Previous Years Solved Papers 1987-1995)**

### **Contents**

1.	Network Theory .....	2
2.	Electromagnetics .....	13
3.	Control Systems .....	24
4.	Electronic Devices and Circuits .....	37
5.	Analog Circuits .....	48
6.	Digital Circuits and Computer Organization .....	62
7.	Signals and Systems .....	72
8.	Communication Systems .....	82
9.	Engineering Mathematics .....	93



# Network Theory


## UNIT I

### CONTENTS

1. Basics of Network Analysis **3**
2. Sinusoidal Steady State **4**
3. Network Theorems **5**
4. Transient Analysis **6**
5. Two Port Networks **6**
6. Graph Theory and State Equations **7**
7. Network Functions **7**


## 1. Basics of Network Analysis

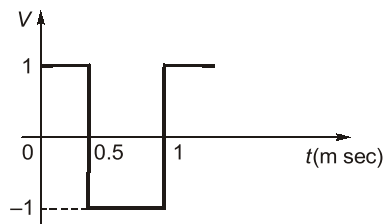- 1.1 A square waveform as shown in figure is applied across 1 mH ideal inductor. The current through the inductor is a ..... wave of ..... peak amplitude.



[1987 : 2 Marks]

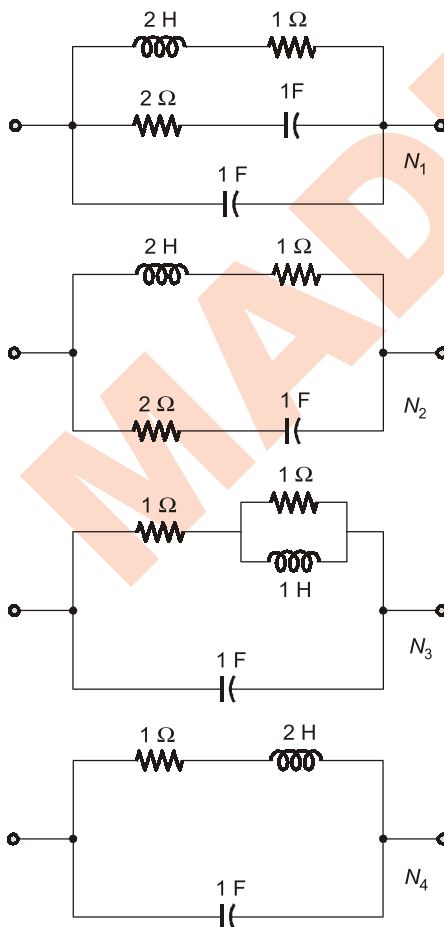- 1.2 Of the networks,  $N_1$ ,  $N_2$ ,  $N_3$  and  $N_4$  of figure, the networks having identical driving point function are




- (a)  $N_1$  and  $N_2$  (b)  $N_2$  and  $N_4$   
(c)  $N_1$  and  $N_3$  (d)  $N_1$  and  $N_4$

[1992 : 2 Marks]

- 1.3 A network contains linear resistors and ideal voltage sources. If values of all the resistors are doubled, then the voltage across each resistor is  
(a) halved  
(b) doubled  
(c) increased by four times  
(d) not changed

[1993 : 2 Marks]

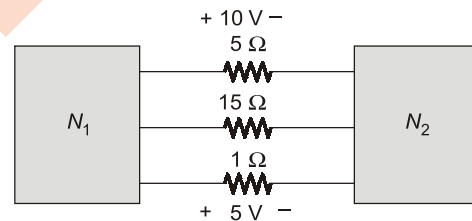- 1.4 The two electrical subnetworks  $N_1$  and  $N_2$  are connected through three resistors as shown in Fig. The voltages across 5 ohm resistor and 1 ohm resistor are given to be 10 V and 5 V, respectively. Then voltage across 15 ohm resistor is




- (a) -105 V (b) +105 V  
(c) -15 V (d) +15 V

[1993 : 2 Marks]

- 1.5 A dc circuit shown in figure has a voltage source  $V$ , a current source  $I$  and several resistors. A particular resistor  $R$  dissipates a power of 4 Watts when  $V$  alone is active. The same resistor  $R$  dissipates a power of 9 Watts when  $I$  alone is active. The power dissipated by  $R$  when both sources are active will be

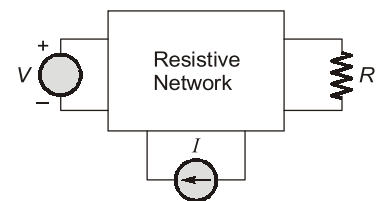- (a) 1 W  
(b) 5 W  
(c) 13 W  
(d) 25 W



[1993 : 1 Mark]


- 1.6 Two 2 H inductance coils are connected in series and are also magnetically coupled to each other the coefficient of coupling being 0.1. The total inductance of the combination can be

(a) 0.4 H (b) 3.2 H  
(c) 4.0 H (d) 4.4 H

[1995 : 1 M]

## 2. Sinusoidal Steady State

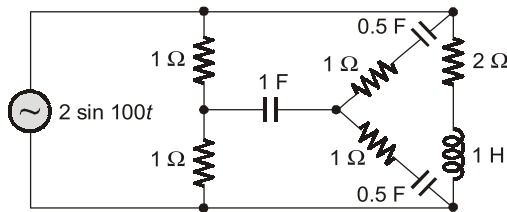
- 2.1 The value of current through the 1 Farad capacitor of figure is



(a) zero (b) one  
(c) two (d) three

[1987 : 2 Marks]

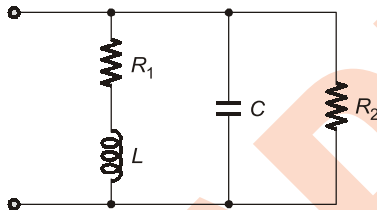
- 2.2 The half – power bandwidth of the resonant circuit of figure can be increased by:



(a) increasing  $R_1$  (b) decreasing  $R_1$   
(c) increasing  $R_2$  (d) decreasing  $R_2$

[1989 : 2 Marks]

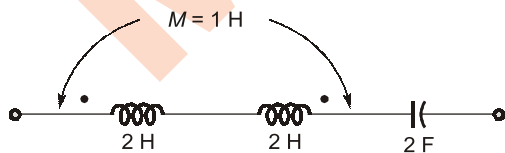- 2.3 The resonant frequency of the series circuit shown in figure is



(a)  $\frac{1}{4\pi\sqrt{3}}$  Hz (b)  $\frac{1}{4\pi}$  Hz  
(c)  $\frac{1}{2\pi\sqrt{10}}$  Hz (d)  $\frac{1}{4\pi\sqrt{2}}$  Hz

[1990 : 2 Marks]

- 2.4 In a series RLC high  $Q$  circuit, the current peaks at a frequency

(a) equal to the resonant frequency  
(b) greater than the resonant frequency  
(c) less than the resonant frequency  
(d) none of the above is true

[1991 : 2 Marks]

- 2.5 For the series  $R$ - $L$ - $C$  circuit of fig. 1, the partial phasor diagram at a certain frequency is shown in fig. 2. The operating frequency of the circuit is

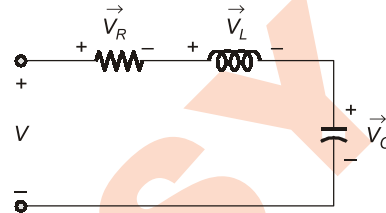


Figure-1


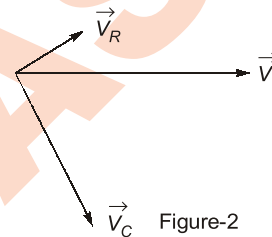


Figure-2

(a) equal to the resonance frequency  
(b) less than the resonance frequency  
(c) greater than the resonance frequency  
(d) not zero

[1992 : 2 Marks]

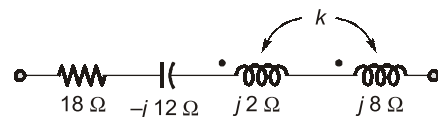
- 2.6 In the series circuit shown in figure, for series resonance, the value of the coupling coefficient  $k$  will be



(a) 0.25 (b) 0.5  
(c) 0.999 (d) 1.0

[1993 : 1 Mark]

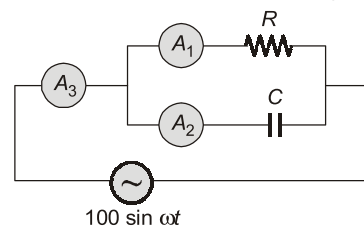- 2.7 In figure,  $A_1$ ,  $A_2$  and  $A_3$  are ideal ammeters. If  $A_1$  reads 5 A,  $A_2$  reads 12 A, then  $A_3$  should read



(a) 7 A (b) 12 A  
(c) 13 A (d) 17 A

[1993 : 2 Marks]



2.8 A series LCR circuit consisting of  $R = 10 \Omega$ ,  $|X_L| = 20 \Omega$  and  $|X_C| = 20 \Omega$  is connected across an a.c. supply of 200 V rms. The rms voltage across the capacitor is

- (a)  $200 \angle -90^\circ \text{ V}$  (b)  $200 \angle +90^\circ \text{ V}$   
(c)  $400 \angle +90^\circ \text{ V}$  (d)  $400 \angle -90^\circ \text{ V}$

[1994 : 1 Mark]

2.9 A DC voltage source is connected across a series  $R$ - $L$ - $C$  circuit. Under steady-state conditions, the applied DC voltage drops entirely across the

- (a)  $R$  only (b)  $L$  only  
(c)  $C$  only (d)  $R$  and  $L$  combination

[1995 : 1 M]

2.10 Consider a DC voltage source connected to a series  $R$ - $C$  circuit. When the steady-state reaches, the ratio of the energy stored in the capacitor to the total energy supplied by the voltage source, is equal to

- (a) 0.362 (b) 0.500  
(c) 0.632 (d) 1.000 [1995 : 1 M]

2.11 The current,  $i(t)$ , through a  $10\text{-}\Omega$  resistor in series with an inductance, is given by

$$i(t) = 3 + 4 \sin(100t + 45^\circ) + 4 \sin(300t + 60^\circ) \text{ Amperes.}$$

The RMS value of the current and the power dissipated in the circuit are:

- (a)  $\sqrt{41} \text{ A}$ , 410 W, respectively  
(b)  $\sqrt{35} \text{ A}$ , 350 W, respectively  
(c) 5 A, 250 W, respectively  
(d) 11 A, 1210 W, respectively [1995 : 1 M]

2.12 A series  $R$ - $L$ - $C$  circuit has a  $Q$  of 100 and an impedance of  $(100 + j0) \Omega$  at its resonant angular frequency of  $10^7$  radians/sec. The values of  $R$  and  $L$  are:

$R = \text{___ ohms}$ .  $L = \text{___ mH}$ . [1995 : 1 M]

2.13 The rms value of a rectangular wave of period  $T$ , having a value of  $+V$  for a duration,  $T_1$  ( $< T$ ) and  $-V$  for the duration,  $T - T_1 = T_2$ , equals


- (a)  $V$  (b)  $\frac{T_1 - T_2}{T} V$   
(c)  $\frac{V}{\sqrt{2}}$  (d)  $\frac{T_1}{T_2} V$  [1995 : 1 M]

### 3. Network Theorems

3.1 If an impedance  $Z_L$  is connected across a voltage source  $V$  with source impedance  $Z_S$ , then for maximum power transfer the load impedance must be equal to

- (a) source impedance  $Z_S$   
(b) complex conjugate of  $Z_S$   
(c) real part of  $Z_S$   
(d) imaginary part of  $Z_S$  [1988 : 2 Marks]

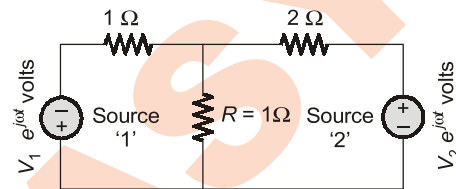3.2 In the circuit of figure, the power dissipated in the resistor  $R$  is 1 W when only source '1' is present and '2' is replaced by a short. The power dissipated in the same resistor  $R$  is 4 W when only source '2' is present and '1' is replaced by a short. When both the sources '1' and '2' are present, the power dissipated in  $R$  will be :



- (a) 1 W (b) 3 W  
(c) 4 W (d) 5 W


[1989 : 2 Marks]

3.3 A load,  $Z_L = R_L + jX_L$  is to be matched, using an ideal transformer, to a generator of internal impedance,  $Z_S = R_S + jX_S$ . The turns ratio of the transformer required is

- (a)  $\sqrt{|Z_L / Z_S|}$  (b)  $\sqrt{|R_L / R_S|}$   
(c)  $\sqrt{|R_L / Z_S|}$  (d)  $\sqrt{|Z_L / R_S|}$


[1989 : 2 Marks]

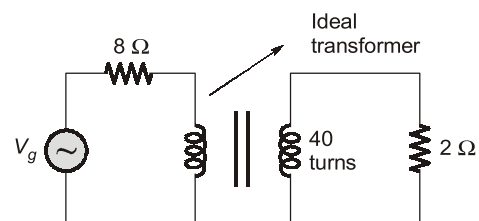3.4 If the secondary winding of the ideal transformer shown in the circuit of figure has 40 turns, the number of turns in the primary winding for maximum power transfer to the  $2 \Omega$  resistor will be



- (a) 20 (b) 40  
(c) 80 (d) 160 [1993 : 1 Mark]

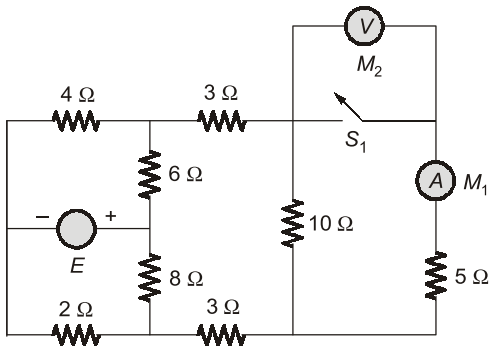3.5 In the circuit of figure, when switch  $S_1$  is closed, the ideal ammeter  $M_1$  reads 5 A. What will the ideal voltmeter  $M_2$  read when  $S_1$  is kept open? (The value of  $E$  is not specified).




[1993 : 2 Marks]

- 3.6 A generator of internal impedance,  $Z_G$ , delivers maximum power to a load impedance,  $Z_L$ , only if  $Z_L = \dots\dots\dots$

[1994 : 1 Mark]

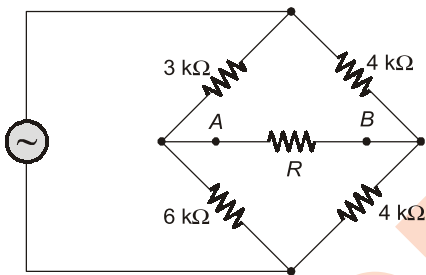- 3.7 The value of the resistance,  $R$ , connected across the terminals,  $A$  and  $B$ , (ref. Fig.), which will absorb the maximum power, is



- (a) 4.00 kΩ (b) 4.11 kΩ  
(c) 8.00 kΩ (d) 9.00 kΩ [1995 : 1 M]

#### 4. Transient Analysis

- 4.1 A  $10\ \Omega$  resistor, a 1 H inductor and  $1\ \mu\text{F}$  capacitor are connected in parallel. The combination is driven by a unit step current. Under the steady state condition, the source current flows through :  
(a) the resistor  
(b) the inductor  
(c) the capacitor only  
(d) all the three elements [1989 : 2 Marks]

- 4.2 If the Laplace transform of the voltage across a capacitor of value of  $\frac{1}{2}\text{F}$  is


$$V_C(s) = \frac{s+1}{s^3 + s^2 + s + 1},$$

the value of the current through the capacitor at  $t = 0^+$  is

- (a) 0 A (b) 2 A  
(c)  $(1/2)\text{ A}$  (d) 1 A

[1989 : 2 Marks]

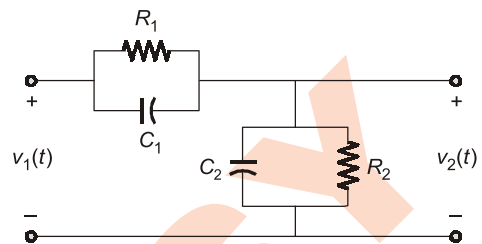- 4.3 For the compensated attenuator of figure, the impulse response under the condition  $R_1 C_1 = R_2 C_2$  is



- (a)  $\frac{R_2}{R_1 + R_2} [1 - e^{-\frac{t}{R_1 C_1}}] u(t)$   
(b)  $\frac{R_2}{R_1 + R_2} \delta(t)$   
(c)  $\frac{R_2}{R_1 + R_2} u(t)$   
(d)  $\frac{R_2}{R_1 + R_2} e^{-\frac{t}{R_1 C_1}} u(t)$

[1992 : 2 Marks]

- 4.4 A ramp voltage,  $v(t) = 100t$  Volts, is applied to an RC differentiating circuit with  $R = 5\text{ k}\Omega$  and  $C = 4\ \mu\text{F}$ . The maximum output voltage is

- (a) 0.2 volt (b) 2.0 volts  
(c) 10.0 volts (d) 50.0 volts

[1994 : 1 Mark]

- 4.5 The RMS value of a rectangular wave of period  $T$ , having a value of  $+V$  for a duration,  $T_1$  ( $< T$ ) and  $-V$  for the duration,  $T - T_1 = T_2$  equals

- (a)  $V$  (b)  $\frac{T_1 - T_2}{T} V$   
(c)  $\frac{V}{\sqrt{2}}$  (d)  $\frac{T_1}{T_2} V$  [1995 : 1 M]

#### 5. Two Port Networks

- 5.1 Two two-port networks are connected in parallel. The combination is to be represented as a single two-port network. The parameters of this network are obtained by addition of the individual

- (a)  $z$  parameters (b)  $h$  parameters  
(c)  $y$  parameters (d) ABCD parameters

[1988 : 2 Marks]

5.2 For the transfer function of a physical two-port network:

- (a) all the zeros must lie only in the left half of the  $s$ -plane
- (b) the poles may lie anywhere in the  $s$ -plane
- (c) the poles lying on the imaginary axis must be simple
- (d) a pole may lie at origin


[1989 : 2 Marks]

5.3 The condition  $AD - BC = 1$  for a two-port network implies that the network is a:

- (a) reciprocal network
- (b) lumped element network
- (c) lossless network
- (d) unilateral element network

[1989 : 2 Marks]

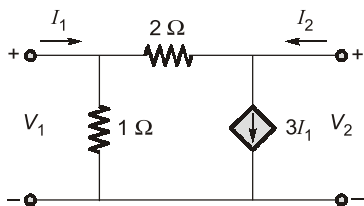5.4 The open circuit impedance matrix of the two port network shown in figure is



- (a)  $\begin{bmatrix} -2 & 1 \\ -8 & 3 \end{bmatrix}$
- (b)  $\begin{bmatrix} -2 & -8 \\ -8 & 3 \end{bmatrix}$
- (c)  $\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$
- (d)  $\begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix}$

[1990 : 2 Marks]

5.5 Two Two-port networks are connected in cascade. The combination is to be represented as a single two-port network. The parameters of the network are obtained by multiplying the individual

- (a)  $z$ -parameter matrices
- (b)  $h$ -parameter matrices
- (c)  $y$ -parameter matrices
- (d) ABCD parameter matrices

[1991 : 2 Marks]

5.6 For a 2-port network to be reciprocal,

- (a)  $z_{11} = z_{22}$
- (b)  $y_{21} = y_{12}$
- (c)  $h_{21} = -h_{12}$
- (d)  $AD - BC = 0$

[1992 : 2 Marks]

5.7 The condition, that a 2-port network is reciprocal, can be expressed in terms of its ABCD parameters as \_\_\_\_.

[1994 : 1 Mark]

## 6. Graph Theory and State Equations


6.1 Relative to a given fixed tree of a network,

- (a) Link currents form an independent set.
- (b) Branch currents form an independent set.
- (c) Link voltages form an independent set.
- (d) Branch voltages form an independent.

[1992 : 2 Marks]

## 7. Network Functions

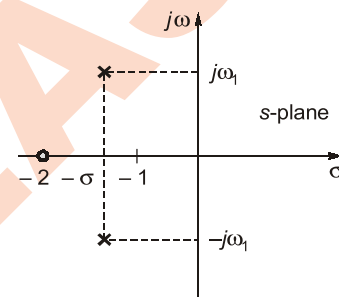7.1 A driving point admittance function has pole and zero locations as shown below. The range of  $s$  for which the function can be realized using passive elements is



- (a)  $\sigma < -1$
- (b)  $\sigma > 1$
- (c)  $\sigma < 1$
- (d)  $\sigma > -1$

[1988 : 2 Marks]

7.2 The necessary and sufficient condition for a rational function of  $s$ ,  $T(s)$  to be a driving point impedance of an RC network is that all poles and zeros should be

- (a) Simple and lie on the negative real axis of the  $s$ -plane
- (b) Complex and lie in the left half of the  $s$ -plane
- (c) Complex and lie in the right half of the  $s$ -plane
- (d) Simple and lie on the positive real axis of the  $s$ -plane

[1991 : 2 Marks]

7.3 Indicate True/False and give reason (For the following question)

$Z(s) = \frac{5}{s^2 + 4}$  represents the input impedance of a network.

[1994 : 2 Marks]

**Answers Network Theory**

1.1 (0.5)	1.2 (c)	1.3 (d)	1.4 (a)	1.5 (d)	1.6 (d)	2.1 (a)
2.2 (a) & (d)	2.3 (b)	2.4 (a)	2.5 (b)	2.6 (a)	2.7 (c)	2.8 (d)
2.9 (c)	2.10 (b)	2.11 (c)	2.12 (100, 1)	2.13 (a)	3.1 (b)	3.2 (a)
3.3 (a)	3.4 (c)	3.5 (5)	3.6 Sol.	3.7 (a)	4.1 (b)	4.2 (c)
4.3 (b)	4.4 (b)	4.5 (a)	5.1 (c)	5.2 (c & d)	5.3 (a)	5.4 (a)
5.5 (d)	5.6 (b & c)	5.7 (1)	6.1 (a)	7.1 (b)	7.2 (a)	7.3 (False)

**Explanations Network Theory****1. Basics of Network Analysis****1.1 (0.5)**

Triangular wave, 0.5 Amp peak.

$$i_L = \frac{1}{L} \int V dt$$


So, the current through inductor is the integration of the applied voltage across the inductor.

Integration of square wave is a triangular wave.

So, the current through the inductor is a **triangular wave**.

Now,  $v(t) = u(t) - 2u(t - 0.5) + 2u(t - 1) + \dots$

$\therefore i_L(t) = r(t) - 2r(t - 0.5) + 2r(t - 1) + \dots$

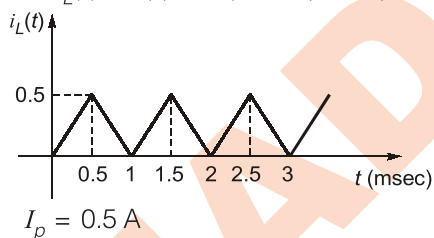**1.2 (c)**

$$N_1: Y_1(s) = s + \frac{1}{2s+1} + \frac{1}{\frac{1}{s} + 2}$$

$$Y_1(s) = \frac{2s^2 + 2s + 1}{2s + 1}$$

$$N_2: Y_2(s) = \frac{1}{2s+1} + \frac{1}{2 + \frac{1}{s}} = \frac{1+s}{2s+1}$$

$$N_3: Y_3(s) = s + \frac{1}{1 + \frac{1}{1 + \frac{1}{s}}} = s + \frac{1+s}{s+1+s}$$

$$Y_3(s) = \frac{2s^2 + 2s + 1}{2s + 1}$$

$N_4:$

$$Y_4(s) = s + \frac{1}{2s+1} = \frac{2s^2 + s + 1}{2s + 1}$$

So,  $N_1$  and  $N_3$  networks having identical driving point function.

**1.3 (d)**

If all resistors are doubled then the current get halved.

$$I' = \frac{I}{2}$$

$$R' = 2R$$

$$V' = \frac{I}{2} \cdot 2R = IR = V$$

**1.4 (a)**

Current through  $5 \Omega$  resistor,

$$i_5 = \frac{10}{5} = 2 \text{ Amp.}$$

Current through  $1 \Omega$  resistor,

$$i_1 = \frac{5}{1} = 5 \text{ Amp.}$$

So, the current through  $15 \Omega$  resistor,

$$i_{15} = -(i_1 + i_5) = -(5 + 2) = -7 \text{ Amp.}$$

Voltage across  $15 \Omega$  resistor.

$$V_{15} = 15(i_{15}) = 15(-7) = -105 \text{ V}$$

**1.5 (d)**

$$P_1 = 4 \text{ W and } P_2 = 9 \text{ W}$$

From superposition theorem

$$P = (\sqrt{P_1} + \sqrt{P_2})^2 = (\sqrt{4} + \sqrt{9})^2$$

$$P = (2 + 3)^2 = 25 \text{ W}$$

**1.6 (d)**

$$L = L_1 + L_2 \pm 2M = L_1 + L_2 \pm 2k\sqrt{L_1 L_2}$$


$$L = 2 + 2 \pm 2(0.1)\sqrt{2 \times 2} = 4 \pm 0.4$$

$$L = 3.6 \text{ H and } 4.4 \text{ H}$$

## 2. Sinusoidal Steady State

### 2.1 (a)

The given circuit is a bridge,

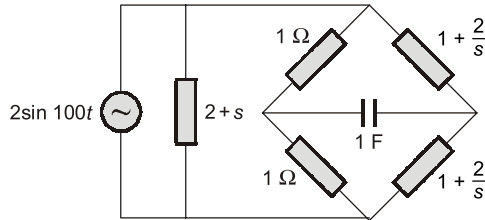

Product of opposite arms are equal,

$$1 \left( 1 + \frac{2}{s} \right) = 1 \left( 1 + \frac{2}{s} \right)$$

So, the current through the diagonal element (1 F capacitor) is zero.

### 2.2 (a) & (d)

Selectivity  $\propto Q$

$$Q = \frac{f_r}{B.W.} ; Q \propto \frac{1}{B.W.}$$

$$B.W. \propto \frac{1}{Q} ; B.W. \propto \frac{1}{\text{selectivity}}$$

If  $R_1 \rightarrow 0$

and  $R_2 \rightarrow \infty$

then the circuit will have only  $L$  &  $C$  elements and has high selectivity.

So, the half power bandwidth can be increased by reducing the selectivity.

So, by increasing the series resistance  $R_1$  and decreasing the parallel resistance  $R_2$ , the half power bandwidth can be increased.

### 2.3 (b)

$$L_{eq} = L_1 + L_2 - 2M$$

$$L_{eq} = 2 + 2 - 2(1) = 2 \text{ H}$$

At resonance

$$X_L = X_C$$

$$\omega L_{eq} = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{L_{eq} C}$$

$$\omega = \frac{1}{\sqrt{2 \times 2}} = \frac{1}{2} \text{ rad/sec}$$

$$2\pi f = \frac{1}{2}$$

$$f = \frac{1}{4\pi} \text{ Hz}$$

### 2.4 (a)

At resonance frequency

$$Z_{min} = R$$

$$I_{max} = \frac{V}{Z_{min}}$$

### 2.5 (b)

Given network is the series  $R$ - $L$ - $C$  circuit in resistor  $R$ , voltage  $V_R$  and current  $I_R$  is in phase and in series circuit current is same in all the elements.

$$I = I_R$$

So, the current is leading the voltage in the circuit. So, the given circuit will behave as capacitive circuit.

$$V_C > V_L$$

$$IX_C > IX_L$$

$$X_C > X_L$$

$$\frac{1}{\omega C} > \omega L$$

$$\omega^2 < \frac{1}{LC}$$

$$\omega^2 < \omega_r^2$$

$$\omega < \omega_r$$

### 2.6 (a)

At resonance

$$X_L - X_C = 0$$

$$|X_L| = |X_C|$$

$$|X_L| = |j12|$$

$$X_L = j12$$

$$X_L = X_{L_1} + X_{L_2} + 2k\sqrt{X_{L_1} \cdot X_{L_2}}$$

$$X_L = j2 + j8 + 2k\sqrt{j2j8} = j12$$

$$2k j4 = j2$$

$$k = 0.25$$

### 2.7 (c)

$$A_3^2 = A_1^2 + A_2^2$$

$$A_3^2 = (5)^2 + (12)^2$$

$$A_3^2 = 169$$

$$A_3 = 13 \text{ Amp.}$$

### 2.8 (d)

$$\therefore X_L = X_C$$

So, the circuit is at resonance.

$$I = \frac{V}{R} = \frac{200}{10} = 20 \text{ Amp.}$$

Voltage across the capacitor

$$V_c = I(-jX_c) = 20(-j20) = -j400$$

$$V_c = 400 \angle -90^\circ \text{ V}$$

**2.9 (c)**

For DC supply

Inductor behave as short circuit

capacitor behave as open circuit

So, under steady state conditions, the applied dc voltage drops entirely across the capacitor (c) only.

**2.10 (b)**

$$W_s = CV_s^2 ; W_c = \frac{1}{2} CV_s^2$$

$$\frac{W_c}{W_s} = 0.5$$

**2.11 (c)**

$$I_{\text{rms}} = \sqrt{3^2 + \left(\frac{4}{\sqrt{2}}\right)^2 + \left(\frac{4}{\sqrt{2}}\right)^2} = 5 \text{ Amp.}$$

Power is dissipated only in the  $10 \Omega$  resistor.

$$P = I_{\text{rms}}^2 R = (5)^2 \times 10 = 250 \text{ W}$$

**2.12 (100, 1)**


$$Z = R + j(X_L - X_C) = 100 + j0$$

Compare the real part

$$R = 100 \Omega$$

$$Q = \frac{\omega L}{R}$$

$$L = \frac{QR}{\omega} = \frac{100 \times 100}{10^7} = 1 \text{ mH}$$

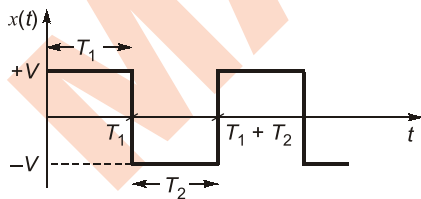**2.13 (a)**

RMS value of  $x(t)$

$$= \sqrt{\frac{1}{T} \int_0^T x^2(t) dt} = \sqrt{\frac{1}{T_1 + T_2} \left[ \int_0^{T_1} (V)^2 dt + \int_{T_1}^{T_1 + T_2} (-V)^2 dt \right]}$$

$$= \sqrt{\frac{1}{T_1 + T_2} [V^2 T_1 + V^2 T_2]} = \sqrt{V^2} = V$$

**3. Network Theorems****3.1 (b)**

According to maximum power transfer theorem,

$$Z_L = Z_S^*$$

**3.2 (a)**

$$P_1 = 1 \text{ W} ; P_2 = 4 \text{ W}$$

Since the polarity of both the sources are different

$$P = (\sqrt{P_1} - \sqrt{P_2})^2$$

$$P = (\sqrt{1} - \sqrt{4})^2 = (1 - 2)^2 = 1 \text{ W}$$

**3.3 (a)**

$$\frac{Z_L}{Z_S} = \left(\frac{n_2}{n_1}\right)^2 ; \frac{n_2}{n_1} = \sqrt{\frac{Z_L}{Z_S}}$$

**3.4 (c)**

$$\left(\frac{n_2}{n_1}\right)^2 = \frac{|Z_L|}{|Z_S|}$$

$$\left(\frac{n_2}{n_1}\right)^2 = \frac{2}{8} = \frac{1}{4}$$

$$\frac{n_2}{n_1} = \frac{1}{2}$$

$$n_1 = 2n_2 = 2 \times 40 = 80$$

**3.5 (5)**

Across switch  $S_1$ ,

$$I_{\text{sc}} = 5 \text{ A}$$

$$R_{\text{Th}} = [(4 \parallel 6 + 2 \parallel 8) + 3 + 3] \parallel 10 + 5$$

$$R_{\text{Th}} = (2.4 + 1.6 + 3 + 3) \parallel 10 + 5$$

$$= 10 \parallel 10 + 5 = 5 + 5$$

$$R_{\text{Th}} = 10 \Omega$$

$$V_{\text{o/c}} = V_{AB} = I_{\text{sc}} R_{\text{Th}} = 5 \times 10 = 50 \text{ V}$$

**3.6 Sol.**

$$Z_L = Z_G^*$$

$$Z_G = R_G + jX_G$$

$$Z_L = R_G - jX_G$$

**3.7 (a)**

Maximum power will be absorbed by  $R$  when

$$R = R_{\text{Th}}$$

$$R_{AB} = R_{\text{Th}} = (3 \parallel 6) + (4 \parallel 4)$$

$$R_{\text{Th}} = R = 2 + 2 = 4 \text{ k}\Omega$$

## 4. Transient Analysis

### 4.1 (b)

At steady state

Inductor behave as short circuit.

So, under steady state condition the source current flows through the inductor.

### 4.2 (c)

$$Z_C(s) = \frac{1}{Cs} = \frac{2}{s}$$

$$I_C(s) = \frac{V_C(s)}{Z_C(s)} = \frac{s(s+1)}{2(s^3 + s^2 + s + 1)} = \frac{s(s+1)}{2(s^2 + 1)(s+1)}$$

$$I_C(s) = \frac{s}{2(s^2 + 1)}$$

$$i(0^+) = \lim_{s \rightarrow \infty} s I_C(s) = \lim_{s \rightarrow \infty} \frac{s^2}{2(s^2 + 1)}$$

$$= \frac{1}{2+0} = \frac{1}{2} \text{ Amp.}$$

### 4.3 (b)

$$Z_2(s) = \frac{R_2 \times \frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}} = \frac{R_2}{R_2 C_2 s + 1}$$

$$Z_1(s) = \frac{R_1 \times \frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} = \frac{R_1}{R_1 C_1 s + 1}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

$$R_1 C_1 = R_2 C_2$$

$$\frac{V_2(s)}{V_1(s)} = \frac{\frac{R_2}{R_2 C_2 s + 1}}{\frac{R_1}{R_2 C_2 s + 1} + \frac{R_2}{R_2 C_2 s + 1}} = \frac{R_2}{R_1 + R_2}$$

$$V_2(s) = \frac{R_2}{R_1 + R_2} V_1(s)$$

For impulse response.

$$V_1(s) = 1$$

$$v_1(t) = \delta(t)$$


$$v_2(t) = \frac{R_2}{R_1 + R_2} \delta(t)$$

### 4.4 (b)

$$V_o = RC \frac{dV_i}{dt} = (5 \times 10^3)(4 \times 10^{-6}) \frac{d}{dt} (100t)$$

$$V_o = 2 \text{ Volts}$$

### 4.5 (a)

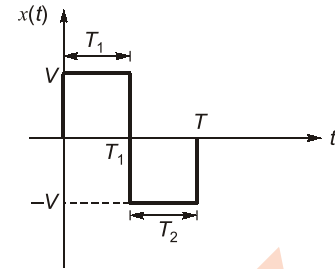

$$T = T_1 + T_2$$

$$\text{RMS} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \left[ \int_0^{T_1} V^2 dt + \int_{T_1}^T (-V)^2 dt \right]}$$

$$\text{RMS} = \sqrt{\frac{1}{T} [V^2 [T_1 - 0] + V^2 [T - T_1]]}$$

$$= \sqrt{\frac{1}{T} [V^2] [T_1 + T - T_1]}$$

$$\text{RMS} = \sqrt{\frac{1}{T} V^2 T} = \sqrt{V^2} = V$$

## 5. Two Port Networks

### 5.1 (c)

$$[Y] = [Y]_A + [Y]_B$$

### 5.2 (c) & (d)

The poles lying on the imaginary axis must be simple.

A pole may lie at origin.

### 5.3 (a)

For reciprocal network,

$$AD - BC = 1$$

### 5.4 (a)

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{12} = \frac{1 \times I_2}{I_2} = 1 \Omega$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$Z_{22} = \frac{2I_2 + 1I_2}{I_2} = 3 \Omega$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{11} = -\frac{2I_1 \times 1}{I_1} = -2$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \frac{-6I_1 + V_1}{I_1} = \frac{-6I_1 - 2I_1}{I_1}$$

$$Z_{21} = -8$$

**5.5 (d)**

ABCD parameter matrices,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

**5.6 (b) & (c)**

$$y_{21} = y_{12} \quad ; \quad h_{21} = -h_{12}$$

**5.7 (1)**

$$AD - BC = 1$$

## 7. Network Functions

**7.1 (b)**

$$\sigma - 1 > 0$$

$$\sigma > 1$$

**7.2 (a)**

Simple and lie on the negative real axis of the s-plane.

The poles and zeros of the  $Z_{RC}(s)$  should be simple and alternate on the negative real axis of the s-plane.

**7.3 (False)**

For  $Z(s)$  to represent the input impedance of a passive network, the numerator and denominator degrees should not differ by more than 1.

So,  $Z(s) = \frac{5}{s^2 + 4}$  can not represent the input impedance of a network **(False)**.

■■■



# Electromagnetics

## UNIT II

### CONTENTS

1. Basics of Electromagnetics **14**
2. Uniform Plane Waves **15**
3. Transmission Lines **16**
4. Waveguides **17**
5. Antennas **17**

## 1. Basics of Electromagnetics

1.1 An electrostatic field is said to be conservative when:

- (a) The divergence of the field is equal to zero
- (b) The curl of the field is equal to zero
- (c) The curl of the field is equal to  $-\frac{\partial E}{\partial t^2}$
- (d) The Laplacian of the field is equal to  $\mu\epsilon\frac{\partial^2 E}{\partial t^2}$

[1987 : 2 Marks]

1.2 On either side of a charge - free interface between two media

- (a) the normal components of the electric field are equal
- (b) the tangential component of the electric field are equal
- (c) the normal components of the electric flux density are equal
- (d) the tangential components of the electric flux density are equal

[1988 : 2 Marks]

1.3 Vector potential is a vector

- (a) whose curl is equal to the magnetic flux density
- (b) whose curl is equal to the electric field intensity
- (c) whose divergence is equal to the electric potential
- (d) which is equal to the vector product  $E \times H$

[1988 : 2 Marks]

1.4 The electric field strength at a far - off point  $P$  due to a point charge,  $+q$  located at the origin,  $O$  is 100 millivolts/metre. The point charge is now enclosed by a perfectly conducting hollow metal sphere with its centre at the origin,  $O$ . The electric field strength at the point,  $P$

- (a) remains unchanged in its magnitude and direction
- (b) remains unchanged in its magnitude but reverse in direction
- (c) would be that due to a dipole formed by the charge,  $+q$ , at  $O$  and  $-q$  induced
- (d) would be zero

[1989 : 2 Marks]

1.5 Which of the following field equations indicate that the free magnetic charge do not exist

- (a)  $\vec{H} = \frac{1}{\mu} \nabla \times \vec{A}$
- (b)  $\vec{H} = \oint \frac{I \vec{dl} \times \vec{R}}{4\pi R^2}$
- (c)  $\nabla \cdot \vec{H} = 0$
- (d)  $\nabla \times \vec{H} = \vec{J}$

[1990 : 2 Marks]

1.6 Given  $\vec{V} = x \cos^2 y \hat{i} + x^2 e^z \hat{j} + z \sin^2 y \hat{k}$  and  $S$  the surface of unit cube with one corner at the origin and edges parallel to the coordinate axis, the value of the integral  $\iint_C \vec{V} \cdot \hat{n} dS$  is \_\_\_\_\_.

[1993 : 2 Marks]

1.7 For a uniformly charged sphere of radius  $R$  and charge density  $\rho$ , the ratio of magnitude of electric fields at distances  $R/2$  and  $2R$  from the centre,

i.e.,  $\frac{E(r=R/2)}{E(r=2R)}$  is \_\_\_\_\_

[1993 : 2 Marks]

1.8 Match List-I with List-II and select the correct answer using the code given below the Lists:

List-I

List-II

A.  $\nabla \times \vec{H} = \vec{J}$

1. Continuity equation

B.  $\oint_C \vec{E} \cdot d\vec{l} = -\oint_s \frac{\partial B}{\partial t} \cdot d\vec{s}$

2. Faraday's Law

C.  $\nabla \cdot \vec{J} = -\frac{\partial \rho}{\partial t}$

3. Ampere's Law

4. Gauss's Law

5. Biot-Savart Law

Codes:

	A	B	C
(a)	3	2	1
(b)	2	1	3
(c)	4	3	1
(d)	1	2	3

[1994 : 2 Marks]

1.9 The electric field strength at distant point,  $P$ , due to a point charge,  $+q$ , located at the origin, is  $100 \mu\text{V/m}$ . If the point charge is now enclosed by a perfectly conducting metal sheet sphere whose center is at the origin, then the electric field strength at the point,  $P$ , outside the sphere, becomes

- (a) zero (b)  $100 \mu\text{V/m}$   
(c)  $-100 \mu\text{V/m}$  (d)  $50 \mu\text{V/m}$

[1995 : 1 M]

1.10 In the infinite plane,  $y = 6 \text{ m}$ , there exists a uniform surface charge density of  $(1/6000\pi) \mu\text{C/m}^2$ . The associated electric field strength is

- (a)  $30 \hat{i} \text{ V/m}$  (b)  $3 \hat{j} \text{ V/m}$   
(c)  $30 \hat{k} \text{ V/m}$  (d)  $60 \hat{j} \text{ V/m}$

[1995 : 1 M]

## 2. Uniform Plane Waves

2.1 For an electromagnetic wave incident from one medium to a second medium, total reflection takes place when

- (a) The angle of incidence is equal to the Brewster angle with  $E$  field perpendicular to the plane of incidence  
(b) The angle of incidence is equal to the Brewster angle with  $E$  field parallel to the plane of incidence  
(c) The angle of incidence is equal to the critical angle with the wave moving from the denser medium to a rarer medium  
(d) The angle of incidence is equal to the critical angle with the wave moving from a rarer medium to a denser medium

[1987 : 2 Marks]

2.2 In a good conductor the phase relation between the tangential components of electric field  $E_t$  and the magnetic field  $H_t$  is as follows

- (a)  $E_t$  and  $H_t$  are in phase  
(b)  $E_t$  and  $H_t$  are out of phase  
(c)  $H_t$  leads  $E_t$  by  $90^\circ$   
(d)  $E_t$  leads  $H_t$  by  $45^\circ$

[1988 : 2 Marks]

2.3 The skin depth of copper at a frequency of 3 GHz is 1 micron ( $10^{-6}$  metre). At 12 GHz, for a non magnetic conductor whose conductivity is 1/9 times that of copper, the skin depth would be

- (a)  $\sqrt{9 \times 4}$  microns (b)  $\sqrt{9/4}$  microns  
(c)  $\sqrt{4/9}$  microns (d)  $1/\sqrt{9 \times 4}$  microns

[1989 : 2 Marks]

2.4 The incoming solar radiation at a place on the surface of the earth is  $1.2 \text{ kW/m}^2$ . The amplitude of the electric field corresponding to this incident power is nearly equal to

- (a)  $80 \text{ mV/m}$  (b)  $2.5 \text{ V/m}$   
(c)  $30 \text{ V/m}$  (d)  $950 \text{ V/m}$

[1990 : 2 Marks]

2.5 The electric field component of a uniform plane electromagnetic wave propagating in the  $Y$ -direction in a lossless medium will satisfy the equation

- (a)  $\frac{\partial^2 E_y}{\partial y^2} = \mu \epsilon \frac{\partial^2 E_y}{\partial t^2}$  (b)  $\frac{\partial^2 E_y}{\partial x^2} = \mu \epsilon \frac{\partial^2 E_y}{\partial t^2}$   
(c)  $\frac{\partial^2 E_x}{\partial y^2} = \mu \epsilon \frac{\partial^2 E_x}{\partial t^2}$  (d)  $\frac{\sqrt{E_x^2 + E_z^2}}{\sqrt{H_x^2 + H_z^2}} = \sqrt{\mu/\epsilon}$

[1991 : 2 Marks]


2.6 A material is described by the following electrical parameters at a frequency of 10 GHz:  $\sigma = 10^6 \text{ mho/m}$ ,  $\mu = \mu_0$  and  $\epsilon/\epsilon_0 = 10$ . The material at this frequency is

considered to be ( $\epsilon_0 = \frac{1}{36\pi} \times 10^{-9} \text{ F/m}$ )

- (a) a good conductor  
(b) a good dielectric  
(c) neither a good conductor, nor a good dielectric  
(d) a good magnetic material

[1993 : 2 Marks]

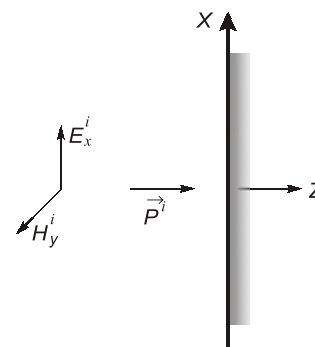2.7 A plane wave is incident normally on a perfect conductor as shown in figure. Here  $E_x^i$ ,  $H_y^i$  and  $\vec{P}^i$  are electric field, magnetic field and Poynting vector, respectively, for the incident wave. The reflected wave should have



- (a)  $E_x^r = -E_x^i$  (b)  $H_y^r = -H_y^i$   
 (c)  $\vec{P}^r = -\vec{P}^i$  (d)  $E_x^r = E_x^i$

[1993 : 2 Marks]

- 2.8** A long solenoid of radius  $R$ , and having  $N$  turns per unit length carries a time dependent current  $I(t) = I_0 \cos(\omega t)$ . The magnitude of induced electric field at a distance  $R/2$  radially from the axis of the solenoid is

- (a)  $\frac{R}{2} \mu_0 N I_0 \omega \sin(\omega t)$   
 (b)  $\frac{R}{4} \mu_0 N I_0 \omega \cos(\omega t)$   
 (c)  $\frac{R}{4} \mu_0 N I_0 \omega \sin(\omega t)$   
 (d)  $R \mu_0 N I_0 \omega \sin(\omega t)$

[1993 : 2 Marks]

**2.9**  $\oint_C \vec{A} \cdot d\vec{l} = \int_S \underline{\hspace{1cm}} \cdot d\vec{s}$

[1994 : 1 Mark]

- 2.10** A plane electromagnetic wave traveling along the  $+z$  direction, has its electric field given by  $E_x = 2 \cos(\omega t)$  and  $E_y = 2 \cos(\omega t + 90^\circ)$  the wave is

- (a) linearly polarized  
 (b) right circularly polarized  
 (c) left circularly polarized  
 (d) elliptically polarized

[1994 : 1 Mark]

- 2.11** The intrinsic impedance of a lossy dielectric medium is given by

- (a)  $\frac{j\omega\mu}{\sigma}$  (b)  $\frac{j\omega\epsilon}{\mu}$   
 (c)  $\sqrt{\frac{j\omega\mu}{(\sigma + j\omega\epsilon)}}$  (d)  $\sqrt{\frac{\mu}{\epsilon}}$

[1995 : 1 M]

- 2.12** Copper behaves as a  
 (a) conductor always  
 (b) conductor or dielectric depending on the applied electric field strength  
 (c) conductor or dielectric depending on the frequency  
 (d) conductor or dielectric depending on the electric current density

[1995 : 1 M]

### 3. Transmission Lines

- 3.1** A transmission line of real characteristic impedance is terminated with an unknown load. The measured value of VSWR on the line is equal to 2 and a voltage minimum point is found to be at the load. The load impedance is then  
 (a) Complex (b) Purely capacitive  
 (c) Purely resistive (d) Purely inductive

[1987 : 2 Marks]

- 3.2** A Two-wire transmission line of characteristic impedance  $Z_0$  is connected to a load of impedance  $Z_L$  ( $Z_L \neq Z_0$ ). Impedance matching cannot be achieved with

- (a) a quarter - wavelength transformer  
 (b) a half - wavelength transformer  
 (c) an open - circuited parallel stub  
 (d) a short-circuited parallel stub

[1988 : 2 Marks]

- 3.3** A 50 ohm lossless transmission line has a pure reactance of ( $j100$ ) ohms as its load. The VSWR in the line is

- (a) 1/2 (Half) (b) 2 (Two)  
 (c) 4 (Four) (d)  $\infty$  (Infinity)

[1989 : 2 Marks]

- 3.4** The input impedance of a short circuited lossless transmission line quarter wave long is

- (a) purely reactive  
 (b) purely resistive  
 (c) infinite  
 (d) dependent on the characteristic impedance of the line

[1991 : 2 Marks]

- 3.5** A transmission line whose characteristic impedance is a real

- (a) must be a lossless line  
 (b) must be a distortionless line  
 (c) may not be a lossless line  
 (d) may not be a distortionless line

[1992 : 2 Marks]

- 3.6** Consider a transmission line of characteristic impedance 50 ohm. Let it be terminated at one end by ( $+j50$ ) ohm. The VSWR produced by it in the transmission line will be

- (a) +1 (b) 0  
 (c)  $\infty$  (d)  $+j$

[1993 : 2 Marks]

3.7 A load impedance,  $(200 + j0) \Omega$  is to be matched to a  $50 \Omega$  lossless transmission line by using a quarter wave line transformer (QWT). The characteristic impedance of the QWT required is \_\_\_\_\_. [1994 : 1 Mark]

3.8 If a pure resistance load, when connected to a lossless  $75 \text{ ohm}$  line, produces a VSWR of 3 on the line, then the load impedance can only be  $25 \text{ ohms}$ . True/False (Give Reason) [1994 : 2 Marks]

#### 4. Waveguides

4.1 The cut off frequency of a waveguide depends upon  
 (a) The dimensions of waveguide  
 (b) The dielectric property of the medium in the waveguide  
 (c) The characteristic impedance of the waveguide  
 (d) The transverse and axial components of the fields [1987 : 2 Marks]

4.2 For a normal mode EM wave propagating in a hollow rectangular wave guide  
 (a) the phase velocity is greater than the group velocity.  
 (b) the phase velocity is greater than velocity of light in free space.  
 (c) the phase velocity is less than the velocity of light in free space.  
 (d) the phase velocity may be either greater than or less than the group velocity. [1988 : 2 Marks]

4.3 Choose the correct statements  
 For a wave propagating in an air filled rectangular waveguide  
 (a) Guided wavelength is never less than the free space wavelength.  
 (b) Wave impedance is never less than the free space impedance.  
 (c) Phase velocity is never less than the free space velocity.  
 (d) TEM mode is possible if the dimensions of the wave guide are properly chosen. [1990 : 2 Marks]

4.4 The interior of a  $\frac{20}{3} \text{ cm} \times \frac{20}{4} \text{ cm}$  rectangular waveguide is completely filled with a dielectric of  $\epsilon_r = 4$ . Waves of free space wave lengths shorter than ..... can be propagated in the  $TE_{11}$  mode. [1994 : 1 Mark]

#### 5. Antennas

5.1 The electric field  $E$  and the magnetic field  $H$  of a short dipole antenna satisfy the condition  
 (a) the  $r$  component of  $E$  is equal to zero  
 (b) both  $r$  and  $\theta$  components of  $H$  are equal to zero  
 (c) the  $\theta$  component of  $E$  dominates the  $r$  component in the far - field region  
 (d) the  $\theta$  and  $\phi$  components of  $H$  are of the same order of magnitude in the near field region [1988 : 2 Marks]

5.2 Two isotropic antennas are separated by a distance of two wavelengths. If both the antennas are fed with currents of equal phase and magnitude, the number of lobes in the radiation pattern in the horizontal plane are  
 (a) 2 (b) 4  
 (c) 6 (d) 8 [1990 : 2 Marks]

5.3 In a broad side array of 20 isotropic radiators, equally spaced at distance of  $\lambda/2$ , the beam width between first nulls is  
 (a)  $51.3^\circ$  (b)  $11.46^\circ$   
 (c)  $22.9^\circ$  (d)  $102.6^\circ$  [1991 : 2 Marks]

5.4 Two dissimilar antennas having their maximum directivities equal, which of the following statements are right?  
 (a) must have their beam widths also equal  
 (b) cannot have their beam widths equal because they are dissimilar antenna  
 (c) may not necessarily have their maximum power gains equal  
 (d) must have their effective aperture areas (capture areas) also equal [1992 : 2 Marks]

5.5 The beamwidth between first nulls of a uniform linear array of  $N$  equally spaced (element spacing =  $d$ ), equally excited antennas, is determine by  
 (a)  $N$  alone and not by  $d$   
 (b)  $d$  alone and not by  $N$   
 (c) the ratio,  $(N/d)$   
 (d) the product,  $(Nd)$  [1992 : 2 Marks]

5.6 For a half-wave dipole antenna, which of the following statements are right?

- (a) the radiation intensity is maximum along the normal to the dipole axis
- (b) the current distribution along its length is uniform irrespective of the length
- (c) the effective length equals its physical length
- (d) the input impedance is independent of the location of the feed-point

[1994 : 1 Mark]

5.7 An antenna, when radiating, has a highly directional radiation pattern. When the antenna is receiving, its radiation pattern

- (a) is more directive
- (b) is less directive
- (c) is the same
- (d) exhibits no directivity at all

[1995 : 1 M]

■■■

## Answers Electromagnetics

1.1	(b)	1.2	(b & c)	1.3	(a)	1.4	(a)	1.5	(c)	1.6	(1)	1.7	(2)
1.8	(a)	1.9	(b)	1.10	(b)	2.1	(c)	2.2	(d)	2.3	(b)	2.4	(d)
2.5	(c & d)	2.6	(a)	2.7	(a & c)	2.8	(c)	2.9	(sol.)	2.10	(c)	2.11	(d)
2.12	(a)	3.1	(c)	3.2	(b)	3.3	(d)	3.4	(c)	3.5	(b & c)	3.6	(c)
3.7	(100)	3.8	(False)	4.1	(a, b)	4.2	(a & b)	4.3	(a & c)	4.4	(8)	5.1	(b, c)
5.2	(d)	5.3	(b)	5.4	(a, c)	5.5	(d)	5.6	(a)	5.7	(b)		

## Explanations Electromagnetics

### 1. Basics of Electromagnetics

#### 1.1 (b)

An electrostatic field is said to be conservative when the closed line integral of the field is zero.

$$\oint \vec{E} \cdot d\vec{l} = 0$$

Stoke's theorem

$$\oint_c \vec{E} \cdot d\vec{l} = \int_s (\nabla \times \vec{E}) \cdot d\vec{s}$$

So,  $\nabla \times \vec{E} = 0$

#### 1.2 (b) & (c)

Boundary conditions:  $E_{t_1} = E_{t_2}$  and  $D_{N_1} = D_{N_2}$

#### 1.3 (a)

Vector potential in magnetic fields is the measure of work done to move a current element  $I d\vec{l}$


$$\vec{A} = \frac{W}{I d\vec{l}}$$

It relates to  $\vec{B}$  (which is force experienced by a current element) as  $\nabla \times \vec{A} = \vec{B}$ .

$$\nabla \times \vec{A} = \vec{B} = \mu \vec{H}$$
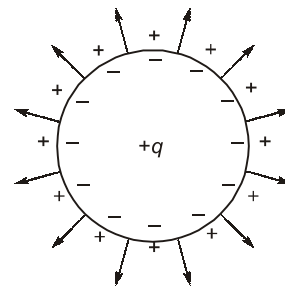
#### 1.4 (a)

The radially outward field is normal to conductor and no induction effects  $E$  is same.



#### 1.5 (c)

Magnetic field lines are closed around the current and have no sources or sink points.

$$\oiint \vec{B} \cdot d\vec{s} = \iiint \nabla \cdot \vec{B} dv$$

$$\nabla \cdot \vec{B} = 0$$

In any closed surface,

Entering flux = Leaving flux

Dipole is the cause of magnetic fields.

Magnetic monopoles or free charges do not exist is justified by  $\nabla \cdot \vec{B} = 0$ .

According to the Gauss's law for magnetic fields,

$$\oint_s \vec{B} \cdot d\vec{s} = 0$$

$$\nabla \cdot \vec{B} = 0$$

$$\nabla \cdot \mu \vec{H} = 0$$

$$\mu \nabla \cdot \vec{H} = 0$$

$$\nabla \cdot \vec{H} = 0$$

**1.6 (1)**

$$\oiint \vec{V} \cdot d\vec{s} = \iiint (\nabla \cdot \vec{V}) dv$$

$$\nabla \cdot \vec{V} = \cos^2 y + \sin^2 y = 1$$

$$\int (\nabla \cdot \vec{V}) dv = 1$$

**1.7 (2)**

$$D = \frac{\rho_v r}{3} \quad r < R$$

$$D = \frac{\rho_v R^3}{3r^2} \quad r > R$$

Applying Gauss law with spherical Gaussian surface concentric with the charge.

$$E(\text{at } r = R/2) = \frac{\rho_v R}{6\epsilon}$$

$$E(2R) = \frac{\rho_v R}{12\epsilon}$$

$$\text{So, } \frac{E(\text{at } r = R/2)}{E(\text{at } r = 2R)} = 2$$

**1.8 (a)**

(A) - 3, (B) - 2, (C) - 1


$$\nabla \times \vec{H} = \vec{J} \rightarrow \text{Ampere's law}$$

$$\oint_c \vec{E} \cdot d\vec{l} = -\oint_s \frac{\partial B}{\partial t} \cdot d\vec{s} \rightarrow \text{Faraday's law}$$

$$\nabla \cdot \vec{J} = -\frac{\partial \rho}{\partial t} \rightarrow \text{Continuity equation}$$

**1.9 (b)**

The radially outward field is normal to conductor and no induction effects  $E$  is same.

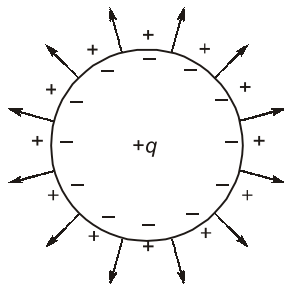**1.10 (b)**

$$\vec{E} = \frac{\rho_s}{2\epsilon} \hat{a}_n$$

$$\text{Where, } \hat{a}_n = \hat{a}_y$$

$$\rho_s = \frac{1}{6000\pi} \times 10^{-6} \text{ C/m}^2$$

$$\vec{E} = \frac{10^{-6} \times \pi}{2 \times 8.854 \times 10^{-12} \times 6000\pi} \hat{a}_y$$

$$\vec{E} = 3\hat{a}_y = 3j \text{ V/m}$$

**2. Uniform Plane Waves****2.1 (c)**

$$\theta_c = \sin^{-1}\left(\frac{n_2}{n_1}\right) = \sin^{-1}\sqrt{\frac{\epsilon_{r2}}{\epsilon_{r1}}}$$

For total internal reflection,

$$\theta_i \geq \theta_c$$

$$\theta_i \geq \sin^{-1}\left(\sqrt{\frac{\epsilon_{r2}}{\epsilon_{r1}}}\right) \text{ with } \epsilon_{r1} > \epsilon_{r2}$$

For total internal reflection to take place, the wave should move from a denser medium to a rarer medium and the angle of incidence should be greater than or equal to the critical angle.

**2.2 (d)**

$\eta$  = intrinsic impedance

$$= \frac{E_t}{H_t} = \sqrt{\frac{j\omega\mu}{\sigma + j\omega\epsilon}}$$

For a good conductor

$$\sigma \gg \omega\epsilon$$

$$\frac{E_t}{H_t} = \sqrt{\frac{j\omega\mu}{\sigma}} = \sqrt{\frac{\omega\mu}{\sigma}} e^{j\pi/4}$$

So,  $E_t$  leads  $H_t$  by an angle of  $45^\circ$ .

**2.3 (b)**

We know that: For a good conductor,

$$\text{Skin depth} = \delta = \frac{1}{\sqrt{\pi f \mu \sigma}}$$

$$\delta \propto \frac{1}{\sqrt{f\sigma}}$$

$$\frac{\delta_2}{\delta_1} = \sqrt{\frac{f_1 \sigma_1}{f_2 \sigma_2}}$$

Given that,

$$\delta_1 = 1 \text{ micron}$$

$$f_1 = 3 \text{ GHz}$$

$$f_2 = 12 \text{ GHz}$$

$$\frac{\sigma_2}{\sigma_1} = \frac{1}{9}$$

$$\frac{\delta_2}{1} = \sqrt{\frac{3}{12} \times \frac{9}{1}} = \sqrt{\frac{9}{4}}$$

$$\delta_2 = \sqrt{\frac{9}{4}} \text{ microns}$$

#### 2.4 (d)

$$\text{Power density, } P = \frac{E^2}{2\eta}$$

$$E = \sqrt{2\eta P}$$

$$\eta = \eta_0 = 120\pi$$

$$P = 1.2 \text{ kW/m}^2 = 1200 \text{ W/m}^2$$

$$E = \sqrt{2 \times (120\pi) \times (1200)}$$

$$E \approx 950 \text{ V/m}$$

#### 2.5 (c & d)

When  $E$  is a function of  $y$  and directed in  $x$  and  $z$  possibly orthogonal to propagation.

$$E_y = H_y = 0$$

$$\frac{\partial^2 E_x}{\partial y^2} = \mu \epsilon \frac{\partial^2 E_x}{\partial t^2}$$

$$\frac{E}{H} = \frac{\sqrt{E_x^2 + H_z^2}}{\sqrt{H_x^2 + H_z^2}} = \eta = \sqrt{\frac{\mu}{\epsilon}}$$

#### 2.6 (a)

Loss tangent,

$$\frac{\sigma}{\omega \epsilon} = \frac{10^6}{2\pi(10 \times 10^9)(8.854 \times 10^{-12} \times 10)}$$

$$\frac{\sigma}{\omega \epsilon} = 1.798 \times 10^5 \gg 1$$

So, the given material at  $f = 10 \text{ GHz}$  is considered as a good conductor.

#### 2.7 (a & c)

Reflection coefficient for electric fields

$$\Gamma_E = \frac{\sqrt{\frac{j\omega\mu}{\sigma}} - 120\pi}{\sqrt{\frac{j\omega\mu}{\sigma}} + 120\pi} = -1 \text{ for conductors}$$

$$\text{As } \eta = \sqrt{\frac{j\omega\mu}{\sigma}} \approx 0 \text{ with } \sigma \text{ being large}$$

when  $E$  reflection completely out of phase,  
 $H$  reflects in phase

$$E_x^r = -E_x^i$$

$$H_x^r = H_x^i$$

$$\text{So, } \vec{P}^r = -\vec{P}^i$$

#### 2.8 (c)

$$H \cdot l = nI(t)$$

where,  $n$  = Total number of turns

$$N = \frac{n}{l}$$

$$H = NI(t)$$

$$B = \mu_0(H) = \mu_0 NI(t)$$

$$B = \mu_0 NI_0 \cos(\omega t)$$

According to Maxwell's equation,

$$\oint E \cdot d\vec{l} = -\int \frac{\partial \vec{B}}{\partial t} \cdot d\vec{s}$$

$$E \cdot 2\pi \frac{R}{2} = \mu_0 NI_0 \omega \sin(\omega t) \frac{\pi R^2}{4}$$

$$E = \frac{R}{4} \mu_0 NI_0 \omega \sin(\omega t)$$

#### 2.9 Sol.

Using Stoke's theorem

$$\oint_C \vec{A} \cdot d\vec{l} = \int_S \nabla \times \vec{A} \cdot d\vec{s}$$

#### 2.10 (c)

Two equal  $E$  field components out of phase by  $90^\circ$  gives circular polarization.


$$E_x = 2\cos\omega t$$

$$E_y = 2\cos(\omega t + 90^\circ) = -2\sin\omega t$$

Tracing with time for sense of rotation as left or right.

$$t = 0 \quad E_x = 2 \quad E_y = 0$$
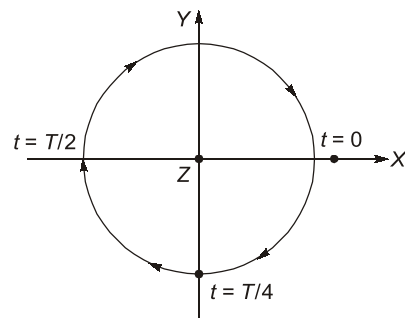
$$t = \frac{T}{4} \quad E_x = 0 \quad E_y = -2$$



Left circular for  $+z$  propagation.



**2.12 (a)**

A material behave as conductor if,

$$\frac{\sigma}{\omega \epsilon} > 1$$

$$\sigma > \omega \epsilon$$

For copper, conductivity  $\sigma = 5.8 \times 10^7$  mho/m

$$\epsilon = 8.856 \times 10^{-12} \text{ F/m}$$

So, even at very large frequencies,

$$\sigma > \omega \epsilon$$

So, copper always behave as conductor for practical frequencies.

**3. Transmission Lines****3.1 (c)**

Given, voltage minimum ( $V_{\min}$ ) point is at load.

If  $V_{\min}$  or  $V_{\max}$  occurs at the load for a lossless transmission line then load impedance  $Z_L$  is purely resistive.

If  $Z_L$  (resistive)  $> Z_0$ , voltage maxima occurs at the load.

If  $Z_L$  (resistive)  $< Z_0$ , voltage minima occurs at the load.

**3.2 (b)**

$\lambda/2$  length transmission line has  $Z_{\text{in}} = Z_L$  and hence cannot be a impedance matching device.

**3.3 (d)**

$$\text{Reflection coefficient} = \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= \frac{j100 - 50}{j100 + 50}$$

$$|\Gamma| = \frac{\sqrt{(100)^2 + (50)^2}}{\sqrt{(100)^2 + (50)^2}} = 1$$

$$\text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \frac{2}{0} = \infty$$

**3.4 (c)**

For a quarter wave transformer ( $\lambda/4$ ),

$$Z_{\text{in}} = \frac{Z_0^2}{Z_L}$$

$$Z_L = 0$$

$$Z_{\text{in}} = \frac{Z_0^2}{0} = \infty$$

**3.5 (b & c)**

For a distortionless line,

$$RC = LG$$

$$\alpha = \sqrt{RG}$$

$$\beta = \omega \sqrt{LC}$$

$$Z_o = R_o = \sqrt{\frac{L}{C}} \text{ (real)}$$

For a lossless line,

$$R = 0$$

$$G = 0$$

$$\alpha = 0$$

$$\beta = \omega \sqrt{LC}$$

$$Z_o = R_o = \sqrt{\frac{L}{C}} \text{ (real)}$$

$Z_o$  is real means either lossless or distortionless and lossless lines also satisfies  $LG = RC$  which means they are distortionless.

**3.6 (c)**

$$\text{Reflection coefficient} = \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{j50 - 50}{j50 + 50} = \frac{-50 + j50}{50 + j50}$$

$$|\Gamma| = \frac{\sqrt{(50)^2 + (50)^2}}{\sqrt{(50)^2 + (50)^2}} = 1$$

$$\text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \frac{2}{0} = \infty$$

**3.7 (100)**

For quarter wave line transformer,

$$Z_0^2 = Z_{\text{in}} Z_L$$

$$Z_0^2 = (50)(200)$$

$$Z_0 = 100 \Omega$$

**3.8 (False)**

For a pure resistive load of a lossless line,

$$\text{VSWR} = \frac{R_L}{R_0} \quad \text{if } R_L > R_0$$

$$\text{VSWR} = \frac{R_0}{R_L} \quad \text{if } R_0 > R_L$$

Given that, VSWR = 3

So,  $R_L = \text{VSWR} \times R_0 = 3 \times 75 = 225 \Omega$

$$\text{or } R_L = \frac{R_0}{\text{VSWR}} = \frac{75}{3} = 25 \Omega$$

Hence,  $R_L = 25$  or  $75$

#### 4. Waveguides

##### 4.1 (a, b)

$$f_c = \frac{v_o}{2\pi} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

$$\text{Where, } v_o = \frac{c}{\sqrt{\mu_r \epsilon_r}}$$

$$f_c = \frac{c}{\sqrt{\mu_r \epsilon_r} \times 2} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

So,  $f_c$  depends on 'a' and 'b' (dimensions of waveguide)

$$f_c \propto \frac{1}{\sqrt{\mu_r \epsilon_r}}$$

So,  $f_c$  depends upon the dielectric property of the medium in the waveguide.

##### 4.2 (a & b)

$$v_p > c > v_g$$

$$v_p = \frac{c}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

$$v_g = c \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$

##### 4.3 (a & c)

$$\lambda_g = \frac{\lambda}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

$$\lambda_g > \lambda$$

$$\eta_{TE} = \frac{\eta_0}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

$$\eta_{TE} > \eta_0$$

$$\eta_{TM} = \eta_0 \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$

$$\eta_{TM} < \eta_0$$

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{\mu \epsilon}} = \frac{c}{\sqrt{\mu_r \epsilon_r} \sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

$$v_p > c$$

##### 4.4 (8)

$$v = \frac{1}{\sqrt{\mu \epsilon}} = \frac{1}{\sqrt{\mu_0 \epsilon_0 \epsilon_r}}$$

$$= \frac{1}{\sqrt{\mu_0 \epsilon_0}} \times \frac{1}{\sqrt{\epsilon_r}}$$

$$v = \frac{3 \times 10^8}{\sqrt{4}} = 1.5 \times 10^8 \text{ m/sec}$$

$$m = n = 1$$

$$f_c = \frac{v}{2\pi} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

$$= \frac{1.5 \times 10^8}{2} \sqrt{\left(\frac{3}{20}\right)^2 + \left(\frac{4}{20}\right)^2} \times 10^2$$

$$f_c = \frac{7.5 \times 10^9}{20} \times 5 = 1.875 \times 10^9 \text{ Hz}$$

$$\lambda_c = \frac{v}{f_c} = \frac{1.5 \times 10^8}{1.875 \times 10^9} = 8 \text{ cm}$$

So, waves of free space wavelength shorter than 8 cm can be propagated.

$$\lambda_c = 8 \text{ cm}$$

#### 5. Antennas

##### 5.1 (b, c)

Every dipole antenna has fields in directions of  $r$ ,  $\theta$ ,  $\phi$  with  $E_r$ ,  $E_\theta$ ,  $H_\phi$ .

These fields depend on  $1/r$ ,  $1/r^2$  and  $1/r^3$  with distance.

$1/r$  terms are called as radiation fields and exist even at far away distance.

$E_\theta$  and  $H_\phi$  have 1 terms each depending on  $1/r$ .  $1/r^2$  and  $1/r^3$  terms are called as induction fields and exist at closer distances with zero values far away.

$E_r$  has only  $1/r^2$  and  $1/r^3$  terms.

Option (a)-wrong- $E_r$  exists.

Option (b)-right- $E_\phi$  only exists.

Option (c)-right- $E_\theta$  has  $1/r$  terms which  $E_r$  does not have.

Option (d)-wrong- $H_\theta$  does not exist.

**5.2 (d)**

Given that:  $d = 2\lambda$  and  $\alpha = 0$

$$\psi = \alpha + \beta d \cos\theta$$

$$\psi = 0 + \frac{2\pi}{\lambda} \cdot 2\lambda \cdot \cos\theta = 4\pi \cos\theta$$

When  $\psi = 0, 2\pi, -2\pi, 4\pi, -4\pi$  maxima occurs in that direction.

$$\text{Maximum at } \theta = 0, \frac{\pi}{3}, \frac{\pi}{2}, \frac{2\pi}{3}, \pi, \frac{4\pi}{3}, \frac{3\pi}{2}, \frac{5\pi}{3}$$

So, number of lobes in the radiation pattern in the horizontal plane = 8.

**5.3 (b)**

Electric field strength of  $N$  element array

$$E_T = NE_o \frac{\sin(N\psi/2)}{\sin(\psi/2)}$$

For null points  $\sin\left(N\frac{\psi}{2}\right) = 0$

with  $\sin\left(\frac{\psi}{2}\right) \neq 0$  (denominator term)

$$\left(N\frac{\psi}{2}\right) = 2n\pi \text{ for null points}$$

$$\psi = \frac{4n\pi}{N}$$

$$\alpha + \beta d \cos\theta = \frac{4n\pi}{N}$$

With  $\alpha = 0$  for broadside array.

$$\frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} \cos\theta = \frac{4n\pi}{N}$$

$$\cos\theta = \frac{4n}{N}$$

with  $n = 1$  for 1<sup>st</sup> null points

$$\cos\theta_{NP1} = \frac{4}{20}$$

$$\theta_{NP1} = 78.46^\circ$$

with  $n = 2$  for 2<sup>nd</sup> null points

$$\cos\theta_{NP2} = \frac{8}{20}$$

$$\theta_{NP2} = 66.42^\circ$$

Beam width between first nulls =  $12.04^\circ$

**5.4 (a, c)**

$$\text{Directivity} = \frac{4\pi}{\lambda^2} A_e = \frac{4\pi}{\Omega_A}$$

$$\Omega_A = \text{Beam solid angle}$$

$$A_e = \text{Capture area}$$

Power gain depends on efficiency and losses, so they may not be equal is right.

Capture areas depend on gain and frequency also.

**5.5 (d)**

Beam widths depend on the array factor  $\frac{N\psi}{2}$ .

when  $\frac{N\psi}{2} = 2n\pi$  for minima condition

$$\alpha + \beta d \cos\theta = \psi = \frac{4n\pi}{N}$$

$$\cos\theta = \frac{\frac{4n\pi}{N} - \alpha}{\beta d} = \frac{4n\pi - \alpha N}{\beta Nd}$$

$\alpha = 0$  for equally excited (in phase)

$$\cos\theta \propto \frac{1}{Nd}$$

BWFN in both arrays is determined by the product ( $Nd$ ).

**5.6 (a)**

- Dipole antenna has radiation depending as

$$\frac{\cos\left(\frac{\pi}{2} \cos\theta\right)}{\sin\theta} \text{ and maximum at } 90^\circ \text{ to array axis.}$$

- Current distribution is uniform only for very short lengths like hertzian dipole.

- $I_{\text{eff}} = \frac{2I}{\pi}$  for  $\lambda/2$  dipole

- $Z_{\text{in}}$  for any wire antenna depends on loading effects from either sides of the feed points or length on either sides.

**5.7 (b)**

An antenna, when radiating, has a highly directional radiation pattern. When the antenna is receiving, its radiation pattern is the same.

Antenna is a reciprocal device, whose characteristics are the same when it is transmitting or receiving.

# Control Systems

## UNIT III

### CONTENTS


1. Basics of Control Systems, Block Diagram and SFG's **25**
2. Compensators and Controllers **25**
3. Time Response Analysis **26**
4. Stability Analysis **27**
5. Root Locus **27**
6. Frequency Response Analysis **29**
7. State Space Analysis **30**

# III

## Control Systems

### 1. Basics of Control Systems, Block Diagram and SFG's

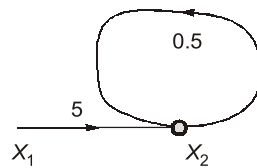- 1.1 In the signal flow graph shown in figure  $X_2 = TX_1$  where  $T$ , is equal to




- (a) 2.5 (b) 5  
(c) 5.5 (d) 10

[1987 : 2 Marks]

- 1.2 For the system shown in figure the transfer function


$\frac{C(s)}{R(s)}$  is equal to :

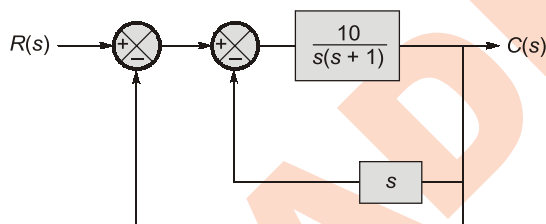

- (a)  $\frac{10}{s^2 + s + 10}$  (b)  $\frac{10}{s^2 + 11s + 10}$   
(c)  $\frac{10}{s^2 + 9s + 10}$  (d)  $\frac{10}{s^2 + 2s + 10}$

[1987 : 2 Marks]

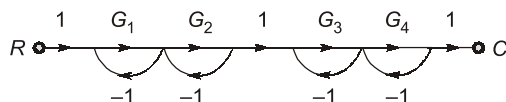- 1.3 The  $C/R$  for the signal flow graph in figure is:




- (a)  $\frac{G_1 G_2 G_3 G_4}{(1 + G_1 G_2)(1 + G_3 G_4)}$   
(b)  $\frac{G_1 G_2 G_3 G_4}{(1 + G_1 + G_2 + G_1 G_2)(1 + G_3 + G_4 + G_3 G_4)}$

(c)  $\frac{G_1 G_2 G_3 G_4}{(1 + G_1 + G_2)(1 + G_3 + G_4)}$

(d)  $\frac{G_1 G_2 G_3 G_4}{(1 + G_1 + G_2 + G_3 + G_4)}$

[1989 : 2 Marks]

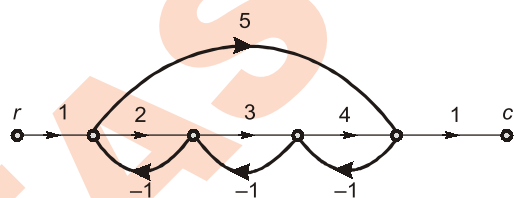- 1.4 In the signal flow graph of figure the gain  $c/r$  will be



- (a) 11/9 (b) 22/15  
(c) 24/23 (d) 44/23

[1991 : 2 Marks]

- 1.5 Signal flow graph is used to find

- (a) Stability of the system  
(b) Controllability of the system  
(c) Transfer function of the system  
(d) Poles of the system.

[1995 : 1 M]

- 1.6 The transfer function of a linear system is the

- (a) ratio of the output,  $v_o(t)$  and input  $v_i(t)$ .  
(b) ratio of the derivatives of the output and the input.  
(c) ratio of the Laplace transform of the output and that of the input with all initial conditions zeros.  
(d) none of these.

[1995 : 1 M]

### 2. Compensators and Controllers

- 2.1 The transfer function of a simple  $RC$  network functioning as a controller is:

$$G_c(s) = \frac{s + z_1}{s + p_1}$$

The condition for the  $RC$  network to act as a phase lead controller is:

- (a)  $p_1 < z_1$  (b)  $p_1 = 0$   
(c)  $p_1 = z_1$  (d)  $p_1 > z_1$

[1990 : 2 Marks]

2.2 A process with open-loop model  $G(s) = \frac{Ke^{-sT_D}}{\tau s + 1}$

- is controlled by a PID controller. For this process.
- (a) the integral mode improves transient performance
  - (b) the integral mode improves steady-state performance
  - (c) the derivative mode improve transient performance
  - (d) the derivative mode improves steady-state performance.


[1992 : 2 Marks]

2.3 Tachometer feedback in a d.c. position control system enhances stability (T/F)

[1994 : 1 Mark]

### 3. Time Response Analysis

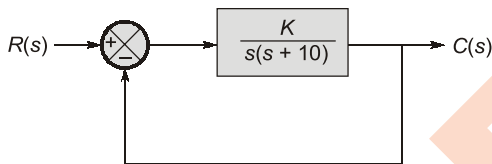3.1 The unity feedback system shown in fig. has:



- (a) Zero steady state position error
- (b) Zero steady state velocity error
- (c) Steady state position error  $\frac{K}{10}$  units
- (d) Steady state velocity error  $\frac{K}{10}$  units

[1987 : 2 Marks]

3.2 The steady state error of a stable 'type 0' unity feedback system for a unit step function is

- (a) 0
- (b)  $\frac{1}{1+K_P}$
- (c)  $\infty$
- (d)  $\frac{1}{K_P}$

[1990 : 2 Marks]

3.3 A second-order system has a transfer function

given by  $G(s) = \frac{25}{s^2 + 8s + 25}$

If the system, initially at rest, is subjected to a unit step input at  $t = 0$ , the second peak in the response will occur at

- (a)  $\pi$  sec
- (b)  $\pi/3$  sec
- (c)  $2\pi/3$  sec
- (d)  $\pi/2$  sec.

[1991 : 2 Marks]

3.4 A unity-feedback control system has the open-

loop transfer function  $G(s) = \frac{4(1+2s)}{s^2(s+2)}$  if the input

to the system is a unit ramp, the steady-state error will be

- (a) 0
- (b) 0.5
- (c) 2
- (d) Infinity

[1991 : 2 Marks]

3.5 The poles of a continuous time oscillator are .....

[1994 : 1 Mark]

3.6 The response of an LCR circuit to a step input is

- (a) Over damped
  - (b) Critically damped
  - (c) Oscillatory
- If the transfer function has
- (1) poles on the negative real axis
  - (2) poles on the imaginary axis
  - (3) multiple poles on the positive real axis
  - (4) poles on the positive real axis
  - (5) Multiple poles on the negative real axis.

[1994 : 2 Marks]

3.7 Match the following codes with List-I with List-II:

#### List-I

- (a) Very low response at very high frequencies
- (b) Over shoot
- (c) Synchro-control transformer output

#### List-II

- (1) Low pass systems
- (2) Velocity damping
- (3) Natural frequency
- (4) Phase-sensitive modulation
- (5) Damping ratio.

[1994 : 2 Marks]

3.8 For a second order system, damping ratio ( $\xi$ ), is  $0 < \xi < 1$ , then the roots of the characteristic polynomial are

- (a) real but not equal
- (b) real and equal
- (c) complex conjugates
- (d) imaginary

[1995 : 1 M]

3.9 If  $L[f(t)] = \frac{2(s+1)}{s^2+2s+5}$  then  $f(0^+)$  and  $f(\infty)$  are

given by

- (a) 0, 2 respectively (b) 2, 0 respectively  
(c) 0, 1 respectively (d) 2/5, 0 respectively.

[Note : 'L' stands for 'Laplace Transform of']

[1995 : 1 M]

3.10 The step error coefficient of a system

$G(s) = \frac{1}{(s+6)(s+1)}$  with unity feedback is

- (a) 1/6 (b)  $\infty$   
(c) 0 (d) 1

[1995 : 1 M]

3.11 The final value theorem is used to find the

- (a) steady state value of the system output  
(b) initial value of the system output  
(c) transient behavior of the system output  
(d) none of these.

[1995 : 1 M]

#### 4. Stability Analysis

4.1 Consider a characteristic equation given by


$$s^4 + 3s^3 + 5s^2 + 6s + K + 10$$

The condition for stability is

- (a)  $K > 5$  (b)  $-10 < K$   
(c)  $K > -4$  (d)  $-10 < K < -4$

[1988 : 2 Marks]

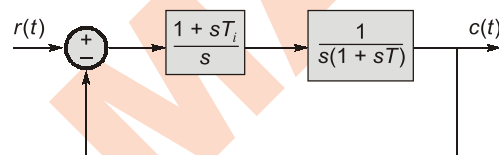4.2 In order to stabilize the system shown in figure  $T_i$  should satisfy,



- (a)  $T_i = -T$  (b)  $T_i = T$   
(c)  $T_i < T$  (d)  $T_i > T$

[1989 : 2 Marks]

4.3 An electromechanical closed-loop control system has the following characteristic equation;

$s^3 + 6Ks^2 + (K+2)s + 8 = 0$ . Where  $K$  is the forward gain of the system. The condition for closed loop stability is:

- (a)  $K = 0.528$  (b)  $K = 2$   
(c)  $K = 0$  (d)  $K = -2.258$

[1990 : 2 Marks]

4.4 If  $s^3 + 3s^2 + 4s + A = 0$ , then all the roots of this equation are in the left half plane provided that

- (a)  $A > 12$  (b)  $-3 < A < 4$   
(c)  $0 < A < 12$  (d)  $5 < A < 12$



[1993 : 2 Marks]

4.5 If  $G(s)$  is a stable transfer function, then  $F(s) = \frac{1}{G(s)}$  is always a stable transfer function. (T/F).

[1994 : 2 Marks]

#### 5. Root Locus

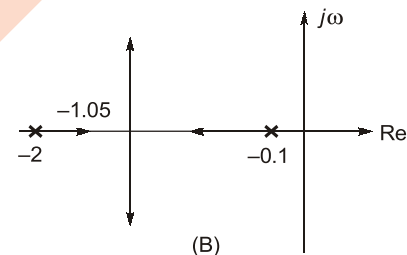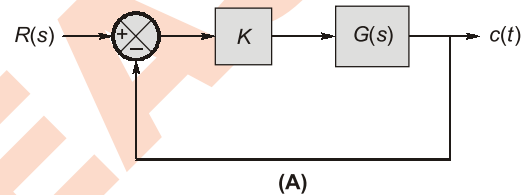5.1 Consider a closed-loop system shown in Figure (A) below. The root locus for it is shown in Figure (B). the closed loop transfer function for the system is



(a)  $\frac{K}{1 + (0.5s + 1)(10s + 1)}$

(b)  $\frac{K}{(s + 2)(s + 0.1)}$


(c)  $\frac{K}{1 + K(0.5s + 1)(10s + 1)}$




(d)  $\frac{K}{K + 0.2(0.5s + 1)(10s + 1)}$  [1988 : 2 Marks]

5.2 The OLTF of a feedback system is

$$G(s)H(s) = \frac{K(s+1)(s+3)}{s^2+4s+8}$$

The root locus for the same is

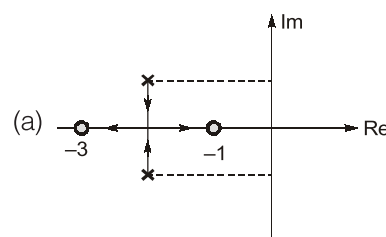


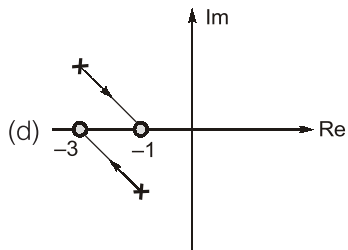
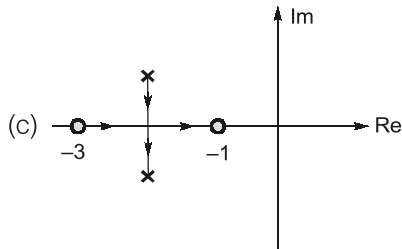
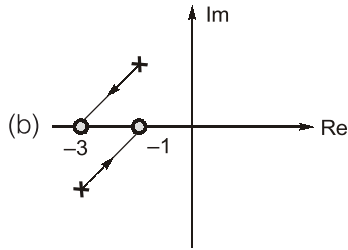


[1989 : 2 Marks]

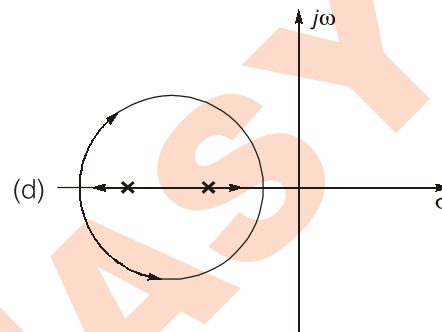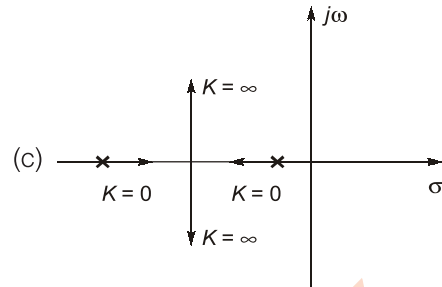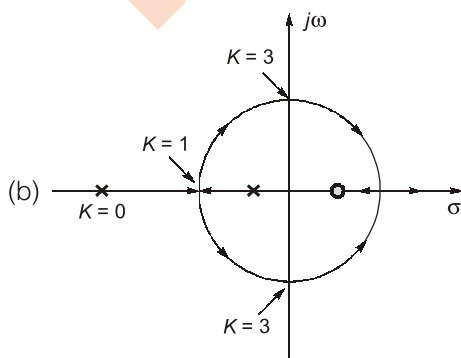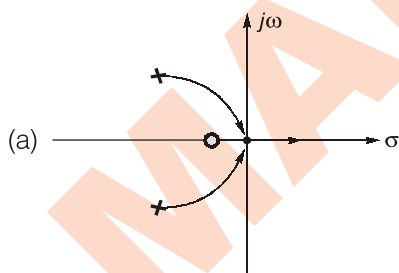5.3 The transfer function of a closed loop system is:

$$T(s) = \frac{K}{s^2 + (3 - K)s + 1}$$

Where  $K$  is the forward path gain. The root locus plot of the system is:



[1990 : 2 Marks]

5.4 The characteristic equation of a feedback control system is given by  $s^3 + 5s^2 + (K + 6)s + K = 0$  Where  $K > 0$  is a scalar variable parameter. In the root-locus diagram of the system the asymptotes of the root-loci for large values of  $K$  meet at a point in the  $s$ -plane, whose coordinates are


- (a)  $(-3, 0)$  (b)  $(-2, 0)$   
(c)  $(-1, 0)$  (d)  $(2, 0)$

[1991 : 2 Marks]



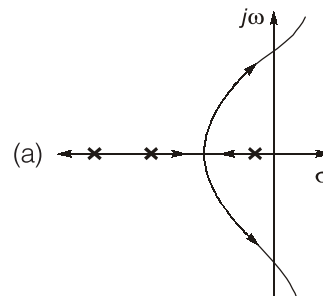
5.5 Given a unity feedback system with open-loop transfer function.

$$G(s) = \frac{K}{s(s+1)(s+2)}$$

The root locus plot of the system is of the form.





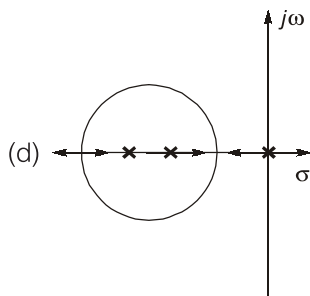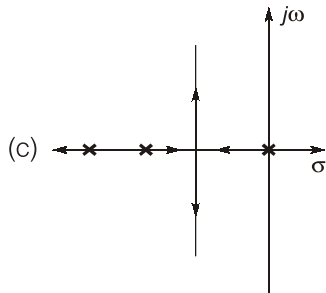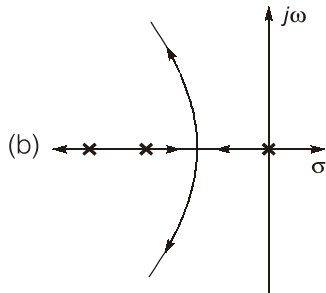

[1992 : 2 Marks]

5.6 If the open-loop transfer function is a ratio of a numerator polynomial of degree 'm' and a denominator polynomial of degree 'n' then the integer (n-m) represents the number of

- (a) breakaway points
- (b) unstable poles
- (c) separate root loci
- (d) asymptotes

[1994 : 1 Mark]

## 6. Frequency Response Analysis

6.1 A system has fourteen poles and two zeros. Its high frequency asymptote in its magnitude plot having a slope of:

- (a) -40 dB/decade
- (b) -240 dB/decade
- (c) -280 dB/decade
- (d) -320 dB/decade

[1987 : 2 Marks]

6.2 The polar plot of  $G(s) = \frac{10}{s(s+1)^2}$  intercepts real axis at  $\omega = \omega_0$ . Then, the real part and  $\omega_0$  are respectively given by:

- (a) -2.5, 1
- (b) -5, 0.5
- (c) -5, 1
- (d) -5, 2

[1987 : 2 Marks]

6.3 The open-loop transfer function of a feedback control system is


$$G(s) \cdot H(s) = \frac{1}{(s+1)^3}$$

The gain margin of the system is

- (a) 2
- (b) 4
- (c) 8
- (d) 16

[1991 : 2 Marks]

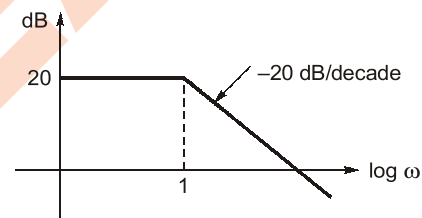6.4 Bode plot of a stable system is shown in figure. The transfer function of the system is



[1992 : 2 Marks]

6.5 The 3-dB bandwidth of a typical second-order system with the transfer function

$$\frac{C(s)}{R(s)} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}, \text{ is given by}$$

- (a)  $\omega_n \sqrt{1 - 2\xi^2}$
- (b)  $\omega_n \sqrt{(1 - \xi^2) + \sqrt{\xi^4 - \xi^2 + 1}}$
- (c)  $\omega_n \sqrt{(1 - 2\xi^2) + \sqrt{4\xi^4 - 4\xi^2 + 2}}$
- (d)  $\omega_n \sqrt{(1 - 2\xi^2) - \sqrt{4\xi^4 - 4\xi^2 + 2}}$

[1994 : 1 Mark]

6.6 The open loop frequency response of a system at two particular frequencies are given by :  $1.2 \angle -180^\circ$  and  $1.0 \angle -190^\circ$ . The closed loop unity feedback control is then \_\_\_\_\_

[1994 : 1 Mark]

- 6.7 The 3-dB bandwidth of a typical second-order system with the transfer function.

$$\frac{C(s)}{R(s)} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}, \text{ is given by}$$

- (a)  $\omega_n \sqrt{1 - 2\xi^2}$   
 (b)  $\omega_n \sqrt{(1 - \xi^2) + \sqrt{\xi^4 - \xi^2 + 1}}$   
 (c)  $\omega_n \sqrt{(1 - 2\xi^2) + \sqrt{4\xi^4 - 4\xi^2 + 2}}$   
 (d)  $\omega_n \sqrt{(1 - 2\xi^2) - \sqrt{4\xi^4 - 4\xi^2 + 2}}$  [1995 : 1 M]

- 6.8 Non-minimum phase transfer function is defined as the transfer function

- (a) which has zeros in the right-half  $s$ -plane  
 (b) which has zeros only in the left-half  $s$ -plane  
 (c) which has poles in the right-half  $s$ -plane  
 (d) which has poles in the left-half  $s$ -plane

[1995 : 1 M]

## 7. State Space Analysis

- 7.1 Given the following state-space description of a system

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -2 & 0 \\ 0 & -4 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u$$

$$y = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

Find the state-transition matrix.

[1988 : 2 Marks]

- 7.2 A linear second-order single-input continuous-time system is described by following set of differential equations

$$\dot{x}_1(t) = -2x_1(t) + 4x_2(t);$$

$$\dot{x}_2(t) = 2x_1(t) - x_2(t) + u(t)$$

Where  $x_1(t)$  and  $x_2(t)$  are the state variables and  $u(t)$  is the control variable. The system is

- (a) controllable and stable  
 (b) controllable but unstable  
 (c) uncontrollable and unstable  
 (d) uncontrollable but stable. [1991 : 2 Marks]

- 7.3 A linear time-invariant system is described by the state variable model

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -1 & 0 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u.$$

$$Y = \begin{bmatrix} 1 & 2 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

- (a) The system is completely controllable  
 (b) The system is not completely controllable  
 (c) The system is completely observable  
 (d) The system is not completely observable

[1992 : 2 Marks]

■■■

**Answers Control Systems**

1.1 (d)	1.2 (b)	1.3 (c)	1.4 (d)	1.5 (c)	1.6 (c)	2.1 (d)
2.2 (b, c)	2.3 (True)	3.1 (a)	3.2 (b)	3.3 (a)	3.4 (a)	3.5 (sol.)
3.6 (sol.)	3.7 (sol.)	3.8 (c)	3.9 (b)	3.10 (a)	3.11 (a)	4.1 (d)
4.2 (d)	4.3 (b)	4.4 (c)	4.5 (False)	5.1 (d)	5.2 (a)	5.3 (a)
5.4 (b)	5.5 (a)	5.6 (d)	6.1 (b)	6.2 (c)	6.3 (c)	6.4 (sol.)
6.5 (c)	6.6 (-10)	6.7 (c)	6.8 (a) & (c)	7.1 Sol.	7.2 (b)	7.3 (b, c)

**Explanations Control Systems****1. Basics of Control Systems, Block Diagram and SFG's****1.1 (d)**

$$\frac{X_2}{X_1} = \frac{5}{\Delta} = \frac{5}{1 - (0.5)} = \frac{5}{0.5} = 10$$

**1.2 (b)**

$$\frac{C(s)}{R(s)} = \frac{\frac{10}{s(s+1)}}{1 + \frac{10}{s(s+1)} \times s}$$

$$= \frac{\frac{10}{s(s+1)}}{1 + \frac{10s}{s(s+1)}} \times 1$$

$$= \frac{10}{s(s+1) + 10s}$$

$$\frac{C(s)}{R(s)} = \frac{10}{s^2 + 11s + 10}$$

**1.3 (c)**

By using Masson's gain formulae

$$\frac{C}{R} = \frac{P_K \Delta_K}{\Delta}$$

$$\frac{C}{R} = \frac{G_1 G_2 G_3 G_4}{1 - [-G_1 - G_2 - G_3 - G_4] + [G_1 G_3 + G_1 G_4 + G_2 G_3 + G_2 G_4]}$$

$$\frac{C}{R} = \frac{G_1 G_2 G_3 G_4}{1 + G_1 + G_2 + G_3 + G_4 + G_1 G_3 + G_1 G_4 + G_2 G_3 + G_2 G_4}$$

$$\frac{C}{R} = \frac{G_1 G_2 G_3 G_4}{(1 + G_1 + G_2)(1 + G_3 + G_4)}$$

**1.4 (d)**

By using Masson's gain formulae,

$$\frac{C}{R} = \frac{\Sigma P_K \Delta_K}{\Delta}$$

$$\frac{C}{R} = \frac{(1 \times 2 \times 3 \times 4 \times 1) + (1 \times 5 \times 1) \times (1 + 3)}{1 - (-2 - 3 - 4 - 5) + (-2) \times (-4)}$$

$$\frac{C}{R} = \frac{24 + 20}{1 + 14 + 8} = \frac{44}{23}$$

**1.5 (c)**

The signal flow graph can not be used to comment on stability, controllability, observability or pole zero locations. It only gives transfer function.

**1.6 (c)**

The transfer function of a linear time invariant system is defined as the ratio of the Laplace transform of the output and that of the input with all initial conditions zero.

**2. Compensators and Controllers****2.1 (d)**

$$\theta = \tan^{-1}\left(\frac{\omega}{z_1}\right) - \tan^{-1}\left(\frac{\omega}{p_1}\right)$$

For phase lead controller

$$\theta > 0$$

$$\tan^{-1}\left(\frac{\omega}{z_1}\right) - \tan^{-1}\left(\frac{\omega}{p_1}\right) > 0$$

$$\tan^{-1}\left(\frac{\omega}{z_1}\right) > \tan^{-1}\left(\frac{\omega}{p_1}\right)$$

$$p_1 > z_1$$

**2.2 (b, c)**

The integral mode improves steady state performance and the derivative mode improves the transient performance.

**2.3 (True)**

The tachometer feedback is a derivative feedback. So, tachometer adds zero at origin. Hence, type decreases and stability is improved (True).

**3. Time Response Analysis****3.1 (a)**

$$K_p = \lim_{s \rightarrow 0} G(s)H(s) = \lim_{s \rightarrow 0} \frac{K}{s(s+10)} = \infty$$

$$e_{ss} = \frac{A}{1+K_p} = \frac{A}{1+\infty} = 0$$

**3.2 (b)**

The steady state error of a stable 'type 0' unity feedback system for a unit step function is  $\frac{1}{1+K_p}$ .

**3.3 (a)**

$$\omega_n^2 = 25$$

$$\omega_n = 5$$

$$2\xi\omega_n = 8$$

$$\xi = \frac{8}{2\omega_n} = \frac{4}{5} = 0.8$$

$$\omega_d = \omega_n \sqrt{1-\xi^2} = 5\sqrt{1-(0.8)^2} = 3$$

For 2<sup>nd</sup> peak  $n = 3$

$$t_p = \frac{n\pi}{\omega_d} = \frac{3\pi}{3} = \pi \text{ sec.}$$

**3.4 (a)**

$$K_V = \lim_{s \rightarrow 0} sG(s)H(s) = \lim_{s \rightarrow 0} \frac{s4(1+2s)}{s^2(s+2)}$$

$$= \lim_{s \rightarrow 0} \frac{4(1+2s)}{s(s+2)} = \infty$$

$$e_{ss} = \frac{A}{K_V} = \frac{A}{\infty} = 0$$

**3.5 Sol.**

The poles of a continuous time oscillator are pure imaginary.

**3.6 Sol.**

a - 1, b - 5, c - 2.

(a) Overdamped  $\rightarrow$  (1) poles on the negative real axis  $\xi > 1$ .

$$s = -\xi\omega_n \pm \omega_n\sqrt{\xi^2 - 1}$$

(b) Critically damped  $\rightarrow$  (5) Multiple poles on the negative real axis.

$$\xi = 1$$

$$s = -\omega_n, -\omega_n$$

(c) Oscillatory  $\rightarrow$  (2) Poles on the imaginary axis.

$$\xi = 0$$

$$s = \pm j\omega_n$$

**3.7 Sol.**

(a) - 1, (b) - 5, (c) - 4.

(a) Very low response at very high frequencies  $\rightarrow$  Low pass system.

(b) Overshoot  $\rightarrow$  Damping ratio.

(c) Synchro-control transformer output  $\rightarrow$  Phase-sensitive modulation.

**3.8 (c)**

$$\xi < 1$$

For underdamped system, roots or poles are:

$$s = -\xi\omega_n \pm j\omega_n\sqrt{1-\xi^2}$$

**3.9 (b)**

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s) = \frac{2s^2 + 2s}{s^2 + 2s + 5} = 2$$

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \frac{2s^2 + 2s}{s^2 + 2s + 5} = 0$$

**3.10 (a)**

$$K_p = \lim_{s \rightarrow 0} G(s)H(s)$$

$$= \lim_{s \rightarrow 0} \frac{1}{(s+6)(s+1)} = \frac{1}{6}$$

**3.11 (a)**

The final value theorem is used to find the steady state value of the system.

**4. Stability Analysis****4.1 (d)**

Using R-H criterion:

$$\begin{array}{l|lll}
 s^4 & 1 & 5 & K+10 \\
 s^3 & 3 & 6 & 0 \\
 s^2 & 3 & K+10 & 0 \\
 s^1 & \frac{-12-3K}{3} & 0 & 0 \\
 s^0 & K+10 & & 
 \end{array}$$

For stable system, all the coefficients of 1<sup>st</sup> column should be positive.

$$\text{So, } \frac{-12-3K}{3} > 0$$

$$-12 - 3K > 0$$

$$-12 > +3K$$

$$-4 > K$$

$$\text{and } K+10 > 0$$

$$K > -10$$

So, the range of  $K$

$$-10 < K < -4$$

#### 4.2 (d)

Characteristic equation

$$1 + GH = 0$$

$$1 + \frac{(1+sT_i)}{s} \times \frac{1}{s(1+sT)} \times 1 = 0$$

$$s^2(1+sT) + (1+sT_i) = 0$$

$$s^3T + s^2 + sT_i + 1 = 0$$

Using R-H method

$$\begin{array}{l|ll}
 s^3 & T & T_i \\
 s^2 & 1 & 1 \\
 s^1 & T_i - T & \\
 s^0 & 1 & 
 \end{array}$$

For stability, 1<sup>st</sup> column should be positive.

$$\text{So, } T_i - T > 0$$

$$T_i > T$$

#### 4.3 (b)

$$s^3 + 6Ks^2 + (K+2)s + 8 = 0$$

Using R-H criteria

$$\begin{array}{l|ll}
 s^3 & 1 & K+2 \\
 s^2 & 6K & 8 \\
 s^1 & \frac{6K^2 + 12K - 8}{6K} & 0 \\
 s^0 & 8 & 
 \end{array}$$

For stable system, 1<sup>st</sup> column element should be positive.

$$\frac{6K^2 + 12K - 8}{6K} > 0$$

$$6K^2 + 12K - 8 > 0$$

$$3K^2 + 6K - 4 > 0$$

$$K = \frac{-6 \pm \sqrt{36 + 48}}{6} = -2.528, +0.528$$

$$K > 0.528$$

$$K > -2.528$$

So,  $K > 0.528$

So, from given option for

$K = 2$  system will be stable.

#### 4.4 (c)

$$s^3 + 3s^2 + 4s + A = 0$$

Using R-H criteria

$$\begin{array}{l|ll}
 s^3 & 1 & 4 \\
 s^2 & 3 & A \\
 s^1 & \frac{12-A}{3} & 0 \\
 s^0 & A & 
 \end{array}$$

For stable system

$$A > 0$$

$$\text{and } \frac{12-A}{3} > 0$$

$$12 - A > 0$$

$$12 > A$$

$$0 < A < 12$$

#### 4.5 (False)

$$\text{T.F. of } G(s) = \frac{(s+Z_1)(s+Z_2)}{(s+P_1)(s+P_2)}$$

$$\text{T.F. of } F(s) = \frac{(s+P_1)(s+P_2)}{(s+Z_1)(s+Z_2)}$$

The condition for stability is that none of the pole of  $G(s)$  should be on the right half of  $s$ -plane, but  $G(s)$  may have zeros in the right half of  $s$ -plane. These zeros become pole of  $F(s)$ . Therefore the  $F(s)$  need not be stable (**False**).

## 5. Root Locus

#### 5.1 (d)

$$G(s) = \frac{1}{(s+0.1)(s+2)}$$

$$\text{T.F.} = \frac{K \cdot G(s)}{1 + KG(s)}$$

$$\begin{aligned} \text{T.F.} &= \frac{K}{(s+0.1)(s+2)} \\ &= \frac{K}{1 + \frac{K}{(s+0.1)(s+2)}} \\ \text{T.F.} &= \frac{K}{(s+0.1)(s+2) + K} \\ \text{T.F.} &= \frac{K}{K + 0.2(1+10s)(1+0.5s)} \end{aligned}$$

**5.2 (a)**

(b) & (d) options are wrong, because root locus is symmetrical about real axis.

Option (c) is wrong because root locus directions are from pole to zeros.

**5.4 (b)**

$$\begin{aligned} \text{O.L.T.F.} &= G(s)H(s) = \frac{K(s+1)}{s^3 + 5s^2 + 6s} \\ &= \frac{K(s+1)}{s(s^2 + 5s + 6)} \\ G(s)H(s) &= \frac{K(s+1)}{s(s+2)(s+3)} \\ \text{Poles} &\rightarrow 0, -2, -3 \\ \text{Zeros} &\rightarrow -1 \\ \text{Centroid} &= \frac{(-2-3)-(-1)}{3-1} \\ &= \frac{-5+1}{2} = -2 = (-2, 0) \end{aligned}$$

**5.5 (a)**

$$\begin{aligned} P &= 3 \\ z &= 0 \\ P - z &= 3 - 0 = 3 \\ \theta &= \frac{(2q+1)180^\circ}{P-z} \\ \theta &= 60^\circ, 180^\circ, 300^\circ \end{aligned}$$

So, only option (a) satisfy this.

**5.6 (d)**

(n - m)  
difference between poles and zeros gives number of asymptotes.

**6. Frequency Response Analysis****6.1 (b)**

$$\begin{aligned} P &= 14 \\ z &= 2 \end{aligned}$$

$$\begin{aligned} P - z &= 14 - 2 = 12 \\ \text{Slope} &= -20(P - z) = -20(12) \\ &= -240 \text{ dB/decade} \end{aligned}$$

**6.2 (c)**

$$\begin{aligned} G(s) &= \frac{10}{s(s+1)^2} \\ \angle G &= -180^\circ = -90^\circ - 2\tan^{-1}(\omega) \\ 2\tan^{-1}(\omega) &= 45^\circ \\ \omega &= 1 \\ \omega_{pc} &= 1 \text{ rad/sec.} \\ |G|_{\omega=\omega_{pc}} &= \frac{10}{\omega(1+\omega^2)} = \frac{10}{1(1+1)} = 5 \end{aligned}$$

At  $\omega = \omega_{pc}$  the polar plot crosses the negative real axis at -5.

**6.3 (c)**

$$\begin{aligned} \omega_{pc} &\Rightarrow \\ -3\tan^{-1}(\omega_{pc}) &= -180^\circ \\ \tan^{-1}(\omega_{pc}) &= 60^\circ \\ \omega_{pc} &= \sqrt{3} \text{ rad/sec.} \\ |G.H.| &= X = \frac{1}{(\sqrt{1+\omega_{pc}^2})} \\ &= \frac{1}{(\sqrt{1+(\sqrt{3})^2})} = \frac{1}{2} \\ \text{G.M.} &= \frac{1}{X} = 2 \end{aligned}$$

**6.4 Sol.**

Corner frequency = 1 rad/sec.

$$\begin{aligned} \frac{1}{T} &= 1 \\ T &= 1 \\ y &= mX + C \\ 20 &= 0 + C \\ C &= 20 \\ C &= 20 \log(k) = 20 \\ \log(k) &= 1 \\ k &= 10 \\ \text{T.F.} &= \frac{k}{(1+Ts)} = \frac{10}{(1+s)} \end{aligned}$$

**6.5 (c)**

$$\omega_n \sqrt{(1-2\xi^2) + \sqrt{4\xi^4 - 4\xi^2 + 2}}$$

**6.6 (-10)**

At  $180^\circ \rightarrow |GH| = 1.2$

$$\text{G.M.} = 20 \log \left( \frac{1}{|GH|} \right) = 20 \log \left( \frac{1}{1.2} \right)$$

$$= -1.6 \text{ dB}$$

At  $|GH| = 1 \rightarrow \phi = -190^\circ$

$$\text{P.M.} = 180^\circ + \phi$$

$$= 180^\circ - 190^\circ = -10^\circ$$

Since both G.M. and P.M. are negative.

So, the system is unstable.

**6.7 (c)**

Given that

$$\text{Transfer function, } H(s) = \frac{C(s)}{R(s)} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

Put  $s = j\omega$

$$H(j\omega) = \frac{\omega_n^2}{(j\omega)^2 + 2\xi\omega_n(j\omega) + \omega_n^2}$$

$$= \frac{\omega_n^2}{(\omega_n^2 - \omega^2) + j2\xi\omega_n \omega}$$

$$H(j\omega) = \frac{1}{\left(1 - \frac{\omega^2}{\omega_n^2}\right) + j\frac{2\xi\omega}{\omega_n}}$$

$$\text{Let } x = \frac{\omega}{\omega_n}$$

$$H(j\omega) = \frac{1}{(1 - x^2) + j2\xi x}$$

$$|H(j\omega)| = \frac{1}{\sqrt{(1 - x^2)^2 + (2\xi x)^2}}$$

$$\text{at 3dB frequency } H(j\omega_c) = \frac{1}{\sqrt{2}}$$

$$\text{So, } \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(1 - x^2)^2 + (2\xi x)^2}}$$

$$\sqrt{(1 - x^2)^2 + (2\xi x)^2} = \sqrt{2}$$

$$(1 - x^2)^2 + (2\xi x)^2 = 2$$

$$1 + x^4 - 2x^2 + 4\xi^2 x^2 = 2$$

$$x^4 - 2x^2 + 4\xi^2 x^2 = 1$$

$$x^4 + x^2(4\xi^2 - 2) - 1 = 0$$

$$x^2 = \frac{-(4\xi^2 - 2) \pm \sqrt{(4\xi^2 - 2)^2 - 4(1)(-1)}}{2}$$

$$x^2 = (1 - 2\xi^2) \pm \sqrt{4\xi^4 - 4\xi^2 + 2}$$

$$x = \sqrt{(1 - 2\xi^2) \pm \sqrt{4\xi^4 - 4\xi^2 + 2}} = \frac{\omega_c}{\omega_n}$$

$$\frac{\omega_c}{\omega_n} = \sqrt{(1 - 2\xi^2) \pm \sqrt{4\xi^4 - 4\xi^2 + 2}}$$

$$\omega_c = \omega_n \sqrt{(1 - 2\xi^2) \pm \sqrt{4\xi^4 - 4\xi^2 + 2}}$$

Since  $\omega_c$  cannot be negative.

$$\omega_c = \omega_n \sqrt{(1 - 2\xi^2) + \sqrt{4\xi^4 - 4\xi^2 + 2}}$$

**6.8 (a) & (c)**

The non-minimum phase transfer function is defined as the transfer function which has zeros (or) poles in right side of s-plane.

**7. State Space Analysis****7.1 Sol.**

$$A = \begin{bmatrix} -2 & 0 \\ 0 & -4 \end{bmatrix}$$

$$sI - A = \begin{bmatrix} s+2 & 0 \\ 0 & s+4 \end{bmatrix}$$

$$[sI - A]^{-1} = \frac{1}{(s+2)(s+4)} \begin{bmatrix} s+4 & 0 \\ 0 & s+2 \end{bmatrix}$$

$$[sI - A]^{-1} = \begin{bmatrix} \frac{1}{s+2} & 0 \\ 0 & \frac{1}{s+4} \end{bmatrix}$$

State transition matrix

$$\phi(t) = e^{At} = L^{-1}\{[sI - A]^{-1}\}$$

$$\phi(t) = e^{At} = \begin{bmatrix} e^{-2t} & 0 \\ 0 & e^{-4t} \end{bmatrix}$$

**7.2 (b)**

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -2 & 4 \\ +2 & -1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u(t)$$

$$Q_c = [B \ AB]$$

$$B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$AB = \begin{bmatrix} -2 & 4 \\ +2 & -1 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 4 \\ -1 \end{bmatrix}$$

$$Q_c = \begin{bmatrix} 0 & 4 \\ 1 & -1 \end{bmatrix}$$

$$|Q_c| = 0 - 4 = -4 \neq 0$$

Hence the given system is controllable.

Characteristic equation

$$[sI - A] = 0$$

$$\begin{bmatrix} s+2 & -4 \\ -2 & s+1 \end{bmatrix} = 0$$

$$(s+2)(s+1) - 8 = 0$$

$$s^2 + 3s - 6 = 0$$

$$s = \frac{-3 \pm \sqrt{9+24}}{2}$$

$$s = -4.37, 1.37$$

Since 1 pole lie in R.H.S. of s-plane.

So, the given system is unstable.

### 7.3 (b) & (c)

$$A = \begin{bmatrix} -1 & 0 \\ 0 & -2 \end{bmatrix}$$

$$B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$AB = \begin{bmatrix} -1 & 0 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ -2 \end{bmatrix}$$

$$Q_c = [B \ AB]$$

$$Q_c = \begin{bmatrix} 0 & 0 \\ 1 & -2 \end{bmatrix}$$

$$|Q_c| = 0 - 0 = 0$$

So, the given system is not completely controllable.

$$A^T = \begin{bmatrix} -1 & 0 \\ 0 & -2 \end{bmatrix}$$

$$C = [1 \ 2]$$

$$C^T = \begin{bmatrix} 1 \\ 2 \end{bmatrix}$$

$$A^T C^T = \begin{bmatrix} -1 & 0 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 1 \\ 2 \end{bmatrix} = \begin{bmatrix} -1 \\ -4 \end{bmatrix}$$

$$Q_o = [C^T \ A^T C^T]$$

$$Q_o = \begin{bmatrix} 1 & -1 \\ 2 & -4 \end{bmatrix}$$

$$|Q_o| = -4 - (-2) = -2 \neq 0$$

So, the given system is completely observable.

(b) The system is not completely controllable.

(c) The system is completely observable.

■■■



# Electronic Devices and Circuits

## UNIT IV

### CONTENTS

1. Basic Semiconductor Physics **38**
2. PN-Junction Diodes and Special Diodes **39**
3. BJT and FET Basics **40**

# IV

# Electronic Devices and Circuits

## 1. Basic Semiconductor Physics

- 1.1 Consider two energy levels:  $E_1$ ,  $E$  eV above the Fermi level and  $E_2$ ,  $E$  eV below the Fermi level.  $P_1$  and  $P_2$  are respectively the probabilities of  $E_1$  being occupied by an electron and  $E_2$  being empty. Then
- $P_1 > P_2$
  - $P_1 = P_2$
  - $P_1 < P_2$
  - $P_1$  and  $P_2$  depend on number of free electrons

[1987 : 2 Marks]

- 1.2 In an intrinsic semiconductor the free electron concentration depends on
- effective mass of electrons only
  - effective mass of holes only
  - temperature of the semiconductor
  - width of the forbidden energy band of the semiconductor

[1987 : 2 Marks]

- 1.3 According to the Einstein relation, for any semiconductor the ratio of diffusion constant to mobility of carriers
- depends upon the temperature of the semiconductor
  - depends upon the type of the semiconductor
  - varies with life time of the semiconductor
  - is a universal constant

[1987 : 2 Marks]

- 1.4 Direct band gap semiconductors
- exhibit short carrier life time and they are used for fabricating BJT's
  - exhibit long carrier life time and they are used for fabricating BJT's
  - exhibit short carrier life time and they are used for fabricating lasers
  - exhibit long carrier life time and they are used for fabricating lasers

[1987 : 2 Marks]

- 1.5 Due to illumination by light, the electron and hole concentrations in a heavily doped  $N$  type semiconductor increases by  $\Delta n$  and  $\Delta p$  respectively if  $n_i$  is the intrinsic concentration then,

- $\Delta n < \Delta p$
- $\Delta n > \Delta p$
- $\Delta n = \Delta p$
- $\Delta n \times \Delta p = n_i^2$

[1989 : 2 Marks]

- 1.6 The concentration of ionized acceptors and donors in a semiconductor are  $N_A$ ,  $N_D$  respectively. If  $N_A > N_D$  and  $n_i$  is the intrinsic concentration, the position of the Fermi level with respect to the intrinsic level depends on

- $N_A - N_D$
- $N_A + N_D$
- $\frac{N_A N_D}{n_i^2}$
- $n_i$

[1989 : 2 Marks]

- 1.7 Under high electric fields, in a semiconductor with increasing electric field,

- the mobility of charge carriers decreases
- the mobility of the carriers increases
- the velocity of the charge carriers saturates
- the velocity of the charge carriers increases

[1990 : 2 Marks]

- 1.8 A silicon sample is uniformly doped with  $10^{16}$  phosphorus atoms/cm<sup>3</sup> and  $2 \times 10^{16}$  boron atoms/cm<sup>3</sup>. If all the dopants are fully ionized, the material is

- $n$ -type with carrier concentration of  $10^{16}$ /cm<sup>3</sup>
- $p$ -type with carrier concentration of  $10^{16}$ /cm<sup>3</sup>
- $p$ -type with carrier of  $2 \times 10^{16}$ /cm<sup>3</sup>
- $n$ -type with a carrier concentration of  $2 \times 10^{16}$ /cm<sup>3</sup>

[1991 : 2 Marks]

- 1.9 A semiconductor is irradiated with light such that carriers are uniformly generated throughout its volume. The semiconductor is  $n$ -type with  $N_D = 10^{19}$ /cm<sup>3</sup>. If the excess electron concentration in the steady state is  $\Delta n = 10^{15}$ /cm<sup>3</sup> and if  $\tau_p = 10 \mu\text{sec}$ . (minority carrier life time) the generation rate due to irradiation

- is  $10^{20}$   $e-h$  pairs/cm<sup>3</sup>/s
- is  $10^{24}$   $e-h$  pairs/cm<sup>3</sup>/s
- is  $10^{10}$   $e-h$  pairs/cm<sup>3</sup>/s
- cannot be determined, the given data is insufficient

[1992 : 2 Marks]

1.10 A  $p$ -type silicon sample has a higher conductivity compared to an  $n$ -type silicon sample having the same dopant concentration. (True/False)

[1994 : 1 Mark]

1.11 The drift velocity of electrons, in silicon

- (a) is proportional to the electric field for all values of electric field
- (b) is independent of the electric field.
- (c) increases at low values of electric field and decreases at high values of electric field exhibiting negative differential resistance.
- (d) increases linearly with electric field at low values of electric field and gradually saturates at higher values of electric field.

[1995 : 1 M]

1.12 The probability that an electron in a metal occupies the fermi level, at any temperature. ( $T > 0K$ )

- (a) 0
- (b) 1
- (c) 0.5
- (d) 1.0

[1995 : 1 M]

1.13 In a  $p$ -type Si sample the hole concentration is  $2.25 \times 10^{15}/\text{cm}^3$ . The intrinsic carrier concentration is  $1.5 \times 10^{10}/\text{cm}^3$  the electron concentration is

- (a) zero
- (b)  $10^{10}/\text{cm}^3$
- (c)  $10^5/\text{cm}^3$
- (d)  $1.5 \times 10^{25}/\text{cm}^3$

[1995 : 1 M]

1.14 A small concentration of minority carries is injected into a homogeneous semiconductor crystal at one point. An electric field of 10 V/cm is applied across the crystal and this moves the minority carries a distance of 1 cm in 20  $\mu\text{sec}$ . The mobility (in  $\text{cm}^2/\text{V-sec}$ ) will be

- (a) 1,000
- (b) 2,000
- (c) 5,000
- (d) 500,000

[1995 : 1 M]

## 2. PN-Junction Diodes and Special Diodes

2.1 The diffusion capacitance of a  $p$ - $n$  junction

- (a) decreases with increasing current and increasing temperature
- (b) decreases, with decreasing current and increasing temperature
- (c) increases with increasing current and increasing temperature
- (d) does not depend on current and temperature

[1987 : 2 Marks]


2.2 For a  $pn$ -junction match the type of breakdown with phenomenon

- 1. Avalanche breakdown
- 2. Zener breakdown
- 3. Punch through
- A. Collision of carriers with crystal ions
- B. Early effect
- C. Rupture of covalent bond due to strong electric field.

- (a) 1-B, 2-A, 3-C
- (b) 1-C, 2-A, 3-B
- (c) 1-A, 2-B, 3-C
- (d) 1-A, 2-C, 3-B

[1988 : 2 Marks]

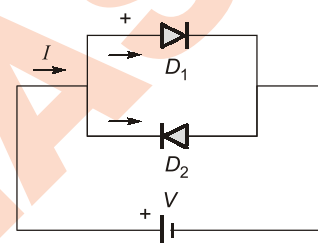2.3 In the circuit shown below the current voltage relationship when  $D_1$  and  $D_2$  are identical is given by (Assume Ge diodes)



- (a)  $V = \frac{kT}{q} \sinh\left(\frac{I}{2}\right)$
- (b)  $V = \frac{kT}{q} \ln\left(\frac{I}{I_0}\right)$
- (c)  $V = \frac{kT}{q} \sinh^{-1}\left(\frac{I}{2}\right)$
- (d)  $V = \frac{kT}{q} [\exp(-I) - 1]$

[1988 : 2 Marks]

2.4 The switching speed of  $P^+N$  junction (having a heavily doped  $P$  region) depends primarily on

- (a) the mobility of minority carriers in the  $P^+$ -region.
- (b) the lifetime of minority carriers in the  $P^+$ -region
- (c) the mobility of majority carriers in the  $N$ -region
- (d) the lifetime of majority carriers in the  $N$ -region

[1989 : 2 Marks]

2.5 In a Zener diode

- (a) only the  $P$ -region is heavily doped
- (b) only the  $N$ -region is heavily doped
- (c) both  $P$  and  $N$ -regions are heavily doped
- (d) both  $P$  and  $P$ -regions are lightly doped

[1989 : 2 Marks]

- 2.6 In a junction diode
- (a) the depletion capacitance increases with increase in the reverse bias
  - (b) the depletion capacitance decreases with increase in the reverse bias
  - (c) the depletion capacitance increases with increase in the forward bias
  - (d) the depletion capacitance is much higher than the depletion capacitance when it is forward biased

[1990 : 1 Mark]


- 2.7 In a uniformly doped abrupt  $p$ - $n$  junction the doping level of the  $n$ -side is four(4) times the doping level of the  $p$ -side the ratio of the depletion layer width of  $n$ -side versus  $p$ -side is
- (a) 0.25
  - (b) 0.5
  - (c) 1.0
  - (d) 2.0

[1990 : 2 Marks]

- 2.8 The small signal capacitance of an abrupt  $P^+n$  junction is  $1 \text{ nF/cm}^2$  at zero bias. If the built-in voltage is 1 volt, the capacitance at a reverse bias voltage of 99 volts is
- (a) 10
  - (b) 0.1
  - (c) 0.01
  - (d) 100

[1991 : 2 Marks]

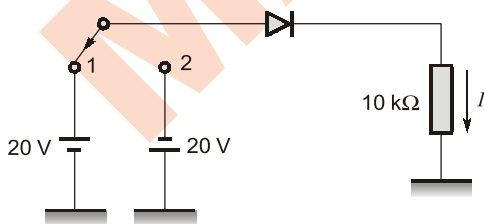- 2.9 Referring to the below figure the switch  $S$  is in position 1 initially and steady state condition exist from time  $t = 0$  to  $t = t_0$ , the switch is suddenly thrown into position 2. The current  $I$  through the  $10 \text{ K}$  resistor as a function of time  $t$ , from  $t = 0$  is? (give the sketch showing the magnitudes of the current at  $t = 0$ ,  $t = t_0$  and  $t = \infty$ ).



[1991 : 2 Marks]

- 2.10 The built-in potential (diffusion potential) in a  $p$ - $n$  junction
- (a) is equal to the difference in the Fermi-level of the two sides, expressed in volts
  - (b) increases with the increase in the doping levels of the two sides

- (c) increases with the increase in temperature
- (d) is equal to the average of the Fermi levels of the two sides

[1993 : 2 Marks]

- 2.11 The diffusion potential across a  $p$ - $n$  junction
- (a) decreases with increasing doping concentration
  - (b) increases with decreasing band gap
  - (c) does not depend on doping concentrations
  - (d) increases with increase in doping concentration

[1995 : 1 M]

- 2.12 A Zener diode works on the principle of
- (a) tunneling of charge carriers across the junction
  - (b) thermionic emission
  - (c) diffusion of charge carriers across the junction
  - (d) hopping of charge carriers across the junction

[1995 : 1 M]

- 2.13 The depletion capacitance,  $C_j$  of an abruptly  $p$ - $n$  junction with constant doping on either side varies with R.B.  $V_R$  as

- (a)  $C_j \propto V_R$
- (b)  $C_j \propto V_R^{-1}$
- (c)  $C_j \propto V_R^{-1/2}$
- (d)  $C_j \propto V_R^{-1/3}$

[1995 : 1 M]

### 3. BJT and FET Basics

- 3.1 The pinch off voltage for a  $n$ -channel JFET is 4 V, when  $V_{GS} = 1 \text{ V}$ , the pinch-off occurs for  $V_{DS}$  equal to
- (a) 3 V
  - (b) 5 V
  - (c) 4 V
  - (d) 1 V

[1987 : 2 Marks]

- 3.2 In an  $n$ -channel JFET,  $V_{GS}$  is held constant.  $V_{DS}$  is less than the breakdown voltage. As  $V_{DS}$  is increased
- (a) conducting cross-sectional area of the channel 'S' and the channel current density 'J' both increase
  - (b) 'S' decrease and 'J' decrease
  - (c) 'S' decreases and 'J' increase
  - (d) 'S' increases and 'J' decreases

[1988 : 2 Marks]

- 3.3 In MOSFET devices the  $n$ -channel type is better than the  $P$ -channel type in the following respects
- (a) it has better noise immunity
  - (b) it is faster
  - (c) it is TTL compatible
  - (d) it has better drive capability

[1988 : 2 Marks]

- 3.4** In a MOSFET, the polarity of the inversion layer is the same as that of the  
 (a) charge on the gate electrode  
 (b) minority carriers in the drain  
 (c) majority carriers in the substrate  
 (d) majority carriers in the source  
**[1989 : 2 Marks]**
- 3.5** The 'Pinch-off' voltage of a JFET is 5.0 volts, Its 'cut-off' voltage is  
 (a)  $(5.0)^{1/2}$  V (b) 2.5 V  
 (c) 5.0 V (d)  $(5.0)^{3/2}$  V  
**[1990 : 2 Marks]**
- 3.6** Which of the following effects can be caused by a rise in the temperature?  
 (a) increase in MOSFET current ( $I_{DS}$ )  
 (b) increase in BJT current ( $I_C$ )  
 (c) decrease in MOSFET current ( $I_{DS}$ )  
 (d) decrease in BJT current ( $I_C$ )  
**[1990 : 2 Marks]**
- 3.7** In a transistor having finite  $\beta$ , forward bias across the base emitter junction is kept constant and the reverse bias across the collector base junction is increased. Neglecting the leakage across the collector base junction and the depletion region generations current, the base current will \_\_\_\_ (increase/decrease/remains constant).  
**[1992 : 2 Marks]**
- 3.8** An n-channel JFET has a pinch-off voltage  $V_p = -5$  V,  $V_{DS}(\text{max}) = 20$  V, and  $g_m = 2$  mA/V. The min 'ON' resistance is achieved in the JFET for  
 (a)  $V_{GS} = -7$  V and  $V_{DS} = 0$  V  
 (b)  $V_{GS} = 0$  V and  $V_{DS} = 0$  V  
 (c)  $V_{GS} = 0$  V and  $V_{DS} = 20$  V  
 (d)  $V_{GS} = -7$  V and  $V_{DS} = 20$  V  
**[1992 : 2 Marks]**
- 3.9** The threshold voltage of an n-channel MOSFET can be increased by  
 (a) increasing the channel dopant concentration  
 (b) reducing the channel dopant concentration  
 (c) reducing the gate oxide thickness  
 (d) reducing the channel length  
**[1994 : 1 Mark]**
- 3.10** The transit time of the current carries through the channel of a JFET decides its \_\_\_\_\_ characteristic  
 (a) source (b) drain  
 (c) gate (d) source and drain  
**[1994 : 1 Mark]**
- 3.11** Channel current is reduced on application of a more positive voltage to the gate of the depletion mode n-channel MOSFET. (True/False)  
**[1994 : 1 Mark]**
- 3.12** The break down voltage of a transistor with its base open is  $BV_{CEO}$  and that with emitter open is  $BV_{CBO}$ , then  
 (a)  $BV_{CEO} = BV_{CBO}$   
 (b)  $BV_{CEO} > BV_{CBO}$   
 (c)  $BV_{CEO} < BV_{CBO}$   
 (d)  $BV_{CEO}$  is not related to  $BV_{CBO}$   
**[1995 : 1 Mark]**
- 3.13** Match the following:  
**List-I**  
 A. The current gain of a BJT will be increased  
 B. The current gain of a BJT will be reduced  
 C. The break-down voltage of a BJT will be reduced  
**List-II**  
 1. The collector doping concentration is increased  
 2. The base width is reduced  
 3. The emitter doping concentration to base doping concentration ratio is reduced  
 4. The base doping concentration is increased keeping the ratio of the emitter doping concentration to base doping concentration constant  
 5. The collector doping concentration is reduced  
**[1994 : 2 Marks]**
- 3.14** The transit time of current carriers through the channel of an FET decides its \_\_\_\_ Characteristics.  
**[1994 : 1 Mark]**
- 3.15** The break down voltage of a transistor with its base open is  $BV_{CEO}$  and that with emitter open is  $BV_{CBO}$ , then  
 (a)  $BV_{CEO} = BV_{CBO}$   
 (b)  $BV_{CEO} > BV_{CBO}$   
 (c)  $BV_{CEO} < BV_{CBO}$   
 (d)  $BV_{CEO}$  is not related to  $BV_{CBO}$  **[1995 : 1 M]**
- 3.16** A BJT is said to be operating in the saturation Region if  
 (a) Both the Junctions are reverse biased.  
 (b) Base-Emitter Junction is reverse biased and Base-Collector Junction is forward biased.  
 (c) Base-Emitter Junction is forward biased and Base-Collector Junction is reverse-biased.  
 (d) Both the junctions are forward biased.  
**[1995 : 1 M]**

**3.17** A BJT is said to be operating in the saturation region if

- (a) both junctions are reverse biased.
- (b) base-emitter junction is R.B and base collector junction is forward biased.
- (c) base-emitter junction is forward biased and base-collector junction reverse biased.
- (d) both the junctions are forward biased.

[1995 : 1 M]

**3.18** In a JFET

**List-I**

- A. The pinch-off voltage decreases
- B. The transconductance increases
- C. The transit time of the carriers in the channel is reduced

**List-II**

- 1. The channel doping is reduced
- 2. The channel length is increases
- 3. The conductivity of the channel is increased
- 4. The channel length is reduced
- 5. The GATE area is reduced

[1995 : 2 M]

■■■

## Answers Electronic Devices and Circuits

1.1	(b)	1.2	(c)	1.3	(a)	1.4	(c)	1.5	(c)	1.6	(a)	1.7	(a, c)
1.8	(b)	1.9	(a)	1.10	(False)	1.11	(d)	1.12	(c)	1.13	(c)	1.14	(c)
2.1	(b)	2.2	(d)	2.3	(b)	2.4	(d)	2.5	(c)	2.6	(b)	2.7	(a)
2.8	(b)	2.9	(sol.)	2.10	(a & b)	2.11	(d)	2.12	(a)	2.13	(c)	3.1	(a)
3.2	(c)	3.3	(b)	3.4	(d)	3.5	(c)	3.6	(b, c)	3.7	(sol.)	3.8	(b)
3.9	(b)	3.10	(b)	3.11	(False)	3.12	(c)	3.13	(A-2, B-3, C-1)	3.14	(sol.)		
3.15	(c)	3.16	(d)	3.17	(d)	3.18	(A-1, B-3, C-4)						

## Explanations Electronic Devices and Circuits

### 1. Basic Semiconductor Physics

**1.2 (c)**

By mass action law:

$$n \cdot p = n_i^2$$

$n_i$  = intrinsic carrier concentration

$p$  = hole concentration

$n$  = electron concentration

$$n_i^2 \propto T^3$$

$$n_i \propto T^{3/2}$$

For intrinsic semiconductor,

$$n = p = n_i$$

$$n \propto T^{3/2}$$

**1.3 (a)**

We know that

$$\text{Einstein equation} \rightarrow \frac{D}{\mu} = \frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T = \frac{T(^{\circ}\text{K})}{11600}$$

Where,

$T$  = Temperature in  $^{\circ}\text{K}$

$V_T$  = Thermal voltage

$D$  = Diffusion constant

$\mu$  = Mobility

$D_n$  = Electron diffusion constant

$D_p$  = Hole diffusion constant

$\mu_n$  = Electron mobility

$\mu_p$  = Hole mobility

**1.4 (c)**

DBG (Direct Band Gap) semiconductors exhibit short carrier life time they are used for fabricating lasers. In DBG semiconductor during the recombination the energy is released in the form of light.

**1.5 (c)**

$$\Delta n = \Delta p$$

Due to illumination by light EHP (electron-hole pair) generation occurs.


So,  $\Delta n = \Delta p$

Where

$\Delta n$  = increase in electron concentration due to illumination by light

$\Delta p$  = increase in hole concentration due to illumination by light

### 1.7 (a) & (c)

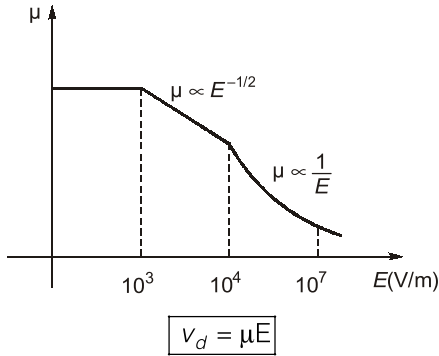

Where

$v_d$  = Drift velocity

$\mu$  = Mobility

$E$  = Applied electric field

For high electric field, with increasing electric field:

1. The mobility of charge carriers decreases as electric field increases.

$$\mu \propto \frac{1}{E}$$

2. The velocity (drift velocity) of charge carriers saturates.

### 1.8 (b)

$P$ -type with carrier concentration of  $10^{16}/\text{cm}^3$ .

Given that,

$N_D = n$  = Phosphorus atoms =  $10^{16}/\text{cm}^3$

$N_A = p$  = Boron atoms =  $2 \times 10^{16}/\text{cm}^3$

$$\therefore N_A > N_D$$

So, the resultant material will be  $p$ -type semiconductor carrier concentration

$$\begin{aligned} &= N_A - N_D \\ &= 2 \times 10^{16} - 10^{16} \\ &= 10^{16}/\text{cm}^3 \end{aligned}$$

### 1.9 (a)

$10^{20}$  e-h pairs/ $\text{cm}^3/\text{s}$

Given that,  $\Delta n = 10^{15}/\text{cm}^3$

$$\tau_p = 10 \mu\text{sec} = 10 \times 10^{-6} \text{ sec.}$$

$$\begin{aligned} \text{Generation rate} &= \frac{\Delta P}{\tau_p} = \frac{10^{15}}{10 \times 10^{-6}} \\ &= 10^{20} \text{ e-h pairs}/\text{cm}^3/\text{s} \end{aligned}$$

### 1.10 Sol. (False)

The given statement is false, because for a given semiconductor the electron mobility ( $\mu_n$ ) is always higher than the hole mobility ( $\mu_p$ ).

$\mu_n > \mu_p$  (for a given semiconductor) we know that, the conductivity of a given  $n$ -type semiconductor

$$\sigma_n = nq\mu_n$$

the conductivity of a given  $p$ -type semiconductor.

$$\sigma_p = pq\mu_p$$

given that  $n = p$  = same dopant concentration

$$q = 1.602 \times 10^{-19} \text{ Col.}$$

So,


$$\sigma_n > \sigma_p$$

### 1.11 (d)

$$v_d = \mu E$$

where,  $v_d$  = Drift velocity ;  $\mu$  = Mobility

$E$  = Applied electric field

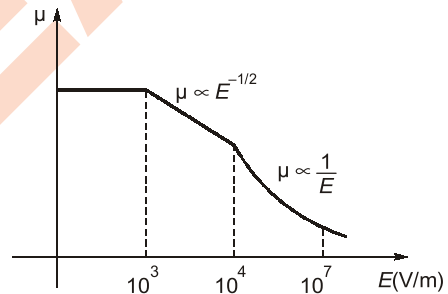

So,

1. For smaller electric field applied, mobility of charge carrier will remain almost constant. So for smaller electric field applied, drift velocity ( $v_d$ ) increases linearly with electric field.
2. For large electric field applied, mobility of charge carrier will be very small, so the drift velocity gradually saturates at higher values of electric field.

### 1.13 (c)

By Mass Action Law

$$n \cdot p = n_i^2$$

Where,  $n$  = electron concentration

$p$  = hole concentration

$n_i$  = intrinsic carrier concentration

$$p = 2.25 \times 10^{15}/\text{cm}^3$$

$$n_i = 1.5 \times 10^{10}/\text{cm}^3$$

$$n = \frac{n_i^2}{p} = \frac{(1.5 \times 10^{10})^2}{2.25 \times 10^{15}} = \frac{2.25 \times 10^{20}}{2.25 \times 10^{15}}$$

$$n = 10^5/\text{cm}^3$$



**1.14 (c)**

$$\text{Velocity} = \frac{\text{Distance}}{\text{Time}}$$

$$v_d = \frac{1}{20 \times 10^{-6}} = 50,000 \text{ cm/sec}$$

$$\text{Drift velocity} = v_d = \mu E$$

Where,

$\mu$  = Mobility

$E$  = Electric field

$$\mu = \frac{v_d}{E} = \frac{50,000}{10} = 5,000 \text{ cm}^2/\text{volt-sec}$$

**2. PN-Junction Diodes and Special Diodes****2.1 (b)**

Decreases with decreasing current and increasing temperature.

$$\text{Diffusion capacitance} = C_D = \tau g = \frac{\tau}{r}$$

$$r = \frac{\eta V_T}{I_f}$$

$$C_D = \frac{\tau I_f}{\eta V_T} = \frac{\tau I_f}{\eta kT}$$

$$C_D \propto I_f$$

$$C_D \propto \frac{1}{T}$$

**2.2 (d)**

1-A, 2-C, 3-B

Avalanche breakdown  $\rightarrow$  Collision of carriers with crystal ions.

Zener breakdown  $\rightarrow$  Rupture of covalent bond due to strong electric field.

Punch through  $\rightarrow$  Early effect.

**2.3 (b)**

$$V = \frac{KT}{q} \ln \left( \frac{I}{I_o} \right)$$

Diode  $D_1$  is in forward bias

Diode  $D_2$  is in reverse bias

So, the current through diode  $D_1$  is forward current  $I_f$  and current through diode  $D_2$  is reverse current  $I_o$

So, total current  $= I = I_f + I_o$

$$I = I_o (e^{V_d/\eta V_T} - 1) = I_o e^{V_d/\eta V_T} - I_o$$

$$I = (I_o e^{V_d/\eta V_T} - I_o) + I_o = I_o e^{V_d/\eta V_T}$$

$$e^{V_d/\eta V_T} = \frac{I}{I_o}$$

$$\frac{V_d}{\eta V_T} = \ln \left( \frac{I}{I_o} \right)$$

$$V_d = \eta V_T \ln \left( \frac{I}{I_o} \right)$$

$$V_d = \frac{KT}{q} \ln \left( \frac{I}{I_o} \right) \quad \{\text{For Ge, } \eta = 1\}$$

$$\therefore V_d = V$$

$$V = \frac{KT}{q} \ln \left( \frac{I}{I_o} \right)$$

**2.4 (d)**

The lifetime of majority carriers in the  $N$ -region.

The switching speed of a  $P^+N$  (heavily doped  $p$ -region) junction depends on the lifetime ( $\tau$ ) of majority carriers (electrons) in the  $N$ -region (lightly doped region).

**2.5 (c)**

Both  $P$  and  $N$ -regions are heavily doped.

In a Zener diode  $P$  and  $N$  both the regions are heavily doped.

Doping level of Zener diode is  $1 : 10^5$ .

**2.6 (b)**

The depletion capacitance decreases with increase in the reverse bias.

Depletion width  $= W$

$$W \propto \sqrt{V_{RB}}$$

$$W \propto \sqrt{\text{Reverse bias voltage}}$$

$$\text{Capacitance} = C = \frac{A\epsilon}{W}$$

$$C \propto \frac{1}{W}$$

$$C \propto \frac{1}{\sqrt{\text{Reverse bias voltage}}}$$

**2.7 (a)**

In the step graded diode, by using charge density condition or charge neutrality condition

$$\frac{W_N}{W_P} = \frac{N_A}{N_D}$$

$$\frac{W_N}{W_P} = \frac{N_A}{4N_A} = \frac{1}{4} = 0.25$$



**2.8 (b)**

For abrupt p-n junction

$$C_j \propto V^{-1/2}$$

$$C_j \propto \frac{1}{\sqrt{V}}$$

$$\frac{C_2}{C_1} = \sqrt{\frac{V_1}{V_2}} = \sqrt{\frac{1+0}{1+99}} = \sqrt{\frac{1}{100}} = \frac{1}{10}$$

$$C_2 = \frac{C_1}{10} = \frac{1}{10} = 0.1 \text{ nF/cm}^2$$

**2.9 Sol.**

When diode instantaneously switched from a conduction state it needs some time to return to non-conduction state, so diode behaves as short circuit for the little time, even in reverse direction. This is due to accumulation of stored excess minority carrier charge when diode is forward biased.

Time required to return back to state of non conduction is 'Reverse recovery time' which is 'storage time' and 'transition time'.

- Storage Time is the period for which diode remains in conduction state even in reverse direction.
- Transition time is time elapsed in returning back to state of non conduction.

For  $0 < t < t_o$ ;  $V_m = 20 \text{ V}$ , 'D' is Forward biased

$$i = \frac{V_m}{R} = \frac{20}{10 \text{ k}\Omega} = 2 \text{ mA}$$

For  $t > t_o$ ;  $V_m = -20$

During storage time:  $t_o < t < t_o + t_s$ ;


$$i = \frac{V_m}{R} = -\frac{20}{10 \text{ k}\Omega} = -2 \text{ mA}$$

During transition time:  $t_o + t_s < t < t_o + t_s + t_t$

$i$  decreases exponentially to  $(-I_o)$

For  $t > t_o + t_s + t_t$

$$i = (-I_o)$$

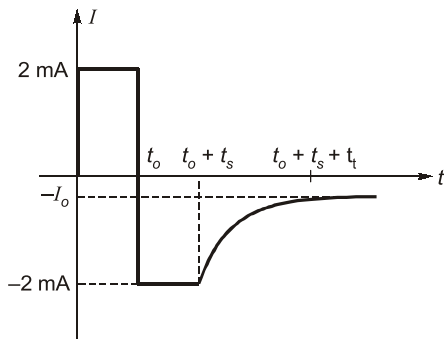**2.10 (a) & (b)**

Increases with the increase in the doping levels of the two sides.

Built in potential or diffusion potential across a p-n junction diode.

$$V_o = kT \ln \left( \frac{N_A N_D}{n_i^2} \right)$$

$$\text{So, } V_o \propto n_i^2$$

$$V_o \propto N_A \cdot N_D$$

So, option (a) and option (b) both are correct.

**2.11 (d)**

Increases with increase in doping concentration contact potential of diffusion potential across a pn junction

$$V_o = kT \ln \left( \frac{N_A N_D}{n_i^2} \right)$$

at constant temperature

$$V_o \propto N_A N_D$$

**2.12 (a)**

Tunneling of charge carriers across the junction a Zener diode works on the principle of tunneling of charge carriers across the junction which leads the junction to breakdown.

**2.13 (c)**

$$C_j \propto V_R^{-1/2}$$

The depletion layer capacitance of a diode is given

$$C_T \propto V^{-n}$$

$$n = \frac{1}{2} \text{ for step graded or abrupt p-n junction}$$

$$C_T \propto V_R^{-1/2}$$

**3. BJT and FET Basics****3.1 (a)**

Given that,

$$V_p = 4 \text{ V}$$

$$V_{GS} = 1 \text{ V}$$

$$|V_{DS}| = |V_p| - |V_{GS}|$$

$$|V_{DS}| = 4 - 1 = 3 \text{ V}$$

**3.2 (c)**

$V_{GS}$  is held constant and  $V_{DS}$  is increased then the depletion width increases, so the cross-sectional area of the channel 'S'.

$$\therefore \text{Current density} = \frac{I}{A} = \frac{I}{S} = J$$

$$S \downarrow \rightarrow J \uparrow$$

So, the channel current density increases.

**3.3 (b)**

$n$ -channel MOSFET is faster than the  $p$ -channel MOSFET.

Mobility of electrons is always higher than the mobility of holes.

$$\mu_n > \mu_p$$

In  $n$ -channel the charge carriers are electrons whereas in  $p$ -channel MOSFET the charge carriers are holes.

**3.4 (d)**

In a MOSFET, the polarity of the inversion layer is the same as that of the majority carriers in the source.

**3.5 (c)**

Pinch-off voltage = Cut-off voltage

So, cut-off voltage = 5.0 V

**3.6 (b) & (c)**

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

as temperature increases,  $I_{CO}$  increases, so the current ( $I_C$ ) increases in BJT with rise in temperature.

$\therefore$  mobility decreases as temperature increases.

$$T \uparrow \rightarrow \mu \downarrow$$

So, in MOSFET, current ( $I_{DS}$ ) decreases with rise in temperature.

$$T \uparrow \rightarrow I_{DS} \downarrow$$

**3.7 Sol. (decrease)**

As the reverse bias increase at CB (collector base) junction then the collector current ( $I_C$ ) increases and the effective base width decreases, so the recombination in base decreases.

**3.8 (b)**

$$V_{GS} = 0 \text{ V and } V_{DS} = 0 \text{ V}$$

For  $n$ -channel JFET, JFET offers minimum 'ON' resistance when  $V_{GS}$  is positive and large and voltage  $V_{DS}$  is very small, ideally  $V_{DS} = 0 \text{ V}$ .

**3.9 (b)**

For the NMOS threshold voltage is given by

$$V_T = V_{To} + \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$\gamma = \frac{\sqrt{2qN_A\epsilon_s}}{C_{ox}} = \frac{t_{ox}\sqrt{2qN_A\epsilon_s}}{3.45 \times 10^{-11}}$$

So, the threshold voltage of an  $n$ -channel MOSFET can be increased by reducing the channel dopant concentration.

**3.10 (b)**

The transit time of the current carries through the channel of a JFET decides its drain characteristic.

**3.11 Sol. (False)**

For depletion mode  $n$ -channel MOSFET, if the GATE terminal is made more positive then the channel becomes more and more  $n$ -type hence the drain current will increase.

**3.12 (c)**

The relationship between open base breakdown voltage ( $BV_{CEO}$ ) of BJT with open emitter voltage ( $BV_{CBO}$ ) is given by

$$BV_{CEO} = BV_{CBO} \sqrt{\frac{1}{\beta}}$$

$$\therefore \beta > 1$$

$$\text{So, } BV_{CEO} < BV_{CBO}$$

**3.13 Sol.****(A-2, B-3, C-1)**

- As the base width of the BJT is reduced then the recombination current (base current  $I_B$ ) decreases as a result collector current ( $I_C$ ) increases. So, the current gain of the BJT increases.

$$\alpha = \frac{I_C}{I_E}$$

- If the emitter doping concentration to base doping concentration ratio is reduced then the emitter injection efficiency decreases, so the current gain ( $\alpha$ ) of BJT reduces.
- If the collector doping concentration is increased then the breakdown ( $V_{BR}$ ) of a BJT will be reduced.

**3.14 Sol.**

The transit time of a current carriers through the channel of an FET decides its **switching** characteristics.

**3.15 (c)**

The relationship between open base breakdown voltage ( $BV_{CEO}$ ) of BJT with open emitter voltage ( $BV_{CBO}$ ) is given by

$$BV_{CEO} = BV_{CBO} \sqrt{\frac{1}{\beta}}$$

$$\therefore \beta > 1$$

So,  $BV_{CEO} < BV_{CBO}$

**3.16 (d)**

Both the junctions are forward biased.

When emitter base ( $E-B$ ) junction and collector base ( $C-B$ ) junction both are forward biased then the BJT is said to be operating in saturation region.

**3.7 (d)**

In saturation region:

Collector-base ( $C-B$ ) junction  $\rightarrow$  Forward bias

Emitter-base ( $E-B$ ) junction  $\rightarrow$  Forward bias.

**3.18 Sol.**

A-1, B-3, C-4

- As the channel doping is reduced then the pinch-off voltage decreases.

- $g_m = \frac{I_D}{V_{GS}}$

So, the transconductance increases as drain current increases and the drain current increases as the conductivity of the channel is increased.

- If the channel length is reduced then the transit time of the carriers in the channel is reduced.


■■■

### CONTENTS

1. Operational Amplifiers **49**
2. Diodes Applications **50**
3. BJT Analysis **51**
4. FET and MOSFET Analysis **53**
5. Frequency Response of Amplifier **53**
6. Feedback Amplifiers **53**
7. Oscillator Circuits **54**
8. Power Amplifiers **54**


## 1. Operational Amplifiers

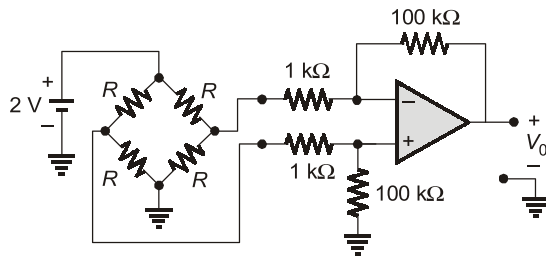- 1.1 In figure shown below, if the CMRR of the operational amplifier is 60 dB, then the magnitude of the output voltage is:



[1987 : 2 Marks]

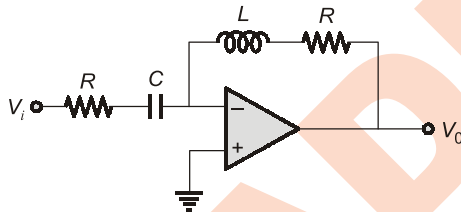
- 1.2 The Op-Amp shown in figure below is ideal.  $R = \sqrt{LC}$ . The phase angle between  $V_0$  and  $V_i$ , at  $\omega = 1/\sqrt{LC}$



- (a)  $\pi/2$   
(b)  $\pi$   
(c)  $3\pi/2$   
(d)  $2\pi$

[1988 : 2 Marks]

- 1.3 Refer to figure shown below:

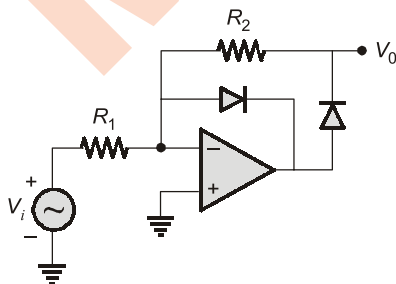


- (a) For  $V_i > 0$ ,  $V_0 = -\frac{R_2}{R_1} V_i$   
(b) For  $V_i > 0$ ,  $V_0 = 0$

(c) For  $V_i < 0$ ,  $V_0 = -\frac{R_2}{R_1} V_i$

(d) For  $V_i < 0$ ,  $V_0 = 0$

[1989 : 2 Marks]

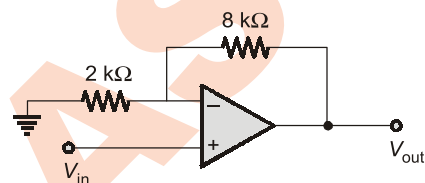
- 1.4 The Op-Amp of figure shown below has a very poor open loop voltage gain of 45 but is otherwise ideal. The gain of the Amplifier equals:



- (a) 5  
(b) 20  
(c) 4  
(d) 4.5

[1990 : 2 Marks]

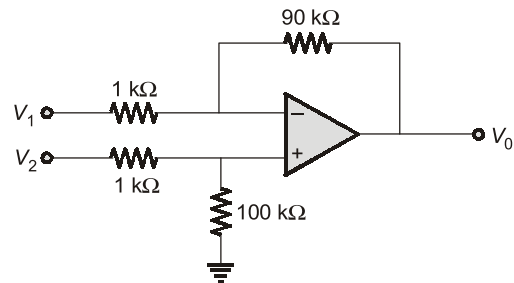
- 1.5 The CMRR of the differential Amplifier of the figure shown below is equal to



- (a)  $\infty$   
(b) 0  
(c) 1000  
(d) 1800

[1990 : 2 Marks]

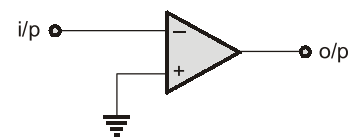
- 1.6 If the input to the circuit of figure is a sine wave the output will be



- (a) A half-wave rectified sine wave  
(b) A full-wave rectified sine wave  
(c) A triangular wave  
(d) A square wave

[1990 : 2 Marks]

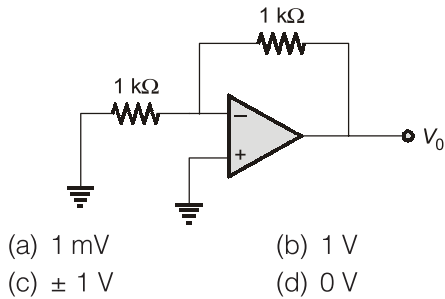
- 1.7 An Op-Amp has an offset voltage of 1 mV and is ideal in all other respects. If this Op-Amp is used in the circuit shown in fig. The output voltage will be (Select the nearest value).



- (a) 1 mV  
(b) 1 V  
(c)  $\pm 1$  V  
(d) 0 V


[1992 : 2 Marks]

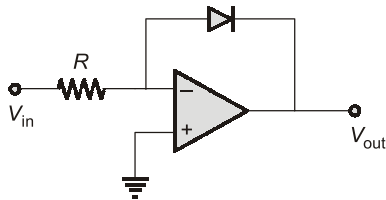- 1.8 The circuit of fig. uses an ideal OP-Amp for small positive values of  $V_{in}$ , the circuit works as




- (a) a half wave rectifier  
(b) a differentiator  
(c) a logarithmic Amplifier  
(d) an exponential Amplifier [1992 : 2 Marks]

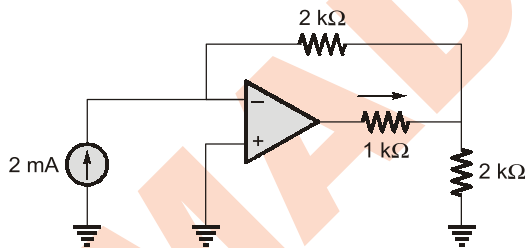- 1.9 Assume that the operational amplifier in figure is ideal the current  $I$  through the 1 kΩ resistor is \_\_\_\_.



[1992 : 2 Marks]

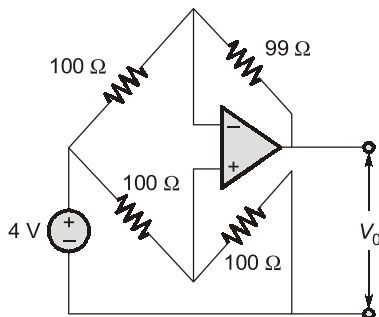- 1.10 For the ideal Op-Amp circuit of fig. Determine the output voltage  $V_o$




[1993 : 2 Marks]

- 1.11 The frequency compensation is used in OP-Amps to increase its \_\_\_\_.

[1994 : 1 Mark]

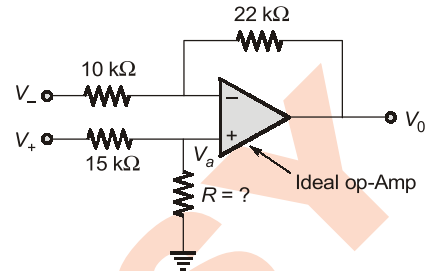- 1.12 In the given circuit figure, if the voltage inputs  $V_-$  and  $V_+$  are to be Amplified by the same Amplification factor, the value of ' $R$ ' should be




[1995 : 1 M]

- 1.13 An op-Amp is used as a zero-crossing detector. If maximum output available from the Op-Amp is  $\pm 12$  V<sub>p-p</sub> and the slew rate of the Op-Amp is 12 V/μ sec then the maximum frequency of the input signal that can be applied without causing a reduction in the P – P output is

[1995 : 1 M]

## 2. Diodes Applications

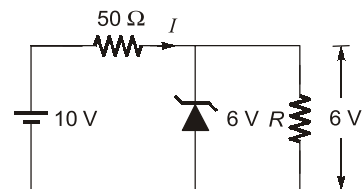
- 2.1 The 6 V Zener diode shown below has zero Zener resistance and a knee current of 5 mA. The minimum value of  $R$ . So that the voltage across it does not fall below 6 V is




- (a) 1.2 kΩ  
(b) 50 Ω  
(c) 80 Ω  
(d) 0 Ω

[1992 : 2 Marks]

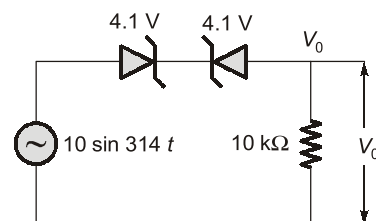- 2.2 The wave shape of  $V_o$  in figure is



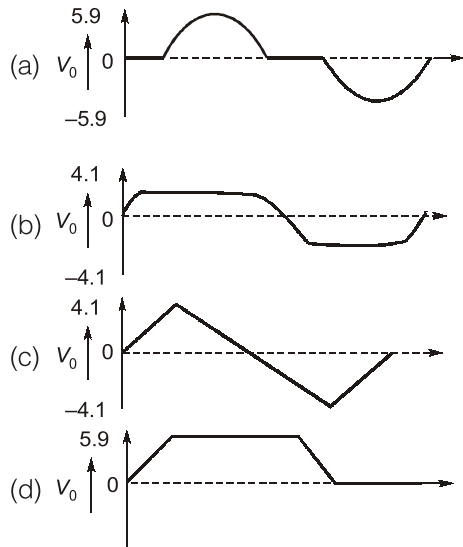

[1993 : 1 Mark]

2.3 The Ebers Moll model is applicable to

- (a) Bipolar junction transistors
- (b) NMOS transistors
- (c) Unipolar junction transistors
- (d) Junction field-effect

[1995 : 1 M]

### 3. BJT Analysis

3.1 The configuration of cascode amplifier is

- (a) CE – CE
- (b) CE – CB
- (c) CC – CB
- (d) CC – CC


[1987 : 2 Marks]

3.2 The quiescent collector current  $I_C$  of a transistor is increased by changing resistances. As a result

- (a)  $g_m$  will not be affected
- (b)  $g_m$  will decrease
- (c)  $g_m$  will increase
- (d)  $g_m$  will increase or decrease depending upon bias stability.

[1988 : 2 Marks]

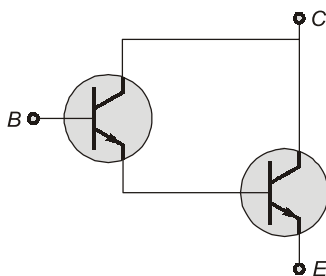
3.3 Each transistor in the Darlington pair (see Fig. below) has  $h_{FE} = 100$ . The overall  $h_{FE}$  of the composite transistor neglecting the leakage currents is



- (a) 10000
- (b) 10001
- (c) 10100
- (d) 10200

[1988 : 2 Marks]

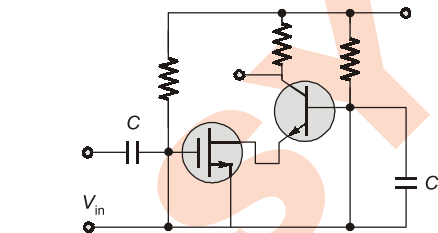3.4 The amplifier circuit shown below uses a composite transistor of a MOSFET and BIPOLAR in cascade. All capacitances are large.  $g_m$  of the MOSFET = 2 mA/V, and  $h_{fe}$  of the BIPOLAR = 99. The overall transconductance  $g_m$  of the composite transistor is




- (a) 198 mA/V
- (b) 9.9 mA/V
- (c) 4.95 mA/V
- (d) 1.98 mA/V

[1988 : 2 Marks]

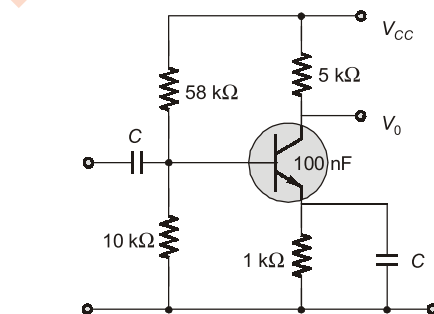3.5 The transistor in the amplifier shown below has following parameters :


$h_{fe} = 100$ ,  $h_{ie} = 2 \text{ k}\Omega$ ,  $h_{re} = 0$ ,  $h_{oe} = 0.05 \text{ mhos}$ .  $C$  is very large. The output impedance is



- (a) 20 kΩ
- (b) 16 kΩ
- (c) 5 kΩ
- (d) 4 kΩ


[1988 : 2 Marks]

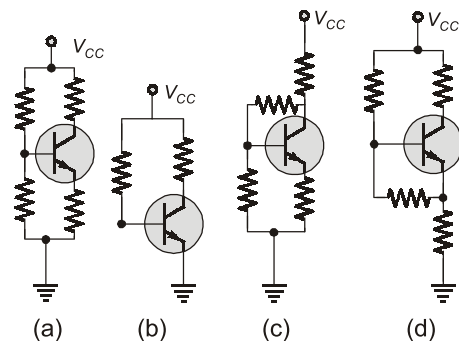3.6 Of the four biasing circuits shown in Fig. For a BJT, indicate the one which can have maximum bias stability



[1989 : 2 Marks]

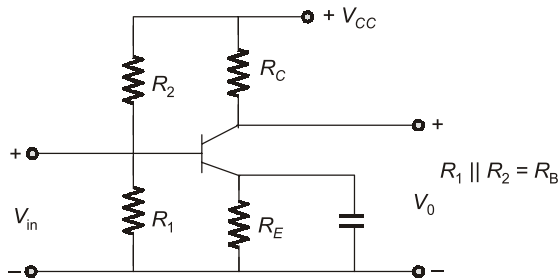3.7 For good stabilized biasing of the transistor of the CE Amplifier of fig, we should have



- (a)  $\frac{R_E}{R_B} \ll 1$       (b)  $\frac{R_E}{R_B} \gg 1$   
 (c)  $\frac{R_E}{R_B} \ll h_{FE}$       (d)  $\frac{R_E}{R_B} \gg h_{FE}$


[1990 : 2 Marks]

3.8 Which of the following statements are correct for basic transistor Amplifier configurations?

- (a) CB Amplifiers has low input impedance and low current gain  
 (b) CC Amplifiers has low output impedance and a high current gain.  
 (c) CE Amplifier has very poor voltage gain but very high input impedance  
 (d) The current gain of CB Amplifier is higher than the current gain of CC Amplifiers


[1990 : 2 Marks]

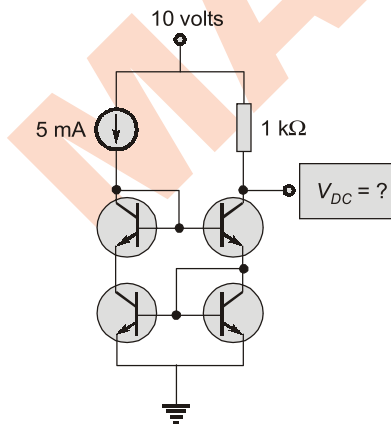3.9 In figure all transistors are identical and have a high value of beta. The voltage  $V_{DC}$  is equal to \_\_\_\_.



[1991 : 2 Marks]

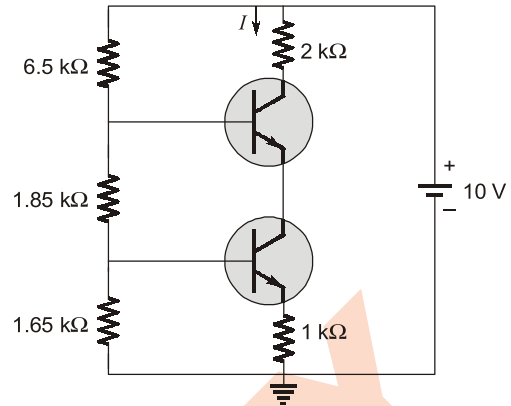3.10 If the transistor in fig. has high value of  $\beta$  and  $V_{BE}$  of 0.65 the current  $I$  flowing through the 2 kilo ohms resistance will be \_\_\_\_.




[1992 : 2 Marks]

3.11 The Bandwidth of an n-stage tuned Amplifier, with each stage having a bandwidth of  $B$ , is given by

- (a)  $B/n$       (b)  $B/\sqrt{n}$   
 (c)  $B\sqrt{2^{1/n} - 1}$       (d)  $B/\sqrt{2^{1/n} - 1}$

[1993 : 1 Mark]

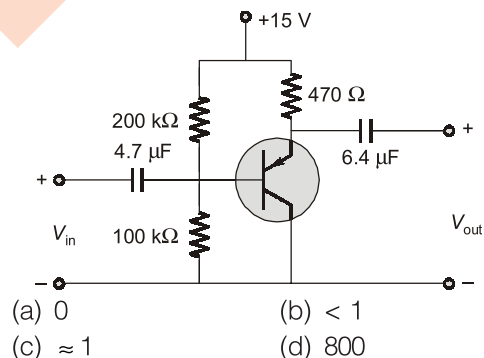3.12 For the Amplifier circuit of fig. The transistor has a  $\beta$  of 800. The mid band voltage gain  $V_0/V_i$  of the circuit will be.



- (a) 0      (b)  $< 1$   
 (c)  $\approx 1$       (d) 800

[1993 : 1 Mark]

3.13  $\alpha$  cut-off frequency of a bipolar junction transistor

- (a) increase with the increase in base width  
 (b) increase with the increase in emitter width  
 (c) increases with the increase in collector width  
 (d) increase with decrease in the base width

[1993 : 2 Marks]

3.14 In order to reduce the harmonic distortion in an Amplifier its dynamic range has to be \_\_\_\_.


[1994 : 1 Mark]

3.15 A Common Emitter transistor Amplifier has a collector current of 1.0 mA when its a base current is 25  $\mu$ A at the room temperature. It's input resistance is approximately equal to \_\_\_\_.

[1994 : 1 Mark]



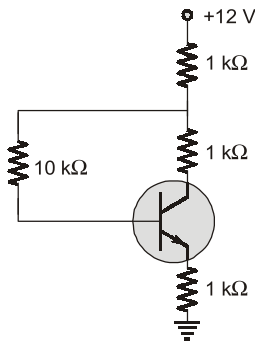
- 3.16 A transistor having  $\alpha = 0.99$  and  $V_{BE} = 0.7$  V, is used in the circuit of the figure is the value of the collector current will be



[1995 : 1 M]

#### 4. FET and MOSFET Analysis

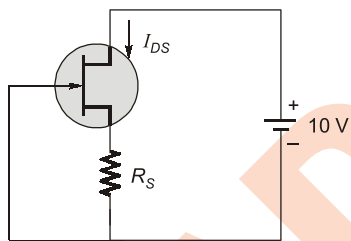- 4.1 The JFET in the circuit shown in fig. has an  $I_{DSS} = 10$  mA and  $V_P = -5$  V. The value of the resistance  $R_S$  for a drain current  $I_{DS} = 6.4$  mA is (Select the Nearest value)



- (a) 150 ohms (b) 470 ohms  
(c) 560 ohms (d) 1 Kilo ohm

[1992 : 2 Marks]

- 4.2 An  $n$ -channel JFET has  $I_{DSS} = 1$  mA and  $V_P = -5$  V. Its maximum transconductance is \_\_\_\_\_

[1995 : 1 M]

#### 5. Frequency Response of Amplifier

- 5.1 In a multi-stage RC-Coupled Amplifier the coupling capacitor.
- Limits the low frequency response
  - Limits the high frequency response
  - Does not effect the frequency response
  - Blocks the d.c components without effecting the frequency response.

[1993 : 1 Mark]

- 5.2 An RC-Coupled Amplifier is assumed to have a single-pole low frequency transfer function. The maximum lower-cutoff frequency allowed for the Amplifier to pass 50 Hz. Square wave with no more than 10% tilt is \_\_\_\_\_.


[1995 : 1 M]

- 5.3 An Amplifier has an open-loop gain of 100 and its lower and upper-cut-off frequency of 100 Hz and 100 kHz respectively, a feedback network with a feedback factor of 0.99 is connected to the amplifier. The new lower-and upper-cut-off frequencies are at \_\_\_\_\_ and \_\_\_\_\_.

[1995 : 1 M]

#### 6. Feedback Amplifiers

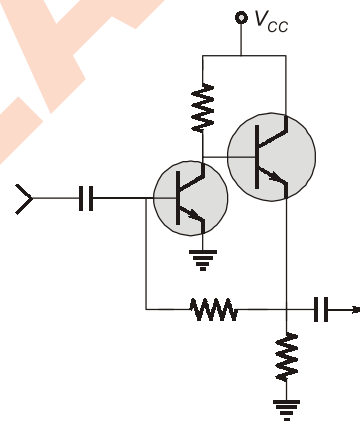- 6.1 The feedback amplifier shown in Fig. has:



- current – series feedback with large input impedance and large output impedance.
- voltage – series feedback with large input impedance and low output impedance.
- voltage – shunt feedback with low input impedance and low output impedance.
- current – shunt feedback with low input impedance and output impedance.

[1989 : 2 Marks]

- 6.2 Two non-inverting amplifiers, one having a unity gain and the other having a gain of twenty, are made using identical operational amplifiers. As compared to the unity gain amplifier, the amplifier with gain twenty has

- less negative feedback
- greater input impedance
- less bandwidth
- none of the above.

[1991 : 2 Marks]

- 6.3** Negative feed back in Amplifiers  
 (a) improves the signal to noise ratio at the input  
 (b) improves the signal to noise ratio at the output  
 (c) does not effect the signal to noise ratio at the output  
 (d) reduces distortion **[1993 : 1 Mark]**
- 6.4** To obtain very high input and output impedances in a feedback Amplifier, the mostly used is  
 (a) Voltage - series (b) Current - series  
 (c) Voltage - shunt (d) Current - shunt **[1995 : 1 M]**

## 7. Oscillator Circuits


- 7.1** Match the following
- | List-I          | List-II                            |
|-----------------|------------------------------------|
| (a) Hartley     | (1) Low frequency oscillator       |
| (b) Wein-bridge | (2) High frequency oscillator      |
| (c) Crystal     | (3) Stable frequency oscillator    |
|                 | (4) Relaxation oscillator          |
|                 | (5) Negative Resistance oscillator |
- [1994 : 2 Marks]**

## 8. Power Amplifiers

- 8.1** In case of class A amplifiers the ratio (efficiency of transformer coupled amplifier)/(efficiency of a transformer less amplifier) is  
 (a) 2.9 (b) 1.36  
 (c) 1.0 (d) 0.5 **[1987 : 2 Marks]**
- 8.2** In a transistor push-pull Amplifier  
 (a) there is no d.c present in the output  
 (b) there is no distortion in the output  
 (c) there is no even harmonics in the output  
 (d) there is no add harmonics in the output **[1993 : 1 Mark]**

- 8.3** A Class – A transformer coupled, transistor power Amplifier is required to deliver a power output of 10 watts. The maximum power Rating of the transistor should not be less than  
 (a) 5 W (b) 10 W  
 (c) 20 W (d) 40 W **[1994 : 1 Mark]**

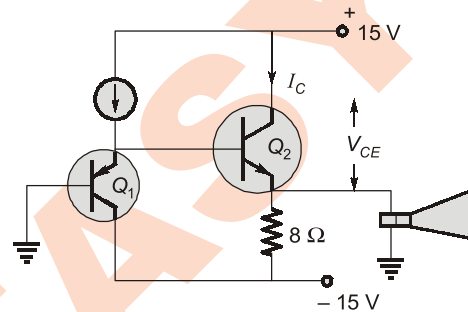- 8.4** The circuit shown in the figure supplies power to an  $8\ \Omega$  speaker, LS. The values of  $I_C$  and  $V_{CE}$  for this circuit will be  $I_C = \underline{\hspace{1cm}}$  and  $V_{CE} = \underline{\hspace{1cm}}$



**[1995 : 1 M]**

- 8.5** A power Amplifier delivers 50 W output at 50% efficiency. The ambient temperature is  $25^\circ\text{C}$ . If the maximum allowable junction temperature is  $150^\circ\text{C}$ , then the maximum thermal resistance  $\theta_{g_c}$  that can be tolerated is \_\_\_\_\_ **[1995 : 1 M]**

■■■

**Answers Analog Circuits**

1.1 (100)	1.2 (c)	1.3 (b, c)	1.4 (d)	1.5 (c)	1.6 (d)	1.7 (*)
1.8 (c)	1.9 (-4)	1.10 (0.02)	1.11 (sol.)	1.12 (33)	1.13 (159)	2.1 (c)
2.2 (a)	2.3 (a)	3.1 (b)	3.2 (c)	3.3 (d)	3.4 (d)	3.5 (d)
3.6 (a)	3.7 (b)	3.8 (a, b)	3.9 (5)	3.10 (1)	3.11 (c)	3.12 (c)
3.13 (d)	3.14 (large)	3.15 (1)	3.16 (3.75)	4.1 (a)	4.2 (0.4)	5.1 (a)
5.2 (1.59)	5.3 (10)	6.1 (c)	6.2 (a, c)	6.3 (b, d)	6.4 (b)	
7.1 (a-2, b-1, c-3)		8.1 (b)	8.2 (a, c)	8.3 (c)		

**Explanations Analog Circuits****1. Operational Amplifiers****1.1 Sol.**

By voltage divider rule:

$$V^- = 2 \frac{R}{R+R} = 1V ; V^+ = 2 \frac{R}{R+R} = 1V$$

$$\text{So, } v_d = V^+ - V^- = 1 - 1 = 0V$$

$$V_c = \frac{V^+ + V^-}{2} = \frac{1+1}{2} = 1V$$

$$A^- = -\frac{R_f}{R_1} = -\frac{100k}{1k} = -100$$

$$A^+ = \left(1 + \frac{R_f}{R_1}\right) \times \left(\frac{100}{100+1}\right) = \left(1 + \frac{100k}{1}\right) \left(\frac{100}{101}\right) = 100$$

$$A_d = \frac{A^+ - A^-}{2}$$

$$A_d = \frac{100 - (-100)}{2} = 100$$

$$\therefore \text{CMRR} = 60 \text{ dB} = 10^3$$

$$\text{So, } \frac{A_d}{A_c} = 10^3$$

$$\Rightarrow A_c = \frac{A_d}{10^3} = \frac{1}{10}$$

$$\text{Now } V_o = |A_c| V_c + |A_d| v_d$$

$$\therefore V_o = |A_c| V_c = \frac{1}{10} \times 1 = 100 \text{ mV}$$

**1.2 (c)**

$$\frac{V_o}{V_i} = -\frac{Z_f}{Z_1} \dots \text{For inverting amplifiers}$$

$$\frac{V_o}{V_i} = -\frac{(R + j\omega L)}{R + \frac{1}{j\omega C}}$$

$$R = \sqrt{\frac{L}{C}} \text{ and } \omega = \frac{1}{\sqrt{LC}}$$

$$\frac{V_o}{V_i} = \frac{\left(\sqrt{\frac{L}{C}} + j\sqrt{\frac{1}{LC}} \cdot L\right)}{\sqrt{\frac{L}{C}} + \frac{1}{j\sqrt{LC}}}$$


$$= -\frac{\left(\sqrt{\frac{L}{C}} + j\sqrt{\frac{L}{C}}\right)}{\sqrt{\frac{L}{C}} + \frac{1}{j\sqrt{\frac{L}{C}}}} = -\frac{\left(\sqrt{\frac{L}{C}}(1+j)\right)}{\sqrt{\frac{L}{C}}\left(1+\frac{1}{j}\right)}$$

$$V_o = -\frac{(1+j)}{1-j} = -\frac{(\angle 45^\circ)}{(-\angle 45^\circ)} = -[45^\circ + 45^\circ] = -90^\circ$$

$$\frac{V_o}{V_i} = -\frac{\pi}{2} = 2\pi - \frac{\pi}{2} = \frac{3\pi}{2}$$

**1.3 (b) & (c)**

Case 1:  $V_i > 0 \rightarrow$

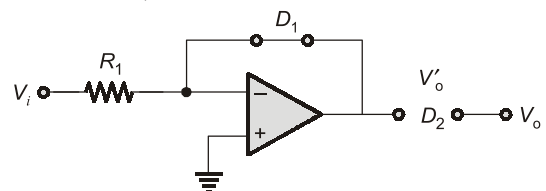


When  $V_i > 0$  then  $V_o'$  is negative.

So, diode  $D_1$  is forward bias and diode  $D_2$  is reverse bias.

So,  $V_o = 0V$

Case 2:  $V_i < 0 \rightarrow$

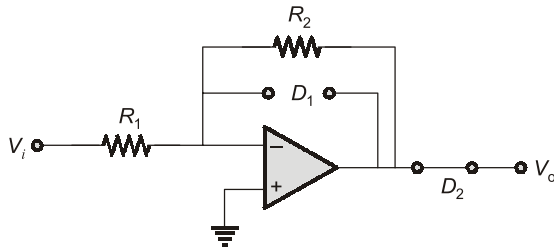

When  $V_i$  is negative then  $V_o$  is positive.

So, diode  $D_1$  is reverse bias and diode  $D_2$  is forward bias

$$V_o = -\frac{R_2}{R_1} V_i$$

**1.4 (d)**

$$\frac{1}{\beta} = 1 + \frac{R_f}{R_1} = 1 + \frac{8k}{2k} = 1 + 4 = 5$$

$$\beta = \frac{1}{5} = 0.2$$

$$A\beta = 45 \times 0.2 = 9$$

So,  $A\beta$  is not very greater than 1

$$\text{So, } A_f = \frac{A}{1 + A\beta} = \frac{45}{1 + 9} = 4.5$$

**1.5 (c)**

$$A_1 = -\frac{R_f}{R_1} = -\frac{90k}{1k} = -90$$

$$A_2 = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{100}{100 + 1}\right) = 90.09$$

$$A_d = \frac{A_2 - A_1}{2} = \frac{90.09 - (-90)}{2} = 90$$

$$A_c = A_1 + A_2 = -90 + 90.09 = 0.09$$

$$\text{CMRR} = \left|\frac{A_d}{A_c}\right| = \frac{90}{0.09} = 1000$$

**1.6 (d)**

The open loop gain of amplifier is very high, so it will act as a comparator.

So, if sinusoidal signal is applied to the input of the high gain comparator, then the comparator generates the square wave output.

**1.7 (\*)**

$$V_o = \text{Gain}(V_{in})$$

$$V_{in} = V_{\text{offset voltage}} = 1 \text{ mV}$$

$$\text{Gain} = 1 + \frac{R_f}{R_1} = 1 + \frac{1k}{1k} = 2$$

$$V_o = 2 \times 1 \times 10^{-3} = 2 \text{ mV}$$

**1.8 (c)**

Logarithmic amplifier

$$I = \frac{V_{in}}{R}$$

$$I_f = I_o e^{V_d / \eta V_T}$$

$$I = I_f = I_o e^{V_d / \eta V_T}$$

$$\frac{V_{in}}{R} = I_o e^{V_d / \eta V_T}$$


$$e^{V_d / \eta V_T} = \frac{V_{in}}{R I_o}$$

$$\frac{V_d}{\eta V_T} = \ln\left(\frac{V_{in}}{R I_o}\right)$$

$$V_o = -V_d$$

$$V_o = -\eta V_T \ln\left(\frac{V_{in}}{R I_o}\right)$$

**1.9 (-4)**

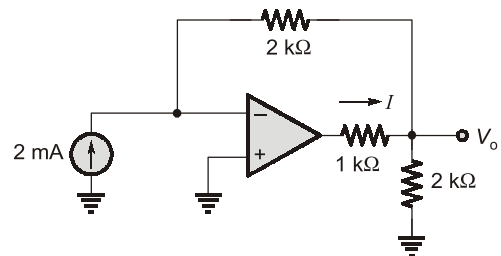

$$V_o = -2 \times 10^{-3} \times 2 \times 10^3 = -4 \text{ V}$$

Apply KCL at output node

$$I + 2 \text{ mA} = \frac{V_o}{2k} = -\frac{4}{2k} = -2 \text{ mA}$$

$$I = -4 \text{ mA}$$

**1.10 (0.02)**

$$V_o^- = -\frac{R_f}{R_1} V_{in} = -\frac{99}{100} \times 4$$

$$= -0.99 \times 4 = -3.96$$

$$V_x = 4 \times \frac{100}{100 + 100} = 2 \text{ V}$$

$$V_o^+ = \left(1 + \frac{R_f}{R_1}\right) V_x = \left(1 + \frac{99}{100}\right) \times 2$$

$$= 1.99 \times 2 = 3.98$$

$$V_o = V_o^+ + V_o^- = 3.98 - 3.96 = 0.02 \text{ V}$$

**1.11 Sol.**

To increase the stability of op-amps, frequency compensation is used in op-amps.

**1.12 (33)**

$$A^- = -\frac{R_f}{R_1}$$

$$A^- = -\frac{22 \text{ k}}{10 \text{ k}} = -2.2$$

$$|A^-| = 2.2$$

$$V_a = V_+ \left( \frac{R}{R+15} \right)$$

$$A^+ = 1 + \frac{R_f}{R_1}$$

$$\frac{V_o}{V_a} = 1 + \frac{R_f}{R_1} = \frac{V_o}{V_+ \left( \frac{R}{R+15} \right)}$$

$$\frac{V_o}{V_+} = \left( 1 + \frac{22}{10} \right) \times \left( \frac{R}{R+15} \right)$$

$$|A^+| = 3.2 \left( \frac{R}{R+15} \right)$$

$$\frac{3.2R}{R+15} = 2.2$$

$$3.2R = 2.2R + 33$$

$$R = 33 \text{ k}\Omega$$

**1.13 (159)**

$$f_{\max} = \frac{S.R.}{2\pi V_o}$$

$$f_{\max} = \frac{12}{10^{-6}} \times \frac{1}{2\pi \times 12} = 159 \text{ kHz}$$

**2. Diodes Applications****2.1 (c)**

$$I = \frac{10-6}{50} = \frac{4}{50} = 80 \text{ mA}$$

$$I = I_z + I_L = I_{z\min} + I_{L\max} = I_{z\max} + I_{L\min}$$


$$I_{z\min} = 5 \text{ mA}$$

$$80 = 5 + I_{L\max}$$

$$I_{L\max} = 75 \text{ mA}$$

$$I_{L\max} = \frac{V_L}{R_{\min}}$$


$$R_{\min} = \frac{V_L}{I_{L\max}} = \frac{6}{75 \times 10^{-3}} = 80 \Omega$$

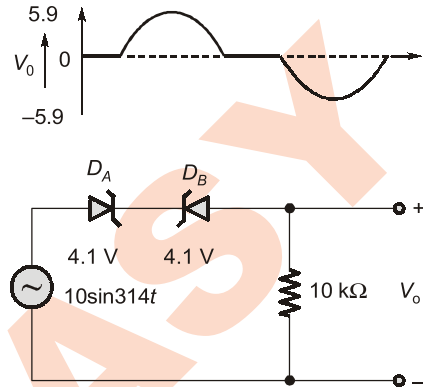**2.2 (a)**

**Case 1:** During +ve half cycle

Diode  $D_A$  is forward bias, so  $D_A$  is short circuit.


Diode  $D_B$  is reverse bias, so  $D_B$  is in conducting state when  $V_i > 4.1 \text{ V}$ .

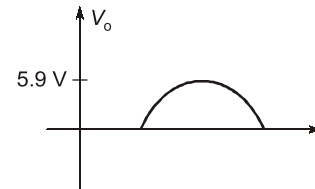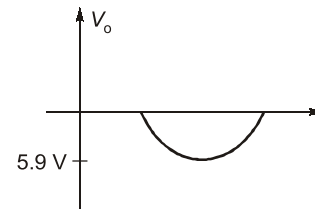

**Case 2:** During -ve half cycle

Diode  $D_B$  is forward bias, so  $D_B$  is short circuit.

Diode  $D_A$  is reverse bias, so  $D_A$  is in conducting state when  $|V_i| > 4.1 \text{ V}$ .

**2.3 (a)**

Ebers Moll model is a composite model and is used to predict the operation of BJT all of its possible modes.

It consists of two ideal diodes placed back to back with reverse saturation currents  $I_{EO}$  and  $I_{CO}$  and two dependent current controlled sources shunting the diodes.

### 3. BJT Analysis

**3.1 (b)**

Cascode amplifier is the common emitter followed by common base configuration.


**3.2 (c)**

$$g_m = \frac{I_c}{V_T}$$

So, if  $I_c \uparrow$  then  $g_m \uparrow$   $g_m \propto I_c$

So, if the quiescent collector current  $I_c$  increases then the transconductance  $g_m$  also increases.


**3.3 (d)**

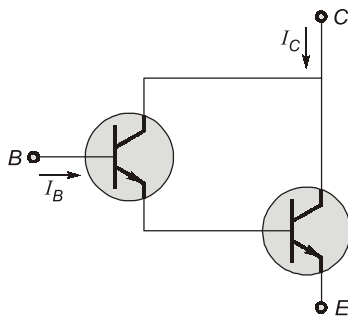

So, overall  $\beta$  of the composite transistor

$$\begin{aligned} \frac{I_C}{I_B} &= \beta = \beta_1 + \beta_2 + \beta_1 \beta_2 \\ &= 10200 \end{aligned}$$

**3.4 (d)**

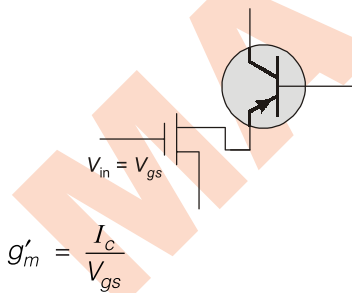

$$g'_m = \frac{I_c}{V_{gs}}$$

$$I_c = \alpha I_E = \frac{\beta}{1+\beta} I_E$$


$$g'_m = \frac{\frac{\beta}{1+\beta} I_E}{V_{gs}} = \frac{\beta I_E}{(1+\beta) V_{gs}}$$

$$I_D = I_E$$

$$g'_m = \frac{\beta}{(1+\beta)} \times \frac{I_D}{V_{gs}} = \frac{\beta}{1+\beta} g_m = \frac{99}{1+99} \times 2 \text{ mA/V}$$

$$g'_m = 1.98 \text{ mA/V}$$

**3.5 (d)**

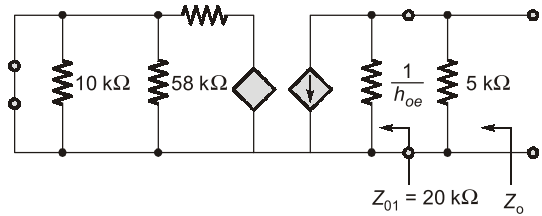

$$\text{Output admittance, } Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s}$$

$$= 0.05 \times 10^{-3} - \frac{100 \times 0}{2 \times 10^3 + 10 \times 10^3}$$

$$Y_o = 0.05 \times 10^{-3}$$

$$Z_{o1} = \frac{1}{Y_o} = \frac{1}{0.05 \times 10^{-3}} = 20 \text{ k}\Omega$$

Output impedance,

$$Z_o = Z_{o1} \parallel 5 \text{ k} = 20 \text{ k} \parallel 5 \text{ k} = \frac{20 \times 5}{20 + 5}$$


$$Z_o = 4 \text{ k}\Omega$$

**3.6 (a)**

In the BJT self bias circuit or potential divider circuit provides the maximum bias stability.

**3.7 (b)**

$$\frac{R_E}{R_B} \gg 1$$

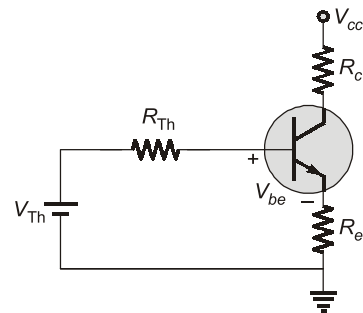

Simplified self bias circuit using Thevenin theorem

Thevenin open circuit voltage

$$V_{Th} = \frac{V_{cc} R_1}{R_1 + R_2}$$

Thevenin internal resistance

$$R_{Th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = R_B$$

Apply KVL to input mesh

$$V_{Th} = I_B R + V_{be} + I_E R_E$$

Put

$$I_E = I_B + I_C$$

$$V_{Th} = I_B R_B + V_{be} + (I_B + I_C) R_E$$

Differentiate w.r.t.  $I_C$ , keeping  $\beta$  and  $V_{be}$  constant.

$$0 = (R_B + R_E) \frac{\partial I_B}{\partial I_C} + R_E + 0$$

$$\frac{\partial I_B}{\partial I_C} = -\frac{R_E}{R_B + R_E}$$

$$S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}}$$

$$S = \frac{1 + \beta}{1 + \beta \left( \frac{R_E}{R_B + R_E} \right)}$$

$$\beta \gg 1$$

$$\beta \frac{R_E}{R_B + R_E} \gg 1$$

$$S = \frac{\beta}{\beta \left( \frac{R_E}{R_B + R_E} \right)}$$

$$S = 1 + \frac{R_B}{R_E}$$

For better stability

$$S \cong 1$$

$$\text{So, } \frac{R_B}{R_E} \ll 1 ; \frac{R_E}{R_B} \gg 1$$

### 3.8 (a) & (b)

In common base (CB) amplifiers input impedance ( $Z_i$ ) is low and current gain ( $\alpha$ ) is also low.

$$\alpha = \frac{I_C}{I_E}$$

In common collector (CC) amplifiers output impedance ( $Z_o$ ) is low and current gain ( $\gamma$ ) is high

$$\gamma = \frac{I_E}{I_B} = 1 + \beta$$

### 3.9 (5)

Given that  $\beta$  is very large

$$\text{So, } I_C = I_E$$


So, the current through  $1 \text{ k}\Omega$  resistance

$$I = 5 \text{ mA}$$

$$V_{DC} = 10 - IR = 10 - 5 \times 10^{-3} \times 1 \times 10^3$$

$$V_{DC} = 5 \text{ V}$$

### 3.10 (1)

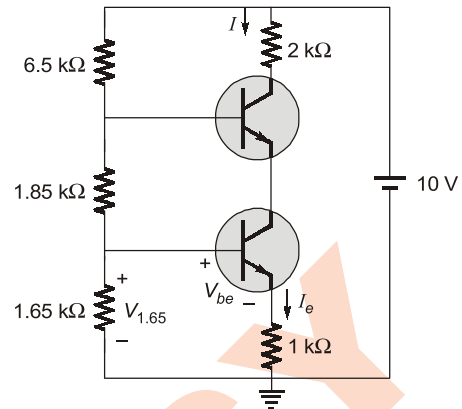

Given that  $\beta$  is very large.

$$\text{So, } I_b = 0$$

$$\text{So, } V_{1.65} = 10 \times \frac{1.65}{1.65 + 1.85 + 6.5} = 1.65 \text{ V}$$

Apply KVL at input mesh,

$$V_{1.65} = V_{be} + I_e R_e = 0.65 + I_e \times 1 \text{ k} = 1.65$$

$$I_e = 1 \text{ mA}$$

$\therefore \beta$  is very large,

$$\text{So, } I_C \cong I_e$$


$$I = I_C = 1 \text{ mA}$$

### 3.11 (c)

The overall bandwidth of an  $n$ -stage tuned amplifier is

$$BW^* = B\sqrt{2^{1/n} - 1}$$

### 3.12 (c)

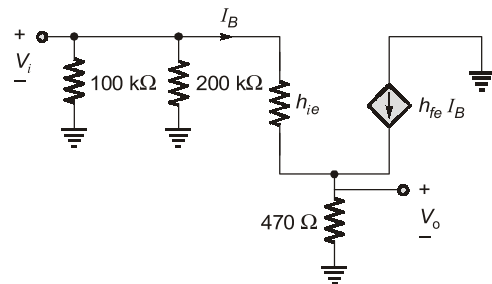

$$A_V = \frac{V_o}{V_i} = \frac{I_B(1 + h_{fe})R_E}{I_B[h_{fe} + (1 + h_{fe})]R_E} \cong 1$$

### 3.13 (d)

$$f_\infty = \frac{DB}{\pi W_B^2}$$

Thus, if  $W_B$  will decrease  $f_\infty$  will increase.

**3.14 Sol.**


In order to reduce the harmonic distortion in an amplifier its dynamic range has to be **large**.

**3.15 (1)**

For common emitter configuration,

Input resistance =  $R_i$

$$\begin{aligned} &= \frac{V_T}{I_B} = \frac{25 \times 10^{-3}}{25 \times 10^{-6}} \\ &= 1 \text{ k}\Omega \end{aligned}$$

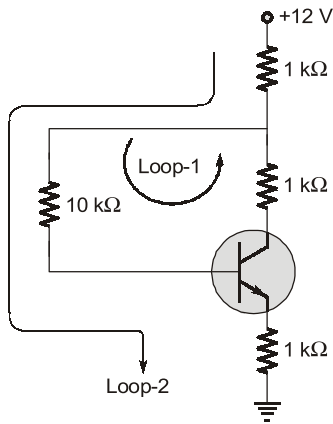**3.16 (3.75)**

$I_C$  cannot be 5.32 mA because  $I_C = 5.32$  mA will make  $V_{CE}$  negative which implies transistor is in saturation. Through KVL,

$$12 I_B + 2 I_C = 11.2 \quad (\text{Loop-1})$$

$$10 I_B - I_C = 0.6 \quad (\text{Loop-2})$$

Upon solving

$$I_C \cong 3.75 \text{ mA}$$

**4. FET and MOSFET Analysis****4.1 (a)**

$$I_{DS} = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$6.4 \times 10^{-3} = 10 \times 10^{-3} \left[ 1 - \frac{V_{GS}}{(-5)} \right]^2$$

$$0.64 = \left( 1 + \frac{V_{GS}}{5} \right)^2$$

$$1 + \frac{V_{GS}}{5} = 0.8$$

$$\frac{V_{GS}}{5} = -0.2$$

$$V_{GS} = -1 \text{ V}$$

$$V_{GS} = -I_{DS} R_S$$

$$-1 = -6.4 \times 10^{-3} R_S$$

$$R_S = \frac{1}{6.4 \times 10^{-3}} = 156 \Omega$$

$$R_S \cong 150 \Omega$$

**4.2 (0.4)**

$$g_{m(\max)} = \frac{2 I_{DSS}}{|V_P|} = \frac{2 \times 1 \times 10^{-3}}{|-5|} = 0.4 \text{ ms}$$

**5. Frequency Response of Amplifier****5.1 (a)**

The low frequency of operation of a multi-stage RC coupled amplifier is limited by the coupling capacitor.

**5.2 (1.59)**

$$\% \text{ Tilt} = \frac{\pi f_L}{f} \times 100\%$$

$$f_L = \frac{f \times \% \text{ Tilt}}{\pi \times 100} = \frac{50 \times 10}{\pi \times 100} = 1.59 \text{ Hz}$$

**5.3 (10)**

$$1 + A\beta = 1 + 100 \times 0.99 = 1 + 99 = 100$$

$$f_L^* = \frac{f_L}{1 + A\beta} = \frac{100}{100} = 1 \text{ Hz}$$

$$f_H^* = f_H(1 + A\beta) = 100 \times 10^3 \times (100) = 10 \text{ MHz}$$

**6. Feedback Amplifiers****6.1 (c)**

Emitter is output node, it is voltage sampler voltage shunt feedback.

**6.2 (a, c)**

For identical operational amplifiers, Gain-bandwidth product is constant

$$G.B.W = \text{Constant}$$

$$A_1 \times BW_1 = A_2 \times BW_2$$

$$BW_2 = \frac{A_1 \times BW_1}{A_2} = \frac{1 \times BW_1}{20} = \frac{BW_1}{20}$$

So, as compare to the unity gain amplifier with gain twenty has less bandwidth.



**6.3 (b) & (d)**

Negative feedback in amplifiers

(b) improves the signal to noise ratio at the output

(d) reduces distortion.

**6.4 (b)**

Current-series feedback amplifiers has very high input and very high output impedances.

$$R_{if} = R_i(1 + A\beta) = R_i(1 + G_m\beta)$$

$$R_{of} = R_o(1 + A\beta) = R_o(1 + G_m\beta)$$

**7. Oscillator Circuits****7.1 Sol.**

a-2, b-1, c-3

(a) Hartley oscillator

(2) High frequency oscillator

(b) Wein-bridge oscillator

(1) Low frequency oscillator

(c) Crystal oscillator

(3) Stable frequency oscillator

**8. Power Amplifiers****8.1 (b)**

Class A amplifier ratio

$$= \frac{\text{efficiency of transformer coupled amplifier}}{\text{efficiency of transformer less amplifier}}$$

$$= \frac{50\%}{25\%} = 2$$

**8.2 (a, c)**

The output of push pull power amplifier consists of only odd harmonics terms.

$$I_o = 2k[B_1 \cos \omega t + B_3 \cos 3\omega t + B_5 \cos 5\omega t + \dots]$$

**8.3 (c)**

$$\frac{P_{D\max}}{P_{AC\max}} = 2$$

For class-A transformer coupled amplifier,


$$P_{D\max} = 2 \times P_{AC\max} = 20 \text{ W}$$

$\therefore$  Power rating  $\geq 20 \text{ W}$

**8.4 (15)**

$$I_C = \frac{15}{8} \text{ Amp.}$$

$$V_{CE} = 15 \text{ V}$$

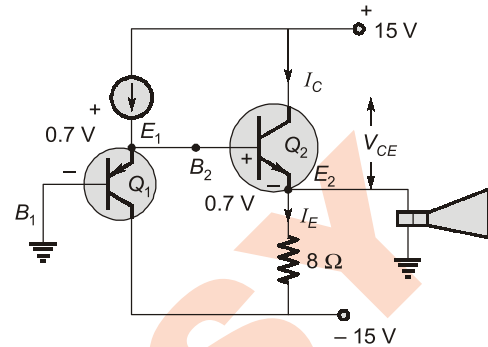

$$V_{E_1 B_1} = 0.7 \text{ V}$$

$$V_{E_1} - V_{B_1} = 0.7 \text{ V}$$

$$V_{E_1} - 0 = 0.7 \text{ V}$$

$$V_{E_1} = 0.7 \text{ V}$$

$$V_{E_1} = V_{B_2} = 0.7 \text{ V}$$

$$V_{B_2 E_2} = 0.7 \text{ V}$$

$$V_{B_2} - V_{E_2} = 0.7 \text{ V}$$

$$0.7 \text{ V} - V_{E_2} = 0.7 \text{ V}$$

$$V_{E_2} = 0 \text{ V}$$

Apply KVL at emitter terminal

$$0 = I_E R_E - 15$$

$$I_E = \frac{15}{R_E} = \frac{15}{8}$$

$$V_{CE} = V_C - V_E = 15 - 0 = 15 \text{ V}$$

**8.5 (2.5)**

Power dissipated ( $P_D$ ) =  $50 \times 50\%$

$$\frac{P_o}{P_{in}} = \frac{1}{2}$$

$$P_{in} = 2P_o = 2 \times 50 = 100 \text{ W}$$

$$P_D = P_{in} - P_o = \frac{T_j - T_A}{\theta}$$

$$\theta = \frac{T_j - T_A}{P_D} = \frac{150 - 25}{50} = \frac{125}{50}$$

$$\theta = 2.5^\circ \text{C/W}$$

# Digital Circuits and Computer Organization

## UNIT VI

### CONTENTS

1. Number Systems **63**
2. Boolean Algebra **63**
3. Logic Gates **63**
4. Combinational Circuits **64**
5. Sequential Circuits **64**
6. Logic Families **65**
7. Memories **66**
8. ADC and DAC **66**

## 1. Number Systems


- 1.1 The subtraction of a binary number  $Y$  from another binary number  $X$ , done by adding the 2's complement of  $Y$  to  $X$ , results in a binary number without overflow. This implies that the result is:
- negative and is in normal form
  - negative and is in 2's complement form
  - positive and is in normal form
  - positive and is in 2's complement form
- [1987 : 1 Mark]
- 1.2 2's complement representation of a 16-bit number (one sign bit and 15 magnitude bits) if FFFF. Its magnitude in decimal representation is
- 0
  - 1
  - 32,767
  - 65,535
- [1993 : 1 Mark]

## 2. Boolean Algebra

- 2.1 The number of Boolean functions that can be generated by  $n$  variables is equal to:
- $2^{2^{n-1}}$
  - $2^{2^n}$
  - $2^{n-1}$
  - $2^n$
- [1990 : 1 Mark]

## 3. Logic Gates

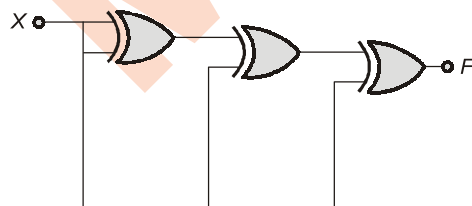- 3.1 For the circuit shown below the output  $F$  is given by



- $F = 1$
- $F = 0$
- $F = X$
- $F = \bar{X}$

[1988 : 1 Mark]

- 3.2 Minimum number of 2-input NAND gates required to implement the function,

$$F = (\bar{X} + \bar{Y})(Z + W) \text{ is}$$

- 3
- 4
- 5
- 6

[1988 : 1 Mark]

- 3.3 Indicate which of the following logic gates can be used to realized all possible combinational Logic functions:

- OR gates only
- NAND gates only
- EX-OR gates only
- NOR gates only


[1989 : 1 Mark]

- 3.4 Boolean expression for the output of XNOR (equivalence) logic gate with inputs  $A$  and  $B$  is

- $A\bar{B} + \bar{A}B$
- $\bar{A}\bar{B} + AB$
- $(\bar{A} + B)(A + \bar{B})$
- $(\bar{A} + \bar{B})(A + B)$

[1993 : 1 Mark]

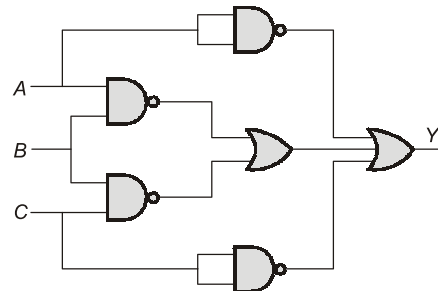- 3.5 For the logic circuit shown in Figure, the output is equal to



- $\overline{ABC}$
- $\bar{A} + \bar{B} + \bar{C}$
- $\overline{AB} + \overline{BC} + \bar{A} + \bar{C}$
- $\overline{AB} + \overline{BC}$

[1993 : 1 Mark]

- 3.6 The output of a logic gate is '1' when all its inputs are at logic '0'. The gate is either

- a NAND or an EX-OR gate
- a NOR or an EX-NOR gate
- an OR or an EX-NOR gate
- an AND or an EX-OR gate

[1994 : 1 Mark]


- 3.7 A ring oscillator consisting of 5 inverters is running at a frequency of 1.0 MHz. The propagation delay per gate is \_\_\_\_\_ n sec.

[1994 : 1 Mark]

3.8 The minimum number of NAND gates required to implement the Boolean function  $A + \bar{A}\bar{B} + A\bar{B}C$  is equal to

- (a) Zero (b) 1  
(c) 4 (d) 7 [1995 : 1 M]

3.9 The output of the circuit shown in figure is equal to

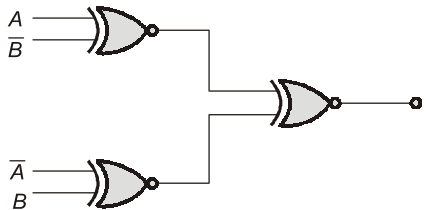
- 
- (a) 0 (b) 1  
(c)  $\bar{A}B + A\bar{B}$  (d)  $(\bar{A} \oplus B) \oplus (\bar{A} \oplus B)$  [1995 : 1 M]

#### 4. Combinational Circuits

4.1 The minimal function that can detect a "divisible by 3" 8421 BCD code digit (representation is  $D_8 D_4 D_2 D_1$ ) is given by


- (a)  $D_8 D_1 + D_4 D_2 + \bar{D}_8 \bar{D}_2 \bar{D}_1$   
(b)  $D_8 D_1 + D_4 D_2 \bar{D}_1 + \bar{D}_4 D_2 D_1 + \bar{D}_8 \bar{D}_4 \bar{D}_2 \bar{D}_1$   
(c)  $D_8 D_1 + D_4 D_2 + \bar{D}_8 \bar{D}_4 \bar{D}_2 \bar{D}_1$   
(d)  $D_4 D_2 \bar{D}_1 + D_4 D_2 D_1 + D_8 \bar{D}_4 D_2 D_1$  [1990 : 1 Mark]

4.2 The logic realized by the circuit shown in figure is

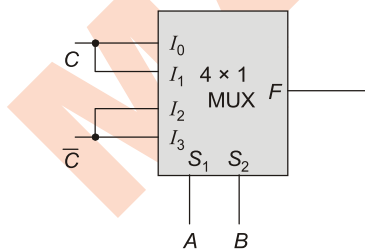- 
- (a)  $F = A \odot C$  (b)  $F = A \oplus C$   
(c)  $F = B \odot C$  (d)  $F = B \oplus C$  [1992 : 1 Mark]


#### 5. Sequential Circuits

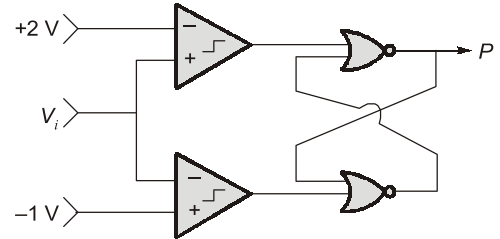5.1 Choose the correct statements relating to the circuit of figure




- (a) For  $V_i = -2\text{ V}$ ,  $P = 0$   
(b) For  $V_i = +3\text{ V}$ ,  $P = 0$   
(c) For  $V_i = 0\text{ V}$ ,  $P = 0$  always  
(d) For  $V_i = 0\text{ V}$ ,  $P$  can be either 0 or 1. [1987 : 1 Mark]

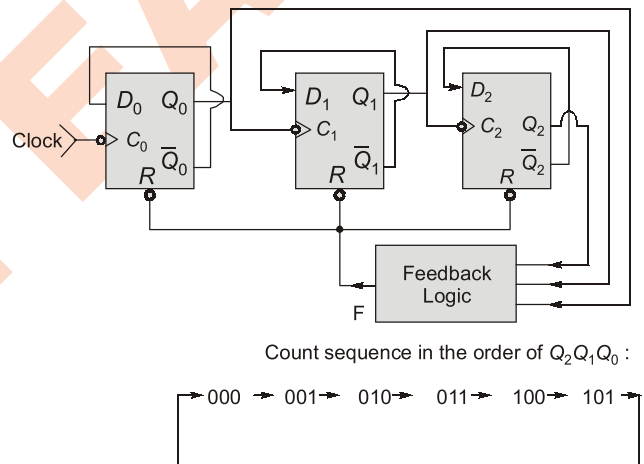5.2 A ripple counter using negative edge-triggered D-flip flops is shown in figure below. The flip-flops are cleared to '0' at the R input. The feedback logic is a to be designed to obtain the count sequence shown in the same figure. The correct feedback logic is:



- (a)  $F = \bar{Q}_2 Q_1 \bar{Q}_0$  (b)  $F = Q_2 \bar{Q}_1 \bar{Q}_0$   
(c)  $F = \bar{Q}_2 \bar{Q}_1 Q_0$  (d)  $F = \bar{Q}_2 \bar{Q}_1 Q_0$  [1987 : 1 Mark]

5.3 The circuit given below is a

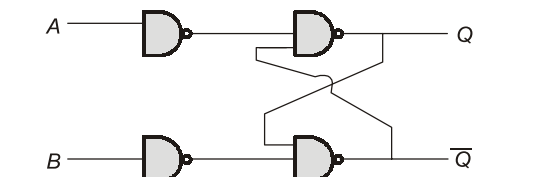- 
- (a) J-K Flip-flop (b) Johnson's counter  
(c) R-S latch (d) None of above. [1988 : 1 Mark]

5.4 A 4-bit modulo-16 ripple counter uses JK flip-flops. If the propagation delay of each FF is 50 ns, the maximum clock frequency that can be used is equal to:


- (a) 20 MHz (b) 10 MHz  
(c) 5 MHz (d) 4 MHz

[1990 : 1 Mark]

- 5.5 An *S-R* FLIP-FLOP can be converted into a *T* flip-flop by connecting to \_\_\_\_\_ *Q* and \_\_\_\_\_ to  $\bar{Q}$ .

[1991 : 1 Mark]

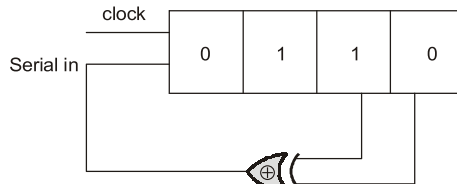- 5.6 The initial contents of the 4-bit serial-in-parallel-out, right-shift, Shift Register shown in the figure is 0110. After three clock pulses are applied, the contents of the Shift Register will be



- (a) 0000 (b) 0101  
(c) 1010 (d) 1111

[1992 : 1 Mark]

- 5.7 A pulse train with a frequency of 1 MHz is counted using a modulo-1024 ripple-counter built with *J-K* flip flops. For proper operation of the counter. The maximum permissible propagation delay per flip flop stage is \_\_\_\_\_ n sec.

[1993 : 1 Mark]

- 5.8 Synchronous counters are \_\_\_\_\_ than the ripple counters.

[1994 : 1 Mark]

- 5.9 A switch-tail ring counter is made by using a single *D* flip-flop. The resulting circuit is a  
(a) *SR* flip-flop (b) *JK* flip-flop  
(c) *D* flip-flop (d) *T* flip-flop

[1995 : 1 M]

- 5.10 An *R-S* latch is  
(a) combinatorial circuit  
(b) synchronous sequential circuit.  
(c) one bit memory element  
(d) one clock delay element

[1995 : 1 M]

## 6. Logic Families

- 6.1 Fill in the blanks of the statements below concerning the following Logic Families :

Standard TTL (74 XXLL), Low power TTL (74L XX)  
Low power schottky

TTL(74L SXX), Schottky TTL(74 SXX), Emitter coupled Logic (ECL), CMOS

- (a) Among the TTL Families, \_\_\_\_\_ family requires considerably less power than the standard TTL (74 XX) and also has comparable propagation delay.

- (b) Only the \_\_\_\_\_ family can operate over a wide range of power supply voltages

[1987 : 1 Mark]

- 6.2 Given that for a logic family,  
 $V_{OH}$  is the minimum output high-level voltage.  
 $V_{OL}$  is the maximum output-low-level voltage.  
 $V_{IH}$  is the minimum acceptable input high-level voltage and  
 $V_{IL}$  is the maximum acceptable input low-level voltage,

The correct relationship is

- (a)  $V_{IH} > V_{OH} > V_{IL} > V_{OL}$   
(b)  $V_{OH} > V_{IH} > V_{IL} > V_{OL}$   
(c)  $V_{IH} > V_{OH} > V_{OL} > V_{IL}$   
(d)  $V_{OH} > V_{IH} > V_{OL} > V_{IL}$

[1987 : 2 Marks]

- 6.3 Among the digital IC-families-ECL, TTL and CMOS:


- (a) ECL has the least propagation delay  
(b) TTL has the largest fan-out  
(c) CMOS has the biggest noise margin  
(d) TTL has the lowest power consumption

[1989 : 1 Mark]

- 6.4 A logic family has threshold voltage  $V_R = 2$  V, minimum guaranteed output high voltage  $V_{OH} = 4$  V, minimum accepted input high voltage  $V_{IH} = 3$  V, maximum guaranteed output low voltage  $V_{OL} = 1$  V, and maximum accepted input low voltage  $V_{IL} = 1.5$  V. Its noise margin is  
(a) 2 V (b) 1 V  
(c) 1.5 V (d) 0.5 V


[1989 : 1 Mark]

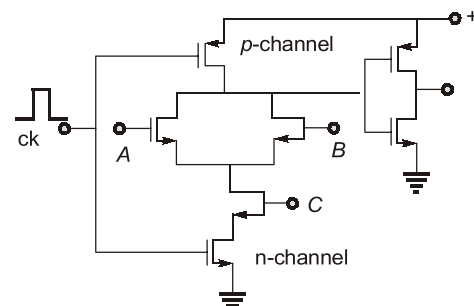- 6.5 In figure, the Boolean expression for the output in terms of inputs *A*, *B* and *C* when the clock 'ck' is high, is given by




[1991 : 1 Mark]

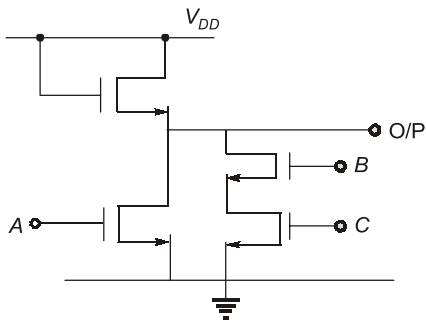- 6.6 The CMOS equivalent of the following  $n$ MOS gate (figure) is (draw the circuit).



[1991 : 1 Mark]

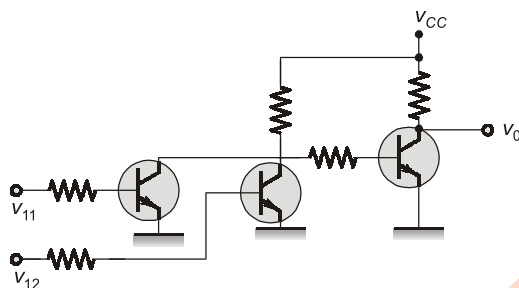- 6.7 Figure shows the circuit of a gate in the Resistor Transistor Logic (RTL) family. The circuit represents a



- (a) NAND (b) AND  
(c) NOR (d) OR [1992 : 1 Mark]

- 6.8 In the output stage of a standard TTL, we have a diode between the emitter of the pull-up transistor and the collector of the pull-down transistor. The purpose of this diode is to isolate the output node from the power supply  $V_{CC}$ .

[1994 : 2 Marks]

## 7. Memories

- 7.1 Choose the correct statement from the following:
- (a) PROM contains a programmable AND array and a fixed OR array.
  - (b) PLA contains a fixed AND array and a programmable OR array.
  - (c) PROM contains a fixed AND array and a programmable OR array.
  - (d) PLA contains a programmable AND array and a programmable OR array.

[1992 : 1 Mark]

- 7.2 A PLA can be
- (a) as a microprocessor
  - (b) as a dynamic memory

- (c) to realize a sequential logic
- (d) to realize a combinational logic.

[1994 : 1 Mark]

- 7.3 A dynamic RAM consists of

- (a) 6 transistors
- (b) 2 transistors and 2 capacitors
- (c) 1 transistor and 1 capacitor
- (d) 2 capacitors only

[1994 : 1 Mark]

- 7.4 The minimum number of MOS transistors required to make a dynamic RAM cell is


- (a) 1 (b) 2
- (c) 3 (d) 4

[1995 : 1 M]


## 8. ADC and DAC

- 8.1 Which of the resistance networks of figure can be used as 3 bit  $R$ - $2R$  ladder DAC. Assume  $V_0$  corresponds to LSB.


(i)

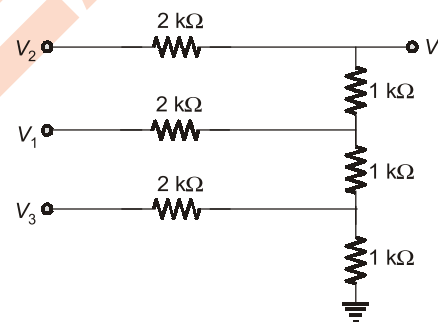

(ii)

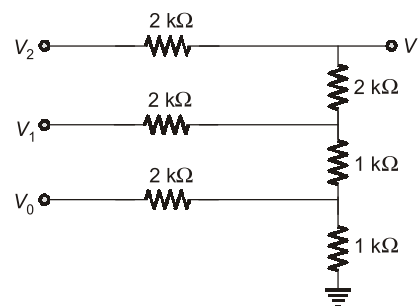

(iii)

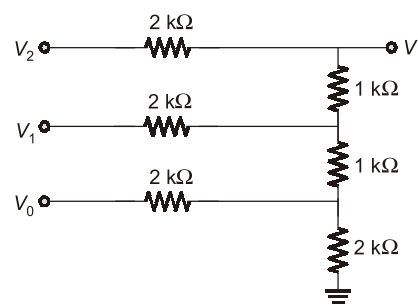

- (a) Both (i) and (ii)      (b) Both (i) and (ii)  
(c) Only (iii)              (d) Only (ii)

[1990 : 1 Mark]

8.2 (a) Successive approximation

(b) Dual-slope

(b) Parallel Comparator

Maximum conversion time for 8 bit ADC in clock cycles

- (1) 1              (2) 2              (3) 16  
(4) 256          (5) 512

[1994 : 1 Mark]

8.3 For an ADC, match the following: if

**List – I**

(A) Flash converter

(B) Dual slope converter

(C) Successive Approximation Converter

**List – II**

(1) requires a conversion time of the order of a few seconds

(2) requires a digital-to-analog converter

(3) minimizes the effect of power supply interference.

(4) requires a very complex hardware

(5) is a tracking A/D converter.

[1995 : 1 M]

■■■

**Answers Digital Circuits and Computer Organization**

1.1 (b, c)	1.2 (b)	2.1 (b)	3.1 (b)	3.2 (b)	3.3 (b, d)	3.4 (b, c)
3.5 (b)	3.6 (b)	3.7 (100)	3.8 (a)	3.9 (b)	4.1 (b)	4.2 (b)
4.3 (b)	4.4 (c)	5.1 (b)	5.2 (a)	5.3 (c)	5.4 (c)	5.5 (sol.)
5.6 (c)	5.7 (100)	5.8 (sol.)	5.9 (d)	5.10 (c)	6.1 (a, b)	6.2 (b)
6.3 (a)	6.4 (d)	6.5 (sol.)	6.6 (sol.)	6.7 (d)	6.8 (sol.)	7.1 (c, d)
7.2 (d)	7.3 (c)	7.4 (b)	8.1 (c)	8.2 (sol.)	8.3 (A-4, B-3, C-2)	

**Explanations Digital Circuits and Computer Organization****1. Number Systems****1.1 (b) & (c)**

Negative and is in 2's complement form.  
Positive and is in normal form

**1.2 (b)**

1

F F F F

1 1 1 1 1 1 1 1 1 1 1 1

2's complement

0 0 0 0 0 0 0 0 0 0 0 1

= 0 0 0 1

= 1

**2. Boolean Algebra****2.1 (b)**

Boolean functions possible are  $2^{2^n}$

**3. Logic Gates****3.1 (b)**

Output of 1<sup>st</sup> EX-OR gate

$$F_1 = X \oplus X = 0$$

Output of 2<sup>nd</sup> EX-OR gate


$$F_2 = X \oplus 0 = X$$

Output of 3<sup>rd</sup> EX-OR gate

$$F = X \oplus X = 0$$

**3.2 (b)**


$$F = (\bar{X} + \bar{Y})(Z + W) = (\bar{X}\bar{Y}) \cdot (Z + W) = \bar{X}\bar{Y}Z \cdot \bar{X}\bar{Y}W$$

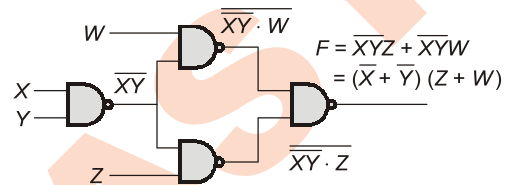**3.3 (b) & (d)**

NAND and NOR gates can be used to realize all possible combinational logic functions.

**3.4 (b) & (c)**

$$\bar{A}\bar{B} + AB \text{ and } (\bar{A} + B)(A + \bar{B})$$

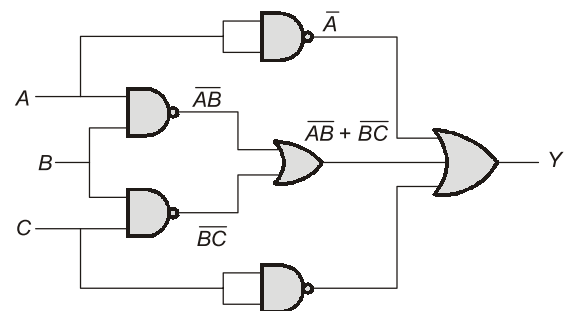**3.5 (b)**

$$Y = \bar{A} + \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}$$

$$Y = \bar{A} + (\bar{A} + \bar{B}) + (\bar{B} + \bar{C}) + \bar{C}$$

$$Y = \bar{A} + \bar{B} + \bar{C}$$

**3.6 (b)**

$$\text{NOR gate} \rightarrow F = \overline{A + B} = \bar{A}\bar{B}$$

$$\text{EX-NOR gate} \rightarrow F = A \odot B = \bar{A}\bar{B} + AB$$



**3.7 (100)**

$$f_{\text{clk}} = \frac{1}{2Nt_{\text{pdFF}}}$$

$$t_{\text{pdFF}} = \frac{1}{2Nf_{\text{clk}}} = \frac{1}{2 \times 5 \times 10^6}$$

$$t_{\text{pdFF}} = 100 \text{ nsec}$$

**3.8 (a)**

$$F = A + A\bar{B} + A\bar{B}C = A(1 + \bar{B} + \bar{B}C) = A$$

So, to implement A, zero NAND gates are required.

**3.9 (b)**

$$Y = (A \odot \bar{B}) \odot (\bar{A} \odot B)$$

$$Y = A \odot \bar{B} \odot \bar{A} \odot B$$

$$Y = (A \odot \bar{A}) \odot (\bar{B} \odot B) = 0 \odot 0$$

$$Y = 1$$

**4. Combinational Circuits****4.1 (b)**

Truth table:

	$D_8$	$D_4$	$D_2$	$D_1$	$Y$
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1

K-Map:

$D_8 D_4$ \ $D_2 D_1$	00	01	11	10
00	1	0	1	0
01	0	0	0	1
11	X	X	1	X
10	0	1	X	X

$$Y = D_8 D_1 + D_4 D_2 \bar{D}_1 + \bar{D}_4 D_2 D_1 + \bar{D}_8 \bar{D}_4 \bar{D}_2 \bar{D}_1$$

**4.2 (b)**


$$F = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C}$$

$$F = \bar{A}C(\bar{B} + B) + A\bar{C}(\bar{B} + B)$$

$$F = \bar{A}C + A\bar{C} = A \oplus C$$

**4.3 (b)**

Two bit binary multiplier

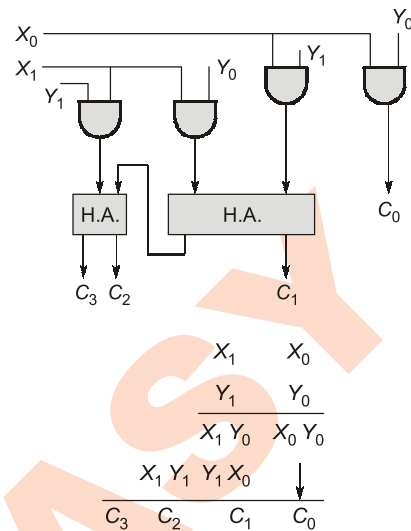**4.4 (c)**

$A$	$B$	$D$ (difference)	$X$ (borrow)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = A \oplus B = \bar{A}B + A\bar{B}$$

$$X = \bar{A}B$$

**5. Sequential Circuits****5.1 (b)**

For  $V_i = +3 \text{ V}$ ,  $P = 0$

When  $V_i = +3 \text{ V}$

Output of comparator 1 = logic 1

Output of comparator 2 = logic 0

$$P = 1 + (\text{output of 2nd NOR gate})$$

$$P = \bar{1}$$

$$P = 0$$

**5.2 (a)**

$$D_0 = \bar{Q}_0$$

$$D_1 = \bar{Q}_1$$

$$D_2 = \bar{Q}_2$$

So, flip-flop will be cleared at

$$\text{NAND gate} \rightarrow \frac{1}{Q_2} \frac{1}{Q_1} \frac{0}{Q_0}$$

**5.3 (c)** $R$ -S latch.**5.4 (c)**

$$f_{\text{clk}} = \frac{1}{nt_{\text{pdff}}}$$

$$= \frac{1}{4 \times 50 \times 10^{-9}} \quad \left\{ \begin{array}{l} 2^4 = 16 \\ n = 4 \end{array} \right.$$


$$f_{\text{clk}} = 5 \text{ MHz}$$

**5.5 Sol.**

$$S = T\bar{Q}_n$$

$$R = TQ_n$$

$S$ - $R$  flip-flop can be converted into  $T$ -flip-flop by connecting  $R$  to  $Q_n$  and  $S$  to  $\bar{Q}_n$ .

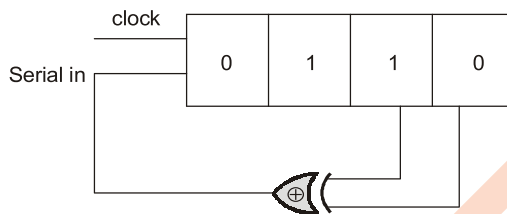**5.6 (c)**

$$\text{Serial in} = D_1 \oplus D_0$$

	0	1	1	0
1 <sup>st</sup> clk	1	0	1	1
2 <sup>nd</sup> clk	0	1	0	1
3 <sup>rd</sup> clk	1	0	1	0

**5.7 (100)**Ripple counter  $\rightarrow n$ -states

$$n = \log_2(1024) = 10$$

$$t_{\text{pdff}} = \frac{1}{nf_{\text{clk}}} = \frac{1}{10 \times 10^6} = 100 \text{ n-sec}$$

**5.8 Sol.**

Synchronous counters are faster than ripple counters.

**5.9 (d)**

If a switch tail ring counter using single  $D$  flip-flop, the complementary output  $\bar{Q}$  is connected to  $D$ , so it becomes a  $T$  flip-flop.

**5.10 (c)**

An  $R$ - $S$  latch is a one bit memory element.

## 6. Logic Families

**6.1 (a) & (b)**

74LS and CMOS.

**6.2 (b)**

$$V_{\text{OH}} > V_{\text{IH}} > V_{\text{IL}} > V_{\text{OL}}$$

**6.3 (a)**

ECL is the fastest logic family.

**6.4 (d)**

$$(\text{NM})_H = V_{\text{OH}} - V_{\text{IH}} = 4 - 3 = 1 \text{ V}$$

$$(\text{NM})_L = V_{\text{IL}} - V_{\text{OL}} = 1.5 - 1 = 0.5 \text{ V}$$


$$\text{Noise margin} = \min \text{ of } [(\text{NM})_H, (\text{NM})_L] \\ = 0.5 \text{ V}$$

**6.5 Sol.**

When clock is high then  $p$ -channel is off, so the input to CMOS is logic 0, then the output of the CMOS inverter is logic 1.

**6.6 Sol.**

CMOS circuit: PMOS and NMOS both

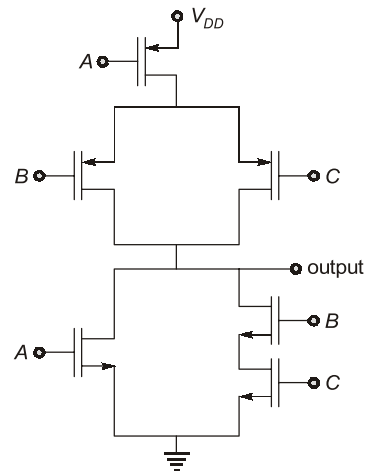

$$\text{Output} = \overline{A + BC}$$

**6.7 (d)**

Output  $V_o$  will be low when all the inputs are low. If any of the input is/are active high then the output will be high. So, the given circuit represents the OR gate.

**6.8 Sol.**

The purpose of keeping a diode is the output of TTL circuit is to keep pull-up transistor in the OFF state as long as pull-down transistor is the ON state.

**7. Memories****7.1 (c, d)**

PROM contains a fixed AND array and a programmable OR array

PLA contains a programmable AND array and a programmable OR array.

**7.2 (d)**

PLA is a type of fixed architecture logic devices with programmable AND gates followed by programmable OR gates. The PLA can be used to implement a complex combinational circuits.

**7.3 (c)**

A dynamic RAM consists of 1 transistor and 1 capacitor or 2 MOSFETs.

**8. ADC and DAC****8.1 (c)**

$R$ - $2R$  ladder DAC has  $R$  with ground &  $2R$  with input.

**8.2 Sol.**

(a) Successive approximation:

$$T_{\max} = nT_{\text{clk}} = 8T_{\text{clk}}$$

(b) Dual-slope:

$$\begin{aligned} T_{\max} &= 2^{n+1} T_{\text{clk}} = 2^{(8+1)} T_{\text{clk}} \\ &= 2^9 T_{\text{clk}} = 512 T_{\text{clk}} \end{aligned}$$

(c) Parallel Comparator:

$$T_{\max} = 1 T_{\text{clk}}$$

■■■

# Signals and Systems

## UNIT VII

### CONTENTS

1. Basics of Signals and Systems **73**
2. LTI Systems Continuous and Discrete (Time Domain) **73**
3. Fourier Series **73**
4. Fourier Transforms , Frequency Response and Correlation **73**
5. Laplace Transform **74**
6. Z-Transform **75**
7. Sampling **75**

## 1. Basics of Signals and Systems

- 1.1 An excitation is applied to a system at  $t = T$  and its response is zero for  $-\infty < t < T$ . Such a system is a  
 (a) non-causal system (b) stable system  
 (c) causal system (d) unstable system

[1991 : 2 Marks]


- 1.2 Which of the following signals is/are periodic?

- (a)  $s(t) = \cos 2t + \cos 3t + \cos 5t$   
 (b)  $s(t) = \exp(j8\pi t)$   
 (c)  $s(t) = \exp(-7t)\sin 10\pi t$   
 (d)  $s(t) = \cos 2t \cos 4t$

[1992 : 2 Marks]

## 2. LTI Systems Continuous and Discrete (Time Domain)

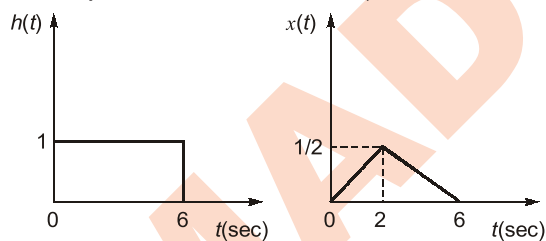- 2.1 The impulse response and the excitation function of a linear time invariant causal system are shown in figure (a) and (b) respectively. The output of the system at  $t = 2$  sec. is equal to



- (a) 0 (b)  $1/2$   
 (c)  $3/2$  (d) 1 [1990 : 2 Marks]

- 2.2 Let  $h(t)$  be the impulse response of a linear time invariant system. Then the response of the system for any input  $u(t)$  is

- (a)  $\int_0^t h(\tau)u(t-\tau)d\tau$   
 (b)  $\frac{d}{dt} \int_0^t h(\tau)u(t-\tau)d\tau$   
 (c)  $\int_0^t \left[ \int_0^t h(\tau)u(t-\tau)d\tau \right] dt$   
 (d)  $\int_0^t h^2(\tau)u(t-\tau)d\tau$

[1995 : 1 M]

## 3. Fourier Series

- 3.1 A half-wave rectified sinusoidal waveform has a peak voltage of 10 V. Its average value and the peak value of the fundamental component are respectively given by

- (a)  $\frac{20}{\pi}$  V,  $\frac{10}{\sqrt{2}}$  V (b)  $\frac{10}{\pi}$  V,  $\frac{10}{\sqrt{2}}$  V  
 (c)  $\frac{10}{\pi}$  V, 5 V (d)  $\frac{20}{\pi}$  V, 5 V

[1987 : 2 Marks]

- 3.2 Fourier series of the periodic function (period  $2\pi$ ) defined by

$$f(x) = \begin{cases} 0, & -\pi < x < 0 \\ x, & 0 < x < \pi \end{cases}$$

$$\text{is } \frac{\pi}{4} + \sum_{n=1}^{\infty} \left[ \frac{1}{\pi n^2} [\cos(n\pi) - 1] \cos(nx) - \frac{1}{n} \cos(n\pi) \sin(nx) \right].$$

By putting  $x = \pi$  in the above, one can deduce

that the sum of the series  $1 + \frac{1}{3^2} + \frac{1}{5^2} + \frac{1}{7^2} + \dots$  is

[1993 : 2 Marks]

- 3.3 The Fourier series of an odd periodic function, contains only

- (a) odd harmonics (b) even harmonics  
 (c) cosine terms (d) sine terms

[1994 : 1 Mark]

## 4. Fourier Transforms, Frequency Response and Correlation

- 4.1 Specify the filter type if its voltage transfer function  $H(s)$  is given by

$$H(s) = \frac{K(s^2 + \omega_0^2)}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

- (a) all pass filter (b) low pass filter  
 (c) band pass filter (d) notch filter

[1988 : 2 Marks]

4.2 The magnitude and phase functions for a distortionless filter should respectively be

(Magnitude) (Phase)

- (a) Linear Constant  
(b) Constant Constant  
(c) Constant Linear  
(d) Linear Linear

[1990 : 2 Marks]

4.3 If  $G(f)$  represents the Fourier transform of a signal  $g(t)$  which is real and odd symmetric in time, then

- (a)  $G(f)$  is complex  
(b)  $G(f)$  is imaginary  
(c)  $G(f)$  is real  
(d)  $G(f)$  is real and non-negative

[1992 : 2 Marks]

4.4 Match each of the items, A, B and C with an appropriate item from 1, 2, 3, 4 and 5.

List-I

- A. Fourier transform of a Gaussian function  
B. Convolution of a rectangular pulse with itself  
C. Current through an inductor for a step input voltage

List-II

1. Gaussian function  
2. Rectangular pulse  
3. Triangular pulse  
4. Ramp function  
5. Zero

[1995 : 2 M]

## 5. Laplace Transform

5.1 Laplace transforms of the functions  $tu(t)$  and  $u(t)$  are respectively:

- (a)  $\frac{1}{s^2}, \frac{s}{s^2 + 1}$  (b)  $\frac{1}{s}, \frac{1}{s^2 + 1}$   
(c)  $\frac{1}{s^2}, \frac{1}{s^2 + 1}$  (d)  $s, \frac{s}{s^2 + 1}$

[1987 : 2 Marks]

5.2 The Laplace transform of a function  $f(t)u(t)$ , where  $f(t)$  is periodic with period  $T$ , is  $A(s)$  times the Laplace transform of its first period. Then

- (a)  $A(s) = s$   
(b)  $A(s) = 1/(1 - \exp(-Ts))$   
(c)  $A(s) = 1/(1 + \exp(-Ts))$   
(d)  $A(s) = \exp(Ts)$

[1988 : 2 Marks]

5.3 The transfer function of a zero-order hold is

- (a)  $\frac{1 - \exp(-Ts)}{s}$  (b)  $1/s$   
(c) 1 (d)  $\frac{1}{[1 - \exp(-Ts)]}$

[1988 : 2 Marks]

5.4 The transfer function of a zero-order hold is

- (a)  $\frac{1 - \exp(-Ts)}{s}$  (b)  $1/s$   
(c) 1 (d)  $1/[1 - \exp(-Ts)]$


[1988 : 2 Marks]

5.5 The response of an initially relaxed linear constant parameter network to a unit impulse applied at  $t = 0$  is  $4e^{-2t}u(t)$ . The response of this network to a unit step function will be

- (a)  $2[1 - e^{-2t}]u(t)$  (b)  $4[e^{-t} - e^{-2t}]u(t)$   
(c)  $\sin 2t$  (d)  $(1 - 4e^{-4t})u(t)$

[1990 : 2 Marks]

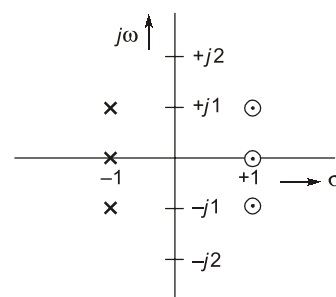5.6 The pole-zero pattern of a certain filter is shown in figure. The filter must be of the following type



- (a) low-pass (b) high-pass  
(c) all-pass (d) band-pass

[1991 : 2 Marks]

5.7 The voltage across an impedance in a network is  $V(s) = Z(s)I(s)$ , where  $V(s)$ ,  $Z(s)$  and  $I(s)$  are the Laplace transform of the corresponding time functions  $v(t)$ ,  $z(t)$  and  $i(t)$ . The voltage  $v(t)$  is


- (a)  $v(t) = z(t) \cdot i(t)$   
(b)  $v(t) = \int_0^t i(\tau)z(t - \tau)d\tau$   
(c)  $v(t) = \int_0^t i(\tau)z(t + \tau)d\tau$   
(d)  $v(t) = z(t) + i(t)$

[1991 : 2 Marks]

- 5.8 The Laplace transform of the periodic function  $f(t)$  described by the curve below, i.e.

$$f(t) = \begin{cases} \sin t & \text{if } (2n-1)\pi \leq t \leq 2n\pi \quad (n = 1, 2, 3, \dots) \\ 0 & \text{otherwise} \end{cases}$$

is \_\_\_\_\_.

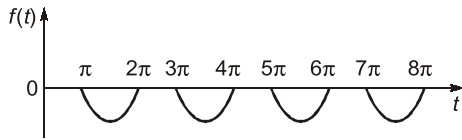

[1993 : 2 Marks]

- 5.9 If  $F(s) = L[f(t)] = \frac{K}{(s+1)(s^2+4)}$  then  $\lim_{t \rightarrow \infty} f(t)$  is given by
- (a)  $K/4$  (b) zero  
(c) infinite (d) undefined

[1993 : 2 Marks]

- 5.10 The Laplace transform of a unit ramp function starting at  $t = a$ , is

(a)  $\frac{1}{(s+a)^2}$  (b)  $\frac{e^{-as}}{(s+a)^2}$   
(c)  $\frac{e^{-as}}{s^2}$  (d)  $\frac{a}{s^2}$

[1994 : 1 Mark]

- 5.11 Indicate whether the following statement is TRUE/FALSE, Give reason for your answer. If  $G(s)$  is a stable transfer function, the  $F(s) = \frac{1}{G(s)}$  is always a stable transfer function.

[1994 : 1 Mark]

- 5.12 If  $L[f(t)] = \frac{2(s+1)}{s^2+2s+5}$ , then  $f(0^+)$  and  $f(\infty)$  are given by
- (a) 0, 2 respectively  
(b) 2, 0 respectively  
(c) 0, 1 respectively  
(d) 2/5, 0 respectively

[Note: 'L' stands for 'Laplace transform of']

[1995 : 1 M]

- 5.13 The transfer function of a linear system is the
- (a) ratio of the output,  $v_o(t)$ , and input,  $v_i(t)$   
(b) ratio of the derivatives of the output and the input  
(c) ratio of the Laplace transform of the output and that of the input with all initial conditions zeros  
(d) none of these


[1995 : 1 M]

- 5.14 The final value theorem is used to find the
- (a) steady state value of the system output  
(b) initial value of the system output  
(c) transient behaviour of the system output  
(d) none of these

[1995 : 1 M]

## 6. Z-Transform

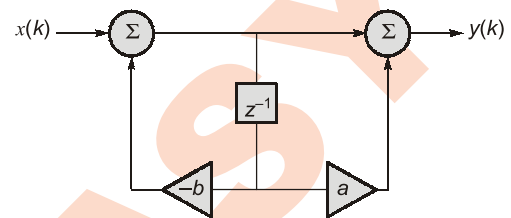- 6.1 Consider the system shown in the figure below. The transfer function  $Y(z)/X(z)$  of the system is



(a)  $\frac{1+az^{-1}}{1+bz^{-1}}$  (b)  $\frac{1+bz^{-1}}{1+az^{-1}}$   
(c)  $\frac{1+az^{-1}}{1-bz^{-1}}$  (d)  $\frac{1-bz^{-1}}{1+az^{-1}}$

[1988 : 2 Marks]

- 6.2 The z-transform of the following real exponential sequence
- $$x(nT) = a^n, nT \geq 0$$
- $$= 0, nT < 0, a > 0$$

(a)  $\frac{1}{1-z^{-1}}; |z| > 1$  (b)  $\frac{1}{1-az^{-1}}; |z| > a$   
(c) 1 for all  $z$  (d)  $\frac{1}{1-az^{-1}}; |z| < a$

[1990 : 2 Marks]

- 6.3 A linear discrete-time system has the characteristics equation,  $z^3 - 0.81z = 0$ . The system
- (a) is stable  
(b) is marginally stable  
(c) is unstable  
(d) stability cannot be assessed from the given information

[1992 : 2 Marks]


## 7. Sampling

- 7.1 A signal containing only two frequency components (3 kHz and 6 kHz) is sampled at the rate of 8 kHz, and then passed through a low pass filter with a cut-off frequency of 8 kHz. The filter output

- (a) is an undistorted version of the original signal
- (b) contains only the 3 kHz component
- (c) contains the 3 kHz component and a spurious component of 2 kHz
- (d) contains both the components of the original signal and two spurious components of 2 kHz and 5 kHz.

[1988 : 2 Marks]

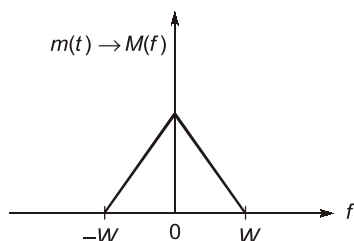- 7.2 Increased pulse-width in the flat-top sampling, leads to



- (a) attenuation of high frequencies in reproduction
- (b) attenuation of low frequencies in reproduction
- (c) greater aliasing errors in reproduction
- (d) no harmful effects in reproduction

[1994 : 1 Mark]

- 7.3 A 1.0 kHz signal is flat-top sampled at the rate of 1800 samples/sec and the samples are applied to an ideal rectangular LPF with cut-off frequency of 1100 Hz, then the output of the filter contains
- (a) only 800 Hz component
  - (b) 800 Hz and 900 Hz components
  - (c) 800 Hz and 1000 Hz components
  - (d) 800 Hz, 900 Hz and 1000 Hz components

[1995 : 1 M]

■■■

## Answers Signals and Systems

1.1	(c)	1.2	(a, b, d)	2.1	(b)	2.2	(a)	3.1	(c)	3.2	(1.23)	3.3	(d)
4.1	(d)	4.2	(c)	4.3	(b)	4.4	(A-1, B-3, C-4)	5.1	(c)	5.2	(b)		
5.3	(a)	5.4	(a)	5.5	(a)	5.6	(c)	5.7	(b)	5.8	(sol.)	5.9	(d)
5.10	(c)	5.11	(sol.)	5.12	(b)	5.13	(c)	5.14	(a)	6.1	(a)	6.2	(b)
6.3	(a)	7.1	(d)	7.2	(a)	7.3	(c)						

## Explanations Signals and Systems

### 1. Basics of Signals and Systems

1.1 (c)

For the given system if the response is zero prior to the application of the excitation. Then such a system is called causal system.

1.2 (a, b, d)

- (a)  $s(t)$  is periodic as the ratio of any two frequencies  $= \frac{p}{q}$  is rational where  $p$  and  $q$  are integers.

- (b)  $s(t)$  is periodic with  $\omega = 8\pi$

- (d)  $2\cos A \cos B = \cos(A - B) + \cos(A + B)$

$$s(t) = \frac{1}{2} [\cos 2t + \cos 6t]$$

So,  $s(t)$  is periodic with fundamental frequency 2 rad/sec.

### 2. LTI Systems Continuous and Discrete (Time Domain)

2.1 (b)

For causal LTI system

$$h(t) = 0 \quad \text{for } t < 0$$

$$y(t) = x(t) * h(t)$$

$$y(t) = \int_{-\infty}^{\infty} x(\tau) h(t - \tau) d\tau$$


$$y(t) = \int_0^t x(\tau) h(t - \tau) d\tau$$

as  $x(t) = 0 \quad t < 0$

and  $h(t) = 0 \quad t < 0$
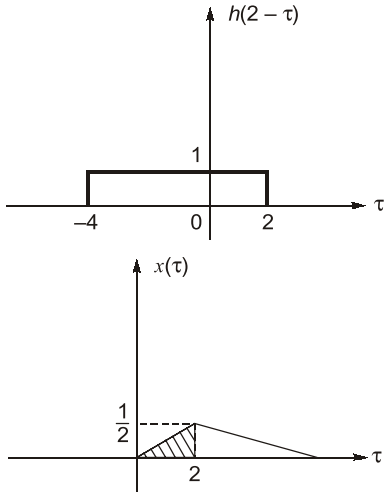
$$y(2) = \int_0^2 x(\tau) h(2 - \tau) d\tau$$





$$\text{So, } y(2) = \frac{1}{2} \times \left( 2 \times \frac{1}{2} \right)$$

$$y(2) = \frac{1}{2}$$

**2.2 (a)**


For LTI system

$$y(t) = u(t) * h(t)$$

$$y(t) = \int_{-\infty}^{\infty} h(\tau) u(t - \tau) d\tau$$

$$\therefore u(t) = 0 \text{ for } t < 0$$

$$y(t) = \int_0^t h(\tau) u(t - \tau) d\tau$$

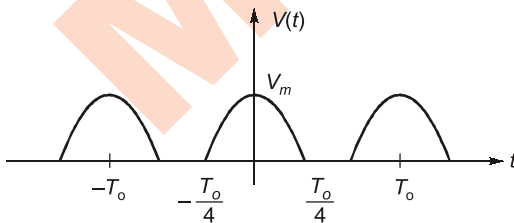**3. Fourier Series****3.1 (c)**

$$V(t) = V_m \cos(\omega_o t) \quad |t| \leq \frac{T_o}{4}$$

Time period =  $T_o$

$$f_o = \frac{1}{T_o} = \text{fundamental frequency}$$

$$= 1^{\text{st}} \text{ harmonics}$$

Fourier series of  $v(t)$  is given by

$$v(t) = a_0 + a_1 \cos(\omega_o t) + a_2 \cos(2\omega_o t) + \dots$$

$a_0$  = dc value = average value

$$a_0 = \frac{1}{T_o} \int_{T_o} v(t) dt$$

$$= \frac{1}{T_o} \int_{-T_o/4}^{T_o/4} V_m \cos(\omega_o t) dt$$

$$a_0 = \frac{1}{T_o} \frac{V_m [\sin \omega_o t]_{-T_o/4}^{T_o/4}}{\omega_o}$$

$$a_0 = \frac{V_m}{T_o} \frac{2\pi}{T_o} \left[ \sin\left(\frac{2\pi}{T_o} \cdot \frac{T_o}{4}\right) - \sin\left\{\frac{2\pi}{T_o} \left(-\frac{T_o}{4}\right)\right\} \right]$$

$$a_0 = \frac{V_m}{2\pi} \left[ \sin\left(\frac{\pi}{2}\right) - \sin\left(-\frac{\pi}{2}\right) \right]$$

$$= \frac{V_m}{2\pi} [1 - (-1)] = \frac{V_m}{2\pi} \times 2$$

$$a_0 = \frac{V_m}{\pi}$$

$$\text{So, average value} = a_0 = \frac{V_m}{\pi} = \frac{10}{\pi} V$$

$$a_1 = \frac{2}{T_o} \int_{T_o} v(t) \cos(\omega_o t) dt$$

$$a_1 = \frac{2}{T_o} \int_{-T_o/4}^{T_o/4} V_m \cos(\omega_o t) \cos(\omega_o t) dt$$

$$a_1 = \frac{2}{T_o} \int_{-T_o/4}^{T_o/4} V_m \cos^2(\omega_o t) dt$$

$$a_1 = \frac{2V_m}{T_o} \int_{-T_o/4}^{T_o/4} \frac{(1 + \cos 2\omega_o t)}{2} dt$$


$$a_1 = \frac{2V_m}{2T_o} \left[ \int_{-T_o/4}^{T_o/4} dt + \int_{-T_o/4}^{T_o/4} \cos 2\omega_o t dt \right]$$

$$a_1 = \frac{V_m}{T_o} \times \left[ \frac{T_o}{4} - \left(-\frac{T_o}{4}\right) \right] = \frac{V_m}{T_o} \times \frac{T_o}{2}$$

$$a_1 = \frac{V_m}{2}$$

$$V_m = 10$$

$$\text{So, } a_1 = \frac{10}{2} = 5 V$$

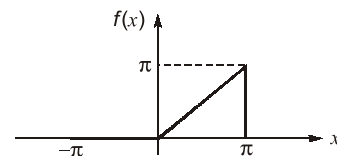**3.2 (1.23)**

Time period =  $T = \pi - (-\pi) = 2\pi$

At the point of discontinuity  $x = \pi$

$f(x)$  expressed in Fourier series converge to the middle value =  $\frac{\pi}{2}$ .

From the given trigonometric form of Fourier series, at  $x = \pi$ .

$$f(\pi) = \frac{\pi}{4} + \frac{2}{\pi}s = \frac{\pi}{2}$$

where,  $s = 1 + \frac{1}{3^2} + \frac{1}{5^2} + \dots$

$$\frac{2}{\pi}s = \frac{\pi}{2} - \frac{\pi}{4} = \frac{\pi}{4}$$

$$s = \frac{\pi^2}{8}$$

### 3.3 (d)

The Fourier series of an odd periodic function does not contain the dc term ( $a_0 = 0$ ) and cosine terms. The Fourier series of an odd periodic function contains only sine terms.

## 4. Fourier Transforms , Frequency Response and Correlation

### 4.1 (d)

Given that,

$$H(s) = \frac{K(s^2 + \omega_0^2)}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$$

$$s = j\omega$$

$$H(0) = \frac{K(0 + \omega_0^2)}{0 + 0 + \omega_0^2} = K$$

$$H(0) \neq 0$$

$$H(\infty) = \frac{Ks^2 \left(1 + \frac{\omega_0^2}{s^2}\right)}{s^2 \left(1 + \left(\frac{\omega_0}{Q}\right)\frac{1}{s} + \frac{\omega_0^2}{s^2}\right)}$$

$$H(\infty) = \frac{K(1+0)}{1+0+0} = K$$

$$H(\infty) \neq 0$$

Here the given transfer function is a notch filter.

### 4.2 (c)

For distortionless transmission

$$|H(f)| = \text{constant and}$$

$$\angle H(f) = -kf, \text{ where } k \text{ is a constant}$$

$H(f)$  is the transfer function.

So, the magnitude function of a distortionless filter should be constant.

The phase function of a distortionless filter should be linear.

### 4.3 (b)

Fourier transform of real and odd symmetric signal is imaginary and odd function of frequency.

### 4.4 Sol.

(A) - 1, (B) - 3, (C) - 4

(A) Fourier transform of a Gaussian function is also a Gaussian function

$$e^{-\pi t^2} \xleftrightarrow{F.T.} e^{-\pi f^2}$$

(B) Convolution of a rectangular pulse with itself is a triangular pulse.

(C) Current through an inductor for a step input voltage is ramp function

$$i = \frac{1}{L} \int V dt = \frac{1}{L} \int u(t) dt = \frac{1}{L} r(t)$$

## 5. Laplace Transform

### 5.1 (c)

$$tu(t) \xleftrightarrow{L.T.} \frac{1}{s^2}$$

$$u(t) \sin at \xleftrightarrow{L.T.} \frac{a}{s^2 + a^2}$$

$$u(t) \sin t \xleftrightarrow{L.T.} \frac{1}{s^2 + 1^2} = \frac{1}{s^2 + 1}$$

### 5.2 (b)


The given function represents a causal periodic signal.


$$f(t)u(t) = 0 \quad t < 0$$

$$\text{Period of } f(t) = T \quad \text{for } t > 0$$

$$\text{Let } f_1(t) = f(t)u(t) \quad 0 \leq t \leq T$$

$$= 0 \quad \text{otherwise}$$

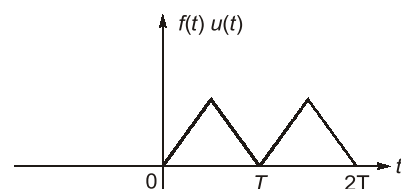

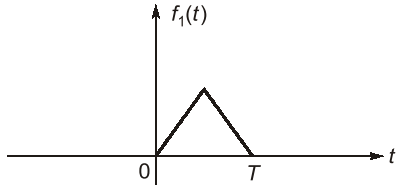

$$f(t) u(t) = \sum_{n=0}^{\infty} f_1(t - nT)$$

Let,  $f_1(t) \rightarrow F_1(s)$


$$f_1(t - nT) \rightarrow e^{-nTs} F_1(s)$$

$$\begin{aligned} f(t) u(t) \rightarrow F(s) &= \sum_{n=0}^{\infty} e^{-nTs} F_1(s) \\ &= \frac{F_1(s)}{1 - e^{-Ts}} \end{aligned}$$

$$\begin{aligned} f(t) u(t) &\rightarrow \left[ \frac{1}{1 - e^{-Ts}} \right] \times \left[ \text{Transform of the 1st} \right. \\ &\quad \left. \text{period of } f(t) u(t) \right] \\ A(s) &= \frac{1}{1 - e^{-Ts}} \end{aligned}$$

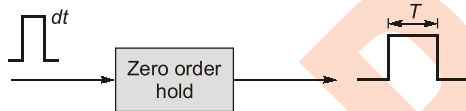**5.3 (a)**

A zero order hold system holds the input signal value for a period of  $T$ , i.e. for an input of short duration ( $\Delta$ ) pulse, it produces an output pulse of duration  $T$ , the sampling period.



Input,  $x(t) = \delta(t)$

So,  $X(s) = 1$

Output,  $y(t) = u(t) - u(t - T)$

So,  $Y(s) = \frac{1}{s} - \frac{e^{-Ts}}{s} = \frac{1 - e^{-Ts}}{s}$

Transfer function,

$$H(s) = \frac{Y(s)}{X(s)} = \frac{1 - e^{-Ts}}{s}$$

**5.4 (a)**

The impulse response  $h(t)$  of zero order hold system is

$$h(t) = u(t) - u(t - T)$$

Where  $T$  is the sampling period.

$$H(s) = \frac{1}{s} - \frac{1}{s} e^{-Ts}$$

$$H(s) = \frac{1 - \exp(-Ts)}{s}$$

**5.5 (a)**

Given that,  $h(t) = 4e^{-2t}$

So,  $H(s) = 4 \frac{1}{(s+2)}$

Given that

$$x(t) = u(t)$$

So,  $X(s) = \frac{1}{s}$

We know that,

$$H(s) = \frac{Y(s)}{X(s)}$$

$$Y(s) = H(s) X(s)$$

$$Y(s) = \frac{4}{(s+2)} \times \frac{1}{s} = 2 \left[ \frac{1}{s} - \frac{1}{s+2} \right]$$

Taking inverse Laplace transform on both side.

$$y(t) = 2[1 - e^{-2t}]u(t)$$

**5.6 (c)**

In the given pole-zero pattern, poles and zeros are symmetrical about imaginary axis. This is the case of all-pass filter.

**5.7 (b)**

We know that,



Multiplication of two functions in frequency ( $s$ ) domain is equivalent to the convolution in time domain.


$$\text{So, } v(t) = \int_0^t i(\tau) z(t - \tau) d\tau$$

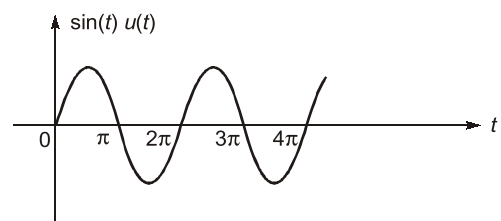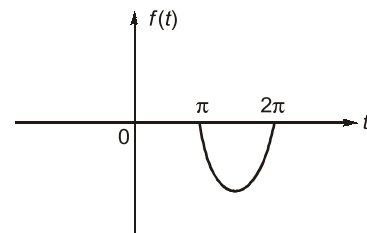**5.8 Sol.**

The given signal  $f(t)$  is a causal periodic signal with period,  $T_0 = 2\pi$

$$\begin{aligned} f_1(t) &= f(t) & 0 < t < 2\pi \\ &= 0 & \text{otherwise} \end{aligned}$$



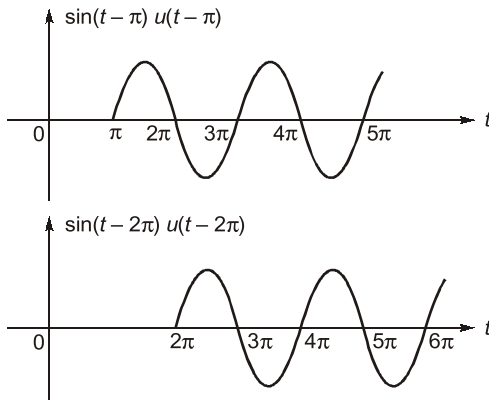

$$\text{So, } f_1(t) = -[\sin(t - \pi)u(t - \pi) + \sin(t - 2\pi)u(t - 2\pi)]$$

$$\sin(t) u(t) \rightarrow \frac{1}{s^2 + 1}$$

$$\sin(t - \pi) u(t - \pi) \rightarrow \frac{e^{-\pi s}}{s^2 + 1}$$

$$\sin(t - 2\pi) u(t - 2\pi) \rightarrow \frac{e^{-2\pi s}}{s^2 + 1}$$

$$F_1(s) = -\left[\frac{e^{-\pi s}}{s^2 + 1} + \frac{e^{-2\pi s}}{s^2 + 1}\right]$$

$$F_1(s) = -e^{-\pi s} \left[ \frac{1 + e^{-\pi s}}{s^2 + 1} \right]$$

$$F(s) = \frac{F_1(s)}{1 - e^{-T_0 s}} = \frac{F_1(s)}{1 - e^{-2\pi s}}$$

$$F(s) = -e^{-\pi s} \left[ \frac{1 + e^{-\pi s}}{s^2 + 1} \right] \times \frac{1}{(1 - e^{-2\pi s})}$$

$$F(s) = -e^{-\pi s} \frac{(1 + e^{-\pi s})}{(s^2 + 1)(1 + e^{-\pi s})(1 - e^{-\pi s})}$$

$$F(s) = \frac{-e^{-\pi s}}{(s^2 + 1)(1 - e^{-\pi s})}$$

**5.9 (d)**

$$F(s) = \frac{K}{(s + 1)(s^2 + 4)}$$

So, poles =  $-1, \pm 2j$

Since all the poles are not in the left half of s-plane.

So, the final value theorem cannot be applied.

So,  $\lim_{t \rightarrow \infty} f(t)$  is indeterminate.

**5.10 (c)**

$$r(t) \xrightarrow{\text{L.T.}} \frac{1}{s^2}$$

$$r(t - a) \xrightarrow{\text{L.T.}} e^{-as} \times \frac{1}{s^2} = \frac{e^{-as}}{s^2}$$

**5.11 Sol.**

If  $G(s)$  is stable then all its poles must lie in the left half of s-plane and there is no restriction on its zeros, which can lie also in the right half of s-plane.

The inverse function  $F(s) = \frac{1}{G(s)}$  may or may not

be stable. The zeros of  $G(s)$  may lie in the right half of s-plane.

Hence the given statement is not true.

So,  $F(s) = \frac{1}{G(s)}$  is not always a stable transfer function.

**5.12 (b)**

Initial value theorem

$$f(0^+) = \lim_{s \rightarrow \infty} \frac{s2(s+1)}{s^2 + 2s + 5}$$

$$f(0^+) = \lim_{s \rightarrow \infty} \frac{2s^2 + 2s}{s^2 + 2s + 5}$$

$$f(0^+) = \lim_{s \rightarrow \infty} \frac{s^2(2 + 2/s)}{s^2\left(1 + \frac{2}{s} + \frac{5}{s^2}\right)}$$

$$f(0^+) = \lim_{s \rightarrow \infty} \frac{2 + 2/s}{1 + \frac{2}{s} + \frac{5}{s^2}} = \frac{2 + 0}{1 + 0 + 0} = 2$$

Final value theorem

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{s2(s+1)}{s^2 + 2s + 5}$$

$$f(\infty) = 0$$

**5.13 (c)**

$$H(s) = \frac{Y(s)}{X(s)}$$


**5.14 (a)**

Final value theorem is used to find the final value or the steady state value of the system output

$$f(\infty) = \lim_{s \rightarrow 0} sF(s)$$

## 6. Z-Transform

## 6.1 (a)

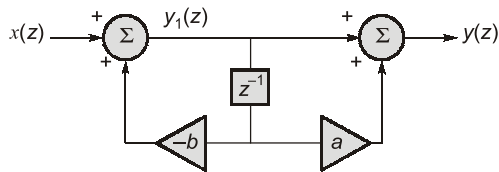

$$y_1(z) = x(z) - bz^{-1} y_1(z)$$

$$y_1(z)[1 + bz^{-1}] = x(z)$$

$$y_1(z) = \frac{x(z)}{(1 + bz^{-1})}$$

$$y(z) = y_1(z) + az^{-1} y_1(z)$$

$$y(z) = y_1(z) [1 + az^{-1}]$$

$$y(z) = \frac{x(z)}{(1 + bz^{-1})} \times (1 + az^{-1})$$

Transfer function

$$H(z) = \frac{y(z)}{x(z)} = \frac{1 + az^{-1}}{1 + bz^{-1}}$$

## 6.2 (b)

Given that

$$x(n) = a^n u(n) \quad a > 0$$

$$x(n) \xrightarrow{\text{Z.T.}} X(z) = \frac{z}{z - a}; |z| > |a|$$

$$X(z) = \frac{1}{1 - az^{-1}}; |z| > a$$

## 6.3 (a)

Given that,

Characteristic equation

$$z^3 - 0.81z = 0$$

$$z(z^2 - 0.81) = 0$$

$$z(z - 0.9)(z + 0.9) = 0$$

So, poles are  $z = 0, 0.9$  and  $-0.9$

As all the three poles are inside the unit circle, so the system is stable.

## 7. Sampling

## 7.1 (d)

$$f_s = 8000 \text{ samples/sec}$$

$$f_{m1} = 3 \text{ kHz}$$

$$f_{m2} = 6 \text{ kHz}$$

The spectrum of sampled signal would have

$$nf_s \pm f_m$$

So,

$$3 \text{ kHz}, 8 \pm 3, 16 \pm 3, \dots = 3 \text{ kHz}, 5 \text{ kHz},$$

$$11 \text{ kHz}, \dots$$

$$6 \text{ kHz}, 8 \pm 6, 16 \pm 6, \dots = 6 \text{ kHz}, 2 \text{ kHz},$$


$$14 \text{ kHz}, \dots$$

cut-off frequencies of L.P.F. = 8 kHz

So, the filter output would have

3 kHz, 6 kHz, 2 kHz and 5 kHz

## 7.2 (a)

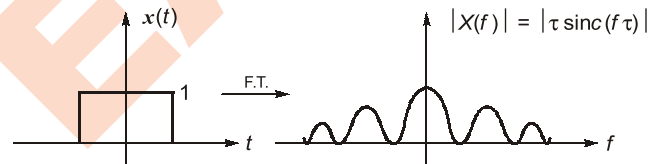

As pulse width  $\tau$  is increased, the width  $1/\tau$  of the first lobe of the spectrum is decreased.

Hence, increased pulse-width in the flat-top sampling, leads to attenuation of high frequencies in reproduction.

## 7.3 (c)

$$f_s = 1800 \text{ samples/sec}; \quad f_m = 1000 \text{ Hz}$$

The spectrum of sampled signal would have

$$nf_s \pm f_m$$

So,

$$1000 \text{ Hz}, 1800 \pm 1000 \text{ Hz}, 3600 \pm 1000 \text{ Hz} \dots$$

$$\text{So, } 1000 \text{ Hz}, 800 \text{ Hz}, 2800 \text{ Hz}, 2600 \text{ Hz}, 4600 \text{ Hz}, \dots$$

The cut-off frequency of LPF is 1100 Hz

So, the output of filter will contain

800 Hz and 1000 Hz components.

# Communication Systems

## UNIT VIII

### CONTENTS

1. Analog Communication Systems **83**
2. Random Signals and Noise **84**
3. Digital Communication Systems **85**
4. Information Theory and Coding **86**

## 1. Analog Communication Systems

- 1.1 In a superheterodyne AM receiver, the image channel selectivity is determined by
- The preselector and RF stages
  - the preselector, RF and IF stages
  - The IF stages
  - all the stages

[1987 : 2 Marks]

- 1.2 A carrier  $A_c \cos \omega_c t$  is frequency modulated by a signal  $E_m \cos \omega_m t$ . The modulation index is  $m_f$ . The expression for the resulting FM signal is
- $A_c \cos [\omega_c t + m_f \sin \omega_m t]$
  - $A_c \cos [\omega_c t + m_f \cos \omega_m t]$
  - $A_c \cos [\omega_c t + 2\pi m_f \sin \omega_m t]$
  - $A_c \cos \left[ \omega_c t + \frac{2\pi m_f E_m \cos \omega_m t}{\omega_m} \right]$

[1989 : 2 Marks]

- 1.3 Which of the following schemes suffer(s) from the threshold effect?
- AM detection using envelope detection
  - AM detection using synchronous detection
  - FM detection using a discriminator
  - SSB detection with synchronous detection

[1989 : 2 Marks]

- 1.4 A signal  $x(t) = 2 \cos (\pi \cdot 10^4 t)$  volts is applied to an FM modulator with the sensitivity constant of 10 kHz/volt. Then the modulation index of the FM wave is
- 4
  - 2
  - $4/\pi$
  - $2/\pi$

[1989 : 2 Marks]

- 1.5 In commercial TV transmission in India, picture and speech signals are modulated respectively as

(Picture)		(Speech)
(a) VSB	and	VSB
(b) VSB	and	SSB
(c) VSB	and	FM
(d) FM	and	VSB

[1990 : 2 Marks]

- 1.6 The maximum power efficiency of an AM modulator is
- 25%
  - 50%
  - 33%
  - 100%

[1992 : 2 Marks]

- 1.7 Which of the following demodulator(s) can be used for demodulating the signal  $x(t) = 5(1 + 2 \cos 200 \pi t) \cos 20000 \pi t$
- Envelope demodulator
  - Square-law demodulator
  - Synchronous demodulator
  - None of the above

[1993 : 2 Marks]

- 1.8 A superheterodyne radio receiver with an intermediate frequency of 455 kHz is tuned to a station operating at 1200 kHz. The associated image frequency is \_\_\_\_ kHz.

[1993 : 2 Marks]

- 1.9  $v(t) = 5[\cos(10^6 \pi t) - \sin(10^3 \pi t) \times \sin(10^6 \pi t)]$  represents
- DSB suppressed carrier signal
  - AM signal
  - SSB upper sideband signal
  - Narrow band FM signal

[1994 : 1 Mark]

- 1.10 A 10 MHz carrier is frequency modulated by a sinusoidal signal of 500 Hz, the maximum frequency deviation being 50 kHz. The bandwidth required, as given by the Carsons' rule is \_\_\_\_.

[1994 : 1 Mark]

- 1.11 Match List-I with List-II and select the correct answer using the code given below the Lists:

List-I	List-II
A. SSB	1. Envelope detector
B. AM	2. Integrate and dump
C. BPSK	3. Hilbert transform
	4. Ratio detector
	5. PLL

Codes:

	A	B	C
(a)	3	1	2
(b)	3	2	1
(c)	2	1	3
(d)	1	2	3

[1994 : 2 Marks]

1.12 The image (second) channel selectivity of a superheterodyne communication receiver is determined by

- (a) antenna and preselector
- (b) the preselector and RF amplifier
- (c) the preselector and IF amplifier
- (d) the RF and IF amplifier

[1995 : 1 M]

1.13 A PLL can be used to demodulate

- (a) PAM signals
- (b) PCM signals
- (c) FM signals
- (d) DSB - SC signals

[1995 : 1 M]

1.14 A PAM signal can be detected by using

- (a) an ADC
- (b) an integrator
- (c) a band pass filter
- (d) a high pass filter

[1995 : 1 M]

## 2. Random Signals and Noise

2.1 The variance of a random variable  $X$  is  $\sigma_x^2$ . Then the variance of  $-kx$  (Where  $k$  is an positive constant) is

- (a)  $\sigma_x^2$
- (b)  $-k \sigma_x^2$
- (c)  $k \sigma_x^2$
- (d)  $k^2 \sigma_x^2$

[1987 : 2 Marks]

2.2 White Gaussian noise is passed through a linear narrow band filter. The probability density function of the envelope of the noise at the filter output is

- (a) Uniform
- (b) Poisson
- (c) Gaussian
- (d) Rayleigh

[1987 : 2 Marks]

2.3 In a radar receiver the antenna is connected to the receiver through a waveguide. Placing the preamplifier on the antenna side of the waveguide rather than on the receiver side leads to

- (a) A reduction in the overall noise figure
- (b) A reduction in interference
- (c) An improvement in selectivity characteristics
- (d) An improvement in directional characteristics

[1987 : 2 Marks]

2.4 Zero mean Gaussian noise of variance  $N$  is applied to a half wave rectifier. The mean squared value of the rectifier output will be

- (a) Zero
- (b)  $N/2$
- (c)  $N/\sqrt{2}$
- (d)  $N$

[1989 : 2 Marks]

2.5 A part of a communication system consists of an amplifier of effective noise temperature,  $T_e = 21^\circ \text{K}$ , and a gain of 13 dB, followed by a cable with a loss of 3 dB. Assuming the ambient temperature to be  $300^\circ \text{K}$ , we have for this part of the communication system,


- (a) effective noise temperature =  $30^\circ \text{K}$
- (b) effective noise temperature =  $36^\circ \text{K}$
- (c) noise figure = 0.49 dB
- (d) noise figure = 1.61 dB

[1991 : 2 Marks]

2.6 Two resistors  $R_1$  and  $R_2$  (in ohms) at temperatures  $T_1^\circ \text{K}$  and  $T_2^\circ \text{K}$  respectively, are connected in series. Their equivalent noise temperature is \_\_\_\_\_  $^\circ \text{K}$ .

[1991 : 2 Marks]

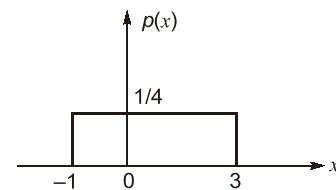2.7 For a random variable 'X' following the probability density function,  $p(x)$ , shown in figure, the mean and the variance are, respectively



- (a) 1/2 and 2/3
- (b) 1 and 4/3
- (c) 1 and 2/3
- (d) 2 and 4/3

[1992 : 2 Marks]

2.8 For a narrow band noise with Gaussian quadrature components, the probability density function of its envelope will be

- (a) uniform
- (b) Gaussian
- (c) exponential
- (d) Rayleigh

[1995 : 1 M]



### 3. Digital Communication Systems

- 3.1 Companding in PCM systems lead to improved signal to quantization noise ratio. This improvement is for
- lower frequency components only
  - higher frequency components only
  - lower amplitudes only
  - higher amplitudes only

[1987 : 2 Marks]

- 3.2 A signal having uniformly distributed amplitude in the interval  $(-V \text{ to } +V)$ , is to be encoded using PCM with uniform quantization. The signal to quantizing noise ratio is determined by the
- dynamic range of the signal
  - sampling rate
  - number of quantizing levels
  - power spectrum of signal

[1988 : 2 Marks]

- 3.3 The message bit sequence to a DPSK modulator is 1, 1, 0, 0, 1, 1. The carrier phase during the reception of the first two message bits is  $\pi, \pi$ . The carrier phase for the remaining four message bits is
- $\pi, \pi, 0, \pi$
  - $0, 0, \pi, \pi$
  - $0, \pi, \pi, \pi$
  - $\pi, \pi, 0, 0$

[1988 : 2 Marks]

- 3.4 In a digital communication system, transmissions of successive bits through a noisy channel are assumed to be independent events with error probability  $p$ . The probability of at most one error in the transmission of an 8-bit sequence is

- $\frac{7(1-p)}{8} + \frac{p}{8}$
- $(1-p)^8 + 8p(1-p)^7$
- $(1-p)^8 + (1-p)^7$
- $(1-p)^8 + p(1-p)^7$

[1988 : 2 Marks]

- 3.5 In binary data transmission DPSK is preferred to PSK because
- a coherent carrier is not required to be generated at the receiver
  - for a given energy per bit, the probability of error is less
  - the  $180^\circ$  phase shifts of the carrier are unimportant
  - more protection is provided against impulse noise

[1989 : 2 Marks]

- 3.6 A 4 GHz carrier is DSB-SC modulated by a low pass message signal with maximum frequency of 2 MHz. The resultant signal is to be ideally sampled. The minimum frequency of the sampling impulse train should be
- 4 MHz
  - 8 MHz
  - 8 GHz
  - 8.004 GHz

[1990 : 2 Marks]


- 3.7 In a BPSK signal detector, the local oscillator has a fixed phase error of  $20^\circ$ . This phase error deteriorates the SNR at the output by a factor of
- $\cos 20^\circ$
  - $\cos^2 20^\circ$
  - $\cos 70^\circ$
  - $\cos^2 70^\circ$

[1990 : 2 Marks]

- 3.8 A signal has frequency components from 300 Hz to 1.8 kHz. The minimum possible rate at which the signal has to be sampled is

[1991 : 2 Marks]

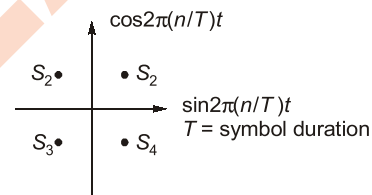- 3.9 For the signal constellation shown in the figure, the type of modulation is



[1991 : 2 Marks]

- 3.10 A signal has frequency components from 300 Hz to 1.8 kHz. The minimum possible rate at which the signal has to be sampled is \_\_\_\_\_ (fill in the blank)

[1991 : 2 Marks]

- 3.11 The bit stream 01001 is differentially encoded using 'Delay and Ex OR' scheme for DPSK transmission. Assuming the reference bit as a '1' and assigning phases of '0' and ' $\pi$ ' for 1's and 0's respectively, in the encoded sequence, the transmitted phase sequence becomes

- $\pi 0 \pi \pi 0$
- $0 \pi \pi 0 0$
- $0 \pi \pi \pi 0$
- $\pi \pi 0 \pi \pi$

[1992 : 2 Marks]

- 3.12 Coherent demodulation of FSK signal can be detected using

- correlation receiver
- bandpass filters and envelope detectors
- matched filter
- discriminator detection

[1992 : 2 Marks]

- 3.13** Source encoding in a data communication system is done in order to  
 (a) enhance the information transmission  
 (b) bandpass filters and envelope rate detectors  
 (c) conserve the transmitted power  
 (d) discriminator detection [1992 : 2 Marks]

- 3.14** Sketch the waveform (with properly marked axes) at the output of a matched filter matched for a signal  $s(t)$ , of duration  $T$ , given by

$$s(t) = \begin{cases} A & \text{for } 0 \leq t < \frac{2}{3}T \\ 0 & \text{for } \frac{2}{3}T \leq t < T \end{cases}$$

[1993 : 2 Marks]

- 3.15** Increased pulse width in the flat top sampling, leads to  
 (a) attenuation of high frequencies in reproduction  
 (b) attenuation of low frequencies in reproduction  
 (c) greater aliasing errors in reproduction  
 (d) no harmful effects in reproduction

[1994 : 1 Mark]

- 3.16** The bandwidth required for the transmission of a PCM signal increases by a factor of \_\_\_\_ when the number of quantization levels is increased from 4 to 64.

[1994 : 1 Mark]

- 3.17** If the number of bits per sample in a PCM system is increased from a  $n$  to  $n + 1$ , the improvement in signal to quantization noise ratio will be  
 (a) 3 dB (b) 6 dB  
 (c)  $2n$  dB (d)  $n$  dB [1995 : 1 M]

- 3.18** A 1.0 kHz signal is flat top sampled at the rate of 1800 samples/sec and the samples are applied to an ideal rectangular LPF with cut-off frequency of 1100 Hz, then the output of the filter contains  
 (a) only 800 Hz component  
 (b) 800 Hz and 900 Hz components  
 (c) 800 Hz and 1000 Hz components  
 (d) 800 Hz, 900 Hz and 100 Hz components

[1995 : 1 M]

- 3.19** The signal to quantization noise ratio in an  $n$ -bit PCM system  
 (a) depends upon the sampling frequency employed  
 (b) is independent of the value of ' $n$ '  
 (c) increasing with increasing value of ' $n$ '  
 (d) decreases with the increasing value of ' $n$ '

[1995 : 1 M]

- 3.20** For a given data rate, the bandwidth  $B_p$  of a BPSK signal and the bandwidth  $B_0$  of the OOK signal are related as

- (a)  $B_p = B_0/4$  (b)  $B_p = B_0/2$   
 (c)  $B_p = B_0$  (d)  $B_p = 2B_0$

[1995 : 1 M]

#### 4. Information Theory and Coding

- 4.1** A source produces 4 symbols with probability  $\frac{1}{2}, \frac{1}{4}, \frac{1}{8}$  and  $\frac{1}{8}$ . For this source, a practical coding

scheme has an average codeword length of 2 bits/symbols. The efficiency of the code is

- (a) 1 (b)  $7/8$   
 (c)  $1/2$  (d)  $1/4$

[1989 : 2 Marks]

- 4.2** An image uses  $512 \times 512$  picture elements. Each of the picture elements can take any of the 8 distinguishable intensity levels. The maximum entropy in the above image will be  
 (a) 2097152 bits (b) 786432 bits  
 (c) 648 bits (d) 144 bits

[1990 : 2 Marks]

■■■

**Answers Communication Systems**

1.1 (a)	1.2 (a)	1.3 (c)	1.4 (a)	1.5 (c)	1.6 (b)	1.7 (c)
1.8 (2110)	1.9 (d)	1.10 (101)	1.11 (a)	1.12 (b)	1.13 (c)	1.14 (b)
2.1 (d)	2.2 (d)	2.3 (a)	2.4 (b)	2.5 (b, c)	2.6 (sol.)	2.7 (b)
2.8 (d)	3.1 (c)	3.2 (c)	3.3 (c)	3.4 (b)	3.5 (a)	3.6 (b)
3.7 (b)	3.8 (3600)	3.9 (sol.)	3.10 (3600)	3.11 (c)	3.12 (a)	3.13 (a)
3.14 (sol.)	3.15 (a)	3.16 (3)	3.17 (b)	3.18 (c)	3.19 (c)	3.20 (c)
4.1 (b)	4.2 (b)					

**Explanations Communication Systems****1. Analog Communication Systems****1.1 (a)**

The image rejection should be achieved before IF stage because once it enters into IF amplifier it becomes impossible to remove it from wanted signal. So image channel selectivity depends upon preselector and RF amplifiers only. The IF amplifiers help in rejection of adjacent channel frequency and not image frequency.

**1.2 (a)**

$$X_{Fm}(t) = A_c \cos\left[\omega_c t + k_f \int m(t) dt\right]$$

$$X_{Fm}(t) = A_c \cos\left[\omega_c t + k_f \int E_m \cos \omega_m t dt\right]$$

$$X_{Fm}(t) = A_c \cos\left[\omega_c t + \frac{k_f E_m}{\omega_m} \sin \omega_m t\right]$$

Modulation index

$$m_f = \frac{k_f E_m}{\omega_m}$$

$$X_{FM}(t) = \left[ A_c \cos[\omega_c t + m_f \sin \omega_m t] \right]$$

**1.3 (c)**

FM detection using a discriminator suffers from the threshold effect.

**1.4 (a)**

$$\text{Modulation index} = M_f = \frac{k_f A_m}{\omega_m} = \frac{\Delta \omega}{\omega_m}$$

$$M_f = \frac{(2\pi \times 10 \times 10^3) \times (2)}{\pi \times 10^4} = 4$$

**1.5 (c)**

In commercial TV transmission in India, picture signal is modulated using VSB modulation and speech or audio signal is modulated using FM modulation.

**1.6 (b)**

When the message signal is symmetrical square wave, 50% power efficiency can be achieved by an AM modulator.

**1.7 (c)**

Given that

$$x(t) = 5(1 + 2\cos 200\pi t) \cos 20000\pi t \quad \dots(i)$$

The standard equation for AM signal is

$$X_{AM}(t) = A_c(1 + m \cos \omega_m t) \cos \omega_c t$$

By comparing the equation (i) and equation (ii), we have  $m = 2$

Since the modulation index is more than 1 here, so it is the case of over modulation. When the modulation index of AM wave is more than 1 (over modulation) then the detection is possible only with synchronous modulator only. Such signals can not be detected with envelope detector.

**1.8 (2110)**

$$f_{si} = f_s + 2IF$$

$$f_{si} = 1200 + 2(455)$$

$$f_{si} = 2110 \text{ kHz}$$

**1.9 (d)**

$$v(t) = 5\cos(10^6\pi t) - \frac{5}{2}\cos(10^6 - 10^3)\pi t + \frac{5}{2}(10^6 + 10^3)\pi t$$

So, carrier and upper side-band are in phase and lower side band is out of phase with carrier and upper side-band.

So, the given signal is narrow band FM signal.

**1.10 (101)**

By Carson's rule

$$BW = 2(\Delta f + f_m)$$

$$BW = 2(50 + 0.5)$$

$$BW = 101 \text{ kHz}$$

**1.11 (a)**

SSB  $\rightarrow$  Hilbert transform

AM  $\rightarrow$  Envelope detector

BPSK  $\rightarrow$  Integrate and dump

**1.12 (b)**

The image rejection should be achieved before IF stage because once it enters into IF amplifier it becomes impossible to remove it from wanted signal. So image channel selectivity depends upon preselector and RF amplifiers only. The IF amplifier helps in rejection of adjacent channel frequency and not image frequency.

**1.13 (c)**

PLL (Phase Locked Loop) is used to demodulate the FM signals.

**1.14 (b)**

An integrator.

**2. Random Signals and Noise****2.1 (d)**

$$\text{Var}(-Kx) = E[(-Kx)^2] - (E[-Kx])^2$$

$$\sigma^2 = E[K^2 x^2] - K^2 E[x^2]$$

$$\sigma^2 = K^2(E[x^2] - E[x]^2)$$

$$\sigma^2 = K^2 \sigma_x^2$$

**2.2 (d)**

Narrow band representation of noise is

$$n(t) = n_c(t) \cos \omega_c t - n_s(t) \sin \omega_c t$$

Its envelope is  $R(t) = \sqrt{n_c^2(t) + n_s^2(t)}$

Where  $n_c(t)$  and  $n_s(t)$  are two independent, zero mean Gaussian processes, with same variance. The resulting envelope is Rayleigh variable.

**2.3 (a)**

A pre amplifier is a very large gain amplifier with low noise figure.

Noise figure of cascaded amplifier can be given as:

$$F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots + \frac{F_n - 1}{G_1 G_2 G_3 \dots G_{n-1}}$$

Therefore placing the pre amplifier on the antenna side of the waveguide will result in the reduction of overall noise figure of the system.

**2.4 (b)**

Half wave rectification can be represented as

$$y = x \quad \text{for } x \geq 0$$

$$= 0 \quad \text{for } x < 0$$

$$\text{So, } f(y) = \frac{1}{2} \delta(y) + \frac{1}{\sqrt{2\pi N}} e^{-y^2/2N}$$

$$E[Y^2] = \int_0^\infty y^2 f(y) dy$$

$$E[Y^2] = \int_0^\infty y^2 \left[ \frac{1}{2} \delta(y) + \frac{1}{\sqrt{2\pi N}} e^{-y^2/2N} \right] dy$$

$$E[Y^2] = 0 + \int_0^\infty \frac{y^2}{\sqrt{2\pi N}} e^{-y^2/2N} dy$$

$$\text{Let, } \frac{y}{\sqrt{N}} = t$$

$$dy = \sqrt{N} dt$$

$$E[Y^2] = \frac{1}{\sqrt{2\pi N}} \int_0^\infty N t^2 e^{-t^2/2} \sqrt{N} dt$$

$$= \frac{N}{\sqrt{2\pi}} \int_0^\infty t^2 e^{-t^2/2} dt$$

$$E[Y^2] = \frac{N}{2}$$

**2.5 (b) & (c)**

Given that

$$T_e = 21^\circ\text{K}$$

$$T_a = 300^\circ\text{K}$$

$$\text{Gain} = (G)_{\text{dB}} = 13$$

$$13 = 10 \log_{10}(G)$$

$$G = 19.95$$

$$\text{Cable loss} = (3)_{\text{dB}} = 10 \log_{10}(L)$$

$$L = 1.995$$

For a cable,

$$\text{Noise figure} = F_2 = \text{cable loss} = L$$

$$F_2 = 1.995$$

$$\text{Noise figure of amplifier} = F_1 = 1 + \frac{T_e}{T_a}$$

$$F_1 = 1 + \frac{21}{300} = 1.07$$

Noise figure of cascaded amplifier

$$F = F_1 + \frac{F_2 - 1}{G}$$

$$= 1.07 + \frac{1.995 - 1}{19.95} = 1.12$$

$$F = 0.49 \text{ dB}$$


$T'_e$  of the cascaded amplifier.

$$T'_e = (F - 1)T_a$$

$$T'_e = (1.12 - 1)300$$

$$T'_e = 36^\circ\text{K}$$

## 2.6 Sol.

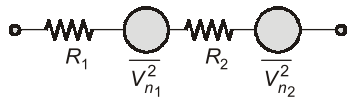

$$\overline{V_n^2} = \overline{V_{n1}^2} + \overline{V_{n2}^2}$$

$$\overline{V_n^2} = 4KT_e BR = 4KT_e B(R_1 + R_2)$$

$$\overline{V_{n1}^2} = 4KT_1 BR_1$$

$$\overline{V_{n2}^2} = 4KT_2 BR_2$$

So,

$$4KT_e B(R_1 + R_2) = 4KT_1 BR_1 + 4KT_2 BR_2$$

$$4KT_e B(R_1 + R_2) = 4KB(R_1 T_1 + R_2 T_2)$$

$$T_e(R_1 + R_2) = R_1 T_1 + R_2 T_2$$

$$T_e = \frac{R_1 T_1 + R_2 T_2}{R_1 + R_2}$$

## 2.7 (b)

$$\text{Mean} = \mu_X = E[X] = \int_{-\infty}^{\infty} xp(x)dx$$

$$\mu_X = \int_{-1}^3 x \frac{1}{4} dx = \frac{1}{4} \left[ \frac{x^2}{2} \right]_{-1}^3$$

$$\mu_X = \frac{1}{4} \times \frac{1}{2} [9 - (-1)^2] = \frac{1}{8} \times 8$$

$$\mu_X = 1$$

$$\text{Variance} = \sigma_X^2 = E[(x - \mu_X)^2] = \int_{-\infty}^{\infty} (x - \mu_X)^2 p_X(x) dx$$

$$\sigma_X^2 = \int_{-1}^3 (x - 1)^2 \frac{1}{4} dx = \frac{1}{4} \int_{-1}^3 (x - 1)^2 dx$$

$$\sigma_X^2 = \frac{1}{4} \int_{-1}^3 (x^2 + 1 - 2x) dx$$

$$\sigma_X^2 = \frac{1}{4} \left[ \frac{x^3}{3} + x - \frac{2x^2}{2} \right]_{-1}^3$$

$$\sigma_X^2 = \frac{1}{4} \left[ \left( \frac{27}{3} + 3 - 9 \right) - \left( -\frac{1}{3} - 1 - 1 \right) \right]$$

$$\sigma_X^2 = \frac{1}{4} \left[ 3 + \frac{1}{3} + 2 \right] = \frac{1}{4} \times \frac{1}{3} [9 + 1 + 6]$$

$$\sigma_X^2 = \frac{4}{3}$$

## 2.8 (d)

For a narrow band noise with Gaussian quadrature components the probability density function (PDF) of its envelope will be Rayleigh.

## 3. Digital Communication Systems

### 3.1 (c)


Companding results in making SNR uniform, throughout the signal, irrespective of amplitude levels. Since, in uniform quantization, step size is same, the quantization noise power is uniform, throughout the signal.

Thus, higher amplitudes of signal, will have better SNR than the lower amplitudes.

Hence, companding is used for improving SNR at lower amplitudes.
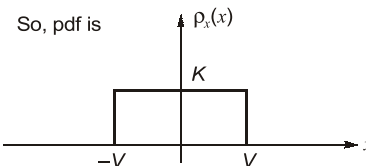
### 3.2 (c)

Since the signal is uniformly distributed in the interval  $-V$  to  $+V$ .



Area under pdf is unity

$$K[V - (-V)] = 1$$

$$2VK = 1$$

$$K = \frac{1}{2V}$$

$$\text{So, } p_X(x) = \frac{1}{2V} \quad -V \text{ to } V$$

$$= 0 \quad \text{otherwise}$$

$$\text{Signal power} = s = \int_{-\infty}^{\infty} x^2 p_x(x) dx$$

$$s = \int_{-V}^V x^2 \frac{1}{2V} dx = \frac{1}{2V} \left[ \frac{x^3}{3} \right]_{-V}^V$$

$$s = \frac{1}{2V} \left[ \frac{V^3}{3} - \frac{(-V^3)}{3} \right] = \frac{1}{2V} \cdot \frac{2V^3}{3} = \frac{V^2}{3}$$

In uniform quantization,

$$\text{Quantization noise power} = \text{QNP} = \frac{\Delta^2}{12}$$

$$\text{where, step size} = \Delta = \frac{V_{p-p}}{L} = \frac{V_{p-p}}{2^n}$$


$$\text{QNP} = \frac{V_{p-p}^2}{12 \times 2^{2n}} = \frac{(2V)^2}{12 \times 2^{2n}} = \frac{V^2}{3 \times 2^{2n}}$$

$$\text{SQNR} = \frac{S}{\text{QNP}} = \frac{V^2}{3} \times \frac{3 \times 2^{2n}}{V^2} = 2^{2n}$$

So,  $\text{SQNR} \propto 2^{2n}$

So, signal to quantizing noise ratio is determined by the number of quantizing levels.

### 3.3 (c)

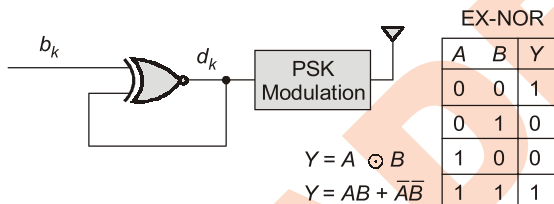


0 → is represented with a carrier has phase ' $\pi$ '

1 → is represented with a carrier has phase '0'

$$d_k = b_k \oplus d_{k-1} \text{ or } d_k = b_k \odot d_{k-1}$$

Logic function here is EX-NOR.

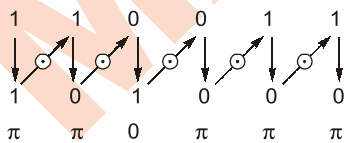

Hence, the answer is 0,  $\pi$ ,  $\pi$ ,  $\pi$ .

### 3.4 (b)

Let getting an error be success.

$$P(\text{success}) = P$$

$$P(\text{failure}) = 1 - P$$

$$P(x = \text{at most } 1) = P(x = 0) + P(x = 1)$$

$$= {}^8C_0(P)^0 * (1 - P)^{8-0} + {}^8C_1(P)^1 (1 - P)^{8-1}$$

$$= (1 - P)^8 + 8P(1 - P)^7$$

### 3.5 (a)

A coherent carrier is not required to be generated at the receiver.

### 3.6 (b)

$$f_c = 4 \text{ GHz} = 4000 \text{ MHz}$$

$$f_m = 2 \text{ MHz}$$

$$f_H = f_c + f_m = 4000 + 2 = 4002 \text{ MHz}$$

$$f_L = f_c - f_m = 4000 - 2 = 3998 \text{ MHz}$$

$$f_s = \frac{2f_H}{K}$$

$$K = \left\lfloor \frac{f_H}{f_H - f_L} \right\rfloor = \left\lfloor \frac{4002 \text{ MHz}}{4 \text{ MHz}} \right\rfloor = \lfloor 1000.5 \rfloor = 1000$$

$$f_s = \frac{2 \times 4002 \text{ MHz}}{1000} = 8.004 \text{ MHz} \approx 8 \text{ MHz}$$

### 3.7 (b)

In BPSK if detector has a fixed phase error  $\phi$  then the output power would change by a factor  $\cos^2 \phi$ .

### 3.8 (3600)

3600 samples/sec

Given that

$$f_H = 1800 \text{ Hz}$$

$$f_L = 300 \text{ Hz}$$

$$\text{So, } \boxed{\text{B.W.} = f_H - f_L}$$

$$\text{B.W.} = 1800 - 300 = 1500 \text{ Hz}$$

$$\boxed{K = \frac{f_H}{\text{B.W.}}}$$

$$K = \frac{1800}{1500}$$

$$\text{So, } K = 1$$

$$\boxed{(f_s)_{\min} = \frac{2f_H}{K}}$$

$$(f_s)_{\min} = \frac{2 \times 1800}{1} = 3600 \text{ samples/sec}$$

### 3.9 Sol.

For different phases are given which are  $90^\circ$  apart with adjacent signal. So, it is the clear of QPSK (Quadrature Phase Shift Keying).

### 3.10 (3600)

$$f_s = 3600 \text{ samples/sec}$$


$$f_H = 1800 \text{ Hz}$$

$$f_L = 300 \text{ Hz}$$

$$\text{B.W.} = f_H - f_L = 1800 - 300 = 1500 \text{ Hz}$$

$$K = \frac{f_H}{\text{B.W.}} = \frac{1800}{1500} = 1$$

$$f_{s(\min)} = \frac{2f_H}{K} = \frac{2 \times 1800}{1} = 3600 \text{ samples/sec}$$

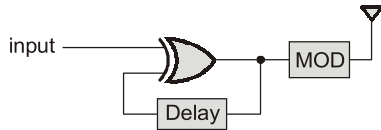
**3.11 (c)**

EX-XOR		
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$$Y = A \oplus B$$

$$Y = A\bar{B} + \bar{A}B$$


Given that  
reference bit = 1  
logic 0  $\rightarrow \pi$   
logic 1  $\rightarrow 0^\circ$

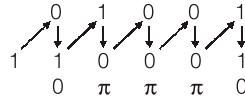**3.12 (a)**


Coherent demodulation of FSK signal can be detected using correlation receiver.

**3.13 (a)**

The purpose of source encoding in a data communication system is to represent non-electrical discrete symbols with binary codes and thus enhance the information transmission and purpose of channel encoding is to decrease the probability of error. The channel coding helps in detection and correction of errors.

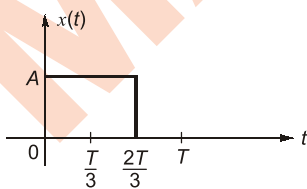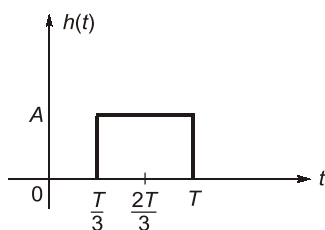**3.14 Sol.**

We know that impulse-response of a matched filter is  
 $h(t) = x(T - t)$



The output of matched filter


$$y(t) = x(t) * h(t)$$

$$\frac{dh}{dt}(t) = A\delta\left(t - \frac{T}{3}\right) - A\delta(t - T)$$


$$y(t) = \int_{-\infty}^t x(t) * A\delta\left(t - \frac{T}{3}\right) - x(t) * A\delta(t - T) dt$$

$$y(t) = \int_{-\infty}^t A \left[ x\left(t - \frac{T}{3}\right) - x(t - T) \right] dt$$

$$= \int_{-\infty}^t y_1(t) dt$$

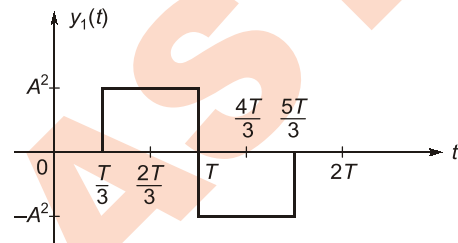

$$y(t) = \int_{-\infty}^t y_1(t) dt$$

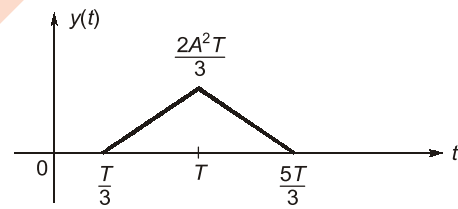**3.15 (a)**

Increased pulse width in the flat-top sampling leads to greater attenuation of high frequencies in reproduction. This effect is known as aperture effect.

**3.16 (3)**

$$(\text{B.W.})_{\text{PCM}} = nfs$$

$$n = \log_2 L$$

$$n_1 = \log_2 4 = 2$$

$$n_2 = \log_2 64 = 6$$

$$(\text{B.W.})_1 = n_1 fs = 2fs$$

$$(\text{B.W.})_2 = n_2 fs = 6fs$$

$$\frac{(\text{B.W.})_2}{(\text{B.W.})_1} = \frac{6fs}{2fs} = 3 \text{ times}$$

$$(\text{B.W.})_2 = 3(\text{B.W.})_1$$

**3.17 (b)**

$$(\text{SQNR})_{\text{dB}} = (1.76 + 6n)_{\text{dB}}$$

$$(\text{SQNR})_1 = 1.76 + 6n$$

$$\begin{aligned} (\text{SQNR})_2 &= 1.76 + 6(n+1) \\ &= 1.76 + 6n + 6 \end{aligned}$$

$$(\text{SQNR})_2 - (\text{SQNR})_1 = (1.76 + 6n + 6) - (1.76 + 6n)$$

$$(\text{SQNR})_2 - (\text{SQNR})_1 = 6 \text{ dB}$$

So, for every one bit increase in bits per sample will result in 6 dB improvement in signal to quantization noise ratio.

**3.18 (c)**

Given that

$$f_m = 1 \text{ kHz}$$

$$f_s = 1.8 \text{ k samples/sec}$$

The frequency components in the sampled signal are

$$nf_s \pm f_m$$

$$n = 0 \Rightarrow f_m = 1 \text{ kHz} = 1000 \text{ Hz}$$

$$n = 1 \Rightarrow 1.8 \pm 1 = 800 \text{ Hz and } 2800 \text{ Hz}$$

$$n = 2 \Rightarrow 3.6 \pm 1 = 2600 \text{ Hz and } 4600 \text{ Hz}$$

Cut-off frequency of LPF 1100 Hz.

So, 800 Hz and 1000 Hz components.

**3.19 (c)**

The signal to quantization noise ratio in an  $n$ -bit PCM system is given by

$$(\text{SQNR})_{\text{dB}} = 1.76 + 6n$$

$$\text{SQNR} = \frac{3}{2} 2^{2n}$$

From the above equation it is clear that SQNR increases with increase in value of ' $n$ '.

**4. Information Theory and Coding****4.1 (b)**

$$\text{Entropy} = H = - \sum_{i=1}^n P_i \log_2(P_i)$$

$$H = - \left[ \frac{1}{2} \log_2 \left( \frac{1}{2} \right) + \frac{1}{4} \log_2 \left( \frac{1}{4} \right) + \frac{1}{8} \log_2 \left( \frac{1}{8} \right) + \frac{1}{8} \log_2 \left( \frac{1}{8} \right) \right]$$

$$H = \frac{1}{2} + \frac{1}{4} \times 2 + \frac{1}{8} \times 3 + \frac{1}{8} \times 3$$

$$H = 1 + \frac{3}{4} = \frac{7}{4}$$

$$\text{Code efficiency} = \eta = \frac{H}{L}$$

$$\eta = \frac{7/4}{2} = \frac{7}{8}$$

**4.2 (b)**

$$n = \log_2 L = \log_2 8 = 3$$

$$\text{Maximum entropy} = 512 \times 512 \times n$$

$$= 512 \times 512 \times 3 = 786432 \text{ bits/image}$$

■■■



# Engineering Mathematics

## UNIT IX

### CONTENTS

1. Linear Algebra **94**
2. Differential Equations **94**
3. Transform Theory **94**

# IX

## Engineering Mathematics

### 1. Linear Algebra

1.1 The rank of  $(m \times n)$  matrix (where  $m < n$ ) cannot be more than

- (a)  $m$  (b)  $n$   
(c)  $mn$  (d) none

[1994 : 1 Mark]

1.2 Solve the following system of equations

$$x_1 + x_2 + x_3 = 3$$

$$x_1 - x_2 = 0$$

$$x_1 - x_2 + x_3 = 1$$

- (a) Unique solution  
(b) No solution  
(c) Infinite number of solutions  
(d) Only one solution

[1994 : 2 Marks]

### 2. Differential Equations

2.1  $y = e^{-2x}$  is a solution of the differential equation  $y'' + y' - 2y = 0$ . (True/False).

[1994 : 1 Mark]

### 3. Transform Theory

3.1 If  $L\{f(t)\} = \frac{2(s+1)}{s^2 + 2s + 5}$  then  $f(0^+)$  and  $f(\infty)$  are given by \_\_\_\_\_

- (a) 0, 2 respectively (b) 2, 0 respectively  
(c) 0, 1 respectively (d) 2/5, 0 respectively

[1995 : 2 M]

■■■

**Answers Differential Equations**

1.1 (a)      1.2 (a)      2.1 (True)      3.1 (b)

**Explanations Differential Equations****1. Linear Algebra****1.1 (a)**

If  $A$  is a matrix of order  $m \times n$  ( $m < n$ ) then rank of  $A$  is  $\leq \min \{m, n\}$

$$\therefore r(A) \nless m$$

**1.2 (a)**

Augmented matrix  $(AB) =$

$$\begin{bmatrix} 1 & 1 & 1 & 3 \\ 1 & -1 & 0 & 0 \\ 1 & -1 & 1 & 1 \end{bmatrix} \begin{matrix} R_2 - R_1 \\ R_3 - R_1 \end{matrix}$$

$$\begin{bmatrix} 1 & 1 & 1 & 3 \\ 0 & -2 & -1 & -3 \\ 0 & -2 & 0 & -2 \end{bmatrix} R_3 - R_2$$

$$\begin{bmatrix} 1 & 1 & 1 & 3 \\ 0 & -2 & -1 & -3 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

$$\therefore \rho(A) = \rho(AB) = 3$$

$\Rightarrow$  Unique solution.

**2. Differential Equations****2.1 (True)**

$$y + y'' - 2y = 0$$

$$(D^2 + D - 2) = 0$$

Auxiliary equation is

$$m^2 + m - 2 = 0$$

$$(m + 2)(m - 1) = 0$$

$$m = -2, 1$$

complementary function is  $C_1 e^{-2x} + C_2 e^x$

$$\therefore \text{solution is } y = C_1 e^{-2x} + C_2 e^x$$

$$\therefore y = e^{-2x} \text{ is a solution of } y'' + y' - 2y = 0$$

**3. Transform Theory****3.1 (b)**

$$F(s) = \frac{2(s+1)}{s^2 + 2s + 5}$$

$$= \frac{2(s+1)}{(s+1)^2 + 4} = \frac{2(s+1)}{(s+1)^2 + 2^2}$$

By first shifting theorem

$$f(t) = 2e^{-t} \cos 2t$$

$$f(0^+) = \lim_{t \rightarrow 0} f(t) = \lim_{t \rightarrow 0} 2e^{-t} \cos 2t = 2$$

$$f(\infty) = \lim_{t \rightarrow \infty} f(t) = \lim_{t \rightarrow \infty} 2e^{-t} \cos 2t = 0$$

■■■