



**MADE EASY**

Leading Institute for ESE, GATE & PSUs

Detailed Solutions

**ESE-2024  
Mains Test Series**

**Electrical Engineering  
Test No : 15**

**Section-A**

**Q.1 (a) Solution:**

The input power,


$$P_{\text{in}} = 200 \text{ W}$$

$$P_{\text{in}} = V_{\text{in}} \cdot I_a \cos \phi$$

$$200 = 120 \times 4 \times \cos \phi$$

$$\cos \phi = \frac{200}{120 \times 4} = \frac{5}{12}$$

$$\phi = 65.37^\circ$$

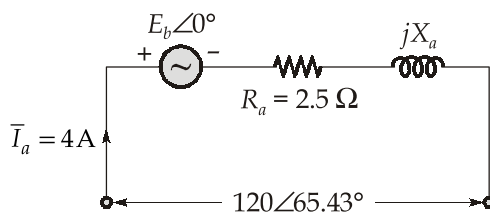

$\bar{E}_b$  and  $\bar{I}_a$  will be in phasor,

(i) From the circuit the following can be written

$$\bar{V}_{\text{in}} = \bar{E}_b + I_a [R_a + jX_a]$$

$$120 \angle 65.37^\circ = \bar{E}_b + 4 \angle 0^\circ [2.5 + jX_a]$$

$$50.01 + j109.08 = (E_b + 10) + j4X_a$$

On comparing,

$$50.01 = E_b + 10$$

$$E_b = 40.01 \text{ Volt}$$

$$\text{Armature reactance, } X_a = \frac{109.08}{4} = j27.27 \Omega$$

(ii) We know, back emf

$$(E_b)_{\text{rms}} = \left( \frac{Z\phi NP}{60 A} \right) \times \frac{1}{\sqrt{2}}$$

$$40.01 = \frac{840 \times \phi_m \times 4000 \times 2}{60 \times 2\sqrt{2}}$$

$$\phi_m = 1.01 \text{ mWb}$$

### Q.1 (b) Solution:

Let  $f$  be the output expression for different combinations of  $A, B, C, D, E$ .

(i) Either  $A$  or  $B$  or both must go,

$$f = 0, \text{ for } AB = 00$$

(ii) Either  $E$  or  $C$ , but not both must go,

$$f = 0, \text{ for } CE = 11$$

(iii) Either both  $A$  and  $C$  go or neither goes,

$$f = 0, \text{ for } AC = 01 \text{ and } AC = 10$$

(iv) If  $D$  goes, then  $E$  also must go,

$$f = 0, \text{ for } DE = 10$$

(v) If  $B$  goes, then  $A$  and  $D$  must also go,

$$f = 0, \text{ for } ABD = 010, 011, 110$$

Using the conditions (i) to (v). The truth table can be build as

$AB = 00$				$AB = 01$				$AB = 10$				$AB = 11$			
$C$	$D$	$E$	$f$	$C$	$D$	$E$	$f$	$C$	$D$	$E$	$f$	$C$	$D$	$E$	$f$
0	0	0	0	0	0	0	0 (v)	0	0	0	0 (iii)	0	0	0	0 (iii)
0	0	1	0	0	0	1	0 (v)	0	0	1	0 (iii)	0	0	1	0 (iii)
0	1	0	0	0	1	0	0 (v)	0	1	0	0 (iii)	0	1	0	0 (iii)
0	1	1	0	0	1	1	0 (iv)	0	1	1	0 (iii)	0	1	1	0 (iii)
1	0	0	0	1	0	0	0 (iii)	1	0	0	1	1	0	0	0 (v)
1	0	1	0	1	0	1	0 (ii)	1	0	1	0 (ii)	1	0	1	0 (ii)
1	1	0	0	1	1	0	0 (iii)	1	1	0	0 (iv)	1	1	0	0 (iv)
1	1	1	0	1	1	1	0 (ii)	1	1	1	0 (ii)	1	1	1	0 (ii)

Hence, the only possible combination for which  $f = 1$  is

$$A = 1, B = 0, C = 1, D = 0, E = 0$$

$$f = A\bar{B}C\bar{D}\bar{E}$$

**Q.1 (c) Solution:**

$$H(Z) = \frac{1}{1 - 2r \cos \theta z^{-1} + r^2 z^{-2}} = \frac{z^2}{z^2 - 2zr \cos \theta + r^2}$$

It has a pair of poles at  $z = r$ .

$$z^2 - 2zr \cos \theta + r^2 = 0$$

$$\text{at } z = r, \text{ i.e., } r^2 - 2r^2 \cos \theta + r^2 = 0 \text{ at } z = r$$

$$2r^2 = 2r^2 \cos \theta$$

$$1 - \cos \theta = 0$$

$$\cos \theta = 1$$

$$H(Z) = \frac{z^2}{z^2 - 2rz + r^2} = \frac{z^2}{(z - r)^2}$$

$$\frac{H(Z)}{z} = \frac{z}{(z - r)^2}$$

$$\frac{z}{(z - r)^2} = \frac{A}{z - r} + \frac{B}{(z - r)^2}$$

$$z = A(z - r) + B$$

$$z = Az + B - Ar$$

Comparing coefficient of  $z$  and constant term, we get

$$A = 1$$

and

$$B - Ar = 0$$

$$B = Ar$$

$$\therefore A = 1,$$

$$B = Ar$$

$$B = r$$

$$\therefore \frac{z}{(z - r)^2} = \frac{1}{z - r} + \frac{r}{(z - r)^2}$$

$$H(Z) = \frac{z^2}{(z - r)^2} = \frac{z}{z - r} + \frac{zr}{(z - r)^2}$$

Applying inverse Z-transform, we get

$$h(n) = r^n u(n) + n r^n u(n)$$

$$h(n) = (n + 1) r^n u(n)$$

**Q.1 (d) Solution:**

Given, differential equation,

$$\left[ \frac{\partial}{\partial t^2} y(t) \right] + 16y(t) = 16u(t-3) - 16$$

$$Y(0) = 0; \quad \dot{y}(0) = 0$$

by taking Laplace transform,

$$s[sY(s) - Y(0)] - \dot{y}(0) + 16Y(s) = 16\left(\frac{e^{-3s}}{s}\right) - \frac{16}{s}$$

$$s^2Y(s) + 16Y(s) = 16\left[\frac{e^{-3s}}{s}\right] - \frac{16}{s}$$

$$Y(s)[s^2 + 16] = \frac{16e^{-3s} - 16}{s}$$

$$Y(s) = \frac{16e^{-3s} - 16}{s(s^2 + 16)}$$

$$\therefore Y(s) = \frac{16e^{-3s}}{s(s^2 + 16)} - \frac{16}{s(s^2 + 16)}$$

Let  $Y_1(s) = \frac{16}{s(s^2 + 16)}$

$$Y_1(s) = \frac{1}{s} - \frac{s}{s^2 + 16}$$

$$\begin{aligned} \therefore Y(s) &= \frac{e^{-3s}}{s} - \frac{e^{-3s}s}{s^2 + 16} - \left[ \frac{1}{s} - \frac{s}{s^2 + 16} \right] \\ &= \frac{e^{-3s}}{s} - \frac{se^{-3s}}{s^2 + 16} - \frac{1}{s} + \frac{s}{s^2 + 16} \end{aligned}$$

by taking Inverse Laplace transform

$$\therefore y(t) = u(t-3) - \cos(4(t-3))u(t-3) - u(t) + \cos 4t$$

$$\therefore y(t) = -u(t) + u(t-3) - \cos(4t-12)u(t-3) + \cos 4t$$

**Q.1 (e) Solution:**

(i) From the circuit given:

$$I_2 = \bar{Q}_1; \quad K_2 = Q_0$$

$$I_1 = Q_2; \quad K_1 = \bar{Q}_2$$

$$I_0 = Q_1; \quad K_0 = \bar{Q}_1$$



$Q_2$	$Q_1$	$Q_0$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	1	1	1	0	1	0	1
1	0	0	1	0	1	0	0	1
1	1	0	0	0	1	0	1	0
1	1	1	0	1	1	0	1	0
0	1	1	0	1	0	1	1	0
0	0	1	1	1	0	1	0	1

This is a divide by 5 counter, So  $N = 5$ .

(ii)  $Q_2 = 1; Q_1 = 0; Q_0 = 1$

$Q_2$	$Q_1$	$Q_0$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
1	0	1	1	1	1	0	0	1
0	1	0	0	0	0	1	1	0
0	0	1	1	1	0	1	0	1
1	0	0	1	0	1	0	0	1
1	1	0	0	0	1	0	1	0
1	1	1	0	1	1	0	1	0
0	1	1	0	1	0	1	1	0
0	0	1	1	1	0	1	0	1

This is also a divide by 5 counter, So,  $N = 5$ .

### Q.2 (a) Solution:

An noninverting amplifier is shown in figure. The input resistance seen by the signal source is designated  $R_{if}$ . The equivalent circuit, including a finite open loop gain  $A_{OL}$ , Finite open-loop input differential resistance  $R_i$  and non-zero output resistance  $R_o$ , is shown in figure (b).

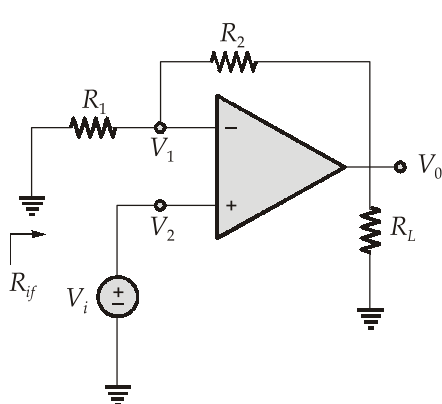


Figure (a)

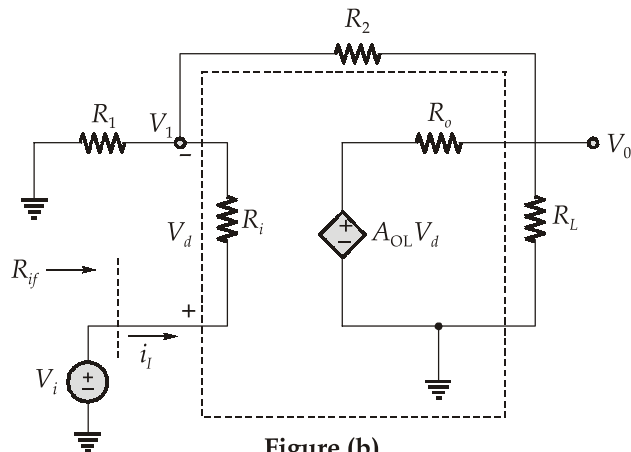


Figure (b)

Writing a KCL equation at the output node yields.

$$\frac{V_o}{R_L} + \frac{V_o - A_{OL}V_d}{R_o} + \frac{V_o - V_1}{R_2} = 0 \quad \dots(i)$$

Solving for the output voltage, we have

$$V_o = \frac{\frac{V_1}{R_2} + \frac{A_{OL}V_d}{R_o}}{\frac{1}{R_L} + \frac{1}{R_o} + \frac{1}{R_2}} \quad \dots(ii)$$

KCL equation at the  $V_1$  node yields.

$$i_I = \frac{V_1}{R_1} + \frac{V_1 - V_o}{R_2} \quad \dots(iii)$$

$$V_o = V_1 + \frac{V_1 R_2}{R_1} - i_I R_2 \quad \dots(iv)$$

Combining equations (ii) and (iv) and rearranging terms, we obtain,

$$i_I \left( 1 + \frac{R_o}{R_L} + \frac{R_o}{R_2} \right) = V_1 \left\{ \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \left( 1 + \frac{R_o}{R_L} + \frac{R_o}{R_2} \right) - \frac{R_o}{R_2^2} \right\} - \frac{A_{OL}V_d}{R_2} \quad \dots(v)$$

From figure (b), we see that,

$$V_d = i_I R_i \quad \dots(vi)$$

and

$$V_1 = V_i - i_I R_i \quad \dots(vii)$$

Substituting equations (vi) and (vii) in (v) to we obtain an equation in  $i_I$  and  $v_i$  so that the input resistance  $R_{if}$  can be found as

$$R_{if} = \frac{V_1}{i_I}$$

Setting,  $R_o = 0$  reduces equation (v) to

$$i_I = V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{A_{OL}v_d}{R_2} \quad \dots(viii)$$

Substituting, equation (vi) and (vii) into (viii), we find that the input resistance can be written in the form.

$$R_{if} = \frac{V_1}{i_I} = \frac{R_i(1 + A_{OL}) + R_2 \left( 1 + \frac{R_i}{R_1} \right)}{1 + \frac{R_2}{R_1}} \quad \dots(ix)$$


Equation (ix) describes the closed-loop input resistance of the noninverting amplifier with a finite open loop gain and a finite open-loop input resistance. In the limit as  $A_{OL} \rightarrow \infty$ , or as the open loop input resistance approaches infinity, we see that  $R_{if} \rightarrow \infty$ , which is a property of the ideal noninverting amplifier.

### Q.2 (b) Solution:

Total series impedance per phase,

$$Z = (0.03 + j0.1) \times 100 = (3 + j10) \Omega$$

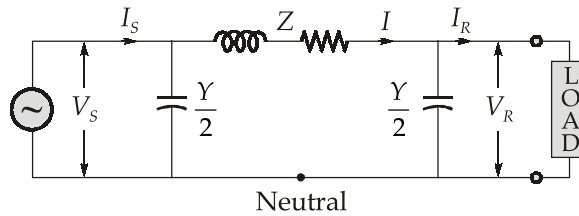Total admittance per phase,  $Y = j2\pi fC = j2\pi \times 50 \times 0.01 \times 10^{-6} \times 100 = j314 \times 10^{-6} S$



$$A = D = 1 + \frac{1}{2}YZ$$

$$= 1 + \frac{1}{2}j(314) \times 10^{-6} \times (3 + j10)$$

$$= 1 + j157 (3 + j10) \times 10^{-6}$$

$$= 0.99843 + j0.000471 = 0.99843 \angle 0.027^\circ$$

$$B = Z = 3 + j10 = 10.44 \angle 73.3^\circ \Omega$$

$$C = Y + \frac{1}{4}Y^2Z = j314 \times 10^{-6} + \frac{1}{4}(j314 \times 10^{-6})^2(3 + j10)S$$

$$= j314 \times 10^{-6} \left[ 1 + \frac{(j314 \times 10^{-6})(3 + j10)}{4} \right]$$

$$= j314 \times 10^{-6} [0.9992 + j2.355 \times 10^{-4}]$$

$$= 313.75 \times 10^{-6} \angle 90^\circ S$$

Taking receiving end phase voltage as reference

$$V_R = \frac{11000}{\sqrt{3}} \angle 0^\circ = 6350.85 \angle 0^\circ V$$

So, load current,

$$I_L = I_L \angle -36.87^\circ = \frac{2 \times 10^6 \angle -36.87^\circ}{\sqrt{3} \times 11000 \times 0.8}$$

$$= 131.216 \angle -36.87^\circ A$$

Capacitor current,  $I_C = j \frac{\text{MVAR}}{\sqrt{3}V_C} = j \frac{10^6}{\sqrt{3} \times 11000} = j52.486 \text{ A}$

Receiving end current,  $I_R = I_L + I_C = 131.216 \angle -36.87^\circ + 52.486 \angle 90^\circ$   
 $= (104.976 - j26.242) = 108.206 \angle -14.03^\circ \text{ A}$

Phase voltage at sending end,  $V_S = AV_R + BI_R$   
 $= (0.99843 \angle 0.027^\circ \times 6351 \angle 0^\circ)$   
 $+ (10.44 \angle 73.3^\circ \times 108.206 \angle -14.03^\circ)$   
 $= 6341.028 \angle 0.027^\circ + 1129.71 \angle 59.27^\circ$   
 $= 6986.537 \angle 8.014^\circ \text{ V}$

Sending end line voltage  $= \sqrt{3}V_S = \sqrt{3} \times 6986.537$   
 $= 12101.03 \angle 8.014^\circ \text{ V or } 12.1 \text{ kV}$

Sending end current,  $I_S = CV_R + DI_R$   
 $= (313.75 \times 10^{-6} \angle 90^\circ \times 6350.85 \angle 0^\circ)$   
 $+ (0.99843 \angle 0.027^\circ \times 108.206 \angle -14.03^\circ)$   
 $= (1.9925 \angle 90^\circ) + (108.036 \angle -14.003^\circ)$   
 $= 107.571 \angle -12.973^\circ \text{ A}$

**Q.2 (c) Solution:**

(i) Here  $V_{ml} = \sqrt{2} \times V_l = \sqrt{2} \times 230 \text{ V}$

Average output voltage,  $V_0 = \frac{3 V_{ml}}{\pi} = \frac{3\sqrt{2} \times 230}{\pi} = 310.609 \text{ V}$

But,  $V_0 = E + I_0 R$

$\therefore$  Average value of battery charging current,  
 $I_0 = \frac{V_0 - E}{R} = \frac{310.56 - 240}{8} = 8.82 \text{ A or } 8.826 \text{ A}$

Power delivered to battery  $= EI_0 = 240 \times 8.826 = 2118.274 \text{ W}$

Power delivered to load,  $P_d = EI_0 + I_{or}^2 \cdot R$

Since, load current is ripple free,  
 $I_{or} = I_0 = 8.826 \text{ A}$

$\therefore P_d = 240 \times 8.826 + 8.826^2 \times 8 = 2741.46 \text{ W}$

(ii) For ripple free load current, phase - a current  $i_a$ , or transformer secondary current  $i_s$ , would be constant at  $I_0 = 8.826 \text{ A}$  from  $\omega t = 30^\circ$  to  $150^\circ$  and  $-I_0$  from  $210^\circ$  to  $330^\circ$  and so on. As positive and negative half cycles are identical, average value of  $i_s = 0$ , i.e.  $I_{dc} = 0$ .

$$a_n = \frac{2}{\pi} \int_{\pi/6}^{5\pi/6} I_0 \cos n\omega t \cdot d(\omega t)$$

or,

$$a_1 = \frac{2}{\pi} \int_{\pi/6}^{5\pi/6} I_0 \cos \omega t \cdot d(\omega t) = \frac{2I_0}{\pi} [\sin 150^\circ - \sin 30^\circ] = 0$$

$$b_1 = \frac{2}{\pi} \int_{\pi/6}^{5\pi/6} I_0 \sin \omega t \cdot d(\omega t)$$

$$= \frac{2I_0}{\pi} [-\cos 150^\circ + \cos 30^\circ] = \frac{2\sqrt{3}}{\pi} I_0$$

Fundamental component of source current is given by

$$i_{s1} = \frac{2\sqrt{3}}{\pi} I_0 \sin \omega t \text{ and } \phi_1 = \tan^{-1} \left[ \frac{0}{b_1} \right] = 0^\circ$$

Input displacement factor,  $DF = \cos \phi_1 = 1$

(iii) Rms value of fundamental component of source current,

$$i_{s1} = \frac{2\sqrt{3}}{\pi} \times \frac{I_0}{\sqrt{2}}$$

Rms value of source current,

$$I_s = \left[ \frac{I_0^2 \times 2\pi}{\pi \times 3} \right]^{1/2} = \sqrt{\frac{2}{3}} \cdot I_0$$

Current distortion factor,

$$CDF = \frac{I_{s1}}{I_s} = \frac{2\sqrt{3} \times I_0}{\pi \cdot \sqrt{2}} \times \frac{\sqrt{3}}{\sqrt{2} \cdot I_0} = \frac{3}{\pi} = 0.955$$

(iv) Input p.f. =  $CDF \times DF$

$$= 0.955 \times 1 = 0.955 \text{ (lagging)}$$

(v) HF = THD =  $\left[ \left( \frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2} = \left[ \left( \frac{1}{0.955} \right)^2 - 1 \right]^{1/2} = 0.3106$

(vi) Transformer rating =  $\sqrt{3} V_s \cdot I_s = \sqrt{3} \times 230 \times \sqrt{\frac{2}{3}} \times 8.826 = 2870.825 \text{ VA}$

Also, transformer rating =  $\frac{P_d}{\text{TUF}} = \frac{2741.46}{0.9541} = 2873.346 \text{ VA}$

## Q.3 (a) Solution:


$$(i) \quad x(t) = \sum_{k=1}^{\infty} \frac{1}{k^2} \cos(5\pi kt)$$

$$\cos \omega_o t \xrightarrow{FT} \pi \delta(\omega - \omega_o) + \pi \delta(\omega + \omega_o)$$

$$\cos(5\pi kt) \xrightarrow{FT} \pi \delta(\omega - 5\pi k) + \pi \delta(\omega + 5\pi k)$$

$$\sum_{k=1}^{\infty} \frac{1}{k^2} \cos(5\pi kt) \xrightarrow{FT} \sum_{k=1}^{\infty} \left[ \frac{\pi}{k^2} \delta(\omega - 5\pi k) + \frac{\pi}{k^2} \delta(\omega + 5\pi k) \right]$$
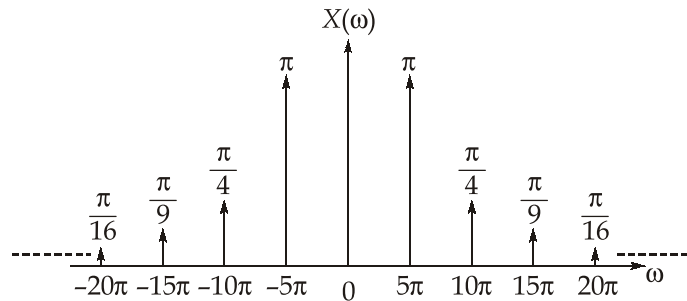
$$\therefore X(\omega) = \sum_{k=1}^{\infty} \frac{1}{k^2} [\pi \delta(\omega - 5\pi k) + \pi \delta(\omega + 5\pi k)]$$




$$(ii) \quad g(t) = \sum_{k=1}^{10} \cos(8\pi kt)$$

$$\cos(8\pi kt) \xrightarrow{FT} \pi \delta(\omega - 8\pi k) + \pi \delta(\omega + 8\pi k)$$


$$\sum_{k=1}^{10} \cos(8\pi kt) \xrightarrow{FT} \sum_{k=1}^{10} [\pi \delta(\omega - 8\pi k) + \pi \delta(\omega + 8\pi k)]$$
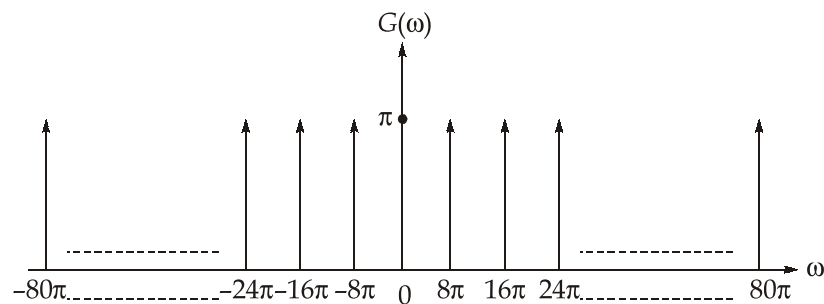
$$\therefore G(\omega) = \sum_{k=1}^{10} [\pi \delta(\omega - 8\pi k) + \pi \delta(\omega + 8\pi k)]$$



(iii)

$$h(t) = \frac{\sin 9\pi t}{\pi t}$$

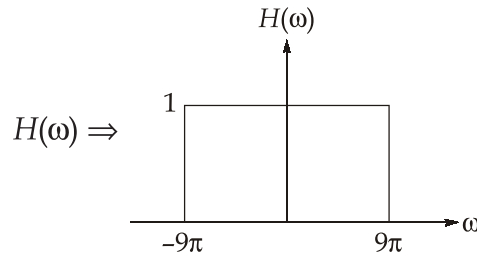

$H(\omega)$  is a low pass filter which allows only frequencies less than or equal to  $9\pi$  rad/sec, when  $x(t)$  is the input to  $h(t)$ , we get,

Output as  $\pi\delta(\omega - 5\pi) + \pi\delta(\omega + 5\pi)$

When  $g(t)$  is the input to  $h(t)$ , we get output as  $\pi\delta(\omega - 8\pi) + \pi\delta(\omega + 8\pi)$ .


$\therefore$

$$y(t) = h(t) * [h(t) * x(t) + h(t) * g(t)]$$

$$Y(\omega) = H(\omega) [H(\omega) X(\omega) + H(\omega) G(\omega)]$$

$$Y(\omega) = H(\omega) X(\omega) + H(\omega) G(\omega)$$
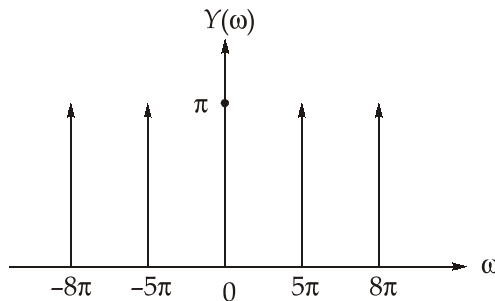
$$Y(\omega) = \pi\delta(\omega - 5\pi) + \pi\delta(\omega + 5\pi) + \pi\delta(\omega - 8\pi) + \pi\delta(\omega + 8\pi)$$



$$(iv) \quad \pi\delta(\omega - 5\pi) + \pi\delta(\omega + 5\pi) \xrightarrow{IFT} \cos 5\pi t$$

$$\pi\delta(\omega - 8\pi) + \pi\delta(\omega + 8\pi) \xrightarrow{IFT} \cos 8\pi t$$

$$y(t) = \cos 5\pi t + \cos 8\pi t$$

**Q.3 (b) Solution:**

For truth table of seven segment display when inputs  $b_3 b_2 b_1 b_0 = 0000$ , a decimal 0 will be displayed i.e., all segments lit except  $X_5$ .

$$\therefore X_0 = X_1 = X_2 = X_3 = X_4 = X_6 = 1; X_5 = 0$$

and  $E = 0$  because 0000 is a valid input combination.

The values at the outputs for all other input combinations can be derived in similar manner as below:

Decimal digit	$b_3$	$b_2$	$b_1$	$b_0$	$E$	$X_6$	$X_5$	$X_4$	$X_3$	$X_2$	$X_1$	$X_0$
0	0	0	0	0	0	1	0	1	1	1	1	1
1	0	0	0	1	0	0	0	1	1	0	0	0
2	0	0	1	0	0	1	1	0	1	1	0	1
3	0	0	1	1	0	1	1	1	1	1	0	0
4	0	1	0	0	0	0	1	1	1	0	1	0
5	0	1	0	1	0	1	1	1	0	1	1	0
6	0	1	1	0	0	1	1	1	0	1	1	1
7	0	1	1	1	0	0	0	1	1	1	0	0
8	1	0	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	0	1	1	1	1	1	1	0
Invalid	1	0	1	0	1	1	1	0	0	1	1	1
Invalid	1	0	1	1	1	1	1	0	0	1	1	1
Invalid	1	1	0	0	1	1	1	0	0	1	1	1
Invalid	1	1	0	1	1	1	1	0	0	1	1	1
Invalid	1	1	1	0	1	1	1	0	0	1	1	1
Invalid	1	1	1	1	1	1	1	0	0	1	1	1

From the above, we can write

$$E = \Sigma m(10, 11, 12, 13, 14, 15)$$

$$X_6 = \Sigma m(0, 2, 3, 5, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$X_5 = \Sigma m(2, 3, 4, 5, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$X_4 = \Sigma m(0, 1, 3, 4, 5, 6, 7, 8, 9)$$

$$X_3 = \Sigma m(0, 1, 2, 3, 4, 7, 8, 9)$$


$$X_2 = \Sigma m(0, 2, 3, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$X_1 = \Sigma m(0, 4, 5, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$X_0 = \Sigma m(0, 2, 6, 8, 10, 11, 12, 13, 14, 15)$$



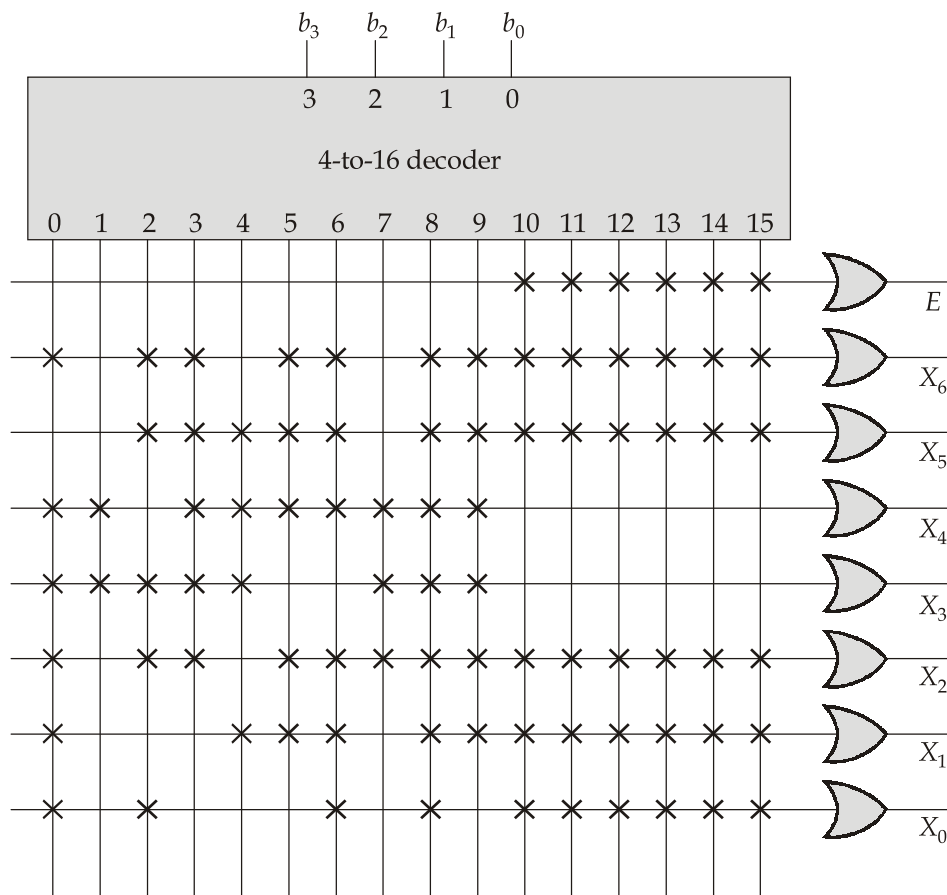The above can be implemented using a ROM as below:



### Q.3 (c) Solution:

- (i) When main thyristor  $T_1$  is turned-on, an oscillatory current in the circuit  $C$ ,  $T_1$ ,  $L$  and  $D$  is set up and it is given by

$$i_c(t) = V_s \cdot \sqrt{\frac{C}{L}} \sin \omega_0 t$$

$\therefore$  Peak value of current through capacitor

$$I_p = V_s \cdot \sqrt{\frac{C}{L}} = 230 \sqrt{\frac{40}{20}} = 325.269 \text{ A}$$

Peak value of current through main thyristor

$$T_1 = I_p + I_0 = 325.269 + 120 = 445.269 \text{ A}$$

Peak value of current through auxiliary thyristor  $TA = I_0 = 120 \text{ A}$

- (ii)

$$I_0 = C \frac{V_s}{t_c}$$

∴ Circuit turn-off time for main thyristor,

$$t_c = C \frac{V_s}{I_0} = 40 \times 10^{-6} \frac{230}{120} = 76.67 \mu\text{s}$$

An examination of figure reveals that when  $T_1$  conducts and during the time upper plate of  $C$  is positive,  $v_{TA} = -v_c$  i.e. auxiliary thyristors  $TA$  is reverse biased by  $v_c$ .

This gives circuit turn-off time  $t_{c1}$  for  $TA = \frac{\pi}{2\omega_0}$ .

Here,


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{10^6}{\sqrt{20 \times 40}} = \frac{10^6}{\sqrt{800}}$$

Circuit turn-off time for auxiliary thyristor,

$$t_{c1} = \frac{\pi}{2\omega_0} = \frac{\pi\sqrt{800}}{2 \times 10^6} = 44.43 \mu\text{s} \text{ or } 44.428 \mu\text{s}$$
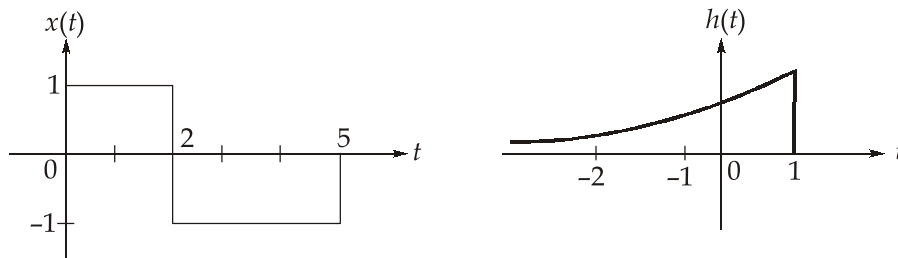
#### Q.4 (a) Solution:


Given that,  $h(t) = e^{2t} u(1-t)$  and  $x(t) = u(t) - 2u(t-2) + u(t-5)$



Using convolution integral,


$$\begin{aligned} y(t) &= \int_{-\infty}^{\infty} h(\tau) x(t-\tau) d\tau \\ &= \int_{-\infty}^{\infty} e^{2\tau} u(1-\tau) [u(t-\tau) - 2u(t-2-\tau) + u(t-5-\tau)] d\tau \end{aligned}$$

- For  $t \leq 1$ ,

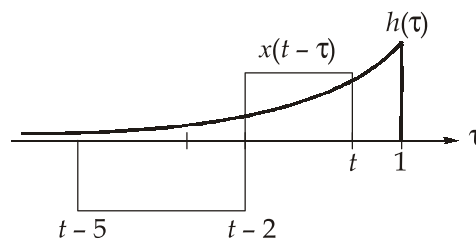

$$\begin{aligned}
 y(t) &= \int_{t-5}^t e^{2\tau} [u(t-\tau) - 2u(t-2-\tau) + u(t-5-\tau)] d\tau \\
 &= \int_{t-5}^{t-2} (-1)e^{2\tau} d\tau + \int_{t-2}^t e^{2\tau} d\tau \\
 &= -\frac{1}{2} [e^{2(t-2)} - e^{2(t-5)}] + \frac{1}{2} [e^{2t} - e^{2(t-2)}] \\
 y(t) &= \frac{1}{2} [1 - 2e^{-4} + e^{-10}] e^{2t}; t \leq 1
 \end{aligned}$$

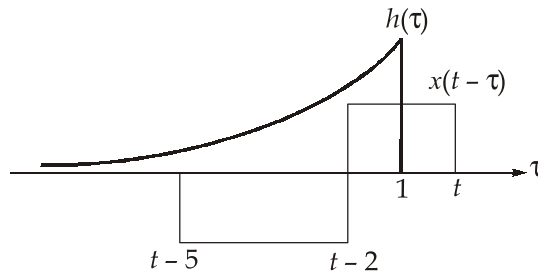
- For  $1 < t \leq 3$  or  $(t-2) \leq 1 < t$ ,



$$\begin{aligned}
 y(t) &= \int_{t-5}^{t-2} -e^{2\tau} d\tau + \int_{t-2}^1 e^{2\tau} d\tau \\
 &= -\frac{1}{2} [e^{2(t-2)} - e^{2(t-5)}] + \frac{1}{2} [e^2 - e^{2(t-2)}] \\
 y(t) &= \frac{1}{2} [-2e^{-4} + e^{-10}] e^{2t} + \frac{1}{2} e^2; 1 < t \leq 3
 \end{aligned}$$

- For  $3 < t \leq 6$  or  $(t-5) \leq 1 < (t-2)$ ,
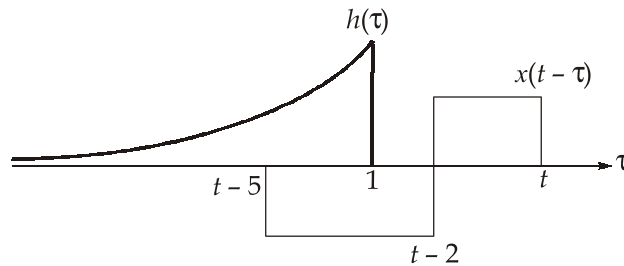
$$y(t) = \int_{t-5}^1 -e^{2\tau} d\tau = \frac{1}{2} [e^{2(t-5)} - e^2]; 3 < t \leq 6$$



- For  $t - 5 > 1$  or  $t > 6$ ,

$$y(t) = 0; t > 6$$

The overall solution is given by,

$$y(t) = \begin{cases} \frac{1}{2} [1 - 2e^{-4} + e^{-10}] e^{2t} & ; t \leq 1 \\ \frac{1}{2} [-2e^{-4} + e^{-10}] e^{2t} + \frac{1}{2} e^2 & ; 1 < t \leq 3 \\ \frac{1}{2} [e^{2(t-5)} - e^2] & ; 3 < t \leq 6 \\ 0 & ; t > 6 \end{cases}$$

#### Q.4 (b) Solution:

$$\begin{aligned} \text{Given, } S_{G1} &= P_{G1} + jQ_{G1} \\ S_{D1} &= P_{D1} + jQ_{D1} = 2 + j1 \\ S_{G2} &= P_{G2} + jQ_{G2} = 0.5 + j1 \\ S_{D2} &= P_{D2} + jQ_{D2} = 0 + j0 \end{aligned}$$

Using nominal  $\pi$ -method for transmission line

$$\begin{aligned} y_{\text{series}} &= \frac{1}{0.02 + j0.08} = 2.941 - j11.764 \\ &= 12.13 \angle -75.96^\circ \text{ p.u.} \end{aligned}$$

$\therefore$  Each off diagonal term =  $-2.941 + j11.764$  p.u.

$$\begin{aligned} \text{Each self term} &= (2(2.941 - j11.764) + j0.01) \\ &= 5.882 - j23.528 \\ &= 24.23 \angle -75.95^\circ \text{ p.u.} \end{aligned}$$

$$Y_{\text{bus}} = \begin{bmatrix} 24.23 \angle -75.95^\circ & 12.13 \angle 104.04^\circ & 12.13 \angle 104.04^\circ \\ 12.13 \angle 104.04^\circ & 24.23 \angle -75.95^\circ & 12.13 \angle 104.04^\circ \\ 12.13 \angle 104.04^\circ & 12.13 \angle 104.04^\circ & 24.23 \angle -75.95^\circ \end{bmatrix} \text{ } \Omega$$

$$\text{Also given, } V_2^0 = 1 + j0 \text{ and } \delta_3^0 = 0$$

$$\begin{aligned} P_2 &= |V_2| |V_1| |Y_{21}| \cos(\theta_{21} + \delta_1 - \delta_2) + |V_2|^2 |y_{22}| \cos(\theta_{22}) \\ &\quad + |V_2| |V_3| |Y_{23}| \cos(\theta_{23} + \delta_3 - \delta_2) \\ P_3 &= |V_3| |V_1| |Y_{31}| \cos(\theta_{31} + \delta_1 - \delta_3) \\ &\quad + |V_3| |V_2| |Y_{32}| \cos(\theta_{32} + \delta_2 - \delta_3) + V_3^2 |Y_{33}| \cos(\theta_{33}) \end{aligned}$$

$$Q_2 = \left[ -|V_2||V_1||Y_{21}|\sin(\theta_{21} + \delta_1 - \delta_2) - V_2^2|Y_{22}|\sin(\theta_{22}) \right. \\ \left. - |V_2||V_3||Y_{23}|\sin(\theta_{23} + \delta_3 - \delta_2) \right]$$

$$P_2^0 = [(1.04)(1)(12.13)\cos(104.04 + 0 - 0) + (1)^2(24.23)\cos(-75.95^\circ) \\ + (1)(1.04)(12.13)\cos(104.04^\circ + 0 - 0)] \\ = -3.064 + 5.8822 - 3.0604 \\ = -0.2385 \text{ p.u.}$$

$$P_3^0 = [(1.04)(1.04)(12.13)\cos(104.04 + 0 - 0) + (1.04) \times 12.13(\cos 104.04) \\ + (1.04)^2(24.23)\cos(-75.95)] \\ = -3.18285 - 3.0604 + 6.3622 \\ = 0.119 \text{ p.u.}$$

Similarly,  $Q_2^0 = -0.9715 \text{ p.u.}$

Checking for  $Q_3$  range

$$Q_3 = -|V_3||V_1|Y_{31}\sin(\theta_{31} + \delta_1^{(0)} - \delta_3^{(0)}) - |V_3|^2 Y_{33}\sin(\theta_{33}) \\ - V_3 V_2 Y_{32}\sin(\theta_{32} + \delta_2^{(0)} - \delta_3^{(0)}) \\ = -12.7278 + 25.423 - 12.238 = 0.2686$$

$$Q_{G3}^{(0)} = Q_{D3} + \Delta Q_3^{(0)} = 0.6 + 0.2686 = 0.8686 \text{ p.u.}$$

Power residual,

$$\Delta P_2^0 = P_2(\text{specified}) - \Delta P_2^0(\text{Calculated}) = 0.5 - (-0.235) \\ = 0.7385 \text{ p.u.}$$

$$\Delta P_3^0 = -1.5 - (0.119) = -1.619 \text{ p.u.}$$

$$\Delta Q_2^0 = 1 - (-0.9715) = 1.9715 \text{ p.u.}$$

So matrix equations for the solution of load flow by FDLF method,

$$\begin{bmatrix} \frac{\Delta P_2^{(0)}}{|V_2^{(0)}|} \\ \frac{\Delta P_3^{(0)}}{|V_3^{(0)}|} \end{bmatrix} = \begin{bmatrix} -B_{22} & -B_{23} \\ -B_{32} & -B_{33} \end{bmatrix} \begin{bmatrix} \Delta \delta_2^{(0)} \\ \Delta \delta_3^{(0)} \end{bmatrix}$$

$$\text{and} \quad \left[ \frac{\Delta Q_2^{(0)}}{|V_2^{(0)}|} \right] = [-B_{22}] [\Delta |V_2^{(0)}|]$$

Here  $B_{22}$  and  $B_{33}$  are the imaginary parts of  $Y_{22}$  and  $Y_{33}$

$$\begin{bmatrix} \frac{0.7385}{1} = 0.7385 \\ \frac{-1.619}{1.04} = -1.5567 \end{bmatrix} = \begin{bmatrix} 23.528 & -11.764 \\ -11.764 & 23.528 \end{bmatrix} \begin{bmatrix} \Delta \delta_2^{(0)} \\ \Delta \delta_3^{(0)} \end{bmatrix}$$

Solving above equation,

$$\Delta \delta_2^{(0)} = -0.0023 \text{ rad}$$

$$\Delta \delta_3^{(0)} = -0.0673 \text{ rad}$$

$$\delta_2^{(1)} = 0 - 0.0023 = -0.0023 \text{ rad or } -0.13178^\circ$$

$$\delta_3^{(1)} = 0 - 0.0673 = -0.0673 \text{ rad or } -3.856^\circ$$

$$Q_2^{(0)} = \left( -1.04 \times 1 \times 12.13 \sin \left( 104.04^\circ + 0 + 0.0023 \times \frac{180}{\pi} \right) - (24.23) \sin(-75.95^\circ) \right.$$

$$\left. - (1.04)(12.13 \sin \left( 104.04 + 0.0023 \times \frac{180}{\pi} - 0.0673 \times \frac{180}{\pi} \right)) \right)$$

$$= -12.231 + 23.50 - 12.411 = -1.14227 \text{ p.u.}$$

$$\Delta Q_2^{(0)} = 1 - (-1.14227) = -2.14227 \text{ p.u.}$$


$$-2.14227 = 23.528 (\Delta V_2^{(0)})$$

$$\Delta |V_2^{(0)}| = 0.091$$




$$|V_2^{(1)}| = |V_2^{(0)}| + \Delta |V_2^{(0)}| = 1 + 0.091 = 1.091 \text{ p.u.}$$

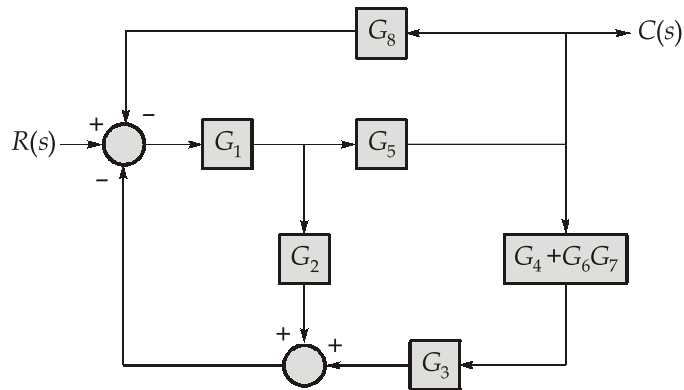**Q.4 (c) Solution:**

Combining blocks  $G_6$  and  $G_7$  and adding the forward path block  $G_4$ , gives



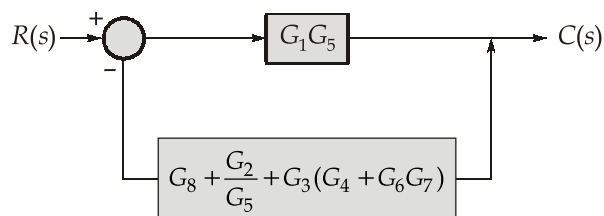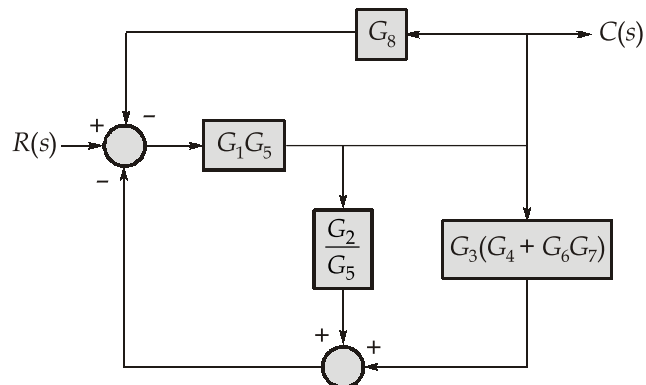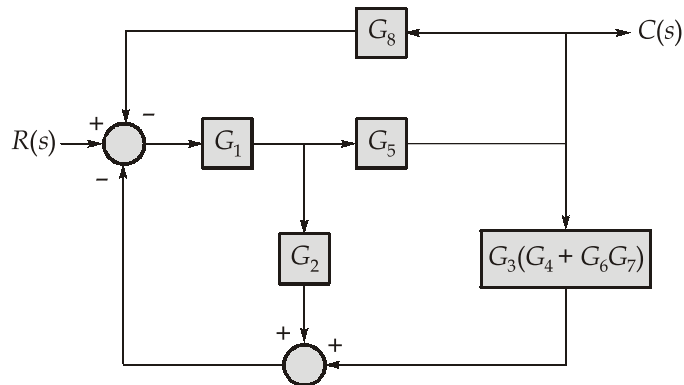
Combining  $G_3$  and  $(G_4 + G_6G_7)$  gives



$$\begin{aligned}
 \frac{C(s)}{R(s)} &= \frac{G_1 G_5}{1 + G_1 G_5 \left[ G_8 + \frac{G_2}{G_5} + G_3 (G_4 + G_6 G_7) \right]} \\
 &= \frac{G_1 G_5}{1 + G_1 G_5 G_8 + G_1 G_2 + G_1 G_3 G_5 (G_4 + G_6 G_7)} \\
 &= \frac{G_1 G_5}{1 + G_1 (G_2 + G_5 G_8 + G_3 G_4 G_5 + G_3 G_5 G_6 G_7)}
 \end{aligned}$$

### Section-B

Q.5 (a) Solution:

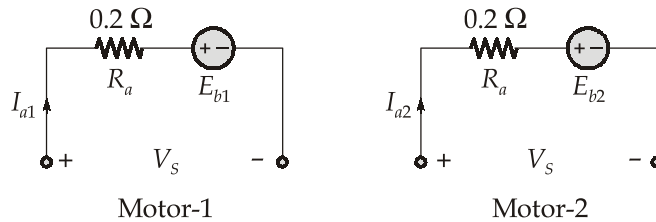

For motor-1,

The speed

$$N_1 = 600 \text{ rpm}$$

$$I_{a1} = I_{a2} = 50 \text{ A}$$

Back emf,

$$E_{b1} = V_s - I_{a1} \cdot R_a = 400 - 50 \times 0.2 = 390 \text{ volt}$$

It will also be the same for motor-2,

$$E_{b2} = E_{b1} = 390 \text{ volt}$$

Since current is constant in all cases

$$E_b \propto N$$

$\Rightarrow$

$$E_b = kN$$


$$E_{b1} = K_1 N_1 \text{ and } E_{b2} = K_2 N_2$$

$$390 = K_1(600) ; 390 = K_2(650)$$

$$K_1 = 0.65 \text{ V/rpm}; K_2 = 0.6 \text{ V/rpm}$$

Now motors are mechanically coupled,

So,

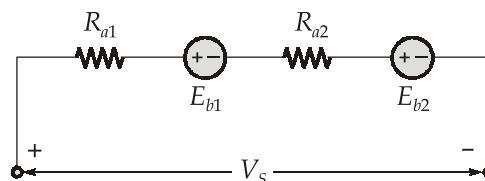



$$E_{b1} + E_{b2} = V_S - I_a (R_{a1} + R_{a2})$$

$$= 500 - 50 (2 \times 0.2) = 480 \text{ V}$$

Let speed is  $N$ ,

So,

$$E_{b1} = K_1 \cdot N = 0.65 N$$

$$E_{b2} = K_2 \cdot N = 0.6 N$$

$$E_{b1} + E_{b2} = 0.65 N + 0.6 N = 480 \text{ V}$$

$$1.25 N = 480$$

$$N = 384 \text{ rpm}$$

### Q.5 (b) Solution:

Given, variable capital cost of cable = 20000  $a$  per km

Annual charges on account of interest and depreciation

$$P_2 a = \text{Rs } 20000 a \times \frac{12}{100} = 2400 a \text{ per km}$$

Resistance of each conductor of ' $a$ '  $\text{cm}^2$  cross-sectional area,

$$R = \frac{0.173}{a} \text{ per km}$$

Current in each conductor,

$$I = \frac{\text{Power supplied (in kW)}}{\sqrt{3} \times \text{line voltage in kV} \times \text{p.f.}}$$

$$= \frac{1500}{\sqrt{3} \times 11 \times 0.8} = 98.412 \text{ A}$$

Total power loss in all three conductors for 1 km length

$$W = 3I^2R = 3 \times (98.412)^2 \times \frac{0.173}{a} = \frac{5026.47}{a} \text{ Watt}$$

$$\text{Energy loss per annum} = \text{Loss (kW)} \times \text{working hour/annum}$$

$$= \frac{5026.47}{a \times 1000} \times 300 \times 8 = \frac{12063.528}{a} \text{ kWh}$$

Annual cost of energy loss,

$$\frac{P_3}{a} = 0.02 \times \frac{12063.528}{a} = \frac{241.27}{a}$$

For most economical cross section of conductor

$$2400 a = \frac{241.27}{a}$$

$$a^2 = \frac{241.27}{2400} \text{ or } a = 0.317 \text{ cm}^2$$

Diameter of conductor,  $d = \sqrt{\frac{4a}{\pi}} = \sqrt{\frac{4 \times 0.317}{\pi}} = 0.635 \text{ cm}$

So, current density,  $D = \frac{I}{a} = \frac{98.412}{0.317} = 310.4 \text{ A/cm}^2$

### Q.5 (c) Solution:

XRA 11H	(To reset the CY flag)
MVI C, FFH	(Load FFH to register C immediately)
MOV A, C	(Transfer FFH to accumulator from register C)
ADI 01H	(Add 01H to FFH which gives 100H as result)
MOV C, A	(Move contents of accumulator to register C)
OUT Display	(Display the content of register C to LED location)
HLT	(Stop the operation)

(Display is the location where LED's are connected for display of content.)


### Q.5 (d) Solution:

Given transfer function,


$$\frac{C(s)}{R(s)} = \frac{24}{s^3 + 9s^2 + 26s + 24}$$

$$\frac{C(s)}{R(s)} = \frac{24}{(s+2)(s+3)(s+4)}$$


Block diagram model,

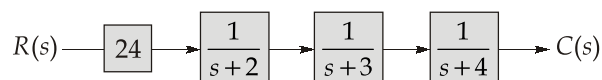

State model:

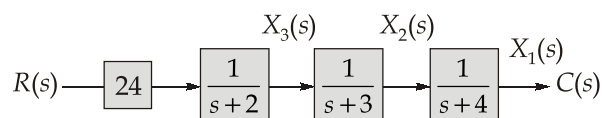

The above block diagram can be draw as

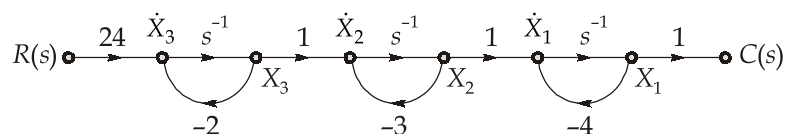

$$\frac{X_1(s)}{X_2(s)} = \frac{1}{s+4} = \frac{s^{-1}}{1+4s^{-1}} = \frac{s^{-1}}{1-(-4s^{-1})}$$

$$\frac{X_2(s)}{X_3(s)} = \frac{1}{s+3} = \frac{s^{-1}}{1+3s^{-1}} = \frac{s^{-1}}{1-(-3s^{-1})}$$

$$\frac{X_3(s)}{R(s)} = \frac{24}{s+2} = \frac{24s^{-1}}{1+2s^{-1}} = \frac{24s^{-1}}{1-(-2s^{-1})}$$

∴

$$\dot{X}_1 = X_2 - 4X_1$$

$$\dot{X}_2 = X_3 - 3X_2$$

$$\dot{X}_3 = -2X_3 + 24R$$

$$\begin{bmatrix} \dot{X}_1 \\ \dot{X}_2 \\ \dot{X}_3 \end{bmatrix} = \begin{bmatrix} -4 & 1 & 0 \\ 0 & -3 & 1 \\ 0 & 0 & -2 \end{bmatrix} \begin{bmatrix} X_1 \\ X_2 \\ X_3 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 24 \end{bmatrix} R$$

$$C = [1 \quad 0 \quad 0] \begin{bmatrix} X_1 \\ X_2 \\ X_3 \end{bmatrix}$$

### Q.5 (e) Solution:

Given, characteristic equation of the control system,

$$s^5 + 2s^4 + 4s^3 + 8s^2 + 3s + 1 = 0$$

RH-criteria,

$$\begin{array}{c|ccc} s^5 & 1 & 4 & 3 \\ s^4 & 2 & 8 & 1 \\ s^3 & 0 & 2.5 & \\ s^2 & \infty & & \\ s^1 & & & \\ s^0 & & & \end{array}$$

Here, the RH-criteria fails. To remove the above difficulty,

1. Replace 0 by  $\epsilon$  (very small number) and complete the array with  $\epsilon$
2. Examine the sign change by taking  $\epsilon \rightarrow 0$ .

Now, Routh array becomes,

$$\begin{array}{c|ccc}
 s^5 & 1 & 4 & 3 \\
 s^4 & 2 & 8 & 1 \\
 s^3 & \epsilon & 2.5 & 0 \\
 s^2 & \frac{5-8\epsilon}{\epsilon} & 1 & 0 \\
 s^1 & \frac{2.5\frac{5-8\epsilon}{\epsilon} - \epsilon}{\frac{5-8\epsilon}{\epsilon}} & & \\
 s^0 & \epsilon & & \\
 & 1 & & 
 \end{array}$$

Now putting  $\epsilon \rightarrow 0$ , Routh's array becomes,

$$\begin{array}{c|ccc}
 s^5 & 1 & 4 & 3 \\
 s^4 & 2 & 8 & 1 \\
 s^3 & \epsilon & 2.5 & 0 \\
 s^2 & \frac{5-8\epsilon}{\epsilon} = -\infty & 1 & 0 \\
 s^1 & 2.5 & & \\
 s^0 & 1 & & 
 \end{array}$$

There are two sign changes in first column elements of this array. Therefore the system is unstable.

#### Q.6 (a) Solution:

(i) Using table, the amplitude of the 60 Hz fundamental frequency is

$$V_1 = m_a V_{dc} = (0.8)(100) = 80 \text{ V}$$

The current amplitudes are determined using phasor analysis,

$$I_n = \frac{V_n}{Z_n} = \frac{V_n}{\sqrt{R^2 + (n\omega_0 L)^2}}$$

For the fundamental frequency,

$$\begin{aligned}
 I_1 &= \frac{80}{\sqrt{10^2 + [(1)(2\pi 60)(0.02)]^2}} \\
 &= 6.39 \text{ A}
 \end{aligned}$$

(ii) With  $m_f = 21$ , the first harmonics are at  $n = 21, 19$  and  $23$ . Using table,

$n$	$f_n(\text{Hz})$	$V_n(\text{V})$	$Z_n(\Omega)$	$I_{n,\text{rms}}(\text{A})$	$P_n(\text{W})$
1	60	80.0	12.5	4.52	204.0
19	1140	22.0	143.6	0.11	0.1
21	1260	81.8	158.7	0.36	1.3
23	1380	22.0	173.7	0.09	0.1

$$V_{21} = (0.82)(100) = 82 \text{ V}$$

$$V_{19} = V_{23} = (0.22)(100) = 22 \text{ V}$$

Current at each of the harmonics is determined.

Power at each frequency is determined,

$$P_n = (I_{n,\text{rms}})^2 R = \left( \frac{I_n}{\sqrt{2}} \right)^2 R$$

The resulting voltage amplitudes, currents, and powers at these frequencies are summarized in table.

Power absorbed by the load resistor is,

$$P = \sum P_n \approx 204.0 + 0.1 + 1.3 + 0.1 = 205.5 \text{ W}$$

Higher order harmonics contribute little power and can be neglected.

(c) The THD of the load current is determined with the rms current of the harmonics approximated by the first few terms indicated in table.

$$\begin{aligned} \text{THD}_1 &= \frac{\sqrt{\sum_{n=2}^{\infty} I_{n,\text{rms}}^2}}{I_{1,\text{rms}}} \approx \frac{\sqrt{(0.11)^2 + (0.36)^2 + (0.09)^2}}{4.52} \\ &= 0.087 = 8.7\% \end{aligned}$$

By using the truncated Fourier series in table, the THD will be underestimated. However, since the impedance of the load increases and the amplitudes of the harmonics generally decrease as  $n$  increases, the above approximation should be acceptable. (Including currents through  $n = 100$  gives a THD of 9.1 percent).


#### Q.6 (b) (i) Solution:

1. Impedance of 66 kV feeder =  $(120 + j400) \Omega$

Equivalent impedance of transformer

referred to LV side =  $(0.4 + j1.5)\Omega$

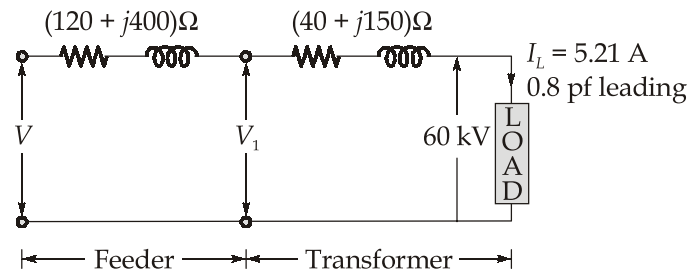referred to HV side =  $(40 + j150)\Omega$



Load of 250 kW at 0.8 pf leading at 6 kV

$$I_L = \frac{250}{6 \times 0.8} = 52.08 \angle 36.86^\circ \text{ A}$$

$$I_L' \text{ (HV side)} = \frac{52.08}{10} = 5.21 \angle 36.86^\circ \text{ A}$$

$$\begin{aligned} \text{Sending end voltage, } V &= 60 \times 10^3 + 5.21 (160 \times 0.8 - 550 \times 0.6) \\ &= 58.95 \text{ kV} \end{aligned}$$

2. Primary voltage of transformer,

$$V_1 = 60 \times 10^3 + 5.21 (40 \times 0.8 - j150 \times 0.6) = 59.7 \text{ kV}$$

$$\text{Active power loss} = (5.21)^2 \times 160 \times 10^{-3} = 4.34 \text{ kW}$$

$$\text{Reactive power loss} = (5.21)^2 \times 550 \times 10^{-3} = 14.92 \text{ kVAR}$$

$$\begin{aligned} \text{Power received} &= (250 - j250 \tan \cos^{-1} 0.8) \\ &= (250 - j187.5) \text{ kVA} \end{aligned}$$

3. Complex power input =  $\vec{S}$

$$\vec{S} = (250 + 4.34) + j(-187.5 + 14.92)$$

$$\vec{S}_{\text{input}} = (254.34 - j172.60) \text{ kVA}$$

**Q.6 (b) (ii) Solution:**

$$1. \quad P_C = 95 \text{ Watt} \rightarrow \text{Core loss}$$

$$I_2 \text{ (H.V. side)} = \frac{20 \times 10^3}{2000} = 10 \text{ A}$$

$$\text{Full load } P_C = 10^2 \times 2.65 = 265 \text{ watt}$$

$$P_{\text{out}} = 20 \times 0.8 = 16 \text{ kW}$$

$$\text{Percentage, } \eta = \frac{x \times \text{kVA} \times \cos \phi}{x \times \text{kVA} \times \cos \phi + P_C + P_{Cu}(f_L)} \times 100$$

$$\% \eta = \frac{16}{16 + 0.95 + 0.265} \times 100 = 97.80\%$$

$$2. \quad X_{eq} \text{ (HV)} = \sqrt{Z_{eq}^2 - R_{eq}^2} = \sqrt{(4.23)^2 - (2.65)^2}$$

$$= 3.2970 \, \Omega \approx 3.30 \, \Omega$$

$$\text{Voltage drop across impedance} = I_2(R_{eq} \cos \phi + X_{pu} \sin \phi)$$

$$\text{Voltage drop} = 10(2.65 \times 0.8 + 3.3 \times 0.6) = 41 \text{ Volt}$$

$$\text{HV side applied voltage} = 2000 + 41 = 2041 \text{ Volt}$$

$$3. \quad \% \text{ voltage regulation} = \frac{2041 - 2000}{2000} \times 100 = 2.05\%$$

**Q.6 (c) Solution:**

$$(i) \quad \text{The transfer function of the given system is } \frac{C(s)}{R(s)} = \frac{10}{s^2 + 2s + 10}$$

$$\text{Here} \quad H(s) = 1 \text{ and } G(s) = \frac{10}{s(s+2)}$$

$$\text{Therefore,} \quad \frac{C(s)}{R(s)} = \frac{G(s)}{1 + G(s)H(s)}$$

The characteristic equation is

$$s^2 + 2s + 10 = 0$$

Comparing with characteristic equation of second-order unity feedback system,

$$\text{We get} \quad \omega_n = \sqrt{10} = 3.16 \text{ rad/sec}$$

$$\text{and} \quad 2\xi\omega_n = 2$$

$$\text{or} \quad \xi = \frac{1}{\omega_n} = \frac{1}{3.16} = 0.32$$

$$\omega_d = \omega_n \sqrt{1 - \xi^2} = 3.16 \sqrt{1 - 0.32^2} = 3 \text{ rad/sec}$$

$$\beta = \tan^{-1} \frac{\sqrt{1 - \xi^2}}{\xi} = \tan^{-1} \frac{\sqrt{1 - 0.32^2}}{0.32} = 71.34^\circ$$

Now the output response is given by

$$c(t) = 1 - \frac{e^{-\xi\omega_n t}}{\sqrt{1 - \xi^2}} \sin(\omega_d t + \beta)$$

Substituting the values in the expression, we get

$$c(t) = 1 - \frac{e^{-0.32 \times 3.16 t}}{\sqrt{1 - 0.32^2}} \sin(3t + 71.34^\circ)$$

$$\text{or} \quad c(t) = 1 - 1.05e^{-t} \sin(3t + 71.34^\circ)$$

- (ii) The natural frequency ( $\omega_n$ ) and damping ratio ( $\xi$ ) have been calculated in part (i) above as

$$\omega_n = 3.16 \text{ rad/sec}$$

- (iii) Peak overshoot

$$\%M_p = 100 \times e^{-\frac{0.32}{\sqrt{1-\xi^2}}\pi} = 100 \times e^{-\frac{0.32}{\sqrt{1-0.32^2}}\pi} = 34.63\%$$

Peak time,  $t_p = \frac{\pi}{\omega_n \sqrt{1-\xi^2}} = \frac{\pi}{3.16 \sqrt{1-0.32^2}} = 1.04 \text{ sec}$

- (iv) Steady-state error

The input is  $= 1 + 4t$ . In Laplace transform for

$$R(s) = \frac{1}{s} + \frac{4}{s^2} = \frac{s+4}{s^2}$$

Now 
$$E(s) = \frac{R(s)}{1+G(s)H(s)} = \left[ \frac{1}{1 + \frac{10}{s(s+2)} \times 1} \right] \times \frac{s+4}{s^2} = \frac{s(s+4)(s+2)}{s^2(s^2+2s+10)}$$

$$e_{ss} = \lim_{s \rightarrow 0} sE(s) = \frac{s \times s(s+4)(s+2)}{s^2(s^2+2s+10)} = \frac{8}{10} = 0.8$$

(v) Now 
$$G(s) = \frac{10}{s(s+2)}$$

It is given that poles are added at  $\pm j\sqrt{3}$ . This mean  $G(s)$  will have another denominator term equal to  $(s^2 + 3)$ . Therefore

$$G(s) = \frac{10}{s(s+2)(s^2+3)}$$

The characteristic equation is  $1 + GH = 0$  ;

i.e 
$$1 + \frac{10}{s(s+2)(s^2+3)} = 0$$

or 
$$s(s+2)(s^2+3) + 10 = 0$$

or 
$$s^4 + 2s^2 + 3s^2 + 6s + 10 = 0$$

Now, we have to find the absolute stability. This we will ascertain by Routh Hurwitz criterion.



$s^4$	1	3	10
$s^3$	2	6	0
$s^2$	0	10	0

A zero has appeared in the first column  $s^2$  row.

Therefore, putting  $s = \frac{1}{z}$  in the characteristic equation, we get

$$10z^4 + 6z^3 + 3z^2 + 2z + 1 = 0$$

Developing the Routh's array, we get


$z^4$	1	3	1
$z^3$	2	6	0
$z^2$	$-1/3$	10	0
$z^1$	20	0	0
$z^0$	1	0	0

Sign  
change  
Sign  
change

There are two sign changes in the first column of the Routh's array. Hence, there are two roots lying on the right hand side of  $s$ -plane. Hence, the closed-loop system unstable.
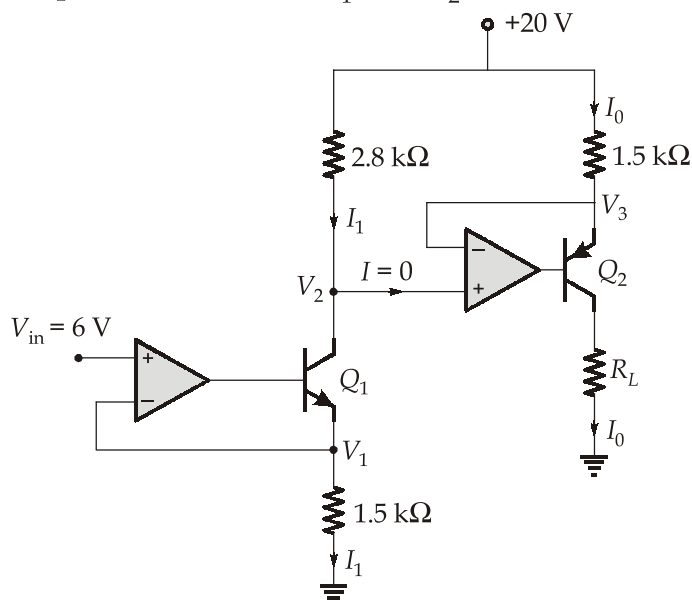
### Q.7 (a) (i) Solution:

Assuming: both op-amps to be ideal and  $Q_1$  and  $Q_2$  to be in saturation.



Here,

$$V_1 = V_{in} = 6 \text{ V (voltage follower)}$$

So,

$$I_1 = \frac{V_1}{1.5} = \frac{6}{1.5} = 4 \text{ mA}$$

By KVL,

$$\begin{aligned} V_2 &= V_{CC} - (I_1)2.8 \\ &= 20 - 4 \times 2.8 = 8.8 \text{ V} \end{aligned}$$

Using the virtual-short concept,

$$V_3 = V_2 = 8.8 \text{ V}$$

So,

$$I_0 = \frac{V_{CC} - V_3}{1.5} = \frac{20 - 8.8}{1.5} = 7.467 \text{ mA}$$

So, output current,

$$I_0 = 7.467 \text{ mA}$$

For maximum value of  $R_L$ , the transistor  $Q_2$  should be at boundary of active and saturation.

So,

$$(V_{EC})_{sat} = 0.2 \text{ V}$$

Applying KVL in transistor  $Q_2$ ,

$$\begin{aligned} V_{CC} &= I_0(1.5 + R_L) + (V_{EC})_{sat} \\ 20 &= 7.467(1.5 + R_L) + 0.2 \end{aligned}$$

$$R_L + 1.5 = \frac{20 - 0.2}{7.467}$$

$$R_L = \frac{19.8}{7.467} - 1.5 = 1.151 \text{ k}\Omega$$

$$R_L = 1.151 \text{ k}\Omega$$

So, maximum value of  $R_L = 1.15 \text{ k}\Omega$

### Q.7 (a) (ii) Solution:

Given,

$$m(t) = 5 \sin(2\pi \times 1000t) + 2 \sin(2\pi \times 2000t)$$

$$f_s = 56000 \text{ Hz}$$

To avoid slope overload distortion, we have

$$\frac{\Delta}{T_s} \geq \left. \frac{dm(t)}{dt} \right|_{\max}$$

or

$$\Delta f_s \geq \left. \frac{dm(t)}{dt} \right|_{\max}$$

$$\begin{aligned}\Delta \times 56000 &= 10000\pi \cos(2\pi \times 1000t) + 8000\pi \cos(2\pi \times 2000t) \Big|_{\max} \\ &= 10000\pi + 8000\pi\end{aligned}$$

$$\Delta \times 56000 = 18000\pi$$

$$\therefore D = \frac{18000\pi}{56000} = 1 \text{ V}$$

**Q.7 (b) Solution:**

**Step-1:** Establishing bus (1) with its impedance to the reference bus.

$$Z_{\text{bus}, 1} = [j 1.2] \text{ } 1 \times 1 \text{ bus impedance matrix.}$$

**Step-2:** Establishing bus (2) with its impedance to bus.

$$Z_{\text{bus}, 2} = \begin{bmatrix} j1.2 & j1.2 \\ j1.2 & j1.4 \end{bmatrix}$$

The term  $j 1.4$  above is sum of  $j 1.2$  and  $j 0.2$ . The element  $j 1.4$  in the new row and column are the repetition of the element of row 1 and column 1 of the matrix being modified.

**Step-3:** Bus (3) with the impedance connecting to bus (2),

$$Z_{\text{bus}, 3} = \begin{bmatrix} j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.4 \\ j1.2 & j1.4 & j1.55 \end{bmatrix}$$

**Step-4:** Add the impedance  $Z_s = j 1.5$  between the reference bus and bus (3).

Using below equation - Type 3 modification

$$Z_{\text{bus}, \text{new}} = Z_{\text{busold}} - \frac{1}{Z_{kk} + Z_s} \begin{bmatrix} Z_{1k} \\ Z_{2k} \\ '' \\ '' \\ Z_{nk} \end{bmatrix} [Z_{k1} \ Z_{k2} \ \dots \ Z_{kn}] \quad \dots(i)$$

$$\begin{aligned}Z_{\text{bus}, 4} &= \begin{bmatrix} j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.4 \\ j1.2 & j1.4 & j1.55 \end{bmatrix} - \frac{1}{j1.55 + j1.5} \begin{bmatrix} j1.2 \\ j1.4 \\ j1.55 \end{bmatrix} [j1.2 \ j1.4 \ j1.55] \\ &= \begin{bmatrix} j0.7279 & j0.6492 & j0.5302 \\ j0.6492 & j0.7574 & j0.6885 \\ j0.5902 & j0.6885 & j0.7623 \end{bmatrix}\end{aligned}$$

**Step-5:** Add the impedance  $Z_s = j 0.3$  between the bus (1) and bus (3).

Use type 4 modification:

$$Z_{\text{bus, new}} = Z_{\text{Bus, old}} - \frac{1}{Z_{kk} + Z_{ii} + Z_s - 2Z_{ik}} \begin{bmatrix} Z_{1i} & - & Z_{1k} \\ \vdots & & \vdots \\ Z_{ni} & - & Z_{nk} \end{bmatrix} \times [Z_{i1} - Z_{k1} \dots Z_{in} - Z_{kn}]$$

$$Z_{\text{bus, 5}} = \begin{bmatrix} j0.7279 & j0.6492 & j0.5902 \\ j0.6492 & j0.7574 & j0.6885 \\ j0.5902 & j0.6885 & j0.7623 \end{bmatrix} - \frac{1}{j0.6098} \begin{bmatrix} j0.3177 \\ j0.0393 \\ -j0.1721 \end{bmatrix} \times [j0.3177 - j0.0393 - j0.1721]$$

$$Z_{\text{bus, 5}} = \begin{bmatrix} j0.7279 & j0.6492 & j0.5902 \\ j0.6492 & j0.7574 & j0.6885 \\ j0.5902 & j0.6885 & j0.7623 \end{bmatrix} - \begin{bmatrix} j0.031 & -j0.0087 & -j0.03886 \\ -j0.00887 & j0.002533 & j0.01109 \\ -j0.03886 & j0.01109 & j0.04857 \end{bmatrix}$$

$$= j \begin{bmatrix} 0.6969 & 0.65807 & 0.62906 \\ 0.65807 & 0.75487 & 0.67741 \\ 0.62906 & 0.67741 & 0.71373 \end{bmatrix}$$

**Step-6:** Add the impedance  $Z_s = j 0.25$  between the bus (3) and bus (4).

i.e. repeat the step. (2) or similar as step (2),

$$Z_{\text{bus, 6}} = j \begin{bmatrix} 0.6969 & 0.65807 & 0.62906 & 0.62906 \\ 0.65807 & 0.75487 & 0.67741 & 0.67741 \\ 0.62906 & 0.67741 & 0.71373 & 0.71373 \\ 0.62906 & 0.67741 & 0.71373 & 0.96373 \end{bmatrix}$$

**Step-7:** Add the impedance  $Z_s = j 0.12$  between the bus (2) and bus (4).

Similar as step (5),

$$Z_{\text{bus, 7}} = j[Z_{\text{Bus, 6}}] - \frac{j}{0.48377} \begin{bmatrix} 0.02901 \\ 0.077457 \\ -0.03632 \\ -0.28632 \end{bmatrix} [0.02901, 0.077457 - 0.03632 - 0.28632]$$

$$Z_{\text{bus, 7}} = j[Z_{\text{Bus, 6}}] - j \begin{bmatrix} 0.00174 & 0.004645 & -0.002178 & -0.01717 \\ 0.004645 & 0.0124 & -0.005815 & -0.04584 \\ -0.002178 & -0.005815 & 0.002727 & 0.21496 \\ -0.01717 & -0.04584 & 0.021496 & 0.169456 \end{bmatrix}$$

$$Z_{\text{bus}, 7} = j \begin{bmatrix} 0.69516 & 0.653425 & 0.631238 & 0.64623 \\ 0.653425 & 0.742467 & 0.683225 & 0.72325 \\ 0.631238 & 0.683225 & 0.711003 & 0.692234 \\ 0.64623 & 0.72325 & 0.692234 & 0.794274 \end{bmatrix}$$

**Note:** If any element removing from the system then connected those element with  $-Z_b$  ( $Z_b$  with negative sign) in respective buses.

**Q.7 (c) Solution:**

(i) Given, message signal  $m(t)$

$$\therefore f_m = 10 \text{ kHz}$$

Since, the VCO output is an FM signal

$\therefore$  The bandwidth of FM signal is according to Carson's formula,

$$\text{Bandwidth} = 2\Delta f + 2f_m$$

where, frequency deviation,

$$\Delta f = K_f (\text{maximum } m(t))$$

$$\therefore \Delta f = 25 \text{ kHz/mV} \times 2 \text{ mV} = 50 \text{ kHz}$$

$$\therefore \text{Bandwidth} = 2 \times 50 \text{ k} + 2 \times 10 \text{ k} = 120 \text{ kHz}$$

(ii) The output of VCO is the FM signal,

$$\text{i.e., } S_{FM}(t) = A_c \cos \left[ 2\pi f_c t + 2\pi K_f \int m(t) dt \right]$$

$$\text{or, } = A_c \cos [2\pi f_c t + \theta_c(t)]$$

The output of the filter,  $f_c \pm n f_m$

$$\text{Given, } f_c = 5 \text{ MHz and } f_m = 10 \text{ kHz}$$


$$\text{For } n = 1, 5000 \text{ K} + 1 \times 10 \text{ K} = 5010 \text{ K}$$

$$n = 2, 5000 \text{ K} + 2 \times 10 \text{ K} = 5020 \text{ K}$$

$$n = 3, 5000 \text{ K} + 3 \times 10 \text{ K} = 5030 \text{ K}$$

$$\vdots \quad \quad \quad \vdots \quad \quad \quad \vdots$$

Given, bandpass filter,

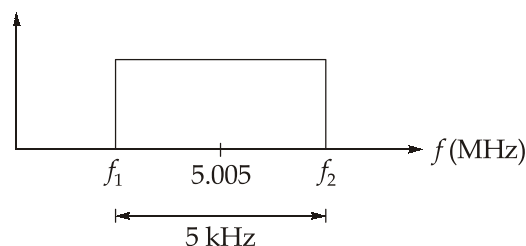

$$\therefore \quad f_1 = 5005 \text{ K} - 2.5 \text{ K} = 5.0025 \text{ MHz}$$

$$f_2 = 5005 \text{ K} + 2.5 \text{ K} = 5.0075 \text{ MHz}$$

$\therefore$  The given bandpass filter does not capture any of the frequency components of FM.

Hence, the output of BPF is zero.

### Q.8 (a) Solution:

The process of conversion of an analog signal to digital signal is referred to as analog to digital conversion, whereas the process of conversion of a digital signal to analog signal is referred to as digital to analog conversion.


#### Digital to Analog Converters :

1. R-2R ladder digital to analog converter
2. Weighted-resistor type analog converter

#### Analog to Digital Converters :

1. Counter type ADC
2. Successive approximation type ADC
3. Flash type ADC
4. Ramp type ADC
5. Dual slope type ADC

#### Circuit Diagram of Dual Slope ADC :

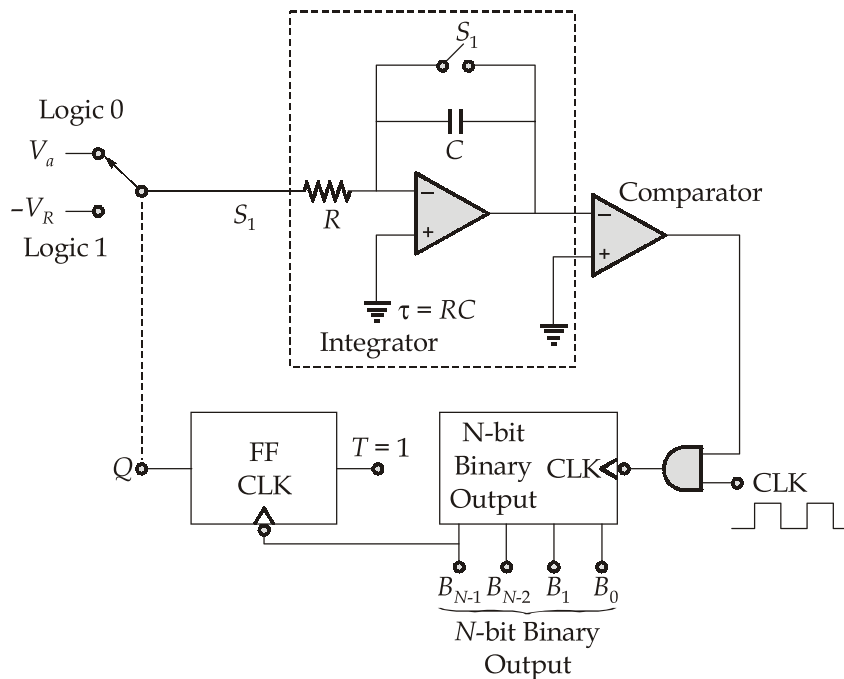

The conversion process begins at  $t = 0$  with the switch  $S_1$  in position 0 thereby connecting the analog voltage  $V_a$  to the input of the integrator.


The integrator output

$$V_o = -\frac{1}{\tau} \int_0^t V_a dt = -\left(\frac{V_a}{\tau}\right)t$$

This results in high  $V_c$ , thus enabling the AND gate and the clock. The counter counts from 00 --- 00 to 111 --- 11. When  $2^N - 1$  clock pulses are applied. At the next clock pulse  $2^N$ , the counter is cleared and  $Q$  becomes 1. This controls the state of  $S_1$  which now moves to position 1 at  $T_1$ , thereby connecting  $-V_R$  to the input of the integrator.

The output of the integrator now starts to move in the positive direction. The counter continues to count until  $V_o < 0$ . As soon as  $V_o$  goes positive at  $T_2$ ,  $V_c$  goes low disabling the AND gate.

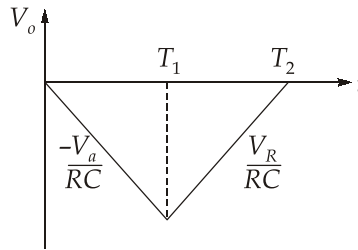The counter will stop counting in the absence of the clock pulses. The waveforms of voltage  $V_o$  and  $V_c$  are shown in figure below.



The time  $T_1$  is given by :

$$T_1 = 2^N T_c$$

where  $T_c$  is the time period of the clock pulses. When the switch  $S_1$  is in position 1,

$$V_o = -\frac{V_a}{\tau} T_1 + \frac{V_R}{\tau} (t - T_1) \quad (V_o = 0 \text{ at } t = T_2)$$

Therefore,

$$T_2 - T_1 = \frac{V_a}{V_R} T_1 = \frac{V_a}{V_R} 2^N T_c$$

Let the count recorded in the counter be  $n$  at  $T_2$ .

Therefore,

$$T_2 - T_1 = n \cdot T_c = \frac{V_a}{V_R} 2^N T_c$$

$\therefore$

$$n = \frac{V_a}{V_R} 2^N$$

Q.8 (b) Solution:

$$G(s)H(s) = \frac{1.25(s+1)}{(s+0.5)(s-2)} = \frac{1.25(j\omega+1)}{(j\omega+0.5)(j\omega-2)}$$

At  $\omega = 0$ ;

$$G(j\omega)H(j\omega) = \frac{1.25 \times 1}{0.5 \times 2} = -1.25$$

Gives,

$$M = \frac{1.25\sqrt{1+\omega^2}}{\sqrt{0.5^2 + \omega^2}\sqrt{(-2)^2 + \omega^2}}$$

and

$$\phi = \tan^{-1} \omega - \tan^{-1} \left( \frac{\omega}{0.5} \right) - \tan^{-1} \left( \frac{\omega}{-2} \right)$$

When,  $\omega = 0$ ;

$$M = \frac{1.25}{\sqrt{0.5^2 \times 4}} = 1.25 \angle 0 - 0 - (-180^\circ) = -1.25 \angle 180^\circ$$

$\omega = \infty$ ;

$$M = 0 \angle 90^\circ - 90^\circ - (-270^\circ) = 0 \angle 270^\circ$$

Intersection with negative real axis

$$\begin{aligned} G(j\omega)H(j\omega) &= \frac{1.25(1+j\omega)}{(0.5+j\omega)(j\omega-2)} \\ &= \frac{1.25(1+j\omega)(0.5-j\omega)(-2-j\omega)}{(0.5+j\omega)(0.5-j\omega)(-2+j\omega)(-2-j\omega)} \\ &= \frac{1.25(1+j\omega)(-1+1.5j\omega-\omega^2)}{(0.25+\omega^2)(4+\omega^2)} \\ &= \frac{-1.25(1+2.5\omega^2)}{(0.25+\omega^2)(4+\omega^2)} + \frac{1.25j\omega(0.5-\omega^2)}{(0.25+\omega^2)(4+\omega^2)} \end{aligned}$$

Equating imaginary part to zero gives

$$0.5 - \omega^2 = 0$$

or


$$\omega = 0.707$$

Putting the value of  $\omega$  in the real part gives

$$a = \frac{-1.25(1+2.5 \times 0.5)}{(0.25+0.5)(4+0.5)} = -0.833$$



Nyquist plot is shown in figure below,

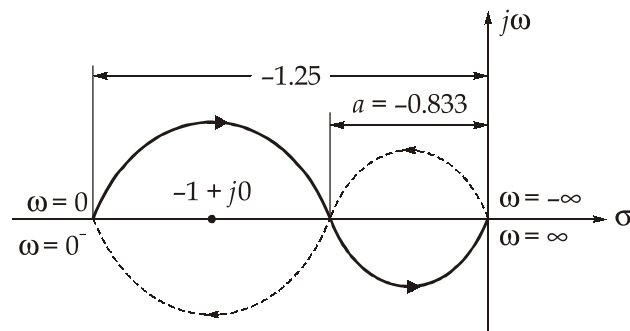

It can be seen that the Nyquist plot makes one clockwise encirclement of point  $-1 + j0$  and hence  $N = -1$ . Also, from  $G(s)H(s)$ , we get  $P = 1$ , substituting the values in

$$N = P - Z$$

we get,


$$-1 = 1 - Z$$

or

$$Z = 2$$

Which means two roots of characteristics equation lying on the right hand side of the  $s$ -plane. Therefore, the closed-loop system is unstable. The open-loop system is also unstable as  $P = 1$ .

#### Q.8 (c) Solution:

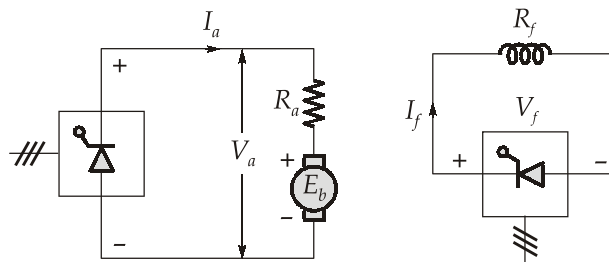

For continuous conduction, output voltage of three-phase full converter is given by,

$$V_0 = \frac{3V_{mL}}{\pi} \cos \alpha$$

For maximum possible field current  $\alpha = 0^\circ$

$$V_f = \frac{3 \times 230 \times \sqrt{2}}{\pi} = 310.61 \text{ V}$$

Field current,

$$I_f = \frac{V_f}{R_f} = \frac{310.61}{200} = 1.553 \text{ A}$$

(i) Rated shaft power  $P_{\text{shaft}} = 15000 \text{ W}$   
 $P_{\text{dev}} = P_{\text{shaft}} + P_{\text{rot}}$

$$P_{\text{dev}} = 15000 + 500$$

$$= 15500 \text{ W}$$

$$\text{Back emf } E_b = K I_f \omega$$

$$= 1.2 \times 1.553 \times \frac{2\pi \times 1200}{60} = 234.19 \text{ V}$$

$$\text{Rated developed power} = E_b I_a$$

$$\frac{15500}{234.19} = I_a$$

$$\text{Rated armature current} = 66.19 \text{ A}$$

Armature supply voltage,

$$V_a = E_b + I_a R_a$$

$$= 234.19 + 66.19 \times 0.25$$

$$V_a = 250.74 \text{ V}$$

$V_a$  is output voltage of three phase full converter

$$V_a = V_0$$

$$= \frac{3V_{mL}}{\pi} \cos \alpha$$

$$250.74 = \frac{3 \times 230\sqrt{2}}{\pi} \cos \alpha$$

$$\alpha = 36.17^\circ$$

(ii) For armature current of 10% of rated value

$$(I_a)_{\text{no load}} = 66.19 \times \frac{10}{100} = 6.619 \text{ A}$$

Delay angle is same as part (i) i.e.,

$$\alpha = 36.17^\circ$$

Back emf at no load,

$$(E_b)_{\text{no load}} = V_a - (I_a)_{\text{no-load}} R_a$$

$$(E_b)_{\text{no load}} = 250.74 - 6.619 \times 0.25$$

$$= 249.085 \text{ V}$$

No load speed can be calculated as,

$$E_b = K I_f \omega$$

$$(\omega)_{\text{no load}} = \frac{(E_b)_{\text{no-load}}}{K I_f}$$

$$\frac{2\pi(N)_{\text{no-load}}}{60} = \frac{(E_b)_{\text{no-load}}}{K I_f}$$

$$(N)_{\text{no load}} = \frac{60 \times (E_b)_{\text{no-load}}}{2\pi K I_f} = \frac{60 \times 249.085}{2\pi \times 1.2 \times 1.553}$$

$$\text{No load speed } (N)_{\text{no load}} = 1276.34 \text{ rpm}$$

$$\text{(iii) Speed regulation} = \frac{\text{No load speed} - \text{Full load speed}}{\text{Full load speed}}$$

$$= \frac{1276.34 - 1200}{1200}$$

$$\% \text{ speed regulation} = 6.362\%$$

