



**GATE
2025**

Electronics Engineering


Memory based
Questions & Solutions

Exam held on
15/02/2025 (Afternoon Session)



ANALOG CIRCUITS


Q.1 Consider the following circuit:

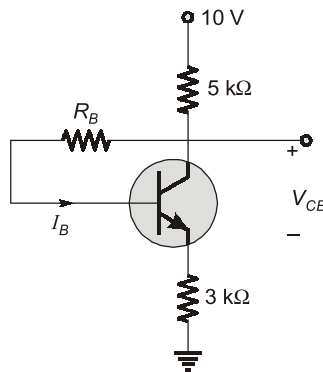

If $I_B = 10 \mu\text{A}$ and $\beta = 100$, then V_{CE} is _____.

Ans. (1.92)

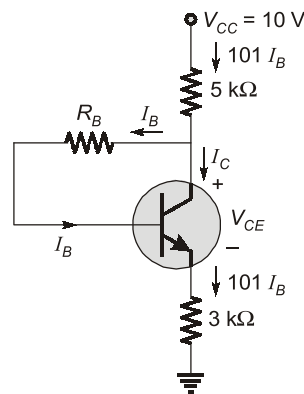Since, $I_C = \beta I_B = 100 I_B$; $I_E = 101 I_B$,




By KVL:

$$\begin{aligned} I_B &= 0.01 \text{ mA} \\ 10 &= 5 \times 101 I_B + V_{CE} + 3 \times 101 I_B \\ V_{CE} &= 10 - 808 \times 0.01 \\ V_{CE} &= 1.92 \text{ V} \end{aligned}$$

End of Solution

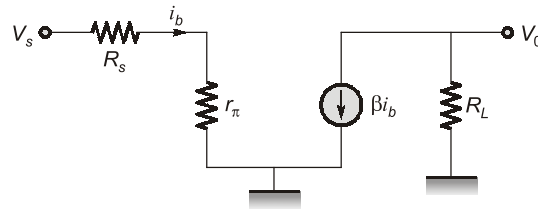Q.2 Calculate the value of $\frac{V_0}{V_s}$.




- (a) $\frac{\beta R_L}{R_s + r_\pi}$

(c) $\frac{\beta}{R_s + r_\pi}$

(b) $\frac{-\beta R_L}{R_s + r_\pi}$

(d) $\frac{-R_L}{R_s + r_\pi}$

Ans. (b)

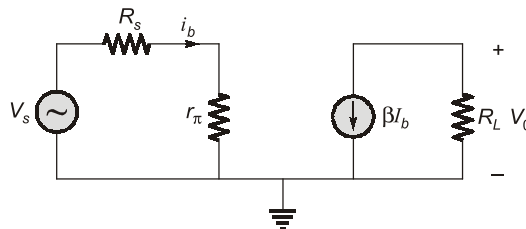


$$\frac{V_0}{V_s} = \frac{-\beta I_b \times R_L}{I_b(R_s + r_\pi)}$$

$$\frac{V_0}{V_s} = \frac{-\beta R_L}{R_s + r_\pi}$$

End of Solution

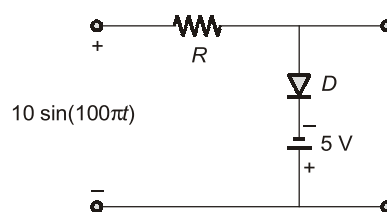Q.3 For the circuit of diode shown in figure below, the ON-time of the diode is _____ msec.



Ans. (13.33)

Given,

$$2\pi ft = 100\pi t$$

$$f = 50 \text{ Hz}$$

$$T_0 = \frac{1}{f} = 20 \text{ msec}$$

$$V_i = 10 \sin(100\pi t) = 10 \sin \alpha,$$

$$\alpha = 100\pi t$$

Diode conducts if $V_i > -5 \text{ V}$

Diode is OFF if $V_i < -5 \text{ V}$



ANNOUNCING

FOUNDATION COURSES for ESE 2026 & GATE 2026

The foundation batches are taught comprehensively which cover the requirements of all technical-syllabus based examinations.

- ✓ Classes by experienced & renowned faculties.
- ✓ Efficient teaching with comprehensive coverage.
- ✓ Comprehensive & updated study material.
- ✓ Similar teaching pedagogy in offline & online classes.
- ✓ Exam oriented learning ecosystem.
- ✓ Systematic subject sequence and timely completion.
- ✓ Concept practice through workbook solving.
- ✓ Regular performance assessment through class tests.

Commencement Dates :



Offline Batches at Delhi 18 Feb 2025

Teaching Hours

GATE Exclusive

- CE, ME : 950 to 1000 Hrs.
- EE : 800 to 850 Hrs.
- EC, IN, CS : 650-700 Hrs.

GATE + ESE

- CE, ME, EE, EC : 1200-1250 Hrs.



Live-Online Batches Evening : 18 Feb (All) Morning : 27 Feb (CE)

Teaching Hours

GATE Exclusive

- CE, ME, EE : 750 to 800 Hrs.
- EC, IN, CS : 650-700 Hrs.

GATE + ESE

- CE, ME, EE, EC :
1050 to 1100 Hrs.

More batches to be announced in Mar, Apr, May 2025

Note : Courses with SES (State Engineering Services) are also available.


Low Cost EMI Facility Available

Admissions Open

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Kolkata | Pune

www.madeeasy.in

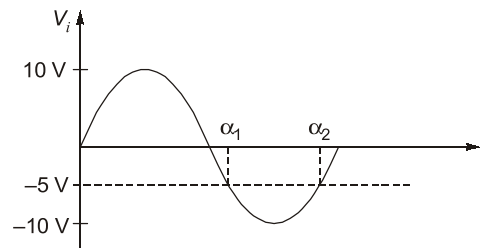

$$10 \sin \alpha = -5$$

$$\alpha = \sin^{-1}\left(\frac{-5}{10}\right)$$

$$\alpha = \frac{7\pi}{6}, \frac{11\pi}{6}$$

$$100\pi t_1 = \frac{7\pi}{6}$$

$$t_1 = 11.66 \text{ msec}$$

$$\alpha_2 = 100\pi t_2 = \frac{11\pi}{6}$$

$$t_2 = 18.33 \text{ msec}$$






Diode is OFF from t_1 to t_2

$$t_{\text{OFF}} = t_2 - t_1 = 6.66 \text{ msec}$$


$$t_{\text{ON}} = T_0 - T_{\text{OFF}} = 13.33 \text{ msec}$$

End of Solution

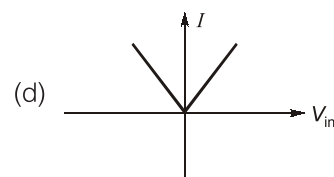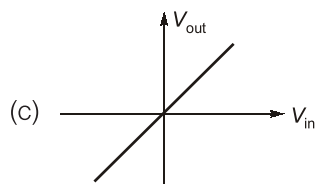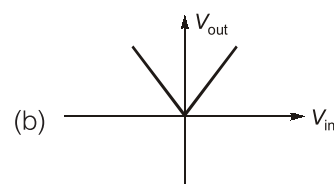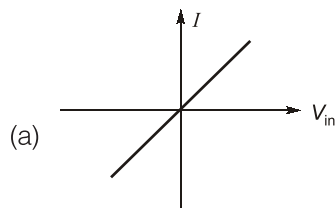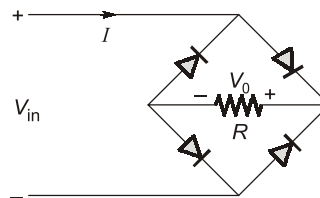Q.4 For the circuit show which of the following is correct?



Ans. (a, b)

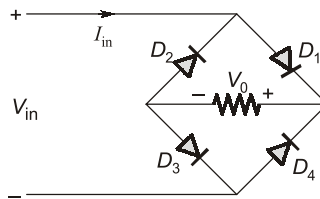


Given, V_{in} is steep of $-M$ to $+M$

For V_0 versus V_{IN} :

Let $V_{IN} = +M$

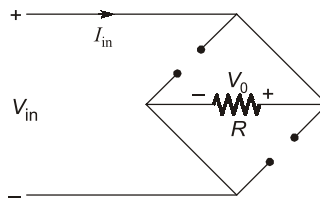In the bridge rectifier, D_1 and D_3 are forward bias, and D_2 and D_4 are reverse bias,




$$\therefore V_{in} - V_0 = 0 \Rightarrow V_{in} = V_0$$

$$\therefore \text{For } V_{in} = +M \Rightarrow V_0 = M$$

Let $V_{IN} = -M$


diodes, D_1 and D_3 are reverse bias,

D_2 and D_4 are forward bias.

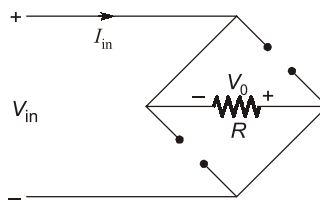


$$\therefore V_{in} + V_0 = 0$$

$$V_D = -V_{in} = -[-M] = M$$

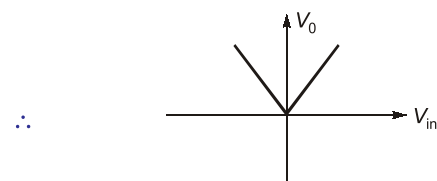

For I_{in} Versus V_{in} :

Let $V_{in} = +M$

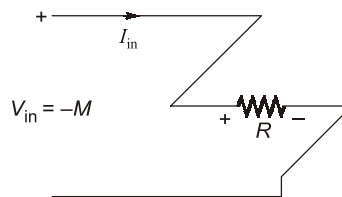

$$\therefore V_{in} - I_{IN} R = 0$$



Foundation Courses for

ESE 2026

GATE 2026



Tablet Course

- Pre-loaded full fledged recorded course
- Android OS based 10.5 inch Samsung tablet
- Internet access does not required
- Classes by senior faculties
- Validity: 2 Years
- Learn at your own pace
- Tablet is reusable for normal purpose after validity expires



Recorded Course

- Recorded Course
- Full fledged holistic preparation
- Classes by senior faculties
- Lectures can be watched anytime/ anywhere
- Courses are accessible on PC & Mac desktops/laptops/android/ iOS mobile devices.
- Learn at your own pace
- Validity: 1 year
- Internet connection required

Teaching Hours

- ✓ **GATE Exclusive** • CE, ME, EE : 800 to 900 Hrs.
• EC, IN, CS, CH : 650-700 Hrs.
- ✓ **GATE + ESE** • CE, ME, EE, EC : 1100 to 1200 Hrs.
- ✓ **GATE + SES-GS** • CE, ME, EE : 1150 to 1250 Hrs.
• EC, IN, CS, CH : 950-1050 Hrs.
- ✓ **GATE + ESE + SES-GS** • CE, ME, EE, EC : 1450 to 1550 Hrs.

Note : State Engineering Services Examination.

- The course is offered with a validity options of 1 year and 2 years.

Low Cost EMI Facility Available

Admissions open

For online courses, download the MADE EASY PRIME app now



Android



iOS

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Kolkata | Pune


www.madeeasyprime.com

$$\therefore \quad \text{if } V_{in} = M \Rightarrow I_{IN} = \frac{M}{R}$$

$$\text{Let } V_{in} = -M$$


$$\begin{aligned} \therefore \quad V_{in} - I_{NR} &= 0 \\ V_{in} &= I_{IN} R \\ -M &= I_{IN} R \end{aligned}$$
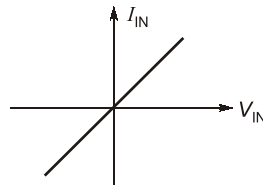
$$\therefore \quad I_{IN} = -\frac{M}{R}$$



End of Solution

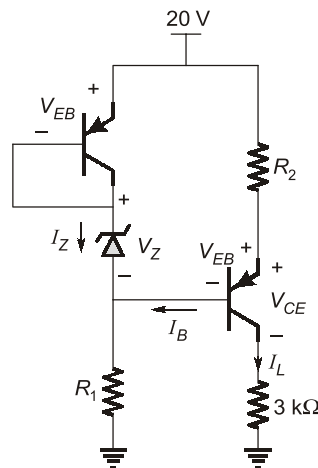Q.5 Find R_1 and R_2 . If $V_{BE1} = V_{BE2} = 0.7$ V, $\beta = 120$, $V_z = 5$ V, $I_z = 25$ mA, $I_L = 12$ mA.



Ans. (0.413)

$$I_{C2} = I_L = 12 \text{ mA}$$

$$I_{B2} = \frac{I_{C2}}{\beta} = \frac{12}{120} \text{ mA} = 0.1 \text{ mA}$$

$$\text{KCL:} \quad I_1 = I_z + I_{B2} = 25.1 \text{ mA}$$

$$\text{KVL:} \quad 20 = 0.7 + 5 + I_1 \times R_1$$

$$R_1 = 0.5697 \text{ k}\Omega \approx 0.6 \text{ k}\Omega$$


$$I_2 = I_{E2} = (1 + \beta) I_{B2} = 12.1 \text{ mA}$$

$$\text{KVL:} \quad 20 = I_2 R_2 + 0.7 + I_1 \times R_1$$

$$R_2 = \frac{20 - 0.7 - 14.3}{12.1} = 0.4 \text{ k}\Omega$$

End of Solution

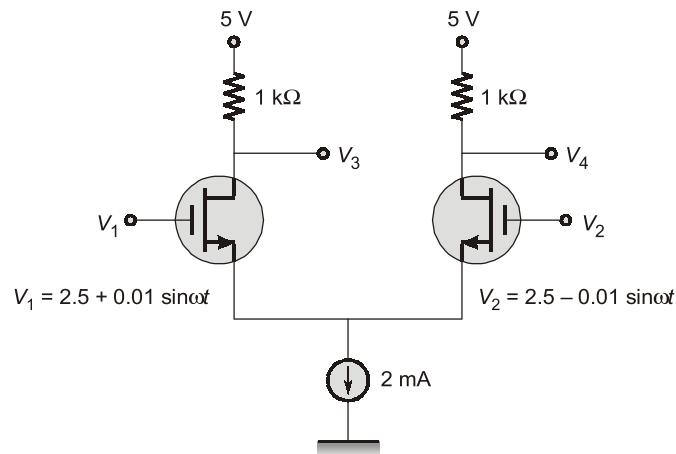Q.6 In the given differential amplifier output V_3 is equal to
(Given $g_m = 5 \text{ mS}$)



- (a) $4 - 0.01 \sin \omega t$ (b) $3 - 0.05 \sin \omega t$
(c) $2 - 0.01 \sin \omega t$ (d) $4 - 0.05 \sin \omega t$

Ans. (d)

$$I_{DS} = \frac{2}{2} = 1 \text{ mA}$$

$$\frac{V_d}{2} = 0.01 \sin \omega t$$

$$V_d = 0.02 \sin \omega t$$

$$V_{CM} = 2.5 \text{ V}$$

$$g_m = 5 \text{ ms}$$

$$A_{DM} = \frac{V_o}{V_d} = -\frac{g_m \times R_D}{2} = -\frac{5 \times 1}{2} = -2.5$$

$$V_o = -2.5 \times V_d = -2.5 \times 0.02 \sin \omega t$$

$$V_o = -0.05 \sin \omega t$$

AC voltage,

DC voltage,

In given circuit,

$$A_{CM} = 0$$

Hence, common mode input effect is cancelled.

$$V_o = -0.05 \sin \omega t + 4$$

End of Solution



Conventional Questions Practice Programme for ESE Mains 2025

Offline

Live-Online

Admissions Open



Batches
commencing
from
24 FEB 2025







Course includes
Mains Test Series (12 tests)

Commencing from **15 June 2025**

Note : Solo Mains Test Series is also available.

This course is offered in offline mode at Delhi Centre.

Key Features:

-  Classes by senior faculties
-  Comprehensive coverage
-  Discussion on important questions
-  Improvement of 'answer presentation'
-  Updated ESE Mains Workbooks
-  Mains Test Series is included

Duration: 300-350 Hrs | 80-90 days

Timing : 7 days/week | 4 hours/day

Streams: CE, ME, EE, E&T

Fee:

₹18,000 + GST
For Outsiders

₹14,000 + GST
For **MADE EASY Students**
(Foundation, RIB and Mains Course)

**Fee is same
for Offline & Live-online Batches**


• Test series is available at all MADE EASY Centres.

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Kolkata | Pune

 www.madeeasy.in

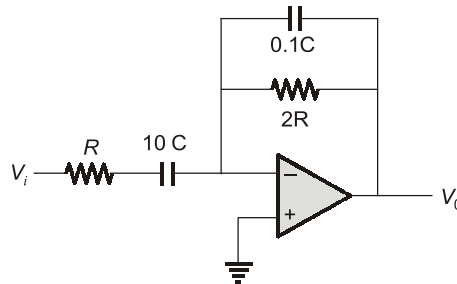Q.7 Find high frequency (f_H), if $f_L = 1$ MHz.



Ans. (50)

We know that,

$$f_L = \frac{1}{2\pi R_1 C_1}$$

$$10^6 = \frac{1}{2\pi \times R \times 10C}$$

$$\frac{1}{RC} = 2\pi \times 10^7$$

$$f_H = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi \times 2R \times 0.1C}$$

$$= \frac{1}{0.4\pi} \times \frac{1}{RC} = \frac{2\pi \times 10^7}{0.4\pi}$$

$$f_H = 5 \times 10^7 \text{ Hz} = 50 \text{ MHz}$$

End of Solution

Q.8 Identify correct statement regarding ideal op-amp.

- (a) Output impedance is infinite.
- (b) Input impedance is infinite.
- (c) Open loop common mode gain is infinity.
- (d) Open loop differential mode gain is infinite.

Ans. (b, d)

End of Solution

Q.9 Identify the correct statements.

- (a) Common source amplifiers have infinite input resistance.
- (b) Common gate amplifiers have infinite input resistance.
- (c) V_{in} and V_o of common drain amplifier are in-phase.
- (d) V_{in} and V_o of common source amplifier are in-phase.

Ans. (a, c)

End of Solution

COMMUNICATION SYSTEMS

Q.10 Maximum peak frequency deviation of a frequency modulated signal

$$S(t) = A_c \cos[\omega_c t + 3 \sin 2\pi f_1 t + 4 \sin 6\pi f_1 t]$$

is

- (a) f_1 (b) $12f_1$
(c) $15f_1$ (d) $2f_1$

Ans. (c)

$$S(t) = A_c \cos[\omega_c t + 3 \sin 2\pi f_1 t + 4 \sin 6\pi f_1 t]$$

Maximum frequency, $\Delta f = \left| \frac{1}{2\pi} \frac{d}{dt} \phi(t) \right|_{\max}$

$$S_{Fm}(t) = A_c \cos[\omega_c t + \phi(t)]$$

From comparison, $\phi(t) = 3 \sin 2\pi f_1 t + 4 \sin 6\pi f_1 t$

$$\Delta f = \left| \frac{1}{2\pi} [3 \times 2\pi f_1 \cos 2\pi f_1 t + 4 \times 6\pi f_1 \cos 6\pi f_1 t] \right|_{\max}$$

$$= |3f_1 \cos 2\pi f_1 t + 12f_1 \cos 6\pi f_1 t|_{\max}$$

$$= 3f_1 + 12f_1$$

$$= 15f_1$$

End of Solution

Q.11 Find minimum hamming distance d_{\min}

$$G = \begin{bmatrix} 100101 \\ 010011 \\ 001110 \end{bmatrix}$$

Ans. (3)

Minimum number of columns of G matrix that sum to zero equals to d_{\min}

For given 'G', sum of 3 columns equals to zero

i.e. sum of 1st, 2nd, 6th columns

(or) sum of 2nd, 3rd and 5th columns

(or) sum of 4th, 5th, 6th columns equal to zero.

So that d_{\min} equal to 3.

End of Solution



UPPSC-AE 2024 Exam

Live Online Program

Prelims Specific Course

Streams : • CE • ME • EE

Batches Going On | Admissions Open

Subjects that have already been taught will be made available in recorded-mode.

Features:

- 360-degree coverage of the UPPSC-AE 2024 Prelims Specific Course syllabus.
- Structured and effective curriculum aligns with the UPPSC-AE.
- Quality teaching with a clear and concise approach.
- Prelims-specific workbook with a wide range of practice question sets.
- Exam simulated Online test series for UPPSC AE Prelims exam.
- Dedicated doubt chat facility with faculty members.
- Live Classes + accessibility to watch recorded classes 2 times. Subjects that have already been taught will be made available in recorded-mode.
- Option to opt course "with book" or "without books".

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Kolkata | Pune

www.madeeasyprime.com

CONTROL SYSTEM

Q.12 Characteristics equation of a system is given by

$$s^5 + 7s^4 + 3s^3 - 33s^2 + 2s - 40 = 0$$

L is define as number of roots on negative real axis.

I is define as number of roots lie on imaginary axis.

R is define as number of roots lies on positive real axis.


then, which of the following option is correct?

- | | |
|---------------------------|---------------------------|
| (a) $P = 3, I = 2, R = 0$ | (b) $P = 2, I = 2, R = 1$ |
| (c) $P = 0, I = 2, R = 3$ | (d) $P = 1, I = 4, R = 0$ |

Ans. (b)

End of Solution

Q.13 Consider the system shown below:

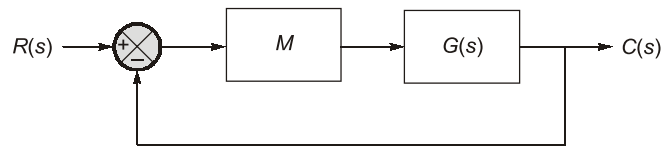

where $G(s) = \frac{10}{s^2}$


- (i) $R(s) = \frac{K_I}{s}$ then system will never be stable.
- (ii) $R(s) = (K_P + sK_D)$ then there is atleast one value of K_P and K_D where system become stable.

Which of the above statement(s) is/are true?

- | | |
|--------------------------------|---------------------------------|
| (a) (i) is true | (b) (ii) is true |
| (c) (i) and (ii) both are true | (d) (i) and (ii) both are false |

Ans. (c)

Given,

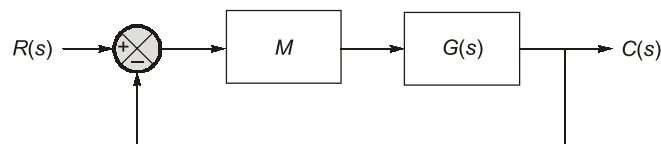

and $G(s) = \frac{1}{s^2}$

- (i) Given, $M = \frac{K}{s}$, then closed loop system,

$$\frac{C(s)}{R(s)} = \frac{M G(s)}{1 + M G(s)} = \frac{\frac{K}{s} \times \frac{1}{s^2}}{1 + \frac{K}{s} + \frac{1}{s^2}} = \frac{K}{s^3 + K}$$

∴ For all values of 'K', the closed loop system is unstable.

(ii) For controller, $M = K_P + K_D s$

Let, $M = 1 + s$


$$\therefore \frac{C(s)}{R(s)} = \frac{(1+s) \times \frac{1}{s^2}}{1 + \frac{s+1}{s^2}} = \frac{(s+1)}{s^2 + s + 1}$$

∴ Closed loop system is stable.


∴ Both statements are correct.

End of Solution

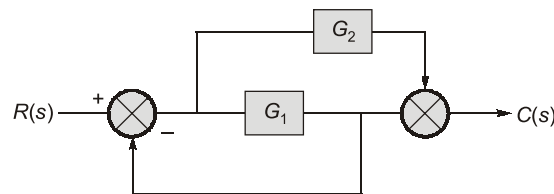Q.14 Consider the system having block diagram given as



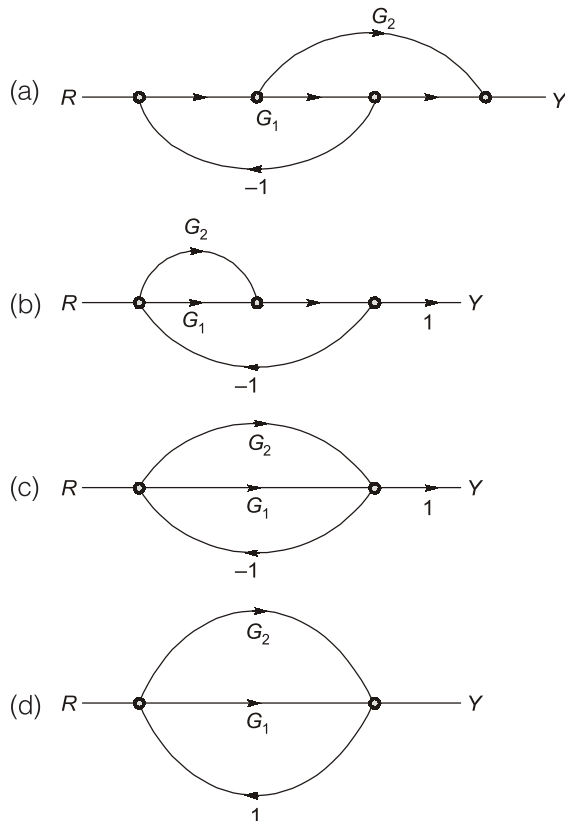The equivalent signal flow graph for the given block diagram is/are





UPPSC-AE 2024 EXAM Postal Package

On the latest UPPSC-AE syllabus & pattern

Only Prelims Package

• CE • ME • EE • AE
(Common for all)

Prelims + Mains Package

• CE • ME • EE
(Seperate)

Prelims Package : 13 Books (12 Printed + 1 E-book)

- 6 Volumes of Engg. Aptitude Books (covering 22 subjects) : Contain theory, solved examples and practice questions.
- 1 Practice Book of Engg. Aptitude containing solved practice Qs.
- 1 Book each containing theory, PYQs and practice questions of :
Geography | Indian Polity | Indian History | GK & Misc.
- 1 book of General Hindi containing theory, PYQs and practice Qs.
- E-copy of Current Affairs covering latest developments along-with practice questions.

Fee :
4,000/-

Prelims + Mains Package

- 6 Volumes of Engg. Aptitude Books (covering 22 subjects) : Contain theory, solved examples and practice questions.
- 1 Practice Book of Engg. Aptitude containing solved practice Qs.
- 1 Book each of : • Geography • Indian Polity • Indian History • GK & Miscellaneous; containing theory, PYQs and practice Qs.
- 1 Book of General Hindi containing theory, PYQs and practice Qs.
- E-copy of Current Affairs covering latest developments along-with practice questions.
- Technical Theory Books : Contain theory, solved examples and practice questions.
- 1 Practice Book of Technical Subjects : Contains 2000+ Questions with detailed solutions.
- 1 PYQ of Technical Papers : Contains subjectwise/yearwise step by step solutions.

Fee :
10,000/-

Address : 44-A/4, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

9021300500

www.madeeasypublications.org

Ans. (a)

From given block diagram,

$$\frac{C(s)}{R(s)} = \frac{G_1 + G_2}{1 - G_1}$$


and in options, from option (a),

$$\frac{Y(s)}{R(s)} = \frac{G_1 + G_2}{1 - G_1}$$

∴ Option (a) only satisfies.

End of Solution

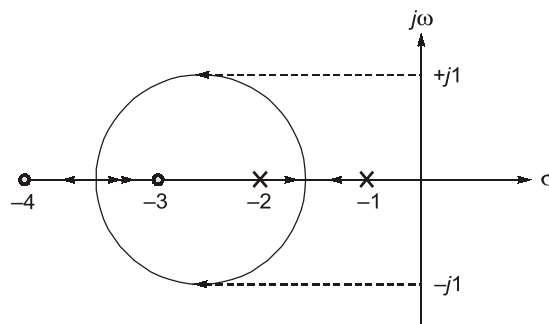Q.15 Consider an open loop system with root locus as shown below:



Then the value of 'K' for which $(-1 + j)$ lies on the root locus is _____.

Ans. (0.2)

From the given, Rootlocus plot,

Openloop transfer function,

$$G(s) = \frac{k(s+3)(s+4)}{(s+1)(s+2)}$$

Given, $(-1 + j)$ is on Rootlocus,

$$\therefore \left| \frac{k(s+3)(s+4)}{(s+1)(s+2)} \right| = 1$$

$$s = (-1 + j)$$

$$\left| \frac{k(3-1+j)(4-1+j)}{(2-1+j)} \right| = 1$$

$$\frac{k(\sqrt{4+1} \times \sqrt{9+1})}{\sqrt{1+1}} = 1$$

$$\therefore k = \frac{\sqrt{2}}{\sqrt{5} \times \sqrt{10}} = \sqrt{\frac{2}{50}} = \frac{1}{5}$$

End of Solution



POSTAL Packages

- **CSE**
- **ESE**
- **GATE**
- **UPPSC-AE**
- **SSC-JE**
- **RRB-JE**

Our Postal Book Packages cater to the needs of college-going students, working professionals, and individuals unable to join classroom courses. These books, offered by MADE EASY, are designed to be compact, comprehensive, and easily understandable. We have put our efforts to ensure error-free content, incorporating smart and shortcut techniques specifically tailored for solving numerical problems.

Revised and updated study materials

Helpline : 8860378004

Salient Features of Postal Study Package

- Complete syllabus coverage aligned with latest pattern/syllabus.
- Detailed theory and practice exercises.
- Latest and updated study material
- Step by step solutions
- Ample no. of practice questions with PYQs.
- Emphasis on technical and non technical sections both.
- Subject-wise theory objective and conventional practice sets.
- Proven track record of student success.

For online purchase, Visit :

www.madeeasypublications.org

For offline purchase, visit in-person at any MADE EASY center.
Books will be sent to your provided address.

Note 1 : Books are usually sent in two or more packages.


Note 2 : Current Affairs for ESE will be sent 1 month prior to the examination.

Address : 44-A/4, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

9021300500

www.madeeasypublications.org

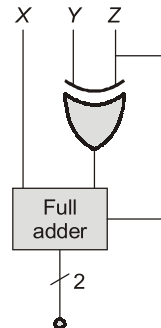Q.17 In the given circuit, if Z is connected as carry to the full adder if $Z = 1$, the below circuit with respect to inputs X, Y acts as




- (a) a subtractor
- (b) an adder
- (c) binary to grey code
- (d) multiplication

Ans. (a)

End of Solution

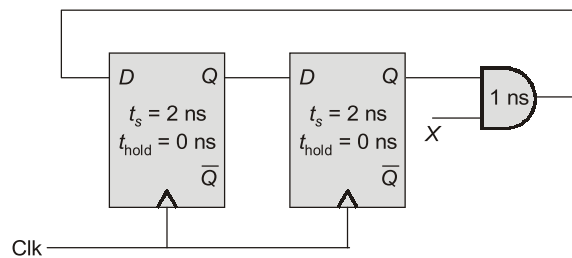Q.18 What is the maximum frequency for Clk in MHz if clock to Q delay of each flip-flop is 2 nsec.



Ans. (200)

Given,

$$\begin{aligned}
 t_{pd} &= 2n \text{ sec} \\
 t_{\text{setup}} (t_s) &= 2n \text{ sec} \\
 t_{\text{comb}} &= 1n \text{ sec} \\
 T_{\text{clkD1}} &= t_p + t_s + t_{\text{comb}} = 2 + 2 + 1 = 5n \text{ sec} \\
 T_{\text{clkD2}} &= t_s + t_p = 2 + 2 = 4n \text{ sec}
 \end{aligned}$$

\therefore Time required for clock,

$$\begin{aligned}
 T_{\text{clk}} &= \text{Max} \{T_{\text{clkD1}}, T_{\text{clkD2}}\} \\
 &= \text{Max} [5n\text{s}, 4 \text{ ns}] \\
 &= 5 \text{ ns}
 \end{aligned}$$

$$\text{Maximum frequency, } f_{\text{mx}} = \frac{1}{T_{\text{clk}}} = \frac{1}{5n\text{s}} = 200 \text{ MHz.}$$

End of Solution

ELECTROMAGNETICS

Q.19 In a transmission line whose characteristic impedance is ($Z_0 = 50 \Omega$) and is terminated with a load of $Z_L = (50 - j75)\Omega$. The average input power is $P_{in} = 10 \text{ mW}$, then the average power delivered to the load is _____mW.

Ans. (6.4)

$$Z_0 = 50 \Omega, \quad Z_L = 50 - j75 \Omega; \quad P_{in} = 10 \text{ mW}$$

$$\begin{aligned} \Gamma &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 - j75 - 50}{50 - j75 + 50} \\ &= \frac{-j75}{100 - j75} = \frac{-j3}{4 - j3} \end{aligned}$$

$$\Rightarrow |\Gamma| = \frac{3}{5} = 0.6$$

$$\begin{aligned} \therefore P_{del} &= \{1 - |\Gamma|^2\} P_i \\ &= [1 - (0.6)^2] * 10 \text{ mW} = 6.4 \text{ mW} \end{aligned}$$

End of Solution

ELECTRONIC DEVICES AND CIRCUITS

Q.20 Which of the following impurities can be called is n-type dopant?

- | | |
|-------------|----------------|
| (a) Gallium | (b) Phosphorus |
| (c) Boron | (d) Arsenic |

Ans. (b, d)

End of Solution

Q.21 $n_i = 2.5 \times 10^{16} \text{ m}^{-3}$; $\mu_n = 0.15 \text{ m}^2/\text{V-sec}$; $\mu_p = 0.05 \text{ m}^2/\text{V-sec}$
Find intrinsic resistivity in $\text{k}\Omega\text{-m}$.

Ans. (1.25)

$$\begin{aligned} \text{Intrinsic resistivity, } \rho_i &= \frac{1}{n_i q (\mu_p + \mu_n)} \\ &= \frac{1}{2.5 \times 10^{16} \times 1.6 \times 10^{-19} (0.15 + 0.05)} \\ &= \frac{1}{2.5 \times 10^{16} \times 1.6 \times 10^{-19} (0.2)} \\ \rho_i &= 1.25 \text{ k}\Omega\text{-m} \end{aligned}$$

End of Solution



Foundation Courses for **JE and AE Exams**

Mode: Live-Online

**Civil
Engineering**

**Mechanical
Engineering**

**Electrical
Engineering**

**Non-technical
Section**

These foundation batches are taught comprehensively which cover the requirements of technical and non-technical syllabus of Junior Engineer and Assistant Engineer level exams.

Duration of Foundation Course : 1 Year

Features



**Classes by
renowned faculties**



**Comprehensive
coverage of all subjects**



**Class PDF
notes**



**Doubt Sessions
on Telegram**



**Lectures will be
in Hinglish**



**1 Year Course
validity**



**Concept Practice
Book in PDF**



**Dedicated for all
AE and JE Exams**



**Technical and
Non- Technical**



**Monthly LIVE
Guidance Session**



**Get Physical books and
Study material (Optional)**



**700+ teaching
hours**



9021300500



www.madeeasyprime.com

Q.22 An electric field of 0.01 V/m is applied along the length of a copper wire of a circular cross-section with a diameter of 1 mm conductivity of copper is 5.8×10^7 s/m. Current flowing through wire is _____ A.

Ans. (0.45)

Given,

$$E = 0.01 \text{ V/m,}$$

$$\sigma = 5.8 \times 10^7 \text{ s/m}$$

\therefore

$$I = \sigma EA$$

$$= 5.8 \times 10^7 \times 0.01 \times \frac{\pi(10^{-3})^2}{4}$$

$$I = 0.45 \text{ A}$$

End of Solution

Q.23 In a semiconductor, mobility of electrons, $\mu_n = 0.38 \text{ m}^2/\text{V-sec}$ at temperature 300 K, then the diffusion coefficient of electrons at temperature 300 K is _____ $\text{cm}^2/\text{V-sec}$ (upto two decimal places)

Ans. (98.26)

Given, $\mu_n = 0.38 \text{ m}^2/\text{V-sec}$

$$D_n = \mu_n V_T$$

$$= 0.38 \times \frac{T}{11600}$$

$$= 0.38 \times \frac{300}{11600}$$

$$= 0.02586 \times 0.38$$

$$= 0.09826 \text{ m}^2/\text{sec}$$

$$D_n = 98.26 \text{ cm}^2/\text{sec}$$

End of Solution

ENGINEERING MATHEMATICS

Q.24 The condition for which rank of matrix should be at least 3 is/are :

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 \\ 0 & 6 & 7 & 8 \\ 0 & 0 & \alpha & \beta \\ 0 & 0 & 0 & \gamma \end{bmatrix}$$

(a) $\alpha = 0, \beta = \gamma \neq 0$

(b) $\alpha = \beta = \gamma = 0$

(c) $\beta = \gamma = 0, \alpha \neq 0$

(d) $\alpha = \beta = \gamma \neq 0$

Ans. (a, c, d)

End of Solution

Q.25 For the given function :

$$f(x) = 2x^3 - 3x^2 - 12x + 1$$

- (a) Local maxima at $x = 2$ (b) Local minima at $x = -1$
 (c) Global maxima does not exist (d) Global minima does not exist

Ans. (c, d)

$$f(x) = 2x^3 - 3x^2 - 12x + 1$$

$$f'(x) = 6x^2 - 6x - 12$$

$$f'(x) = 0$$

$$6x^2 - 6x - 12 = 0$$

$$6(x^2 - x - 2) = 0$$

$$6(x - 2)(x + 1) = 0$$

$$x = 2$$

$$x = -1$$

$$f''(x) = 12x - 6$$

$$f''(x)|_{x=2} = 12 \times 2 - 6$$

$$= 18 > 0$$


$$x = 2 \Rightarrow \text{local minima}$$

$$f''(x)|_{x=-1} = 12 \times -1 - 6$$

$$= -12 - 6$$

$$= -18 < 0$$
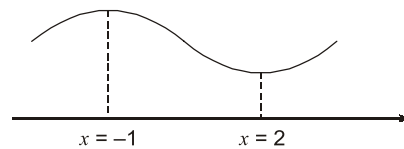
$$x = -1 \Rightarrow \text{local maxima}$$



So function has neither global maxima nor global minima.

End of Solution

**ESE 2025
Prelims**

**Offline
Test Series**



Commencing from
9 Mar 2025

Total 22 Tests

Paper-I : 11 Tests
GS & Engineering Aptitude

- 8 Multiple Subject Tests of 50 Questions (**400 Ques**)
Time : 60 minutes
- +
- 1 Full Syllabus Test of 100 Questions (**300 Ques**)
Time : 120 minutes
- +
- **2 Anubhav Tests**
Full Syllabus

Paper-II : 11 Tests
Engineering Discipline

- 8 Multiple Subject Tests of 75 Questions (**600 Ques**)
Time : 90 minutes
- +
- 1 Full Syllabus Test of 150 Questions (**450 Ques**)
Time : 180 minutes
- +
- **2 Anubhav Tests**
Full Syllabus

Each question carries 2 marks

Negative marking = 2/3 marks



**Latest
Pattern**

Tests are designed as per latest syllabus, trend and pattern of ESE. Paper-I (GS and Engineering aptitude) and Paper-II (Technical) both are covered.



**Care for
Accuracy**

All care has been taken to ensure the highest level of accuracy.



**Cyclic
Revision**

Dynamic test series for cyclic revision of subjects. Tests are time tabled with "New Topics" and "Repeat Topics" to maintain the continuity and a perfect balance between tech and non tech subjects.



**Quality
Questions**

Quality Questions framed by experienced research and development team of MADE EASY.



**Illustrated
Solutions**

Well explained, step-by-step illustrated solutions for easy understanding of aspirants..



**All India
Rank**

Opportunity to evaluate yourself on All India Basis. Compare your performance with quality students of MADE EASY.

**Fee
Structure**

₹ 3,000 + GST

Non-MADE EASY
students

₹ 2,000 + GST

Ex. MADE EASY Students
Enrolled in Postal or any long term/
short term classroom course

₹ 1,000 + GST

If student opts
this test in
live-online mode

Nil

For Current Session
Students Enrolled in
ESE + GATE 2025 Batches.



Scan to Enroll

Note: Anubhav Tests are part of the ESE Offline Prelims 2025 test series.

For outside students Anubhav Tests are free of cost. It will be conducted at all our MADE EASY and NEXT IAS centres across India.

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Kolkata | Pune

Enroll www.madeeasy.in

Q.26 Two fair dice are rolled and random variable X denotes the sum of out comes then expected value of $X = ?$

Ans. (7)

Sum of two dice = $\{2, 3, 4, 5, \dots, 12\}$

x	2	3	4	5	6	7	8	9	10	11	12
$P(x)$	$\frac{1}{36}$	$\frac{2}{36}$	$\frac{3}{36}$	$\frac{4}{36}$	$\frac{5}{36}$	$\frac{6}{36}$	$\frac{5}{36}$	$\frac{4}{36}$	$\frac{3}{36}$	$\frac{2}{36}$	$\frac{1}{36}$

$$\begin{aligned}
 E(X) &= \sum x \cdot P(x) \\
 &= 2 \times \frac{1}{36} + 3 \times \frac{2}{36} + 4 \times \frac{3}{36} + 5 \times \frac{4}{36} + 6 \times \frac{5}{36} + 7 \times \frac{6}{36} \\
 &\quad + 8 \times \frac{5}{36} + 9 \times \frac{4}{36} + 10 \times \frac{3}{36} + 11 \times \frac{2}{36} + 12 \times \frac{1}{36} \\
 &= \frac{252}{36} = 7
 \end{aligned}$$

End of Solution

Q.27 Contour integral evaluated over counter clockwise on the unit circle 'c' in the complex plane, then choose the correct one?

- (a) $\oint_c \cos z \, dz = 0$

(c) $\oint_c \sec z \, dz \neq 0$

(b) $\oint_c z^n \, dz = 0, n = \text{even positive integer}$

(d) $\oint_c e^z \, dz = 0$

Ans. (b, d)

End of Solution

Q.28 For $a = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$ and $b = \begin{bmatrix} 0 \\ 3\sqrt{2} \end{bmatrix}$ the value of $\min_x \|ax - b\|$ is _____.

Ans. (3)

$$\begin{aligned}
 ax - b &= \begin{bmatrix} x \\ x - 3\sqrt{2} \end{bmatrix} \\
 \left\| \begin{bmatrix} x \\ x - 3\sqrt{2} \end{bmatrix} \right\| &= f(x) = \text{norm} \\
 f(x) &= \sqrt{x^2 + (x - 3\sqrt{2})^2} \\
 &= \sqrt{x^2 + x^2 + 18 - 6\sqrt{2}x} \\
 f(x) &= \sqrt{\frac{2x^2 - 6\sqrt{2}x + 18}{g(x)}}
 \end{aligned}$$

$$g(x) = 2x^2 - 6\sqrt{2}x + 18$$

$$g'(x) = 4x - 6\sqrt{2} = 0$$

$$x = \frac{6\sqrt{2}}{4} = \frac{3\sqrt{2}}{2} = \frac{3}{\sqrt{2}}$$

$$\text{Point of minima} = \frac{3}{\sqrt{2}}$$

$$\begin{aligned} f(x)\bigg|_{x=\frac{3}{\sqrt{2}}} &= \sqrt{2\left(\frac{3}{\sqrt{2}}\right)^2 - 6\sqrt{2} \times \frac{3}{\sqrt{2}} + 18} \\ &= \sqrt{9 - 18 + 18} \\ &= 3 \end{aligned}$$

End of Solution

Q.29 If $t^2 y''(t) - 2ty'(t) + 2y(t) = 0$, $y(0) = 1$, $y'(1) = -1$, then maximum value of $y(t)$ over $[0, 1]$ is

- (a) 0.1 (b) 0.5
(c) 0.75 (d) 0.25

Ans. (d)

Cauchy's Euler differential equation,

$$x = e^t$$

$$t = e^u$$

$$\ln t = u$$

$$t^2 y''(t) - 2ty'(t) + 2y(t) = 0$$

$$D(D-1)y - 2Dy + 2y = 0$$

$$(D^2 - D - 2D + 2)y = 0$$

$$(D^2 - 3D + 2)y = 0$$

A.E.

$$m^2 - 3m + 2 = 0$$

$$m = 1, 2$$

$$y = C_1 e^u + C_2 e^{2u}$$

$$y = C_1 t + C_2 t^2$$

$$\frac{dy}{dt} = C_1 + C_2 \times 2t$$

at $t = 0$, $\frac{dy}{dt} = 1$

$\Rightarrow C_1 = 1$

at $t = 1$, $\frac{dy}{dt} = -1$

$$-1 = 1 + C_2 \times 2 \times 1$$

$$-1 = 1 + 2C_2$$

$$-2 = 2C_2$$

$$C_2 = -1$$

$$y = C_1 t + C_2 t^2$$

$$y = t - t^2$$

$$\frac{dy}{dt} = 1 - 2t = 0$$


$$t = \frac{1}{2}$$

$$\frac{d^2y}{dt^2} = -2 < 0$$

$$t = \frac{1}{2} \Rightarrow \text{maxima point}$$

$$y\left(\frac{1}{2}\right) = \frac{1}{2} - \left(\frac{1}{2}\right)^2$$
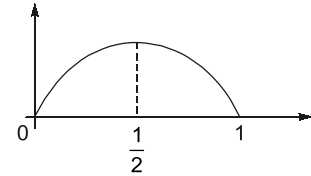
$$= \frac{1}{2} - \frac{1}{4} = \frac{1}{4}$$



End of Solution

GENERAL ENGLISH

- Q.30** Had I been active as a child, I _____ a famous actor.
- (a) can be (b) could have been
(c) will be (d) might be

Ans. (b)

End of Solution

- Q.31** Abuse : Insult : Ridicule : : _____ : Praise : Appreciate
- (a) Honour (b) Extol
(c) Appropriate (d) Prize

Ans. (b)

End of Solution



UPPSC-AE
2024 Preliminary
Examination

**Online
Test Series**

Commencing from
20th FEB'25

Total 10 Tests (Total 1125 Questions)

5 Part Syllabus Tests + 5 Full Syllabus Tests

Paper Pattern:

- Each question carries 2 Marks
- There is a penalty of 0.66 Mark for every wrong answer.

Test Series Features:

- Quality questions as per UPPSC-AE standard and pattern.
- Step by step detailed solutions for tough questions.
- Detailed performance analysis report.

Stream : CE, ME, EE

Test Series Schedule

Test No.	Activate Date	Total Questions	Total Time	Test Type	Syllabus Covered
1	20 th Feb 2025	75 Qs	1 Hour	Part Syllabus Test	General Principles of Design and Drawing, Industrial Safety and Safety Standards, Engineering Materials, Quality Control, Types of Machinery and Maintenance, Production and Construction, Handling and Storage of Products
2	27 th Feb 2025	75 Qs	1 Hour	Part Syllabus Test	Basics of project Management, Information and communication technologies, Ethics and values in engineering profession, intellectual property rights, Role of science and technology in daily life, recent developments in applied sciences, basics of artificial intelligence and robotics
3	6 th Mar 2025	75 Qs	1 Hour	Part Syllabus Test	Green Energy, Energy conversion principles, Climate change, Disaster Management, Basics of thermodynamics, Water resources and conservation processes, Basics of measurement and instrumentation, Human health and sanitation
4	13 th Mar 2025	75 Qs	1 Hour	Part Syllabus Test	General Hindi
5	20 th Mar 2025	75 Qs	1 Hour	Part Syllabus Test	Indian History, Indian Polity, Geography, GK & Miscellaneous and Current Affairs
6	27 th Mar 2025	150 Qs	2 Hours	Full Syllabus Test	Full Syllabus Test (100 Qs. Engineering Aptitude + 25 Hindi + 25 General Studies)
7	3 rd Apr 2025	150 Qs	2 Hours	Full Syllabus Test	Full Syllabus Test (100 Qs. Engineering Aptitude + 25 Hindi + 25 General Studies)
8	5 th Apr 2025	150 Qs	2 Hours	Full Syllabus Test	Full Syllabus Test (100 Qs. Engineering Aptitude + 25 Hindi + 25 General Studies)
9	8 th Apr 2025	150 Qs	2 Hours	Full Syllabus Test	Full Syllabus Test (100 Qs. Engineering Aptitude + 25 Hindi + 25 General Studies)
10	11 th Apr 2025	150 Qs	2 Hours	Full Syllabus Test	Full Syllabus Test (100 Qs. Engineering Aptitude + 25 Hindi + 25 General Studies)

Fee: ₹1000/-
For Non-MADE EASY
Students

₹500/-
For MADE EASY GATE & ESE
Batch Students (Old/Current)

₹500/-
For MADE EASY AE/JE
Batch Students (Old/Current)

Nil
For UPPSC-AE
Batch Students




www.madeeasy.in

| 9021300500

Click to Enroll

NETWORK THEORY

Q.32 Consider the following circuit.

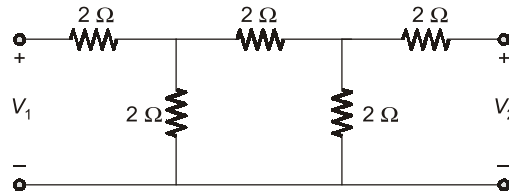

The Z parameter of the circuit is


(a) $\begin{bmatrix} \frac{10}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{10}{3} \end{bmatrix}$

(b) $\begin{bmatrix} \frac{10}{3} & \frac{1}{3} \\ \frac{1}{3} & \frac{10}{3} \end{bmatrix}$

(c) $\begin{bmatrix} \frac{10}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{2}{3} \end{bmatrix}$

(d) $\begin{bmatrix} \frac{2}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{2}{3} \end{bmatrix}$


Ans. (a)

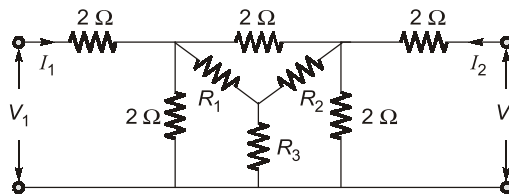

$$R_1 = \frac{2 \times 2}{2 + 2 + 2} = \frac{2}{3} \Omega$$

$$R_1 = \frac{2}{3} \Omega$$

$$R_3 = \frac{2}{3} \Omega$$

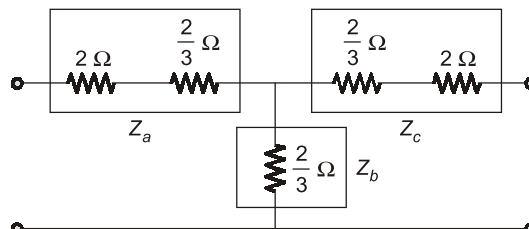


$$Z_{11} = Z_a + Z_b = \frac{10}{3} \Omega$$

$$Z_{22} = Z_b + Z_c = \frac{10}{3} \Omega$$

$$Z_{12} = Z_{21} + Z_b = \frac{2}{3} \Omega$$


End of Solution

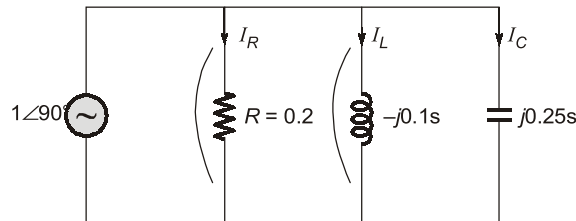Q.33 Find the value of I_R , I_L and I_C ?



- (a) $I_C = 0.25\angle 180^\circ$, $I_L = 0.1\angle 0^\circ$, $I_R = 0.2\angle 90^\circ$
 (b) $I_C = 0.2\angle 180^\circ$, $I_L = 0.1\angle 0^\circ$, $I_R = 0.25\angle 90^\circ$
 (c) $I_C = 0.25\angle 180^\circ$, $I_L = 0.5\angle 0^\circ$, $I_R = 0.5\angle 90^\circ$
 (d) $I_C = 0.5\angle 180^\circ$, $I_L = 0.25\angle 0^\circ$, $I_R = 0.2\angle 90^\circ$

Ans. (a)

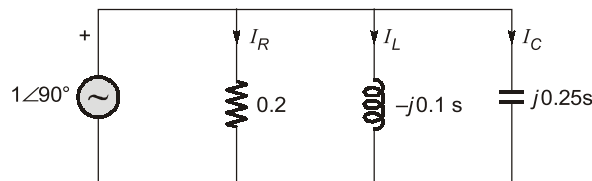


$$I_R = 1\angle 90^\circ (0.2) = 0.2\angle 90^\circ$$

$$I_L = 1\angle 90^\circ (0.1\angle -90^\circ) = 0.1\angle 0^\circ$$

$$I_C = 1\angle 90^\circ (0.25\angle 90^\circ) = 0.25\angle 180^\circ$$

End of Solution

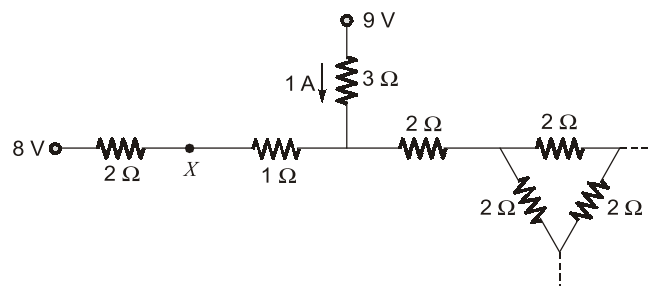
Q.34 Consider the given part of a circuit given below:



The voltage at node X is _____.

- (a) $\frac{20}{3}$ (b) $\frac{10}{3}$
 (c) $\frac{3}{20}$ (d) $\frac{2}{3}$

Ans. (a)

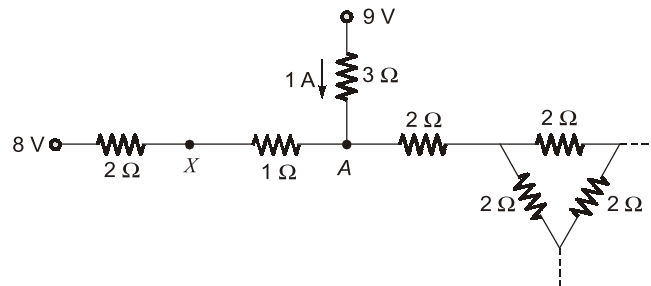


Voltage at node A is $= 9 - (3 \times 1) = 6 \text{ V}$

$$I_D = \frac{8-6}{2+1} = \frac{2}{3} \text{ A}$$

$$V_x = 8 - \left(2 \times \frac{2}{3} \right) = \frac{20}{3} \text{ V}$$


End of Solution

Q.35 Consider the circuit shown below,

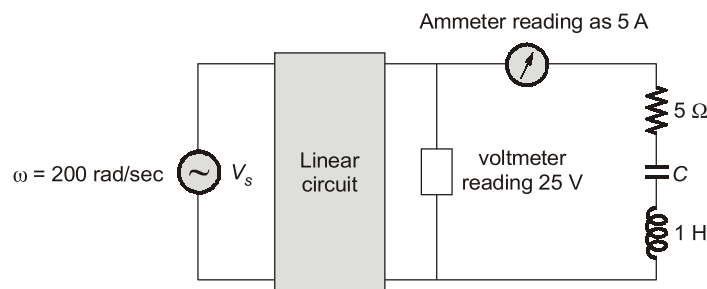

Then the value of capacitor 'C' is _____ μF .

Ans. (25)

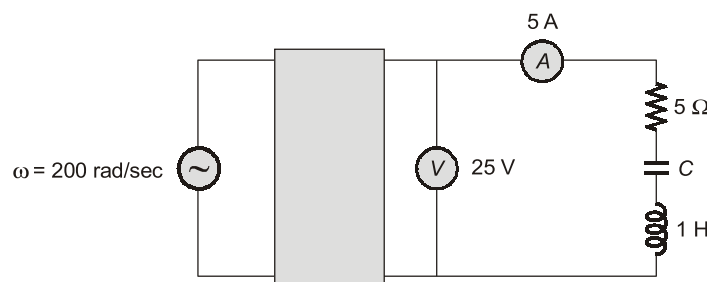

$$X_L = \omega L = 200 \times 1 = 200 \Omega$$

$$Z = \frac{V}{I} = \frac{25}{5} = 5 \Omega$$

$$Z = R + j(X_L - X_C)$$

$$X_L = X_C$$

$$X_L = X_C = 200 \Omega$$

$$\frac{1}{\omega C} = 200$$

RRB-JE

CBT-2 | 2024 Exam

Online Test Series



Launching

10 Full Syllabus Tests (Total 1500 Questions)

Commencing from **11th FEB 2025** | Stream : **CE, ME, EE, EC**

Paper Pattern:

- ➔ Each question carries 1 Mark.
- ➔ There will be a negative marking of 1/3rd Mark for every wrong answer.

Test Series Features:

- ➔ Questions crafted to align with the RRB-JE syllabus and exam format.
- ➔ Comprehensive, step-by-step solutions for tough questions.
- ➔ Detailed performance analysis report to track your progress.

RRB JE CBT 2 Exam Pattern 2024	Subject	No. of Questions	Marks	Duration
	General Awareness	15	15	120 Mins
	Physics & Chemistry	15	15	
	Basics of Computers and Applications	10	10	
	Basics of Environment and Pollution Control	10	10	
	Technical Abilities (CE/ME/EE/EC)	100	100	
	Total	150	150	

Test Series Schedule	Test No.	Activate Date	Total Marks	Total Questions	Total Time
	1	11 th Feb 2025	150 Marks	150 Qs	2 Hours
	2	14 th Feb 2025	150 Marks	150 Qs	2 Hours
	3	18 th Feb 2025	150 Marks	150 Qs	2 Hours
	4	21 st Feb 2025	150 Marks	150 Qs	2 Hours
	5	25 th Feb 2025	150 Marks	150 Qs	2 Hours
	6	28 th Feb 2025	150 Marks	150 Qs	2 Hours
	7	4 th Mar 2025	150 Marks	150 Qs	2 Hours
	8	7 th Mar 2025	150 Marks	150 Qs	2 Hours
	9	11 th Mar 2025	150 Marks	150 Qs	2 Hours
	10	14 th Mar 2025	150 Marks	150 Qs	2 Hours

Fee: ₹500/-



www.madeeasy.in

9021300500

Click to Enroll

$$\frac{1}{200 \times C} = 200$$

$$C = \frac{1}{200 \times 200} = 25 \mu\text{F}$$

End of Solution

REASONING AND APTITUDE

Q.36 A pot has 4 balls, 2 red and 2 blue. Probability that 2 balls are drawn randomly without replacement which are of different colour?

- (a) $\frac{2}{3}$ (b) $\frac{1}{3}$
(c) $\frac{1}{2}$ (d) None of the above

Ans. (a)

4 → Total balls

2 → Red balls





2 → Blue balls

Probability that 2 balls drawn randomly which are of different colour is,

$$P = \frac{{}^2C_1 \times {}^2C_1}{{}^4C_2} = \frac{4}{6} = \frac{2}{3} \quad [\because \text{without replacement}]$$

End of Solution

Q.37 Which of the following is the correct representation for the function $f(x) = \frac{-|x|}{x}$?

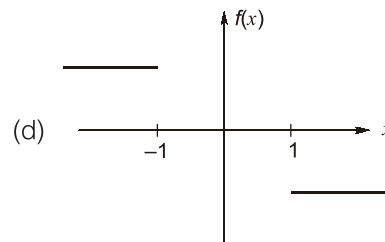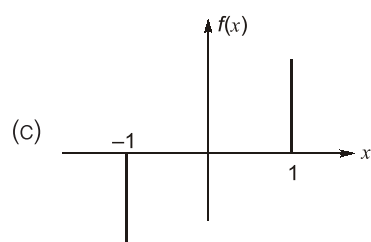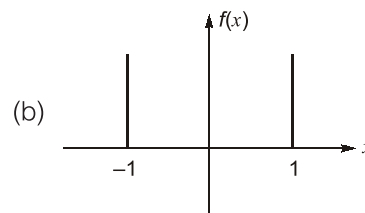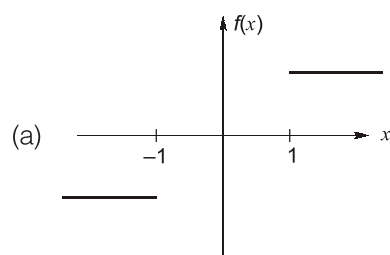

Ans. (d)

Given, $f(x) = -\frac{|x|}{x}$

We know, $|x| = \begin{cases} x; & x \geq 0 \\ -x; & x < 0 \end{cases}$

$$f(1) = \frac{-1}{1} = -1$$


$$f(2) = \frac{-2}{2} = -1$$

$$f(-1) = \frac{-1}{-1} = 1$$

$$f(-2) = \frac{-2}{-2} = 1$$


\therefore If $x > 0$; $f(x) = -\frac{x}{x} = -1$

If $x < 0$; $f(x) = -\frac{(-x)}{x} = 1$

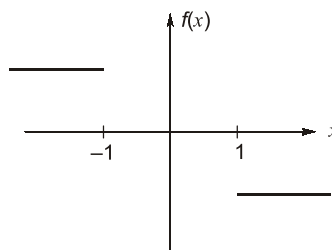

End of Solution

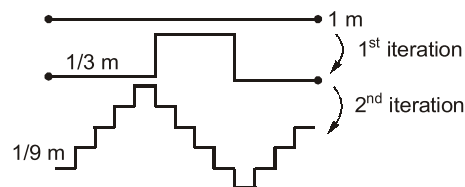Q.38 Consider the following iterations for which the length of the wire as given:



After n^{th} iteration, the length of the wire is


(a) $\left(\frac{1}{3}\right)^n$

(b) $\left(\frac{1}{9}\right)^n$

(c) $\left(\frac{5}{3}\right)^n$

(d) $\left(\frac{5}{3}\right)^{2n}$

Ans. (c)

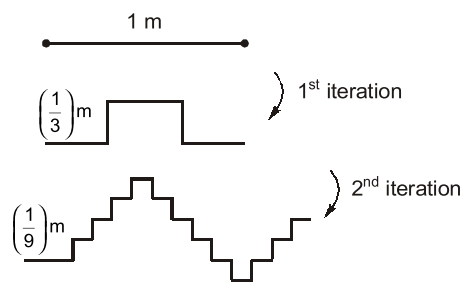

Iteration	Length
0 →	1
1 →	$\left(\frac{1}{3}\right) \times 5$
2 →	$\left(\frac{1}{9}\right) \times 25$
n^{th} →	$\left(\frac{1}{3}\right)^n \times (5)^n = \left(\frac{5}{3}\right)^n$

End of Solution

Q.39 A company charges consultation fee if its 5,00,000 then overhead is 20% of it. If consultation fee is greater than 5,00,000 then overhead is 10% of the difference by which consultation fee is greater than 5,00,000 plus 1,00,000 and a tax of 18% is charged on total of consultation fee + overhead from client. If client can pay only 10,00,000 then maximum consultation fee an employee can pay is

Ans. (725000)

Let, consultation fee = X

Case (i): If $X \leq 500000$

$$\text{Overhead} = 20\% \text{ of } X = 0.2X$$

$$\text{Total cost} = X + 0.2X = 1.2X$$

$$\text{Tax} = 18\% \text{ of } 1.2X = \left(\frac{18}{100}\right) 1.2X = 0.216X$$

$$\text{Total amount paid by client} = 1.2X + 0.216X = 1.416X$$

Given that, the client can only pay 1000000

$$\Rightarrow 1.416X = 1000000$$

$$\Rightarrow X \approx 706215$$

Case (ii): If $X > 500000$

$$\text{Overhead} = 100000 + 10\% [X - 500000]$$

$$= 100000 + 0.1 [X - 500000]$$

$$\text{Total cost} = X + 100000 + 0.1 [X - 500000]$$

$$= 1.1X + 50000$$

$$\text{Tax} = \frac{18}{100} (1.1X + 50000) = 0.198X + 9000$$

$$\begin{aligned} \text{Total amount paid by client} &= 1.1X + 50000 + 0.198X + 9000 \\ &= 1.298X + 59000 \end{aligned}$$

Given that, the client can only pay 1000000


$$\Rightarrow 1.298X + 59000 = 1000000$$

$$\Rightarrow X \approx 725000$$

\therefore Maximum consultation fee that the client can afford = 725000


End of Solution

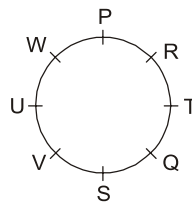- Q.40** In dance chair game, after first round behind P, 4th person left.
 After 2nd round behind Q, 3rd person is left.
 After 3rd round behind V, 3rd person is left.
 After 4th round behind U, 4th person is left.
 Then at the end of the 4th round who will left in the game?



- (a) P, T, Q, U (b) P, T, S, U
 (c) P, W, Q, S (d) W, T, Q, V

Ans. (a)

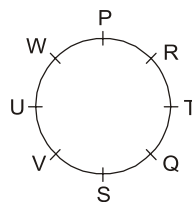

After 1st round – Behind P, 4th person left
 \Rightarrow S eliminated
 Remaining players: P, R, T, Q, V, U, W
 After 2nd round – Behind Q, 3rd person left
 \Rightarrow W eliminated
 Remaining players: P, R, T, Q, V, U
 After 3rd round – Behind V, 3rd person left
 \Rightarrow R eliminated
 Remaining players: P, T, Q, V, U
 After 4th round – Behind U, 4th person left
 \Rightarrow V eliminated
 \therefore Remaining players: P, T, Q, U

End of Solution

Check Your Expected Rank & GATE Score

by

MADE EASY
Rank Predictor

Once GATE releases the Response Sheet.

The link will be live
on the homepage of **www.madeeasy.in**
on the day of the response sheet release.

Q.41 The music has notes C, D, #D, E, #E, F #F, G, #G, H. The note "C" has frequency 1.038 Hz. Each frequency note has frequency $\sqrt[12]{2}$ times the previous note. The ratio of frequencies of #F to C is _____.

- (a) $\sqrt[3]{2}$ (b) $\sqrt{2}$
(c) 1 (d) $\sqrt[6]{2}$

Ans. (b)

Given, Common ratio = $\sqrt[12]{2} = (2)^{1/12}$

#F \rightarrow 7th term

C \rightarrow 1st term

$$\Rightarrow \frac{7^{\text{th}} \text{ term}}{1^{\text{st}} \text{ term}} = \frac{1.038 \times [(2)^{1/12}]^6}{1.038} = (2)^{1/2} = \sqrt{2}$$

End of Solution

SIGNALS AND SYSTEMS

Q.42 If $f(t)$ has Fourier series coefficient C_k and $y(t)$ has Fourier series coefficient d_k , then which of the following is/are true for $y(t) = f(\alpha t)$?

where,

$$f(t) = \sum_{n=-\infty}^{\infty} C_k e^{-jn\frac{2\pi}{T_0}t}$$

$$y(t) = \sum_{n=-\infty}^{\infty} d_k \cdot e^{-jn\frac{2\pi}{T_0}\alpha t}$$

- (a) $C_k = d_k \forall K$
(b) $C_k = \alpha d_k$
(c) If time period of $f(t)$ is T_o , then time period of $f(\alpha T) = \frac{T_o}{\alpha}$
(d) If time period of $f(t)$ is T_o , then time period of $f(\alpha T) = \alpha T_o$

Ans. (a, c)

$$f(t) = \sum_{n=-\infty}^{\infty} C_k e^{-jn\frac{2\pi}{T_0}t}$$

Put $t = \alpha t$:

$$f(\alpha t) = \sum_{n=-\infty}^{\infty} C_k e^{-jn\frac{2\pi}{T_0}(\alpha t)}$$

$$\Rightarrow y(t) = \sum_{n=-\infty}^{\infty} C_k e^{-jn \left(\frac{T_0}{\alpha} \right) t}$$

$$y(t) = \sum_{n=-\infty}^{\infty} d_k e^{-jn \frac{2\pi}{T_0} t}$$

$$= \sum_{n=-\infty}^{\infty} d_k \cdot e^{-jn \omega_0' t}$$

For $y(t)$: $d_k = C_k$, $\omega_0' = \alpha \omega_0$ or $T_0' = \frac{T_0}{\alpha}$

where $T_0' =$ Fundamental period of $y(t)$

$\omega_0' =$ Fundamental frequency of $y(t)$

End of Solution

Q.43 Consider the following statements:

- (a) The ROC of $\delta[n]$ contains entire z-plane.
- (b) DTFT exists for all the signals for which z-transform exists.
- (c) DTFT of a signal exists only if ROC of a signal contains unit circle.
- (d) The ROC of signal may include both poles and zeros.

Which of the above statements are true for a discrete time signal?

Ans. (a, c)

End of Solution

■■■■