



**MADE EASY**

Leading Institute for ESE, GATE & PSUs

Detailed Solutions

**ESE-2025  
Mains Test Series**


**Electrical Engineering  
Test No : 1**

**Section A : Electric Circuits**

**Q.1 (a) Solution:**

The above network can be considered as a series connection of two networks,  $N_1$  and  $N_2$ .

For the network  $N_1$

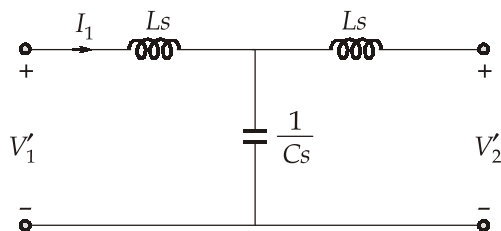

Applying KVL to mesh 1,

$$V_1' = \left( Ls + \frac{1}{Cs} \right) I_1 + \left( \frac{1}{Cs} \right) I_2 \quad \dots(i)$$

Applying KVL to mesh 2,


$$V_2' = \left( \frac{1}{Cs} \right) I_1 + \left( Ls + \frac{1}{Cs} \right) I_2 \quad \dots(ii)$$

Comparing equations (i) and (ii) with Z-parameters equation,

We get,

$$\begin{bmatrix} Z_{11}' & Z_{12}' \\ Z_{21}' & Z_{22}' \end{bmatrix} = \begin{bmatrix} Ls + \frac{1}{Cs} & \frac{1}{Cs} \\ \frac{1}{Cs} & Ls + \frac{1}{Cs} \end{bmatrix}$$

For the network  $N_2$

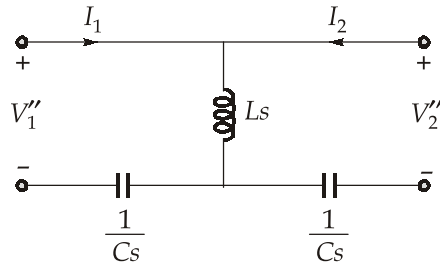

Applying KVL to mesh 1,

$$V_1'' = \left( Ls + \frac{1}{Cs} \right) I_1 + (Ls) I_2 \quad \dots(i)$$

Applying KVL to mesh 2,

$$V_2'' = (Ls) I_1 + \left( Ls + \frac{1}{Cs} \right) I_2 \quad \dots(ii)$$

Comparing equations (i) and (ii) with Z-parameters equations, we get

$$\begin{bmatrix} Z_{11}'' & Z_{12}'' \\ Z_{21}'' & Z_{22}'' \end{bmatrix} = \begin{bmatrix} Ls + \frac{1}{Cs} & Ls \\ Ls & Ls + \frac{1}{Cs} \end{bmatrix}$$

Hence, the overall Z-parameters of the network are

$$\begin{aligned} \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} &= \begin{bmatrix} Z_{11}' + Z_{11}'' & Z_{12}' + Z_{12}'' \\ Z_{21}' + Z_{21}'' & Z_{22}' + Z_{22}'' \end{bmatrix} \\ &= \begin{bmatrix} 2Ls + \frac{2}{Cs} & Ls + \frac{1}{Cs} \\ Ls + \frac{1}{Cs} & 2Ls + \frac{2}{Cs} \end{bmatrix} \\ &= \left( Ls + \frac{1}{Cs} \right) \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix} \end{aligned}$$

### Q.1 (b) Solution:

Applying Kirchhoff current law at node A,

We have,

$$I - \frac{V_A}{j\omega L} - \frac{V_A}{R} - \frac{V_A + 10^4 I_1}{1/j\omega C} = 0$$

and 
$$I_1 = \frac{V_A}{R}$$

Substituting this we have

$$\begin{aligned} I &= \frac{V_A}{j\omega L} + \frac{V_A}{R} + \frac{V_A + \frac{10^4 V_A}{R}}{\frac{1}{j\omega C}} \\ &= V_A \left[ \frac{1}{R} + j \left\{ \omega C \left( 1 + \frac{10^4}{R} \right) - \frac{1}{\omega L} \right\} \right] \\ Y_{in} &= \frac{I}{V_A} = \frac{1}{R} + j \left[ \omega C \left( 1 + \frac{10^4}{1.5 \times 10^4} - \frac{1}{5 \times 10^{-3} \omega} \right) \right] \end{aligned}$$

For resonance,


$$\begin{aligned} \omega_0 C(1 + 0.667) &= \frac{10^3}{5\omega_0} \\ \omega_0 \times 10 \times 10^{-6}(0.667) &= \frac{10^3}{5\omega_0} \\ \omega_0^2 &= \frac{10^3 \times 10^5}{1.667 \times 5} = 11.99 \times 10^6 \\ \omega_0 &= 3.46 \text{ K rad/sec} \\ f_0 &= 551 \text{ Hz} \end{aligned}$$

The quality factor, 
$$\frac{R}{\omega_0 L} = \frac{15 \times 10^3}{3.46 \times 10^3 \times 5 \times 10^{-3}} = 867$$

Hence, Bandwidth, 
$$\frac{f_0}{Q_0} = \frac{551}{867} = 0.635 \text{ Hz}$$
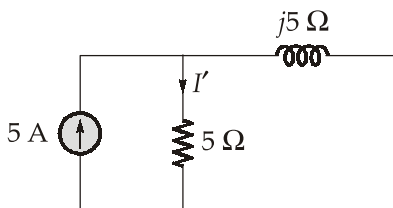
### Q.1 (c) (i) Solution:

Let the current flowing through  $5 \Omega$  resistor is  $I'$  when  $5 \text{ A}$  current source acting alone,  
Replacing the  $10 \text{ V}$  voltage source by its equivalent source impedance,




Using current division rule,

$$I' = \frac{j5}{5 + j5} \times 5 \angle 0^\circ = (2.5 + j2.5) \text{ A}$$

Let the current through  $5 \Omega$  resistor is  $I''$  when  $10 \text{ V}$  voltage source acting alone,

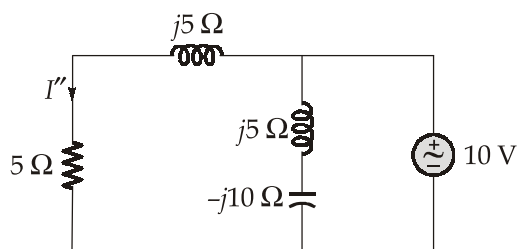Replacing the  $5 \text{ A}$  source by its equivalent source impedance,



$$I'' = \frac{10}{5 + j5} = (1 - j1) \text{ A}$$


Now,

$$\text{current } I = I' + I''$$


$$\begin{aligned} I &= (2.5 + j2.5) + (1 - j1) \\ &= (3.5 + j1.5) \text{ A} \end{aligned}$$
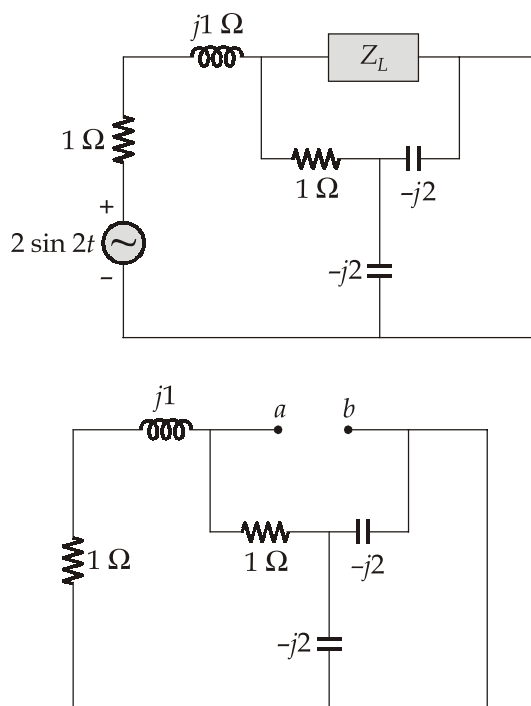
### Q.1 (c) (ii) Solution:

Since  $\omega = 2 \text{ rad/sec}$ , the network is drawn as





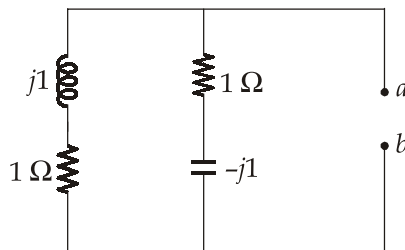


$$Z_L = \frac{(1+j1)(1-j1)}{2} = \frac{1+1}{2} = 1\Omega$$

Hence for maximum power through  $Z_L$ , it should be  $Z_L = 1\Omega$ .


**Q.1 (d) Solution:**

Under steady state condition  $i_L(0^-) = \frac{5}{1} = 5\text{ A}$  and  $V_C(0^-) = 5\text{ Volt}$ .

The transform network becomes

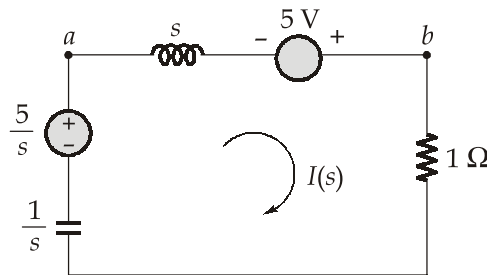

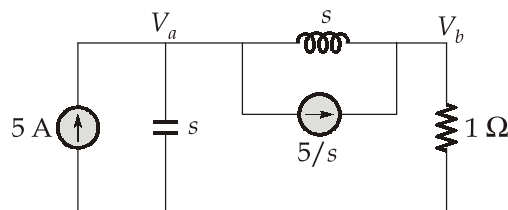Transforming the voltage sources into current sources we have the network



Writing nodal equations at node  $a$  and  $b$  respectively we have,

$$\begin{bmatrix} \left(s + \frac{1}{s}\right) & -\frac{1}{s} \\ -\frac{1}{s} & 1 + \frac{1}{s} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 5 - \frac{5}{s} \\ \frac{5}{s} \end{bmatrix}$$

Using Cramer's rule we have

$$V_a = \frac{\begin{vmatrix} 5 - \frac{5}{s} & -\frac{1}{s} \\ \frac{5}{s} & 1 + \frac{1}{s} \end{vmatrix}}{\begin{vmatrix} s + \frac{1}{s} & -\frac{1}{s} \\ -\frac{1}{s} & 1 + \frac{1}{s} \end{vmatrix}} = \frac{\left(5 - \frac{5}{s}\right)\left(1 + \frac{1}{s}\right) + \frac{5}{s^2}}{\left(s + \frac{1}{s}\right)\left(1 + \frac{1}{s}\right) - \frac{1}{s^2}}$$

$$= \frac{5s^2}{s^3 + s^2 + s} = \frac{5s + \frac{5}{2} - \frac{5}{2}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} = \frac{5\left(s + \frac{1}{2}\right)}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} - \frac{\frac{5}{2} \times \frac{2}{\sqrt{3}} \times \frac{\sqrt{3}}{2}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}$$

$$V_a(t) = 5e^{-t/2} \cos \frac{\sqrt{3}}{2} t - \frac{5}{\sqrt{3}} \sin \frac{\sqrt{3}}{2} t \cdot e^{-t/2}$$

$$= 5e^{-t/2} \left[ \cos \frac{\sqrt{3}}{2} t - \frac{1}{\sqrt{3}} \sin \frac{\sqrt{3}}{2} t \right] \text{ volts}$$

$$\text{Similarly, } V_b(s) = \frac{\begin{vmatrix} s + \frac{1}{s} & 5 - \frac{5}{s} \\ -\frac{1}{s} & \frac{5}{s} \end{vmatrix}}{\frac{(s^3 + s^2 + s)}{s^2}} = \frac{5(s+1)}{s^2 + s + 1} = 5 \left[ \frac{s + \frac{1}{2} - \frac{1}{2}}{s^2 + s + 1} + \frac{1}{s^2 + s + 1} \right]$$

$$= 5 \left[ \frac{s + \frac{1}{2}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} + \frac{\frac{1}{2} \times \frac{2}{\sqrt{3}} \times \frac{\sqrt{3}}{2}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \right]$$

$$V_b(t) = 5e^{-t/2} \cos \frac{\sqrt{3}}{2} t + \frac{5}{\sqrt{3}} e^{-t/2} \sin \frac{\sqrt{3}}{2} t$$

$$= 5e^{-t/2} \left[ \cos \frac{\sqrt{3}}{2} t + \frac{1}{\sqrt{3}} \sin \frac{\sqrt{3}}{2} t \right] \text{ volts}$$

Q.1 (e) Solution:

$$v_s(t) = 2 \cos t$$

Angular frequency,  $\omega = 1 \text{ rad/sec}$ .

$$\therefore X_L = \omega L = 1 \times 1 = 1 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1 \times 1} = 1 \Omega$$


$$\vec{V}_s = 2 \angle 0^\circ$$

$$\omega = 1 \text{ rad/sec},$$

$$X_L = 1 \Omega$$

$$X_C = \frac{1}{|X|} = 1 \Omega$$

Now the circuit in frequency domain

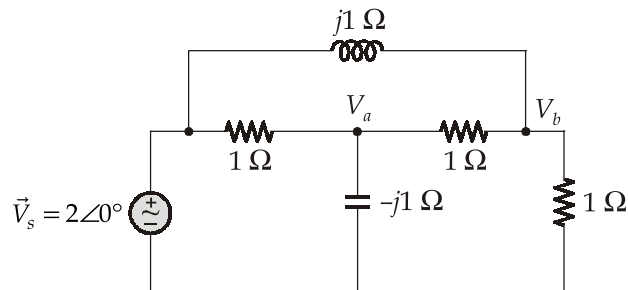

By KCL at node - a

$$\frac{V_a - 2}{1} + \frac{V_a}{-j1} + \frac{V_a - V_b}{1} = 0$$

$$\Rightarrow (2 + j)V_a - V_b = 2 \quad \dots(i)$$

By KCL at node - b

$$\frac{V_b - 2}{j1} + \frac{V_b - V_a}{1} + \frac{V_b}{1} = 0$$

$$\Rightarrow -V_a + (2 - j)V_b = -j2 \quad \dots(ii)$$

From equation (i) and (ii),

$$\begin{bmatrix} 2 + j & -1 \\ -1 & 2 - j \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 2 \\ -j2 \end{bmatrix}$$

$$V_a = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 2 & -1 \\ -j2 & 2-j \end{vmatrix}}{\begin{vmatrix} 2+j & -1 \\ -1 & 2-j \end{vmatrix}} = \frac{4\sqrt{2}\angle -45^\circ}{4} = \sqrt{2}\angle -45^\circ \text{ Volts}$$

Similarly,

$$V_b = \frac{\begin{vmatrix} 2+j & 2 \\ -1 & -j2 \end{vmatrix}}{\begin{vmatrix} 2+j & -1 \\ -1 & 2-j \end{vmatrix}} = \frac{4\sqrt{2}\angle -45^\circ}{4} = \sqrt{2}\angle -45^\circ \text{ Volts}$$

Now,

$$\vec{I}_a = \frac{V_s - V_a}{1} = \frac{2\angle 0^\circ - \sqrt{2}\angle -45^\circ}{1} = \sqrt{2}\angle 45^\circ \text{ A}$$

$$\vec{I}_b = \frac{V_b}{1} = \sqrt{2}\angle -45^\circ \text{ A}$$

Therefore,

$$i_a(t) = \sqrt{2} \cos(t + 45^\circ) \text{ A}$$

$$i_b(t) = \sqrt{2} \cos(t - 45^\circ) \text{ A}$$

### Q.2 (a) (i) Solution:

To obtain  $V_{TH}$ , we remove branch between  $ab$  and obtain  $V_a$  and  $V_b$  and the difference of the two voltages will give  $V_{TH}$ .

$$V_a = \frac{20}{20 + j20} \times 20 = 5 - j5$$

$$V_b = \frac{10}{-j20} \times -j10 = 5 + j0$$

$$V_{TH} = V_a - V_b = -j5 = 5\angle -90^\circ$$

To obtain  $Z_{TH}$  we short circuit the voltage source and see the impedance between  $a$  and  $b$ .

$$\begin{aligned} Z_{TH} &= Z_{ab} = Z_{ac} \parallel Z_{ad} + Z_{cb} \parallel Z_{bd} \\ &= \frac{20 \times j20}{20 + j20} + \frac{(-j10)(-j10)}{-j20} = 10 + j10 - j5 = 10 + j5 \end{aligned}$$

Therefore,

$$\begin{aligned} I &= \frac{V_{TH}}{Z_{TH} + 5} = \frac{5\angle -90^\circ}{10 + j5 + 5} \\ &= \frac{5\angle -90^\circ}{15 + j5} = 0.316\angle -108^\circ \text{ A} \end{aligned}$$

**Q.2 (a) (ii) Solution:**

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$175 \times 10^3 = \frac{1}{2\pi\sqrt{320 \times 10^{-12} L}}$$

$$L = 2.58 \text{ mH}$$

The reactance of the coil at resonance is

$$2\pi \times 175 \times 10^3 \times 2.58 \times 10^{-3} = 2840 \Omega$$

Since

$$Q = \frac{\omega_0 L}{R}$$

$$R = \frac{\omega_0 L}{Q} = \frac{2840}{50} = 56.8 \Omega$$

The impedance of the circuit at resonance is

$$Z = R = 56.8 \Omega$$

Therefore, Current  $I_0 = \frac{0.85}{56.8} = 14.96 \text{ mA}$

The voltage across the capacitor =  $QV$


$$= 50 \times 0.85 = 42.5 \text{ V}$$

The bandwidth of the circuit is

$$\frac{f_0}{Q} = \frac{175 \times 10^3}{50} = 3.5 \text{ kHz}$$

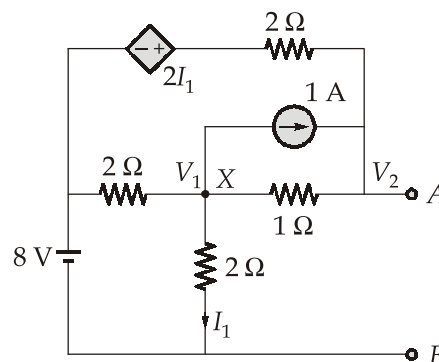**Q.2 (b) Solution:**

To calculate the Thevenin's voltage across A-B, the given circuit is redrawn after opening the resistance across the terminals A-B as shown in figure below,



Let the voltage at node X be  $V_1$  and that at terminal A be  $V_2$ .

Using nodal analysis at node X, we obtain

$$\begin{aligned}\frac{8-V_1}{2} &= \frac{V_1-V_2}{1} + \frac{V_1}{2} + 1 \\ 2V_1 - V_2 &= 3 \quad \dots(i)\end{aligned}$$

Again using nodal analysis at terminal A, we obtain

$$\begin{aligned}\frac{8+2I_1-V_2}{2} + 1 + \frac{V_1-V_2}{1} &= 0 \\ 3V_1 - 3V_2 &= -10 \left( \because I_1 = \frac{V_1}{2} \right) \quad \dots(ii)\end{aligned}$$

Solving the above equation (i) and (ii), we get


$$V_1 = \frac{19}{3} \text{ V} \quad \text{and} \quad V_2 = \frac{29}{3} \text{ V}$$

$\therefore$  The open circuit voltage,

$$V_{oc} = V_2 = \frac{29}{3} \text{ V} = 9.67 \text{ V}$$

$\therefore$  Thevenin's voltage,  $V_{th} = 9.67 \text{ V}$

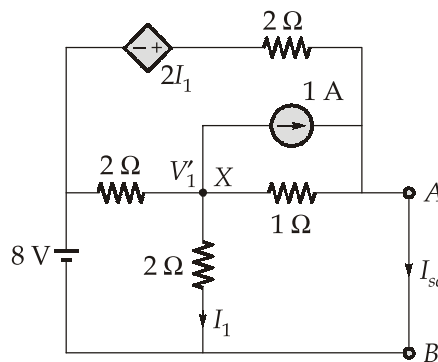Let us now short circuit the terminals A-B, the circuit then becomes as shown in figure below,




Let the voltage at node X be  $V'_1$ . Using nodal analysis at node X, we obtain

$$\begin{aligned}\frac{8-V'_1}{2} &= \frac{V'_1}{2} + 1 + \frac{V'_1}{1} \\ V'_1 &= \frac{3}{2} \text{ V}\end{aligned}$$

$$\text{Short circuit current, } I_{sc} = \frac{8+2I_1}{2} + 1 + \frac{V'_1-0}{1} = 7.25 \text{ A} \quad \left[ \because I_1 = \frac{V'_1}{2} \right]$$

$$\therefore \text{ Thevenin's resistance, } R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{V_{Th}}{I_{sc}} = \frac{9.67}{7.25} = 1.33 \Omega$$

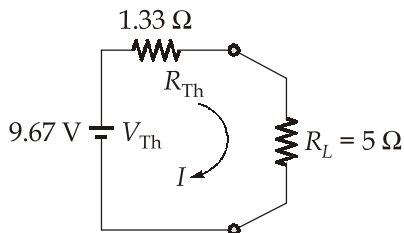The Thevenin equivalent of the given network is as shown below,



$$\therefore \text{Current, } I = \frac{9.67}{1.33 + R_L} = \frac{9.67}{1.33 + 5} \approx 1.527 \text{ A}$$


To get the maximum power transfer through  $R_L$ , as per maximum power transfer theorem,

$$R_L = R_{Th} = 1.33 \Omega$$

$$\therefore P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(9.67)^2}{4 \times 1.33} \approx 17.57 \text{ W}$$

### Q.2 (c) Solution:

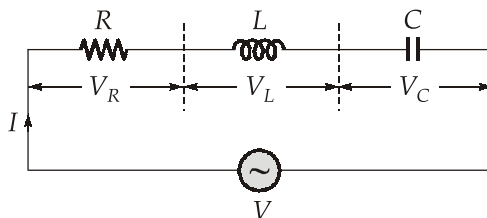(i) Consider series RLC resonant circuit,



The voltage across inductor is  $V_L$  and is given by,

$$V_L = I \cdot (\omega L)$$

but

$$I = \frac{V}{Z}$$

$$v_L = \frac{V(\omega L)}{\left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{1/2}} \quad \dots(i)$$

For maximum voltage across inductor, differentiating equation (i), w.r.t.  $\omega$  and equating it to zero

$$\frac{dV_L}{d\omega} = \frac{Lv}{\left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{1/2}} - \frac{1}{2} \frac{\omega Lv \left[ 2 \left( \omega L - \frac{1}{\omega C} \right) \left( L + \frac{1}{\omega^2 C} \right) \right]}{\left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{3/2}}$$

$$\begin{aligned}
 R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 &= \left( \omega L - \frac{1}{\omega C} \right) \left( L + \frac{1}{\omega^2 L} \right) \omega \\
 \left( \omega L - \frac{1}{\omega C} \right) \left( \omega L + \frac{1}{\omega C} \right) - \left( \omega L - \frac{1}{\omega C} \right)^2 &= R^2 \\
 (\omega L)^2 - \left( \frac{1}{\omega C} \right)^2 - (\omega L)^2 + \left( \frac{1}{\omega C} \right)^2 + \frac{2L}{C} &= R^2 \\
 \frac{2}{(\omega C)^2} &= \frac{2L}{C} - R^2 \\
 \frac{1}{(\omega C)^2} &= \frac{L}{C} - \frac{R^2}{2} \\
 \Rightarrow \frac{1}{\omega^2} &= LC - \frac{R^2 C^2}{2}
 \end{aligned}$$

Put  $\omega = \omega_{L \max}$

$$\omega_{L \max} = \frac{1}{\sqrt{LC - \frac{R^2 C^2}{2}}} = \frac{\frac{1}{\sqrt{LC}}}{\sqrt{1 - \frac{R^2 C}{2L}}} = \frac{\omega_0}{\sqrt{1 - \frac{R^2 C}{2L}}}$$

Hence the frequency at which inductor voltage will be

$$\omega_{L \max} = \frac{\omega_0}{\sqrt{1 - \frac{R^2 C}{2L}}}$$

(ii) Using the result of part-(i),

$$\omega_{L \max} = \frac{1}{\sqrt{20 \times 10^{-6} \times 0.05 \left[ 1 - \frac{50^2 \times 20 \times 10^{-6}}{2 \times 0.05} \right]^{1/2}}}$$

$$\omega_{L \max} = 1414.21 \text{ rad/sec}$$

Voltage across inductor at  $\omega = \omega_{L \max}$  is given as

$$|V_L| = \frac{\omega_{L \max} \cdot L \cdot V}{\left[ R^2 + \left( \omega_{L \max} L - \frac{1}{\omega_{L \max} C} \right)^2 \right]^{1/2}}$$




on putting the values,

$$|V_L|_{\max} = \frac{1414.21 \times 0.05 \times 100}{\sqrt{50^2 + \left( 1414.21 \times 0.05 - \frac{1}{1414.21 \times 20 \times 10^{-6}} \right)^2}}$$

$$|V_L|_{\max} = 115.47 \text{ volts}$$

**Q.3 (a) (i) Solution:**

**With 90 V source:**

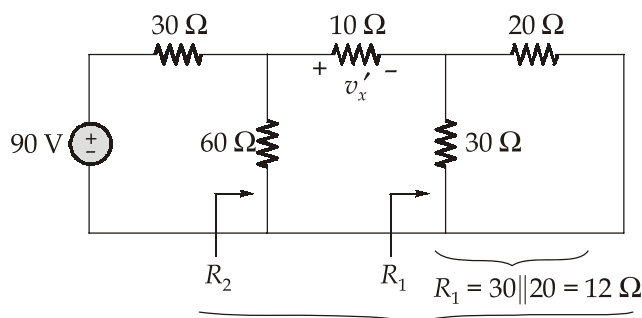



By voltage division,

$$V_{R_2} = \frac{R_2}{30 + R_2} \times 90 = \frac{16.098}{30 + 16.098} \times 90 = 31.429 \text{ Volts}$$


$$\therefore v_x' = V_{R_2} \times \frac{10}{10 + R_1} = 31.429 \times \frac{10}{10 + 12} = 14.286 \text{ Volts}$$

**With 6 A source:**

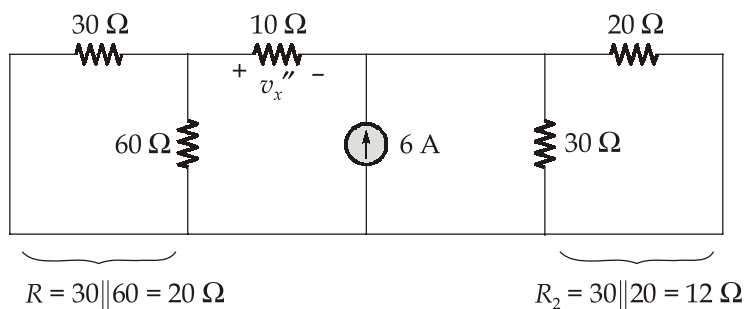

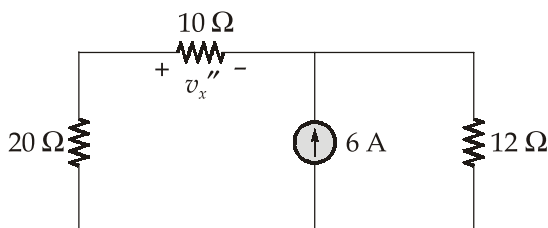


By source transformation

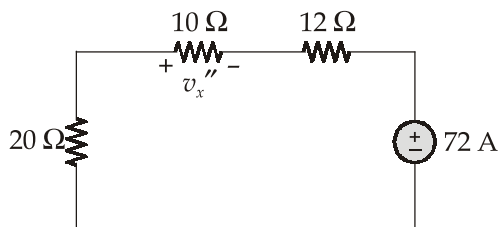


By Voltage division, 
$$v_x'' = (-72) \times \frac{10}{10 + 20 + 12} = -17.143 \text{ Volts}$$

With 40 V source :

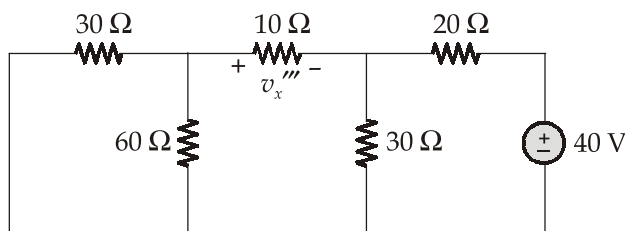

$$R = 30 \parallel 60 = 20 \Omega$$

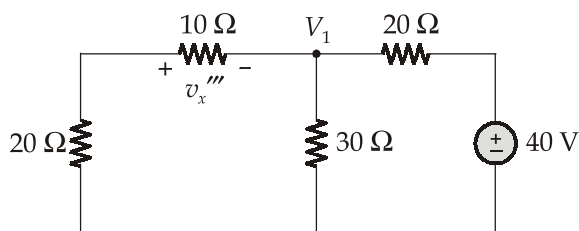

$$R = (20+10) \parallel 30 = 15 \Omega$$

$$\therefore V_1 = 40 \times \frac{15}{15 + 20} = 17.143 \text{ Volts}$$


$$\text{So, } v_x''' = (-V_1) \times \frac{10}{10 + 20} = -17.143 \times \frac{10}{10 + 20} = -5.714 \text{ Volts}$$

By Superposition Theorem,

$$\begin{aligned} v_x &= v_x' + v_x'' + v_x''' \\ &= 14.286 + (-17.143) + (-5.714) = -8.571 \text{ Volts} \end{aligned}$$
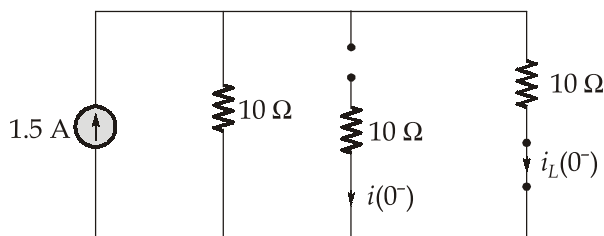
## Q.3 (a) (ii) Solution:

At  $t = 0^-$ , switch is open and the circuit in steady state hence, inductor acts as short-circuit.




$$i_L(0^-) = \frac{1.5 \times 10}{10 + 10} = 0.75 \text{ A}$$

Since inductor current does not change instantly.

$$\therefore i_L(0^-) = i_L(0^+) = 0.75 \text{ A}$$

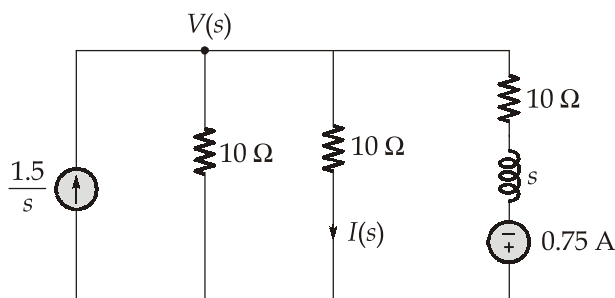For  $t > 0$ , the circuit is transformed into  $s$ -domain and is shown below,



$\therefore$  Applying KCL analysis at node  $V(s)$ ,

$$\therefore \frac{V(s)}{10} + \frac{V(s)}{10} + \frac{V(s) + 0.75}{s + 10} = \frac{1.5}{s}$$

$$V(s) \left[ \frac{1}{10} + \frac{1}{10} + \frac{1}{s + 10} \right] = \frac{1.5}{s} - \frac{0.75}{s + 10}$$

$$V(s) \left[ \frac{10 + s + 5}{5(s + 10)} \right] = \frac{1.5(10 + s) - 0.75s}{s(s + 10)}$$

$$\therefore V(s) = \frac{5(0.75s + 15)}{s(s + 15)} \quad \dots(i)$$

Applying partial fraction expansion on equation (i) we get,

$$V(s) = \frac{A}{s} + \frac{B}{s + 15}$$

$$A = \left. \frac{5(0.75s + 15)}{s + 15} \right|_{s=0} = 5$$

$$B = \frac{5(0.75s + 15)}{s} \bigg|_{s=-15} = -1.25$$

$$\therefore V(s) = \frac{5}{s} - \frac{1.25}{s+15}$$

Now, 
$$I(s) = \frac{V(s)}{10}$$


$$\therefore I(s) = \frac{0.5}{s} - \frac{0.125}{s+15}$$

Now applying inverse Laplace transform, we get,


$$i(t) = (0.5 - 0.125e^{-15t}) \text{ A for } t > 0$$

### Q.3 (b) Solution:


Given two port network,

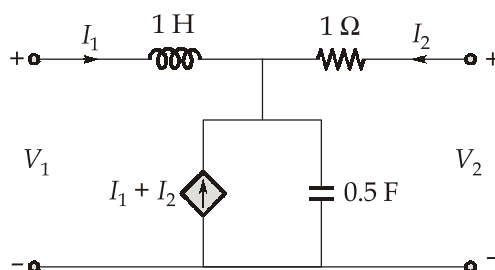

By taking Laplace transform,

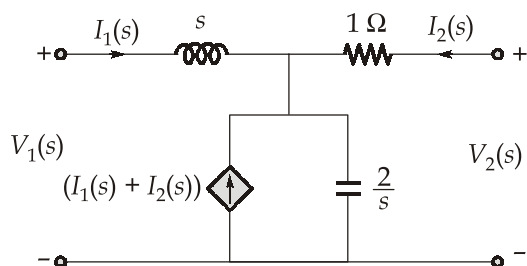

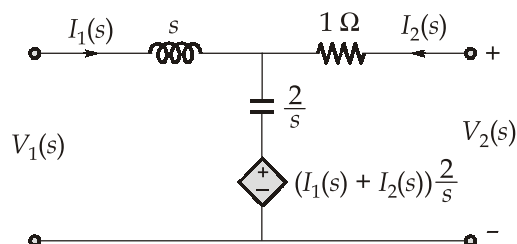By using source transformation theorem, we can redraw the given two port network as



We know that,


transmission parameters can be written as,

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

For A:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

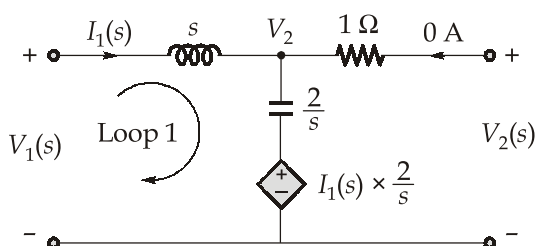

By writing KVL in loop 1,

$$V_1(s) - I_1(s) \cdot s - V_2(s) = 0 \quad \dots(i)$$

where,

$$V_2(s) = \frac{2}{s} \cdot I_1(s) + \frac{2}{s} \cdot I_1(s)$$

$$V_2(s) = \frac{4}{s} I_1(s)$$

$$V_2(s) \cdot \frac{s}{4} = I_1(s) \quad \dots(ii)$$

Substituting equation (ii) in equation (i),

$$V_1(s) - \frac{s}{4} \cdot V_2(s) \cdot s - V_2(s) = 0$$

$$V_1(s) = \left( 1 + \frac{s^2}{4} \right) V_2(s)$$

$$\therefore A = \left. \frac{V_1(s)}{V_2(s)} \right|_{I_2=0} = 1 + \frac{s^2}{4}$$


For C:

From equation (ii),

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{s}{4}$$

For B:

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

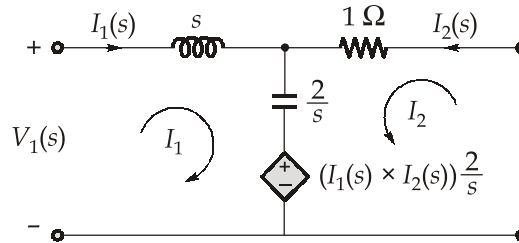

By writing KVL in loop  $L_1$ :

$$V_1(s) - I_1(s) \cdot s - \frac{2}{s}(I_1(s) + I_2(s)) - (I_1(s) + I_2(s)) \frac{2}{s} = 0$$

$$V_1(s) - I_1(s) \cdot s - \frac{4}{s}I_1(s) - \frac{4}{s}I_2(s) = 0$$

$$V_1(s) - \left(s + \frac{4}{s}\right)I_1(s) - \frac{4}{s}I_2(s) = 0 \quad \dots(\text{iii})$$

by writing KVL in loop  $L_2$ :

$$0 - I_2(s) \cdot 1 - (I_1(s) + I_2(s)) \frac{2}{s} - (I_1(s) + I_2(s)) \frac{2}{s} = 0$$

$$-I_1(s) \left(\frac{4}{s}\right) - I_2(s) \left[1 + \frac{4}{s}\right] = 0$$

$$\frac{4}{s} \cdot I_1(s) = -I_2(s) \left[\frac{s+4}{s}\right]$$

$$I_1(s) = -I_2(s) \left[\frac{s+4}{4}\right] \quad \dots(\text{iv})$$

Substituting equation (iv) in equation (iii),

$$V_1(s) + \left(\frac{s^2+4}{s}\right) \left(\frac{s+4}{4}\right) I_2(s) - \frac{4}{s} I_2(s) = 0$$

$$V_1(s) + \left(\frac{s^3+4s^2+4s+16}{4s} - \frac{4}{s}\right) I_2(s) = 0$$

$$V_1(s) + \frac{s^3+4s^2+4s+16-16}{4s} I_2(s) = 0$$

$$V_1(s) = -\left(\frac{s^3+4s^2+4s}{4s}\right) I_2(s) = -\left(\frac{s^2+4s+4}{4}\right) I_2(s)$$

$$\therefore B = \left. \frac{-V_1}{I_2} \right|_{V_2=0} = \left( \frac{s^2 + 4s + 4}{4} \right)$$

For  $D$ :

$$\text{From equation (iv)} \quad D = \left. \frac{-I_1}{I_2} \right|_{V_2=0} = \left( \frac{s+4}{4} \right)$$

$\therefore$  The transmission parameters matrix is

$$[T] = \begin{bmatrix} 1 + \frac{s^2}{4} & \left( \frac{s^2 + 4s + 4}{4} \right) \\ \frac{s}{4} & \left( \frac{s+4}{4} \right) \end{bmatrix}$$

**Q.3 (c) (i) Solution:**


$$V_1 = \frac{10}{\sqrt{2}} \angle 0^\circ \text{V} = 7.07 \angle 0^\circ \text{V}$$

$$\therefore I_1 = \frac{10}{\sqrt{2}} \angle 90^\circ \text{A} = 7.07 \angle 90^\circ \text{A}$$


$$X_C = \frac{1}{\omega C} = \frac{1}{10^6 \times 0.1 \times 10^{-6}} = 10 \Omega$$

$$X_L = 10^6 \times 5 \times 10^{-6} = 5 \Omega$$

Phasor domain circuit will be

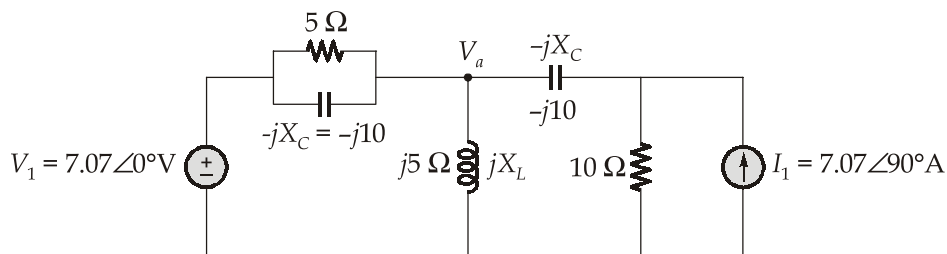

By source transformation

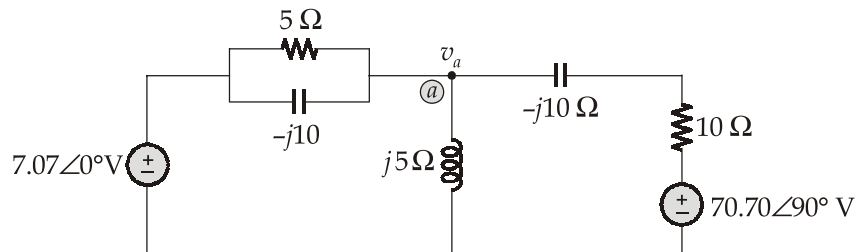

By KCL at node - a,


$$\frac{V_a - 7.07 \angle 0^\circ}{5} + \frac{V_a - 7.07 \angle 0^\circ}{(-j10)} + \frac{V_a}{(j5)} + \frac{V_a - 70.7 \angle 90^\circ}{(10 - j10)} = 0$$

$$V_a \left[ \frac{1}{5} + \frac{1}{-j10} + \frac{1}{j5} + \frac{1}{10 - j10} \right] = \frac{7.07 \angle 0^\circ}{5} + \frac{7.07 \angle 0^\circ}{(-j10)} + \frac{70.7 \angle 90^\circ}{(10 - j10)}$$

$$\Rightarrow V_a = 18.602 \angle 127.87^\circ \text{ Volts}$$


$$\begin{aligned} \therefore V_a(t) &= \sqrt{2} \times 18.602 \sin(10^6 t + 127.87^\circ) \text{ V} \\ &= 26.307 \sin(10^6 t + 127.87^\circ) \text{ V} \end{aligned}$$

**Q.3 (c) (ii) Solution:**

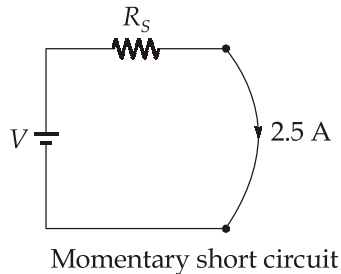

$$\frac{V}{R_S} = 2.5 \text{ A} \quad \dots(i)$$

Figure shows a practical voltage source of  $V$  volts possess an internal series resistance of  $R_S \Omega$  provides a current of  $2.5 \text{ A}$  when (momentarily) short circuited,

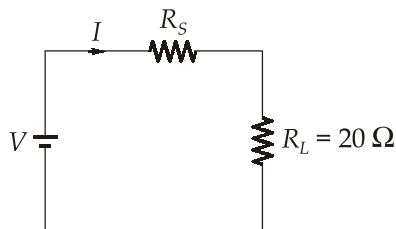

Power consumed =  $80 \text{ W}$

$$I^2 R_L = \left( \frac{V}{R_S + R_L} \right)^2 \times R_L = \frac{V^2}{(R_S + R_L)^2} \times R_L = 80$$

$$\frac{V^2 \times 20}{(R_S + 20)^2} = 80$$



$$V^2 = \frac{80}{20}(R_S + 20)^2$$

$$= R_S^2(2.5)^2 \quad \dots(ii)$$

$$4(R_S + 20)^2 = 6.25 R_S^2$$

$$4(R_S^2 + 20^2 + 40R_S) = 6.25 R_S^2$$

$$2.25R_S^2 - 160R_S - 1600 = 0 \quad \dots(iii)$$

By solving the quadratic equation, we get

$$R_S = 80 \, \Omega$$

1. The open circuit - voltage,

$$V = 2.5 \times 80 = 200 \, \text{V}$$

2. The maximum power delivered to this  $R_L$


$$= \left( \frac{V}{R_S + R_L} \right)^2 \times R_L = \frac{V^2}{4R_L} = 125 \, \text{W}$$

3. The value of  $R_L$  to which it can deliver a maximum power is equal to that of  $R_S$

$$R_L = R_S = 80 \, \Omega$$
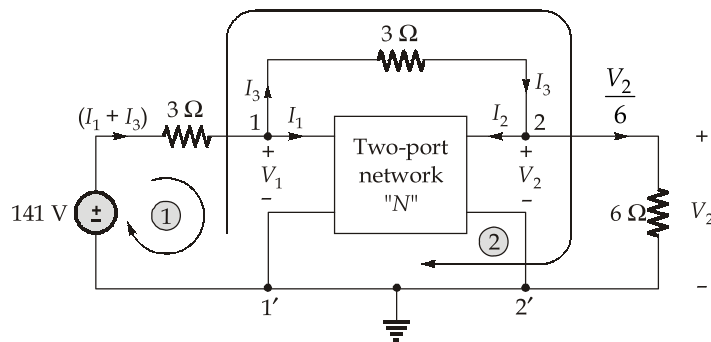
#### Q.4 (a) (i) Solution:

- Considering the given network as shown below:



- From the given z-parameters of the two-port network "N", we can write,

$$V_1 = 2I_1 + I_2 \quad \dots(i)$$

$$V_2 = I_1 + 4I_2 \quad \dots(ii)$$

- By applying KVL in loop (1), we get,

$$3(I_1 + I_3) + V_1 = 141 \, \text{V}$$

$$3I_1 + 3I_3 + 2I_1 + I_2 = 141$$

$$5I_1 + I_2 + 3I_3 = 141 \quad \dots(iii)$$

- By applying KVL in loop (2), we get,

$$\begin{aligned} V_1 - V_2 &= (3)I_3 \\ (2I_1 + I_2) - (I_1 + 4I_2) &= 3I_3 \\ I_1 - 3I_2 - 3I_3 &= 0 \end{aligned} \quad \dots(\text{iv})$$

- By applying KCL at node (2), we get,

$$\begin{aligned} I_3 &= I_2 + \frac{V_2}{6} \\ 6I_3 &= 6I_2 + (I_1 + 4I_2) \\ I_1 + 10I_2 - 6I_3 &= 0 \end{aligned} \quad \dots(\text{v})$$

- By solving the equations (iii), (iv) and (v), we get,

$$\begin{aligned} I_1 &= 24 \text{ A} \\ I_2 &= 1.5 \text{ A} \\ I_3 &= 6.5 \text{ A} \end{aligned}$$

#### Q.4 (a) (ii) Solution:

$$\begin{aligned} V_R(0^+) &= 10 \text{ V} \\ i_L(0^+) &= \frac{10}{R_2} \end{aligned} \quad \dots(\text{i})$$

As the switch is closed at  $t = 0$  sec,  $i_L$  by passes  $R_1$

Hence, the decaying  $i_L$  is through  $R_2$  only

$$\tau = \frac{L}{R_2} = \frac{20 \text{ m}}{R_2} \text{ for } t > 0 \quad \dots(\text{ii})$$

$$V_R(1 \text{ ms}) = 5 \text{ V} \quad \dots(\text{iii})$$

$$\begin{aligned} V_R(1 \text{ ms}) &= i_L(1 \text{ ms}) \times R_2 \\ &= R_2 \times i_L(0^+) e^{\frac{-1 \times 10^{-3} \times R_2}{20 \times 10^{-3}}} \\ &= R_2 \times \frac{10}{R_2} e^{\frac{-R_2}{20}} \end{aligned} \quad \dots(\text{iv})$$

By equating equation (iii) and (iv), we get

$$\begin{aligned} 10 e^{\frac{-R_2}{20}} &= 5 \\ e^{\frac{-R_2}{20}} &= \frac{5}{10} \end{aligned}$$

$$\frac{-R_2}{20} = \ln(0.5) = -0.693$$

$$R_2 = 13.86 \, \Omega$$

At  $t = 0^-$ ,

$$\text{Voltage across } R_1 = V_R = 10 \, \text{V} \quad \dots(\text{vi})$$

$\therefore$  Inductor acts as a short circuit,

$$\text{Current through } R_1 = 2 - \frac{V_R}{R_2} = 2 - \frac{10}{13.86} = 1.28 \, \text{A} \quad \dots(\text{vii})$$


By substituting equation (vii) in equation (vi)

$$1.28 R_1 = 10$$

$$R_1 = 7.82 \, \Omega$$
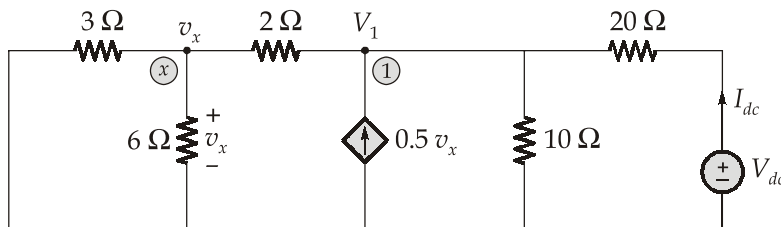
#### Q.4 (b) Solution:

To determine  $R_{Th}$ , deactivate all the independent voltage source by short circuit and independent current source by open circuit & connect a test voltage source  $V_s$  delivering current  $I_s$  at terminals  $a - b$ .



By KCL at node (x)

$$\frac{v_x}{3} + \frac{v_x}{6} + \frac{v_x - v_1}{2} = 0$$

$$v_x \left[ \frac{1}{3} + \frac{1}{6} + \frac{1}{2} \right] = \frac{v_1}{2}$$

$$v_x = 0.5 v_1 \quad \dots(\text{i})$$

KCL at node-1

$$\frac{v_1 - v_x}{2} + \frac{v_1}{10} = I_{dc} + 0.5 v_x$$

$$0.6 v_1 = I_{dc} + V_x \quad \dots(\text{ii})$$

From equation (ii),

$$0.1 v_1 = I_{dc} \quad \dots(\text{iii})$$

Now,


$$\frac{V_{dc} - v_1}{20} = I_{dc}$$

$$\frac{V_{dc} - 10I_{dc}}{20} = I_{dc}$$

$$V_{dc} = 30I_{dc}$$

$$R_{Th} = \frac{V_{dc}}{I_{dc}} = 30 \Omega$$

Calculation of  $V_{Th}$  :

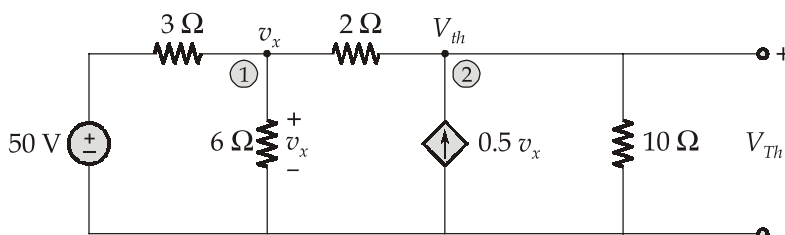

By KCL at node (1)

$$\frac{v_x - 50}{3} + \frac{v_x}{6} + \frac{v_x - V_{Th}}{2} = 0$$

$$v_x \left[ \frac{1}{3} + \frac{1}{6} + \frac{1}{2} \right] = \frac{V_{Th}}{2} + \frac{50}{3}$$

$\Rightarrow$

$$v_x = 0.5 V_{Th} + 16.667 \quad \dots(i)$$

By KCL at node (2)

$$\frac{V_{Th} - v_x}{2} + \frac{V_{Th}}{10} - 0.5v_x = 0$$

$$V_{Th} \left[ \frac{1}{2} + \frac{1}{10} \right] = v_x \quad \dots(ii)$$

From (i) and (ii)


$$0.5 V_{Th} + 16.667 = 0.6 V_{Th}$$

$\Rightarrow$


$$V_{Th} = 166.67 \text{ volts}$$

Thus, Norton's current,  $I_N = \frac{V_{Th}}{R_{Th}} = \frac{166.67}{30} = 5.55 \text{ A}$

Thevenin's equivalent circuit is

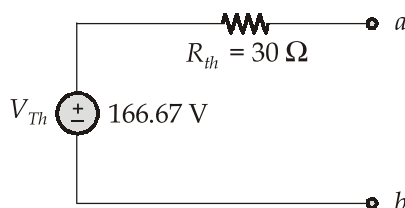


Norton's equivalent circuit is

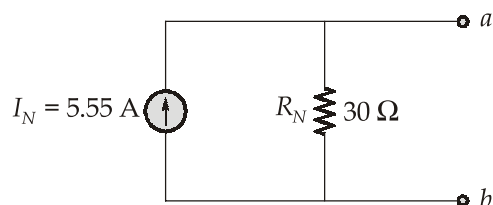

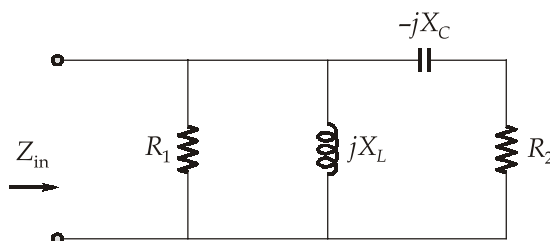**Q.4 (c) (i) Solution:**

At frequency,  $\omega$  rad/s, the reactances are:



Where,  $R_1 = 1 \Omega$ ,  $R_2 = 0.1 \Omega$ ,  $X_L = \omega_0 L$ ;  $X_C = \frac{1}{\omega_0 C}$

$$Y_{in} = \frac{1}{R_1} + \frac{1}{jX_L} + \frac{1}{R_2 - jX_C}$$

$$= \frac{1}{R_1} + \frac{1}{jX_L} + \frac{R_2 + jX_C}{R_2^2 - X_C^2}$$

For the circuit to resonate,

$$\text{Im}[Y_{in}] = 0$$

$$\text{Im}[Y_{in}] = \frac{1}{jX_L} + \frac{jX_C}{R_2^2 + X_C^2} = 0$$

$$\frac{1}{X_L} = \frac{X_C}{R_2^2 + X_C^2}$$

$$\Rightarrow R_2^2 + X_C^2 = X_L X_C$$

$$R_2^2 = X_L X_C - X_C^2$$

$$R_2^2 = \frac{L}{C} - \frac{1}{(\omega_0 C)^2}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC - R_2^2 C^2}}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{20 \times 10^{-3} \times 9 \times 10^{-6} - (0.1 \times 9 \times 10^{-6})^2}}$$

$$\Rightarrow \omega_0 = 2357.02 \text{ rad/sec}$$

Therefore resonance frequency is,

$$\omega_0 = 2357.02 \text{ rad/sec}$$

$\Rightarrow$  At  $\omega = \omega_0$ ,

$$\begin{aligned} Y_{\text{in}} &= \frac{1}{R_1} + \frac{R_2}{R_2^2 + (X_C)^2} \\ &= \frac{1}{1} + \frac{0.1}{(0.1)^2 + (2357.02 \times 10^{-6})^2} = 10.56 \text{ Mho} \end{aligned}$$

Therefore input impedance at  $\omega = \omega_0$ , is

$$Z_{\text{in}} = \frac{1}{Y_{\text{in}}} = \frac{1}{10.56} = 0.09461 \Omega$$

#### Q.4 (c) (ii) Solution:

For the given graph, Kirchhoff's current law for the branch currents ( $i_1, i_2, \dots, i_6$ ) gives the equations

$$\begin{aligned} i_1 + i_2 + i_6 &= 0; & -i_1 + i_3 - i_5 &= 0 \\ -i_2 - i_3 + i_4 &= 0; & -i_4 + i_5 - i_6 &= 0 \end{aligned}$$

In matrix form, these equation can be represented as

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ -1 & 0 & 1 & 0 & -1 & 0 \\ 0 & -1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = 0$$

The complete incidence matrix is

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ -1 & 0 & 1 & 0 & -1 & 0 \\ 0 & -1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & -1 \end{bmatrix}$$

So, the reduced incidence matrix is

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ -1 & 0 & 1 & 0 & -1 & 0 \\ 0 & -1 & -1 & 1 & 0 & 0 \end{bmatrix}$$

Thus the number of possible trees of the graph

$$= \det \left\{ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ -1 & 0 & 1 & 0 & -1 & 0 \\ 0 & -1 & -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \\ 0 & -1 & 0 \\ 1 & 0 & 0 \end{bmatrix} \right\}$$

$$= \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 16$$

### Section B : Engineering Mathematics

**Q.5 (a) Solution:**

We have,  $\frac{dy}{dx} = \frac{y+x+2}{y-x+1}$

Put  $x = X + h$ ,  $y = Y + k$

The given equation reduces to

$$\frac{dY}{dX} = \frac{(Y+k)+(X+h)+2}{(Y+k)-(X+h)+1} = \frac{X+Y+(h+k+2)}{Y-X+(k-h+1)}$$

Now, choose  $h$  and  $k$  so that  $h+k+2=0$ ,  $k-h+1=0$ .

Solving these equations, we get

$$h = -\frac{1}{2}, k = -\frac{3}{2}$$

$$\therefore \frac{dY}{dX} = \frac{X+Y}{Y-X}$$

Put  $Y = VX$  so that  $\frac{dY}{dX} = V + X \frac{dV}{dX}$  ... (ii)

The equation (ii) is transformed as

$$V + X \frac{dV}{dX} = \frac{X + VX}{VX - X} = \frac{1 + V}{V - 1}$$

$$X \frac{dV}{dX} = \frac{1 + V}{V - 1} - V = \frac{-V^2 + V + 1 + V}{V - 1} = \frac{-V^2 + 2V + 1}{V - 1}$$

$$\frac{1}{2} \int \left( \frac{2V - 2}{V^2 - 2V - 1} \right) dV = - \int \frac{dX}{X}$$

$$\frac{1}{2} \log(V^2 - 2V - 1) = -\log X + \log C$$

$$(V^2 - 2V - 1)^{\frac{1}{2}} = -\log X + \log C$$

$$(V^2 - 2V - 1)^{\frac{1}{2}} = \frac{C}{X}$$

$$X^2(V^2 - 2V - 1) = C_1$$

$$\left(y + \frac{3}{2}\right)^2 - 2\left(x + \frac{1}{2}\right)\left(y + \frac{3}{2}\right) - \left(x + \frac{1}{2}\right)^2 = C_1$$

**Q.5 (b) Solution:**


Consider  $\int_C \frac{z^2 - z + 2}{z^4 + 10z^2 + 9} dz = \int_C f(z) dz$  where  $C$  is the contour consisting of the upper half

of a large circle  $|z| = R$  and the real axis from  $-R$  to  $R$ .

By Residue Theorem,

$$\begin{aligned} \int_C f(z) dz &= \int_{-R}^R f(x) dx + \int_{CR} f(z) dz \\ &= 2\pi i (\text{sum of residues}) \end{aligned} \quad \dots(i)$$

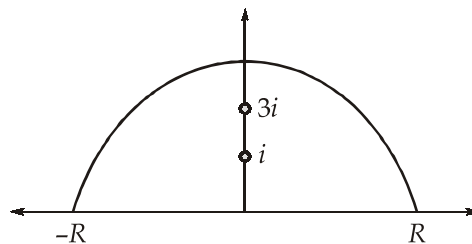Poles of  $f(z)$  are given by  $z^4 + 10z^2 + 9 = 0$





$$(z^2 + 1)(z^2 + 9) = 0$$

$$z = \pm i \text{ and } z = \pm 3i$$

Thus,  $z = \pm i$  and  $z = \pm 3i$

are the simple poles of which only  $z = i$  and  $z = 3i$  lie inside  $C$ .

Sum of residue at these poles.

$$\begin{aligned} &= \lim_{z \rightarrow i} (z - i)f(z) + \lim_{z \rightarrow 3i} (z - 3i)f(z) \\ &= \lim_{z \rightarrow i} \frac{(z - i)(z^2 - z + 2)}{(z - i)(z + i)(z^2 + 9)} + \lim_{z \rightarrow 3i} \frac{(z - 3i)(z^2 - z + 2)}{(z - 3i)(z^2 + 1)(z + 3i)} \\ &= \frac{i^2 - i + 2}{(i^2 + 9)(2i)} + \frac{9i^2 - 3i + 2}{(9i^2 + 1)6i} \\ &= \frac{1 - i}{16i} + \frac{7 + 3i}{48i} = \frac{10}{48i} = \frac{5}{24i} \end{aligned}$$

$$\int_{-\infty}^{\infty} f(x)dx = 2\pi i \times \frac{5}{24i} = \frac{5\pi}{12}$$

**Q.5 (c) Solution:**

$$\begin{aligned} \text{(i)} \quad \operatorname{div} \bar{F} &= \nabla \cdot \bar{F} = \left( \hat{i} \frac{\partial}{\partial x} + \hat{j} \frac{\partial}{\partial y} + \hat{k} \frac{\partial}{\partial z} \right) \cdot (x^2 \hat{i} + z \hat{j} + yz \hat{k}) \\ &= 2x + y \end{aligned}$$

By Divergence Gauss Theorem

$$\begin{aligned} \iint F \cdot \hat{n} \, ds &= \iiint \operatorname{div} F \, dV = \iiint (2x + y) \, dx \, dy \, dz \\ &= \iint dx \, dy \int_0^c (2x + y) \, dz = \iint dx \, dy [2xz + yz]_0^c \\ &= \iint dx \, dy [2cx + cy] \\ &= \int dx \left[ 2cxy + c \frac{y^2}{2} \right]_0^b \\ &= \int_0^a \left[ 2cbx + \frac{cb^2}{2} x \right]_0^a = \frac{abc}{2} (2a + b) \end{aligned}$$

**Q.5 (c) (ii) Solution:**

1. Given :  $f(x) = 2x^3 - 9x^2 + 12x - 5$  ... (i)

It is differentiable for all  $x$  in  $[0, 3]$ . Since, it is a polynomial differentiating (i) w.r.t.  $x$ , we get

$$f'(x) = 2 \times 3x^2 - 9 \times 2x + 12 = 6(x^2 - 3x + 2)$$

Now,  $f'(x) = 0$

$$6(x^2 - 3x + 2) = 0$$

$$(x - 1)(x - 2) = 0$$

$$x = 1, 2$$

Also, 1, 2 both are in  $[0, 3]$ . Therefore, 1 and 2 both are stationary points.

Further,  $f(1) = 2 \times 1^3 - 9 \times 1^2 + 12 \times 1 - 5 = 0$

$$\begin{aligned} f(2) &= 2 \times 2^3 - 9 \times 2^2 + 12 \times 2 - 5 \\ &= 16 - 36 + 24 - 5 = -1 \end{aligned}$$

Also,  $f(0) = -5$

and  $f(3) = 2 \times 3^3 - 9 \times 3^2 + 12 \times 3 - 5$   
 $= 54 - 81 + 36 - 5 = 4$

Therefore, the absolute maxima value is 4 and the absolute minima value is -5. The point of maxima is 3 and the point of minima is 0.

2. Given :  $f(x) = 12x^{4/3} - 6x^{1/3}$ ,  $x \in [-1, 1]$

Differentiating (i) w.r.t.  $x$ , we get

$$\begin{aligned} f'(x) &= 12 \cdot \frac{4}{3} x^{1/3} - 6 \cdot \frac{1}{3} x^{-2/3} \\ &= 16x^{1/3} - \frac{2}{x^{2/3}} = \frac{2(8x - 1)}{x^{2/3}} \end{aligned}$$

Now,  $f'(x) = 0$

$$\frac{2(8x - 1)}{x^{2/3}} = 0$$

$$x = \frac{1}{8}$$

As  $\frac{1}{8} \in [-1, 1]$ ,  $\frac{1}{8}$  is a critical point.

Also, we note that  $f$  is not differentiable at  $x = 0$ .

$$\begin{aligned}
 f\left(\frac{1}{8}\right) &= 12\left(\frac{1}{8}\right)^{4/3} - 6\left(\frac{1}{8}\right)^{1/3} \\
 &= 12\left(\frac{1}{2}\right)^4 - 6 \cdot \frac{1}{2} = 12 \cdot \frac{1}{16} - 3 = \frac{-9}{4} \\
 f(0) &= 12 \cdot 0 - 6 \cdot 0 = 0 \\
 f(-1) &= 12(-1)^{4/3} - 6(-1)^{1/3} \\
 &= 12 \cdot 1 - 6(-1) \\
 &= 18 \\
 f(1) &= 12 \cdot 1^{4/3} - 6 \cdot 1^{1/3} \\
 &= 12 - 6 \\
 &= 6
 \end{aligned}$$

Therefore, the absolute maxima value is 18 and the absolute minima value is  $-\frac{9}{4}$ .

The point of maxima is -1 and the point of minima is  $\frac{1}{8}$ .

#### Q.5 (d) Solution:

It is clear that the given function

$$f(x) = \begin{cases} (1-x) & , \quad x < 1 \\ (1-x)(2-x), & 1 \leq x \leq 2 \\ (3-x) & , \quad x > 2 \end{cases}$$

Continuous and differentiable at all points except possibly at  $x = 1$  and 2.

Continuity at  $x = 1$

$$\begin{aligned}
 \text{LHL} &= \lim_{x \rightarrow 1^-} f(x) = \lim_{x \rightarrow 1^-} (1-x) \\
 &= \lim_{h \rightarrow 0} [1 - (1-h)] = \lim_{h \rightarrow 0} h = 0
 \end{aligned}$$

and

$$\begin{aligned}
 \text{RHL} &= \lim_{x \rightarrow 1^+} f(x) = \lim_{x \rightarrow 1^+} (1-x)(2-x) \\
 &= \lim_{h \rightarrow 0} [1 - (1+h)][2 - (1+h)] \\
 &= \lim_{h \rightarrow 0} -h \cdot (1-h) = 0
 \end{aligned}$$

$$\therefore \quad \text{LHL} = \text{RHL} = f(1) = 0$$

Therefore,  $f$  is continuous at  $x = 1$ ,

$$\begin{aligned}
 Lf'(1) &= \lim_{h \rightarrow 0} \frac{f(1-h) - f(1)}{-h} \\
 &= \lim_{h \rightarrow 0} \frac{1 - (1-h) - 0}{-h} = \lim_{h \rightarrow 0} \left( \frac{h}{-h} \right) = 1
 \end{aligned}$$

and

$$\begin{aligned}
 Rf'(1) &= \lim_{h \rightarrow 0} \frac{f(1+h) - f(1)}{h} \\
 &= \lim_{h \rightarrow 0} \frac{[1 - (1+h)][2 - (1+h)] - 0}{h} \\
 &= \lim_{h \rightarrow 0} \frac{-h(1-h)}{h} = \lim_{h \rightarrow 0} (h-1) = -1
 \end{aligned}$$

Since,  $L[f'(1)] = Rf'(1)$ , therefore  $f$  is differentiable.

at  $x = 1$

Continuity at  $x = 2$ ,

$$\begin{aligned}
 \text{LHL} &= \lim_{x \rightarrow 2^-} f(x) = \lim_{x \rightarrow 2^-} (1-x)(2-x) \\
 &= \lim_{h \rightarrow 0} [-1 - (2-h)][2 - (2-h)] \\
 &= \lim_{h \rightarrow 0} (-1+h)h = 0
 \end{aligned}$$

and

$$\begin{aligned}
 \text{RHL} &= \lim_{x \rightarrow 2^+} f(x) = \lim_{x \rightarrow 2^+} (3-x) \\
 &= \lim_{h \rightarrow 0} [3 - (2+h)] \\
 &= \lim_{h \rightarrow 0} (1-h) = 1
 \end{aligned}$$

Since,  $\text{LHL} \neq \text{RHL}$ , therefore  $f$  is not continuous at  $x = 2$  as such  $f$  cannot be differentiable at  $x = 2$ .

Hence,  $f$  is continuous and differentiable at all points except at  $x = 2$ .

### Q.5 (e) Solution:

Since the total probability is unity.

$$\therefore \int_0^6 f(x) dx = 1$$

$$\int_0^2 kx dx + \int_2^4 2k dx + \int_4^6 (-kx + 6k) dx = 1$$

$$k \left| \frac{x^2}{2} \right|_0^2 + 2k \left| x \right|_2^4 + \left( -\frac{kx^2}{2} + 6kx \right) \Big|_4^6 = 1$$

$$2k + 4k + (-10k + 12k) = 1$$

i.e.,  $k = \frac{1}{8}$

$$\text{Mean of } X = \int_0^6 xf(x) dx$$

$$= \int_0^2 kx^2 dx + \int_2^4 2kx dx + \int_4^6 x(-kx + 6k) dx$$

$$= k \left| \frac{x^3}{3} \right|_0^2 + 2k \left| \frac{x^2}{2} \right|_2^4 + (-k) \left| \frac{x^3}{3} \right|_4^6 + 6k \left| \frac{x^2}{2} \right|_4^6$$

$$= k \left( \frac{8}{3} \right) + k(12) - k \left( \frac{152}{3} \right) + 3k(20) = \frac{24}{8} = 3$$

### Q.6 (a) (i) Solution:

According to this theorem,


If a function  $f(x)$  is such that

(a) It is continuous in closed interval  $[a, b]$

(b) It is derivable in open interval  $(a, b)$

then there exist at least one value 'C' of  $x$  lying in  $(a, b)$  such that,

$$\frac{f(b) - f(a)}{b - a} = f'(C)$$

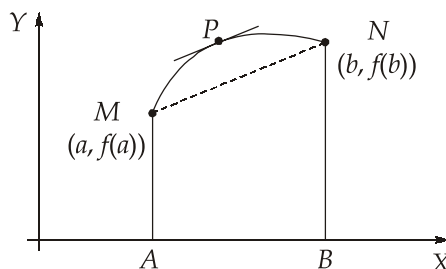

**Geometrical significance:** If the graph of a function is a continuous curve from  $M$  to  $N$  and has a unique tangent at every point between  $M$  and  $N$ , then there exists at least one point 'P' in the curve such that the tangent at  $P$  is parallel to the chord  $MN$  joining its extremities.

**Q.6 (a) (ii) Solution:**

Given equation in symbolic form is,

$$(D^2 - 2D + 2)y = x + e^x \cos x$$

To find complementary function:

Its auxiliary equation is

$$D^2 - 2D + 2 = 0$$

$$\therefore D = \frac{2 \pm \sqrt{(4-8)}}{2} = 1 \pm i$$

Thus complementary function =  $e^x(c_1 \cos x + c_2 \sin x)$

To find particular integral,

$$\begin{aligned} \text{P.I.} &= \frac{1}{D^2 - 2D + 2}(x) + \frac{1}{D^2 - 2D + 2}(e^x \cos x) \\ &= \frac{1}{2} \left[ 1 - \left( D - \frac{D^2}{2} \right) \right]^{-1} (x) + e^x \frac{\cos x}{(D+1)^2 - 2(D+1) + 2} \\ &= \frac{1}{2} \left( 1 + D - \frac{D^2}{2} \right) x + e^x \frac{1}{D^2 + 1} \cos x \\ &= \frac{1}{2} (x + 1 - 0) + e^x \cdot x \frac{1}{2D} \cos x \\ &= \frac{(x+1)}{2} + \frac{xe^x}{2} \int \cos x \, dx = \frac{1}{2} (x+1) + \frac{xe^x}{2} \sin x \end{aligned}$$

Hence the complete solution is,

$$y = e^x (c_1 \cos x + c_2 \sin x) + \frac{1}{2} (x+1) + \frac{xe^x}{2} \sin x$$

**Q.6 (a) (iii) Solution:**

Given matrix,

$$A = \begin{bmatrix} \frac{1}{2}(1+i) & \frac{1}{2}(-1+i) \\ \frac{1}{2}(1+i) & \frac{1}{2}(1-i) \end{bmatrix}$$

Conjugate of A, i.e.,

$$\bar{A} = \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(-1-i) \\ \frac{1}{2}(1-i) & \frac{1}{2}(1+i) \end{bmatrix}$$

∴ Transpose of  $\bar{A}$  i.e.,

$$(\bar{A})^T = A^\theta = \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(1-i) \\ \frac{1}{2}(-1-i) & \frac{1}{2}(1+i) \end{bmatrix} \quad \dots(i)$$

Now,

$$\begin{aligned} A^\theta \cdot A &= \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(1-i) \\ \frac{1}{2}(-1-i) & \frac{1}{2}(1+i) \end{bmatrix} \begin{bmatrix} \frac{1}{2}(1+i) & \frac{1}{2}(-1+i) \\ \frac{1}{2}(1+i) & \frac{1}{2}(1-i) \end{bmatrix} \\ &= \begin{bmatrix} \frac{1}{4}(1+1) + \frac{1}{4}(1+1) & -\frac{1}{4}(1-i)^2 + \frac{1}{4}(1-i)^2 \\ -\frac{1}{4}(1+i)^2 + \frac{1}{4}(1+i)^2 & \frac{1}{4}(1+1) + \frac{1}{4}(1+1) \end{bmatrix} \\ &= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = I \end{aligned}$$

Similarly,

$$AA^\theta = I$$

Hence,  $A$  is a unitary matrix.

Also,

$$A^{-1} = A^\theta = \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(1-i) \\ -\frac{1}{2}(1+i) & \frac{1}{2}(1+i) \end{bmatrix}$$

#### Q.6 (b) (i) Solution:

Here, we have

$$A = \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix}$$

$$A^2 = \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix} \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix} = \begin{bmatrix} 9 & 8 & 8 \\ 8 & 9 & 8 \\ 8 & 8 & 9 \end{bmatrix}$$

$$A^2 - 4A - 5I = \begin{bmatrix} 9 & 8 & 8 \\ 8 & 9 & 8 \\ 8 & 8 & 9 \end{bmatrix} - 4 \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix} - 5 \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$5I = A^2 - 4A$$

Multiplying by  $A^{-1}$  we get

$$5A^{-1} = A - 4I$$

$$= \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix} - 4 \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} -3 & 2 & 2 \\ 2 & -3 & 2 \\ 2 & 2 & -3 \end{bmatrix}$$

$$A^{-1} = \frac{1}{5} \begin{bmatrix} -3 & 2 & 2 \\ 2 & -3 & 2 \\ 2 & 2 & -3 \end{bmatrix}$$

### Q.6 (b) (ii) Solution:

Consider the matrix equation,

$$\lambda_1 X_1 + \lambda_2 X_2 + \lambda_3 X_3 + \lambda_4 X_4 = 0$$

$$\lambda_1(1, 2, 4) + \lambda_2(2, -1, 3) + \lambda_3(0, 1, 2) + \lambda_4(-3, 7, 2) = 0$$

$$\lambda_1 + 2\lambda_2 + 0\lambda_3 - 3\lambda_4 = 0$$

$$2\lambda_1 - \lambda_2 + \lambda_3 + 7\lambda_4 = 0$$

$$4\lambda_1 + 3\lambda_2 + 2\lambda_3 + 2\lambda_4 = 0$$

This is the homogeneous system,

$$\begin{bmatrix} 1 & 2 & 0 & -3 \\ 2 & -1 & 1 & 7 \\ 4 & 3 & 2 & 2 \end{bmatrix} \begin{bmatrix} \lambda_1 \\ \lambda_2 \\ \lambda_3 \\ \lambda_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$R_2 \rightarrow R_2 - 2R_1 \text{ and } R_3 \rightarrow R_3 - 4R_1$$

$$\begin{bmatrix} 1 & 2 & 0 & -3 \\ 0 & -5 & 1 & 13 \\ 0 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} \lambda_1 \\ \lambda_2 \\ \lambda_3 \\ \lambda_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$R_3 \rightarrow R_3 - R_2$$

$$\lambda_1 + 2\lambda_2 - 3\lambda_4 = 0$$

$$-5\lambda_2 + \lambda_3 + 13\lambda_4 = 0$$

$$\lambda_3 + \lambda_4 = 0$$



Let,  $\lambda_4 = t$ ,  $\lambda_3 + t = 0$ ,  $\lambda_3 = -t$ ,

$$-5\lambda_2 - t + 13t = 0$$

$$\lambda_2 = \frac{12}{5}t$$

$$\lambda_1 + \frac{24t}{5} - 3t = 0$$

$$\lambda_1 = \frac{-9t}{5}$$

Hence, the given vectors are linearly dependent, substituting the values of  $\lambda$  in (i),

We get,

$$\frac{-9t}{5}X_1 + \frac{12t}{5}X_2 - tX_3 + tX_4 = 0$$

$$9X_1 - 12X_2 + 5X_3 - 5X_4 = 0$$

#### Q.6 (c) (i) Solution:

To find complementary function:

Its auxiliary equation is,

$$D^2 - 4D + 4 = 0$$

$$\text{i.e., } (D - 2)^2 = 0$$

$$\therefore D = 2, 2$$

$$\therefore \text{Complementary function} = (C_1 + C_2x) e^{2x}$$

To find particular integral,

$$\begin{aligned} \text{P.I.} &= \frac{1}{(D-2)^2} (8x^2 e^{2x} \sin 2x) \\ &= 8e^{2x} \frac{1}{(D+2-2)^2} (x^2 \sin 2x) \\ &= 8e^{2x} \frac{1}{D^2} (x^2 \sin 2x) \\ &= 8e^{2x} \frac{1}{D} \int x^2 \sin 2x \, dx \\ &= 8e^{2x} \frac{1}{D} \left\{ x^2 \left( \frac{-\cos 2x}{2} \right) - \int 2x \left( \frac{-\cos 2x}{2} \right) dx \right\} \end{aligned}$$

$$\begin{aligned}
&= 8e^{2x} \frac{1}{D} \left\{ -\frac{x^2}{2} \cos 2x + \frac{x \sin 2x}{2} - \int 1 \cdot \frac{\sin 2x}{2} dx \right\} \\
&= 8e^{2x} \int \left\{ -\frac{x^2}{x} \cos 2x + \frac{x}{2} \sin 2x + \frac{\cos 2x}{4} \right\} dx \\
&= 8e^{2x} \left[ \left\{ -\frac{x^2}{2} \frac{\sin 2x}{2} - \int (-x) \frac{\sin 2x}{2} dx \right\} + \left\{ \int \frac{x}{2} \sin 2x dx \right\} + \frac{\sin 2x}{8} \right] \\
&= 8e^{2x} \left[ \left( -\frac{x^2}{4} + \frac{1}{8} \right) \sin 2x + \int x \sin 2x dx \right] \\
&= 8e^{2x} \left[ \left( \frac{1}{8} - \frac{x^2}{4} \right) \sin 2x + x \left( -\frac{\cos 2x}{2} \right) - \int 1 \cdot \left( -\frac{\cos 2x}{2} \right) dx \right] \\
&= 8e^{2x} \left[ \left( \frac{1}{8} - \frac{x^2}{4} \right) \sin 2x - \frac{x \cos 2x}{2} + \frac{\sin 2x}{4} \right] \\
&= e^{2x} [(3 - 2x^2) \sin 2x - 4x \cos 2x]
\end{aligned}$$

∴ The complete solution is,

$$y = e^{2x} [C_1 + C_2 x + (3 - 2x^2) \sin 2x - 4x(\cos 2x)]$$

**Q.6 (c) (ii) Solution:**

S. no.	$x$	$y$	$xy$	$x^2$
1	1	1	1	1
2	3	2	6	9
3	4	4	16	16
4	6	4	24	36
5	8	5	40	64
6	9	7	63	81
7	11	8	88	121
8	14	9	126	196
Total	56	40	364	524

Let  $y = a + bx$  be the line of regression of  $y$  on  $x$ ,

where  $a$  and  $b$  are given by the following equations,

$$\Sigma y = na + b\Sigma x$$

$$\text{or } 40 = 8a + 56b \quad \dots(i)$$

$$\Sigma xy = a\Sigma x + b\Sigma x^2$$

$$\text{or } 364 = 56a + 524b \quad \dots(ii)$$

On solving (i) and (ii), we get

$$a = \frac{6}{11}$$

and

$$b = \frac{7}{11}$$

The equation of the required line is

$$y = \frac{6}{11} + \frac{7}{11}x$$

$$\text{or } 7x - 11y + 6 = 0$$

$$\text{If } x = 10, \quad y = \frac{6}{11} + \frac{7}{11} \times 10 = \frac{76}{11} = 6.91$$


### Q.7 (a) Solution:

**Case-I:** When  $m = 0$

$$\text{In this case, } y = x - x^2 \quad \dots(i)$$

$$\text{and } y = 0 \quad \dots(ii)$$

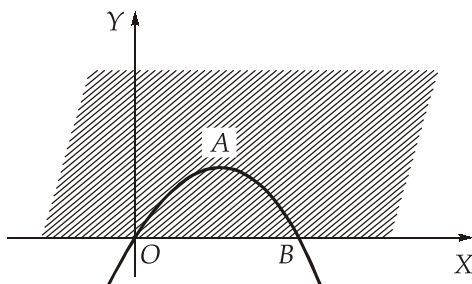are two given curves,  $y > 0$  is total region above X-axis. Therefore, area between  $y = x - x^2$  and  $y = 0$  is area between  $y = x - x^2$  and above the X-axis.




$$\therefore A = \int_0^1 (x - x^2) dx = \left[ \frac{x^2}{2} - \frac{x^3}{3} \right] = \frac{1}{2} - \frac{1}{3} = \frac{1}{6} \neq \frac{9}{2}$$

Hence, no solution exists.

**Case-II:** When  $m < 0$

In this case, area between  $y = x - x^2$  and  $y = mx$  is  $OABCO$  and points of intersection are  $(0, 0)$  and  $\{1 - m, m(1 - m)\}$ .
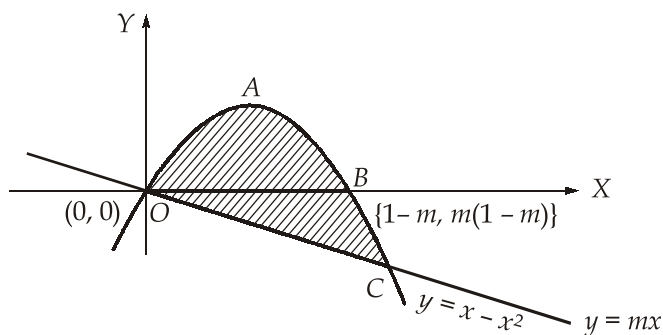
$$\therefore \text{Area of curve } OABCO = \int_0^{1-m} [x - x^2 - mx] dx$$



$$= \left[ (1-m) \frac{x^2}{2} - \frac{x^3}{3} \right]_0^{1-m}$$

$$= \frac{1}{2}(1-m)^3 - \frac{1}{3}(1-m)^3 = \frac{1}{6}(1-m)^3$$

$$\therefore \frac{1}{6}(1-m)^3 = \frac{9}{2}$$


$$\Rightarrow (1-m)^3 = 27$$

$$\Rightarrow 1-m = 3$$

$$\Rightarrow m = -2$$

**Case III** When  $m > 0$

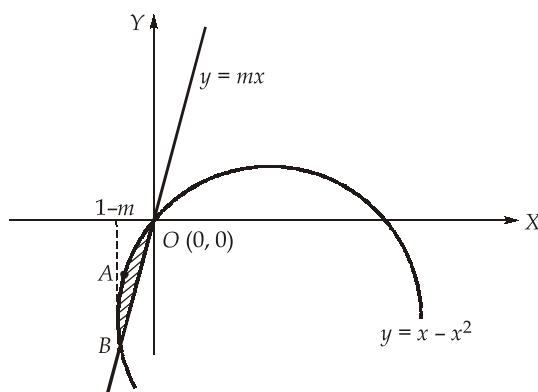In this case,  $y = mx$  and  $y = x - x^2$  intersect in  $(0, 0)$  and  $\{(1 - m), m(1 - m)\}$  as shown in figure.



$$\begin{aligned}
 \therefore \quad \text{Area of shaded region} &= \int_{1-m}^0 (x - x^2 - mx) dx \\
 &= \left[ (1-m) \frac{x^2}{2} - \frac{x^3}{3} \right]_{1-m}^0 \\
 &= -\frac{1}{2}(1-m)(1-m)^2 + \frac{1}{3}(1-m)^3 \\
 &= -\frac{1}{6}(1-m)^3 \\
 \Rightarrow \quad \frac{9}{2} &= -\frac{1}{6}(1-m)^3 && \text{[given]} \\
 \Rightarrow \quad (1-m)^3 &= -27 \\
 \Rightarrow \quad (1-m) &= -3 \\
 \Rightarrow \quad m &= 3 + 1 = 4
 \end{aligned}$$

**Q.7 (b) (i) Solution:**

$$u = \log(x^3 + y^3 + z^3 - 3xyz) \quad \dots(i)$$

Differentiating (i) partially w.r.t. 'x' we get

$$\frac{\partial u}{\partial x} = \frac{3x^2 - 3yz}{x^3 + y^3 + z^3 - 3xyz} \quad \dots(ii)$$

Similarly,

$$\frac{\partial u}{\partial y} = \frac{3y^2 - 3zx}{x^3 + y^3 + z^3 - 3xyz} \quad \dots(iii)$$

$$\frac{\partial u}{\partial z} = \frac{3z^2 - 3xy}{x^3 + y^3 + z^3 - 3xyz} \quad \dots(iv)$$

On adding (ii), (iii) and (iv), we get

$$\begin{aligned}
 \frac{\partial u}{\partial x} + \frac{\partial u}{\partial y} + \frac{\partial u}{\partial z} &= \frac{3(x^2 + y^2 + z^2 - xy - yz - zx)}{x^3 + y^3 + z^3 - 3xyz} \\
 &= \frac{3(x^2 + y^2 + z^2 - xy - yz - zx)}{(x + y + z)(x^2 + y^2 + z^2 - xy - yz - zx)} \\
 &= \frac{3}{(x + y + z)}
 \end{aligned}$$

$$\begin{aligned}
 \left( \frac{\partial}{\partial x} + \frac{\partial}{\partial y} + \frac{\partial}{\partial z} \right)^2 u &= \left( \frac{\partial u}{\partial x} + \frac{\partial u}{\partial y} + \frac{\partial u}{\partial z} \right) \frac{3}{x+y+z} \\
 &= -3(x+y+z)^{-2} - 3(x+y+z)^{-2} - 3(x+y+z)^{-2} \\
 &= \frac{-9}{(x+y+z)^2}
 \end{aligned}$$

**Q.7 (b) (ii) Solution:**

$$x^3 - 2x - 5 = 0$$

Let,

$$f(x) = x^3 - 2x - 5 \quad \dots(i)$$

$$f(2) = 8 - 4 - 5 = -1$$

$$f(2.5) = (2.5)^3 - 2 \times 2.5 - 5 = 5.625$$

Since  $f(2)$  and  $f(2.5)$  are of opposite sign, the root of (1) lies between 2 and 2.5.

$$f'(x) = 3x^2 - 2$$

$$f'(2) = 12 - 2 = 10$$

Let 2 be an approximate root of (1). By Newton-Raphson method

$$a_1 = a - \frac{f(a)}{f'(a)} = 2 - \frac{f(2)}{f'(2)}$$

$$= 2 - \frac{-1}{10} = 2.1$$

$$\begin{aligned}
 f(2.1) &= (2.1)^3 - 2(2.1) - 5 = 9.261 - 4.2 - 5 \\
 &= 0.061
 \end{aligned}$$

$$f'(2.1) = 3(2.1)^2 - 2 = 11.23$$

$$a_2 = 2.1 - \frac{f(2.1)}{f'(2.1)} = 2.1 - \frac{0.061}{11.23} = 2.09457$$

$$\begin{aligned}
 f(2.09457) &= (2.09457)^3 - 2(2.09457) - 5 \\
 &= -0.00016
 \end{aligned}$$

$$\begin{aligned}
 f'(2.09457) &= 3(2.09457)^2 - 2 \\
 &= 11.16167
 \end{aligned}$$

$$a_3 = 2.09457 - \frac{f(2.09457)}{f'(2.09457)} = 2.09456$$

Q.7 (c) Solution:

$$F = \frac{\vec{r}}{|\vec{r}|^3} = \frac{x\hat{i} + y\hat{j} + z\hat{k}}{(x^2 + y^2 + z^2)^{3/2}}$$

$$\text{Curl } \vec{F} = \vec{\nabla} \times \vec{F}$$

$$= \left( \hat{i} \frac{\partial}{\partial x} + \hat{j} \frac{\partial}{\partial y} + \hat{k} \frac{\partial}{\partial z} \right) \times \left( \frac{x\hat{i} + y\hat{j} + z\hat{k}}{(x^2 + y^2 + z^2)^{3/2}} \right)$$

$$= \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ \frac{x}{(x^2 + y^2 + z^2)^{3/2}} & \frac{y}{(x^2 + y^2 + z^2)^{3/2}} & \frac{z}{(x^2 + y^2 + z^2)^{3/2}} \end{vmatrix}$$

$$= \hat{i} \left[ \frac{-3}{2} \frac{2yz}{(x^2 + y^2 + z^2)^{5/2}} + \frac{3}{2} \frac{2yz}{(x^2 + y^2 + z^2)^{5/2}} \right]$$

$$- \hat{j} \left[ \frac{-3}{2} \frac{2xz}{(x^2 + y^2 + z^2)^{5/2}} - \left( \frac{-3}{2} \right) \frac{2xz}{(x^2 + y^2 + z^2)^{5/2}} \right]$$

$$- \hat{k} \left[ \frac{-3}{2} \frac{2xy}{(x^2 + y^2 + z^2)^{5/2}} - \left( \frac{-3}{2} \right) \frac{2xy}{(x^2 + y^2 + z^2)^{5/2}} \right]$$

$$= 0$$

Hence,  $\vec{F}$  is irrotational.

$$\vec{F} = \vec{\nabla} \phi, \quad \text{where } \phi \text{ is called scalar potential}$$

$$d\phi = \frac{\partial \phi}{\partial x} dx + \frac{\partial \phi}{\partial y} dy + \frac{\partial \phi}{\partial z} dz$$

$$= \left( \hat{i} \frac{\partial \phi}{\partial x} + \hat{j} \frac{\partial \phi}{\partial y} + \hat{k} \frac{\partial \phi}{\partial z} \right) (\hat{i} dx + \hat{j} dy + \hat{k} dz)$$

$$= \frac{x dx + y dy + z dz}{(x^2 + y^2 + z^2)^{3/2}}$$

$$\phi = \frac{1}{2} \int \frac{2x dx + 2y dy + 2z dz}{(x^2 + y^2 + z^2)^{3/2}} = \frac{1}{2} \left( \frac{-2}{1} \right) (x^2 + y^2 + z^2)^{-1/2}$$

$$\text{scalar potential } (\phi) = \frac{-1}{(x^2 + y^2 + z^2)^{1/2}} = -\frac{1}{|\vec{r}|}$$

$$\text{Now, Div } \vec{F} = \vec{\nabla} \cdot \vec{F}$$

$$\begin{aligned} &= \left( \hat{i} \frac{\partial}{\partial x} + \hat{j} \frac{\partial}{\partial y} + \hat{k} \frac{\partial}{\partial z} \right) \cdot \frac{x\hat{i} + y\hat{j} + z\hat{k}}{(x^2 + y^2 + z^2)^{3/2}} \\ &= \frac{\partial}{\partial x} \frac{x}{(x^2 + y^2 + z^2)^{3/2}} + \frac{\partial}{\partial y} \frac{y}{(x^2 + y^2 + z^2)^{3/2}} + \frac{\partial}{\partial z} \frac{z}{(x^2 + y^2 + z^2)^{3/2}} \\ &= \frac{(x^2 + y^2 + z^2)^{3/2} - x \left( \frac{3}{2} \right) (x^2 + y^2 + z^2)^{1/2} (2x)}{(x^2 + y^2 + z^2)^3} \\ &\quad + \frac{(x^2 + y^2 + z^2)^{3/2} (1) - y \left( \frac{3}{2} \right) (x^2 + y^2 + z^2)^{1/2} (2y)}{(x^2 + y^2 + z^2)^3} \\ &\quad + \frac{(x^2 + y^2 + z^2)^{3/2} (1) - z \left( \frac{3}{2} \right) (x^2 + y^2 + z^2)^{1/2} (2z)}{(x^2 + y^2 + z^2)^3} \\ &= \frac{(x^2 + y^2 + z^2)^{1/2}}{(x^2 + y^2 + z^2)^3} [x^2 + y^2 + z^2 - 3x^2 + x^2 + y^2 + z^2 - 3y^2 + x^2 + y^2 + z^2 - 3z^2] \\ &= 0 \end{aligned}$$

Hence,  $\vec{F}$  is solenoidal.

#### Q.8 (a) Solution:

(i) Probability of  $S_1$  to be among the eight winners

$$= (\text{Probability of } S_1 \text{ being a pair}) \times (\text{Probability of } S_1 \text{ winning in the group})$$

$$= 1 \times \frac{1}{2} = \frac{1}{2} \quad (\text{Since, } S_1 \text{ is definitely in a group})$$

(ii) If  $S_1$  and  $S_2$  are in the same pair, then exactly one wins,

If  $S_1$  and  $S_2$  are in two pairs separately, then exact one of  $S_1$  and  $S_2$  will be among the eight winner.

If  $S_1$  wins and  $S_2$  losses or  $S_1$  loses and  $S_2$  wins



Now, the probability of  $S_1, S_2$  being in the same pair and one wins

$$= (\text{Probability of } S_1, S_2 \text{ being the same pair}) \times (\text{Probability of anyone winning in the pair})$$

and the probability of  $S_1, S_2$  being the same pair

$$= \frac{n(E)}{n(S)}$$

where,

$n(E)$  = The number of ways in which 16 persons can be divided in 8 pairs

$$\therefore n(E) = \frac{(14)!}{(2!)^7 \times 7!} \text{ and } n(S) = \frac{(16)!}{(2!)^8 \cdot 8!}$$

$\therefore$  Probability of  $S_1$  and  $S_2$  being in the same pair

$$= \frac{(14)! \times (2!)^8 \times 8!}{(2!)^7 \times 7! \times 16!} = \frac{1}{15}$$

The probability of any one winning in the pairs of  $S_1, S_2 = P(\text{certain event}) = 1$

$\therefore$  The pairs of  $S_1, S_2$  being in two pairs separately and  $S_1$  wins,  $S_2$  loses + The probability of  $S_1, S_2$  being in two pairs separately and  $S_1$  loses,  $S_2$  wins

$$= \left[ 1 - \frac{(14)!}{(2!)^7 \times 7!} \times \frac{1}{2} \times \frac{1}{2} + \left[ 1 - \frac{(14)!}{(2!)^7 \times 7!} \times \frac{1}{2} \times \frac{1}{2} \right] \times \frac{1}{2} \times \frac{1}{2} \right]$$


$$= \frac{1}{2} \times \frac{14}{15} \times \frac{(14)!}{14!} = \frac{7}{15}$$

$\therefore$  required probability

$$= \frac{1}{15} + \frac{7}{15} = \frac{8}{15}$$
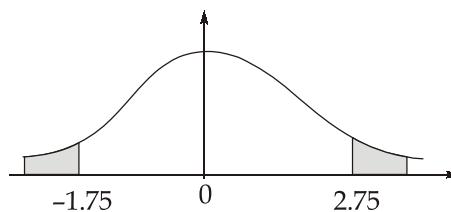
#### Q.8 (b) (i) Solution:

Tolerance limits of the diameter of non-defective plugs are



$$0.752 - 0.004 = 0.748 \text{ cm}$$

$$0.752 + 0.004 = 0.756 \text{ cm}$$

$$Z = \frac{x - \mu}{\sigma}$$

If  $x_1 = 0.748$ ,

$$Z_1 = \frac{0.748 - 0.7515}{0.002} = -1.75$$

If  $x_2 = 0.756$

$$Z_2 = \frac{0.756 - 0.7515}{0.002} = 2.25$$

Area under,


$$\begin{aligned} Z_1 = -1.75 \text{ to } Z_2 = 2.25 \\ &= (\text{Area from } Z = 0 \text{ to } Z_1 = -1.75) \\ &\quad + (\text{Area from } Z = 0 \text{ to } Z_2 = 2.25) \\ &= 0.4599 + 0.4878 = 0.9477 \end{aligned}$$

Number of plugs likely to be rejected

$$= 1000(1 - 0.9477) = 52.3$$

Approximately 52 plugs are likely to be rejected.

**Q.8 (b) (ii) Solution:**

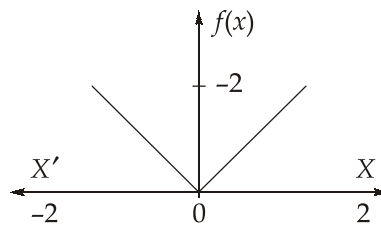

$$f(x) = |x|, \quad -2 < x < 2$$

$$f(x) = 0, \quad 0 < x < 2$$

$$= -x, \quad -2 < x < 0$$

$$a_0 = \frac{1}{c} \int_{-c}^c f(x) dx = \frac{1}{2} \int_0^2 x dx + \frac{1}{2} \int_{-2}^0 (-x) dx$$

$$= \frac{1}{2} \left[ \frac{x^2}{2} \right]_0^2 + \frac{1}{2} \left[ \frac{-x^2}{2} \right]_{-2}^0 = \frac{1}{4} (4 - 0) + \frac{1}{4} (0 + 4) = 2$$

$$\begin{aligned}
 a_n &= \frac{1}{c} \int_{-c}^c f(x) \cos \frac{n\pi x}{c} dx = \frac{1}{2} \int_0^2 x \cos \frac{n\pi x}{2} dx + \frac{1}{2} \int_{-2}^0 (-x) \cos \frac{n\pi x}{2} dx \\
 &= \frac{1}{2} \left[ x \left( \frac{2}{n\pi} \sin \frac{n\pi x}{2} \right) - (1) \left( \frac{4}{n^2 \pi^2} \cos \frac{n\pi x}{2} \right) \right]_0^2 \\
 &\quad + \frac{1}{2} \left[ (-x) \left( \frac{2}{n\pi} \sin \frac{n\pi x}{2} \right) - (-1) \left( -\frac{4}{n^2 \pi^2} \cos \frac{n\pi x}{2} \right) \right]_{-2}^0 \\
 &= \frac{1}{2} \left[ 0 + \frac{4}{n^2 \pi^2} (-1)^n - \frac{4}{n^2 \pi^2} \right] + \frac{1}{2} \left[ 0 - \frac{4}{n^2 \pi^2} + \frac{4}{n^2 \pi^2} (-1)^n \right] \\
 &= \frac{1}{2} \frac{4}{n^2 \pi^2} [(-1)^n - 1 - 1 + (-1)^n] = \frac{4}{n^2 \pi^2} [(-1)^n - 1] \\
 &= \begin{cases} \frac{8}{n^2 \pi^2} & \text{if } n \text{ is odd} \\ 0 & \text{if } n \text{ is even} \end{cases}
 \end{aligned}$$

$$b_n = 0 \text{ as } f(x) \text{ is even function}$$

Fourier series is

$$\begin{aligned}
 f(x) &= \frac{a_0}{2} + a_1 \cos \frac{\pi x}{c} + c_2 \cos \frac{2\pi x}{c} + \dots + b_1 \sin \frac{\pi x}{c} + b_2 \sin \frac{2\pi x}{c} + \dots \\
 &= 1 - \frac{8}{\pi^2} \left[ \frac{\cos \frac{\pi x}{2}}{1^2} + \frac{\cos \frac{3\pi x}{2}}{3^2} + \frac{\cos \frac{5\pi x}{2}}{5^2} + \dots \right]
 \end{aligned}$$

**Q.8 (c) Solution:**

$$h = 0.1$$

Here,  $x_0 = 0, \quad y_0 = 1$

$$f(x, y) = x + y$$

Now,  $K_1 = h_f(x_0, y_0) = 0.1(0 + 1) = 0.1$

$$\begin{aligned}
 K_2 &= hf \left( x_0 + \frac{h}{2} + y_0 + \frac{K_1}{2} \right) = 0.1f(0 + 0.05, 1 + 0.05) \\
 &= 0.1(0.05 + 1.05) \\
 &= 0.11
 \end{aligned}$$

$$\begin{aligned}K_3 &= hf\left(x_0 + \frac{h}{2}, y_0 + \frac{K_2}{2}\right) \\&= 0.1f(0 + 0.05, 1 + 0.055) \\&= 0.1105\end{aligned}$$

$$\begin{aligned}K_4 &= h_f(x_0 + h, y_0 + K_3) \\&= 0.1f(0 + 0.1, 1 + 0.1105) \\&= 0.1(0.1 + 1.1105) \\&= 0.12105\end{aligned}$$

According to Runge-Kutta (Fourth order) Formula,

$$\begin{aligned}y_1 &= y_0 + \frac{1}{6}[K_1 + 2K_2 + 2K_3 + K_4] \\y_1 &= 1 + \frac{1}{6}(0.1 + 0.22 + 0.221 + 0.12105) \\&= 1 + \frac{1}{6}(0.66205) = 1.11034\end{aligned}$$

For the second step,

$$\begin{aligned}x_0 &= 0.1, & y_0 &= 1.11034, \\y &= 0.1\end{aligned}$$

$$\begin{aligned}K_1 &= h_f(x_0, y_0) \\&= 0.1(0.1 + 1.11034) \\&= 0.121034\end{aligned}$$

$$\begin{aligned}K_2 &= hf\left(x_0 + \frac{h}{2}, y_0 + \frac{K_1}{2}\right) \\&= 0.1f(0.1 + 0.05, 1.11034 + 0.060517) \\&= 0.1(0.15 + 1.170857) \\&= 0.1320857\end{aligned}$$

$$\begin{aligned}K_3 &= hf\left(x_0 + \frac{h}{2}, y_0 + \frac{K_2}{2}\right) \\&= 0.1f(0.1 + 0.05, 1.11034 + 0.0660428) \\&= 0.1(0.15 + 1.1763828) \\&= 0.13263828\end{aligned}$$

$$K_4 = hf(x_0 + h, y_0 + K_3)$$

$$\begin{aligned} &= 0.1(0.1 + 0.1, 1.11034 + 0.13263828) \\ &= 0.1(0.2 + 1.24297828) \\ &= 0.144297828 \\ y_1 &= y_0 + \frac{1}{6}[K_1 + 2K_2 + 2K_3 + K_4] \\ &= 1.11034 + \frac{1}{6}[0.121034 + 2 \times 0.1320857 + 2 \times 0.13263828 + 0.144297828] \\ &= 1.11034 + \frac{1}{6} \times 0.794779788 \\ &= 1.11034 + 0.132463298 \\ &= 1.242803298 \end{aligned}$$

○○○○