



# ESE 2025

## Main Exam Detailed Solutions

### Electronics & Telecom. Engineering

#### PAPER-I

**EXAM DATE : 10-08-2025 | 09:00 AM to 12:00 PM**

MADE EASY has taken due care in making solutions. If you find any discrepancy/error/typo or want to contest the solution given by us, kindly send your suggested answer(s) with detailed explanation(s) at:

**[info@madeeasy.in](mailto:info@madeeasy.in)**

Corporate Office : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

Delhi | Hyderabad | Bhopal | Jaipur | Pune

 9021300500

 [www.madeeasy.in](http://www.madeeasy.in)



# ANALYSIS

## Electronics and Telecom. Engineering ESE 2023 Main Examination

**Paper-I**


Sl.	Subjects	Marks
1.	Basic Electronics Engineering (EDC)	32
2.	Materials Science	42
3.	Electronic Measurements and Instrumentation	72
4.	Network Theory	144
5.	Analog Circuits	106
6.	Digital Circuits	52
7.	Basic Electrical Engineering	32
	<b>Total</b>	<b>480</b>

**Scroll down for  
detailed solutions**



**Section-A**

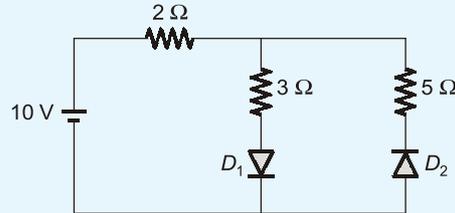
**Q.1** (a) Find the current flowing in the circuit as given in the figure, where two ideal diodes are connected in parallel:



[12 marks : 2025]

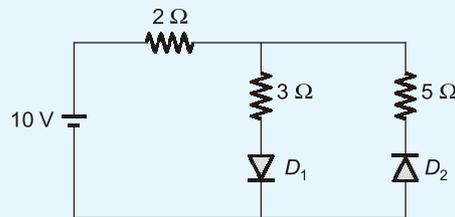
**Solution:**

To determine the current flowing in the circuit, we have to determine whether the diodes  $D_1$  and  $D_2$  are in ON/OFF state.




Assume both the diodes are in non-conducting state:

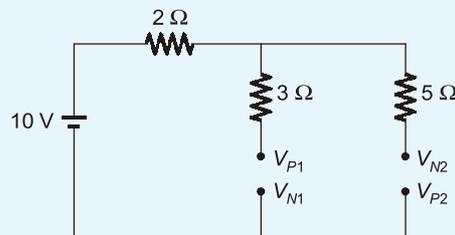In the non-conducting state, the diodes can be considered as open circuit. Hence, the circuit can be drawn as below:



As,  $V_{P1} > V_{M1}$ ; Diode  $D_1$  is in conducting state. As,  $V_{P2} < V_{M2}$ ; Diode  $D_2$  is in non-conducting state.

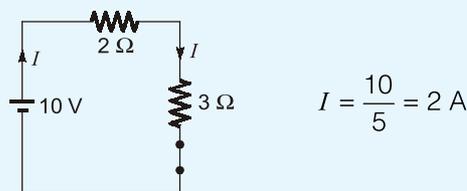Assuming the diode  $D_1$  as conducting (short-circuit) and diode  $D_2$  as non-conducting (open-circuit), the circuit can be drawn as below,



**End of Solution**

# Advance Ranker Batch for ESE & GATE 2026



## Commencement Dates :

CE	9 Aug 2025	ME	10 Aug 2025
CS	13 Aug 2025	EE   EC	11 Aug 2025

## Teaching Hours:

GATE : **300-350 Hrs**  
ESE + GATE : **400-450 Hrs**

## Course Validity :

**Till 28 Feb, 2026**

Mode: **Live-Online**

- ✓ Live-online classes by **experienced faculty**.
- ✓ Specially designed for **repeaters and serious aspirants**.
- ✓ Focus on enhancing **problem-solving skills**, speed, and accuracy.
- ✓ Includes **2000+ advanced-level practice questions** in PDF format.
- ✓ **Dedicated online test series** for GATE and ESE Prelims .
- ✓ Teaching hours : **300–350** for GATE and **400–450** for ESE + GATE.
- ✓ **Timings 6 PM to 9 PM**, suitable for college going students & working professionals.
- ✓ Regular live **Zoom sessions** for doubt resolution and academic guidance.
- ✓ Course is offered for **Civil, Mechanical, Electrical, Electronics and Computer Science**.
- ✓ Course validity till **28<sup>th</sup> February, 2026** for full syllabus coverage and revision.

Low Cost **EMI Facility** Available  
**Admissions Open**

Download  
the App



Android



iOS

📞 9021300500

🌐 [www.madeeasyprime.com](http://www.madeeasyprime.com)



- Q.1** (b) A certain d.c. motor has  $R_A = 1.3 \Omega$ ,  $I_A = 10 \text{ A}$  and produces a back e.m.f.  $E_A = 240 \text{ V}$ , while operating at a speed of 1200 r.p.m. Determine the voltage applied to the armature, the developed torque and the developed power.

[12 marks : 2025]

**Solution:**


We have,

Armature resistance,  $R_A = 1.3 \Omega$

Armature current,  $I_A = 10 \text{ A}$

Back emf,  $E_A = 240 \text{ V}$

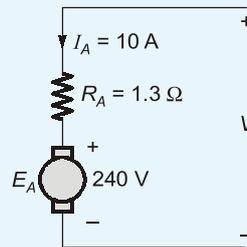Operating speed,  $N_r = 1200 \text{ rpm}$



1. Applied voltage,  $V$ :

The applied voltage ( $V$ ) to the armature of a d.c. motor is the sum of the back e.m.f. ( $E_A$ ) and the voltage drop across the armature resistance ( $R_A$ ) due to the armature current ( $I_A$ ).

$$V = I_A R_A + E_A$$

$$V = I_A R_A + 240$$

$$V = 13 + 240 = 253 \text{ volt}$$

2. Developed torque,  $T_d$ :

$$T_d = \frac{P_{del}}{\omega}, \text{ where } P_{del} = \text{Developed power} = E_A I_A$$

$$T_d = \frac{E_A I_A}{2\pi N} = \frac{240 \times 10}{\frac{2\pi \times 1200}{60}}$$

$$T_d = 19.09 \text{ Nm}$$

3. Developed power:  $P_d$

$$P_d = E_A \cdot I_A = 240 \times 10 = 2.4 \text{ kWatt}$$

End of Solution

- Q.1** (c) Consider a unit cell of simple cubic structure. Find the angle between the normals to pair of planes whose Miller indices are (i) [1 0 1] and [0 1 0], and (ii) [2 1 1] and [1 0 1].

[12 marks : 2025]

**Solution:**

In case of a cubic crystal, the direction  $[hkl]$  is perpendicular to the plane with miller indices  $(hkl)$ . Therefore, the angle between the normals to the planes is the same as the angle between two planes represented by the Miller indices  $(h_1k_1l_1)$  and  $(h_2k_2l_2)$  given as

$$\cos \theta = \frac{h_1h_2 + k_1k_2 + l_1l_2}{\sqrt{h_1^2 + k_1^2 + l_1^2} \sqrt{h_2^2 + k_2^2 + l_2^2}}$$

- (i) For the pair of planes with Miller indices [1 0 1] and [0 1 0],

$$\cos \theta = \frac{0+0+0}{\sqrt{2}\sqrt{1}} = 0 \Rightarrow \theta = 90^\circ$$


- (ii) For the pair of planes with Miller indices [2 1 1] and [1 0 1],

$$\cos \theta = \frac{2+0+1}{\sqrt{4+1+1}\sqrt{1+0+1}} = \frac{3}{\sqrt{6}\sqrt{2}}$$

$$\cos \theta = \frac{\sqrt{3}}{2} \Rightarrow \theta = 30^\circ$$

End of Solution

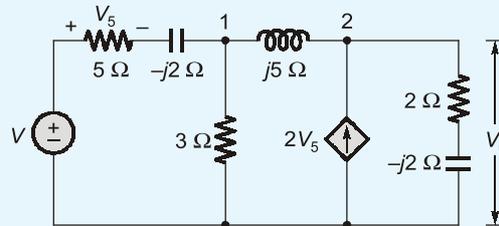
- Q.1** (d) For the circuit shown in the figure, calculate the value of the voltage  $V$  which gives  $V_0 = 5\angle 0^\circ$  volts :



[12 marks : 2025]

**Solution:**

We have,

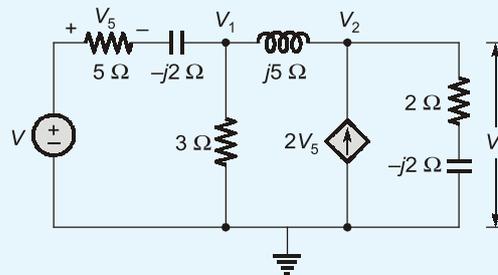

On applying KCL at node 1, we get,

$$\frac{V_1 - V}{5 - j2} + \frac{V_1}{3} + \frac{V_1 - V_2}{j5} = 0 \quad [\because V_2 = V_0 = 5 \angle 0^\circ]$$

$$V_1 \left[ \frac{1}{5 - j2} + \frac{1}{3} + \frac{1}{j5} \right] - \frac{V}{(5 - j2)} = \frac{5}{j5}$$

$$0.52 \angle -14.52^\circ V_1 - 0.186 \angle 21.80^\circ = 1 \angle -90^\circ \quad \dots(1)$$

On applying KCL at node 2, we get

$$\frac{V_2 - V_1}{j5} + \frac{V_2}{(2 - j2)} = 2V_5$$

where,  $V_5 = \left[ \frac{(V - V_1)}{5 - 2j} \times 5 \right]$

Thus,  $\frac{V_2 - V_1}{j5} + \frac{V_2}{2 - j2} = 2 \left[ \frac{5(V - V_1)}{(5 - 2j)} \right]$

$$\frac{V_2 - V_1}{j5} + \frac{V_2}{2 - j2} = \frac{10V}{5 - 2j} - \frac{10V_1}{(5 - 2j)}$$

Substituting  $V_2 = V_0 = 5 \angle 0^\circ$ , we have

$$V_1 \left[ \frac{-1}{j5} + \frac{10}{5 - 2j} \right] - \frac{10V}{(5 - 2j)} = \left[ \frac{-1}{2 - j2} - \frac{1}{j5} \right] 5 \angle 0^\circ$$

$$(1.94 \angle 27.29^\circ) V_1 - 1.86 \angle 21.80^\circ = 1.27 \angle -168.69^\circ \quad \dots(2)$$

Using Carson's rule, we get


$$V = \frac{\begin{vmatrix} 0.52 \angle -14.52^\circ & 1 \angle -90^\circ \\ 1.94 \angle 27.29^\circ & 1.27 \angle -168.69^\circ \end{vmatrix}}{\begin{vmatrix} 0.52 \angle -14.52^\circ & -0.186 \angle 21.80^\circ \\ 1.94 \angle 27.29^\circ & -1.86 \angle 21.80^\circ \end{vmatrix}}$$

$$V = \frac{0.66 \angle -183.21^\circ - 1.94 \angle -62.71^\circ}{-0.9672 \angle 7.28^\circ + 0.36 \angle 49.09^\circ}$$

$$= \frac{-1.55 + j1.76}{-0.72 + j0.15} = 3.19 \angle -36.86^\circ \text{V}$$

End of Solution

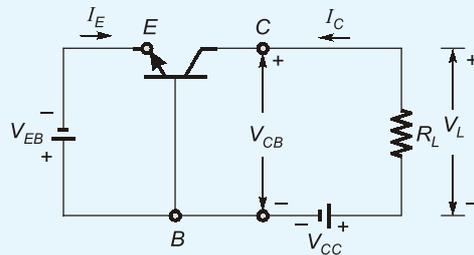**Q.1** (e) Shown below is an *n-p-n* transistor biased in the active region:




Assume that the emitter is much more heavily doped than the base.

- (i) Plot the potential variation across the emitter and collector junction.
- (ii) Plot the minority carrier concentration in each section of the transistor.
- (iii) Show how this transistor configuration works as an amplifier.
- (iv) Plot the collector current against base to emitter voltage for a silicon transistor when it is varied from  $-0.4$  V to  $+0.8$  V. Indicate the cutoff, active and saturation regions.
- (v) From the transistor characteristics, write the analytical expressions for the collector current and the emitter current.
- (vi) Show how these equations are used to replace the *n-p-n* transistor with two back diodes in shunt with two dependent current sources.


[12 marks : 2025]

**Solution:**

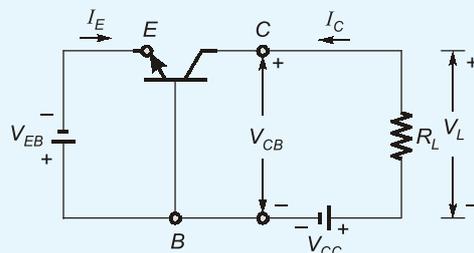


Given, emitter is much more heavily doped than the base.

- (i) It is given that the transistor is biased in active region i.e. emitter – base junction is forward biased and collector – base junction is reverse biased. The reverse biasing of the collector junction increases the collector – base barrier by  $|V_{CB}|$ , and forward biasing of the emitter junction lowers the emitter base barrier by  $|V_{EB}|$ . Since E-B junction is forward biased, the E-B space charge region width is negligible and due to reverse-biased C-B junction, the E-B space charge region width is increased. Thus, the potential variation across the transistor is as shown below,

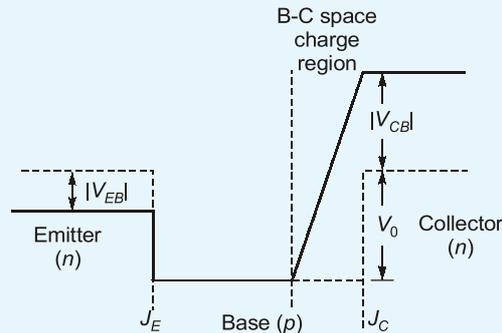

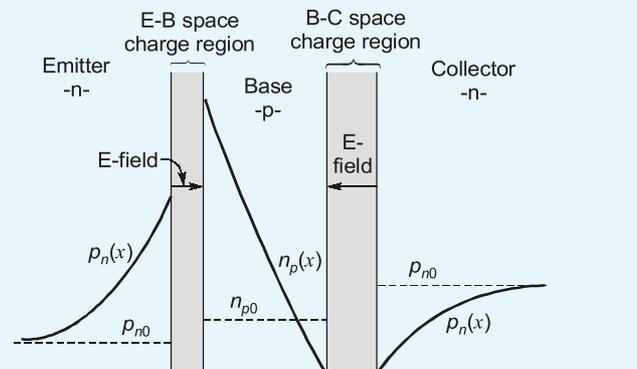(ii) **Minority carrier concentration in each section of the transistor:**

- The quantities  $p_{n0}$  and  $n_{p0}$  gives the thermal equilibrium concentration of the holes and electrons respectively. The emitter doping being much higher, the value of  $p_{n0}$  in the emitter is less than  $n_{p0}$  in the base.
- Since the E-B junction is forward biased, the holes are injected into the emitter and electrons are injected into the base. This injection causes the minority carrier concentration at the junction - holes in the emitter and electrons in the base - to increase slightly above its thermal equilibrium value. The concentration of these minority carriers decreases away from the junction, towards their respective thermal equilibrium values.
- Since the C-B junction is reverse biased, the minority carriers i.e. holes from collector and electrons from base drift across the junction. Therefore, the concentration of minority carriers—electrons in the base and holes in the collector is approximately zero at the C-B junction and increases away from it, towards their respective thermal equilibrium values.




- (iii) Forward biasing E-B junction injects electrons into the base. Because the base is thin and lightly doped, most injected electrons diffuse across the junction and are collected by the reverse-biased C-B depletion region contributing to collector current. Thus, a small change in  $V_{BE}$  causes an exponential change in collector current:

$$I_C \approx I_S e^{V_{BE}/V_T} \quad (\text{Forward active}).$$

This change in current can be converted into a large voltage change across a load resistor, resulting in voltage amplification.

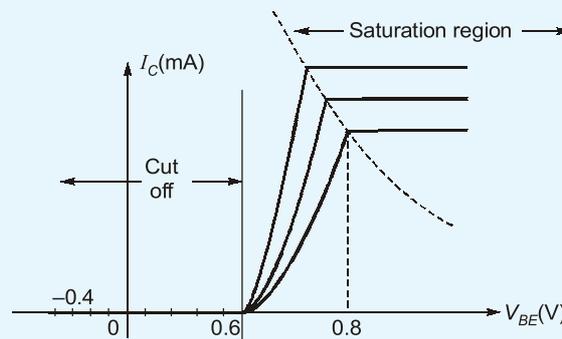- (iv) The  $I_C$  vs  $V_{CE}$  characteristics of the transistor is as shown below,
- (a) **Cut-off region:** When the base-emitter voltage ( $V_{BE}$ ) is less than the “cut-in voltage” (approximately 0.6 V), the transistor is in the cut-off region and the collector current is zero.
  - (b) **Active region:** As  $V_{BE}$  increases beyond the cut-in voltage, a small increase in  $V_{BE}$  leads to an exponential increase in the base current ( $I_B$ ), which in turn causes an increase in the collector current ( $I_C$ ). In this region, the collector current is proportional to the base current i.e.  $I_C = \beta I_B$ .
  - (c) **Saturation region:** When  $V_{BE}$  is increased further (around 0.8 V), the transistor enters the saturation region. In this state, both the emitter-base and collector-base junctions become forward-biased leading to a saturation in the collector current.



- (v) Analytical expressions for collector current and emitter current:  
Let  $I_{ES}$  and  $I_{CS}$  be the E-B and C-B diode saturation currents, and  $\alpha_F$  and  $\alpha_R$  are the forward and reverse common-base transport factors ( $\alpha_F \leq 1$ ,  $\alpha_R \ll \alpha_F$  because the emitter is much more heavily doped). Using the Ebers-Moll model, the collector and emitter current is given by

$$I_C = -I_{CS} \left( e^{V_{BC}/V_T} - 1 \right) + \alpha_F I_{ES} \left( e^{V_{BE}/V_T} - 1 \right),$$


$$I_E = I_{ES} \left( e^{V_{BE}/V_T} - 1 \right) - \alpha_R I_{CS} \left( e^{V_{BC}/V_T} - 1 \right),$$

$$I_B = I_E - I_C$$

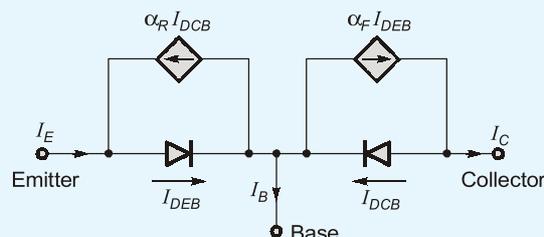- (vi) Using the analytical equations obtained in part (v), the transistor can be analyzed as a two back-to-back diodes connected in series along with two dependent current sources in shunt with the diode as shown below:

$$I_{DEB} = I_{ES} \left( e^{V_{BE}/V_T} - 1 \right)$$

$$I_{DCB} = I_{CS} \left( e^{V_{BC}/V_T} - 1 \right)$$



- Two current sources in shunt model transistor action (carrier transport across the base):
  - (i) A source from emitter to collector of value  $\alpha_F I_{DEB}$  (controlled by E-B diode current).
  - (ii) A source from collector to emitter of value  $\alpha_R I_{DCB}$  (controlled by the C-B diode current).
- ∴ The two diodes account for the junction currents themselves; and the two controlled sources “transfer” a fraction ( $\alpha_F, \alpha_R$ ) of one junction’s injected carriers to the other terminal.

**End of Solution**

- Q.2** (a) (i) The magnetic field of the earth is approximately  $3 \times 10^{-5}$  T (tesla). At what distance from a long-distance wire carrying a steady current of 10 A is the field equal to 10 percent of the earth’s field? Suggest at least two ways to help reduce the effect of electric circuits on the navigation compass in a boat or an airplane.

[12 marks : 2025]

- (ii) A typical deep cycle battery (used for electric trolling motors for fishing boats) is capable of delivering 12.6 V and 10 A for a period of 10 hours. How much charge flows through the battery in this interval? How much energy does the battery deliver?

[8 marks : 2025]

**Solution:**

- (i) Given, Magnetic field,  $B_{\text{earth}} = 3 \times 10^{-5}$  T  
Current,  $I = 10$  A

The magnetic field around an infinitely long, straight wire carrying a current ( $I$ ) at a distance ‘ $r$ ’ is given by

$$B = \frac{\mu_0 I}{2\pi r}$$

where,  $\mu_0 = 4\pi \times 10^{-7}$  H/m

Let ‘ $r$ ’ be the distance from the wire at which the field ‘ $B$ ’ is equal to 10 percent of the earth’s field i.e.  $B = 0.1 B_{\text{earth}}$

$$\begin{aligned} \therefore r &= \frac{\mu_0 I}{2\pi \times B} \\ &= \frac{4\pi \times 10^{-7} \times 10}{2\pi \times 3 \times 10^{-6}} \\ r &= 0.67 \text{ m} \end{aligned}$$

The following ways can be used to reduce the effect of electric circuits on the navigation compass in a boat or an airplane:

1. Increase the distance between the compass and electric circuits/wiring.
2. Use magnetic shielding (soft iron or mu-metal) around sensitive instruments.
3. Twist current-carrying wires together to reduce net magnetic field.
4. Route cables symmetrically to cancel fields.



**Live-Online**

## **General Studies & Engineering Aptitude for ESE 2026 Prelims (Paper-I)**

- ✓ Course duration approx. 3 Months.
- ✓ 200 Hrs of comprehensive classes.
- ✓ Teaching pedagogy similar to the classroom course.
- ✓ Study material will be provided.
- ✓ **Streams** : CE, ME, EE, E&T



### **Total 8 Subjects are covered**

(Engineering Maths and Reasoning Aptitude will not be covered)

- ✓ Current Affairs
- ✓ General Principles of Design, Drawing & Safety
- ✓ Standards and Quality Practices in Production, Construction, Maintenance and Services
- ✓ Basics of Energy and Environment
- ✓ Basics of Project Management
- ✓ Basics of Material Science and Engineering
- ✓ Information and Communication Technologies
- ✓ Ethics and values in Engineering Profession

Batches commenced from  
**25 Aug 2025**



**Scan to enroll**

- (ii) Given, Battery voltage,  $V = 12.6 \text{ V}$   
Current,  $I = 10 \text{ A}$   
Time,  $t = 10 \text{ hours}$

Charge flow through battery,

$$Q = I \times t$$

$$= 10 \times 10 \times 3600$$

$$= 360000 \text{ C}$$

$\therefore Q = 3.6 \times 10^5 \text{ C}$

Energy delivered by battery,

$$E = V \times I \times t$$

$$= 12.6 \times 10 \times 36000 \text{ s}$$

$$E = 4.54 \text{ MJ}$$

(or) 
$$E = \frac{4.54 \times 10^6}{3.6 \times 10^6} \approx 1.26 \text{ kWh}$$

End of Solution

- Q2** (b) During a laboratory experiment, a student tried to build an inverting amplifier as shown in Fig. (i). The student accidentally reversed the connection of the two input terminals and obtained the circuit of Fig. (ii). The student was greatly surprised that the circuit no longer behaved as expected. Calculate the gain in both the cases and explain the stability of both the circuits. Assume open-loop gain of op-amp as  $2 \times 10^5$ ,  $R_i = \infty$ ,  $R_o = 0$  and stray capacitance of  $1 \text{ pF}$  across the input terminals :

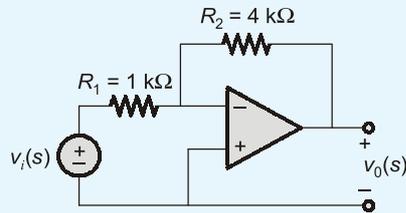


Fig. (i)


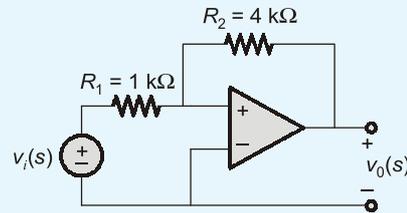


Fig. (ii)

[20 marks : 2025]

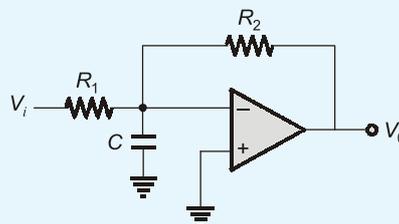**Solution:**

Considering the circuit given in Fig. (i),



For an op-amp,

$$V_o = A_{OL}(V^+ - V^-)$$

$$V_o = A_{OL}(0 - V^-)$$

$$V_o = -A_{OL} \times V^-$$

$$V^- = \frac{-V_o}{A_{OL}} \quad \dots(1)$$

Applying KCL at the inverting terminal,

$$(V_i - V^-)G_1 + (V_0 - V^-)G_2 + (0 - V^-)sC = 0, \text{ where } G_1 = \frac{1}{R_1} \text{ and } G_2 = \frac{1}{R_2}$$

$$V_i G_1 + V_0 G_2 - V^-(G_1 + G_2 + sC) = 0$$

$$V_i G_1 + V_0 G_2 + \frac{V_0}{A_{OL}}(G_1 + G_2 + sC) = 0 \quad \dots \text{using equation (1)}$$

$$V_0 \left[ G_2 + \frac{G_1 + G_2 + sC}{A_{OL}} \right] = -V_i G_1$$

$$\frac{V_0}{V_i} = \frac{-G_1}{G_2 + \frac{G_1 + G_2 + sC}{A_{OL}}}$$

$$A_{CL} = \frac{-G_1 \times A_{OL}}{G_1 + G_2(1 + A_{OL}) + sC}$$

The transfer function has a pole at,

$$s = \frac{-[G_1 + G_2(1 + A_{OL})]}{C}$$

$$s = \frac{-[1 + 0.25(1 + 2 \times 10^5)] \times 10^{-3}}{1 \times 10^{-12}}$$


$$s = -5 \times 10^{13} \text{ rad/sec}$$

Thus, the pole lie in the left half of s-plane. So, the above circuit is stable.

We can write,

$$A_{CL} = \frac{-4}{1 + \frac{s}{5 \times 10^{13}}}$$

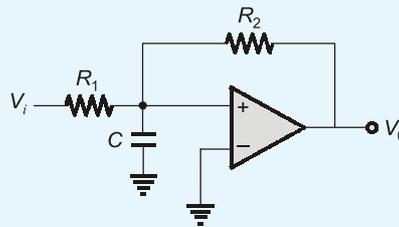Considering the circuit given in Fig. (ii),



$$V_0 = A_{OL}(V^+ - V^-)$$

$$V_0 = A_{OL}V^+$$

$$V^+ = \frac{V_0}{A_{OL}} \quad \dots(1)$$

Applying KCL at the non-inverting terminal,

$$(V_i - V^+)G_1 + (0 - V^+)sC + (V_0 - V^+)G_2 = 0$$

$$V_i G_1 - V^+(G_1 + G_2 + sC) + V_0 G_2 = 0$$

$$V_i G_1 - \frac{V_0}{A_{OL}}(G_1 + G_2 + sC) + V_0 G_2 = 0$$

$$V_0 \left[ \frac{G_1 + G_2 + sC}{A_{OL}} - G_2 \right] = V_i G_1$$

$$\frac{V_0}{V_i} = \frac{G_1}{\frac{G_1 + G_2 + sC}{A_{OL}} - G_2}$$

$$A_{CL} = \frac{G_1 \times A_{OL}}{G_1 + G_2(1 - A_{OL}) + sC}$$

Above circuit has pole at,

$$s = \frac{-[G_1 + G_2(1 - A_{OL})]}{C}$$

$$s = \frac{-[1 + 0.25(1 - 2 \times 10^5)] \times 10^{-3}}{1 \times 10^{-12}}$$

$$s = 5 \times 10^{13} \text{ rad/sec}$$

Thus, the pole lie in the right half of s-plane. So, the above circuit is not stable.

We can write,

$$A_{CL} = \frac{-4}{1 - \frac{s}{5 \times 10^{13}}}$$

End of Solution

**Q2** (c) The state equation of a linear time-invariant system is expressed by

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} [r(t)]$$

(i) Calculate the state transition matrix.

(ii) Find the state vector  $x(t)$  for  $t \geq 0$ , when  $r(t) = u(t)$ .

Assume the initial state to be zero.

[10 + 10 = 20 marks : 2025]

**Solution:**

Given, 
$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} r(t) = Ax + Bu$$

(i) The state transition matrix:

$$\phi(t) = L^{-1}[sI - A]^{-1} \quad \dots(1)$$

Here,

$$[sI - A] = s \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} = \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix}$$

$$[sI - A] = \begin{bmatrix} s & -1 \\ 1 & s+2 \end{bmatrix}$$

$$[sI - A]^{-1} = \frac{\text{Adj}[sI - A]}{|sI - A|} = \frac{\begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix}}{(s(s+2)+1)}$$

$$[sI - A]^{-1} = \frac{\begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix}}{(s^2 + 2s + 1)} = \frac{\begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix}}{(s+1)^2}$$

$$\therefore L^{-1}[sI - A]^{-1} = L^{-1} \begin{bmatrix} \frac{s+1}{(s+1)^2} + \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s+1-1}{(s+1)^2} \end{bmatrix}$$

$$\Rightarrow \phi(t) = L^{-1} \begin{bmatrix} \frac{1}{(s+1)} + \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{1}{(s+1)} - \frac{1}{(s+1)^2} \end{bmatrix}$$

$$\phi(t) = \begin{bmatrix} (e^{-t} + te^{-t})u(t) & te^{-t}u(t) \\ -te^{-t}u(t) & (e^{-t} - te^{-t})u(t) \end{bmatrix}$$

(ii) State vector  $x(t)$  for  $t \geq 0$ , when  $r(t) = u(t)$ :

We know,

$$X(s) = [sI - A]^{-1}[x(0) + BU(s)]$$

Given,

$$x(0) = 0$$

$\therefore$

$$X(s) = [sI - A]^{-1} BU(s)$$

$$= \begin{bmatrix} \frac{s+2}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s}{(s+1)^2} \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} \begin{bmatrix} 1 \\ s \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{(s+1)^2} \\ \frac{s}{(s+1)^2} \end{bmatrix} \begin{bmatrix} 1 \\ s \end{bmatrix} = \begin{bmatrix} \frac{1}{s(s+1)^2} \\ \frac{1}{(s+1)^2} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{s} - \frac{1}{(s+1)} - \frac{1}{(s+1)^2} \\ \frac{1}{(s+1)^2} \end{bmatrix}$$


Take inverse Laplace transform on both sides,

$$x(t) = \begin{bmatrix} (1 - e^{-t} - te^{-t})u(t) \\ te^{-t}u(t) \end{bmatrix}$$

End of Solution

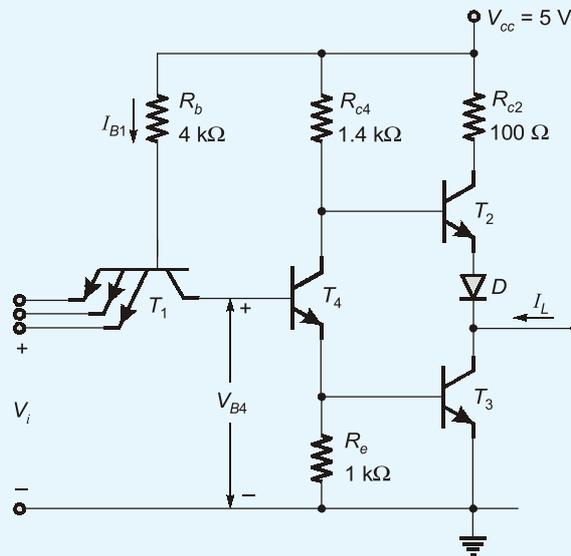**Q.3** (a) Explain the operation of the TTL gate circuit shown below, clearly mentioning the roles of the transistors  $T_2$  and  $T_4$ , and the diode  $D$ .

Assume that when all the inputs are at logic 1, the transistors  $T_3$  and  $T_4$  are both in saturation :



[20 marks : 2025]

**Solution:**

The given TTL gate represents a NAND Gate with totem-pole output.

The totem pole configuration have three stages:

1. Multi-emitter input stage
2. Phase shift stage
3. Totem pole/Active pull-up stage

If any one of the input is LOW or all the inputs are LOW, then the corresponding emitter base junction of transistor  $T_1$  becomes forward biased causing  $V_{B1} = 0.2 + 0.8 = 1\text{ V}$  and collector base junction becomes reverse biased (i.e.  $T_1$  is in active region), and as a result  $T_4$  and  $T_3$  are turned off. The voltage  $V_{C4}$  rises and causes  $T_2$  and diode  $D$  to be turned ON and hence  $Y = \text{HIGH}$ .

Now, if all the inputs are HIGH, the emitter base junction of transistor  $T_1$  is reverse biased and  $V_{B1}$  approaches to  $V_{CC}$ , which causes  $T_4$  and  $T_3$  to go into deep saturation. As  $T_3$  is in saturation, the transistor  $T_2$  and diode  $D$  goes to cutoff state. Therefore output  $Y = \text{LOW}$ .

**Operation:**

TTL NAND gate:

When all inputs ( $A, B, C$ ) are high, the  $BE$  junction of  $T_1$  will be reverse biased but  $BC$  junction of  $T_1$  will be forward biased. Current will flow from  $C_1$  to  $B_4$ . This will turn on  $T_4$  and thus  $T_3$ . Due to  $T_3$  being on, output  $Y$  will be zero.

When one or more of the inputs is low,  $BE$  will be forward biased and  $T_1$  will turn on. This will lead to  $T_4$  and  $T_3$  being turned off and  $Y$  will be logic 1.

A	B	C	$T_1$	$T_4$	$T_3$	$T_2$	Y
0	0	0	Active	Cut-off	Cut-off	Saturation	High
0	0	1	Active	Cut-off	Cut-off	Saturation	High
0	1	0	Active	Cut-off	Cut-off	Saturation	High
0	1	1	Active	Cut-off	Cut-off	Saturation	High
1	0	0	Active	Cut-off	Cut-off	Saturation	High
1	0	1	Active	Cut-off	Cut-off	Saturation	High
1	1	0	Active	Cut-off	Cut-off	Saturation	High
1	1	1	Inverse Active	Saturation	Saturation	Cut-off	Low

Here, transistor  $T_4$  is the pull-down transistor, sinking current to create a logic LOW output when conducting.  $T_3$  is the pull-up transistor, sourcing current to create a logic HIGH output when  $T_4$  is off. The purpose of using diode  $D$  is to ensure that the transistor  $T_2$  is off, when  $T_3$  is ON. In its absence,  $T_2$  would go into saturation causing power loss.

**End of Solution**

**Q3** (b) (i) A thermistor, having  $\beta = 3100\text{K}$ , has a resistance of  $1050\ \Omega$  at  $20^\circ\text{C}$ . The thermistor is used for the measurement of temperature and the resistance measured is  $2300\ \Omega$ . Find the measured temperature if the thermistor is

described by the relation  $R = R_0 \exp\left[\beta\left(\frac{1}{T} - \frac{1}{T_0}\right)\right]$  where the symbols have their standard meanings.

[10 marks : 2025]

(ii) The following are the data for a Hay's bridge :

$$R_1 = 1\ \text{k}\Omega \pm 1\ \text{part in } 10\ \text{K}, \quad R_2 = 16.8\ \text{k}\Omega \pm 1\ \text{part in } 10\ \text{K},$$

$$R_3 = 833 \pm 0.25\ \Omega, \quad C = 1.43 \pm 0.001\ \mu\text{F}$$

The supply frequency is  $50 \pm 0.1\ \text{Hz}$  and the bridge's balanced conditions are

$$L = \frac{CR_1R_2}{1 + \omega^2C^2R_3^2} \quad \text{and} \quad R = \frac{R_1R_2R_3C^2\omega^2}{1 + \omega^2C^2R_3^2}$$

Calculate the values of  $L$  and  $R$  of the coil, and their limits of error.

[10 marks : 2025]

**Solution:**

(i) Given,  $\beta = 3100\ \text{K}$

$$R_0 = 1050\ \Omega \text{ at } T_0 = 20^\circ\text{C} = 273 + 20 = 293\ \text{K}$$

$$\text{Measured } R = 2300\ \Omega$$

It is given that the resistance of thermistor varies with temperature as,

$$R = R_0 \left( \exp\left[\beta\left(\frac{1}{T} - \frac{1}{T_0}\right)\right] \right)$$

$$\frac{R}{R_0} = \exp\left[\beta\left(\frac{1}{T} - \frac{1}{T_0}\right)\right]$$



# Live-Online Course for **GENERAL STUDIES** for State Engineering and SSC Exams

Full Fledged Course for General Studies

**Subject Covered :** History, General Science, Polity, Environment, Geography, General Knowledge, Economy & Current Affairs

**Duration :** 3 Months | **Validity :** Till 31<sup>st</sup> Dec 2025

Batch commencing from

**1<sup>st</sup> Sept, 2025** (8 AM - 11:30 AM) | **25<sup>st</sup> Sept, 2025** (6 PM - 9:30 PM)

## Key Features

- ✓ 250 Hrs of quality teaching by renowned teachers of MADE EASY.
- ✓ Printed study material will be dispatched to your address.
- ✓ Comprehensive coverage as per latest syllabus and trends of various competitive exams.



Scan to enroll

$$\ln\left[\frac{R}{R_0}\right] = \beta\left[\frac{1}{T} - \frac{1}{T_0}\right]$$

Substituting the given values,

$$\ln\left[\frac{2300}{1050}\right] = 3100\left[\frac{1}{T} - \frac{1}{293}\right]$$

$$T \approx 272.8 \text{ K}$$

Convert to °C

$$T = 272.8 - 273 \Rightarrow T = -0.2^\circ\text{C}$$

(ii) Given,

$$R_1 = 1 \text{ k}\Omega \pm (1/10000) \times 100\%$$

$$= 1 \text{ k}\Omega \pm 0.01\%$$

$$= 1 \text{ k}\Omega \pm 0.1 \Omega$$

$$R_2 = 1.68 \text{ k}\Omega \pm (1/10000) \times 100\%$$

$$= 1.68 \text{ k}\Omega \pm 0.01\%$$

$$= 16800 \pm 1.68 \Omega$$

$$R_3 = 833 \pm 0.25 \Omega$$

$$C = 1.43 \pm 0.001 \mu\text{F}$$

$$f = 50 \pm 0.1 \text{ Hz}$$

From the given expressions, the values of  $R$  and  $L$  of the coil can be calculated as below,

$$L = \frac{CR_1R_2}{1 + \omega^2C^2R_3^2}; \quad R = \frac{R_1R_2R_3C^2\omega^2}{1 + \omega^2C^2R_3^2}$$

$$L = \frac{(1.43 \times 10^{-6}) \times 1000 \times 16800}{1 + (2\pi(50))^2 \cdot (1.43 \times 10^{-6})^2 (833)^2} = 21.07 \text{ H}$$

$$R = \frac{(1000)(16800)(833)(1.43 \times 10^{-6})^2 (2\pi \times 50)^2}{1 + (2\pi(50))^2 \cdot (1.43 \times 10^{-6})^2 \cdot (833)^2}$$

$$R = 2477.54 \Omega$$

The relative error for various parameters can be determined as below,

Parameter	Value	Tolerance given	Relative error (fraction)
$R_1$	1000 $\Omega$	$\pm 1$ Part in 10,000	0.0001 (0.01%)
$R_2$	16800 $\Omega$	$\pm 1$ Part in 10,000	0.0001 (0.01%)
$R_3$	833 $\Omega$	$\pm 0.25 \Omega$	0.0003 (0.03%)
$C$	$1.43 \times 10^{-6}$	$\pm 0.001 \mu\text{F}$	0.0007 (0.07%)
$f$	50	$\pm 0.1 \text{ Hz}$	0.002 (0.2%)

We have, 
$$L = \frac{CR_1R_2}{1 + \omega^2C^2R_3^2}, \quad R = \frac{R_1R_2R_3C^2\omega^2}{1 + \omega^2C^2R_3^2}$$

Assume, 
$$D = 1 + \omega^2C^2R_3^2$$

We have, 
$$\omega^2C^2R_3^2 = 0.13984$$

$$D = 1 + \omega^2C^2R_3^2 = 1.13984$$

Relative Error in  $D$ :

$$D = 1 + X; \text{ where } X = \omega^2 C^2 R_3^2$$

$$\begin{aligned} \frac{\Delta X}{X} &= \frac{2\Delta\omega}{\omega} + \frac{2\Delta C}{C} + \frac{2\Delta R_3}{R_3} \\ &= \pm[2(0.002) + 2(0.0007) + 2(0.0003)] \\ &= \pm 0.0060 \text{ (or) } \pm 0.6\% \end{aligned}$$

Absolute change in  $D$ :

$$\begin{aligned} \Delta D &= \Delta X \text{ (since 1 is constant)} \\ \Delta D &= X * 0.0060 = \pm 0.13984 * 0.0060 = \pm 0.000839 \end{aligned}$$

Relative error in  $D$ :

$$\begin{aligned} \frac{\Delta D}{D} &= \pm \frac{0.000839}{1.13984} \approx \pm 0.000737 \\ &= \pm 0.0737\% \end{aligned}$$

Relative error in  $L$ :

$$\begin{aligned} L &= \frac{CR_1R_2}{D} \\ \frac{\Delta L}{L} &= \frac{\Delta C}{C} + \frac{\Delta R_1}{R_1} + \frac{\Delta R_2}{R_2} + \frac{\Delta D}{D} \\ &= \pm(0.0007 + 0.0001 + 0.0001 + 0.000737) \\ &= \pm 0.001637 \text{ (or) } \pm 0.1637\% \\ \Delta L &= \pm 21.07 \times 0.001637 = \pm 0.0345 \text{ H} \end{aligned}$$

Relative error in  $R$ :

$$\begin{aligned} R &= \frac{R_1R_2R_3C^2\omega^2}{D} \\ \frac{\Delta R}{R} &= \frac{\Delta R_1}{R_1} + \frac{\Delta R_2}{R_2} + \frac{\Delta R_3}{R_3} + \frac{2\Delta C}{C} + \frac{2\Delta\omega}{\omega} + \frac{\Delta D}{D} \\ \frac{\Delta R}{R} &= \pm(0.0001 + 0.0001 + 0.0003 + 0.0014 \\ &\quad + 0.0040 + 0.000737) \end{aligned}$$


$$\begin{aligned} \frac{\Delta R}{R} &= \pm 0.006637 \\ \Delta R &= \pm 0.006637 \times 2477.54 \\ \Delta R &= \pm 16.44 \Omega \end{aligned}$$

Thus, we get

$$\begin{aligned} L &= 21.07 \pm 0.0345 \text{ H} \\ R &= 2477.54 \pm 16.44 \Omega \end{aligned}$$

End of Solution

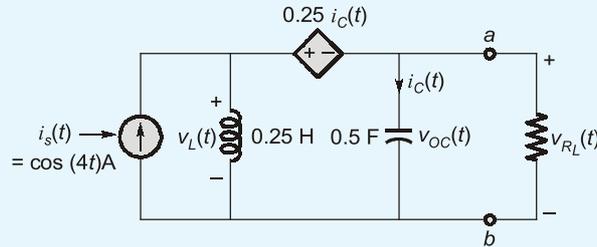- Q3** (c) Find the Thevenin's equivalent of the circuit shown in the figure if  $\omega = 4$  rad/s. Also determine the voltage  $v_{R_L}(t)$ , when a  $1.2 \Omega$  load is connected to terminals a-b:



[20 marks : 2025]


**Solution:**

**Step I: Thevenin Voltage,  $V_{th}$ :** To calculate Thevenin voltage across  $a-b$ , we remove the load resistance. The circuit can thus be drawn as below,

For  $\omega = 4$  rad/sec

$$X_C = \frac{1}{j\omega C} = \frac{1}{j4 \times 0.5} = -j0.5 \Omega$$
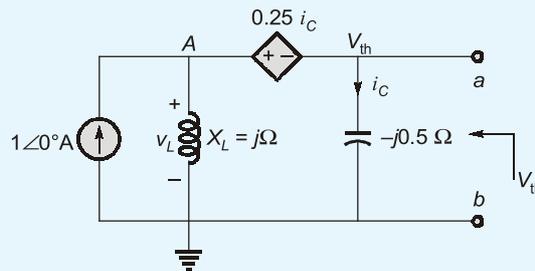
$$X_L = j\omega L = j4 \times 0.25 = j1 \Omega$$



$$V_A - V_{th} = 0.25 i_c$$

$$V_A - V_{th} = 0.25 \left( \frac{V_{th}}{-j0.5} \right)$$

$$V_A = V_{th} \left[ 1 - \frac{0.25}{j0.5} \right]$$

$$V_A = [1.11 \angle 26.56^\circ] V_{th} \quad \dots(1)$$

Applying KCL at node A,


$$\frac{V_A}{j} + \frac{V_{th}}{-j0.5} = 1 \quad \dots(2)$$

Using (1) in (2), we get

$$\frac{1.11 \angle 26.56^\circ V_{th}}{j} + \frac{V_{th}}{-j0.5} = 1$$

$$V_{th} = 0.89 \angle -63.43^\circ \text{ Volt}$$

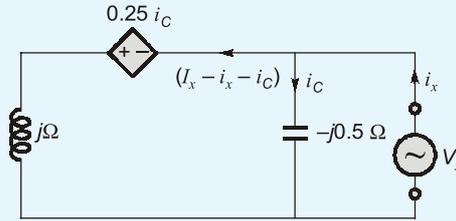**Step II:  $Z_{th}$ :** To calculate  $Z_{th}$ , the independent current source is open-circuited and we connect a voltage source  $V_x$  as shown below,



Using KCL, we can write

$$\frac{V_x}{-j0.5} + \frac{V_x + 0.25i_c}{j} = i_x$$


$$\frac{V_x}{-j0.5} + \frac{V_x + 0.25\left(\frac{V_x}{-j0.5}\right)}{j} = i_x$$

$$V_x \left[ \frac{1}{-j0.5} + \frac{1}{j} + \frac{0.25}{j} \left( \frac{V_x}{-j0.5} \right) \right] = i_x$$


$$\frac{V_x}{i_x} = \frac{1}{\left[ \frac{1}{j} + \frac{1}{-j0.5} + 0.5 \right]}$$

$$Z_{th} = 0.89 \angle -63.43^\circ \Omega$$

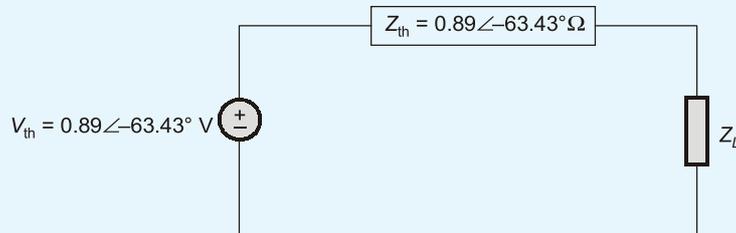**Step III:** Thevenin Equivalent Circuit



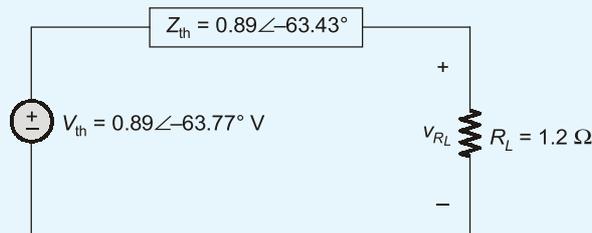**Step IV:** When  $Z_L = R_L = 1.2 \Omega$



$$V_{R_L} = \frac{[0.89 \angle -63.43^\circ](1.2)}{1.2 + 0.89 \angle -63.43^\circ}$$

$$V_{R_L} = 0.6 \angle -37^\circ \text{ volt}$$

$$V_{R_L}(t) = 0.6 \cos(4t - 37^\circ) \text{ volt}$$

Thus,

End of Solution

- Q.4 (a)** Consider that a double-heterojunction LED emitting at a peak wavelength 1400 nm has radiative and non-radiative recombination times of 20 ns and 80 ns respectively. The drive current is 30 mA and the refractive index of the light source material is 3.0. Calculate the power emitted from the device.

[20 marks : 2025]

**Solution:**

Given, wavelength,  $\lambda = 1400 \text{ nm} = 1.4 \times 10^{-6} \text{ m}$   
 Radiative lifetime,  $\tau_r = 20 \text{ nsec}$   
 Non radiative lifetime,  $\tau_{nr} = 80 \text{ nsec}$   
 Drive current,  $I = 30 \text{ mA}$   
 Refractive index,  $n = 3$

Power emitted by double-heterojunction LED is calculated by multiplying the external photon flux (number of photons per second) and the energy of the emitted photons.

$$P_{\text{out}} = N_{\text{photons}} \times E_{\text{photon}}$$

Quantum efficiency for light-emitting diodes (LEDs) is defined as the ratio of number of photons emitted to the number of electrons injected. Thus, we have

$$N_{\text{photons}} = \eta_{\text{total}} \times \frac{I}{q}$$

where the number of electrons per second

$$= \frac{I}{q} = \frac{0.03}{1.6 \times 10^{-19}} \approx 1.875 \times 10^{17} \text{ electrons/sec}$$

and quantum efficiency,  $\eta_{\text{total}} = \eta_{\text{int}} \times \eta_{\text{ext}}$

$$\text{Internal quantum efficiency, } \eta_{\text{int}} = \frac{1}{\left(\frac{1}{\tau_r}\right) + \left(\frac{1}{\tau_{nr}}\right)}$$

$$\eta_{\text{int}} = \frac{1}{\left(\frac{1}{20 \times 10^{-9}}\right) + \left(\frac{1}{80 \times 10^{-9}}\right)}$$

$$\eta_{\text{int}} = 0.8$$

For an LED with refractive index  $n$ , the external quantum efficiency is given by

$$\eta_{\text{ext}} \approx \frac{1}{n(n+1)^2} \approx \frac{1}{3 \times 4^2} = 0.0208$$

$$\therefore \eta_{\text{total}} = \eta_{\text{inter}} \times \eta_{\text{ext}} = 0.8 \times 0.0208 = 0.01664$$

$$\therefore N_{\text{photons}} = \eta_{\text{total}} \times \frac{I}{q} = 0.01664 \times 1.875 \times 10^{17} = 3.12 \times 10^{15} \text{ photons/sec}$$

Energy of a photon is given by

$$E_{\text{photon}} = \frac{hc}{\lambda} = \frac{(6.626 \times 10^{-34})(3 \times 10^8)}{1.4 \times 10^{-6}}$$

$$= 1.419 \times 10^{-19} \text{ J}$$

$$\therefore \text{Power emitted from LED, } P_{\text{out}} = 3.12 \times 10^{15} \times 1.419 \times 10^{-19}$$

$$P_{\text{out}} = 4.427 \times 10^{-4} \text{ W} \approx 0.44 \text{ mW}$$

End of Solution

**Q.4** (b) A spherical nanoparticle has diameter of 10 nm. Determine the surface area to volume ratio and explain how this property affects the behaviour of nanomaterials compared to bulk materials.

[20 marks : 2025]

**Solution:**

Given, diameter of a spherical nanoparticle

$$d = 10 \text{ nm}$$

$$\Rightarrow \text{Radius, } r = \frac{d}{2} = 5 \text{ nm}$$

$$\text{Surface area of nanoparticle, } S.A = 4\pi r^2$$

$$\text{Volume (V) of nanoparticle, } V = \frac{4}{3}\pi r^3$$

Surface area to volume ratio (SA/V)

$$= \frac{4\pi r^2}{\frac{4}{3}\pi r^3} = \frac{3}{r} = \frac{3}{5 \times 10^{-9}} = 0.6 \text{ nm}^{-1}$$

**Effect of SA/V on Nanomaterial behaviour:**

The high surface area to volume ratio in nanoparticles significantly alters their physical and chemical properties compared to bulk materials.

**1. Increased Reactivity**

- More atoms are exposed on the surface and surface atoms are less tightly bound.
- This leads to greater chemical reactivity useful in catalysis and sensors.

**2. Enhanced Mechanical Properties**

- Nanoparticles can be stronger or harder due to their surface effects.
- For example, nanomaterials can have higher tensile strength than bulk counter parts.

**3. Optical properties**

- Nanoparticles exhibit size-dependent optical behavior (quantum effects)
- Gold nanoparticles, for instance, change color based on size.

**4. Thermal and Electrical properties:**

- Conductivity and heat resistance can be different due to limited mean free paths for electrons and phonons.

**5. Biological Interactions:**

- Nanoparticles can easily penetrate cells and interact with biomolecules, important in drug delivery systems.

End of Solution





# GATE 2026 ONLINE TEST SERIES

**Streams:**  
CE, ME, EE, EC, CS, IN, PI, CH

## Tests are live

### Quality Questions

Thoroughly researched, quality questions as per standard & orientation of GATE consisting MCQs, NATs & MSQs

### GATE Interface

Test series interface is exactly similar to actual GATE

### Anywhere, Anytime

Facility to appear in test anywhere & anytime (24 x 7)

### Video Solution

Get video solutions by senior faculties for proper understanding of concepts

### Ask an Expert

Ask your doubt to our experts, Get answer of your queries on chat window

### Step by Step Solutions

Detailed, step by step and well illustrated solutions, For user's better understanding

### Smart Report

Comprehensive and detailed analysis of test-wise performance. Evaluate yourself and get All India Rank

### Virtual Calculator Embedded

Make yourself conversant in use of embedded virtual calculator

Available on android, iOS (Desktop & Laptop)



## 48 TESTS

1584 + Newly Designed Questions



Scan to enroll


Queries : 9021300500

[queryots@madeeasy.in](mailto:queryots@madeeasy.in)

Enroll now [www.madeeasy.in](http://www.madeeasy.in)

- Q.4** (c) (i) A CR tube has an anode-screen distance of 30 cm. The accelerating potential is 1 kV. The tube is placed with its axis vertical. Find the maximum deflection of the spot due to the earth's magnetic field having  $B = 0.018 \times 10^{-3} \text{ Wb/m}^2$ .  
[10 marks : 2025]

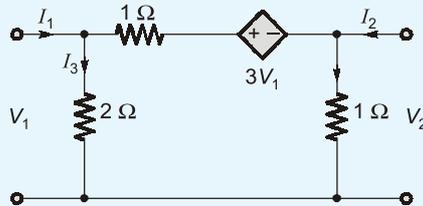
- (ii) Calculate the Y-parameters for the network shown in the figure :



[10 marks : 2025]

**Solution:**

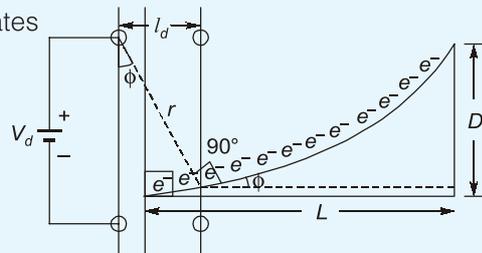- (i) Given for a CR tube,  
 $L = 30 \text{ cm}$ ,  $V_a = 1 \text{ kV}$ ,  $B = 0.018 \times 10^{-3} \text{ Wb/m}^2$   
 Let  $l_d =$  distance between the deflecting plates  
 $V_d =$  Applied potential difference across deflecting plates  
 $D =$  Deflection of the beam  
 $V_a =$  Accelerating potential  
 $B =$  Magnetic flux density  
 $L =$  distance between the centre of plates to the centre of screen



Due to the magnetic field, the electron beam moves along a circular arc. The force on the electrons due to magnetic field,  $Bev$  is equal to the centrifugal force i.e.

$$Bev = \frac{mv^2}{r} \Rightarrow r = \frac{mv}{Be} \quad \dots(i)$$

For an accelerating potential  $V$ , we have Gain in K.E. = Loss in P.E. i.e.

$$\frac{1}{2}mv^2 = qV_a \Rightarrow v = \sqrt{\frac{2qV_a}{m}} \quad \dots(ii)$$

From the given figure,

$$\tan \phi = \frac{D}{L}$$

We have,  $\phi = \frac{l_d}{r}$ . Since  $\phi$  is very small, thus  $\tan \phi \approx \phi$ . Thus, we get

$$\frac{D}{L} = \frac{l_d}{r}$$

Using equation (i), the magnetic deflection is given by

$$D = \frac{Ll_d Bq}{mv}$$

Using equation (ii), we get

$$D = L \cdot I_d \cdot B \sqrt{\frac{q}{2mV_a}}$$

where

$q$  = charge of electron =  $1.6 \times 10^{-19}$  Coulomb

$m$  = mass of electron =  $9.11 \times 10^{-31}$  kg

Substituting the given values, we get

$$\frac{D}{I_d} = 30 \times 10^{-2} \times 0.018 \times 10^{-3} \times \sqrt{\frac{1.6 \times 10^{-19}}{2 \times 9.11 \times 10^{-31} \times 1 \times 10^3}}$$


$$\frac{D}{I_d} = 0.54 \times 10^{-5} \times 0.29 \times \sqrt{10^{-19} \times 10^{28}}$$

$$= 0.1566 \times 10^{-5} \times \sqrt{10^9} = 0.1566 \times 10^{-5} \times 10^4 \times \sqrt{10}$$

$$\frac{D}{I_d} = 0.4952 \times 10^{-1} \Rightarrow \frac{D}{I_d} = 0.04952$$

For  $I_d = 1$  cm  $\Rightarrow$  Max. deflection =  $D_{\max} = 0.04952$  cm

(ii) We have,

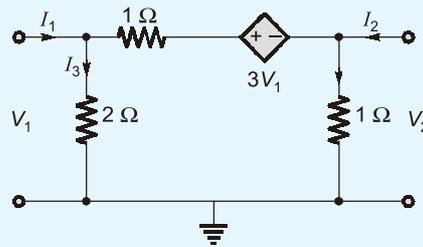

Applying KCL at node 1,

$$\frac{V_1}{2} + \frac{V_1 - 3V_1 - V_2}{1} = I_1$$

$$I_1 = -2V_1 + \frac{V_1}{2} - V_2$$

$$I_1 = \frac{-3V_1}{2} - V_2 \quad \dots(i)$$

Applying KCL at node 2,

$$\frac{V_2}{1} + V_2 + 3V_1 - V_1 = I_2$$

$$I_2 = +2V_1 + 2V_2 \quad \dots(ii)$$

Comparing equations (i) and (ii) with Y-parameter equations,

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

we get the y-parameters matrix as,

$$Y = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{-3}{2} \text{ } \Omega & -1 \text{ } \Omega \\ 2 \text{ } \Omega & 2 \text{ } \Omega \end{bmatrix}$$

End of Solution

**Section-B**

**Q.5** (a) Derive a relation for the value of the capacitor for frequency error compensation of a moving-iron voltmeter in terms of its parameters and the series resistance.

[12 marks : 2025]

**Solution:**


**Frequency errors:** Changes in frequency may cause errors due to changes of reactance of the working coil and also due to changes of magnitude of eddy currents set up in the metal parts of instrument.

**Reactance of instrument coil:** The change of reactance of the instrument coil is important in case of voltmeters where an additional resistance  $R_s$  is used in series with the instrument coil. Let the resistance and inductance of the instrument coil be  $R$  and  $L$ . Then the current  $I$  in the instrument coil for given applied voltage  $V$  is given by:

$$I = \frac{V}{\sqrt{(R + R_s)^2 + \omega^2 L^2}}$$

The deflection of the moving-iron voltmeter depends upon the current through the coil. Therefore, the deflection for a given voltage will be less at high frequencies than at low frequencies. To some extent, compensation to this type of error is possible by connecting a capacitor  $C$  across the series resistance  $R_s$  as shown in figure.

The idea of shunting the series resistor is to make the circuit behave like a pure resistance so that the frequency changes have no effect on the readings of the instrument. Thus, the compensated instrument will have a power factor nearly equal to unity. As the resistance of the meter,  $R$ , is considerably smaller than the series multiplier resistance  $R_s$ , it can be assumed that it is sufficient to ensure that the magnitude  $Z$  of the impedance of the circuit formed by  $L$ ,  $R_s$  and  $C$  has a value  $R_s$  when used on a.c.

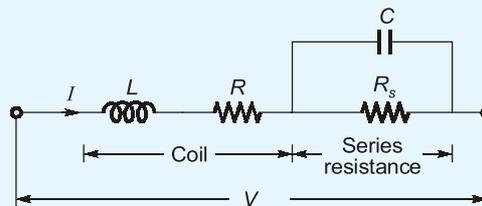

Now,

$$Z = j\omega L + \frac{R_s}{1 + j\omega C R_s}$$

$$= j\omega L + \frac{R_s - j\omega C R_s^2}{1 + \omega^2 C^2 R_s^2}$$

Since  $\omega C R_s \ll 1$ , we can write

$$Z = j\omega L + (R_s - j\omega C R_s^2)(1 - \omega^2 C^2 R_s^2)$$

$$= j\omega L + R_s - j\omega C R_s^2 - \omega^2 C^2 R_s^3 + j\omega^3 C^3 R_s^4$$

$$= R_s - \omega^2 C^2 R_s^3 + j[\omega L - \omega C R_s^2(1 - \omega^2 C^2 R_s^2)]$$

$$= R_s - \omega^2 C^2 R_s^3 + j[\omega L - \omega C R_s^2] \quad \dots \text{as } \omega^2 C^2 R_s^2 \ll 1$$

$$= R_s(1 - \omega^2 C^2 R_s^2) + j\omega(L - CR_s^2)$$

or

$$|Z|^2 = R_s^2(1 - \omega^2 C^2 R_s^2)^2 + \omega^2(L - CR_s^2)^2$$

This must equal  $R_s^2$  in order that the a.c. calibration at all frequencies and d.c. calibration is the same.

$\therefore$

$$\begin{aligned} R_s^2 &= R_s^2(1 - \omega^2 C^2 R_s^2)^2 + \omega^2(L - CR_s^2)^2 \\ &= R_s^2(1 - 2\omega^2 C^2 R_s^2 + \omega^4 C^4 R_s^4) + \omega^2(L - CR_s^2)^2 \\ &= R_s^2(1 - 2\omega^2 C^2 R_s^2) + \omega^2(L - CR_s^2)^2 \end{aligned}$$

$$\text{as } \omega^4 C^4 R_s^4 \ll 1$$

$$= R_s^2 - 2\omega^2 C^2 R_s^4 + \omega^2 L^2 + \omega^2 C^2 R_s^4 - 2\omega^2 LCR_s^2$$

or

$$L^2 - 2LCR_s^2 - C^2 R_s^4 = 0$$

or

$$L = \frac{2CR_s^2 + \sqrt{4C^2 R_s^4 + 4C^2 R_s^4}}{2} = 2.41CR_s^2$$


$\therefore$

$$C = \frac{1}{2.41} \frac{L}{R_s^2} = 0.41 \frac{L}{R_s^2}$$

End of Solution

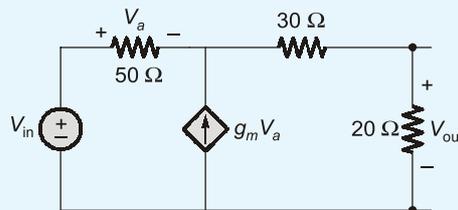**Q.5** (b) For the circuit shown in the figure, find  $\frac{V_{out}}{V_{in}}$  in terms of the parameter  $g_m$ . Then


find  $\frac{V_{out}}{V_{in}}$ , when  $g_m = 2$ :



[12 marks : 2025]

**Solution:**

Considering the given circuit,

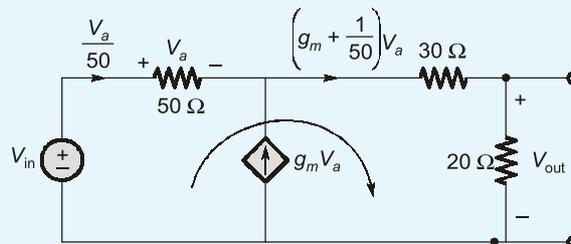

We have,

$$V_{out} = 20 \left[ g_m + \frac{1}{50} \right] V_a$$

$$V_{out} = \left[ 20g_m + \frac{2}{5} \right] V_a \quad \dots(i)$$

On applying KVL around the outer loop,

$$-V_{in} + V_a + 30 \left[ g_m + \frac{1}{50} \right] V_a + V_{out} = 0$$

$$-V_{in} + \left[ 1 + 30g_m + \frac{3}{5} \right] V_a + V_{out} = 0 \quad \dots(ii)$$

Substitute equation (i) in (ii),

$$-V_{in} + \left[ \frac{8}{5} + 30g_m \right] \left[ \frac{V_{out}}{20g_m + \frac{2}{5}} \right] + V_{out} = 0$$

$$-V_{in} + \left[ 1 + \frac{30g_m + \frac{8}{5}}{20g_m + \frac{2}{5}} \right] V_{out} = 0$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{1 + \left( \frac{30g_m + \frac{8}{5}}{20g_m + \frac{2}{5}} \right)} = \frac{1}{1 + \frac{150g_m + 8}{100g_m + 2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{100g_m + 2}{250g_m + 10}$$

For  $g_m = s$ ,


$$\frac{V_{out}}{V_{in}} = \frac{200 + 2}{500 + 10} = \frac{202}{510}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} \simeq 0.3961$$

**End of Solution**

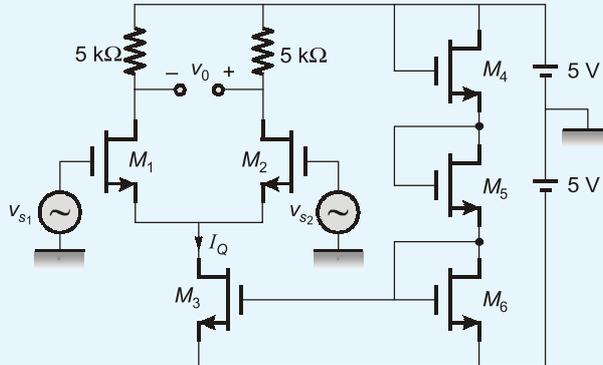**Q5** (c) For the circuit shown in the figure, all the MOSFETs are identical. Assume  $\mu_n C_{ox} = 0.1 \text{ mA/V}^2$ ,  $V_{tn} = 1 \text{ V}$ ,  $\lambda = 0$  and  $I_Q = 1 \text{ mA}$ . Calculate  $\frac{W}{L}$  ratio and voltage


$$\text{gain } A_d = \frac{V_0}{V_{s1} - V_{s2}} :$$



[12 marks : 2025]

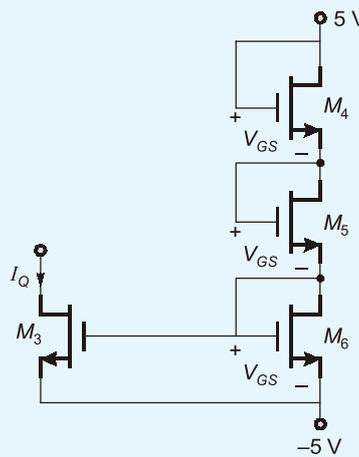**Solution:**

Consider current Mirror part of the circuit.



Since all the MOSFETs are identical, we assume  $V_{GS4} = V_{GS5} = V_{GS6} = V_{GS}$ .

Using KVL :  $5 = V_{GS} + V_{GS} + V_{GS} - 5$

$$\Rightarrow 3V_{GS} = 10 \Rightarrow V_{GS} = \frac{10}{3} \text{ V}$$

For MOSFETs  $M_4$ ,  $M_5$  and  $M_6$ , Drain is shorted to Gate, thus  $V_{DS} > V_{GS} - V_T$  i.e. MOSFETs are in saturation. The drain current,

$$I_{DS} = \frac{\mu_n C_{ox}}{2} \times \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$1 = \frac{0.1}{2} \times \frac{W}{L} \left( \frac{10}{3} - 1 \right)^2$$

$$\Rightarrow \frac{W}{L} = \frac{180}{49} = 3.6735$$

For  $M_1$  and  $M_2$ :

$$I'_{DS} = \frac{I_Q}{2} = 0.5 \text{ mA}$$

Thus,

$$g_m = \sqrt{2\mu_n C_{ox} \times \frac{W}{L} \times I'_{DS}}$$

$$g_m = \sqrt{2 \times 0.1 \times 10^{-3} \times \frac{180}{49} \times 0.5 \times 10^{-3}}$$

$$g_m = 0.6061 \text{ m}\Omega$$

The differential amplifier has a dual input balanced output. Thus, differential voltage gain,

$$A_d = \frac{V_0}{V_{s1} - V_{s2}} = g_m \times R_D = 0.6061 \times 5$$

$$= 3.03$$

End of Solution

- Q.5** (d) Design a J-K counter for states 1, 2, 4, 5, 7, 8, 10, 11, ... . What would happen if the circuit were turned ON and the first state it entered was a don't care state? [12 marks : 2025]

**Solution:**

Since the highest state of the sequence is  $11 = (1011)_2$ , hence the counter requires four J-K flip flops.

Given states: 1, 2, 4, 5, 7, 8, 10, 11

Unused states: 0, 3, 6, 9, 12, 13, 14, 15

**State Table:**

Present State				Next State				Flip-flop Inputs							
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$J_3$	$K_3$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	X	X	X	X	X	X	X	X	X	X	X	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	1	0	0	0	X	1	X	X	1	0	X
0	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	1	0	X	X	0	1	X	X	0
0	1	1	0	X	X	X	X	X	X	X	X	X	X	X	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	1	0	X	0	0	X	1	X	0	X
1	0	0	1	X	X	X	X	X	X	X	X	X	X	X	X
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	0	0	0	1	X	1	0	X	X	1	X	0
1	1	0	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X

Q	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Excitation Table for JK Flip-Flop



# ESE 2026 PRELIM EXAM Online Test Series

TOTAL  
**34 Tests**  
Newly Designed

**2206** Quality  
Questions

*An early start gives  
you an extra edge!!*

Test series is live.



Scan to enroll

## Key Features :



Newly designed quality questions as per standard of ESE



Due care taken for accuracy



Error free comprehensive solutions.



Comprehensive and detailed analysis report of test performance



Including tests of Paper-I (General Studies & Engineering Aptitude) and Paper-II (Technical syllabus)



All India Ranking











Available on android, iOS (Desktop & Laptop)




Streams Offered : CE, ME, EE, E&T

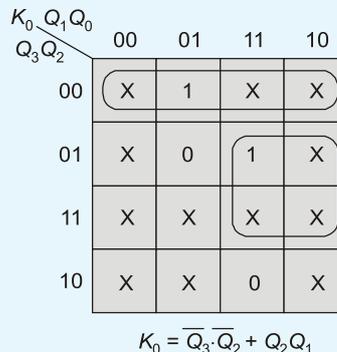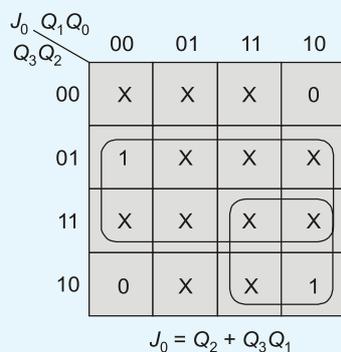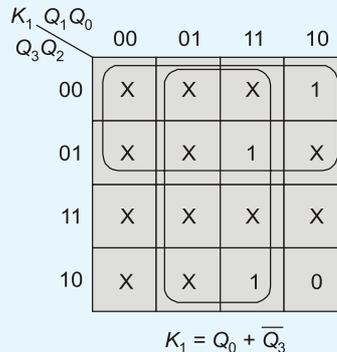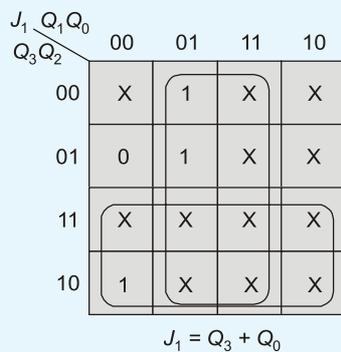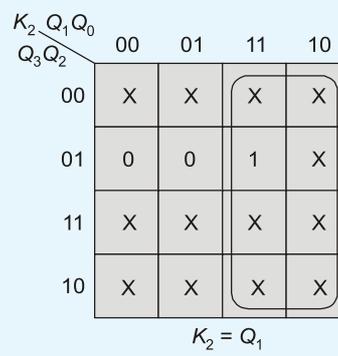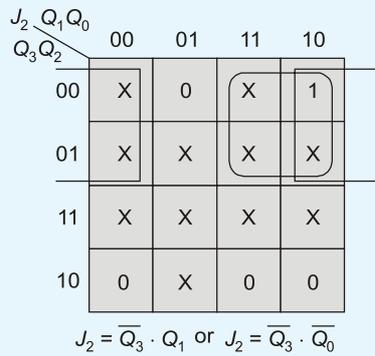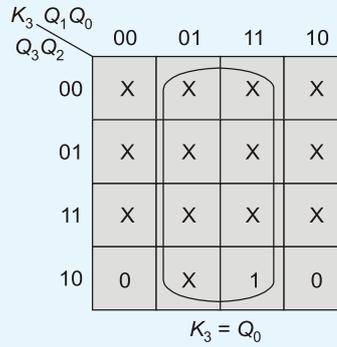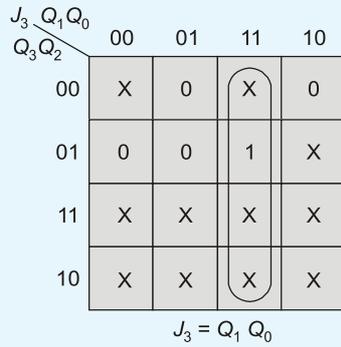Minimization of expression for flip-flops inputs using K-maps:



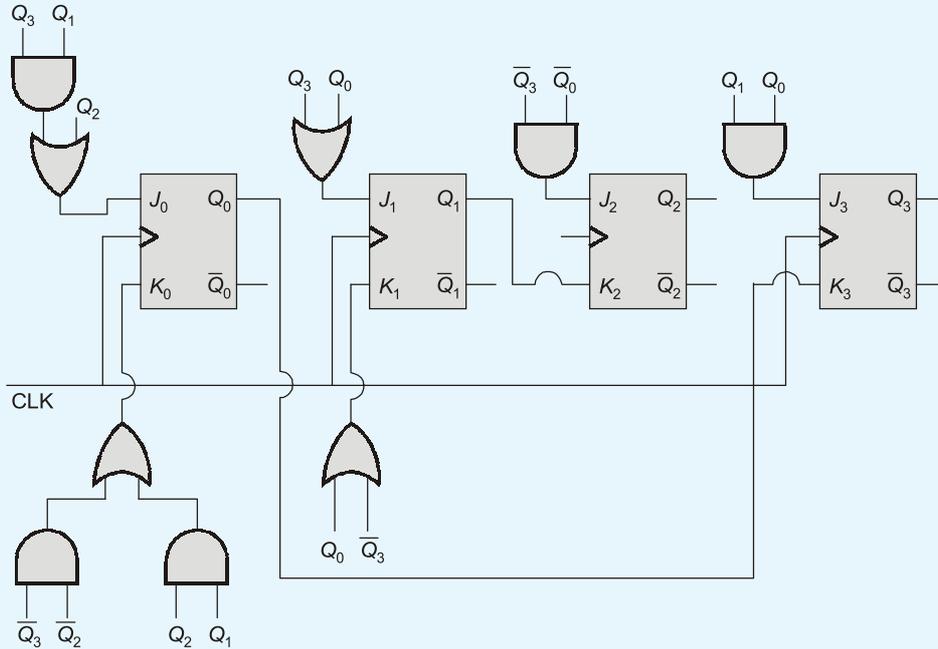**Logic Circuit:**

The J-K counter for the given sequence is as shown below:



**Checking for unused state:**

For the above logic circuit, the next state when the circuit enters into the unused states can be determined as below,

Unused State				Flip-Flop Inputs								Next State			
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_3$	$K_3$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$
0	0	0	0	0	0	1	0	0	1	0	1	0	1	0	0
0	0	1	1	1	1	0	1	1	1	0	1	1	0	0	0
0	1	1	0	0	0	1	1	0	1	1	1	0	0	0	1
1	0	0	1	0	1	0	0	1	1	0	0	0	0	1	1
1	1	0	0	0	0	0	0	1	0	1	0	1	1	1	1
1	1	0	1	0	1	0	0	1	1	1	0	0	1	1	1
1	1	1	0	0	0	0	1	1	0	1	1	1	0	1	1
1	1	1	1	1	1	0	1	1	1	1	1	0	0	0	0



**Solution:**


Transistor is acting as switch:

If  $V_i = V_1$  : Transistor becomes ON and the capacitor discharges to zero . Thus,  $v_o$  becomes zero and the collector current,

$$I_C = \frac{V_{CC} - 0}{R_C} = \frac{V_{CC}}{R_C}$$


If  $V_i = V_2$  : Transistor becomes OFF and the capacitor charges to  $V_{CC}$ . Thus,  $v_o$  becomes  $V_{CC}$  and  $I_C$  becomes 0.

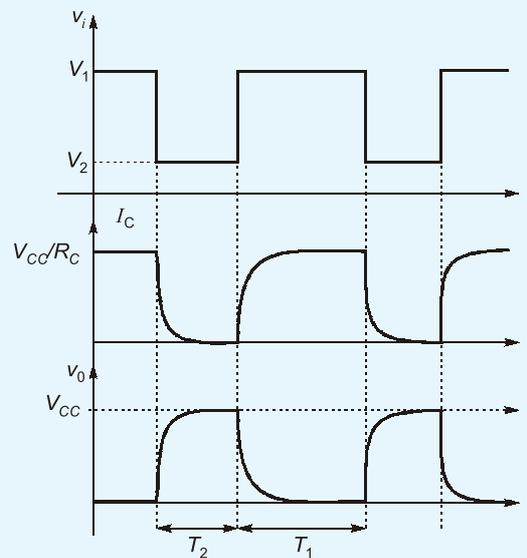Since the time constant are small compared to  $T_1$  or  $T_2$ , the capacitor charges/discharges completely during the time interval. Considering gradual charging and discharging of capacitor, we can draw waveforms as shown below.



End of Solution


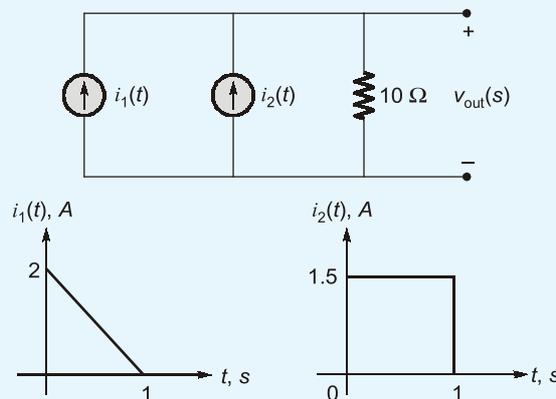
**Q.6** (a) The circuit of the figure has two sources of excitation  $i_1(t)$  and  $i_2(t)$ . Compute  $v_{out}(s)$ :



[20 marks : 2025]


**Solution:**

Given,

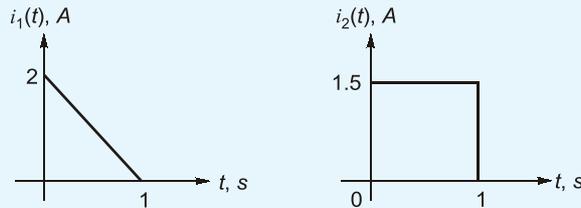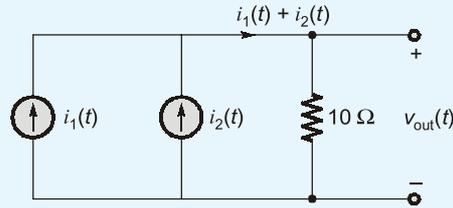

We have,
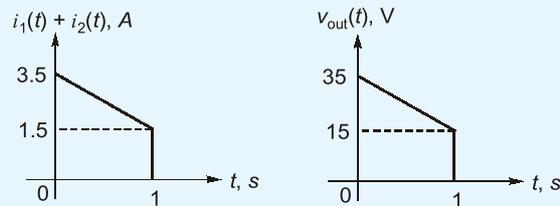
$$v_{out}(t) = 10 \times [i_1(t) + i_2(t)]$$



$\therefore v_{out}(t) = -20t + 35; \quad 0 < t < 1$

To obtain the Laplace Transform, we can write  $v_{out}(t)$  as,

$$v_{out}(t) = (35 - 20t)[u(t) - u(t-1)]$$

$$v_{out}(t) = 35u(t) - 35u(t-1) - 20tu(t) + 20(t-1)u(t-1) + 20u(t-1)$$

$$v_{out}(t) = 35u(t) - 15u(t-1) - 20tu(t) + 20(t-1)u(t-1)$$

We know that,

$$u(t) \longleftrightarrow \frac{1}{s}$$

$$tu(t) \longleftrightarrow -\frac{d}{ds} \left( \frac{1}{s} \right) = \frac{1}{s^2} \quad \text{(Multiplication by } t \text{ property)}$$

$$x(t - t_0) \longleftrightarrow e^{-st_0} X(s) \quad \text{(Time shifting property)}$$

Using the above properties, we can write the Laplace Transform of  $v_{out}(t)$  as,

$$V_{out}(s) = \frac{35}{s} - \frac{15e^{-s}}{s} - \frac{20}{s^2}(1 - e^{-s})$$

**End of Solution**



UPTO  
**100%**

**SCHOLARSHIP**

**NATIONAL  
SCHOLARSHIP  
TEST (NST)**

**Test Date : 2 Nov, 2025**

**Last date to Register :  
28 Oct, 2025**



### Test Pattern

- ✓ Time Duration : 60 Minutes
- ✓ Total Questions : 60 MCQs
- ✓ Weightage Per Question : 2 Marks
- ✓ Negative Marking : 0.66 Marks
- ✓ **Test Syllabus :**
  - Technical Subjects : 40 Questions
  - Reasoning & Aptitude : 10 Questions
  - Engineering Mathematics : 10 Questions
- ✓ Test Fee : Rs. 50/-

### Offline Batches at Delhi

from **First week of Dec 2025**  
**Streams:** CE, ME/PI, EE, EC/IN, CS

### Live-Online Batches

from **Last week of Nov, 2025**  
**Streams:** CE, ME/PI, EE, EC/IN, CS



Scan to register

For more details, visit :



*NST is valid for*  
**Foundation  
Courses for**

**ESE 2027  
GATE 2027**

- Offline Mode
- Live-Online

### Features of **Foundation Courses :**

- ✓ Classes by experienced & renowned faculties.
- ✓ Facility for doubt removal.
- ✓ Systematic subject sequence & timely completion.
- ✓ Concept practice through workbook solving.
- ✓ Comprehensive & updated books (Optional).
- ✓ Exam oriented learning ecosystem.
- ✓ Efficient teaching with comprehensive coverage.
- ✓ Proper notes making & study concentration.
- ✓ Regular performance assessment through class tests.

For more details, visit our website : [www.madeeasy.in](http://www.madeeasy.in)

📍 Corporate Office : 44 - A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi - 110016

📞 9021300500

✉ [nst@madeeasy.in](mailto:nst@madeeasy.in)


🌐 [www.madeeasy.in](http://www.madeeasy.in)

**MADE EASY Centres:** Delhi | Bhopal | Hyderabad | Jaipur | Pune

**Q.6** (b) Consider the circuit given below with the following parameters :  
 $R_{c1} = 3 \text{ K}$ ,  $R_{c2} = 500 \Omega$ ,  $R_e = 50 \Omega$ ,  $R' = R_s = 1.2 \text{ K}$ ,  $h_{fe} = 50$ ,  $h_{ie} = 1.1 \text{ K}$  and  
 $h_{re} = h_{oe} = 0$

Analyze the circuit for—

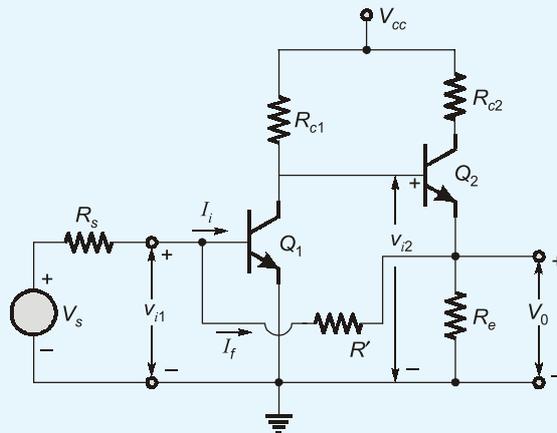- (i) reverse transmission factor,  $\beta$ ;
- (ii) transfer gain;
- (iii) voltage gain with feedback;
- (iv) input resistance with feedback;
- (v) output resistance with feedback.




[20 marks : 2025]

**Solution:**

Given,  $R_{C1} = 3 \text{ k}\Omega$ ,  $R_{C2} = 500 \Omega$ ,  $R_e = 50 \Omega$ ,  $R' = R_s = 1.2 \text{ k}\Omega$ ,  $h_{fe} = 50$ ,  
 $h_{ie} = 1.1 \text{ k}\Omega$ , and  $h_{re} = h_{ce} = 0$ .

**Small signal equivalent circuit:**

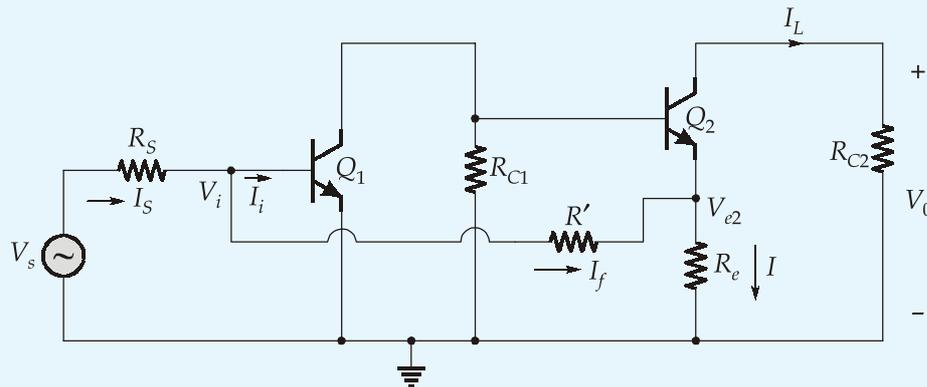

**Step 1:** Identify the type of feedback:

$R'$  is not connected directly to output node  $\Rightarrow$  Current sampling

$R'$  is connected directly to input node  $\Rightarrow$  shunt mixing

$\therefore$  The given feedback amplifier has current shunt feedback (current amplifier)

**Step 2: Calculate the feedback factor ( $\beta$ ):**

$$\text{KCL : } I_f = I_L + I$$

$$\Rightarrow I = I_f - I_L$$

We have, feedback current,

$$I_f = \frac{V_i - V_{e2}}{R'}$$

$$\text{Put } V_i = 0 \Rightarrow I_f = \frac{-V_{e2}}{R'} = \frac{-I R_e}{R'} = \frac{-(I_f - I_L) R_e}{R'}$$

$$\Rightarrow I_f \left[ 1 + \frac{R_e}{R'} \right] = \frac{I_L R_e}{R'}$$

$$\Rightarrow I_f (R' + R_e) = I_L R_e$$

$$\Rightarrow \frac{I_f}{I_L} = \beta = \frac{R_e}{R' + R_e} = \frac{50}{1200 + 50} = \frac{5}{125} = \frac{1}{25}$$


$$\Rightarrow \beta = \frac{1}{25}$$

**Step 3: Draw circuit without feedback:**

Break output loop  $\Rightarrow R'$  and  $R_e$  appear in series between  $B_1$  and ground.

Ground input node  $\Rightarrow R'$  and  $R_e$  appear in parallel between  $E_2$  and ground.

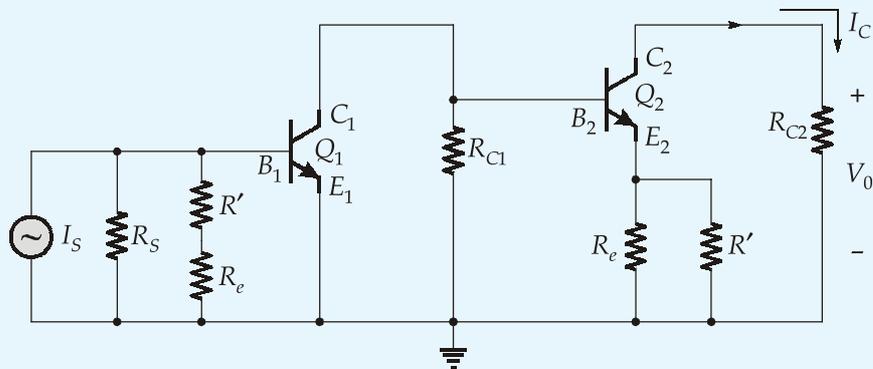
The small signal equivalent circuit without feedback can be drawn as below,



$$R_1 = R' + R_e = 1200 + 50 = 1250 \Omega = 1.25 \text{ k}\Omega$$

$$R_2 = R' \parallel R_e = 1200 \parallel 50 = \frac{1200 \times 50}{(1200 + 50)} = 48 \Omega$$

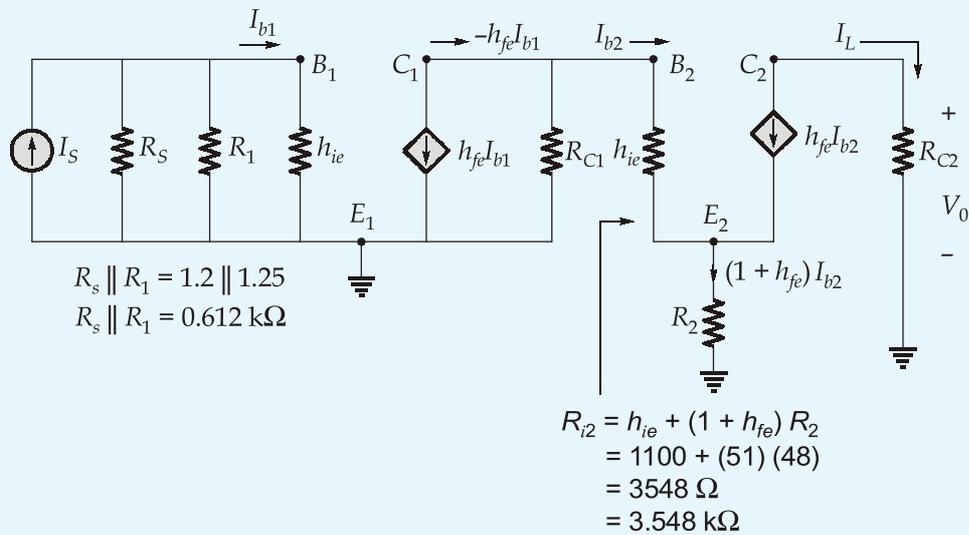Step 4: Replace  $Q_1$  and  $Q_2$  with  $h$ -parameter model:



From the circuit,

$$I_{b1} = \frac{I_S (R_S \parallel R_1)}{(R_S \parallel R_1) + h_{ie}}$$

$$I_{b2} = \frac{-h_{fe} I_{b1} R_{C1}}{R_{C1} + R_{i2}}$$

$\therefore$  Current gain,  $A_I = \frac{I_L}{I_S} = \left( \frac{I_L}{I_{b2}} \right) \cdot \left( \frac{I_{b2}}{I_{b1}} \right) \cdot \left( \frac{I_{b1}}{I_S} \right)$

$$= (-h_{fe}) \cdot \left( \frac{-h_{fe} R_{C1}}{R_{C1} + R_{i2}} \right) \cdot \left( \frac{R_S \parallel R_1}{R_S \parallel R_1 + h_{ie}} \right)$$

$$= (-50) \cdot \left( \frac{-50 \times 3}{3 + 3.548} \right) \cdot \left( \frac{0.612}{0.612 + 1.1} \right) = 409.45$$

Resistance seen by current source ' $I_S$ ' is

$$R_{in} = R_S \parallel R_1 \parallel h_{ie}$$

$$= 1.2 \parallel 1.25 \parallel 1.1$$

$$= 0.612 \parallel 1.1$$

$$= 0.3933 \text{ k}\Omega$$

Output resistance,  $R_{C2} = 500 \Omega$

Desensitivity,  $D = 1 + \beta A_I$

$$= 1 + \left( \frac{1}{25} \times 409.45 \right) = 17.378$$

**With feedback:**

Current gain with feedback,  $A_{If} = \frac{A_I}{1 + \beta A_I} = \frac{409.45}{17.378} = 23.56$

For a current shunt amplifier, the input resistance decreases by a factor of  $(1 + \beta A_I)$  and output impedance increases by a factor of  $(1 + \beta A_I)$ . Thus,

Input resistance with feedback,  $R_{in f} = \frac{R_{in}}{1 + \beta A_f} = \frac{393.3}{17.378} = 22.63 \Omega$


Output resistance with feedback,  $R_{of} = R_o(1 + \beta A_f)$   
 $= 500 \times 17.378 = 8.689 \text{ k}\Omega$

Voltage gain with feedback,  $A_{vf} = \frac{V_o}{V_s} = \frac{I_L R_{c2}}{I_s R_s} = \frac{A_{ff} R_{c2}}{R_s} = \frac{23.56 \times 0.5}{1.2}$

$\Rightarrow A_{vf} = 9.8167$

End of Solution

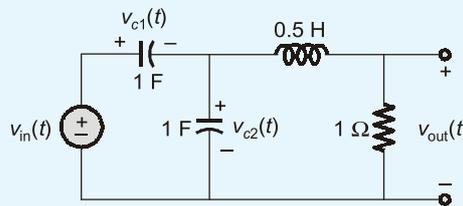**Q.6** (c) Consider the circuit in which  $v_{in}(t) = 5u(t)$  V,  $v_{c1}(0^-) = 3$  V,  $v_{c2}(0^-) = 0$  V and  $i_L(0^-) = 2$  A. Find  $v_{out}(t)$  :



[20 marks : 2025]

**Solution:**

Given,


$$\begin{aligned} v_{in}(t) &= 5u(t) \text{ V} \\ v_{c1}(0^-) &= 3 \text{ V} \\ v_{c2}(0^-) &= 0 \text{ V} \\ i_L(0^-) &= 2 \text{ A} \end{aligned}$$

We can write,

$$V_L(s) = LsI(s) - Li(0^-)$$

$$V_C(s) = \frac{I(s)}{Cs} + \frac{v_c(0^-)}{s}$$

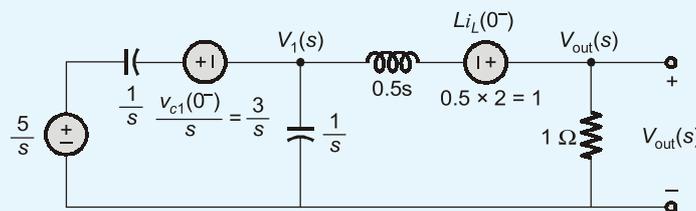Thus, the s-domain equivalent of the given circuit can be drawn as,



Apply KCL at node  $V_1(s)$ :

$$\frac{V_1(s) + \frac{3}{s} - \frac{5}{s}}{\left(\frac{1}{s}\right)} + \frac{V_1(s)}{\left(\frac{1}{s}\right)} + \frac{V_1(s) + 1 - V_{out}(s)}{0.5s} = 0$$

$$V_1(s) \left( s + s + \frac{1}{0.5s} \right) - \frac{V_{out}(s)}{0.5s} = 2 - \frac{1}{0.5s}$$

$$V_1(s) \left[ \frac{2(s^2 + 1)}{s} \right] - V_{out}(s) \left[ \frac{2}{s} \right] = 2 \left( \frac{s-1}{s} \right)$$

$$V_1(s)[2(s^2 + 1)] - 2 V_{out}(s) = 2(s-1) \quad \dots(1)$$

Apply KCL at node  $V_{out}(s)$  :

$$\frac{V_{out}(s) - 1 - V_1(s)}{0.5s} + \frac{V_{out}(s)}{1} = 0$$

$$V_{out}(s) \left[ 1 + \frac{2}{s} \right] - \frac{2}{s} V_1(s) = \frac{2}{s}$$

$$V_{out}(s) \left[ \frac{s}{2} + 1 \right] - V_1(s) = 1$$

$$\Rightarrow V_1(s) = -1 + V_{out}(s) \left[ \frac{s+2}{2} \right] \quad \dots(2)$$

Substitute equation (2) in (1),

$$\left\{ -1 + V_{out}(s) \left[ \frac{s+2}{2} \right] \right\} [2(s^2 + 1)] - 2V_{out}(s) = 2(s-1)$$

$$-2(s^2 + 1) + (s^2 + 1)(s+2)V_{out}(s) - 2V_{out}(s) = 2(s-1)$$

$$V_{out}(s)[(s^2 + 1)(s+2) - 2] = 2(s-1) + 2(s^2 + 1)$$

$$V_{out}(s) = \frac{2s - 2 + 2s^2 + 2}{s^3 + 2s^2 + s + 2 - 2} = \frac{2s^2 + 2s}{s(s^2 + 2s + 1)}$$

$$V_{out}(s) = \frac{2s(s+1)}{s(s^2 + 2s + 1)} = \frac{2(s+1)}{(s^2 + 2s + 1)} = \frac{2(s+1)}{(s+1)^2}$$

$$\therefore V_{out}(s) = \frac{2}{(s+1)}$$

Taking inverse Laplace transform on both sides,

$$v_{out}(t) = 2e^{-t}u(t)$$


**Alternate Method:**

Given,

$$v_{in}(t) = 5u(t) \text{ V,}$$

$$v_c(0^-) = 3 \text{ V, } v_{c2}(0^-) = 0 \text{ V, } i_L(0^-) = 2 \text{ A}$$

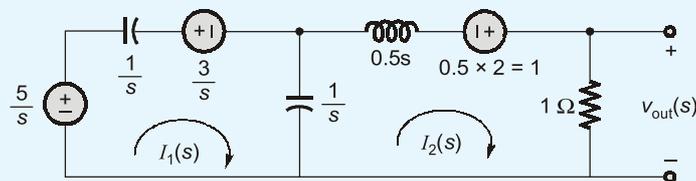The s-domain equivalent of the given circuit is,



Apply KVL around loop 1:

$$-\frac{5}{s} + \left( \frac{1}{s} + \frac{1}{s} \right) I_1(s) - \frac{1}{s} I_2(s) + \frac{3}{s} = 0$$

$$\frac{2}{s} I_1(s) - \frac{1}{s} I_2(s) = \frac{2}{s}$$

$$2I_1(s) - I_2(s) = 2 \quad \dots(1)$$



# Announcing Foundation Courses for **ESE & GATE : 2027**

The foundation batches are taught *comprehensively* which cover the requirements of **"all technical-syllabus based examinations"**.

- ✓ Classes by experienced & renowned faculties.
- ✓ Efficient teaching with comprehensive coverage.
- ✓ Comprehensive & updated study material.
- ✓ Similar teaching pedagogy in offline & online classes.
- ✓ Exam oriented learning ecosystem.
- ✓ Systematic subject sequence and timely completion.
- ✓ Concept practice through workbook solving.
- ✓ Regular performance assessment through class tests.

## BATCH COMMENCING DATES :



### Offline Batches at Delhi

<b>Teaching Hours :</b>	<b>Batch Commencing Dates :</b>						
<b>GATE Exclusive</b> <ul style="list-style-type: none"><li>• CE, ME : 950 to 1000 Hrs.</li><li>• EE : 800 to 850 Hrs.</li><li>• EC, IN, CS : 650-700 Hrs.</li></ul>	<table><tr><td>CE</td><td rowspan="5"><b>First week of December 2025</b></td></tr><tr><td>ME/PI</td></tr><tr><td>EE</td></tr><tr><td>EC/IN</td></tr><tr><td>CS</td></tr></table>	CE	<b>First week of December 2025</b>	ME/PI	EE	EC/IN	CS
CE		<b>First week of December 2025</b>					
ME/PI							
EE							
EC/IN							
CS							
<b>GATE + ESE</b> <ul style="list-style-type: none"><li>• CE, ME, EE, EC: 1200-1250 Hrs.</li></ul>	 Scan to enroll						



### Live-Online Batches

<b>Teaching Hours :</b>	<b>Batch Commencing Dates :</b>						
<b>GATE Exclusive</b> <ul style="list-style-type: none"><li>• CE, ME, EE : 750 to 800 Hrs.</li><li>• EC, IN, CS : 650-700 Hrs.</li></ul>	<table><tr><td>CE</td><td rowspan="5"><b>Last week of November 2025</b></td></tr><tr><td>ME/PI</td></tr><tr><td>EE</td></tr><tr><td>EC/IN</td></tr><tr><td>CS</td></tr></table>	CE	<b>Last week of November 2025</b>	ME/PI	EE	EC/IN	CS
CE		<b>Last week of November 2025</b>					
ME/PI							
EE							
EC/IN							
CS							
<b>GATE + ESE</b> <ul style="list-style-type: none"><li>• CE, ME, EE, EC: 1050-1100 Hrs.</li></ul>	 Scan to enroll						

More batches to be announced soon. | Courses with SES (State Engineering Services) are also available. **Low Cost EMI Facility Available** **Admissions Open**

**Delhi Centre :** 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

**MADE EASY Centres :** Delhi | Bhopal | Hyderabad | Jaipur | Pune  [www.madeeasy.in](http://www.madeeasy.in)

Apply KVL around loop 2:

$$\left(0.5s + 1 + \frac{1}{s}\right)I_2(s) - \frac{1}{s}I_1(s) - 1 = 0$$

$$(0.5s^2 + s + 1)I_2(s) - I_1(s) - s = 0$$

$$I_1(s) = (0.5s^2 + s + 1)I_2(s) - s \quad \dots(2)$$

Substitute equation (2) in(1),

$$2[(0.5s^2 + s + 1)I_2(s) - s] - I_2(s) = 2$$

$$(s^2 + 2s + 2 - 1)I_2(s) = 2 + 2s$$

$$I_2(s) = \frac{2(s+1)}{(s^2 + 2s + 1)} = \frac{2(s+1)}{(s+1)^2} = \frac{2}{(s+1)}$$

We have,  $V_{\text{out}}(s) = 1 \times I_2(s) = \frac{2}{(s+1)}$

Taking inverse Laplace transform on both sides,

$$V_{\text{out}}(t) = 2e^{-t} u(t)$$

End of Solution

- Q.7** (a) (i) A first-order thermometer is used for the measurement of temperature of air cycling at a rate of 1 cycle every 5 minutes. The time constant of the thermometer is 20 seconds. Calculate the attenuation of the indicated temperature in percent. If the temperature undergoes a sinusoidal variation of 20°C, calculate the indicated variation in temperature.

[10 marks : 2025]

- (ii) Compare and contrast Type-I and Type-II superconductors based on the following parameters:

- (1) Magnetic field behaviour
- (2) Critical magnetic field
- (3) Material examples
- (4) Meissner effect
- (5) Applications

[10 marks : 2025]

**Solution:**

- (i) Cycling rate : 1 cycle every 5 minutes  $\Rightarrow$  Period of the temperature cycle = 300 seconds

Time constant ( $\tau$ ) = 20 seconds

Input sinusoidal temperature variation = 20°C

The frequency ( $f$ ) of the temperature cycle is

$$f = \frac{1}{\text{cycle time}} = \frac{1}{300} \text{ Hz}$$

$$\text{Angular frequency } (\omega) = 2\pi f = \frac{2\pi}{300} \simeq 0.02094 \text{ rad/sec}$$

The transfer function of a first-order system is given by

$$T(s) = \frac{1}{1 + \tau s}$$

For a first order system subjected to sinusoidal input, the amplitude attenuation is given by

$$\text{Attenuation factor} = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$$

Substitute  $\omega = 0.02094$  rad/sec,  $\tau = 20$  sec

$$\omega\tau = 0.4188$$

$$\text{Attenuation factor} = \frac{1}{\sqrt{1 + (0.4188)^2}} = 0.922$$



The attenuation in percent is

$$\text{Attenuation} = \{1 - 0.922\} \times 100 = 7.8\%$$

The indicated variation is the input-variation multiplied by attenuation factor.


$$\text{Indicated variation} = 20 * 0.922 = 18.44^\circ\text{C}$$

**(ii) Comparison of Type-I and Type-II superconductors**

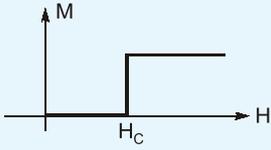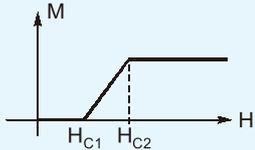Parameters	Type-I Superconductor	Type-II Superconductor
1. Magnetic field behaviour	 <p>Exhibits an abrupt transition from superconducting to normal state at a critical field, <math>H_C</math>. It exhibit perfect diamagnetism until <math>H_C</math>.</p>	 <p>It loses superconductivity gradually and has two critical fields: <math>H_{C1}</math> (below which full diamagnetism) and <math>H_{C2}</math> (above which normal state). Between <math>H_{C1}</math> and <math>H_{C2}</math>: Mixed/Vortex state.</p>
2. Critical magnetic field	Only one ( $H_C$ ), The critical fields of Type I superconductors is generally low.	Two critical fields ( $H_{C1}$ and $H_{C2}$ ). $H_{C2}$ can be very high.
3. Material examples	Pure elemental metals: Pd (lead), Hg (mercury), Al (Aluminium), Sn (tin).	Typically alloys and compounds: YBCO, NbTi, BSCCO.
4. Meissner effect	Complete Meissner effect below $H_C$ (perfect flux expulsion)	It shows partial Meissner effect. It exhibit complete Meissner effect only below $H_{C1}$ . In the mixed state, some flux penetrates in quantized vortices; thus full flux expulsion is lost.
5. Applications	Mostly academic and laboratory demonstrations	Widely used in practical high-field applications: Superconducting magnets (MRI, NMR, particle accelerators), superconducting wires/tapes, power devices, fault-current limiters, etc.

**End of Solution**

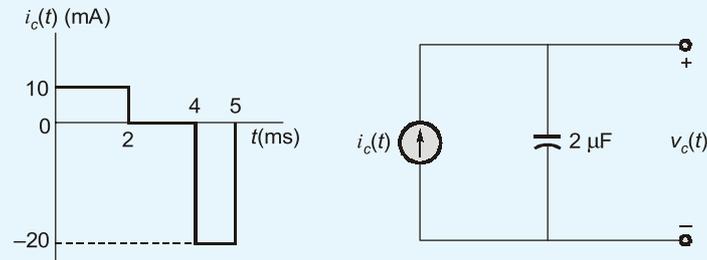- Q.7** (b) The current through a  $2\mu\text{F}$  capacitor is shown in the figure. At  $t = 0$ , the voltage is zero. Sketch the voltage and power waveform with respect to the time (scaled voltage and power):




[20 marks : 2025]

**Solution:**

Given,

$$C = 2 \mu\text{F}$$

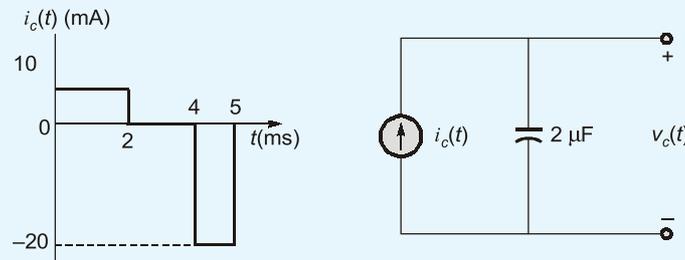

$$\begin{aligned} i_c(t) &= 10 \text{ mA}; 0 < t < 2 \text{ ms} \\ &= 0; 2 \text{ ms} < t < 4 \text{ ms} \\ &= -20 \text{ mA}; 4 \text{ ms} < t < 5 \text{ ms} \end{aligned}$$

We know, voltage across the capacitor is given by

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$

For  $0 < t < 2 \text{ ms}$ :

$$v_c(t) = \frac{1}{2 \times 10^{-6}} \int_0^t (10 \times 10^{-3}) dt = 5000t$$

For  $2 \text{ ms} < t < 4 \text{ ms}$ :

$$v_c(t) = \frac{1}{2 \times 10^{-6}} \int_{2\text{ms}}^t (0) dt + v_c(2\text{ms}) = 0 + 10 = 10 \text{ V}$$

For  $4 \text{ ms} < t < 5 \text{ ms}$ :


$$\begin{aligned} v_c(t) &= \frac{1}{2 \times 10^{-6}} \int_{4\text{ms}}^t (-20 \times 10^{-3}) dt + v_c(4 \text{ ms}) \\ &= -10000(t - 0.004) + 10 = -10000t + 50 \end{aligned}$$

$\therefore$

$$\begin{aligned} v_c(t) &= 5000t; 0 < t < 2 \text{ ms} \\ &= 10; 2 \text{ ms} < t < 4 \text{ ms} \\ &= -10000t + 50; 4 \text{ ms} < t < 5 \text{ ms} \end{aligned}$$

$$\begin{aligned} \text{Power, } p(t) &= v_c(t)i_c(t) = 50t; \quad 0 < t < 2 \text{ ms} \\ &= 0; \quad 2 \text{ ms} < t < 4 \text{ ms} \\ &= 200t - 1; \quad 4 \text{ ms} < t < 5 \text{ ms} \end{aligned}$$

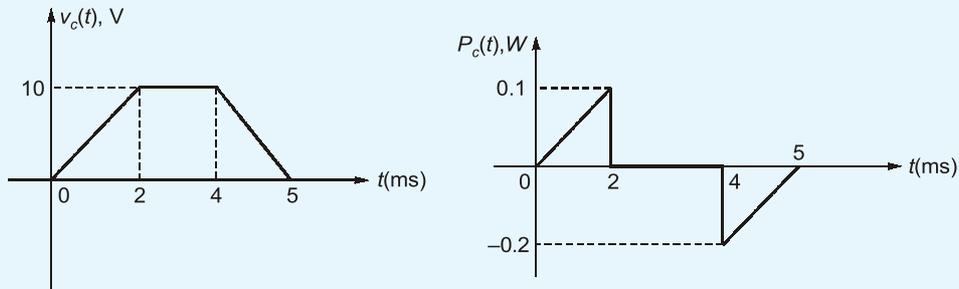The voltage and power waveform with respect to the time is as shown below:



**End of Solution**

**Q.7** (c) (i) A piezoelectric ceramic disc of thickness  $t = 2 \text{ mm}$  and area  $= 1.5 \times 10^{-4} \text{ m}^2$  is subjected to a compressive force of  $F = 50 \text{ N}$  applied perpendicular to its faces. The material has the following properties:

- Piezoelectric coefficient  $= 300 \times 10^{-12} \text{ C/N}$
- Relative permittivity  $= 1200$
- Volume permittivity  $= 8.854 \times 10^{-12} \text{ F/m}$

Determine the following :

- (1) Charge generated on electrodes due to applied force
- (2) Capacitance of the piezoelectric disc
- (3) Voltage generated across the ceramic disc

[10 marks : 2025]

(ii) For a 2-port network, express Z-parameters in terms of inverse hybrid parameters.

[10 marks : 2025]

**Solution:**

(i) Given, Thickness,  $t = 2 \text{ mm} = 0.002 \text{ m}$

$$\text{Area, } A = 1.5 \times 10^{-4} \text{ m}^2$$

$$\text{Applied Force, } F = 50 \text{ N}$$

$$\text{Charge sensitivity, } d = 300 \times 10^{-12} \text{ C/N}$$

$$\text{Relative permittivity, } \epsilon_r = 1200$$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

Charge generated ( $Q$ )

$$Q = d.F = 300 \times 10^{-12} \times 50 = 15 \times 10^{-9} \text{ C}$$

Capacitance of the piezoelectric disc,

$$C = \frac{\epsilon_0 \epsilon_r A}{t} = \frac{8.854 \times 10^{-12} \times 1200 \times 1.5 \times 10^{-4}}{0.002}$$

$$C = 7.97 \times 10^{-10} \text{ F}$$

Voltage generated across the ceramic disc,

$$V = \frac{Q}{C} = \frac{15 \times 10^{-9}}{7.97 \times 10^{-10}} \approx 18.8 \text{ V}$$

(ii) The z-parameter equations are given by,

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \dots(i)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \dots(ii)$$

and inverse hybrid parameters,

$$I_1 = g_{11} V_1 + g_{12}I_2 \quad \dots(iii)$$

$$V_2 = g_{21} V_1 + g_{22}I_2 \quad \dots(iv)$$

For  $I_2 = 0$ :

$$1. \quad Z_{11} = \frac{V_1}{I_1} \quad \text{and} \quad \frac{I_1}{V_1} = g_{11}$$

Thus, 
$$\frac{V_1}{I_1} = \frac{1}{g_{11}} \quad \dots(v)$$

$$Z_{11} = \frac{1}{g_{11}}$$

$$2. \quad \frac{V_2}{I_1} = Z_{21} \quad \text{and} \quad \frac{V_2}{V_1} = g_{21} \quad \Rightarrow \quad V_1 = \frac{V_2}{g_{21}}$$

$$I_1 = g_{11} \left( \frac{V_2}{g_{21}} \right) \quad \dots \text{using equation (v)}$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{g_{21}}{g_{11}}$$

For  $I_1 = 0$

$$1. \quad \frac{V_1}{I_2} = Z_{12}$$

$$-g_{11}V_1 = g_{12}I_2$$

$$\frac{V_1}{I_2} = \frac{-g_{12}}{g_{11}} = Z_{12}$$

$$2. \quad \frac{V_2}{I_2} = Z_{22} \quad \text{and} \quad -g_{11}V_1 = g_{12}I_2$$

$$V_1 = \left[ \frac{-g_{12}I_2}{g_{11}} \right]$$

Using equation (iv),

$$V_2 = g_{21} \left( \frac{-g_{12}I_2}{g_{11}} \right) + g_{22}I_2$$

$$\frac{V_2}{I_2} = \left[ \frac{-g_{21}g_{12}}{g_{11}} + g_{22} \right] = Z_{22}$$


$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{g_{11}} & \frac{-g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{-g_{12}g_{21}}{g_{11}} + g_{22} \end{bmatrix}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{g_{11}} & \frac{-g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{\Delta g}{g_{11}} \end{bmatrix}$$

where  $\Delta g = g_{22}g_{11} - g_{12}g_{21}$

End of Solution

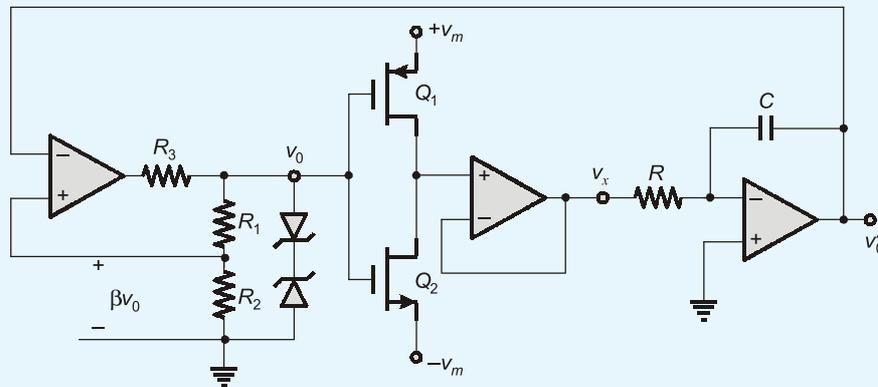**Q.8** (a) Explain the working of each stage of the voltage-controlled oscillator circuit shown below :



Evaluate the effect of change in modulating voltage  $v_m$  to the output frequency.  
[20 marks : 2025]

**Solution:**

The given circuit has three stages:

**Stage 1: Schmitt Trigger**

Stage-1 is a Schmitt Trigger having the output as a square wave with outputs,  $(V_z + V_{D(ON)})$  or  $(V_z - V_{D(ON)})$ . Assuming the diode to be an ideal diode,  $V_{D(ON)} = 0$ . Thus, the square wave generated at the output of Schmitt Trigger has levels i.e.  $v_0 = +V_z$  or  $-V_z$ .

The upper and lower threshold voltage of the Schmitt trigger is given by

$$V_{UT} = \left( \frac{R_2}{R_1 + R_2} \right) V_z = \beta V_z$$

$$V_{LT} = \left( \frac{R_2}{R_1 + R_2} \right) (-V_z) = -\beta V_z$$

We have,

$$v_0 = \begin{cases} V_z; & \text{if } v'_0 > \beta V_0 \\ -V_z; & \text{if } v'_0 < \beta V_0 \end{cases}$$



# Foundation Courses for

## ESE 2027

## GATE 2027



### Tablet Course

- Pre-loaded full fledged recorded course
- Android OS based 10.5 inch Samsung tablet
- Internet access does not required
- Classes by senior faculties
- Validity: 2 Years
- Learn at your own pace
- Tablet is reusable for normal purpose after validity expires



### Recorded Course

- Recorded Course
- Full fledged holistic preparation
- Classes by senior faculties
- Lectures can be watched anytime/anywhere
- Courses are accessible on PC & Mac desktops/laptops/android/iOS mobile devices.
- Learn at your own pace
- Validity: 1 year
- Internet connection required

### Teaching Hours

- ✓ **GATE Exclusive** • CE, ME, EE : 800 to 900 Hrs.  
• EC, IN, CS, CH : 650-700 Hrs.
- ✓ **GATE + ESE** • CE, ME, EE, EC : 1100 to 1200 Hrs.
- ✓ **GATE + SES-GS** • CE, ME, EE : 1150 to 1250 Hrs.
- ✓ **GATE + ESE + SES-GS** • CE, ME, EE, EC : 1450 to 1550 Hrs.  
• EC, IN, CS, CH : 950-1050 Hrs.

**Note :** State Engineering Services Examination. • The course is offered with a validity options of 1 year and 2 years.

**Admissions Open**  
for **ESE 2026**  
& **GATE 2026**

**Admissions Open**  
from **1 Jan 2026** for  
**ESE 2027 & GATE 2027**

**For Online Courses,**  
**Download :**  
**"MADE EASY Prime"**  
**App now**



Android



iOS

**Low Cost  
EMI Facility  
Available**

**Delhi Centre :** 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

**MADE EASY Centres :** Delhi | Bhopal | Hyderabad | Jaipur | Pune

[www.madeeasyprime.com](http://www.madeeasyprime.com)

**Stage 2: Voltage Follower**

The MOS Transistors  $Q_1$  and  $Q_2$  forms CMOS inverter and the op-amp circuit acts as a voltage follower. Thus,

If  $v_0 = V_z$ , then  $Q_1$  : OFF and  $Q_2$  : ON, we get  $v_x = -v_m$

If  $v_0 = -V_z$ , then  $Q_1$  : ON and  $Q_2$  : OFF, we get  $v_x = v_m$

The op-amp prevents loading effect and provides isolation between the stages.

**Stage 3: Integrator**

The third stage is an integrator and converts square wave into triangular wave.

For  $v_x = v_m$ ,

$$v'_0 = -\frac{1}{RC} \int v_m dt = \left( -\frac{v_m}{RC} \right) t$$


It generates a negative ramp until  $v'_0 < \beta v_0$  and thereafter,  $v_x$  switches to  $-v_m$

For  $v_x = -v_m$ ,

$$v'_0 = -\frac{1}{RC} \int -v_m dt = \left( \frac{v_m}{RC} \right) t$$


It generates a positive ramp until  $v'_0 > \beta v_0$  and thereafter,  $v_x$  switches to  $v_m$

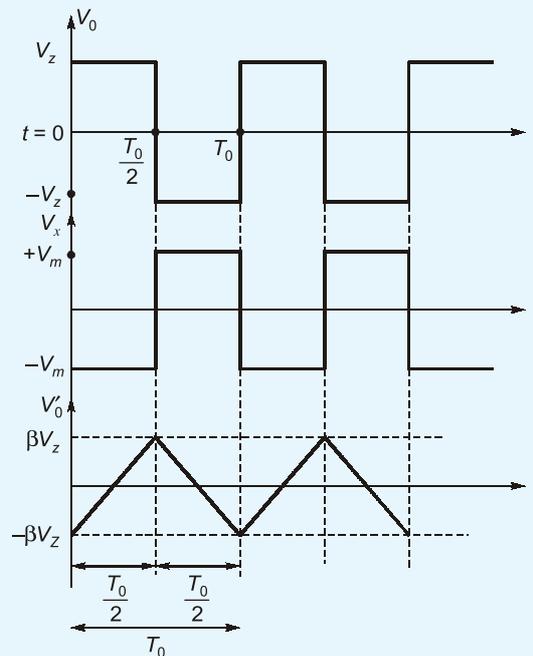The waveform at the various stages of the oscillator is shown below,



Consider  $0 \leq t \leq \frac{T_0}{2}$  :

Assume  $v_0 = V_z$ ;  $v_x = -v_m$

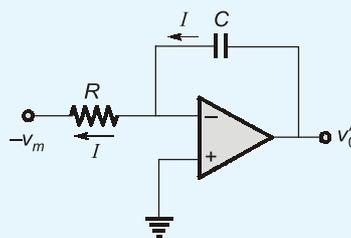

$$I = \frac{0 + v_m}{R} = \frac{v_m}{R}$$

The output is a positive going ramp and  $v'_0$  changes from  $-\beta V_z$  to  $+\beta V_z$ . Thus,

$$\Delta V_c = \Delta v'_0 = 2\beta V_z$$

$$I \times \Delta t = C \times \Delta V_c$$

$$\frac{v_m}{R} \times \frac{T_0}{2} = C \times 2\beta V_z$$

$$T_0 = 4RC \times \frac{\beta V_z}{v_m}$$

$$\text{Oscillation frequency, } f_0 = \frac{1}{T_0} = \frac{1}{4RC} \times \frac{v_m}{\beta V_z}$$

If  $v_m$  increases, then  $f_0$  increases. Thus,  $f_0$  can be controlled through  $v_m$ .

**End of Solution**

- Q.8** (b) Use a decoder to design a binary-to-hexadecimal character generator. The outputs of the character generator are to be connected via current limiting resistors to a common anode seven-segment display. Assume that the inputs are positive logic signals.

[20 marks : 2025]

**Solution:**

Designing of a binary-to-hexadecimal character generator:

**1. Inputs:**

- Binary to hexadecimal means we need 4 input binary bits (A, B, C, D).
- These 4 inputs represent hexadecimal digits 0-F.

**2. Decoder (Driver IC):**

A 4-to-16 line decoder is used to convert the 4-bit binary input into 16 individual output lines, one for each hexadecimal digit (0-F).

**3. Display Type: Common anode display.**

Segments turn ON when a logic 0 (low) is applied to their cathode pins through current-limiting resistors.

**4. Character Generator Design:**

- The outputs of the decoder are given to the character generator which generates an active low signal for the corresponding segments of the seven-segment display (a-g) to display the hexadecimal character.
- The outputs of the character generator are connected to the 7-segment display through current limiting resistors.
- The common anode is tied to  $+V_{CC}$ .

5. **Truth table:** The truth table for the character generator is as below,

Binary Inputs				Hexadecimal Character	7 segment display						
A	B	C	D		a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	1	0	0	1	1	1	1
0	0	1	0	2	0	0	1	0	0	1	0
0	0	1	1	3	0	0	0	0	1	1	0
0	1	0	0	4	1	0	0	1	1	0	0
0	1	0	1	5	0	1	0	0	1	0	0
0	1	1	0	6	0	1	0	0	0	0	0
0	1	1	1	7	0	0	0	1	1	1	1
1	0	0	0	8	0	0	0	0	0	0	0
1	0	0	1	9	0	0	0	0	1	0	0
1	0	1	0	A	0	0	0	1	0	0	0
1	0	1	1	b	1	1	0	0	0	0	0
1	1	0	0	C	0	1	1	0	0	0	1
1	1	0	1	d	1	0	0	0	0	1	0
1	1	1	0	E	0	1	1	0	0	0	0
1	1	1	1	F	0	1	1	1	0	0	0

6. **Design of character generator:**

From the truth table, the outputs of the character generator which drive the common-anode seven-segment display are obtained as below:

$$a = \Sigma m(1, 4, 11, 13)$$

$$b = \Sigma m(5, 6, 11, 12, 14, 15)$$

$$c = \Sigma m(2, 12, 14, 15)$$


$$d = \Sigma m(1, 4, 7, 10, 15)$$

$$e = \Sigma m(1, 3, 4, 5, 7, 9)$$

$$f = \Sigma m(1, 2, 3, 7, 13)$$

$$g = \Sigma m(0, 1, 7, 12)$$

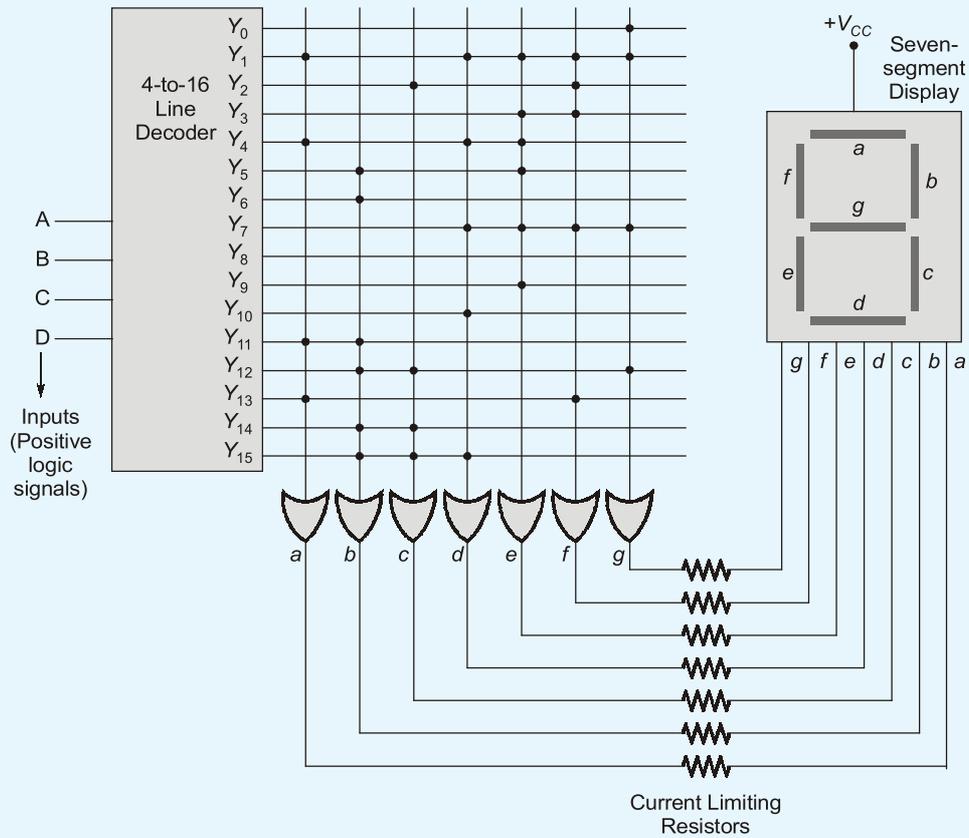Using above expressions, we obtain the interface circuit as below,




End of Solution

**Q.8** (c) (i) A voltage  $50 + 25 \sin \omega t$  volts is applied to a series R-L circuit having a resistance of  $10 \Omega$  and inductance of  $0.1 \text{ H}$ . A wattmeter is connected in the circuit to measure power. Calculate the reading of the wattmeter if  $\omega = 100\pi \text{ rad/s}$ .


[10 marks : 2025]

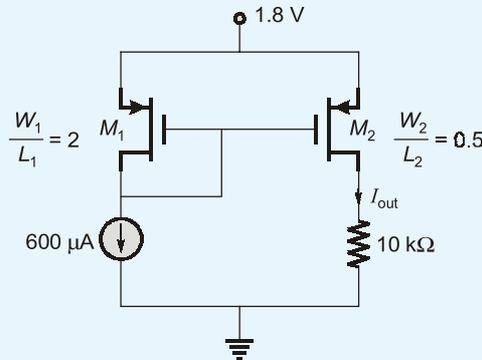(ii) For the circuit shown in the figure, find  $I_{\text{out}}$ . Assume  $\mu_n C_{\text{ox}} = 250 \mu\text{A/V}^2$  and  $V_{\text{tn}} = 0.4 \text{ V}$  for both the MOSFETs:




[10 marks : 2025]

**Solution:**

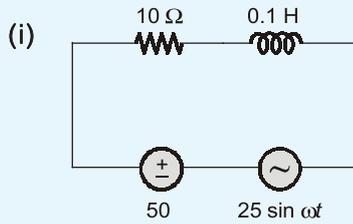


50 V source is applied to the circuit

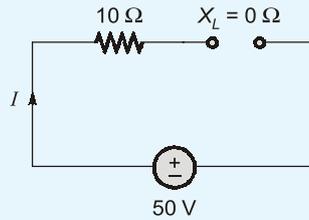

$$I = \frac{50}{10} = 5 \text{ A}$$

$$P_{dc} = I^2 R = 5^2(10) = 250 \text{ watts}$$

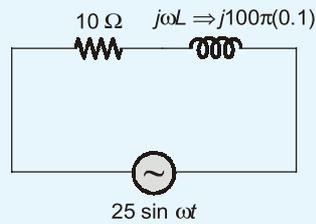25 sin  $\omega t$  source is applied to the circuit, where  $\omega = 100\pi$ .



$$X_L = \omega L \Rightarrow (100\pi)(0.1)$$


$$X_L = 31.416 \Omega$$

$$I_{rms} = \frac{25/\sqrt{2}}{10 + j31.416} \Rightarrow 0.5355 \angle -72.366^\circ \text{ A}$$

$$P_{AC} = (0.5355)^2 \times 10 \Rightarrow 2.8676 \text{ watts}$$

$$\begin{aligned} P_{Total} &= P_{DC} + P_{AC} \\ &= 250 + 2.8676 \\ &= 252.8676 \text{ watts} \end{aligned}$$

(ii)

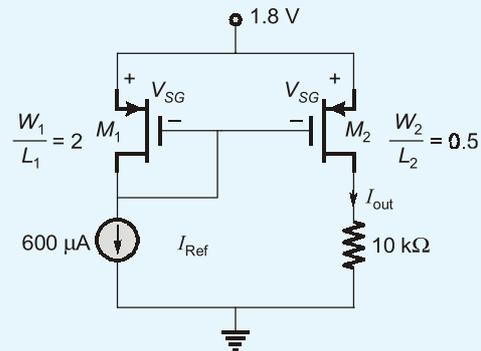

$$\frac{I_{out}}{I_{Ref}} = \frac{\frac{\mu_N C_{ox}}{2} \times \left(\frac{W}{L}\right)_2 \times (V_{SG} - |V_T|)^2}{\frac{\mu_N C_{ox}}{2} \times \left(\frac{W}{L}\right)_1 \times (V_{SG} - |V_T|)^2} = \frac{(W/L)_2}{(W/L)_1}$$

$$\frac{I_{out}}{600 \mu A} = \frac{0.5}{2}$$

$$I_{out} = 150 \mu A$$

End of Solution

