

• Try to avoid over writing



• Improve presentation

**MADE EASY**  
Leading Institute for ESE, GATE & PSUs

# ESE 2026 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

## Electrical Engineering

### Test-2 : Digital Electronics + Microprocessors + Electrical Circuits-1 + Systems and Signal Processing-1

Name : .....

Roll No :

#### Test Centres

#### Student's Signature

Delhi

Bhopal

Jaipur

Pune

Hyderabad

#### Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

#### FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	24
Q.2	
Q.3	31
Q.4	
Section-B	
Q.5	41
Q.6	46
Q.7	53
Q.8	
<b>Total Marks Obtained</b>	<b>195</b>

Signature of Evaluator

Cross Checked by

Sourabh  
Verma

## IMPORTANT INSTRUCTIONS

**CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.**

### DONT'S

1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

### DO'S

1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

Section A : Digital Electronics + Microprocessors

(a) Derive a minimized POS expression for the given function and realize using NOR-gate only.

$$F(A, B, C, D) = \Sigma m(0, 1, 3, 4, 6, 9, 13, 14)$$

[12 marks]

$$F(A, B, C, D) = \Pi M(2, 5, 7, 8, 10, 11, 12, 15)$$

AB \ CD	C+D	C+D̄	C̄+D̄	C̄+D
A+B	0	1	3	2
A+B̄	4	5	7	6
Ā+B̄	12	13	15	14
Ā+B	8	9	11	10

$$F = (C+D+\bar{A}) \cdot (A+\bar{B}+\bar{D}) \cdot (\bar{A}+\bar{C}+\bar{D}) \cdot (B+\bar{C}+D)$$

$$= (\bar{A}+C+D) (A+\bar{B}+\bar{D}) (\bar{A}+\bar{C}+\bar{D}) (B+\bar{C}+D)$$

we know  $\overline{A+B} = \bar{A} \cdot \bar{B}$

$$= (\bar{A} + \overline{\bar{C}\bar{D}}) (A + \overline{\bar{B}\bar{D}}) (\bar{A} \cdot \bar{C}\bar{D}) (\bar{B}\bar{D} + \bar{C})$$



$$= (\bar{A} \cdot \overline{\bar{C}\bar{D}}) \cdot (\bar{A} \cdot \overline{\bar{B}\bar{D}}) (\bar{A} \cdot \bar{C}\bar{D}) (\bar{C} \cdot \bar{B}\bar{D})$$

$\bar{A} \cdot \bar{B} = \overline{A+B}$

$$= \overline{A \cdot \bar{C}\bar{D} + \bar{A} \cdot \bar{B}\bar{D} + A\bar{C}\bar{D} + \bar{C}\bar{B}\bar{D}}$$

$$= \overline{A \cdot (\bar{C}+D) + \bar{A} \cdot \bar{B}\bar{D} + A\bar{C}\bar{D} + \bar{C} \cdot (\bar{B}+D)}$$
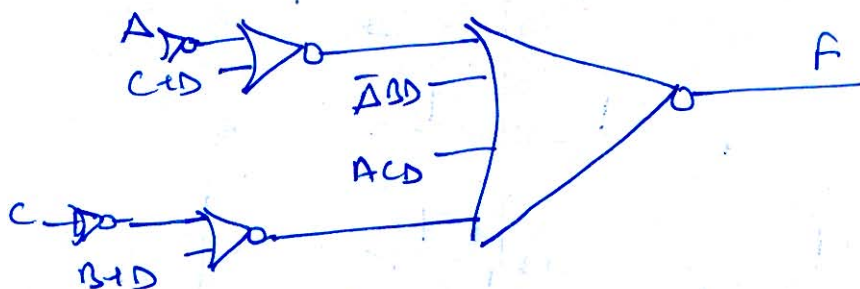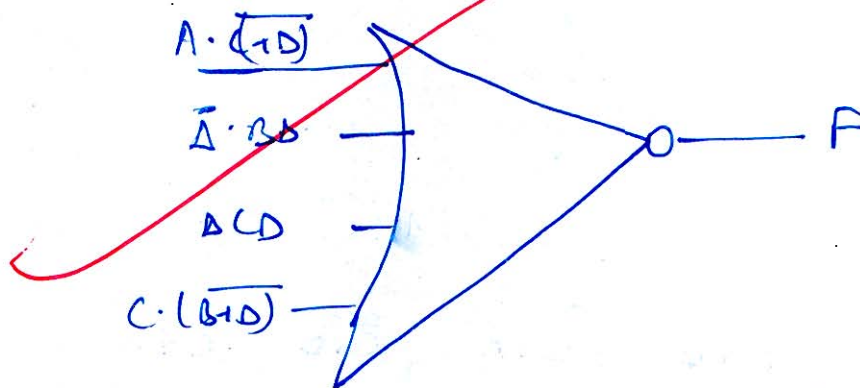
$$F = (\bar{A} + C + D)(A + \bar{B} + D)(\bar{A} + \bar{C} + \bar{D})(B + \bar{C} + D)$$



$$A \cdot \overline{C+D} = \overline{\overline{A \cdot \overline{C+D}}} = \overline{\bar{A} + (C+D)} =$$

8

Go through the made easy solution

(b) Design an odd parity bit generator using four bit input.

[12 marks]

Odd parity bit

no of 1	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Y$
0	0	0	0	0	0
1	0	0	0	1	1
1	0	0	1	0	1
2	0	0	1	1	0
1	0	1	0	0	1
2	0	1	0	1	0
2	0	1	1	0	0
3	0	1	1	1	1
1	1	0	0	0	1
2	1	0	0	1	0
2	1	0	1	0	0
3	1	0	1	1	1
2	1	1	0	0	0
3	1	1	0	1	1
3	1	1	1	0	1
4	1	1	1	1	0

no of 1 = even  $Y = 0$

no of 1 = odd  $Y = 1$  (odd parity)

$$\therefore Y = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$$


K-map

	$\bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$Q_1 \bar{Q}_0$	$Q_1 Q_0$
$\bar{Q}_3 \bar{Q}_2$	0	1		2
$\bar{Q}_3 Q_2$	4		7	6
$Q_3 \bar{Q}_2$	12	13	15	14
$Q_3 Q_2$	8	9	11	10

$$Y = Q_3 \oplus Q_2 \oplus Q_1 \oplus Q_0$$

8

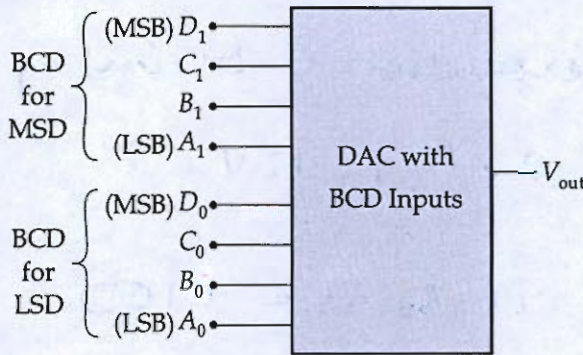(c) A digital to analog converter using BCD input code is shown in the figure below.



If the weight of  $A_1$  is 2 V, then find:

- (i) Step size.
- (ii) Full scale output voltage.
- (iii) Percentage resolution.
- (iv)  $V_{out}$  for  $D_1C_1B_1A_1 = 0110$  and  $D_0C_0B_0A_0 = 0100$ .

[12 marks]

Resol<sup>n</sup> in terms of smallest voltage = step size.

If  $A_1 = 2V$  weight i.e. (0001)

For BCD Input Max<sup>m</sup> weight  $D_1C_1B_1A_1 = 1001$ .

Step size = 2V ← Ans

Full scale o/p voltage = Resol<sup>n</sup> × Decimal equivalent

=  $2 \times 9 = 18V$ .

Percentage Resolution =  $\frac{1}{\text{no. of step discre.}} \times 100$

Total no of step =  $\frac{100}{9999} = 0000$  to 9999

∴ resolution =  $\frac{100}{10000} = 0.01\%$  ← Ans

iv)  $V_{out}$  for  $D_1 C_1 B_1 A_1 = 0110$

$$\begin{aligned} V_{out} &= \text{Resolution} \times \text{Decimal eq. of } 0110 \\ &= 2 \times (6) = 12V \end{aligned}$$

$V_{out}$  for  $D_0 C_0 B_0 A_0 = 0100$

$$\begin{aligned} V_{out} &= \text{Resolution} \times \text{Decimal equivalent of } 0100 \\ &= 2 \times (4) = 6 \text{ Volt} \\ &\quad \swarrow \text{Ans} \end{aligned}$$

4

- (d) List of the functional classification of 8085 instruction set. Give one example for each class.

[12 marks]

Functional classification 8085 instruction set

Program Counter (PC) → address top of next <sup>state</sup>

Stack pointer → Push [SP-2] & Pop [SP+2]

Pair of Accumulator

BC pair, DE pair, HL pair.

There are 5 diff types of instruction type

Register direct Addressing

Immediate Addressing

Register Indirect

Opcode fetch

Memory Read

Memory Write

I/O read

I/O write

4

Incomplete  
solution



- 1 (e) A bar code scanner scans the boxes being shipped from the loading dock and record all the codes in computer memory; the end of the data is indicated by the byte 00. The code 10100011 (A3H) is assigned to 19" television sets. Write a program to count the number of 19" television sets that were shipped from the following data set: Data: FA, 67, A3, B8, A3, A3, FA, 00. Write comments in the program.

[12 marks]

- Q.2 (a) Design a 3-bit counter that goes through the states 2, 4, 5, 7, 2, 4, ... using  $T$ -flip flops. Assume the unused states as don't cares. Check whether the designed counter is self starting or not and there by give the complete sequence diagram for the designed counter.

[20 marks]





- 2 (b) (i) Calculate the delay produced by the following subroutine program of an 8085 microprocessor, which is operating with a clock frequency of 2 MHz.

```
DELAY :   MVI B, 02H
LOOP2  :   MVI C, FFH
LOOP1  :   DCR C
          JNZ LOOP1
          DCR B
          JNZ LOOP2
          RET
```

[14 marks]



2 (b)

(ii) Explain the features of the three sources of interrupts in the 8086 microprocessor.

[6 marks]

Q.2 (c) Draw the state diagram of a modulo-4 UP/DOWN counter. Design the circuit using JK flip flops.

[20 marks]



Q.3 (a) (i) Design a synchronous counter using D-flip flop that counts in the following sequence:  
6, 3, 5, 0, 2, 6, 3, 5, 0, 2, 6

[10 marks]

It is repeating 6 → 3 → 5 → 0 → 2. = used state

Total 5 sequence means 5 state, (Unused state (1, 3, 4))

we know  $2^n > N \Rightarrow 2^n > 5$  so  $n = 3$

no of flip flop required = 3

Dec	Present state			Next State			Flip flop s/d		
	$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1	0	0	1	0
(1)	0	0	1	X	X	X	X	X	X
(2)	0	1	0	1	1	0	1	1	0
(3)	0	1	1	1	0	1	1	0	1
(4)	1	0	0	X	X	X	X	X	X
(5)	1	0	1	0	0	0	0	0	0
(6)	1	1	0	0	1	1	0	1	1
(7)	1	1	1	X	X	X	X	X	X

K-map for  $D_2$

		$Q_1 \bar{Q}_0$	$Q_1 Q_0$
$\bar{Q}_2$	0	X	1
$Q_2$	X	1	1

$D_2 = \bar{Q}_2 \bar{Q}_1$



Q.3 (a) (ii) Explain the working of 3-bit flash type ADC.

[10 marks]


3 bit Flash Type ADC is fastest ADC.

It requires 7 comparators, 02 resistors, 023 encoder

For N bit flash ADC

$(2^N - 1)$  comparators.


$(2^N \times N)$  priority encoder

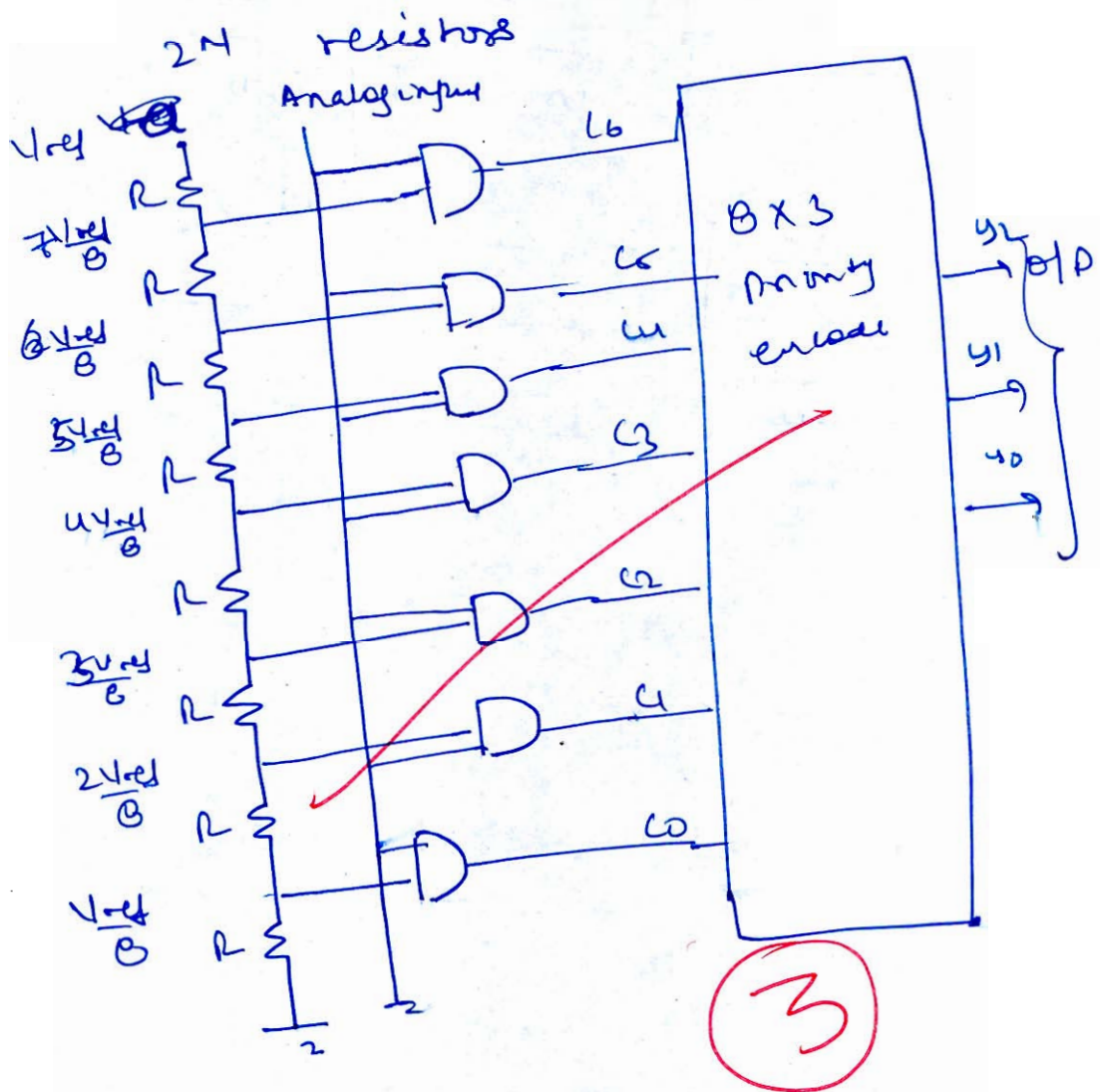

<u>Binary 9/0 Analog</u>	<u>Digital OP</u>	<u>Q/P</u>
	C <sub>6</sub> C <sub>5</sub> C <sub>4</sub> C <sub>3</sub> C <sub>2</sub> C <sub>1</sub> C <sub>0</sub>	Y <sub>2</sub> Y <sub>1</sub> Y <sub>0</sub>
	0 0 0 0 0 0 0	
	0 0 0 0 0 1 0	
	0 0 0 0 1 0 0	
	0 0 0 1 0 0 0	
	0 0 1 0 0 0 0	
	0 1 0 0 0 0 0	
	1 0 0 0 0 0 0	

Q.3 (b)

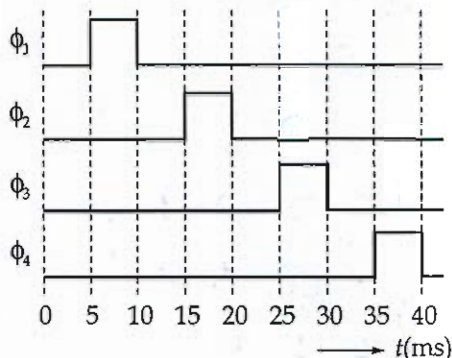- (i) Design a synchronous 3-bit binary up-counter using D-flip flops.
- (ii) A stepper-motor drive circuit requires four periodic signal waveforms, each with a period of 40 ms, as shown below. By using the counter circuit obtained in part (i), design a circuit to generate the necessary signal waveforms for this stepper motor.



[10 + 10 marks]

i)

Synchronous 3 bit Binary up counter using DFF

Present state			next state			Flip flop I/O		
$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

$$D_2 = \sum m(3, 4, 5, 6)$$

$$D_1 = \sum m(1, 2, 5, 6)$$

$$D_0 = \sum m(0, 2, 4, 6)$$

K-map D2

	$\bar{Q}_1\bar{Q}_0$	$\bar{Q}_1Q_0$	$Q_1\bar{Q}_0$	$Q_1Q_0$
$Q_2$	0	1	1	3
$\bar{Q}_2$	1	1	1	6

$$D_2 = \bar{Q}_2Q_1Q_0 + Q_2\bar{Q}_1 + Q_2Q_0$$

$$= Q_2(\bar{Q}_1 + Q_0) + \bar{Q}_2Q_1Q_0$$

$$= Q_2(\bar{Q}_1Q_0 + Q_1Q_0) + \bar{Q}_2Q_1Q_0$$

$$= Q_2 \oplus Q_1Q_0$$

K-map D1

	$\bar{Q}_1\bar{Q}_0$	$\bar{Q}_1Q_0$	$Q_1\bar{Q}_0$	$Q_1Q_0$
$Q_2$		1		1
$\bar{Q}_2$		1		1

$$D_1 = \bar{Q}_1Q_0 + Q_1\bar{Q}_0$$


$$= Q_1 \oplus Q_0$$

K-map D0

	$\bar{Q}_1\bar{Q}_0$	$\bar{Q}_1Q_0$	$Q_1\bar{Q}_0$	$Q_1Q_0$
$Q_2$	1			1
$\bar{Q}_2$	1			1

$$D_0 = \bar{Q}_1\bar{Q}_0 + Q_1Q_0$$

$$D_0 = \bar{Q}_0$$

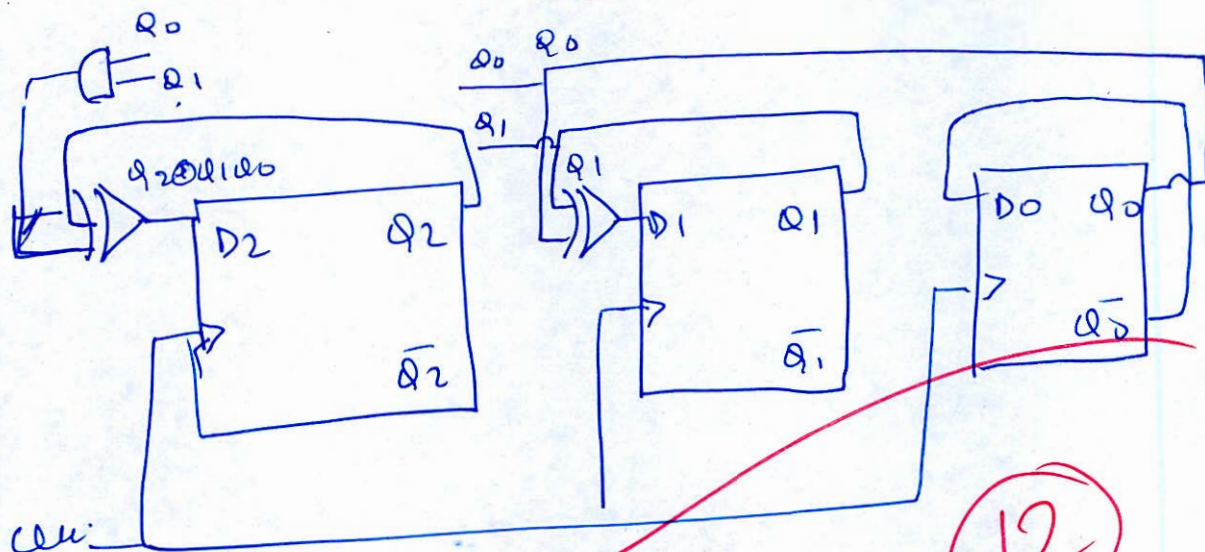

12

$T_2$  times (Given)

~~$T_2 = nT_{clk}$~~

~~$T_{clk} = \frac{1}{BT}$~~

~~$= \frac{1}{320} = \frac{1000}{320} = 3.125 \text{ sec}$~~

Incomplete solution

so As part (i) total 0 state.




3 (c) (i) Write a short note on the flag register of 8086 microprocessor.

[14 marks]

Q) BOB6 total of flag register

S, Z, AC, P, CY, O, D, I, T

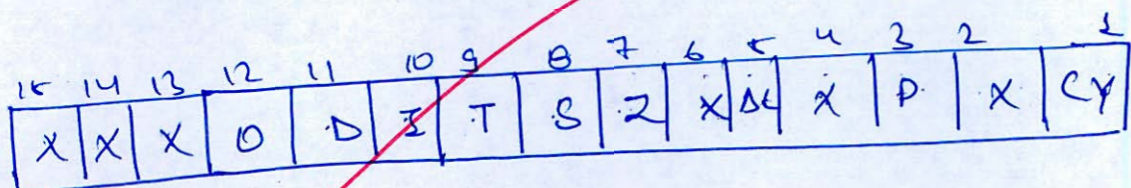

S → sign flag → if MSB = 0 no +ve  
MSB = 1 no -ve

Z → zero flag  
if all are 0 sign flag set  
if not sign flag reset

AC → Auxiliary Carry flag  
Carry Transfer lower nibble to upper nibble

P → Parity flag  
if no of 1's even PF set  
no of 1's odd PF reset

C → Carry flag  
if CY = 1 Carry flag set  
CY = 0 Carry flag reset

O → overflow flag

9

D → Directional flag

I → Interrupt flag

when interrupt occur  
it is 1 otherwise 0

T → Trap flag

Trap is non maskable



- (c) (ii) Write down the purpose of each bit in SIM (Set Interrupt Mask) Instruction. Give three different functions of SIM instruction.

[6 marks]

SIM → It is Mask enable & disable

SME

- Q.4 (a) (i) Write the steps involved in DMA data transfer. Also, describe the functions of 8085 pins which are used in DMA data transfer.

[10 marks]



- Q.4 (a) (ii) How can we generate a square wave with a variable bit rate, using microprocessor?  
Output should be available on a chosen port, using bit 'O'.

[10 marks]

4 (b)

A set of five 16-bit readings of the power consumption of industrial control units is monitored by meters and stored at memory locations starting at 2050H. Each reading occupies two memory locations: the lower order byte is stored first, followed by the higher order byte. The corresponding maximum limits for each control unit are stored at memory locations starting at 2090H, also with the lower order byte stored first followed by the higher order byte. Write an 8085 assembly language program to subtract each reading from its specified maximum limit and store the difference at the same memory locations of the readings. Also provide a provision in the program to call the indicator subroutine if the reading is higher than its maximum limit and then continue checking the remaining reading.

[20 marks]




- 4 (c)
- (i) Given that  $(292)_{10} = 1204$  in some number system, find the base of that system.
  - (ii) In the following series, the same integer is expressed in different number systems. Determine the missing number of the series : 10000, 121, 100, ? , 24, 22, 20.
  - (iii) Add the binary numbers of 1101.101 and 111.011. Find its decimal equivalent.
  - (iv) Subtract 14 from 46 using 8-bit 2's complement arithmetic.

[5 × 4 marks]



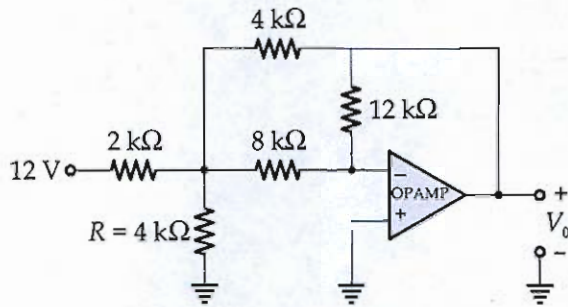**Section B : Electrical Circuits-1 + Systems and Signal Processing-1**


5 (a) In the operational amplifier circuit shown in figure below, calculate the current in  $R = 4\text{ k}\Omega$  resistor, using Thevenin's theorem.



[12 marks]

By virtual short

$$V_A = V_B = 0$$

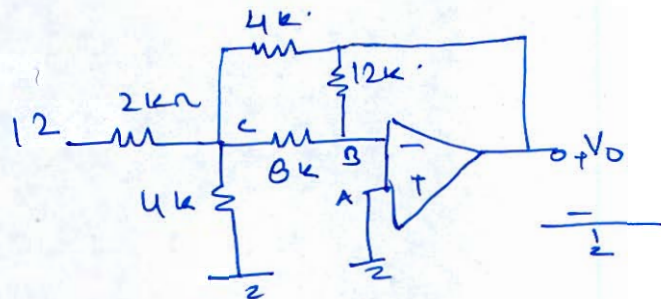

Apply KCL at node c

$$\frac{V_c - 12}{2} + \frac{V_c}{4} + \frac{V_c - V_B}{8} + \frac{V_c - V_0}{4} = 0$$

$$4V_c - 4B + 2V_c + V_c - 0 + 2V_c - 2V_0 = 0$$

$$9V_c - 2V_0 = 4B \quad \text{--- (1)}$$

11

Apply KCL at node B

$$\frac{V_B - V_c}{8} + \frac{V_B - V_0}{12} = 0$$

$$3V_B - 3V_c + 2V_B - 2V_0 = 0$$

Good Approach

As  $V_B = 0$   $3V_c = -2V_0$

Apply in eqn (1)

$$9V_c - 2V_0 = 4B \Rightarrow 9V_c + 3V_c = 4B$$

$$\text{so } V_c = 4V$$

$$I_{4k\Omega} = \frac{V_c}{4} = \frac{4}{4} = 1\text{ mA} \quad \leftarrow \text{Ans}$$



2.5 (b) The input  $x[n]$  and the impulse response  $h[n]$  of a discrete time LTI system are given by:

$$x[n] = u[n]$$

$$h[n] = \alpha^n u[n]; \quad 0 < \alpha < 1$$

Compute the output  $y[n]$  by method of convolution.

[12 marks]

Given:

$$x[n] = u[n], \quad h[n] = \alpha^n u[n] \quad 0 < \alpha < 1$$

To find  $y[n]$  by convolution method.

Sol<sup>n</sup>: we know convolution formulae

$$y[n] = x[n] * h[n]$$

$$= \sum_{k=-\infty}^{\infty} x[k] h[n-k] = \sum_{k=-\infty}^{\infty} h[k] x[n-k]$$

$$= \sum_{k=-\infty}^{\infty} u[k] \cdot \alpha^{n-k} u[n-k] = \sum_{k=0}^{\infty} \alpha^{n-k} u[n-k]$$

$$= \sum_{k=0}^{\infty} \alpha^k u[k] * u[n-k] = \sum_{k=0}^{\infty} \alpha^k u[n-k]$$

$$= \sum_{k=0}^{\infty} \alpha^k =$$

(It is summation  
of GP series

where  $\alpha < 1$

$$= 1 + \alpha + \alpha^2 + \dots + \alpha^n$$

$$y[n] = \frac{1 - \alpha^{n+1}}{1 - \alpha}$$

where  $\alpha < 1$ .

$n \geq 0$


↳ Ans



Good  
Approach



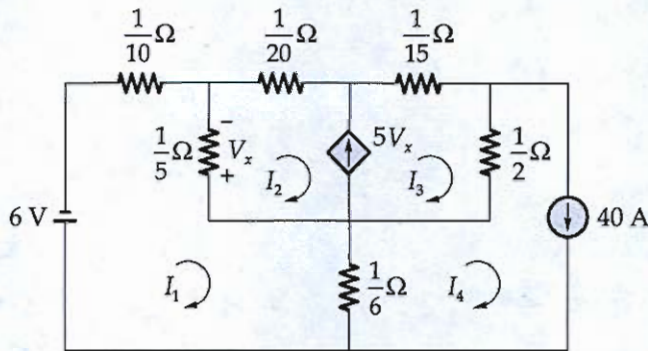
2.5 (c) Find currents  $I_1, I_2, I_3$  and  $I_4$ .



[12 marks]

To find:

$I_1, I_2, I_3, I_4$

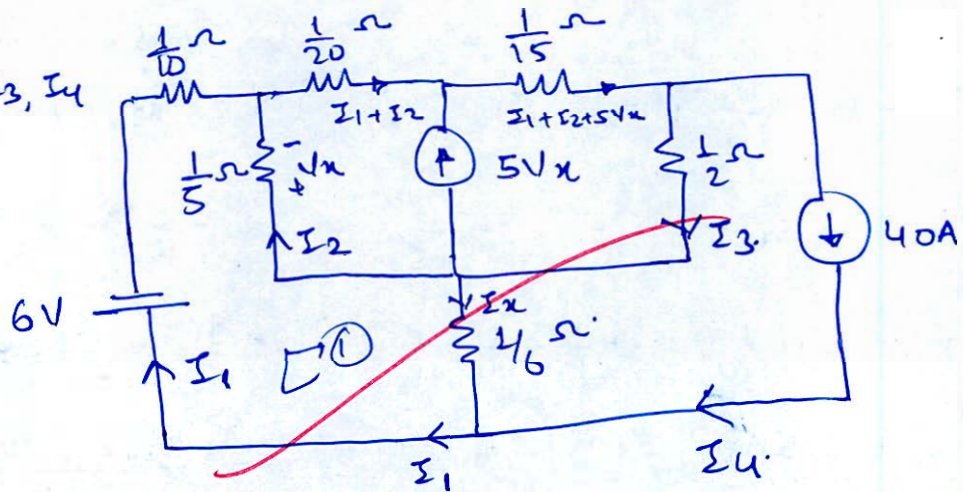

Current in  $\frac{1}{6} \Omega$  resistor =  $I_x$

$$I_x + 5V_x \quad I_x + I_4 = I_1 \Rightarrow I_x = (I_4 - I_1)$$

$$I_x = (I_1 - I_4)$$

Also  $I_x + 5V_x + I_2 = I_3$

$\& I_2 = \frac{V_x}{1/5} = 5V_x$  so  $I_x + 2I_2 = I_3$

so  $I_x = I_3 - 2I_2 = I_1 - I_4 \Rightarrow I_3 + I_4 = I_1 + 2I_2$

Also current in  $\frac{1}{20} \Omega = I_1 + I_2$

$$I_1 + I_2 + 5V_x = I_3 + 40$$

$$I_4 = 40A$$

$$I_1 + 2I_2 = I_3 + 40$$

$$I_2 = 5V_x$$

$$I_x = I_1 - I_4 = I_3 - 2I_2$$

Apply KVL loop 1

$$-6 - \frac{1}{10} I_1 + V_x - \frac{1}{6} I_x = 0 \Rightarrow \frac{1}{6} I_x + \frac{1}{10} I_1 + 6 = V_x$$

$$\frac{(I_1 - I_4)}{6} + \frac{I_1}{10} + 6 = \frac{I_2}{5}$$

$$\frac{I_1}{6} + \frac{I_1}{10} - \frac{40}{6} + 6 = \frac{I_2}{5}$$

$$\frac{5I_1 + 3I_1}{30} - \frac{I_2}{5} = \frac{40}{6} - 6$$

$$\frac{8I_1}{30} - \frac{I_2}{5} = \frac{4}{6} \Rightarrow \frac{8I_1 - 6I_2}{30} = \frac{20}{30}$$

Proof above

$$4I_1 - 3I_2 = 20 \quad \text{--- (1)}$$

$$I_1 + 2I_2 = I_3 + 40$$

$$I_4 = 40A$$

$$I_2 = 5V_x$$

$$I_x = I_1 - I_4 = I_3 - 2I_2$$

Again apply KVL in loop 1

$$-6 - \frac{1}{10} I_1 - \frac{1}{20} (I_1 + I_2) - \frac{1}{15} (I_1 + I_2 + 5V_x) - \frac{1}{5} I_3 - \frac{1}{6} I_x = 0$$

$$-6 - \frac{1}{10} I_1 - \frac{1}{20} I_1 - \frac{I_2}{20} - \frac{1}{15} (I_1 + 2I_2) - \frac{1}{2} I_3 - \frac{1}{6} (I_1 - 40) = 0$$

$$6 + I_1 \left( \frac{1}{10} + \frac{1}{20} + \frac{1}{15} + \frac{1}{6} \right) + I_2 \left( \frac{1}{20} + \frac{2}{15} \right) + \frac{1}{2} I_3 = \frac{40}{6}$$

$$6 + \frac{1}{10} I_1 + \frac{1}{20} I_1 + \frac{I_2}{20} + \frac{1}{15} I_2 + \frac{2}{15} I_2 + \frac{(I_1 + 2I_2 - 40)}{2} + \frac{1}{6} (I_1 - 40) = \frac{40}{6}$$

$$6 + I_1 \left( \frac{6+3+4+10}{60} \right) + I_2 \left( \frac{3+8}{60} \right) + \frac{I_1}{2} + I_2 - 40 = \frac{40}{6}$$

$$I_1 \left( \frac{23}{60} + \frac{1}{2} \right) + I_2 \left( \frac{11}{60} + 1 \right) = 40 + \frac{40}{6} - 6 = \frac{244}{6}$$

$$I_1 (23+30) + I_2 (60+11) = \frac{244}{6} \times 60$$

$$53I_1 + 71I_2 = 2440 \quad \text{--- (2)}$$

Solve eqn 1 & 2

6

Wrong Variable calculated

$$53I_1 + 71 \left( \frac{4I_1 - 20}{3} \right) = 2440 \Rightarrow I_1 (53 + \frac{284}{3})$$

$$\frac{443}{3} I_1 = \frac{8740}{3} \Rightarrow$$


$$\text{so } I_2 = \frac{4I_1 - 20}{3} =$$

$$I_3 = I_1 + 2I_2 - 40 =$$

<del><math>I_1 = 6.586A</math></del>
<del><math>I_2 = 2.101A</math></del>
<del><math>I_3 = -29.22A</math></del>
<del><math>I_4 = 40A</math></del>

Ans

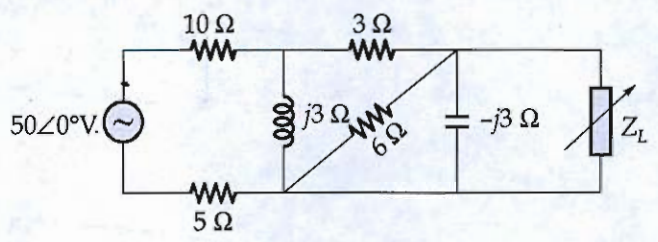
2.5 (d) Find the impedance  $Z_L$  so that maximum power can be transferred to it in the network shown below. Also, find the maximum power delivered to load  $Z_L$ .



[12 marks]


For Max<sup>u</sup> Power find  $V_{th}$  &  $R_{th}$ .

For  $V_{th}$

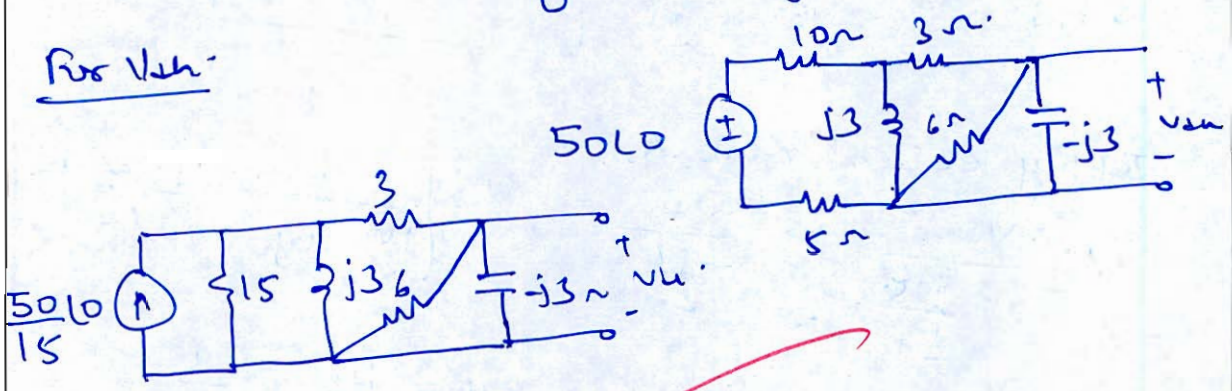

$$6 \parallel -j3 = \frac{6 \times -j3}{6 - j3} = \frac{-j6}{2 - j}$$
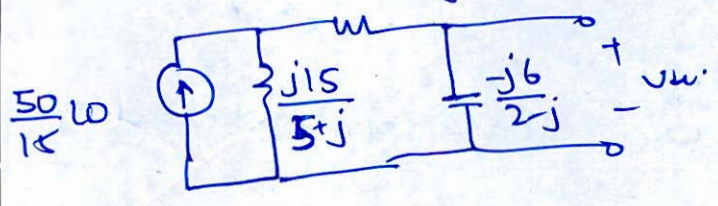
$$15 \parallel j3 = \frac{15 \times j3}{15 + j3} = \frac{j15}{5 + j}$$



$$\frac{50}{15} \times \frac{j15}{5+j}$$


$$= \frac{j50}{5+j}$$

$$= \frac{j50(5-j)}{(5+j)(5-j)}$$

$$= \frac{j250 + 250}{25+1}$$

$$= \frac{250 + j250}{26}$$

$$= 9.615 + j9.615$$

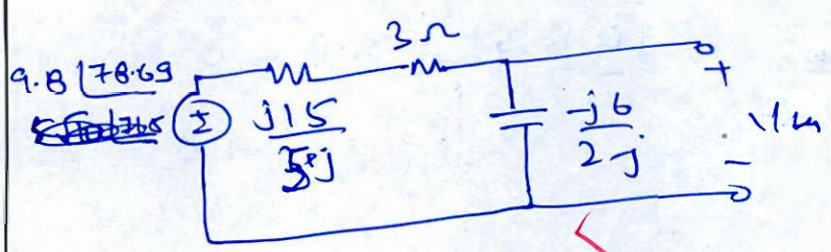


$$V_{th} = (5 + j15) \times \left[ \frac{-j6}{2-j} \right] = 8.82 + j0.36$$


$$= 8.82 \angle 2.33 \text{ volt}$$

For Req

Deactivate  
voltage  
source

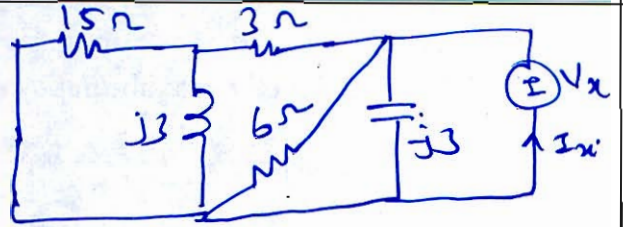
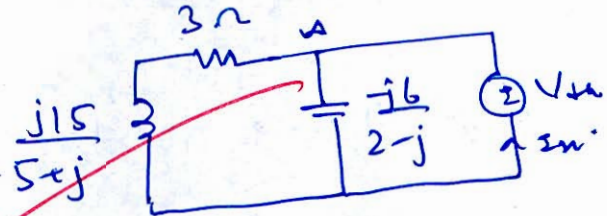
$$\frac{15 \parallel j3}{15 + j3} = \frac{j15}{5+j}$$



Apply KCL at node A

$$I_x = \frac{V_{th}}{3 + \frac{j15}{5+j}} + \frac{V_{th}}{\frac{-j6}{2-j}} \Rightarrow V_{th} \left[ \frac{5+j}{15+10j} + \frac{j-2}{j6} \right]$$

$$I_x = V_{th} \left[ \frac{41}{122} + \frac{12j}{61} \right] \Rightarrow R_{th} = \frac{V_{th}}{I_x} = \frac{1}{\frac{41}{122} + \frac{12j}{61}}$$

$$Z_{th} = 2.216 - 1.297j$$

For Max<sup>m</sup> Power  $Z_L = Z_{th}^* = 2.216 + 1.297j$   
 ↳ Ans

For Max<sup>m</sup> Power delivered to load  ~~$Z_L$~~

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(8.836)^2}{4 \times 2.216} = 8.8 \text{ watt}$$

↳ Ans

④

- 2.5 (e) Show that the resonant frequency  $\omega_0$  of an R-L-C series circuit is geometric mean of  $\omega_1$  and  $\omega_2$ , the lower and upper half-power frequencies respectively.

[12 marks]

To proof:  $\omega_0 = \sqrt{\omega_1 \omega_2}$ .

We know

lower half power freq =  $\omega_1$

upper half power freq =  $\omega_2$ .

For series R-L-C

$\omega_1$  occur

when  $P = \frac{P_{max}}{2}$

$$I = \frac{I_{max}}{\sqrt{2}}$$

$$\frac{V}{Z} = \frac{V}{\sqrt{2}R}$$

$$Z = \sqrt{2}R$$

$$R + j\omega L - \frac{1}{j\omega C} = \sqrt{2}R$$

$$R + (j\omega L - \frac{1}{j\omega C}) = \sqrt{2}R$$

$$\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = \sqrt{2}R$$


$$R^2 + \omega^2 L^2 + \frac{1}{\omega^2 C^2} - \frac{2L}{C} = 2R^2$$

$$R^2 + \frac{2L}{C} + \omega^2 L^2 + \frac{1}{\omega^2 C^2} = 0$$

$$\frac{\omega^4 L^2 C^2 + 1}{\omega^2 C^2} + R^2 + \frac{2L}{C} = 0$$

So by solving  $\omega$  we get

$$\omega_1, \omega_2$$

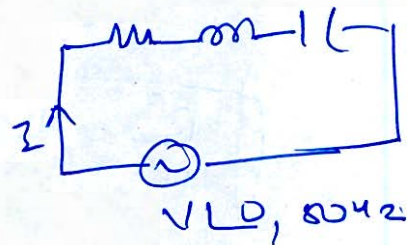

$$\omega_1 = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\omega_2 - \omega_1 = \frac{R}{2L} - \left(-\frac{R}{2L}\right) = \frac{R}{L}$$

$$\omega_1 \omega_2 = \left(-\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}\right) \left(\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}\right)$$

$$= \left(\sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}\right)^2 - \left(-\frac{R}{2L}\right)^2$$

$$= \frac{R^2}{4L^2} + \frac{1}{LC} - \frac{R^2}{4L^2} = \frac{1}{LC}$$

Also resonant frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$  rad/s.

$$\omega_1 \omega_2 = \omega_0^2$$


$$\omega_0 = \sqrt{\omega_1 \omega_2} \text{ rad/s.}$$

∴ Hence proved

9

Good  
Approach

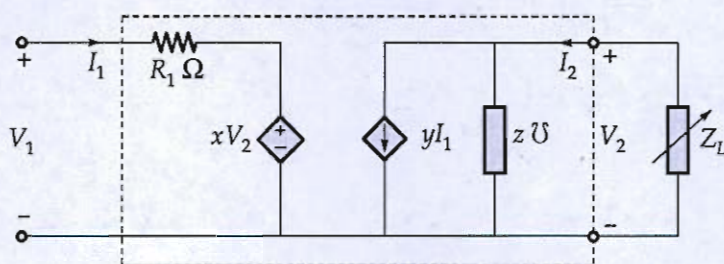2.6 (a) Consider a two port network shown in figure below,



If transmission parameters matrix of the network is  $\begin{bmatrix} 10^{-2} & 10^2 \\ 0 & 10^{-1} \end{bmatrix}$ .

Then, calculate:

- parameters of the circuit:  $R_1$ ,  $x$ ,  $y$  and  $z$ .
- the value of load impedance ( $Z_L$ ), for maximum power transfer.
- maximum power transfer to load for  $V_1 = 0.1$  volt.

[20 marks]

$$\text{Given T parameter} = \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{1}{100} & 100 \\ 0 & \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = \frac{1}{100} V_2 - 100 I_2$$


$$I_1 = -\frac{I_2}{10}$$

Also by Given circuit

in N/w 1  
Apply KVL

$$V_1 - I_1 R_1 - x V_2 = 0$$

$$V_1 = x V_2 + I_1 R_1 \quad (1)$$

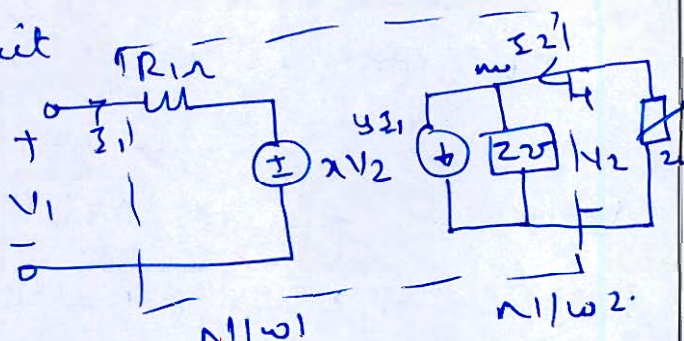

Also Apply KCL in N/w 2 at node n

$$I_2 = y I_1 + V_2 Z \quad \text{so} \quad y I_1 = I_2 - V_2 Z$$

$$I_1 = \frac{I_2}{y} - \frac{Z}{y} V_2 \quad (2)$$

Put value of  $I_1$  in eq<sup>n</sup> (1)

$$V_1 = x V_2 + R_1 \left( \frac{I_2}{y} - \frac{Z}{y} V_2 \right) = V_2 \left( x - \frac{2R_1 Z}{y} \right) + \frac{R_1 I_2}{y}$$

So  $V_1 = \left(x - \frac{2R_1}{y}\right) V_2 + \frac{R_1}{y} (I_2) \quad \text{--- (3)}$

By eq<sup>n</sup> 2  $I_1 = \frac{-2}{y} V_2 + \frac{1}{y} I_2$

Compare above with eq<sup>n</sup> 3 & 2 with Given transmission parameter matrix.

$V_1 = \frac{V_2}{100} - 100 I_2$

$I_1 = -\frac{I_2}{10}$

So  $\frac{1}{y} = -\frac{1}{10} \Rightarrow y = -10$

$\frac{R_1}{y} = -100 \Rightarrow R_1 = 10000 = 1k\Omega$

$\frac{z}{y} = 0 \Rightarrow z = 0$


$x - \frac{2R_1}{y} = \frac{1}{100} \Rightarrow x = \frac{1}{100}$

i) So  $R_1 = 10000\Omega, x = 0.01, y = -10, z = 0$   
 ↳ Ans

ii) Value of  $Z_L$  for Max<sup>u</sup> Power Transfer.

So Draw circuit apply  $R_1, x, y, z$  value

To find  $Z_L$ :  
 remove  $Z_L$ .

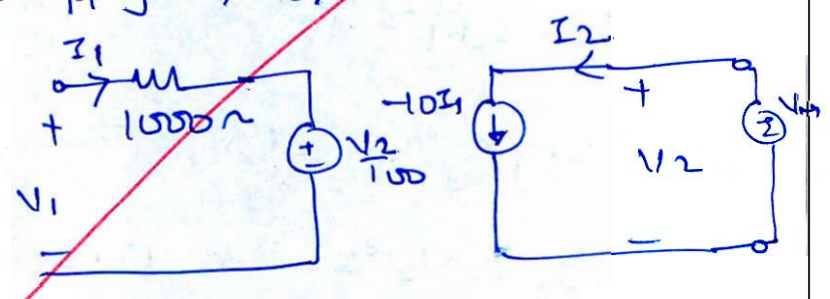

∴  $I_2 = -10 I_1$


∴  $V_{th} = V_2$

∴  $R_{th} = \frac{V_{th}}{I_2}$

Apply KVL loop 1.

$$V_1 - 1000I_1 - \frac{V_2}{100} = 0$$

~~Eq~~ Eq (A)

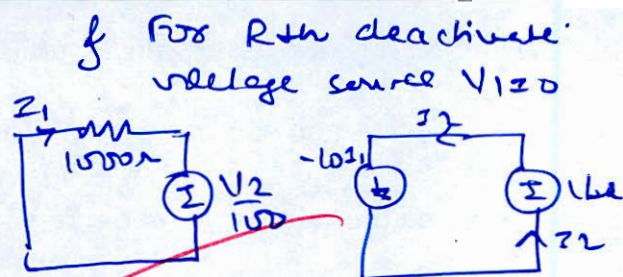

$$-1000I_1 - \frac{V_2}{100} = 0$$

$$I_2 = -10I_1$$

$$-1000I_1 = \frac{V_2}{100}$$

$$-1000 \left( \frac{I_2}{-10} \right) = \frac{V_{th}}{100} \Rightarrow 100 \times 100 = \frac{V_{th}}{I_2}$$

$$Z_L = \frac{V_{th}}{I_2} = 10 \text{ k}\Omega$$

← Ans

For  $V_1 = 0.1 \text{ V}$  max<sup>y</sup> Power Transfer

we know  $P_{max} = \frac{V_{th}^2}{4R_{th}}$

See eq<sup>n</sup> (A) Above.

$$V_1 - 1000I_1 = \frac{V_2}{100} \Rightarrow 0.1 - 1000I_1 = \frac{V_{th}}{100}$$

Also for finding  $V_{th}$  open circuit load that means  $I_2 = 0$  so  $I_1 = 0$  &  $I_2 = -10I_1$

$$+0.1 - 1000(0) = \frac{V_{th}}{100} \Rightarrow V_{th} = 0.1 \times 100 = 10 \text{ V}$$

$$\text{Now } P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{10 \times 10}{4 \times 10000} = 2.5 \text{ mW}$$

$$P_{max} = 0.0025 = 2.5 \times 10^{-3} \text{ watt} = 2.5 \text{ mW}$$

↳ Ans

18

Good  
Approach

Q.6 (b) (i) The transfer function relating the input  $x(t)$  to the output  $y(t)$  of a system is given by

$$G(s) = \frac{1}{(s+3)}. \text{ A unit-step input is applied to the system at time } t = 0. \text{ Assuming that}$$

$y(0) = 3$ , find the value of  $y(t)$  at time  $t = 1$ .

[12 marks]

Given

$$G(s) = \frac{1}{s+3} = \frac{Y(s)}{X(s)}$$

unit step I/P  $x(t) = u(t)$  at  $t=0$ .

$$y(0) = 3$$

To find  $y(t)$  at  $t=1$ .

Ans

$$G(s) = \frac{Y(s)}{X(s)} = \frac{1}{s+3}$$

$$sY(s) + 3Y(s) = X(s)$$

Apply ZLT on above eq<sup>n</sup>.

$$Y(s)[s+3] = X(s)$$

$$y(t) = x(t) \cdot g(t)$$

$$Y(s) = X(s) \cdot G(s)$$

$$= \frac{1}{s} \cdot \frac{1}{s+3} = \frac{1}{3} \left( \frac{1}{s} - \frac{1}{s+3} \right)$$

Apply ZLT

$$y(t) = \frac{1}{3} (1 - e^{-3t}) u(t)$$

Above is forced response

$$y(t)_{\text{total}} = y_{\text{natural resp}} + y_{\text{forced resp}}$$

$$y(t)_{\text{total}} = y_0 + \frac{1}{3} (1 - e^{-3t}) u(t)$$

$y_0$  means value of  $y$  at  $t=0$ .

5

$$y_{total} = 3 + \frac{1}{3}(1 - e^{-3t})u(t)$$

$$y|_{at=1} = 3 + \frac{1}{3}(1 - e^{-3(1)})$$

$$= 3 + \frac{1}{3}(1 - e^{-3})$$

$$y|_{at=1} = 3.316 \rightarrow \underline{\text{Ans}}$$

Q.6 (b) (ii) Consider the signal  $f(t) = 1 + 2\cos(\pi t) + 3\sin\left(\frac{2\pi}{3}t\right) + 4\cos\left(\frac{\pi}{2}t + \frac{\pi}{4}\right)$ , where  $t$  is in seconds. Find its fundamental time period.

(iii) For a periodic signal  $v(t) = 30\sin 100t + 10\cos 300t + 6\sin\left(500t + \frac{\pi}{4}\right)$ , find the fundamental frequency in rad/s.

[6 + 2 marks]

$$f(t) = 1 + 2\cos \pi t + 3\sin \frac{2\pi}{3}t + 4\cos \left(\frac{\pi}{2}t + \frac{\pi}{4}\right)$$

$$\omega_1 = \pi, \quad \omega_2 = \frac{2\pi}{3}, \quad \omega_3 = \frac{\pi}{2}$$

$$T_1 = \frac{2\pi}{\omega_1} = \frac{2\pi}{\pi} = 2, \quad T_2 = \frac{2\pi}{\omega_2} = \frac{2\pi}{2\pi/3} = 3, \quad T_3 = \frac{2\pi}{\omega_3} = \frac{2\pi}{\pi/2} = 4$$

Fundamental Time period

$$T = \text{LCM}(T_1, T_2, T_3) = \text{LCM}(2, 3, 4) = 12$$

But above dc function also given i.e. 1.

So  $f(t) = (\text{Sum of 1 + Periodic } f^n)$

1 is always continuous

if we know

$$f(t) = \text{Sum of periodic + periodic} = \text{periodic}$$

$$\text{HCF}(\omega_1, \omega_2, \omega_3, \omega) = \text{HCF}(1, \pi, \frac{2\pi}{3}, \frac{\pi}{2}) = 1$$

$$\text{Fundamental time period} = T = \frac{2\pi}{\omega} = \frac{2\pi}{1} = 2\pi \text{ sec.}$$

$$v(t) = 30\sin 100t + 10\cos 300t + 6\sin\left(500t + \frac{\pi}{4}\right)$$

$$\omega_1 = 100, \quad \omega_2 = 300, \quad \omega_3 = 500$$

$$\text{Fundamental freq} = \omega_0 = \text{HCF}(\omega_1, \omega_2, \omega_3)$$

$$= \text{HCF}(100, 300, 500) = 100$$

$$\boxed{\omega_0 = 100 \text{ rad/s}} \leftarrow \text{Ans}$$


5

(iii)

6 (c) (i) The figure shows a triangular pulse which is zero for all time except  $-\frac{a}{2} \leq t \leq \frac{a}{2}$ . For

this pulse:

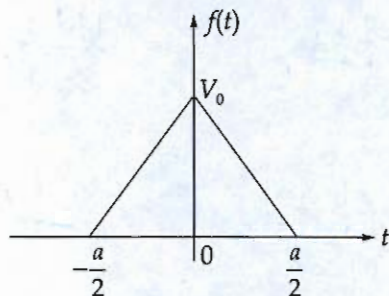- determine the Fourier transform,
- sketch the continuous amplitude spectrum.



[12 marks]

1) To find Fourier transform:

$$f(t) = V_0 \cos\left(\frac{t}{a/2}\right)$$

differentiate  $f(t)$  w.r.to  $t$

$$\text{slope} = \frac{V_0}{a/2} = \frac{2V_0}{a}$$

Now

$$\frac{df(t)}{dt} = \frac{2V_0}{a} \left[ u\left(t + \frac{a}{2}\right) \right]$$

$$- \frac{4V_0}{a} \left[ u(t-0) \right] + \frac{2V_0}{a} \left[ u\left(t - \frac{a}{2}\right) \right]$$

Apply Fourier Transform


$$j\omega F(\omega) = \frac{2V_0}{a} \left[ \frac{e^{+s\frac{a}{2}}}{s} \right] - \frac{4V_0}{a} \times \frac{1}{s} + \frac{2V_0}{a} \frac{e^{-s\frac{a}{2}}}{s}$$

Here  $s = j\omega$

$$j\omega F(\omega) = \frac{2V_0}{a} \frac{e^{j\omega\frac{a}{2}}}{j\omega} - \frac{4V_0}{aj\omega} + \frac{2V_0}{a} \frac{e^{-j\omega\frac{a}{2}}}{j\omega}$$

$$j\omega F(\omega) = \frac{2V_0}{aj\omega} \left[ e^{j\omega\frac{a}{2}} + e^{-j\omega\frac{a}{2}} \right] - \frac{4V_0}{aj\omega}$$
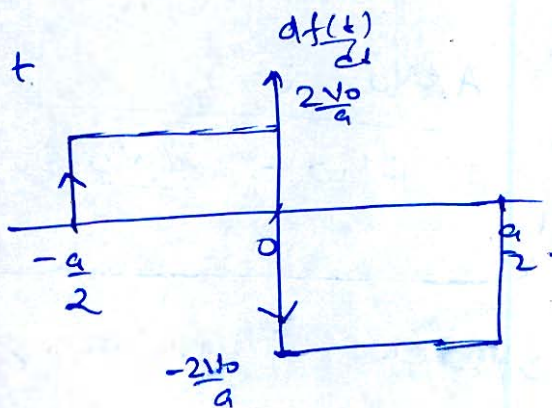
$$= \frac{2V_0}{aj\omega} \left[ 2\cos\left(\frac{\omega a}{2}\right) \right] - \frac{4V_0}{aj\omega}$$



$$\begin{aligned}
 F(\omega) &= \frac{4V_0 \cos\left(\frac{a\omega}{2}\right)}{a(j\omega)^2} - \frac{4V_0}{a(j\omega)^2} \\
 &= \frac{4V_0}{a\omega^2} \left[ \frac{\cos\left(\frac{a\omega}{2}\right)}{-1} + 1 \right] = \frac{4V_0}{a\omega^2} [1 - \cos\left(\frac{a\omega}{2}\right)] \\
 &= \frac{4V_0}{a\omega^2} \times 2\sin^2\left(\frac{a\omega}{4}\right) = \frac{8V_0}{a\omega^2} \frac{\sin^2\left(\frac{a\omega}{4}\right)}{\left(\frac{a\omega}{4}\right)^2} \times \left(\frac{a\omega}{4}\right)^2 \\
 &= \frac{8V_0}{a\omega^2} \times \frac{a^2\omega^2}{16} \left[ \frac{\sin\left(\frac{a\omega}{4}\right)}{\left(\frac{a\omega}{4}\right)} \right]^2 = \frac{aV_0}{2} \text{Sa}^2\left(\frac{a\omega}{4}\right)
 \end{aligned}$$

Also we know  $\Delta \text{tri}\left(\frac{t}{T}\right) \rightarrow \Delta T \text{Sa}^2\left(\omega \frac{T}{2}\right)$

$$V_0 \text{tri}\left(\frac{t}{a/2}\right) \rightarrow \frac{aV_0}{2} \text{Sa}^2\left(\frac{\omega a}{4}\right)$$



$$A_2 = V_0, T_2 = \frac{a}{2}$$

$$\text{So } F(\omega) = \frac{aV_0}{2} \text{Sa}^2\left(\frac{a\omega}{4}\right)$$

→ Ans

u)

Sketch Continuous Amplitude Spectrum

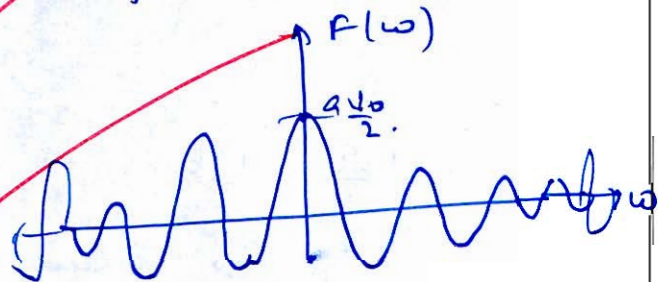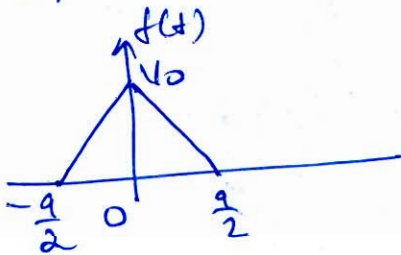

11

Good  
Approach

- 6 (c) (ii) Using duality property show that the Fourier transform of  $\left[ \frac{1}{1+j2\pi t} \right]$  is equal to  $e^f u(-f)$  where  $u(t)$  is the unit step.

[8 marks]

1) duality property states  
if  $x(t) \leftrightarrow X(\omega)$

so w.r.t then  $t \rightarrow -\omega$   
 $X(t) \leftrightarrow 2\pi x(-\omega)$ .

To prove:  $\frac{1}{1+j2\pi t} \leftrightarrow e^f u(-f)$ .

Soln we know Fourier Transform

$$e^{-at} u(t) \leftrightarrow \frac{1}{a+j\omega} = \frac{1}{a+j2\pi f}$$

Apply duality

$$\frac{1}{a+jt} \leftrightarrow 2\pi e^{+a\omega} u(-\omega)$$

If  $a=1$

$$\frac{1}{1+jt} \leftrightarrow 2\pi e^{\omega} u(-\omega)$$

Since:

$$e^{-at} u(t) \leftrightarrow \frac{1}{a+j2\pi f}$$

so  $x(t) \rightarrow x(f)$ .

then for duality  $x(t) \rightarrow x(-f) \cdot \left\{ \begin{array}{l} f \rightarrow t \\ t \rightarrow -f \end{array} \right\}$

$$\frac{1}{a+j2\pi t} \leftrightarrow e^{-a(-f)} u(-(-f))$$

If  $a=1$



$$\frac{1}{1+j2\pi t} \leftrightarrow e^f u(-f)$$

→ hence proved

7



Good Approach

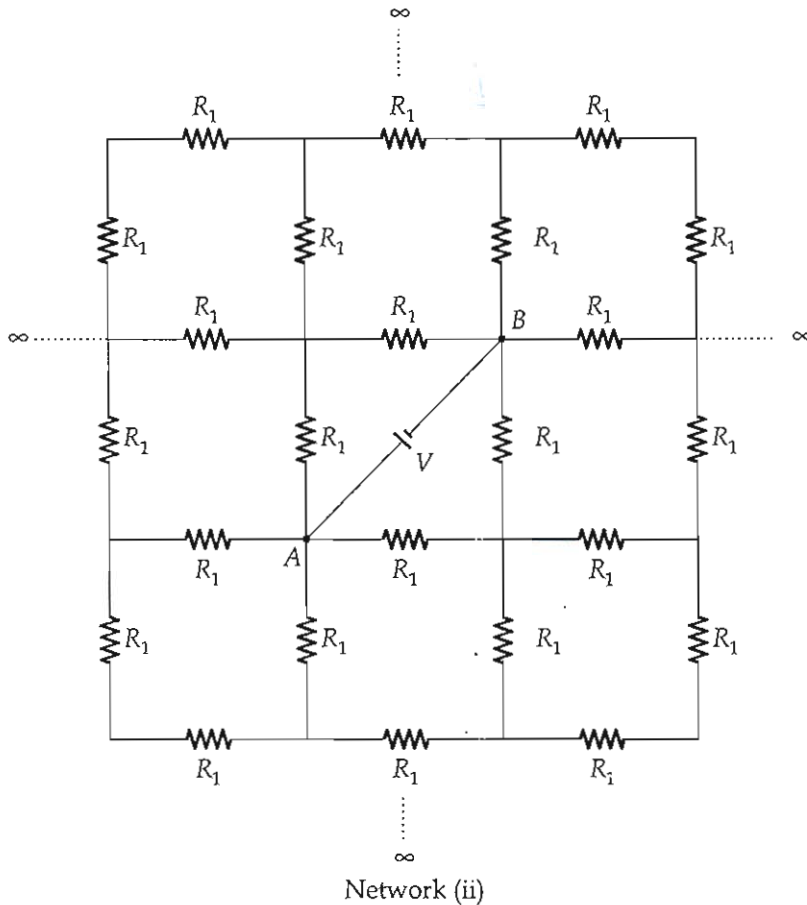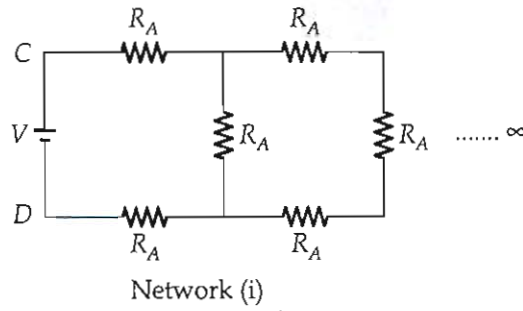Q.7 (a) For the networks shown in figure below,



On applying 10 V voltage source across terminal CD and AB respectively in network (i) and (ii), we get same power delivered by the source. Derive the relationship between the resistance present in network (i) and (ii). And also calculate the power delivered by the source for  $R_A = 10 \Omega$ .

[20 marks]

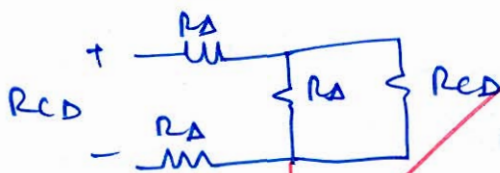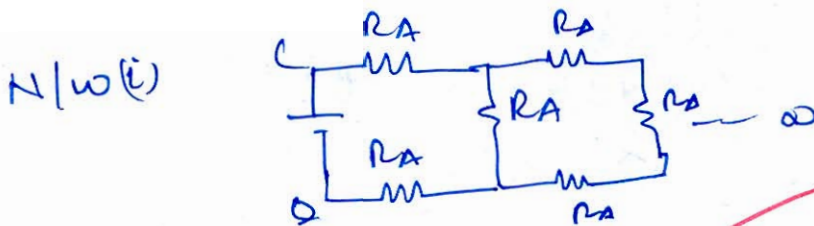

So  $R_{CD} = R_A + \frac{R_A \cdot R_{CD}}{R_A + R_{CD}} + R_A$

$R_{CD} = 2R_A + \frac{R_A \cdot R_{CD}}{R_A + R_{CD}}$

$R_{CD} (R_A + R_{CD}) = 2R_A^2 + 3R_A R_{CD}$


$R_{CD}^2 + R_A R_{CD} = 2R_A^2 + 3R_A R_{CD}$

$$R_{CD}^2 - 2R_A R_{CD} - 2R_A^2 = 0$$

$$R_{CD} = \frac{2R_A \pm \sqrt{4R_A^2 - 4(-2R_A)^2}}{2} = \frac{2R_A \pm 2\sqrt{3}R_A}{2}$$

$$= (1 \pm \sqrt{3})R_A$$

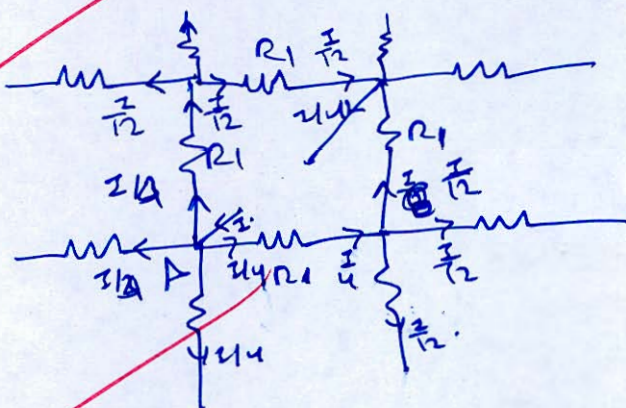As  $R_{CD}$  can't be -ve so  $R_{CD} = (1 + \sqrt{3})R_A$  ✓



$$V_B - \frac{I}{4}R_1 - \frac{I}{12}R_1 - V_A = 0 \Rightarrow V_{BA} = IR_1 \left( \frac{1}{12} + \frac{1}{4} \right)$$

$$= 2IR_1 \frac{1+3}{12} = 3IR_1/3$$

$$R_{AB} = \frac{R_1}{3}$$

Power delivered N/w (1) & N/w 2 same.

$$P_{CD} = P_{AB}$$

$$(I_{CD})^2 R_{CD} = (I_{AB})^2 R_{AB}$$

$$\frac{V_{CD}^2}{R_{CD}} = \frac{V_{AB}^2}{R_{AB}}$$

So  $R_{CD} = R_{AB}$  if  $V_{CD} = V_{AB}$

$$(1 + \sqrt{3})R_A = \frac{R_1}{3}$$

$$R_1 = (3 + 3\sqrt{3})R_A \text{ ✓}$$

$$R_A = \frac{R_1}{3 + 3\sqrt{3}}$$

Power delivered by source for  $R_A = 10 \Omega$

if  $R_A = 10 \Omega$ :

$$R_{CD} = (1 + \sqrt{3})R_A = 10(\sqrt{3} + 1) = 27.32 \Omega$$

$$P = \frac{VCD^2}{RCD} = \frac{10 \times 10}{27.22}$$

$$P = 3.66 \text{ watts} \leftarrow \text{Ans}$$

17



Q.7 (b) Consider a signal  $x(t)$  with Fourier transform  $X(j\omega)$ . Suppose we are given the following facts:

1.  $x(t)$  is real and non-negative.
2.  $F^{-1}\{(1 + j\omega)X(j\omega)\} = Ae^{-2t}u(t)$ , where  $A$  is independent of  $t$ .
3.  $\int_{-\infty}^{\infty} |X(j\omega)|^2 d\omega = 2\pi$

Determine a closed-form expression of  $x(t)$ .

[20 marks]

1 Given  $x(t)$  real & non-ve.

$$2) F^{-1}(X(j\omega) + j\omega X(j\omega)) = Ae^{-2t}u(t)$$

$$F^{-1}(X(j\omega)) + F^{-1}(j\omega X(j\omega)) = Ae^{-2t}u(t)$$

$$x(t) + \frac{dx(t)}{dt} = Ae^{-2t}u(t)$$

$$\text{Or } X(j\omega)[1 + j\omega] = F[Ae^{-2t}u(t)] = \frac{A}{2 + j\omega}$$

$$e^{-at}u(t) \rightarrow \frac{1}{a + j\omega}$$

$$X(j\omega) = \frac{A}{(2 + j\omega)(1 + j\omega)}$$

Apply Partial fraction expansion

$$X(j\omega) = \frac{A}{(2 + j\omega)(1 + j\omega)} = \frac{A_0}{2 + j\omega} + \frac{A_1}{1 + j\omega}$$

$$A_0 |_{j\omega = -2} = \frac{A}{1 - 2} = -A$$

$$A_1 |_{j\omega = -1} = \frac{A}{2 - 1} = A$$

$$X(j\omega) = \frac{-A}{2 + j\omega} + \frac{A}{1 + j\omega}$$

By Applying Inverse Fourier transform

$$x(t) = -A \cdot e^{-2t}u(t) + A e^{-t}u(t)$$

3)

$$\int_{-\infty}^{\infty} |x(j\omega)|^2 d\omega = 2\pi$$

we know by Parseval energy theorem

$$E = \int_{-\infty}^{\infty} |x(t)|^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |X(\omega)|^2 d\omega$$

$$\text{So Energy} = \int_{-\infty}^{\infty} |x(t)|^2 dt = \frac{2\pi}{2\pi} = 1$$

$$\int_{-\infty}^{\infty} [-Ae^{-2t}u(t) + Ae^{-t}u(t)]^2 dt = 1$$

$$\int_{-\infty}^{\infty} [A^2 e^{-4t}u(t) + A^2 e^{-2t}u(t) - 2A^2 e^{-3t}u(t)] dt = 1$$

$$A^2 \int_0^{\infty} e^{-4t} dt + A^2 \int_0^{\infty} e^{-2t} dt - 2A^2 \int_0^{\infty} e^{-3t} dt = 1$$

$$A^2 \left[ \left. \frac{e^{-4t}}{-4} \right|_0^{\infty} + \left. \frac{e^{-2t}}{-2} \right|_0^{\infty} - 2 \left. \frac{e^{-3t}}{-3} \right|_0^{\infty} \right] = 1$$

$$A^2 \left[ -\frac{1}{4}(e^{-\infty} - 1) + \left(-\frac{1}{2}\right)(e^{-\infty} - 1) + \frac{2}{3}(e^{-\infty} - 1) \right] = 1$$

$$A^2 \left[ \frac{1}{4} + \frac{1}{2} - \frac{2}{3} \right] = 1 \Rightarrow A^2 \left[ \frac{3+6-8}{12} \right] = 1$$

$$A^2 = 12$$

$$A = \pm\sqrt{12} = \pm 2\sqrt{3}$$

By Dir 1

So for  $x(t)$  is real & non-negative so  $A = 2\sqrt{3}$

$$\text{Hence } x(t) = A[e^{-t} - e^{-2t}]u(t)$$


$$x(t) = 2\sqrt{3}[e^{-t} - e^{-2t}]u(t)$$

→ Ans

18  
Good Approach



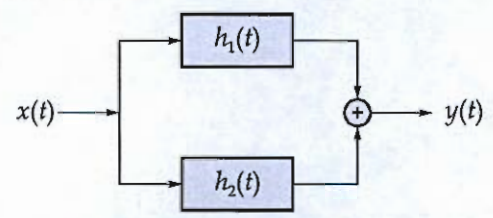7 (c) (i) Consider the parallel combination of two LTI systems shown in the figure,



The impulse responses of the systems are

$$h_1(t) = 2\delta(t+2) - 3\delta(t+1);$$

$$h_2(t) = \delta(t-2)$$

If the input  $x(t)$  is a unit step signal, then find the energy of  $y(t)$ .

[10 marks]

we get  $h_1(t) + h_2(t)$ .

$$= [2\delta(t+2) - 3\delta(t+1)] + \delta(t-2)$$

If  $x(t) = u(t)$ .

$$y(t) = x(t) * [h_1(t) + h_2(t)] = x(t) * [2\delta(t+2) - 3\delta(t+1) + \delta(t-2)]$$

$$y(t) = x(t) * [2\delta(t+2) - 3\delta(t+1) + \delta(t-2)]$$



Now we know convolution property

$$x(t) * \delta(t-t_0) = x(t-t_0)$$


$$y(t) = 2x(t+2) - 3x(t+1) + x(t-2)$$

If  $x(t) = u(t)$

$$so y(t) = 2u(t+2) - 3u(t+1) + u(t-2)$$

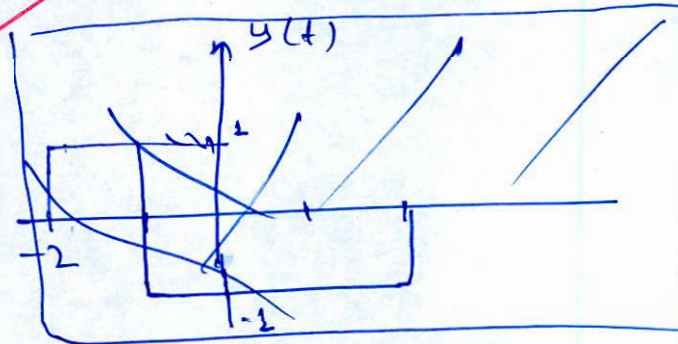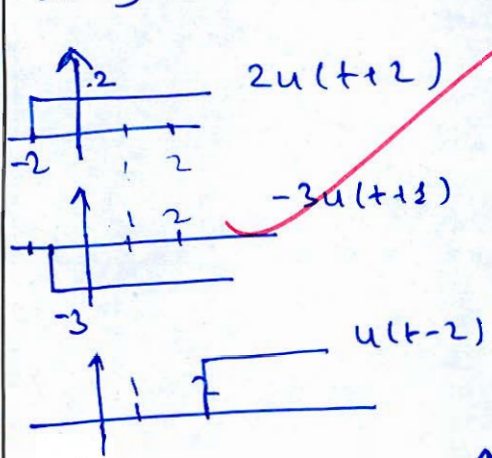

$$y(t) = 2u(t+2) - 3u(t+1) + u(t-2)$$

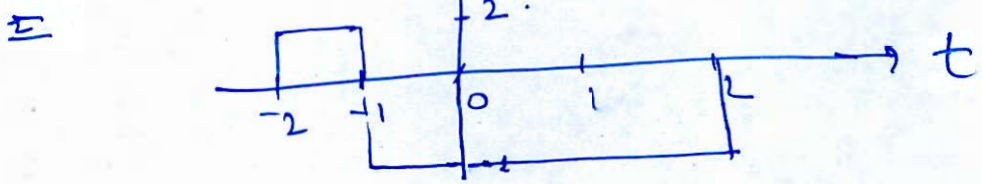

$$\begin{aligned} \text{Energy of } y(t) &= \int_{-\infty}^{\infty} |y(t)|^2 dt \\ &= \int_{-2}^2 y(t)^2 dt \\ &= \int_{-2}^{-1} (2)^2 dt + \int_{-1}^2 (-1)^2 dt = 4[-1 - (-2)] + 1[2 - (-1)] \end{aligned}$$

$$\text{Energy} = 4[1] + 3 = 7 \text{ Joules}$$

↳ Ans

(9)

Good  
Approach

7 (c) (ii) The exponential Fourier series representation of a continuous-time periodic signal

$x(t)$  is defined as  $x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t}$ , where  $\omega_0$  is the fundamental angular frequency

of  $x(t)$  and the coefficients of the series are  $a_k$ . The following information is given about  $x(t)$  and  $a_k$ .

1.  $x(t)$  is real and even, having a fundamental period of 6.
2. The average value of  $x(t)$  is 2.

$$3. a_k = \begin{cases} k, & 1 \leq k \leq 3 \\ 0, & k > 3 \end{cases}$$

Find the average power of the signal  $x(t)$ .

[10 marks]

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t}$$

$$x(t) \longleftrightarrow a_k$$

$$1) x(t) \text{ real even } T = 6$$

$$2) \frac{1}{T} \int_{\langle T \rangle} x(t) dt = 2$$

$$3) a_k = \begin{cases} k & 1 \leq k \leq 3 \\ 0 & k > 3 \end{cases}$$

To find: Avg Power of signal  $x(t)$

$$P_{avg} = \frac{1}{T} \int_{\langle T \rangle} |x(t)|^2 dt$$

$$\omega_0 = \frac{2\pi}{T} = \frac{2\pi}{6} = \frac{\pi}{3}$$

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\frac{\pi}{3}t} = a_1 e^{j\frac{\pi}{3}t} + a_{-1} e^{-j\frac{\pi}{3}t} + a_2 e^{j\frac{2\pi}{3}t} + a_{-2} e^{-j\frac{2\pi}{3}t} + a_3 e^{j\frac{\pi}{3}t} + a_{-3} e^{-j\frac{\pi}{3}t} + a_0$$

$$\text{To find } a_0 = \frac{1}{T} \int_0^T x(t) dt = 2 \rightarrow \text{Given}$$

$$a_n = \frac{1}{T} \int_{\langle T \rangle} x(t) e^{-jn\omega_0 t} dt$$

As  $x(t)$  is real & even  $x(t) = x(-t)$

So it means coefficient is also real & even

$$\text{So } a_k = a_{-k}$$

Avg power we know

$$P = \sum_{n=-\infty}^{\infty} |c_n|^2 = \sum_{k=-\infty}^{\infty} |a_k|^2 = \frac{1}{T} \int_{-T/2}^{T/2} x^2(t) dt$$

$$= a_0^2 + 2(a_1^2 + a_2^2 + a_3^2)$$

As  $a_0 = 2$  &  $a_1 = 1, a_2 = 2, a_3 = 3$   
 $\therefore a_k = k$

So Avg power

$$= 2^2 + 2(1^2 + 2^2 + 3^2)$$


$$= 4 + 2(1 + 4 + 9) = 32$$

$$\boxed{P_{avg} = 32 \text{ watt}} \leftarrow \text{Ans}$$

9

Good Approach

- 3 (a) In the circuit shown in the figure below,  $|V_1| = 200$  V,  $V_2 = 200 \angle 0^\circ$  V and  $|I| = 12$  A. The total power absorbed by the circuit is 1.8 kW. Find  $R_1$ ,  $X_1$  and  $X_2$ .

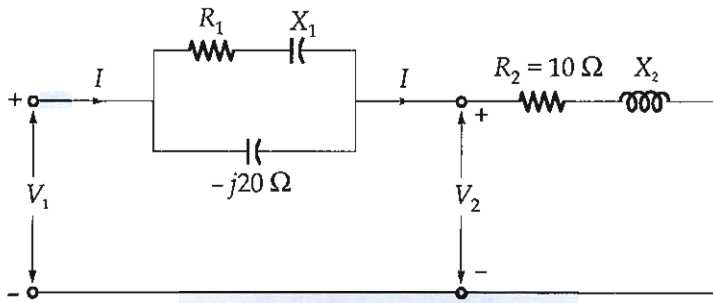

[20 marks]






- Q.8 (b) (i) Consider a continuous-time LTI system for which the input  $x(t)$  and output  $y(t)$  are related by  $y''(t) + y'(t) - 2y(t) = x(t)$ .
1. Find the system function  $H(s)$ .
  2. Determine the impulse response  $h(t)$  for each of the following three cases :  
(1) The system is causal, (2) The system is stable, (3) The system is neither causal nor stable.

[13 marks]



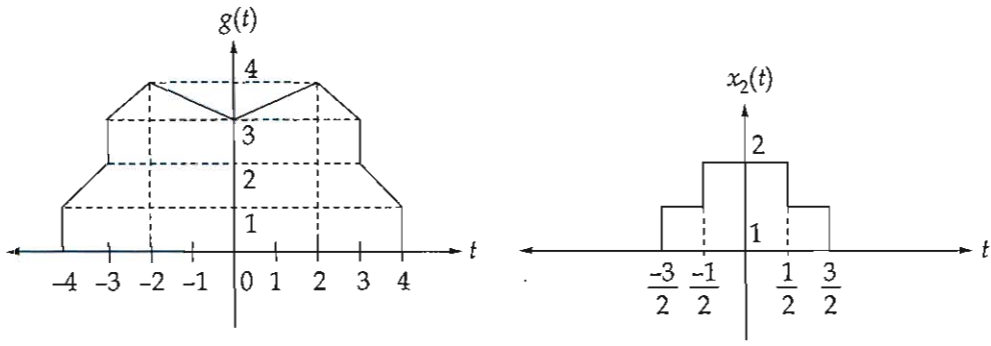Q.8 (b) (ii) The response of an LTI system to an input signal  $x_1(t) = u(t + 1) - u(t - 1)$  is denoted as  $g(t)$ , as illustrated in the figure below. If a new input  $x_2(t)$  is applied to the same system, resulting in an output  $y(t)$ . Determine the value of the output at  $t = 0$ .




[7 marks]

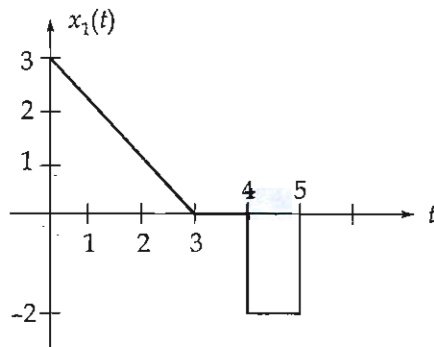(c) Consider a continuous-time LTI system with an impulse response  $h(t)$  defined as a rectangular pulse of amplitude  $A$  and duration  $T$  ( $0 < t < T$ ). When the system is subjected to an input  $x_1(t)$  given below, it produces an output  $y_1(t)$ . It is observed that  $y_1(5) = 0$ .

Furthermore, when the input is  $x_2(t) = \sin\left(\frac{\pi t}{3}\right)u(t)$ , the output  $y_2(t)$  at  $t = 9$  is equal to 9.

Determine the value of the product  $A \times T$ .



[20 marks]



**Space for Rough Work**

---

Space for Rough Work

---

1,  $\pi$ ,  $\frac{4\pi}{3}$ ,  $\frac{5\pi}{3}$

$\Delta m(\frac{h}{2\pi})$

1, 3

$\frac{h}{2\pi}$   
34 + 40  
204 + 40