



MADE EASY

Leading Institute for ESE, GATE & PSUs

ESE 2026 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

Electronics & Telecommunication Engineering

Test-2 : Digital Circuits + Microprocessors and Microcontroller [All topics]

Network Theorv-1 + Signal and Svstems-1 [Part Syllabus]

Name :

Roll No :

Test Centres

Student's Signature

Delhi

Bhopal

Jaipur

Pune

Hyderabad

Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	17
Q.2	
Q.3	
Q.4	33
Section-B	
Q.5	52
Q.6	
Q.7	36
Q.8	38
Total Marks Obtained	176

Signature of Evaluator

Cross Checked by

o Improve your accuracy - -

o Network is important for exam -

o Keep it up. -

Practice more

IMPORTANT INSTRUCTIONS

CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.

DONT'S


1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

DO'S

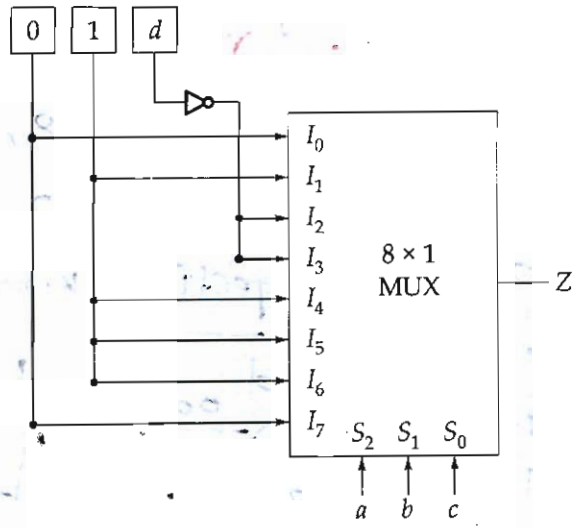1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

Section A : Digital Circuits + Microprocessors & Microcontroller

1 (a) Consider the combinational circuit shown below has four inputs (a, b, c, d) and one output Z.



For the above given combinational circuit,

- (i) construct the truth table.
- (ii) write the minimized logic expression for output $Z = f(a, b, c, d)$.

[12 marks]

ca) Truth Table for the circuit

a	b	c	Z
0	0	0	$I_0 = 0$
0	0	1	$I_1 = 1$
0	1	0	$I_2 = \bar{d}$
0	1	1	$I_3 = d$
1	0	0	$I_4 = 1$
1	0	1	$I_5 = 1$
1	1	0	$I_6 = 1$
1	1	1	$I_7 = 0$

4

a	b	c	d	z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

output (z) can be written -

① $z = \sum m(2, 3, 4, 6, 8, 9, 10, 11, 12, 13)$

respective K-map:

	cd	00	01	11	10
ab	00	0	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$z = a\bar{b} + a\bar{c} + \bar{b}c + \bar{a}b\bar{d}$ - ①

Expression ① is the minimized expression for output z.


Not minimized


1 (b)

(i) Convert n -bit base-3 number to n -bit base-9 number.

(ii) Convert $(211101222211122)_3$ to $()_9$ using the result obtained in part (i).

[6 + 6 marks]

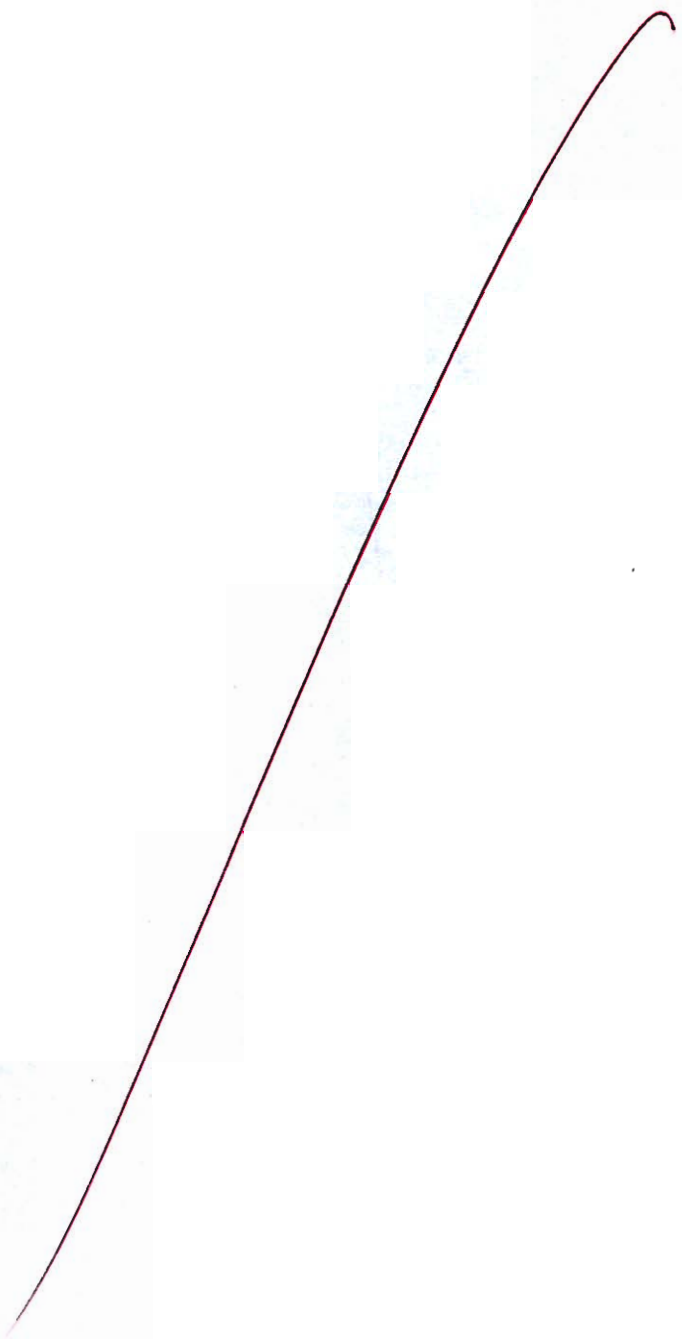

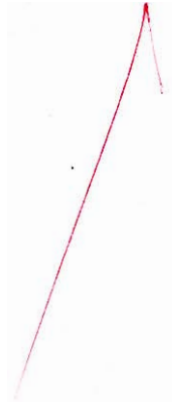

- Q.1 (c) Write an assembly language program using 8086 microprocessor to add two 16-bit hexadecimal numbers stored in memory at addresses 0200 H and 0202 H. Store the result in memory.

[12 marks]



- 1 (d) Using 8085 microprocessor, write an assembly language program to find the 9's complement of a decimal digit stored in memory at address location 2050 H.

[12 marks]



2050H

2051H

2052H

2053H

2054H

2055H

Q.1 (e) Consider the logic function given below:

$$F = ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C + AB$$

- (i) Simplify the above function using K-map.
 (ii) Realize the logic function using only NAND gates.
 (iii) Realize the logic function using only NOR gates.

[12 marks]

Q.1. (e) making a K-map for the above function.

(f)

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10


$$F = AC + AB + A\bar{D}$$

(ii) Using only NAND gates.

$$F = AC + AB + A\bar{D}$$

$$F = \overline{AC} \cdot \overline{AB} \cdot \overline{AD} \quad \text{--- (1)}$$

using (1) to realize circuit

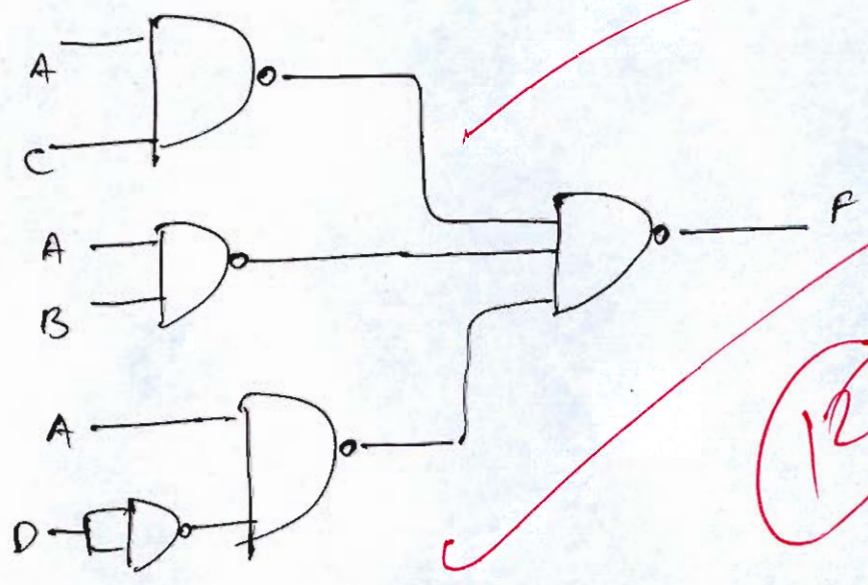


Implementation using NAND

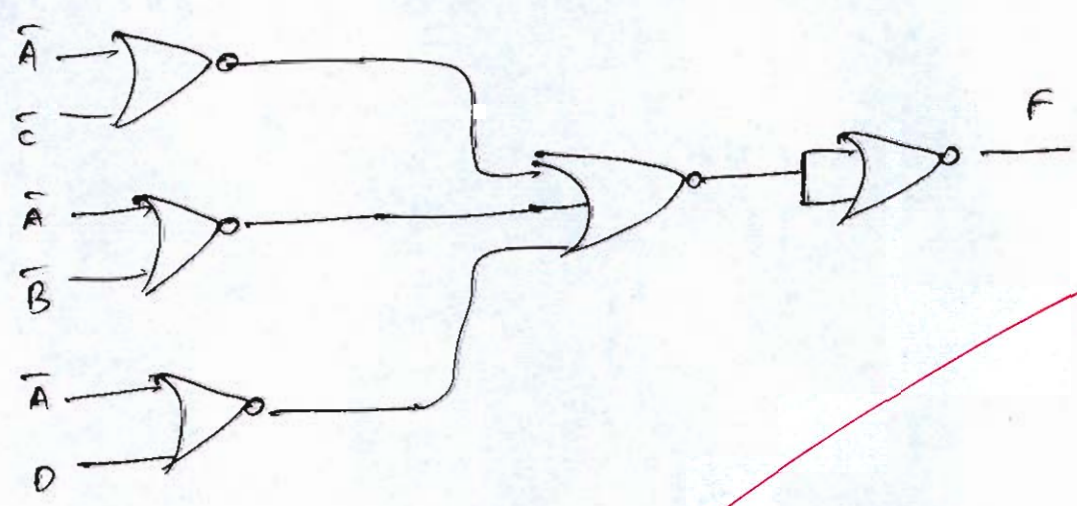(iii) Using NOR, (1) can be rewritten,

$$F = \overline{(\overline{A+C})(\overline{A+B})(\overline{A+D})}$$

$$F = \overline{\overline{A+C} + \overline{A+B} + \overline{A+D}}$$




Implementation using NOR

12
kwf

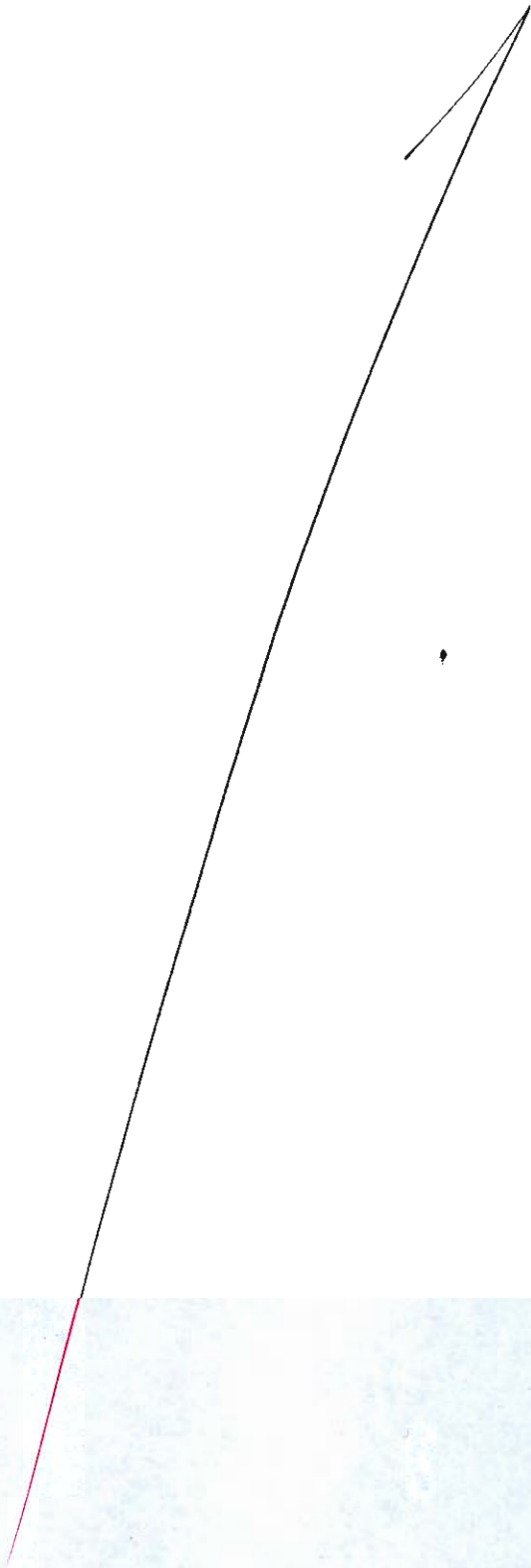
- Q.2 (a) Write an assembly language program for an 8051 microcontroller to generate 100 kHz square wave (70% duty cycle) at Pin P2.0 by using Timer 1 operating in Mode 2. Assume that the microcontroller is operating with 12 MHz crystal oscillator.

[20 marks]


[Faint handwritten assembly code and diagrams are visible through the paper, but they are illegible due to blurriness and bleed-through.]



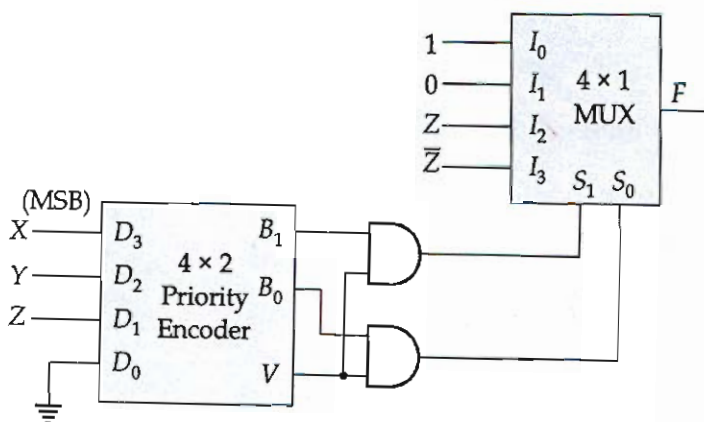- Q.2 (b) For the following combinational circuit, construct the truth table and obtain the simplified SOP expression of the output function (F).




[20 marks]

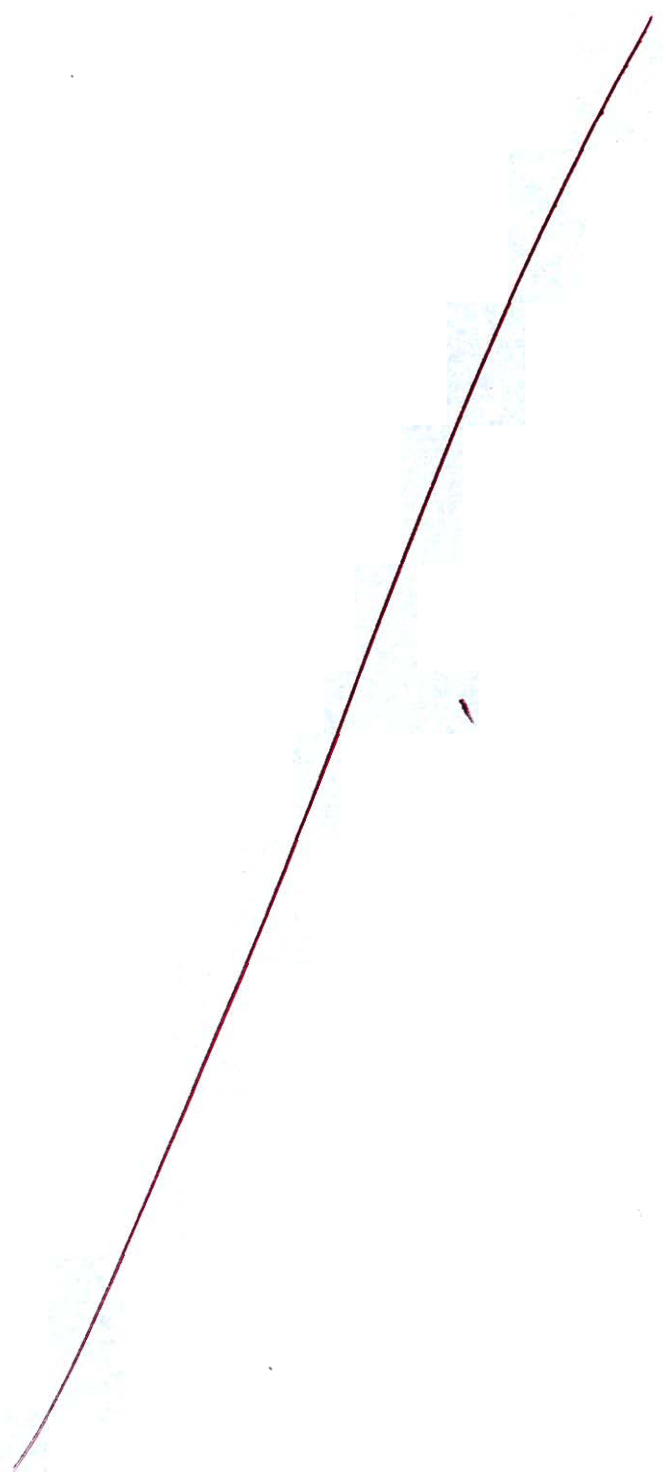


Q.2 (c) Explain different transfer modes of an 8237 DMA controller in active cycle.

[20 marks]

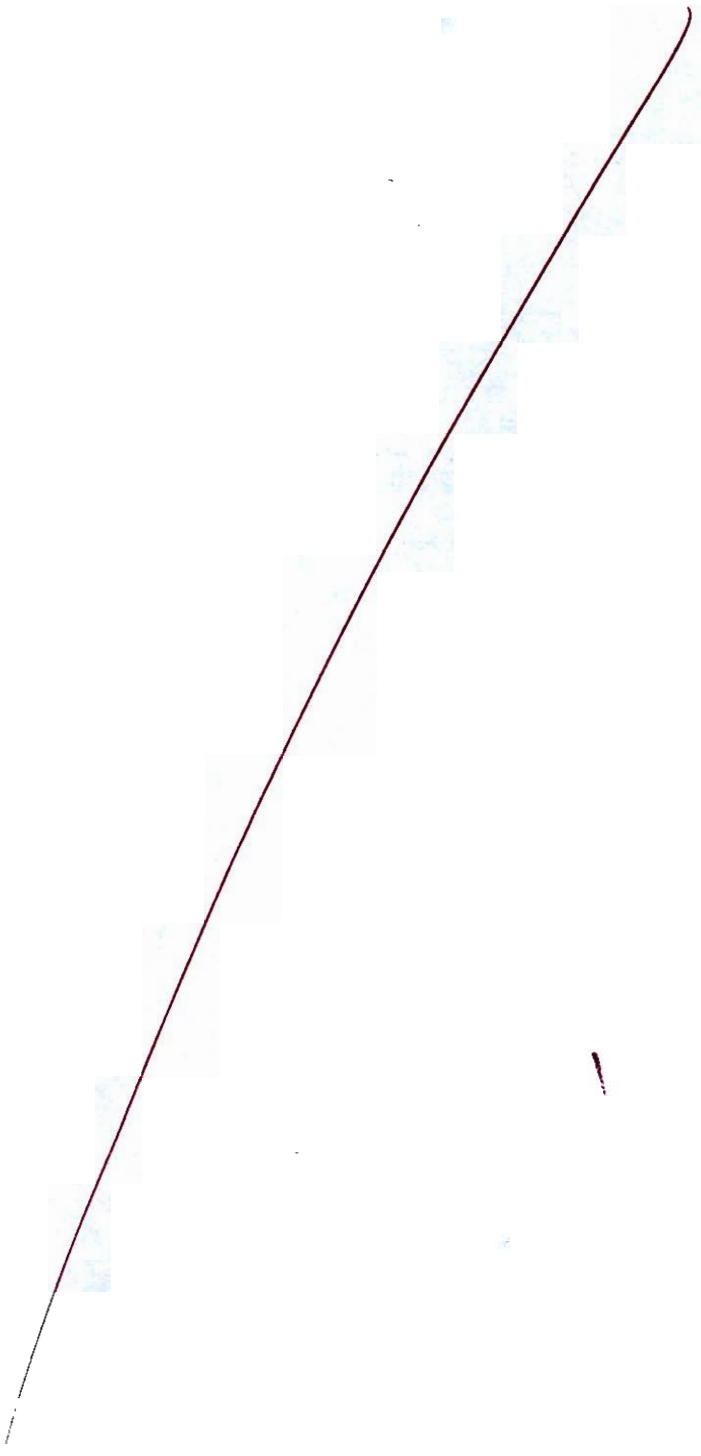

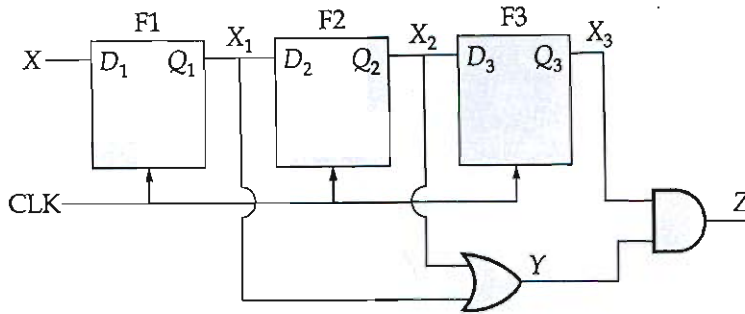
Q.3 (a) (i) A digital design is implemented by the circuit given below:




The design has *D*-type flip flops, F1, F2 and F3 driven by the clock 'CLK'. It has one input 'X' and one output 'Z'.


1. Find output logic expression for 'Z'.
2. Identify the functionality of the given circuit.

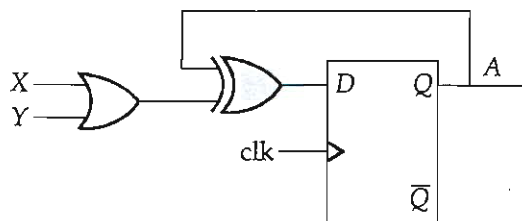(ii) Analyze the logic circuit shown below and also draw the state diagram for the given circuit.



[10 + 10 marks]

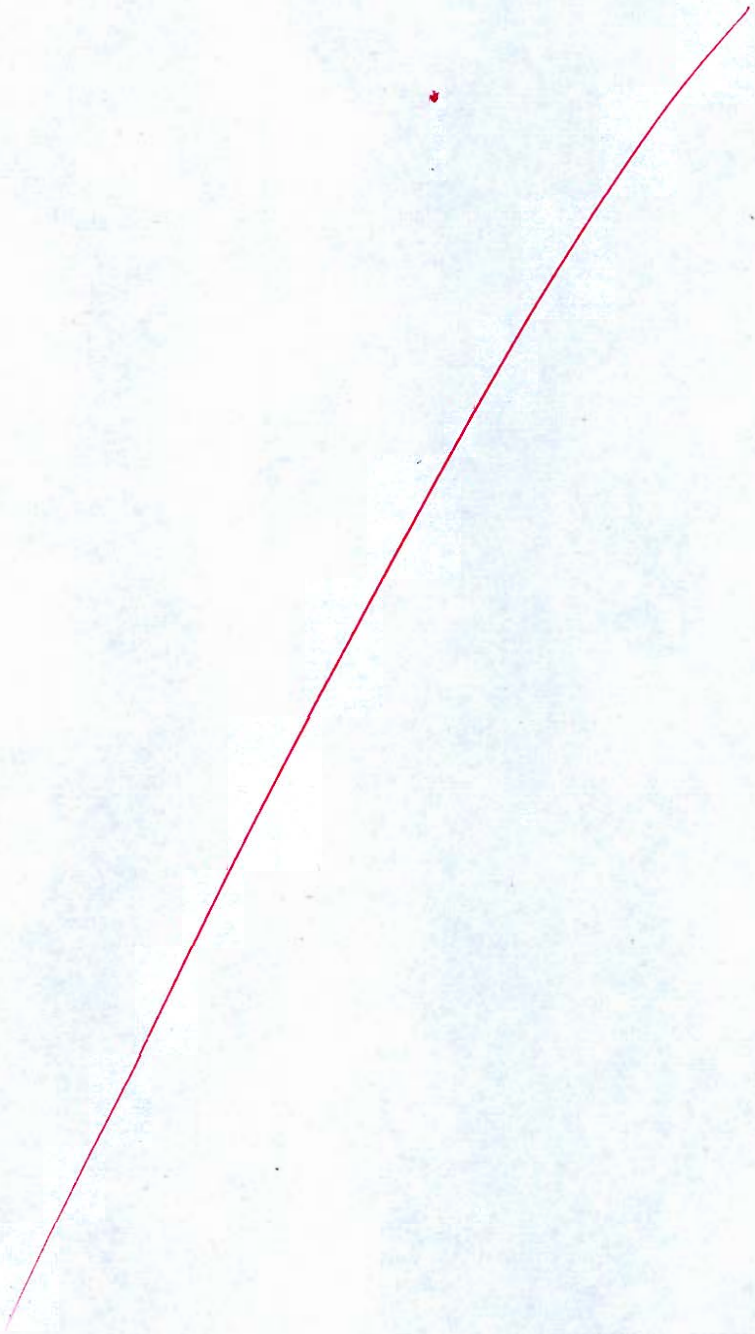

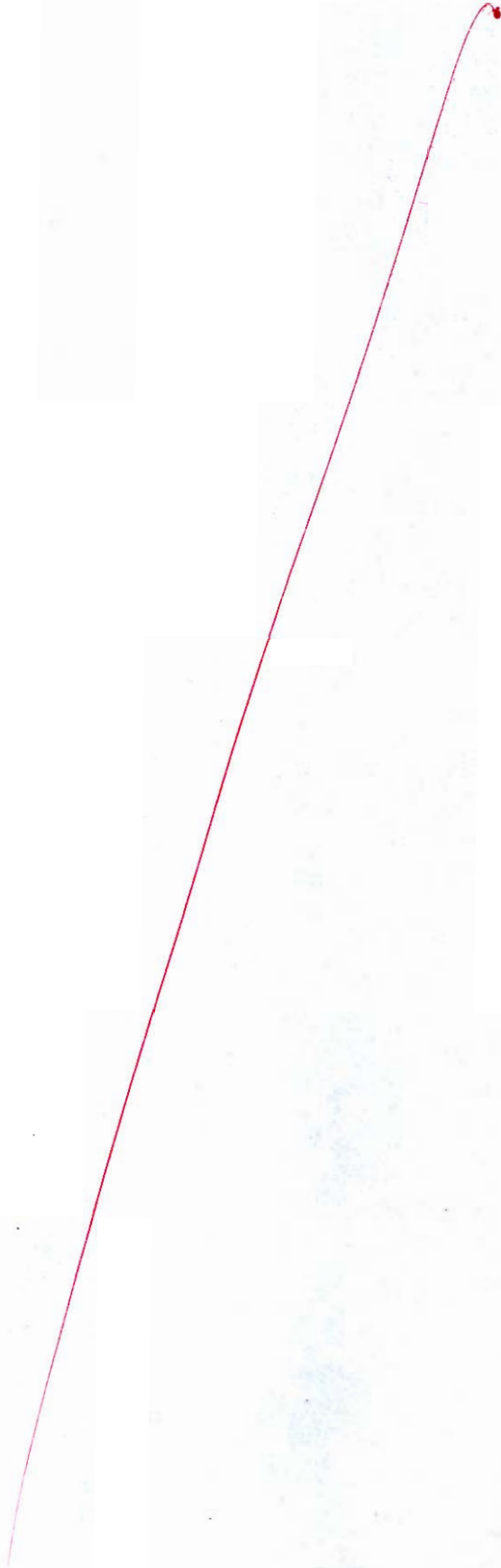


3 (b) Write an assembly language program using 8051 microcontroller (with clock frequency 12 MHz) for a simple traffic light control system using LEDs connected to port 2 of the microcontroller.


Assume LED connections

- P2.0 → Red LED (ON for 5 sec).
- P2.1 → Yellow LED (ON for 5 sec).
- P2.2 → Green LED (ON for 2 sec).


Assume this program cycles through Red-Green-Yellow lights with delays.

[20 marks]

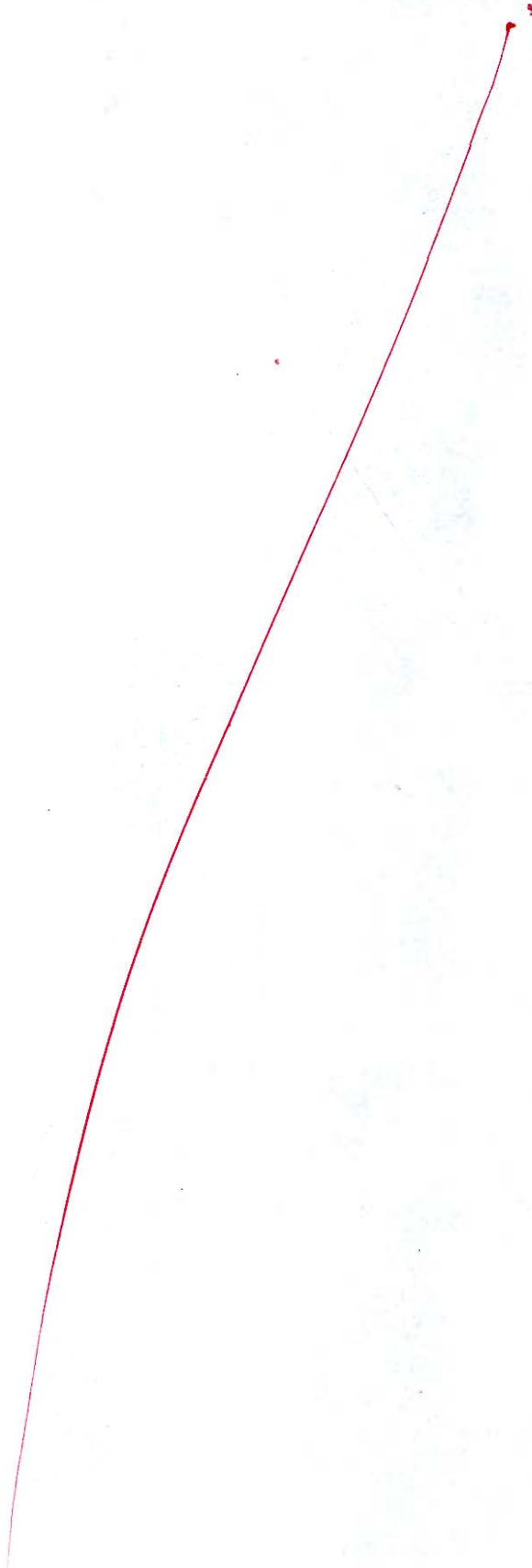


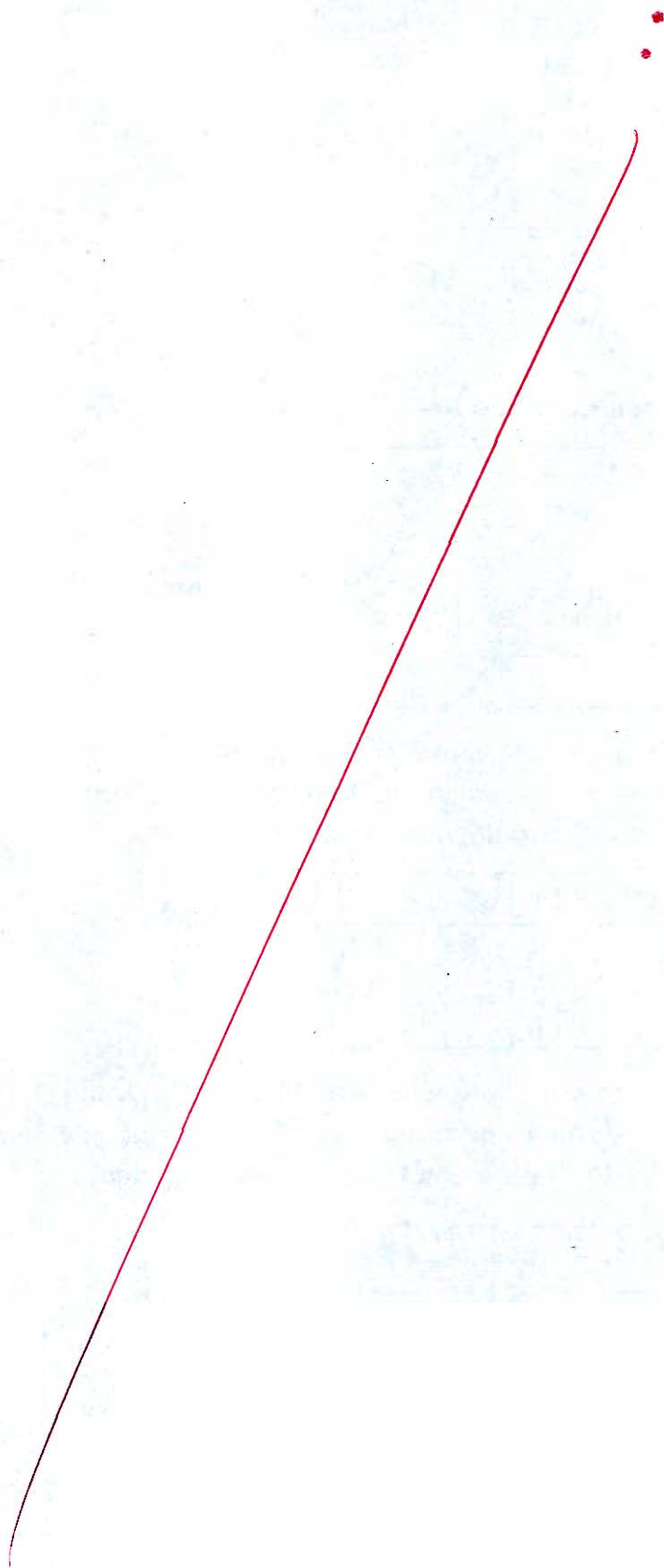

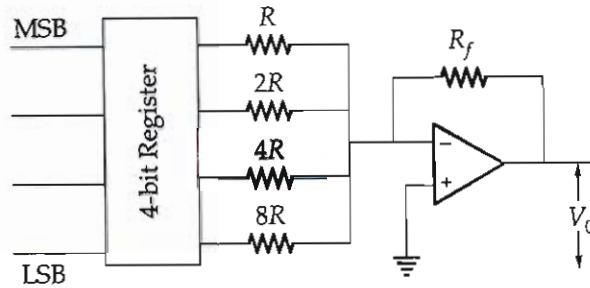- Q.3 (c) (i) Calculate the output voltage for an input code word 0110 if a logic 1 is 10 V and logic 0 is 0 V. Assume $R = R_f = 1 \text{ k}\Omega$.



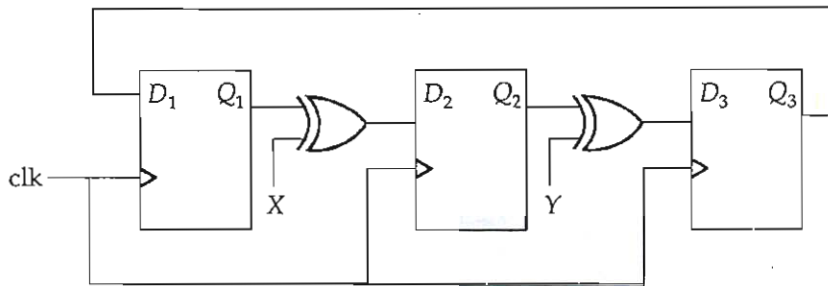
- (ii) Consider the sequential circuit shown below:




1. Fill in the table for the next state values of the three flip-flops for the given current state of the flip-flops and the inputs X and Y. Assume setup and hold times are synchronized with flip-flop inputs.


Q_1	Q_2	Q_3	X	Y	Q_1^+	Q_2^+	Q_3^+
0	0	0	0	1			
1	1	0	1	1			
0	0	1	1	0			

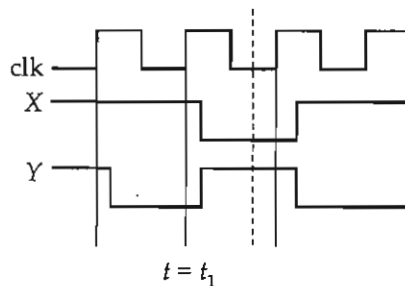2. For the timing diagram shown below, what is the value of Q_1 , Q_2 and Q_3 at the time indicated by the dashed line in the figure if the value at $t = t_1$ for $Q_1Q_2Q_3 = 001$? (Assume the flip-flops are negative edge triggered)



[10 + 10 marks]

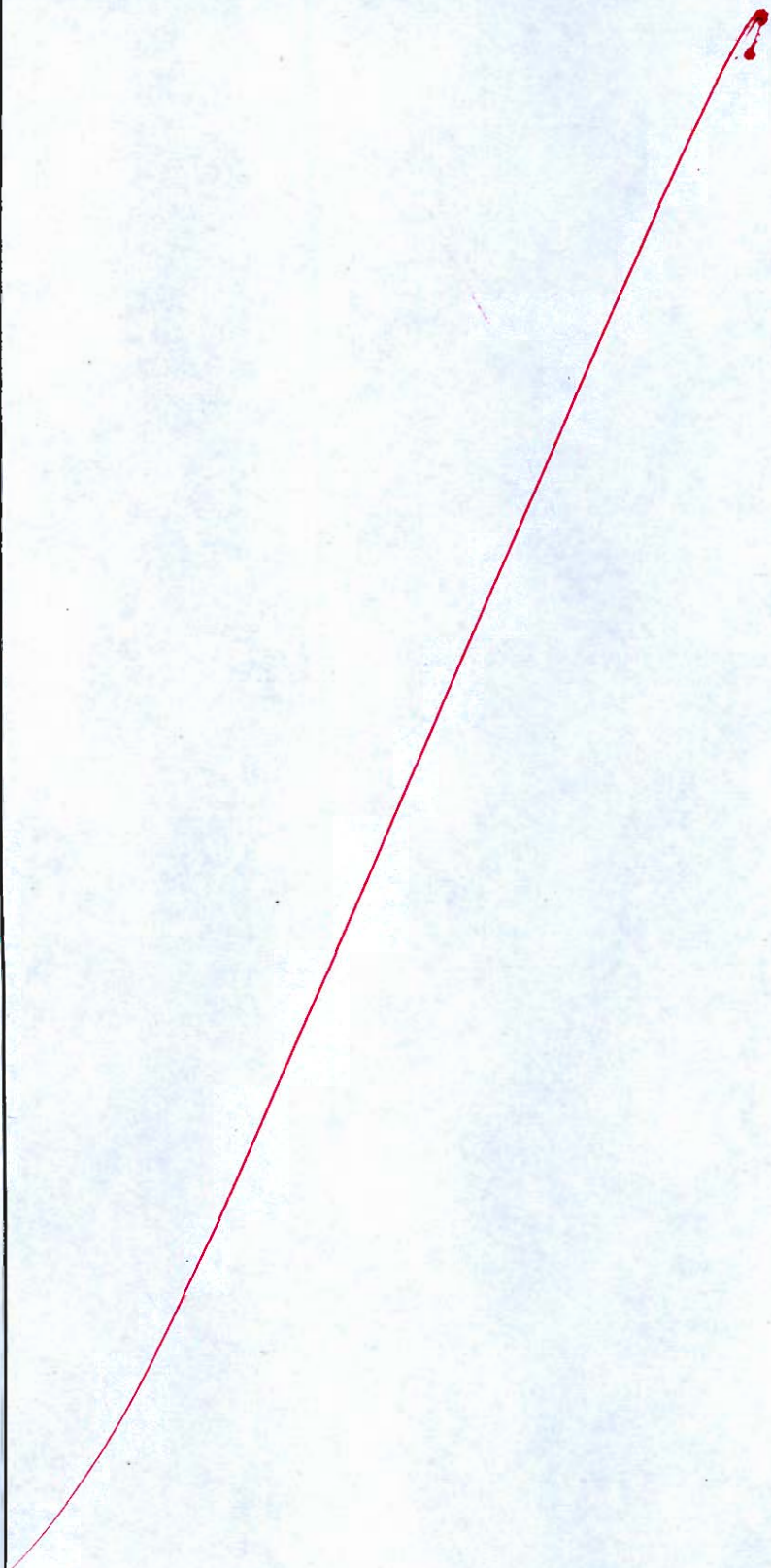


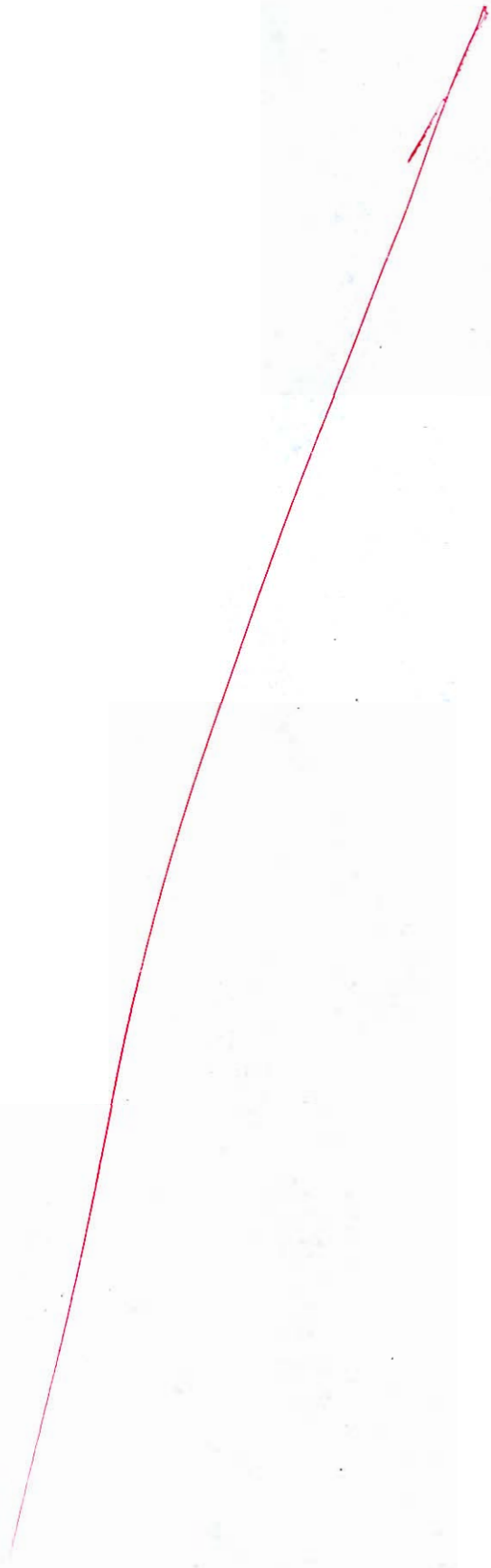

(A) (B) (C) (D)

(A)	(B)	(C)	(D)
0	0	0	0
1	0	0	0
0	1	0	0
1	1	0	0
0	0	1	0
1	0	1	0
0	1	1	0
1	1	1	0
0	0	0	1
1	0	0	1
0	1	0	1
1	1	0	1
0	0	1	1
1	0	1	1
0	1	1	1
1	1	1	1


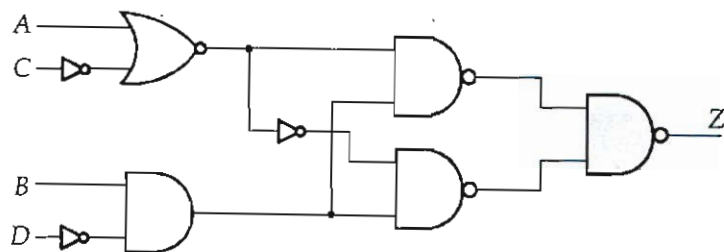
- Q.4 (a) (i) Design an Excess-3 to BCD code converter (Use don't cares for unused codes).
 (ii) The simplified logic expression for output in the circuit shown in below figure is



Q4 (a) (i) Excess-3 to BCD conversion [15 + 5 marks]



(Binary) $b_3 b_2 b_1 b_0$	(Excess-3) $X_3 X_2 X_1 X_0$	(BCD) $A_3 A_2 A_1 A_0$
0 0 0 0	0 1 1 1	0 0 0 0
0 0 0 1	0 1 0 0	0 0 0 1
0 0 1 0	0 1 0 1	0 0 1 0
0 0 1 1	0 1 1 0	0 0 1 1
0 1 0 0	0 1 1 1	0 1 0 0
0 1 0 1	1 0 0 0	0 1 0 1
0 1 1 0	1 0 0 1	0 1 1 0
0 1 1 1	1 0 1 0	0 1 1 1
1 0 0 0	1 0 1 1	1 0 0 0
1 0 0 1	1 1 0 0	1 0 0 1
1 0 1 0	1 1 0 1	X X X X
1 0 1 1	1 1 1 0	X X X X
1 1 0 0	1 1 1 1	X X X X
1 1 0 1	0 0 0 0	X X X X
1 1 1 0	0 0 0 1	X X X X
1 1 1 1	0 0 1 0	X X X X

K-maps!

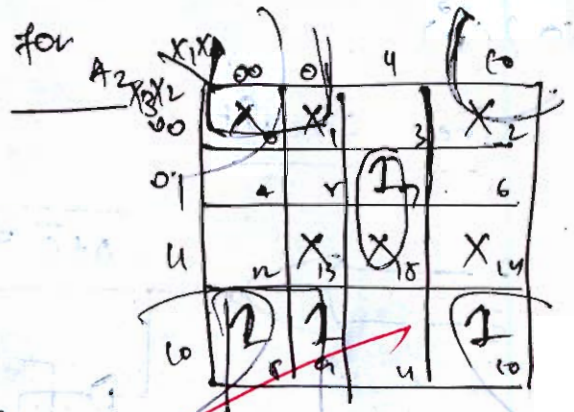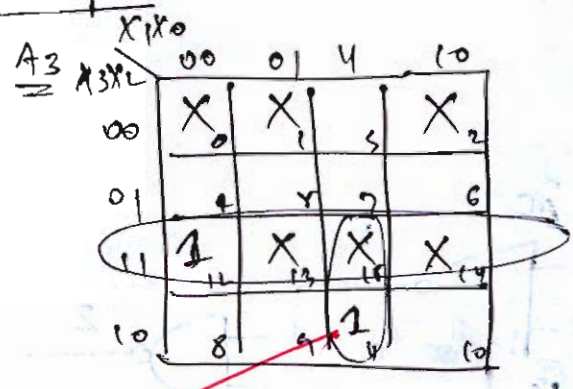

$A_3 = X_3 X_2 + X_3 X_1 X_0$

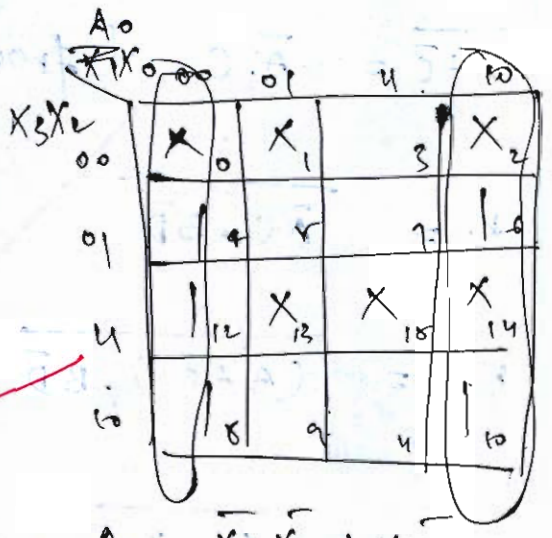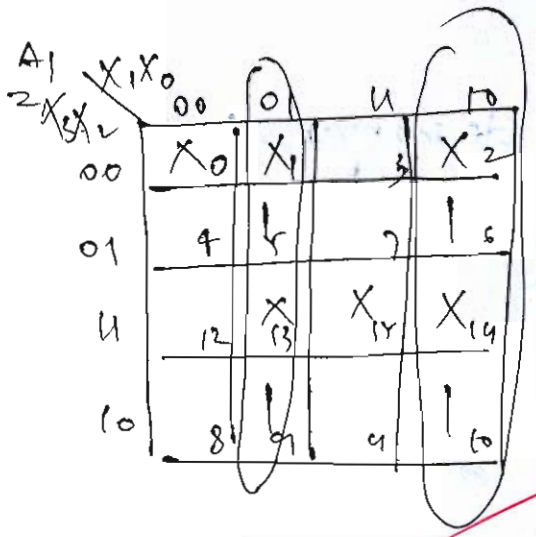$A_2 = \bar{X}_2 \bar{X}_1 + \bar{X}_2 \bar{X}_0 + \bar{X}_2 X_1 X_0$




$A_1 = \bar{X}_1 X_0 + X_1 \bar{X}_0$

$A_0 = \bar{X}_1 \bar{X}_0 + X_1 X_0$

$A_0 = \bar{X}_0$

15


circuit design!

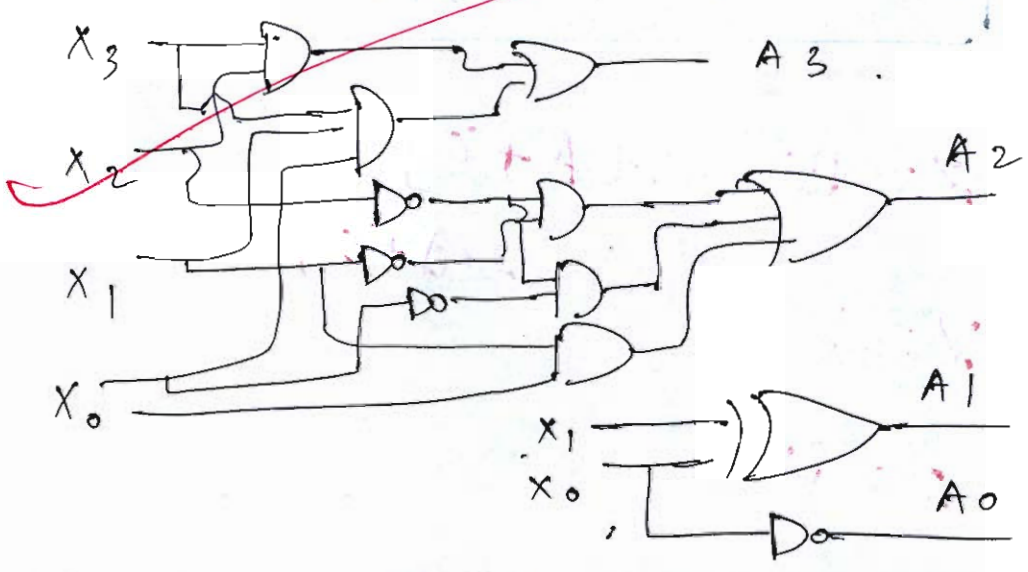

Q4

(a) (ii)

Given circuit

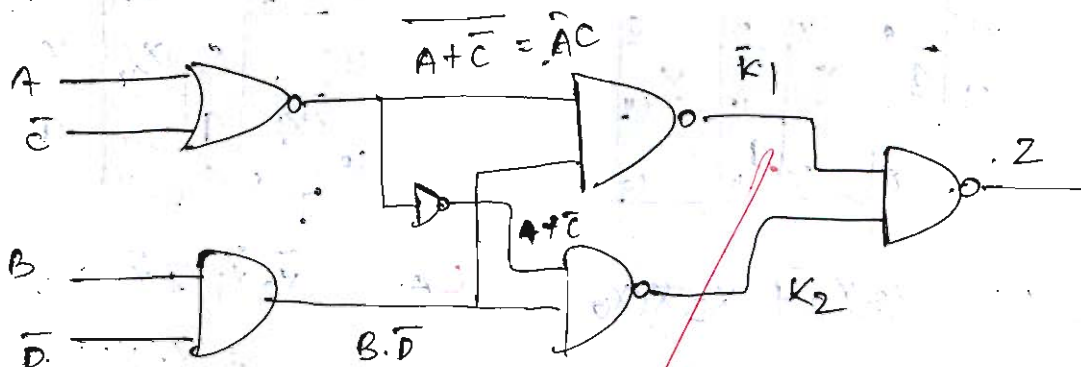

$$\overline{A+C} = \bar{A} \cdot \bar{C} \quad [\text{from de Morgan's law}]$$

$$K_1 = \overline{A+C} \cdot B \cdot \bar{D}$$

$$K_2 = \overline{A+C} \cdot \bar{D}$$

$$Z = \overline{K_1 \cdot K_2} = \overline{K_1} + \overline{K_2}$$

$$Z = \overline{\overline{A+C} \cdot B \cdot \bar{D}} + \overline{\overline{A+C} \cdot \bar{D}}$$

$$Z = \overline{\overline{A+C} \cdot B \cdot \bar{D}} + \overline{\overline{A+C} \cdot \bar{D}}$$

$$Z = B \bar{D} [AC + A + \bar{C}]$$

$$Z = B \bar{D} [(A+A)(A+1) + \bar{C}]$$

$$Z = B \bar{D} [A+1] = B \bar{D}$$

4 (b) Implement the following functions using single (3 x 6 x 4) programmable logic array (PLA) with programmable output polarity feature.

F1(A, B, C) = Σm(1, 2, 4, 6)

F2(A, B, C) = Σm(0, 1, 6, 7)

F3(A, B, C) = Σm(2, 6)

F4(A, B, C) = Σm(1, 2, 3, 5, 7)

[20 marks]

4 (b) given PLA parameters

(3 x 6 x 4)

3: Total number of inputs.

6: Total AND gates in circuit.

4: Total OR output gates.

18

Quop

Statement: In a PLA design, both AND & OR gates are programmable.

K-map for F1

BC	00	01	11	10
A	0	1	3	2
1	1	1	1	1

F1 = ~~AB~~ AC + BC + A^{bar}BC

F2

BC	00	01	11	10
A	0	1	3	2
1	1	1	1	1

F2 = A^{bar}B + AB

F3

BC	00	01	11	10
A	0	1	3	2
1				1


F3 = BC

F4


BC	00	01	11	10
A	0	1	3	2
1			1	1

F4 = C + A^{bar}B

K-map for F_1

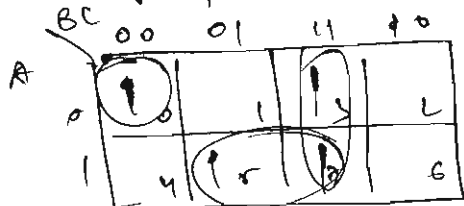

K-map for F_2

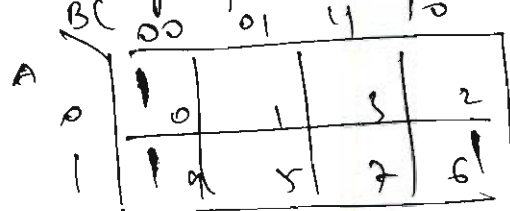


$F_1 = \bar{A}\bar{B}\bar{C} + AC + BC$

$F_2 = AC + \bar{B}C$


∴ 6 common minterms are

$= A\bar{C}, \bar{B}C, \bar{A}BC, \bar{A}\bar{B}, AB, \bar{B}\bar{C}$


PLA structure

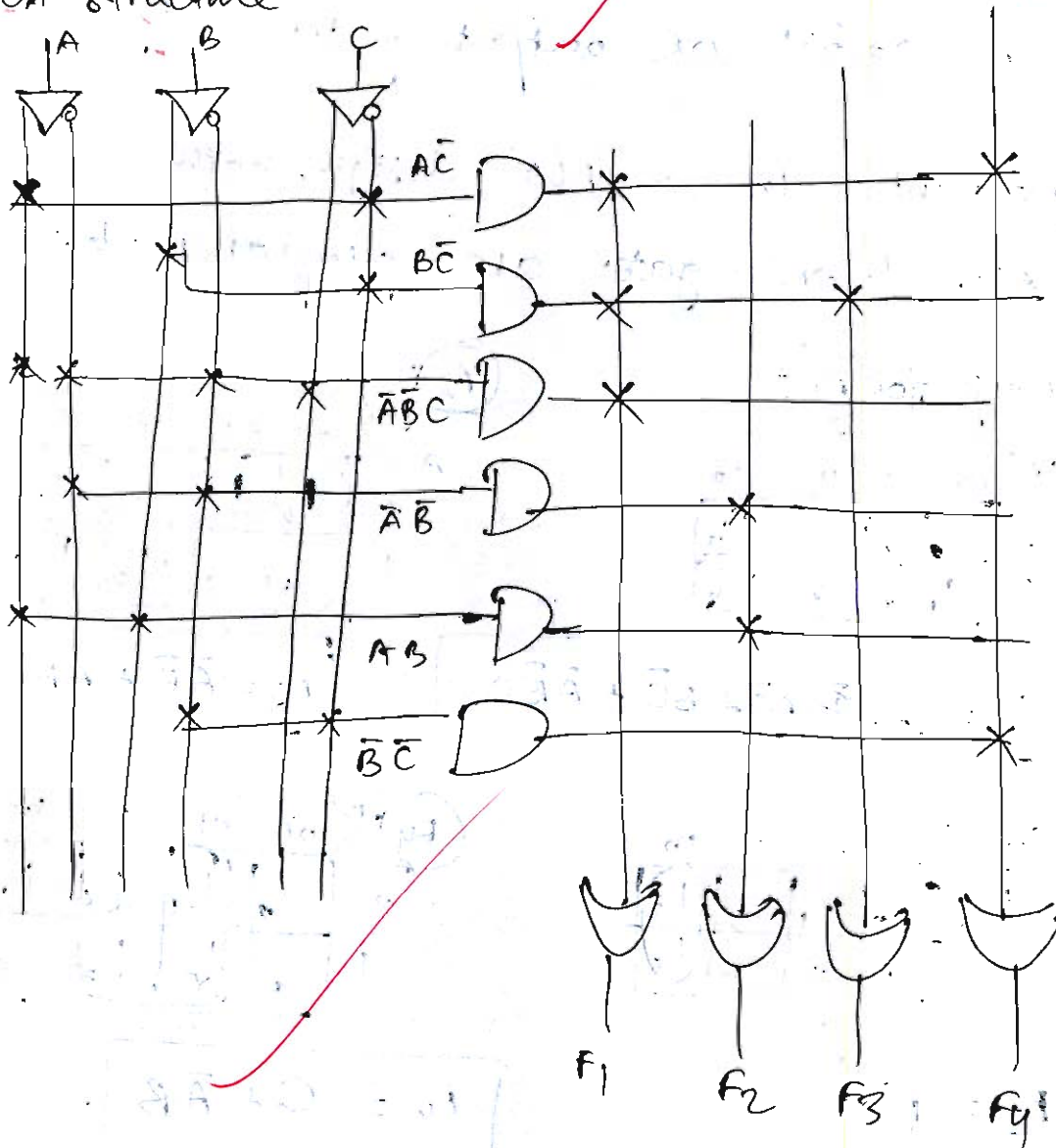



PLA design

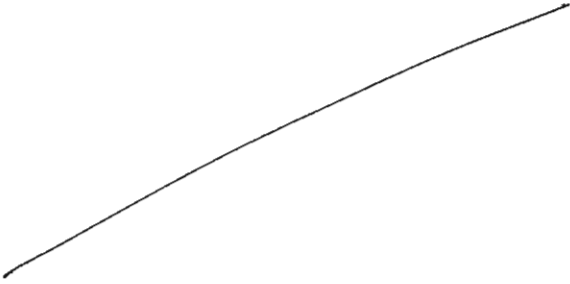- 
- 4 (c) (i) Describe memory segmentation in 8086 microprocessor with the help of block diagram.
- (ii) What are the different addressing modes of 8051 microcontroller?

[10 + 10 marks]

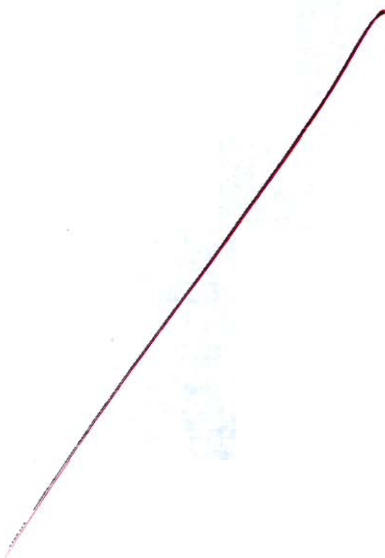

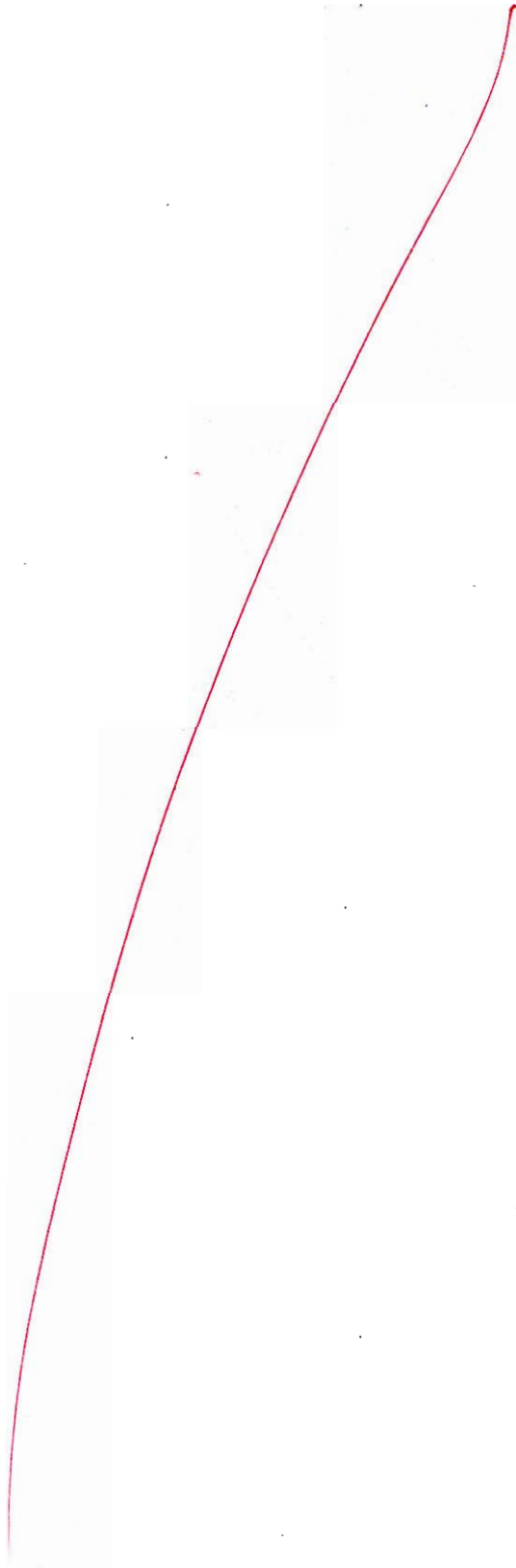

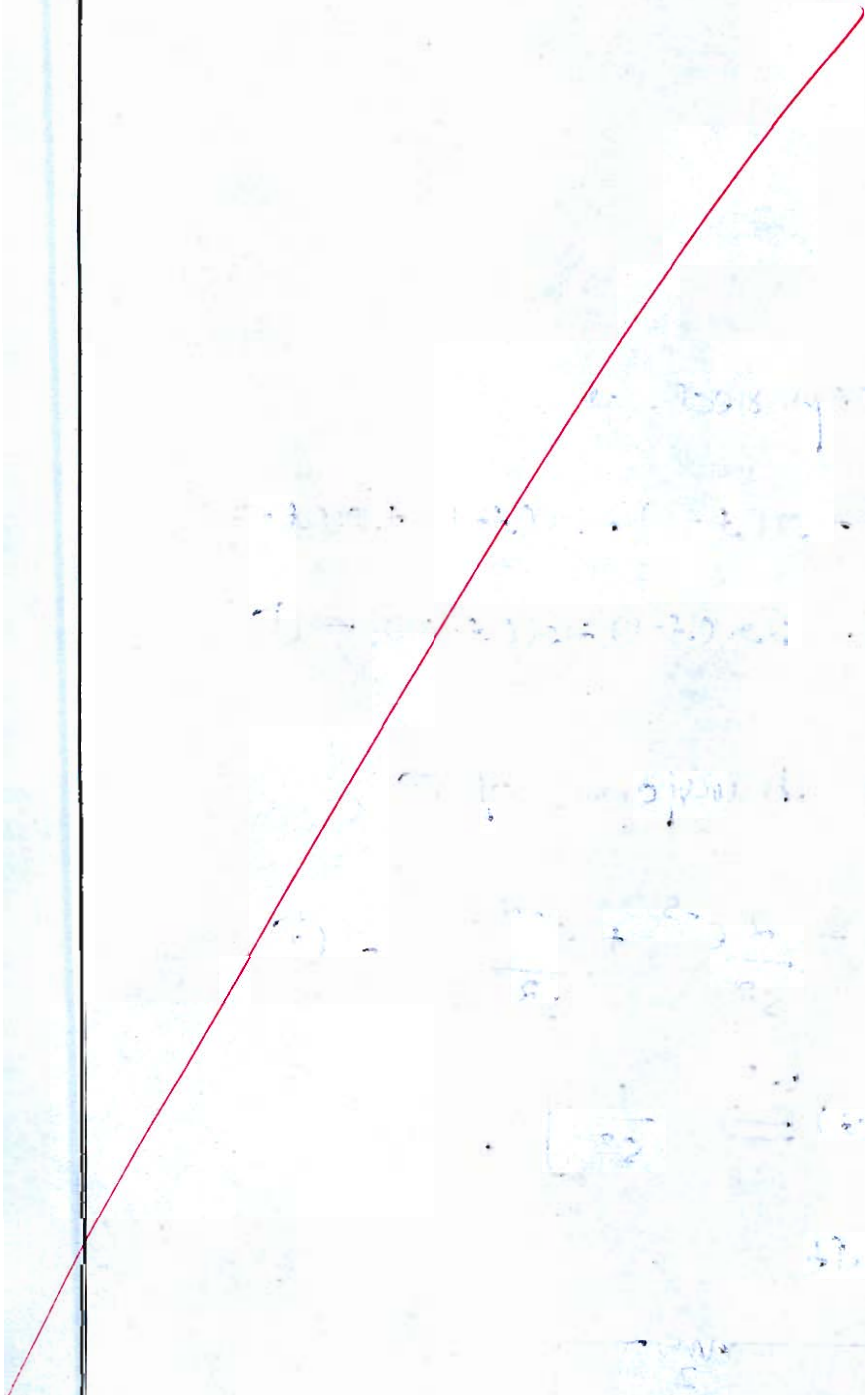

... ..


... ..

... ..

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R}$$

$$\frac{1}{20} + \frac{1}{30} = \frac{1}{R}$$

... ..

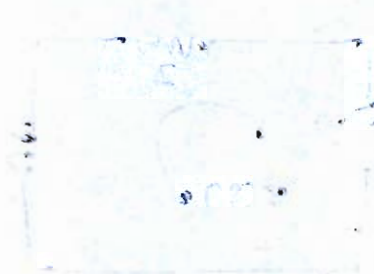

$$\frac{20V}{20\Omega} = i$$

Section B : Network Theory-1 + Signals and Systems-1

- Q.5 (a) A triangular wave shown in figure (a) is applied as an input to a series RL circuit shown in figure (b). Find the current $i(t)$.

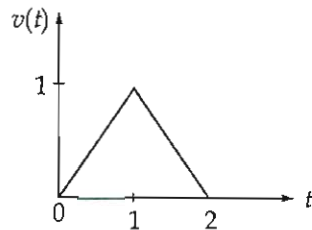


Fig. (a)

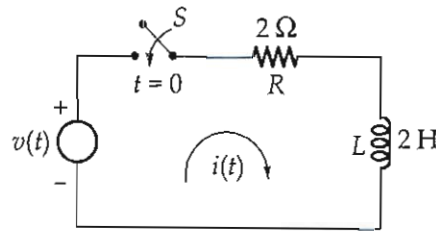


Fig. (b)

(Q5) (a)

[12 marks]

$v(t)$ can be expressed as,

$$v(t) = r(t) - r(t-1) - r(t-1) + r(t-2)$$


$$v(t) = r(t) - 2r(t-1) + r(t-2) \quad \text{--- (1)}$$

taking laplace transform of (1),

$$V(s) = \frac{1}{s^2} - \frac{2e^{-s}}{s^2} + \frac{e^{-2s}}{s^2} \quad \text{--- (2)}$$

$$\left[\begin{matrix} \infty \\ \infty \end{matrix} r(t) \xrightarrow{LT} \frac{1}{s^2} \right]$$

laplace of circuit,

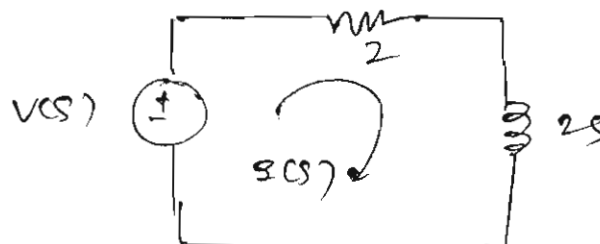

$$I(s) = \frac{V(s)}{2 + 2s}$$

$$z(s) = \frac{1 - 2e^{-s} + e^{-2s}}{s^2(s+1) \cdot 2}$$

$$z(s) = \frac{1}{2s^2(s+1)} - \frac{e^{-s}}{(s+1)s^2} + \frac{e^{-2s}}{2 \cdot s^2(s+1)}$$

solving for function,

$$f(s) = \frac{1}{s^2(s+1)}, \text{ By partial fraction,}$$

$$f(s) = \frac{A}{s} + \frac{B}{s^2} + \frac{C}{(s+1)}$$

$$\text{Here, Numerator} = As^2(s+1) + Bs(s+1) + Cs^2$$

$$= \cancel{As^3} + \cancel{As^2} + Bs^2 + Bs + Cs^2$$

$$\text{on solving, } B=1, A=-1, C=1.$$

$$f(t) = -u(t) + r(t) + e^{-t}u(t)$$

$$\therefore f(t) = -\frac{1}{2}u(t) + \frac{1}{2}r(t) + \frac{1}{2}e^{-t}u(t)$$

$$= \left[-u(t-1) + r(t-1) + e^{-(t-1)}u(t-1) \right]$$


$$+ \frac{1}{2} \left[-u(t-2) + r(t-2) + e^{-(t-2)}u(t-2) \right]$$

↳ current
response.

- Q.5 (b) (i) Find whether the following system is static, linear, time-invariant, causal, invertible.

$$y(t) = \int_t^{t+1} x(\tau - \alpha) d\tau \text{ where, } \alpha \text{ is a constant.}$$

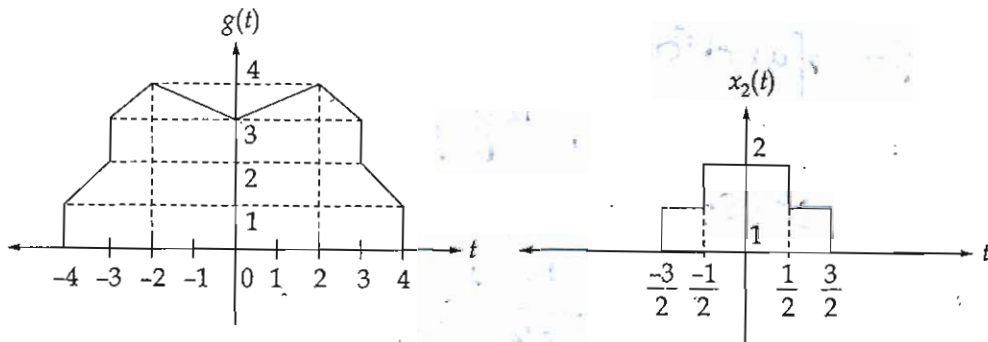- (ii) The response of an LTI system to an input signal $x_1(t) = u(t+1) - u(t-1)$ is denoted as $g(t)$, as illustrated in the figure below. If a new input $x_2(t)$ is applied to the same system, resulting in an output $y(t)$. Determine the value of the output at $t = 0$.



95

(b) (i) given system

[6 + 6 marks]

$$y(t) = \int_t^{t+1} x(\tau - \alpha) d\tau$$

Statement: for system to be static, the present output should depend upon present value of input only.


$$y(0) = \int_0^1 x(\tau - \alpha) d\tau$$

Hence, it is dynamic in nature.

• All integration operations are linear in nature, hence system is linear.

• Time-Invariance

is

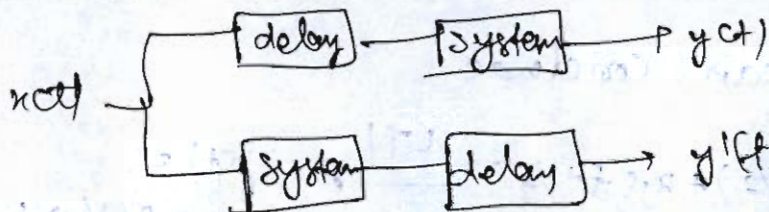

If $y(t) = y'(t) =$ Time Invariant

from above analysis,

System is Time-Invariant.



for causality, $y(t) = 0 \quad t < 0$.

$$y(-1) = \int_{-1}^0 x(z-\alpha) \cdot dz = \text{some value}$$

∴ It is non-causal

since many to one mapping is possible
hence it is non-invertible system.

8 (b) (ii) $x_1(t)$

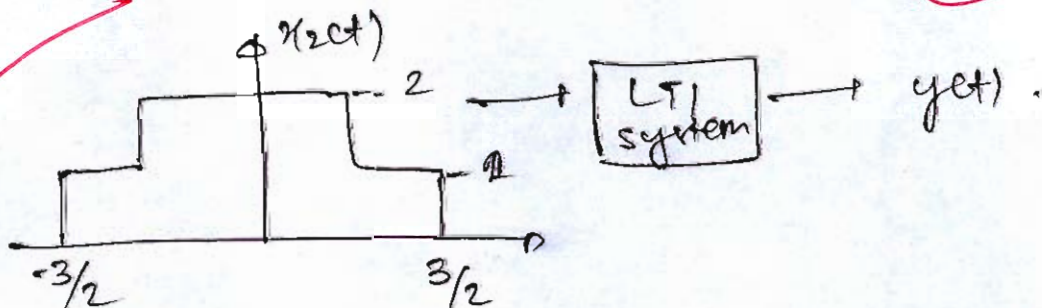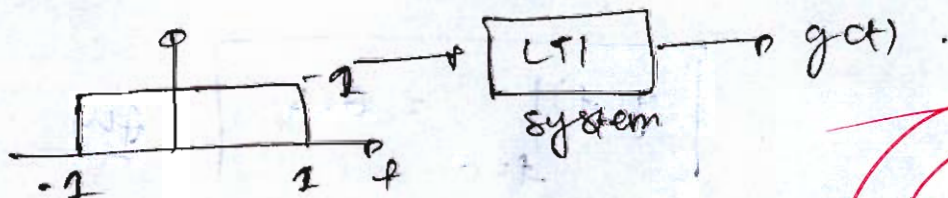

writing $x_2(t)$ in terms of $x_1(t)$,

$$x_2(t) = x_1(t - 1/2) + x_1(t + 1/2)$$

Hence, we can conclude,

$$x_2(t) = x_1(t - 1/2) + x_1(t + 1/2) \xrightarrow[\text{System}]{\text{LTI}} y(t) = g(t - 1/2) + g(t + 1/2)$$

$$\therefore y(t) \Big|_{t=0} = g(-1/2) + g(1/2)$$

from the figure,


$$g(-1/2) = g(1/2) = 3.2x$$

$$y(t) \Big|_{t=0} = 2 \times 3.2x$$

$$\boxed{y(t) \Big|_{t=0} = 6.5}$$

Ans

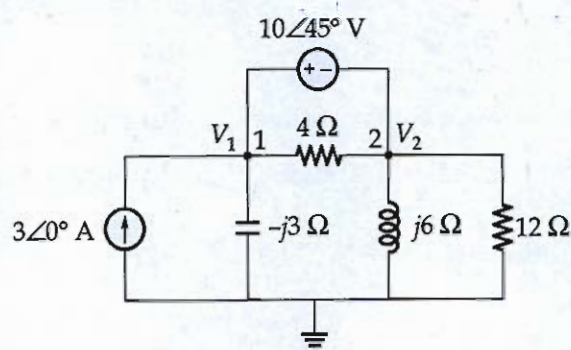2.5 (c) Compute V_1 and V_2 in the below circuit:



[12 marks]

(5) (c) modifying the above circuit; the $4\ \Omega$ resistance can be neglected,

by, ~~using~~ supernodal analysis,

$$\frac{V_1}{-j3} + \frac{V_2}{j6} + \frac{V_2}{12} = 3\angle 0^\circ \quad \text{--- (1)}$$

$$\& \quad V_1 - V_2 = 10\angle 45^\circ \quad \text{--- (2)}$$

put (2) in (1)

$$\frac{V_2}{-j3} + \frac{10\angle 45^\circ}{3\angle -90^\circ} + \frac{V_2}{j6} + \frac{V_2}{12} = 3\angle 0^\circ$$

$$V_2 \times [0.186 \angle 63.43^\circ] = 5.85 \angle -23.7^\circ$$

$$\therefore V_2 = 31.46 \angle -87.17^\circ$$


$$V_1 = 25.83 \angle -70.51^\circ$$

Ans

- Q.5 (d)
- What are eigen functions?
 - Express $\sin t + \cos 2t$ in terms of exponential eigen functions.
 - Using the eigen functions obtained above, calculate the response of the system having difference equation $\frac{d^2y}{dt^2} + 6\frac{dy}{dt} + y(t) = 5\frac{dx}{dt} + x(t)$ for the input $\sin t + \cos 2t$?

[12 marks]

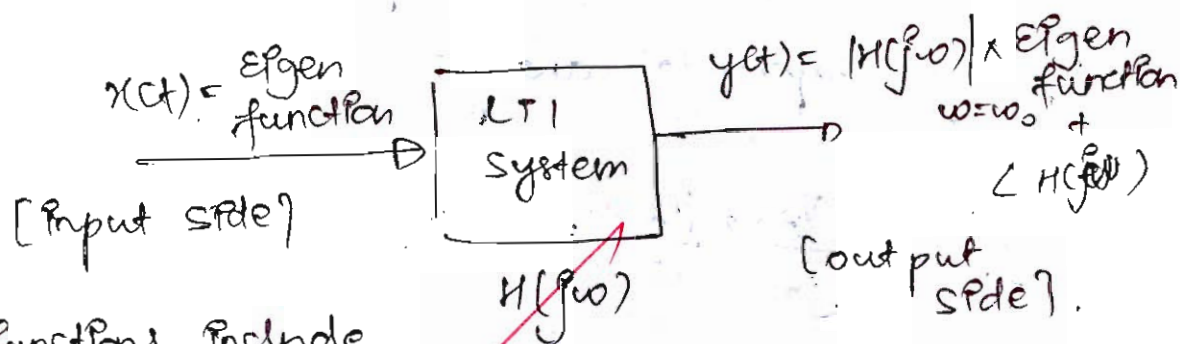Q5 (d) (i) for an LTI System, Eigen function is defined as follows.



functions include,

- $\sin t$
- $\cos t$
- $A_0 e^{j\omega_0 t}$
- A_0 [DC]

They are useful for LTI system analysis.

$$(ii) f(t) = \sin t + \cos 2t$$

we know,

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}; \quad \cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$\therefore f(t) = \frac{e^{jt} - e^{-jt}}{2j} + \frac{e^{j2t} + e^{-j2t}}{2}$$

$$f(t) = \frac{1}{2j} e^{jt} - \frac{1}{2j} e^{-jt} + \frac{1}{2} e^{j2t} + \frac{1}{2} e^{-j2t} \quad \text{--- (1)}$$

(1) is the expression in terms of exponential e^{js} function.

(iii) Taking Laplace of difference equation,

$$[s^2 + 6s + 1] Y(s) = [5s + 1] X(s)$$

$$H(s) = \frac{5s + 1}{s^2 + 6s + 1}$$

$$H(j\omega) = \frac{5j\omega + 1}{6j\omega + 1 - \omega^2} \quad \text{--- (2)}$$

calculating responses,

$$\text{for input, } \frac{1}{2j} e^{jt}, \quad y_1(t) = \frac{5j+1}{6j} \times \frac{1}{2j} e^{jt}$$


$$- \frac{1}{2j} e^{-jt}, \quad y_2(t) = \frac{-5j+1}{+6j} \times \frac{1}{2j} e^{-jt}$$

$$\frac{1}{2} e^{j2t}, \quad y_3(t) = \frac{10j+1}{12j-3} \times \frac{1}{2} e^{j2t}$$

$$-\frac{1}{2} e^{-j2t}, \quad y_4(t) = \frac{-10j+1}{-12j-3} \times \frac{1}{2} e^{j2t}$$


∴ $y_1(t)$, $y_2(t)$, $y_3(t)$ & $y_4(t)$ are the respective answers.

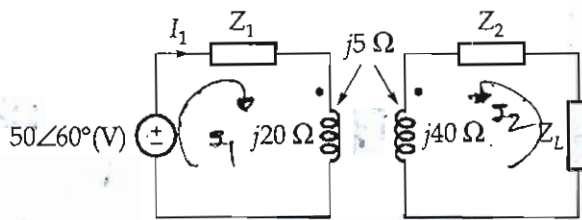- Q.5 (e) For a linear transformer shown in figure below, with $Z_1 = (60 - j100) \Omega$, $Z_2 = (30 + j40) \Omega$ and $Z_L = (80 - j60) \Omega$; find the input impedance and the current I_1 .



[12 marks]

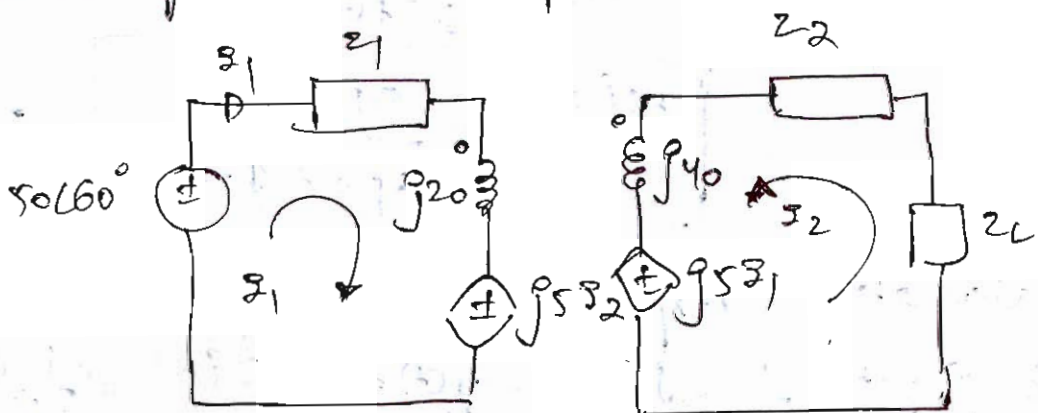- (Q5) (e) redrawing circuit by taking into account of mutual impedance,



from KVL, ②,

$$I_2 = \frac{-j5 I_1}{j40 + 30 + j40 + 80 - j60}$$

$$I_2 = \frac{-j5}{110 + j20} I_1 \quad \text{--- (1)} \quad = 0.044 \angle -100.3^\circ I_1$$

from KVL, (1),

$$I_1 = \frac{50 \angle 60^\circ - j5 I_2}{60 - j100 + j20}$$

$$I_1 = \frac{50 \angle 60^\circ}{60 - j80} + 0.223 \angle 169.69^\circ I_1$$

$$I_1 [1.22 \angle -1.877^\circ] = \frac{50 \angle 60^\circ}{60 - j80}$$

$$I_1 = 0.409 \angle 115^\circ \quad \text{A}$$

Input Impedance $[Z_{in} = \frac{V_1}{I_1}]$

6


$$Z_{in} = \frac{50 \angle 60^\circ}{0.409 \angle 115^\circ}$$


$$Z_{in} = 122.249 - j100.14 \, \Omega$$


$$\text{(or)} \quad Z_{in} = 122.249 \angle -55^\circ \, \Omega$$

- Q.6 (a) (i) Consider the discrete time signals $x[n] = a^n u[n]$, $0 < a < 1$ and $h[n] = u[n]$. Explain the graphical method for computing the discrete-time convolution. Illustrate the steps to obtain the analytical expression for $y[n]$ graphically. Sketch the output signal $y[n]$.
- (ii) Let $y[n]$ denote the convolution of $h[n]$ and $g[n]$, where $h[n] = \left(\frac{1}{2}\right)^n u[n]$ and $g[n]$ is a causal sequence. If $y[0] = 1$ and $y[1] = \frac{1}{2}$, determine the value of $g[1]$.

[12 + 8 marks]

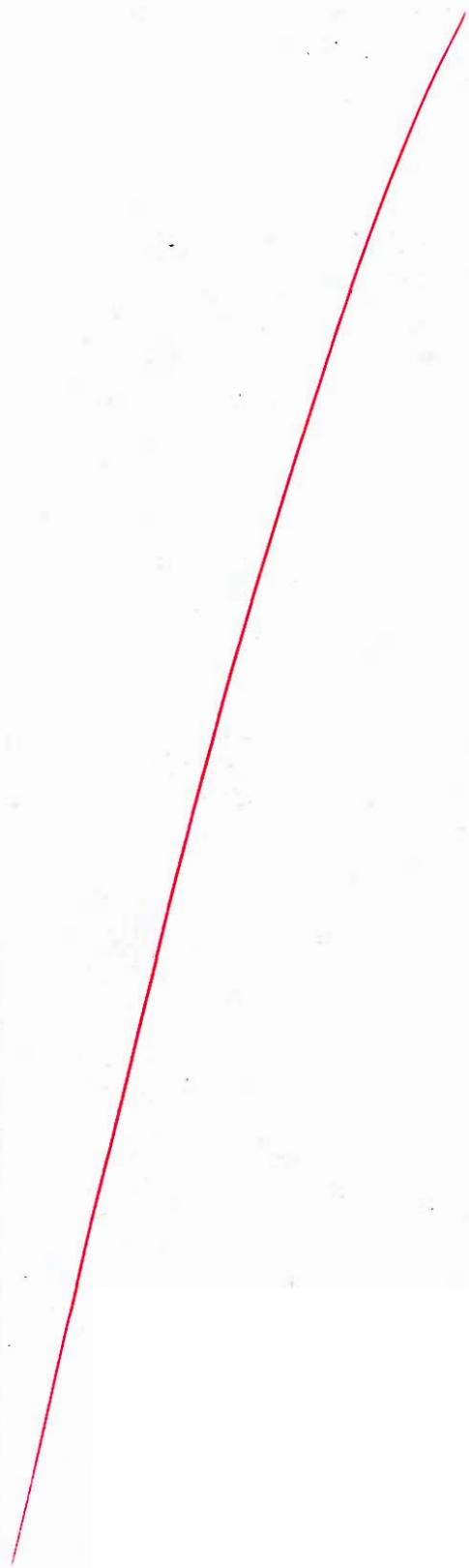


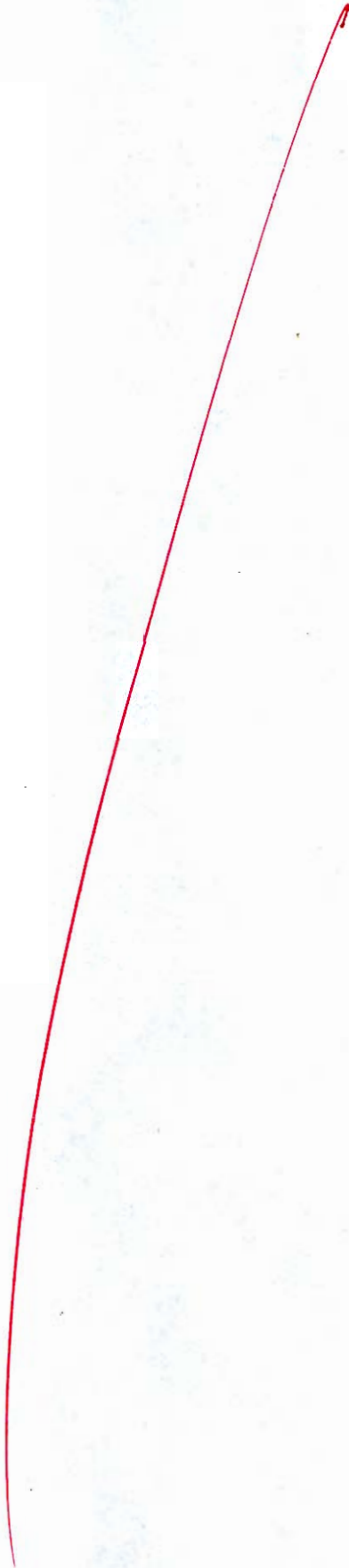

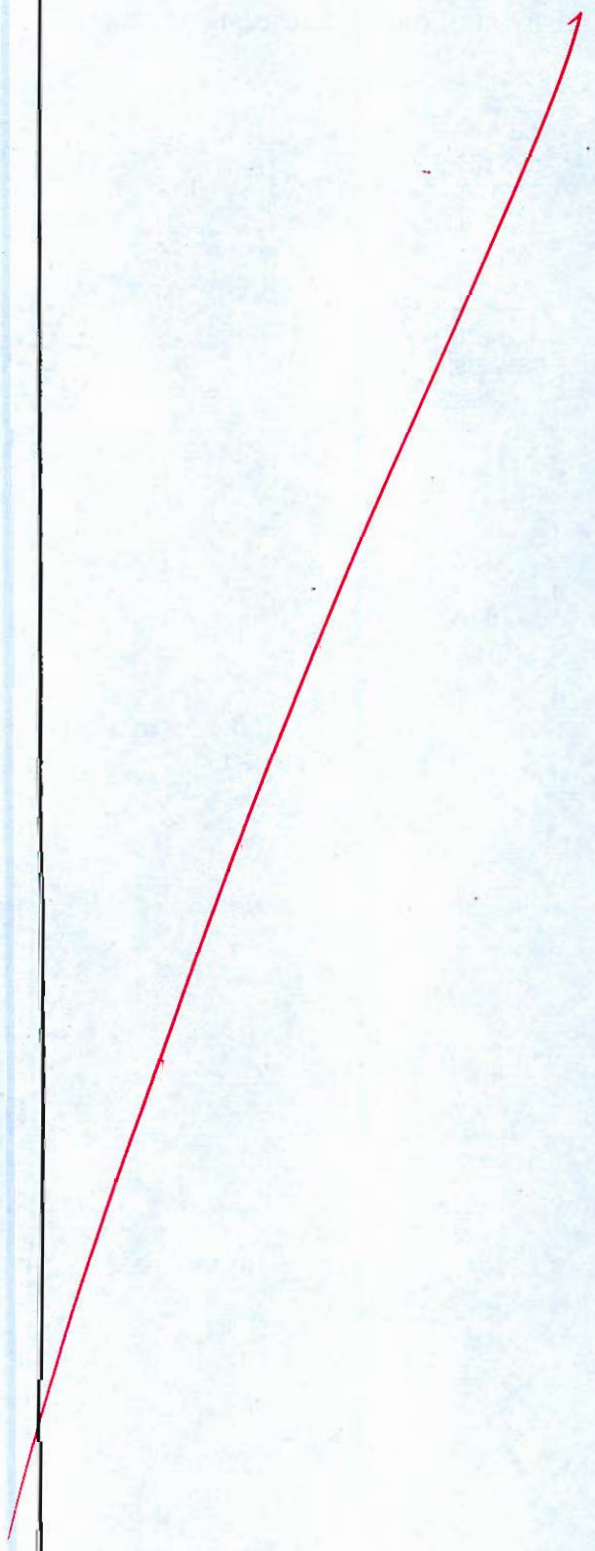


2

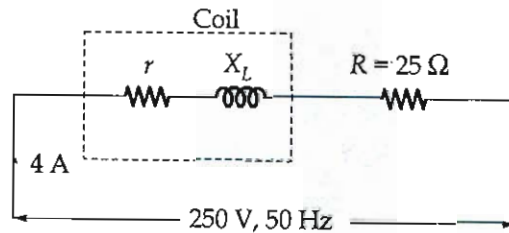
- Q.6 (b) (i) A resistance of $25\ \Omega$ is connected in series with a choke coil. The series combination when connected across a $250\ \text{V}$, $50\ \text{Hz}$ supply, draw a current of $4\ \text{A}$ which lags behind the voltage by 65° . Calculate: total power ($VA = W \pm jVAR$), Power consumed by resistance ($R = 25\ \Omega$), Power consumed by choke coil, and resistance and inductance of the coil.




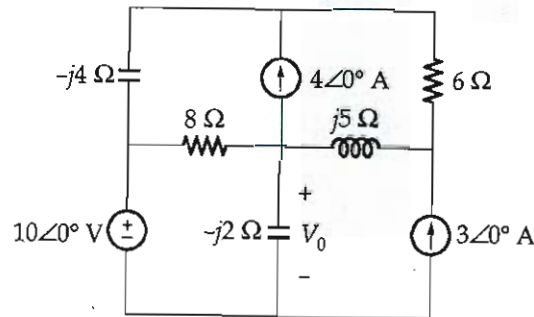
- (ii) Solve for V_0 in the below circuit using mesh analysis.



[10 + 10 marks]

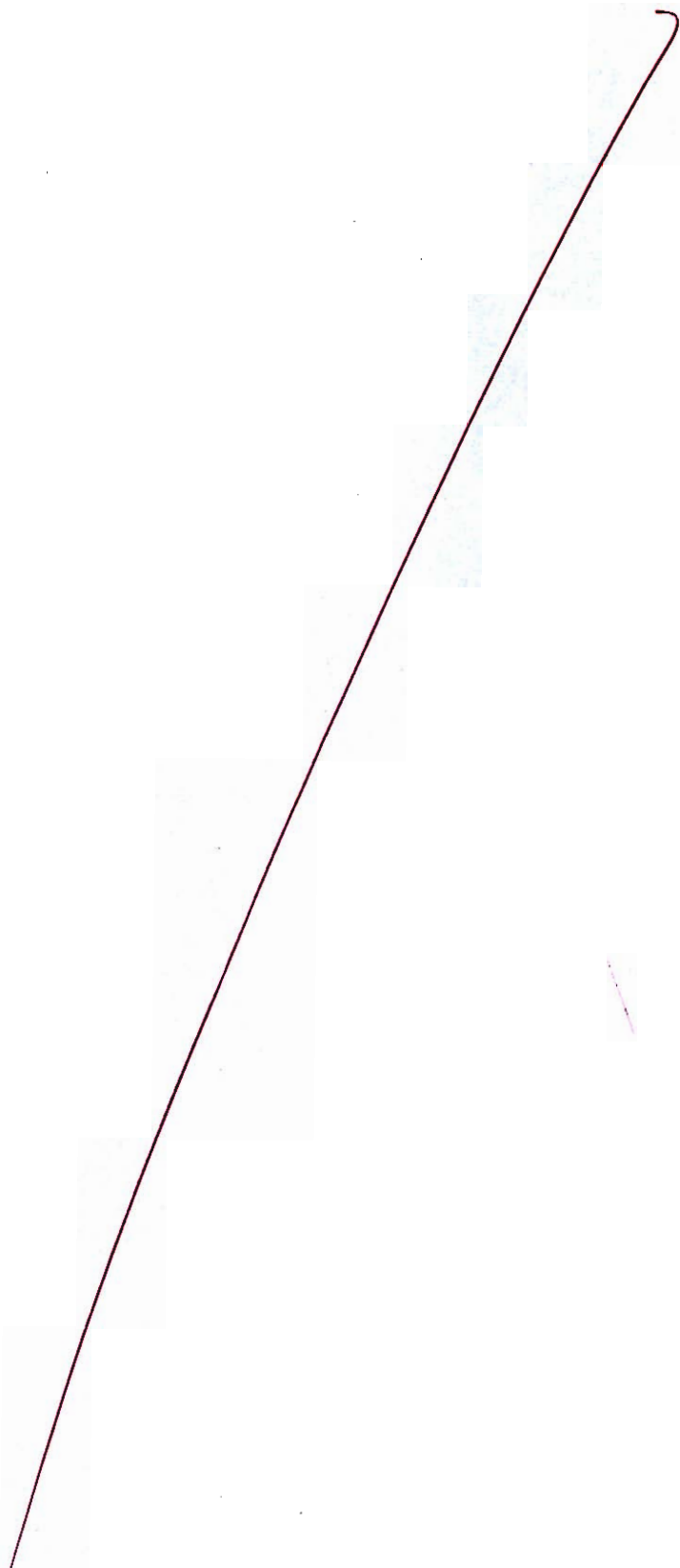

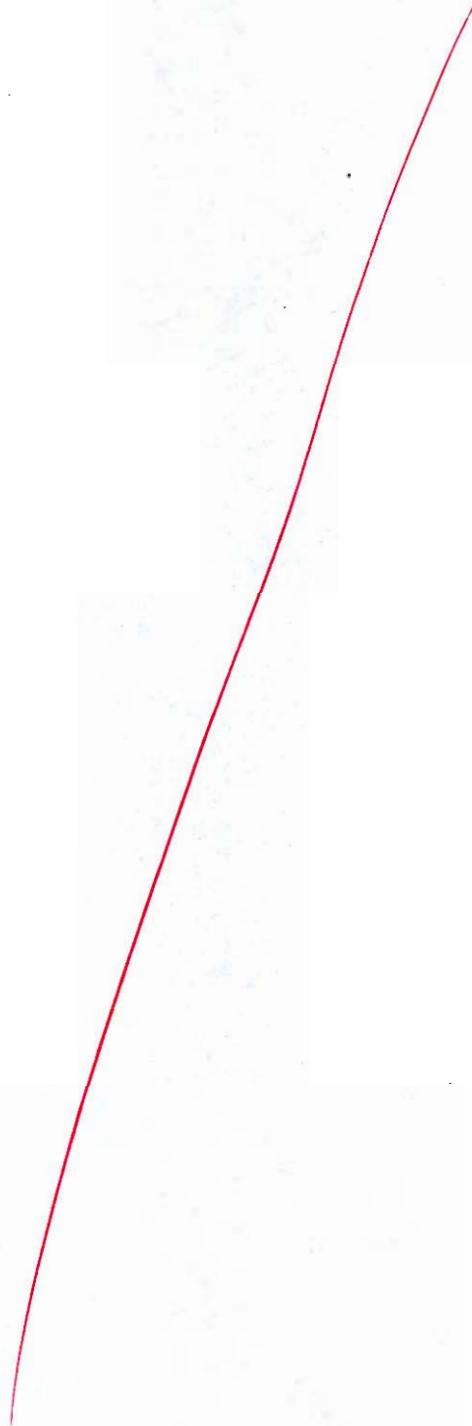

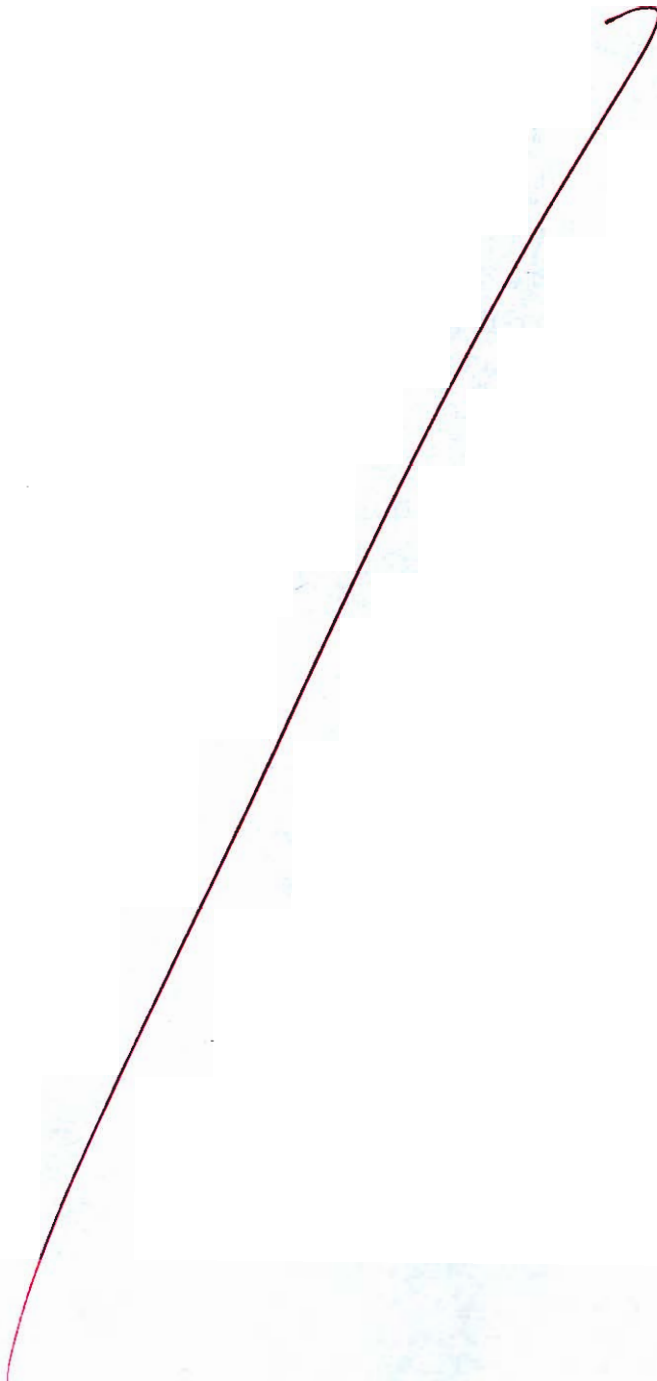

- Q.6 (c) (i) If $i_s = 2 \cos 10t$ (A), find the total energy stored in the passive network shown in figure (a) at $t = 0$ for coefficient of coupling, $k = 0.6$ and terminals x and y left open-circuited.

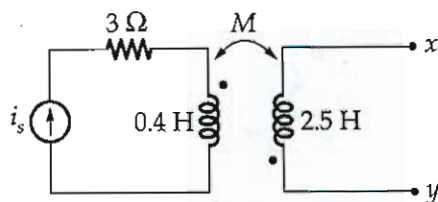


Fig. (a)

- (ii) Determine the amount of energy stored after 0.5s, when the primary side of the circuit shown in figure (b) is connected to a dc source of 15 V and the secondary is short-circuited. Given: $L_1 = 2$ H, $L_2 = 3$ H and $M = 1$ H.



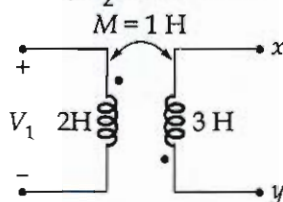


Fig. (b)

[5 + 15 marks]

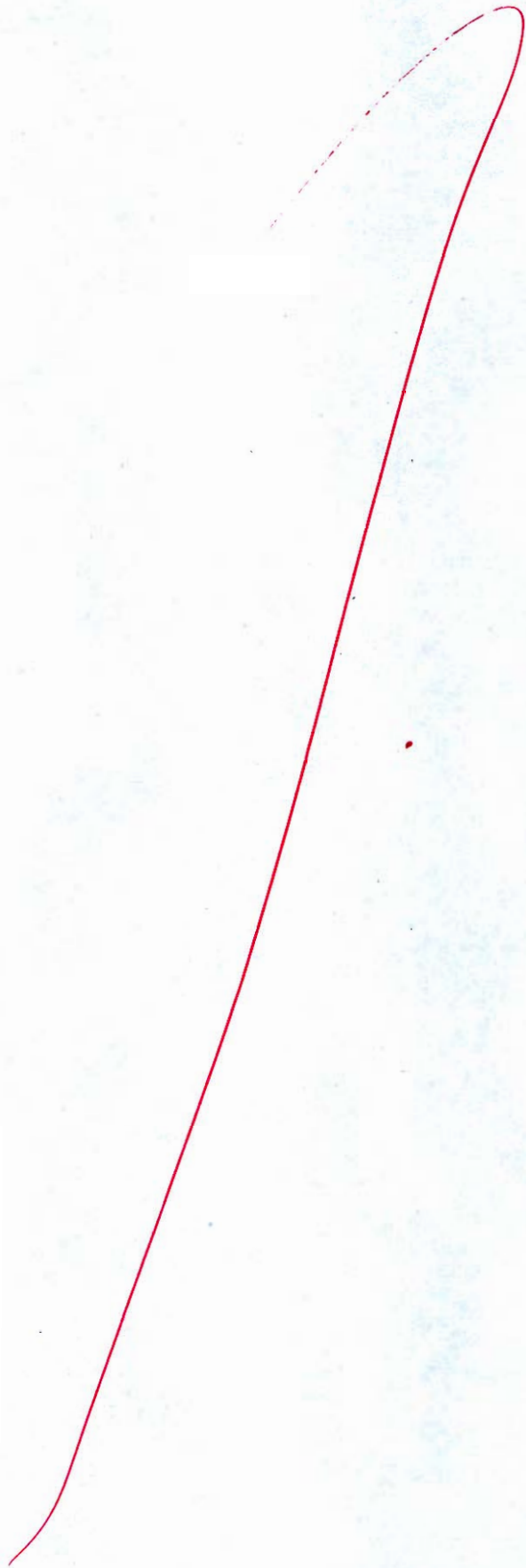

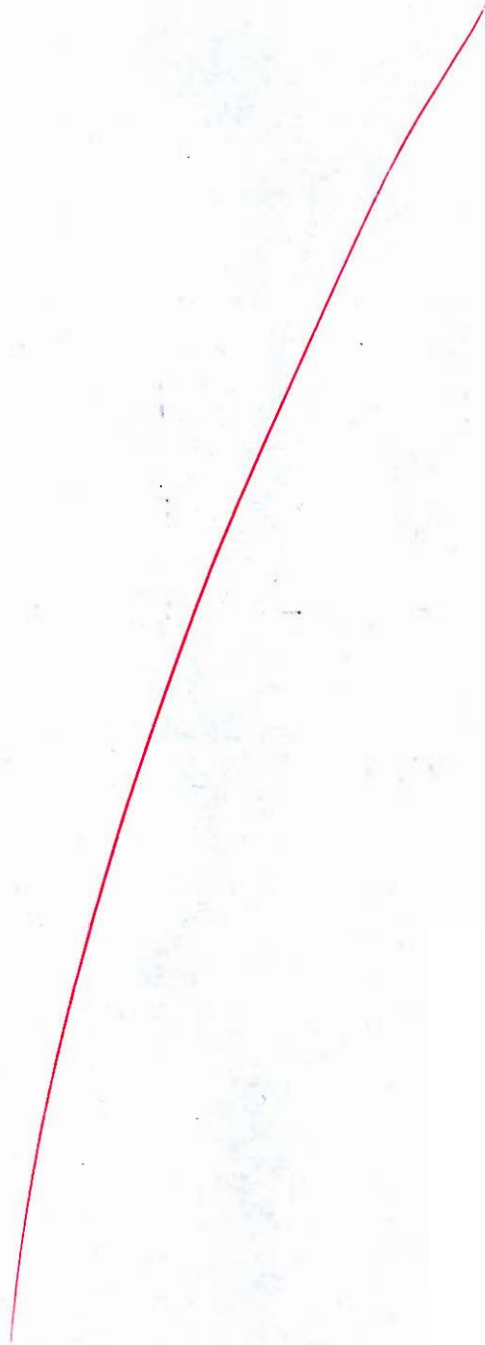

7 (a) (i) Find the Inverse Fourier Transform $x(t)$ for the given frequency domain expression:

$$X(j\omega) = e^{-j5\omega/2} \left[\frac{\sin(\frac{\omega}{2}) + 2 \sin(\frac{3\omega}{2})}{\omega} \right]$$

(ii) Evaluate the following integral involving the doublet function:

$$I = \int_{-\infty}^{\infty} \cos \frac{\pi}{2} t [\delta'(2t-1) + \delta(t-4)] dt$$

[12 + 8 marks]

(P) Given!

$$X(j\omega) = \frac{e^{-j5\omega/2} \sin(\omega/2)}{2(\omega/2)} + \frac{2 e^{j5\omega/2} \sin(3\omega/2)}{\frac{2(3\omega/2)}{3}}$$


$$X(j\omega) = X_1(j\omega) + X_2(j\omega)$$

statement: we know, $\frac{\sin \pi t}{t} = \text{sac}(t)$

12


2. Fourier transform of

$$A_0 \text{sac}(t) \Rightarrow$$

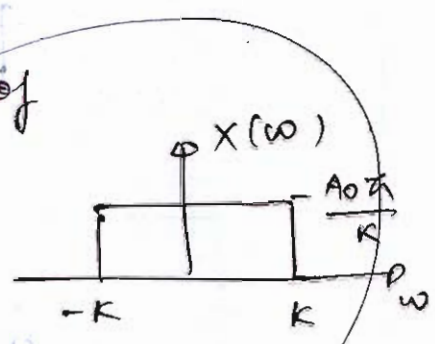

By duality $\omega \leftrightarrow t$


$$X(t)$$

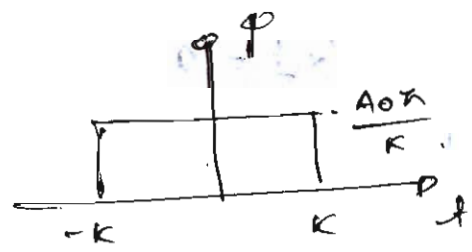

$$\Rightarrow 2\pi \cdot A_0 \text{sac}(K\omega)$$

$$[\text{sac}(-\omega) = \text{sac}(\omega)]$$

$$X(t)$$

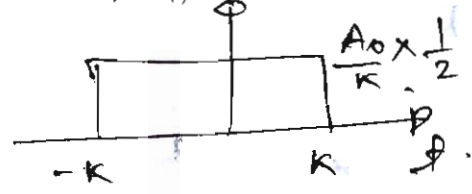


$$\Rightarrow A_0 \text{sac}(K\omega)$$

$$X_1(j\omega) = \frac{1}{2} e^{-j5\omega/2} \text{sinc}(\omega/2)$$


$$A_0 = 1/2$$

$$K = 1/2$$

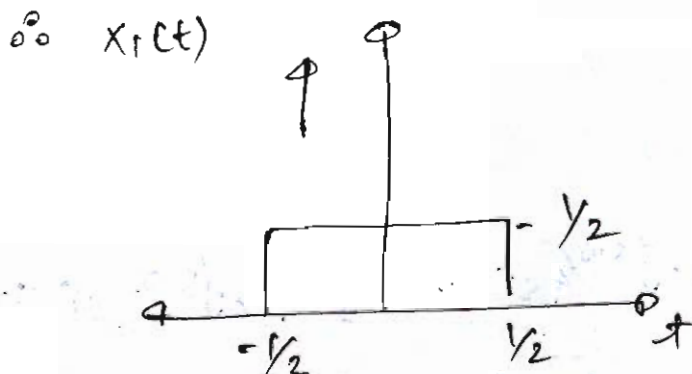

but by ~~frequency~~ ^{time} shifting property,

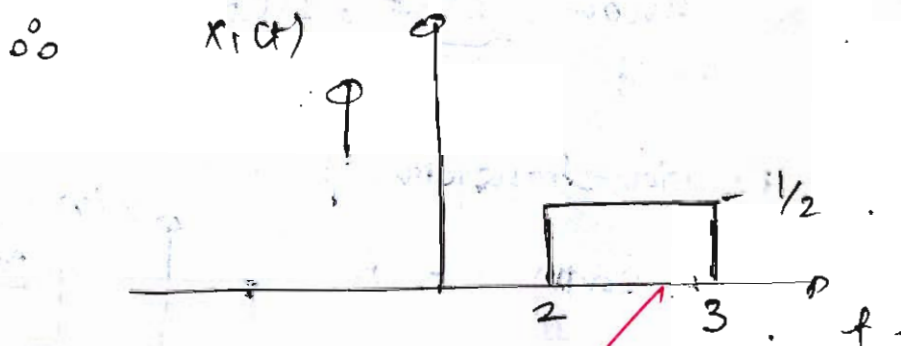
$$\{ x(t-t_0) \Leftrightarrow X(\omega) \cdot e^{-j\omega t_0} \}$$




$$X_2(j\omega) = 3 \cdot e^{-j5\omega/2} \text{sinc}(3\omega/2)$$


$$A_0 = 3$$

$$K = 3/2$$

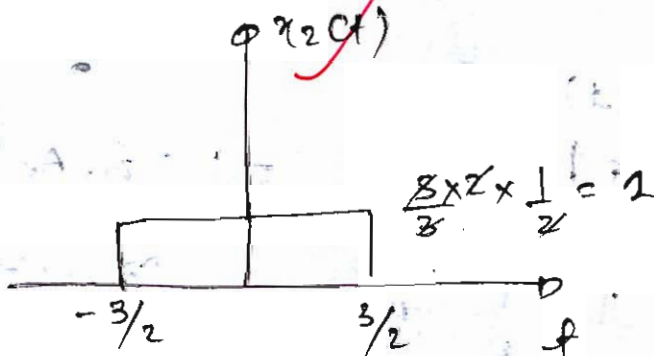

but by shifting, $X_2(t)$

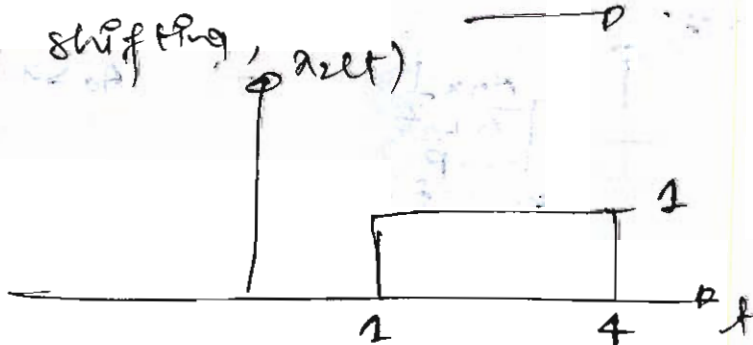

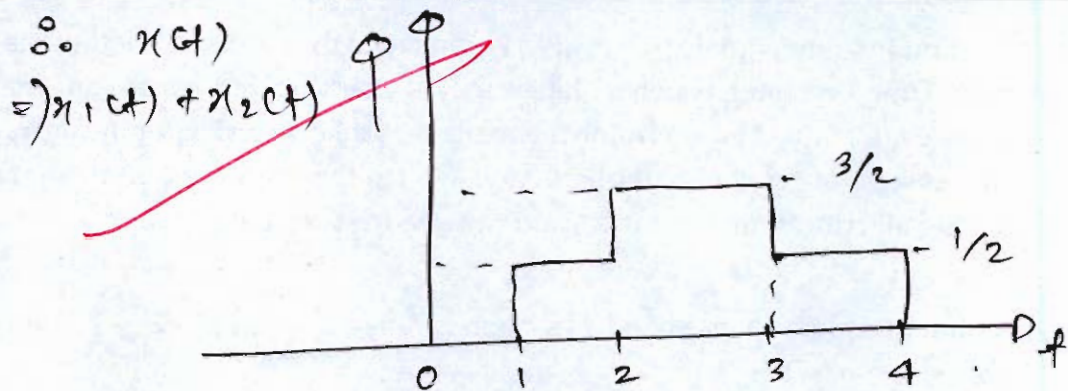

$$(ii) I = \int_{-\infty}^2 \left[\cos \frac{\pi}{2} t \cdot \delta'(2t-1) + \frac{\cos \pi t}{2} \cdot \delta(t-4) \right] dt$$

$$I = \pi_1(t) + \pi_2(t)$$

$$\text{for } \pi_2(t) = \int_{-\infty}^2 \cos \frac{\pi}{2} t \cdot \delta(t-4) dt$$

$$\boxed{\pi_2(t) = 0}$$

$\infty \circ$ Impulse is out of integration range

$$\infty \circ I = \int_{-\infty}^2 \cos \frac{\pi}{2} t \cdot \delta'(2(t-1/2)) dt$$

we know $\int_{-\infty}^{\infty} \pi(t) \cdot \delta'(t) dt = (-1)^n \frac{d^n \pi(t)}{dt^n} \Big|_{t=t_1}$

$$I = \frac{1}{(2)^2} \times \frac{d}{dt} \cos \frac{\pi}{2} t \Big|_{t=1/2}$$

$$I = \frac{1}{4} \times \sin \frac{\pi}{2} t \Big|_{t=1/2} \times \frac{\pi}{2}$$

$$I = \frac{\pi}{8} \times \sin \frac{\pi}{4}$$

$$\Rightarrow \boxed{I = \frac{\pi}{8\sqrt{2}}}$$

ans

Handwritten signature

Q.7(b) (i) A continuous-time signal $x(t) = e^{2t}u(-t)$ is applied to the input of a continuous-time Linear Time-Invariant system. The system is characterized by its unit impulse response $h(t) = u(t-3)$. Determine the mathematical expression for the output $y(t)$ of the system using convolution integral. Sketch the resulting output signal $y(t)$ labelling all critical time instances and the steady state value.

(ii) The unit sample response of a LTI system is $h(n) = 3\left(\frac{1}{2}\right)^n u(n) - 2\left(\frac{1}{3}\right)^{n-1} u(n)$ and the output of the system is $y(n)$ when unit step $u(n)$ is applied at the input. Determine the steady state value of the output as $n \rightarrow \infty$.

[10 + 10 marks]

Q.7 (b) (i) Given: $x(t) = e^{2t}u(-t)$

$$h(t) = u(t-3)$$

Statement: using convolution integral property,

$$y(t) = x(t) * h(t)$$


$$y(t) = \int_{-\infty}^{\infty} x(z) \cdot h(t-z) \cdot dz$$

$$(or) y(t) = \int_{-\infty}^{\infty} x(t-z) \cdot h(z) \cdot dz$$

$$\therefore y(t) = \int_{-\infty}^{\infty} e^{2(t-z)} u(-(t-z)) \cdot u(z-3) \cdot dz$$


$$y(t) = \int_{-\infty}^{\infty} e^{2t} \cdot e^{-2z} u(z-t) \cdot u(z-3) \cdot dz$$

calculating range,

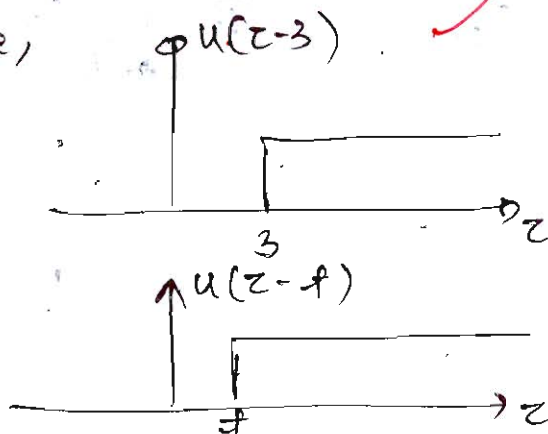

Case - (1) $0 < t < 3$
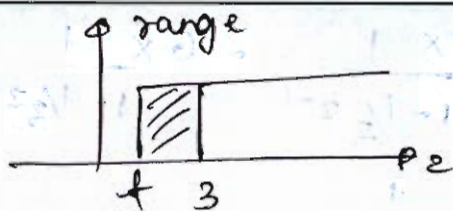
$$y(t) = \int_t^3 e^{2t} \cdot e^{-2z} \cdot dz$$




$$y(t) = e^{2t} \cdot \frac{e^{-2z}}{-2} \Big|_t^3 = -\frac{1}{2} e^{2t} [e^{-6} - e^{-2t}]$$

$$y(t) = \frac{1}{2} - \frac{1}{2} e^{-6} \cdot e^{2t} \quad 0 < t < 3$$


Case - (2) $t > 3$
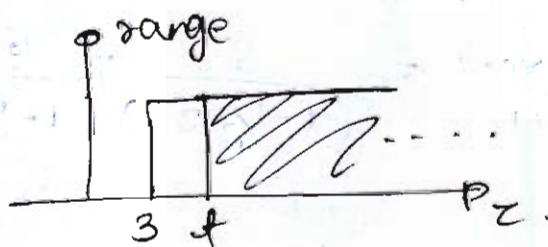
$$y(t) = \int_t^{\infty} e^{2t} \cdot e^{-2z} \cdot dz$$



$$y(t) = e^{2t} \cdot \frac{e^{-2z}}{-2} \Big|_t^{\infty} = -\frac{1}{2} e^{2t} [0 - e^{-2t}]$$

$$y(t) = \frac{1}{2} \quad t > 3$$

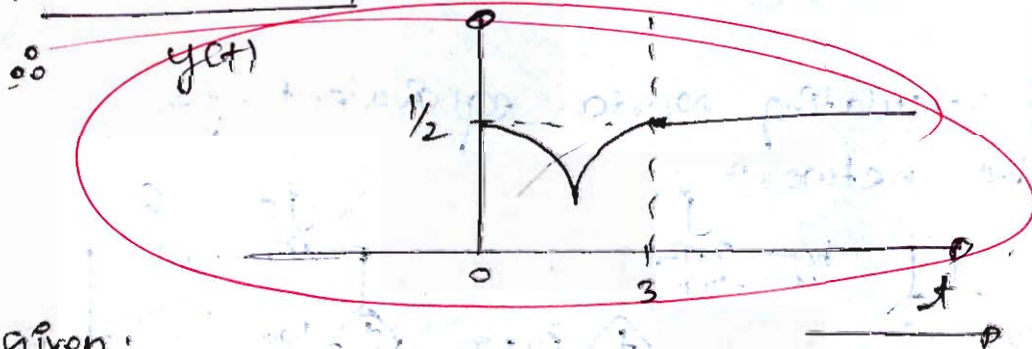

Given:

$$(b) (ii) \cdot h(t) = 3 \left(\frac{1}{2}\right)^n u(t) - 2 \left(\frac{1}{3}\right)^{n-1} u(t)$$

Statement: By F.V.T. of z-T.

$$\lim_{y \rightarrow \infty} y(t) = \lim_{z \rightarrow 0} (1 - z^{-1}) \cdot Y(z)$$

(b) Ans

$$H(z) = \frac{3 \times 1}{1 - \frac{1}{2}z^{-1}} - \frac{6 \times 1}{1 - \frac{1}{3}z^{-1}} = \frac{3}{\frac{1}{2}} - \frac{6}{\frac{2}{3}}$$

$$X(z) = \frac{1}{1 - z^{-1}}$$

$$Y(z) = X(z) \cdot H(z)$$


$$Y(z) = \frac{3}{(1 - z^{-1})(1 - \frac{1}{2}z^{-1})} - \frac{6}{(1 - z^{-1})(1 - \frac{1}{3}z^{-1})}$$

$\lim_{n \rightarrow \infty} y(n) = -3$

but properly,

$$\lim_{z \rightarrow 1} Y(z) = \frac{3}{(1 - \frac{1}{2})} - \frac{6}{(1 - \frac{1}{3})}$$

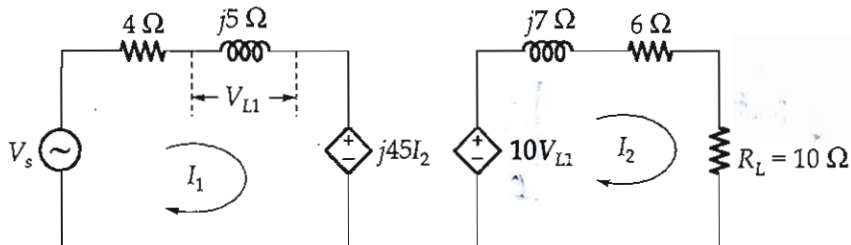
Q.7 (c) In the circuit shown below, if the source voltage $V_s = 110 \angle 53.13^\circ \text{V}$.



With the help of Norton and Maximum power transfer theorem, determine whether the maximum power is transferred to load for $R_L = 10 \Omega$, and also calculate the power delivered to load for $R_L = 10 \Omega$.

[20 marks]

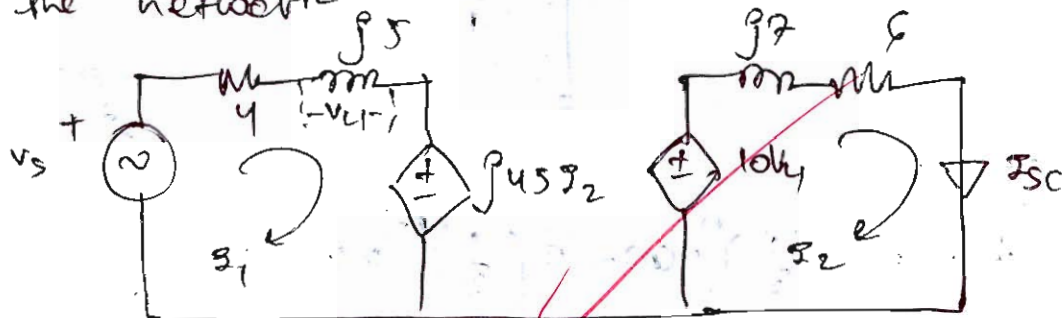Q7 (c) calculating norton equivalent for the network



Here $I_{sc} = I_2$

By KVL, ①,

$$I_1 = \frac{V_s - j45 I_2}{4 + j5} \quad \text{--- ①}$$

By KVL, ②,

$$I_2 = \frac{10 \times [j5] [I_1]}{6 + j7} \quad \text{--- ②}$$

$$I_2 = \left(\frac{50j}{6 + j7} \right) I_1$$

Put ② in ①,

$$I_1 = \frac{V_s}{4 + j5} - \frac{j45}{4 + j5} \times \left[\frac{50j}{6 + j7} \right] I_1$$

$$I_1 [8.10 + j37.44] = \frac{V_s}{4 + j5}$$

$$\therefore I_1 = 0.108 - j0.435$$

$$\boxed{I_1 = 0.44 \angle -76^\circ \text{ A}}$$


$$\therefore I_2 = \frac{(0.108 - j0.435)(4 + j5) - V_s}{-j45}$$

$$I_2 = 1.98 - j1.40$$

$$\boxed{I_2 = 2.43 \angle -35.40^\circ \text{ A}}$$


$$\therefore I_N = I_{sc} = 2.43 \angle -35.40^\circ \text{ A}$$

Calculation of Z_{Th} :

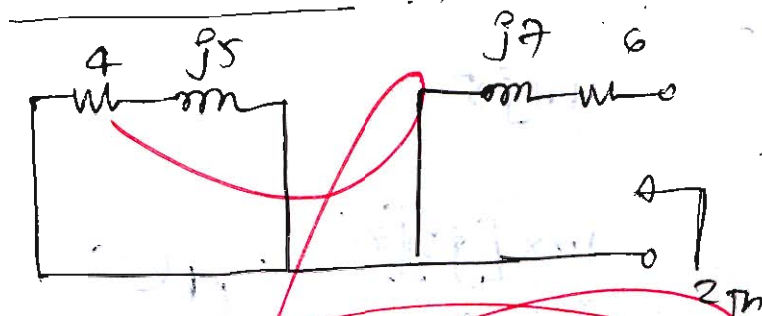

$$Z_{Th} = 6 + j7 \Omega$$

Norton's Equivalent :

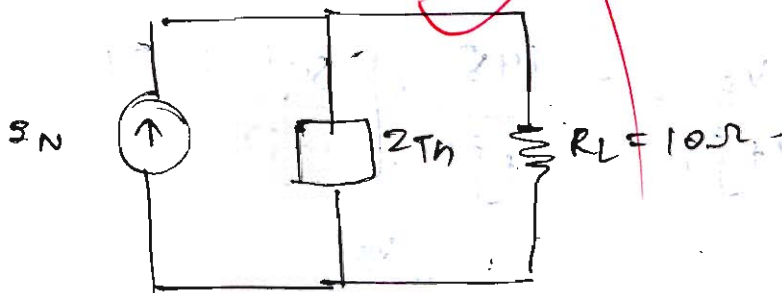

According to maximum power transfer theorem, maximum power would be transmitted when $R_L = Z_{Th}$:

Since load is purely resistive,


for max^m power, $R_L = \sqrt{R_{Th}^2 + X_{Th}^2}$.

$$R_L = \sqrt{(6)^2 + (7)^2}$$

$$R_L = 9.2 \Omega$$

Hence load should be of value 9.2Ω
for maximum power transfer to occur.

Power delivered when $R_L = 10 \Omega$

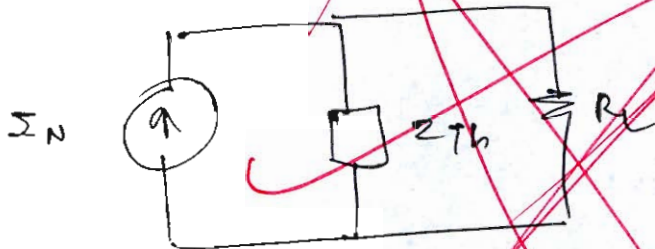

$$P_L = (I_L)^2 \times R_L$$

$$I_L = \frac{I_N \times Z_{Th}}{Z_{Th} + R_L} = \frac{2.43 \angle -35.40^\circ \times (6 + j7)}{16 + j7}$$

$$I_L = 1.264 - j0.21 \text{ A}$$

$$I_L = 1.28 \angle -9.63^\circ$$

$$P_L = (1.28)^2 \times 10$$

$$P_L = 16.384 \text{ watts}$$


improve your accuracy

- Q.8 (a) (i) When connected to a 120 V (rms), 60 Hz power line, a load absorbs 4 kW at a lagging power factor of 0.8. Find the value of capacitance required to be added in parallel to raise the pf to 0.95 while the load absorbs the same power.
- (ii) A series-connected circuit has $R = 4 \Omega$ and $L = 25$ mH.
1. Calculate the value of C that will produce a quality factor of 50.
 2. Find half power frequencies ω_1 , ω_2 and BW.
 3. Determine the average power dissipated at $\omega = \omega_0, \omega_1, \omega_2$.
- (Take $V_m = 100$ V.)

[10 + 10 marks]

(Q8)

(a) (i) Given conditions

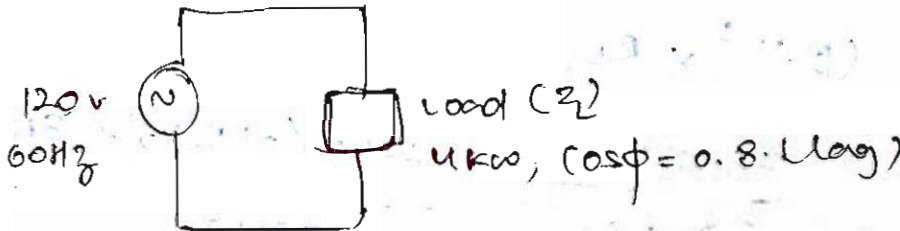

$$\text{let } Z_L = R + jX$$

$$P_{\text{active}} = \frac{V_{\text{rms}}^2}{R}; \quad 4 \times 10^3 = \frac{(120)^2}{R}$$

$$R = 3.6 \Omega$$

$$\cos \phi = \frac{R}{Z} \quad \therefore Z = \frac{R}{\cos \phi}$$

$$\therefore Z = 5.16 \Omega$$


$$(5.16)^2 = (3.6)^2 + X^2$$

$$X_L = 3.70 \Omega$$

$$\therefore Z_L = 3.6 + j 3.70 \Omega$$

A P Q,

120V,
60 Hz

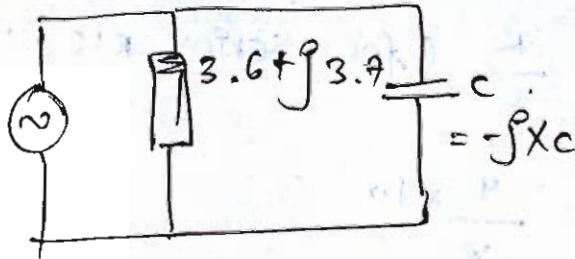

$$\cos \phi = 0.95$$

$$Y_{eq} = \frac{1}{3.6 + j3.7} + \frac{j}{X_c}$$

$$Y_{eq} = 0.135 - j0.1388 + \frac{j}{X_c}$$

$$\cos \phi = \frac{R}{Z} \text{ or } R \cdot Y$$

$$0.95 = 0.135 \times Y$$

$$Y = 7.0325$$

$$X_c = 0.144 \angle 88.84^\circ$$

$$\frac{1}{\omega C} = 0.144$$

$$C = 0.115 \text{ F}$$

(a) (ii) $R = 4 \Omega$

$L = 25 \text{ mH}$

$Q = 50$

1. for series RLC,

$$Q = \frac{X_L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$50 = \frac{1}{4} \sqrt{\frac{25 \text{ m}}{C}}$$

$$C = 6.28 \times 10^{-7} \text{ F}$$

$$20 \quad B.W = \frac{R}{L} \quad (\text{for series RLC circuit})$$

$$B.W = \frac{4 \times 10^3}{28}$$

$$B.W = 160 \text{ rad/sec}$$



(i) An LTI system S is defined by its impulse response:

$$h(t) = \frac{\sin(4(t-1))}{\pi(t-1)}$$


The system is excited by an input signal $x(t) = \cos\left(6t + \frac{\pi}{2}\right)$. Using frequency-domain analysis, determine the mathematical expression for the output $y(t)$.

(ii) The impulse response of a causal discrete time LTI system is given by $h[n] = a^n u[n]$, where $a > 0$ and $u[n]$ is the unit step function. Derive the expression for the unit step response $s[n]$ of the system. It is given that the step response at $n = 2$ is $s[2] = 7$. Determine the value of the parameter a .

[10 + 10 marks]

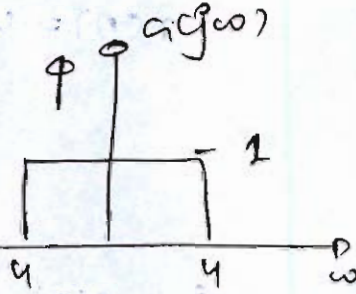
(b) (i) Given: $h(t) = \frac{\sin(4(t-1))}{\pi(t-1)}$

Let, $g(t) = \frac{\sin 4t}{\pi t}$ $\xrightarrow{FT.}$ $ac(\omega) =$



$\downarrow t \rightarrow t-1$

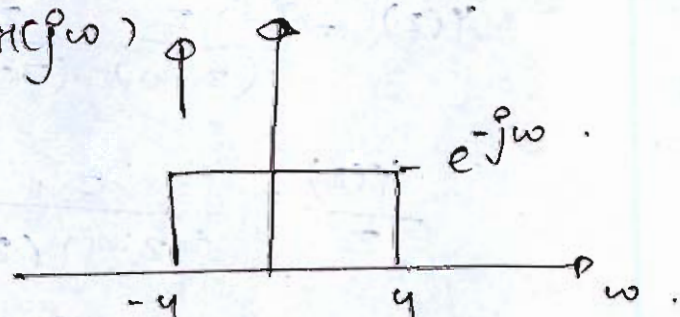~~$H(\omega) = g(t-1) = \frac{\sin 4(t-1)}{\pi(t-1)} \Rightarrow H(\omega) =$~~



$\therefore H(\omega) = e^{-j\omega} [u(\omega+4) - u(\omega-4)]$

Now,

$x(t) = \cos\left(6t + \frac{\pi}{2}\right)$

Here, $\omega = 6$ (for input signal)

but $H(\omega) = 0$, for $\omega = 6$

$\therefore \boxed{y(t) = 0}$

10

Good

(ii) Given: $h[n] = a^n u[n]$

Statement: By property of z-Transform

$$a^n u[n] \Rightarrow \frac{1}{1-a z^{-1}} \quad (\text{or}) \quad \frac{z}{z-a}$$

$$\therefore H(z) = \frac{z}{z-a} = \frac{Y(z)}{X(z)}$$

$$x[n] = u[n] \xrightarrow{\text{z.T}} X(z) = \frac{1}{1-z^{-1}} \quad \text{or} \quad \frac{z}{z-1}$$

$$\therefore Y(z) = X(z) \cdot H(z)$$

$$Y(z) = \frac{z}{z-a} \cdot \frac{z}{z-1}$$

$$\frac{Y(z)}{z} = \frac{z}{(z-a)(z-1)}$$

By partial fractions,

$$\frac{Y(z)}{z} = \frac{A}{z-a} + \frac{B}{z-1}$$

$$\frac{Y(z)}{z} = \frac{a/a-1}{z-a} + \frac{1/1-a}{z-1}$$

$$\therefore y[n] = \frac{a}{a-1} \cdot a^n u[n] + \frac{1}{1-a} u[n] \quad \text{--- (1)}$$

Putting $s[2] = 7$ in (1).

$$y[n] \Big|_{n=2} = 7 = \frac{a}{a-1} \cdot a^n u[2] + \frac{1}{1-a} u[2]$$

$$7 = \frac{a^3}{a-1} - \frac{1}{a-1} \Rightarrow \frac{a^3-1}{a-1}$$

$$a^3 - 1 = 7a - 7$$

$$a^3 - 7a + 6 = 0$$

$$a = -3, 2$$

Given, $a > 0$.

$$\therefore \boxed{a = 2}$$


$$y[n] = \frac{2^{n+1}}{1} \cdot u[n] - u[n]$$

$$\boxed{y[n] = [2^{n+1} - 1] u[n]} \quad \text{--- (2)}$$

Hence (2) represents the step response for the system.

Goal (10)

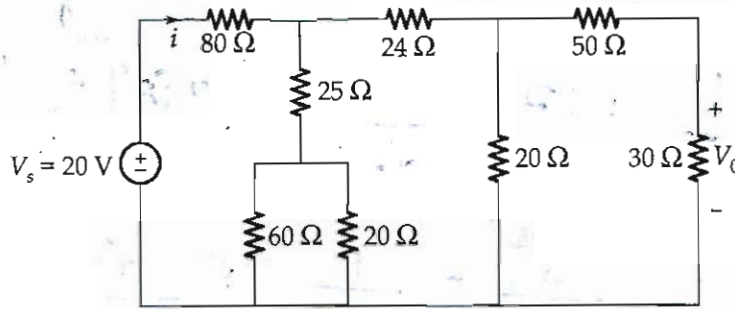Q.8 (c) (i) For the circuit shown in figure below:




Calculate:

1. Input current, i
 2. Output voltage, V_0
 3. Power Efficiency of the system if V_s and i is considered as input and P_0 is considered as output power.
- (ii) Let $u(t)$ be the unit step function and $r(t) = tu(t)$ be the unit ramp function. Derive the expression for the convolution $z(t) = u(t + 1) * r(t - 2)$. Simplify the result and sketch the waveform of $z(t)$.

[12 + 8 marks]

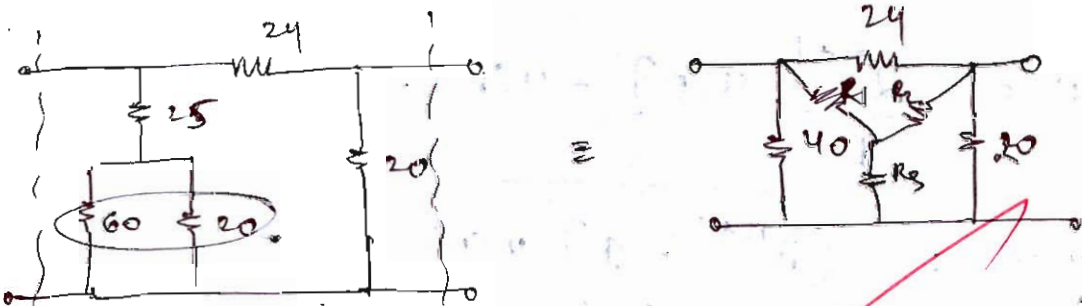Q8 (c) (i) simplifying middle section of the circuit,




$$\frac{60 \times 20}{80} = 15$$

Taking star-delta Transformation,

$$R_1 = \frac{40 \times 24}{84} ; R_2 = \frac{24 \times 20}{84} , R_3 = \frac{40 \times 20}{84}$$

$$R_1 = \frac{80}{7} ; R_2 = \frac{40}{7} , R_3 = \frac{200}{21}$$

circuit,

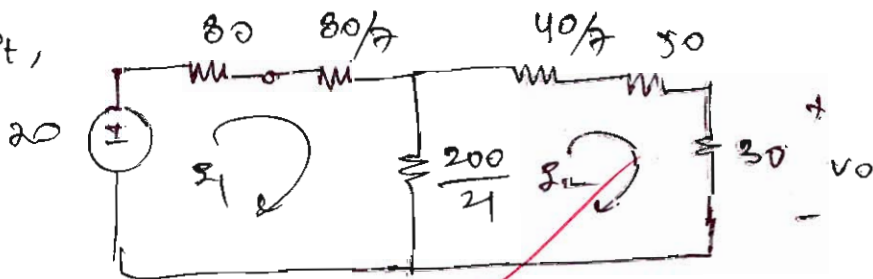

Taking currents I_1 & I_2 ,

$$20 = \left(\frac{80 + 80 + 200}{7} \right) I_1 - \frac{200}{21} I_2 \quad \text{--- (1)}$$

$$\left(\frac{200}{21} + \frac{40}{7} + 80 \right) I_2 = \frac{200}{21} I_1 \quad \text{--- (2)}$$

$$\frac{2000}{21} I_2 = \frac{200}{21} I_1$$

$$\therefore \boxed{10 I_2 = I_1} \quad \text{--- (3)}$$

$$20 = 1000 I_2$$

$$\therefore \boxed{I_2 = 20 \text{ mA}}$$

$$\therefore \boxed{I_1 = 200 \text{ mA}} \quad \text{--- (4)}$$

$$V_0 = 30 \times 20 \text{ mA}$$

$$\boxed{V_0 = 0.6 \text{ V}} \quad \text{--- (5)}$$

Power efficiency η

$$P_{\text{input}} = 20 \times 200 \text{ mwatts}$$

$$P_{\text{out}} = 0.6 \times 20 \text{ mwatts}$$

$$\eta = \frac{\text{output}}{\text{input}} = \frac{0.6 \times 20}{20 \times 200} \times 100$$

$$= 0.3\%$$

Q8 (c) (ii) given: $z(t) = u(t+1) * x(t-2)$.




statement: Convolution of two signals is,

$$y(t) = x(t) * h(t)$$

$$y(t) = \int_{-\infty}^{\infty} x(z) \cdot h(t-z) dz$$

$$\therefore z(t) = \int_{-\infty}^{\infty} x(z-2) \cdot u(t-z+1) dz$$
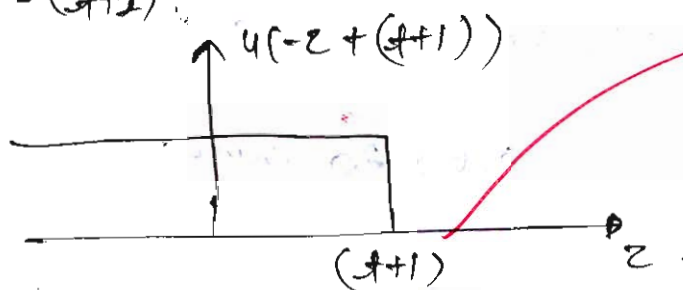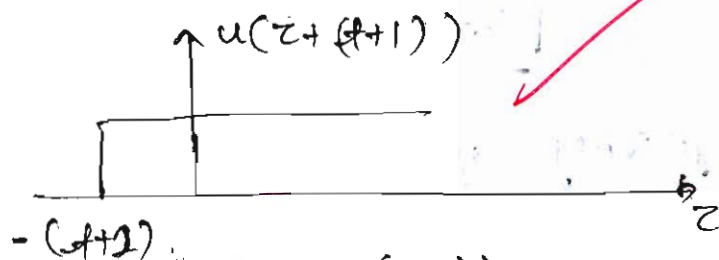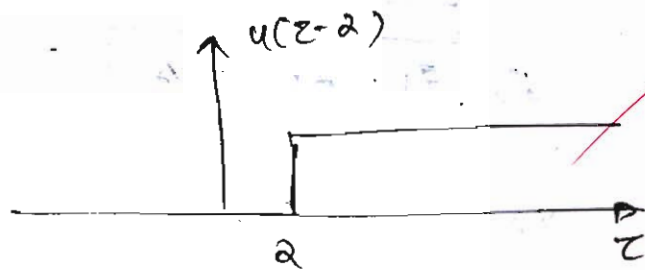
$$z(t) = \int_{-\infty}^{\infty} (z-2)u(z-2) \cdot u(-z+t+1) dz$$




Case ①, $t+1 < 2$.

$$\therefore t < 1$$

$$\therefore z(t) = 0$$

Case - (2), $t+1 > 2$.
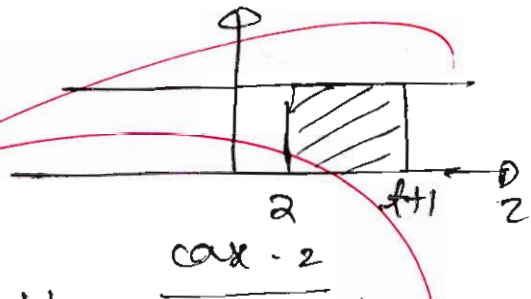
$$\therefore z(t) = \int_2^{t+1} (z-2) \cdot dz$$



$$z(t) = \left. \frac{z^2}{2} - 2z \right|_2^{t+1}$$

$$z(t) = \frac{(t+1)^2}{2} - 2(t+1) - 2 + 4$$

$$z(t) = \frac{(t+1)^2}{2} - 2t, \quad t \geq 1$$

$$\therefore z(t) = \begin{cases} 0, & t < 1 \\ \frac{(t+1)^2}{2} - 2t, & t \geq 1 \end{cases}$$

Ans

Graph??

Handwritten notes and diagrams on a page, including:

- A diagram of a rectangular structure with dimensions and labels.
- Equations involving variables like h , b , and s .
- Text such as "Solve for h " and "Solve for b ".
- Other mathematical expressions and calculations.

Space for Rough Work

$$\frac{1}{s^2(s+1)} = \frac{A}{s^2} + \frac{B}{s+1}$$

$$\frac{A}{s} + \frac{B}{s^2} + \frac{C}{s+1}$$

$$\frac{AC(s+1) + Bs^2}{s^2(s+1)}$$

$$\frac{As(s+1) + B(s+1) + Cs^2}{s^2(s+1)}$$

$$As + A + Bs^2$$

$$\frac{As^2 + As + Bs + B + Cs^2}{\text{deno.}}$$

$$B=0$$

$$A+C=0$$

$$A+B=0$$


$$C=1$$

$$B=1$$

$$A=-1$$

$$\left(\frac{1}{3}\right)^n \cdot \left(\frac{1}{3}\right)^{n-1}$$

$$3 \cdot \left(\frac{1}{3}\right)^n$$

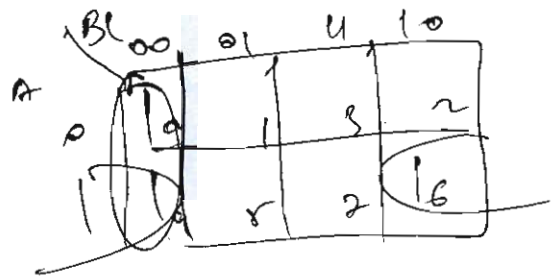

$$A \bar{C} + \bar{B} \bar{C}$$

$$F_1 = \bar{A} \bar{C} + \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C}$$

$$F_2 = \bar{A} \bar{B} + \bar{A} \bar{B}$$

$$F_3 = \bar{B} \bar{C}$$

$$\bar{F}_4 = \bar{A} \bar{C} + \bar{B} \bar{C}$$

Space for Rough Work

$\vec{a} = a_1\hat{i} + a_2\hat{j} + a_3\hat{k}$
 $\vec{b} = b_1\hat{i} + b_2\hat{j} + b_3\hat{k}$
 $\vec{c} = c_1\hat{i} + c_2\hat{j} + c_3\hat{k}$
 $\vec{d} = d_1\hat{i} + d_2\hat{j} + d_3\hat{k}$

$\vec{a} \cdot \vec{b} = a_1b_1 + a_2b_2 + a_3b_3$
 $\vec{a} \cdot \vec{c} = a_1c_1 + a_2c_2 + a_3c_3$
 $\vec{a} \cdot \vec{d} = a_1d_1 + a_2d_2 + a_3d_3$

$\vec{a} \times \vec{b} = (a_2b_3 - a_3b_2)\hat{i} - (a_1b_3 - a_3b_1)\hat{j} + (a_1b_2 - a_2b_1)\hat{k}$
 $\vec{a} \times \vec{c} = (a_2c_3 - a_3c_2)\hat{i} - (a_1c_3 - a_3c_1)\hat{j} + (a_1c_2 - a_2c_1)\hat{k}$
 $\vec{a} \times \vec{d} = (a_2d_3 - a_3d_2)\hat{i} - (a_1d_3 - a_3d_1)\hat{j} + (a_1d_2 - a_2d_1)\hat{k}$



$\vec{a} \cdot (\vec{b} \times \vec{c}) = \begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}$
 $\vec{b} \cdot (\vec{c} \times \vec{a}) = \begin{vmatrix} b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \\ a_1 & a_2 & a_3 \end{vmatrix}$
 $\vec{c} \cdot (\vec{a} \times \vec{b}) = \begin{vmatrix} c_1 & c_2 & c_3 \\ a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \end{vmatrix}$

$\vec{a} \cdot \vec{a} = a_1^2 + a_2^2 + a_3^2$

$\vec{a} \cdot \vec{b} = |\vec{a}||\vec{b}|\cos\theta$
 $\vec{a} \cdot \vec{c} = |\vec{a}||\vec{c}|\cos\phi$
 $\vec{a} \cdot \vec{d} = |\vec{a}||\vec{d}|\cos\psi$