

• Simplify  
your  
answers



• Write  
all steps

**MADE EASY**  
Leading Institute for ESE, GATE & PSUs

# ESE 2026 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

## Electrical Engineering

### Test-5 : Basic Electronics Engineering + Analog Electronics + Electrical Materials + Electrical Machines-1 + Power Systems-2

Name : .....

Roll No :

#### Test Centres

Delhi

Bhopal

Jaipur

Pune

Hyderabad

#### Student's Signature

#### Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

#### FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	48
Q.2	49
Q.3	
Q.4	54
Section-B	
Q.5	33
Q.6	
Q.7	
Q.8	21
<b>Total Marks Obtained</b>	<b>205</b>

Signature of Evaluator

Cross Checked by

## IMPORTANT INSTRUCTIONS

**CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.**

### DONT'S

1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

### DO'S

1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

## Section A : B.E.E. + Analog Electronics + Electrical Materials

Q.1 (a) For a dielectric, establish an expression for the relationship between the polarizability and permittivity. How does this relation lead to Clausius-Mosotti equation?

[12 marks]

Polarizability ( $\alpha$ ) & Permittivity ( $\epsilon$ )

We know for solid dielectric material

$$\vec{D} = \epsilon_0 \vec{E} + \vec{P} \quad \text{so} \quad \vec{P} \text{ (Polarization)} = \vec{D} - \epsilon_0 \vec{E}$$

$$\vec{P} = \epsilon_0 \epsilon_r \vec{E} - \epsilon_0 \vec{E} = \epsilon_0 (\epsilon_r - 1) \vec{E}$$

$$\vec{P} = N \alpha \epsilon_0 \vec{E} = \epsilon_0 (\epsilon_r - 1) \vec{E}_{\text{int}} \quad \text{--- (1)}$$

For  $N$  atoms/ $\text{m}^3$  & polarizability  $\alpha$  ( $\text{Fm}^2$ )

$$\vec{P} = N \alpha \vec{E}_{\text{tot}} \quad \text{--- (2)}$$

$$\text{Now } E_{\text{total}} = E + \frac{yP}{\epsilon_0}$$

For cubical symmetrical structure  $y = \frac{1}{3}$ .

$$E_{\text{total}} = \vec{E}_{\text{int}} + \frac{\vec{P}}{3\epsilon_0}$$

Put  $E_{\text{total}}$  in eq<sup>n</sup> (2)

$$\vec{P} = N \alpha \left[ \vec{E}_{\text{int}} + \frac{\vec{P}}{3\epsilon_0} \right]$$

$$\text{Also } \vec{P} = \epsilon_0 (\epsilon_r - 1) \vec{E}_{\text{int}} = N \alpha \left[ \vec{E}_{\text{int}} + \frac{\epsilon_0 (\epsilon_r - 1) \vec{E}_{\text{int}}}{3\epsilon_0} \right]$$

$$\text{So } \epsilon_0 (\epsilon_r - 1) = N \alpha \left[ 1 + \frac{\epsilon_r - 1}{3} \right]$$

$$\epsilon_0 (\epsilon_r - 1) = \frac{N \alpha}{3} (\epsilon_r + 2)$$

$$\text{So By solving } \boxed{\frac{N \alpha}{3 \epsilon_0} = \frac{\epsilon_r - 1}{\epsilon_r + 2}} \quad \leftarrow \text{Ans}$$

This equation lead to Clausius Mosotti eq<sup>n</sup>

If that polarizability belong to  
electronic & ionic so

$$\alpha_{\text{tot}} = \alpha_e + \alpha_i$$

$$\frac{N\alpha_{\text{tot}}}{3\epsilon_0} = \frac{\epsilon_r - 1}{\epsilon_r + 2}$$

← Clausius Mosotti  
Equation

For optical range or very high freq.

$$\alpha_i = 0, \quad \alpha_{\text{tot}} = \alpha_e, \quad \epsilon_r = n^2$$

So

$$\frac{N\alpha_e}{3\epsilon_0} = \frac{n^2 - 1}{n^2 + 2}$$


(11)

Good  
Approach

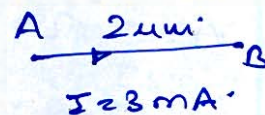- Q.1 (b) (i) Hall measurements are made on a P-type semiconductor bar of  $500 \mu\text{m}$  wide and  $20 \mu\text{m}$  thick. The Hall contacts A and B are displaced  $2 \mu\text{m}$  with respect to each other in the direction of current flow of  $3 \text{ mA}$ . The voltage between A and B with a magnetic field of  $10^{-4} \text{ Wb/cm}^2$  pointing out of the plane of the sample is  $3.2 \text{ mV}$ . When the magnetic field direction is reversed, the voltage changes to  $2.8 \text{ mV}$ . What is the hole concentration and mobility?

[8 marks]

Given:  $500 \mu\text{m}$  wide.  
 $20 \mu\text{m}$  thick.



$$V_{AB} = 3.2 \text{ mV}$$

$$B \text{ (magnetic field)} = 10^{-4} \frac{\text{Wb}}{\text{cm}^2} = \frac{10^{-4}}{10^4} = \frac{1 \text{ Wb}}{\text{m}^2}$$

If B reversed  $V_{\text{new}} = 2.8 \text{ mV}$ .

To find Hole concentration & mobility.

$$\text{Hall voltage } V_H = R_H \frac{B_z I_x}{d}$$

$$\text{So } 3.2 \times 10^{-3} = R_H \times \frac{10^{-4}}{10^4} \times \frac{3 \times 10^{-3}}{2 \times 10^{-6}}$$

$$\text{So Hall coefficient} = R_H = \frac{3.2 \times 10^{-3} \times 2 \times 10^{-6}}{3 \times 10^{-3}}$$

$$R_H = 2.133 \times 10^{-6}$$

$$\text{So } R_H = \frac{1}{nq} = \frac{1}{ne} = \frac{1}{pe}$$

$$\text{Hole concentration} = p = \frac{1}{R_H \cdot e} = \frac{1}{2.133 \times 10^{-6} \times 1.6 \times 10^{19}}$$

$$\text{Hole conc.} = 0.2929 \times 10^{25} = 2.929 \times 10^{24} \text{ / m}^3$$

← Ans

we know Mobility  $(\mu) = \frac{RH}{\rho} = \frac{1}{ne\tau}$ .

$$\rho = \frac{RA}{l}$$

$$R = \frac{\Delta V}{I} = \frac{3.2 - 2.8}{3} = \frac{0.4}{3} \Omega$$

$$A = 500 \times 20 \times 10^{-12} \text{ m}^2$$

$$l = 2 \times 10^6$$

$$\rho = \frac{RA}{l} = \frac{0.4}{3} \times \frac{500 \times 20 \times 10^{-12}}{2 \times 10^6} = \frac{0.4}{3} \times 5 \times 10^{-3}$$

$$\rho = \frac{2}{3} \times 10^{-3}$$

$$\text{Mobility } \mu = \frac{RH}{\rho} = \frac{2.929 \times 10^{24}}{\frac{2}{3} \times 10^{-3}}$$

$$\mu = 4.39 \times 10^{27} \frac{\text{m}^2}{\text{V-s}}$$

← Ans

5

- Q.1 (b) (ii) A sample of Si doped with phosphorus  $10^{17}$  atoms/cm<sup>3</sup>. What would be its resistivity if the electron mobility is  $700 \text{ cm}^2/\text{V}\cdot\text{s}$ ? What would be the Hall voltage in a sample  $100 \mu\text{m}$  thick if  $I_x = 1 \text{ mA}$  and  $B_z = 10^{-5} \text{ Wb}/\text{cm}^2$ .

[4 marks]

Given

$$\mu_e = 700 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}, \quad n = 10^{17} \frac{\text{atoms}}{\text{cm}^3}$$

we know

$$\sigma = ne\mu = \frac{1}{\rho} \quad \text{where } \sigma = \text{conductivity} \\ \mu = \text{mobility}$$

$$\rho = \frac{1}{\sigma} = \frac{1}{ne\mu}$$

$$= \frac{1}{10^{17} \times 1.6 \times 10^{19} \times 700 \times 100} = 0.089 \times 10^{-2} \frac{\text{V}\cdot\text{m}}{\text{m}^2}$$

↳ Ans.

Now for Hall voltage

$$\text{Given: } d = 100 \mu\text{m} = 100 \times 10^{-6}$$

$$I_x = 1 \text{ mA}, \quad B_z = 10^{-5} \frac{\text{wb}}{\text{cm}^2}$$

$$\text{we know Hall voltage } R_H \frac{B_z I_x}{d} = V_H$$

$$\text{so } V_H = \mu \rho \frac{B_z I_x}{d} = \frac{B_z I_x}{ne d}$$

$$\rho = \frac{R_H}{\mu}$$

$$V_H = \frac{10^{-5} \text{ wb} \times 10^{-3} \text{ A}}{10^{17} \frac{\text{atoms}}{\text{cm}^3} \times 1.6 \times 10^{19} \times 100 \times 10^{-6} \text{ m}}$$


$$V_H = \frac{10^{-5-3+4}}{10^{17+6-19} \times 1.6 \times 10^{-4}} = \frac{10^{-4}}{10^4 \times 1.6 \times 10^{-4}} = 0.625 \times 10^{-4}$$

$$V_H = 6.25 \times 10^{-5} = 62.5 \mu\text{V} \quad \leftarrow \underline{\text{Ans}}$$

4

Good Approach

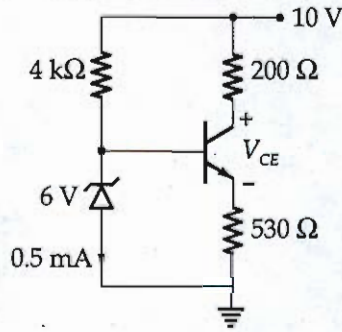Q.1 (c) In the circuit shown below,  $V_{BE} = 0.7$  V. Find the  $\beta$  of the transistor and  $V_{CE}$ .



At node A,  
After apply KCL  
 $I_A = I_B + 0.5$

Apply KVL in inner loop

$$6 - V_{BE} - 0.53 I_E = 0$$

$$6 - 0.7 = 0.53 I_E$$

$$\frac{5.3}{0.53} = I_E \Rightarrow I_E = 10 \text{ mA}$$

$$\text{Also } I_A = \frac{10 - 6}{4} = 1 \text{ mA}$$

$$\text{If } I_A = I_B + 0.5 \Rightarrow I_B = 0.5 \text{ mA}$$

$$\text{we know } I_E = I_B + I_C$$

$$\text{So } I_C = I_E - I_B = 10 - 0.5 = 9.5 \text{ mA}$$


$$\beta = \frac{I_C}{I_B} = \frac{9.5}{0.5} = 19$$

$\text{So } \beta = 19$

↳ Ans

Apply KVL in outer loop.

$$10 - 0.2 I_C - V_{CE} - 0.53 I_E = 0$$

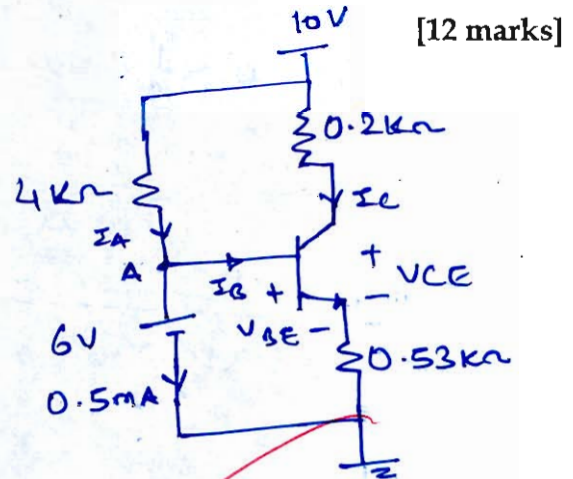

$$\begin{aligned}V_{CE} &= 10 - 0.2 I_C - 0.53 I_E \\ &= 10 - 0.2(9.5) - 0.53(10) \\ &= 10 - 1.9 - 5.3 = 2.8 \text{ volt}\end{aligned}$$

So  $V_{CE} > V_{CEsat} = 0.2$

Our Assumption correct That Transistor is in Active region.

Hence 

$V_{CE} = 2.8 \text{ volt}$
$\beta = 18$

 } Ans

(11)

Good  
Approach

Q.1 (d) Write a short note on Top-down technique and bottom-up technique used in nano-material synthesis.

[12 marks]

Two Synthesis Technique in nanomaterials

- 1) Top down Approach
- 2) Bottom up Approach.

Top down Approach

Element combined to form atom  
Atom combined to form molecule

Molecule combined to form cluster.

Here Breakdown of large component into small segments.


Different type of Theory are

Ion Plasma Exchange Theory

Bottom up Approach

~~slicing of cutting of material piece wise  
layer by layer.~~

Like

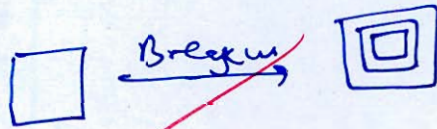

Different type of synthesis technique


- 1) Sol-Gel Analysis
- 2) CVD (Chemical vapour decomposition)
- 3) Ion-distillation

~~Many different type of thing combined to  
form single element~~

6

Elaborate  
it more

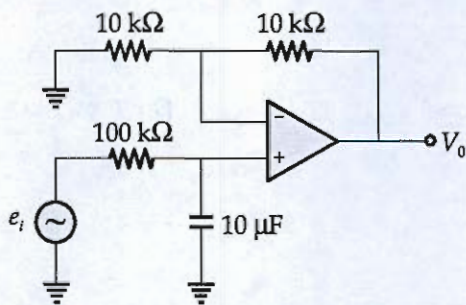Q.1 (e) In the circuit shown in figure below, if  $e_i = \sin t$ , find the voltage  $V_0$ .



[12 marks]

Given  $e_i = \sin t$

By voltage division rule

$$V_+ = \frac{1/sC}{R + 1/sC} e_i = \frac{e_i}{sRC + 1}$$

∴ In opamp due to Virtual Ground

$$V_+ = V_- = \frac{e_i}{sRC + 1} \quad \text{where } R = 100k\Omega, C = 10\mu F, e_i = \sin t$$

Now apply KCL at node c

$$\frac{V_c}{10} + \frac{V_c - V_0}{10} = 0$$

$$V_0 = 2V_c$$


$$V_0 = 2V_- = 2V_+$$

$$V_0 = \frac{2e_i}{sRC + 1}$$

$$= \frac{2 \sin t}{s \times 100 \times 10^3 \times 10 \times 10^{-6} + 1} = \frac{2 \sin t}{s + 1}$$

$$V_0(s) = \frac{2 \sin t}{s + 1}$$

$$V_0(j\omega) = \frac{2 \sin t}{j\omega + 1} = \frac{2}{\sqrt{\omega^2 + 1}} \sin(t - 45^\circ) \Big|_{\omega = 1}$$

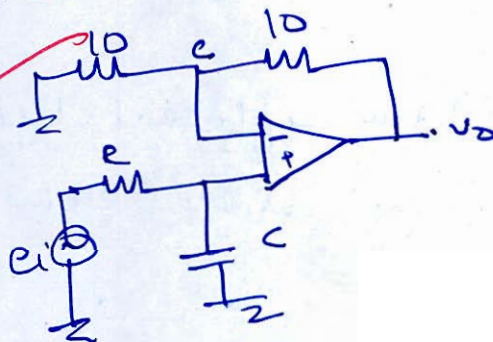

$$V_o(t) = \sqrt{2} \sin(t - 45^\circ)$$

$$V_o(s) = \frac{2s \sin t}{s+1}$$

Ans

11

Good  
Approach

- Q.2 (a) (i) Find out the velocity of light in a material which has a dielectric constant  $\epsilon_r$  of 5.5 and a magnetic susceptibility of  $-2.17 \times 10^{-5}$ .
- (ii) Consider a current of 10 A flowing through a coil of wire. The coil of wire 0.20 m long has 200 turns.
1. What is the magnitude of magnetic field strength  $H$ ?
  2. Calculate the flux density  $B$  if the coil is in a vacuum.
  3. Calculate the flux density inside a bar of titanium (susceptibility =  $1.81 \times 10^{-4}$ ) that is positioned within the coil.
  4. Calculate the magnitude of magnetization  $M$ .

[20 marks]

i) Given  $\epsilon_r = 5.5$  &

$$\chi_m = -2.17 \times 10^{-5}$$

To find velocity of light ( $v$ )

we know  $v = \frac{1}{\sqrt{\mu\epsilon}} = \frac{1}{\sqrt{\mu_0 \mu_r \epsilon_0 \epsilon_r}}$

$$= \frac{1}{\sqrt{\mu_r \epsilon_r}} \times c$$

$$c = \frac{1}{\sqrt{\mu_0 \epsilon_0}} = 3 \times 10^8 \frac{m}{s}$$

Now  $\mu_r = 1 + \chi_m$

$$\text{So } \mu_r = 1 + (-2.17 \times 10^{-5})$$

$$\mu_r = 0.9999783$$

$$\text{So } v = \frac{3 \times 10^8}{\sqrt{0.9999783 \times 5.5}} = 1.279 \times 10^8 \text{ m/s.}$$

↳ Ans.

ii) Given  $I = 10 \text{ A}$      $N = 200$   
 $l = 0.2 \text{ m}$

1) To find  $H$  (magnetic field strength)

we know By Ampere Circuital law

$$\oint \vec{H} \cdot d\vec{l} = NI.$$

$$\text{So } H = \frac{NI}{l} = \frac{200 \times 10}{0.2} = 10^4 \frac{\text{Amp}}{\text{m}}$$

← Ans.

2) To find  $B$  (Magnetic flux density)

In vacuum  $\mu_r = 1$

$$\text{So } B = \mu H = \mu_0 \mu_r H = 4\pi \times 10^{-7} (1) \times 10^4$$

$$B = 4\pi \times 10^{-3} = 0.01256 \frac{\text{wb}}{\text{m}^2}$$

← Ans

3) To find flux density inside bar if.

$$\chi_m = 1.81 \times 10^4$$

$$\text{So } \mu_r = 1 + \chi_m \Rightarrow \mu_r = 1 + 1.81 \times 10^4$$

$$\mu_r = 1.000181$$

$$\text{So } B = \mu H = \mu_0 \mu_r H = 4\pi \times 10^{-7} \times 1.000181 \times 10^4$$

$$B = 12.566 \times 10^{-3} = 1.256 \times 10^{-2} \frac{\text{wb}}{\text{m}^2}$$

← Ans

4) Magnitude of magnetization  $M$ .

$$M = \chi_m H$$

$$\text{So } B = \mu_0 (H + M) = \mu_0 (H + \chi_m H) = \mu_0 H (1 + \chi_m) \\ = \mu_0 \mu_r H = \mu H$$

$$M = 1.81 \times 10^4 \times 10^4 = 1.81 \frac{\text{Amp}}{\text{m}}$$


← Ans

18

Good  
Approach



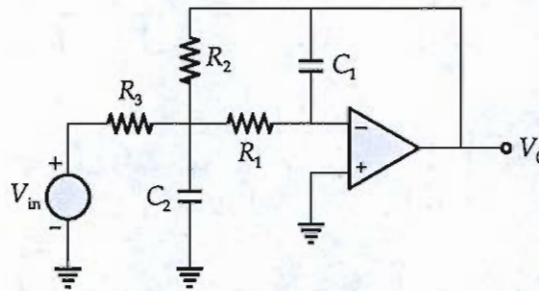Q.2(b) For the circuit shown below, find  $A_v = \frac{V_0}{V_{in}}$ , the damping factor and cutoff frequency.




[20 marks]

Given:

To find  $A_v = \frac{V_0}{V_{in}}$  & damping factor & cutoff freq.

By virtual short

$$V_+ = V_- = 0$$

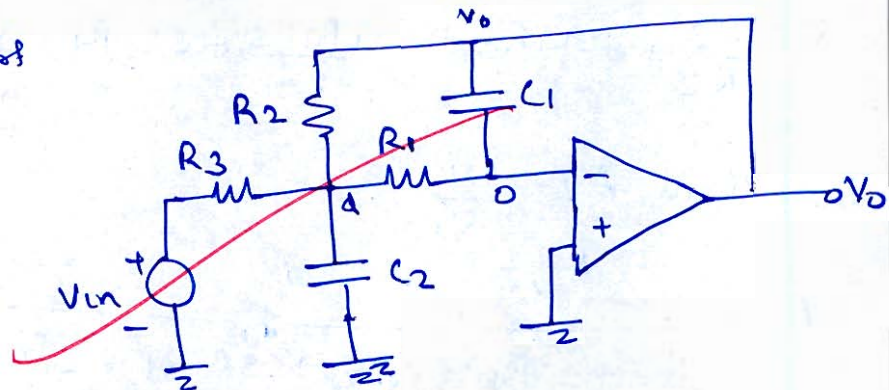

Apply KCL at node d

$$\frac{V_d - V_{in}}{R_3} + \frac{V_d - 0}{R_1} + \frac{V_d - V_0}{R_2} + \frac{V_d}{1/sC_2} = 0$$

$$V_d \left[ \frac{1}{R_3} + \frac{1}{R_1} + \frac{1}{R_2} + sC_2 \right] = \frac{V_0}{R_2} + \frac{V_{in}}{R_3} \quad \text{--- (1)}$$

Now apply KCL at ( $V_-$ ) point.

$$\text{So } \frac{0 - V_d}{R_1} + \frac{0 - V_0}{1/sC_1} + I_{int} = 0 \quad \because \text{(Internal current OP-AMP} \\ \text{= 0 due to high } Z_{in})$$

$$\text{So } sC_1 V_0 = -\frac{V_d}{R_1}$$

$$V_d = -sC_1 R_1 V_0$$

Put value of  $V_d$  in eq<sup>n</sup> (1)

$$-sC_1 R_1 V_0 \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + sC_2 \right] = \frac{V_0}{R_2} + \frac{V_{in}}{R_3}$$

$$\frac{V_0}{R_2} + sC_1 R_1 V_0 \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + sC_2 \right] = -\frac{V_{in}}{R_3}$$

$$V_0 \left[ \frac{1}{R_2} + sC_1 R_1 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + sC_2 \right) \right] = -\frac{V_{in}}{R_3}$$

$$V_0 \left[ \frac{1}{R_2} + sC_1 + sC_1 \frac{R_1}{R_2} + sC_1 \frac{R_1}{R_3} + s^2 R_1 C_1 C_2 \right] = -\frac{V_{in}}{R_3}$$

$$V_0 \left[ \frac{R_3}{R_2} + sC_1 R_3 + sC_1 \frac{R_1 R_3}{R_2} + sC_1 R_1 + s^2 R_1 R_3 C_1 C_2 \right] = -V_{in}$$

So Gain  $A_V = \frac{V_0}{V_{in}}$

$$A_V = \frac{-1}{\frac{R_3}{R_2} + s^2 R_1 R_3 C_1 C_2 + sC_1 R_1 + \frac{sC_1 R_3}{R_2}}$$

Put  $s = j\omega$

$$A_V = \frac{-1}{\frac{R_3}{R_2} - \omega^2 R_1 R_3 C_1 C_2 + j\omega C_1 R_1 \left( 1 + \frac{R_3}{R_2} \right)}$$

See denominator what is written & rearrange

$$s^2 R_1 R_3 C_1 C_2 + sC_1 R_1 \left( 1 + \frac{R_3}{R_2} \right) + \frac{R_3}{R_2} =$$

$$R_1 R_3 C_1 C_2 \left[ s^2 + \frac{sC_1 R_1 (R_2 + R_3)}{R_2 R_1 R_3 C_1 C_2} + \frac{R_3}{R_2 R_1 R_3 C_1 C_2} \right]$$

$$\text{So } A_v = \frac{-1/R_1 R_3 C_1 C_2}{s^2 + \frac{s(R_2 + R_3)}{R_3 R_2 C_2} + \frac{1}{R_1 R_2 C_1 C_2}} \quad \leftarrow \text{Ans}$$

Compare denominator with standard  
2<sup>nd</sup> order Transfer function

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$\text{So } \omega_n^2 = \frac{1}{R_1 R_2 C_1 C_2}, \quad \omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\text{So cut off freq } = f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}} \text{ Hz}$$

↳ Ans

$$2\zeta\omega_n = \frac{(R_2 + R_3)}{R_2 R_3 C_2}$$


$$\zeta = \frac{(R_2 + R_3) \sqrt{R_1 R_2 C_1 C_2}}{2R_2 R_3 C_2} = \frac{(R_2 + R_3)}{2R_3} \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

$$\text{So damping factor} = \frac{R_2 + R_3}{2R_3} \sqrt{\frac{R_1 C_1}{R_2 C_2}} \quad \leftarrow \text{Ans}$$

17


Go through the  
made easy  
solution

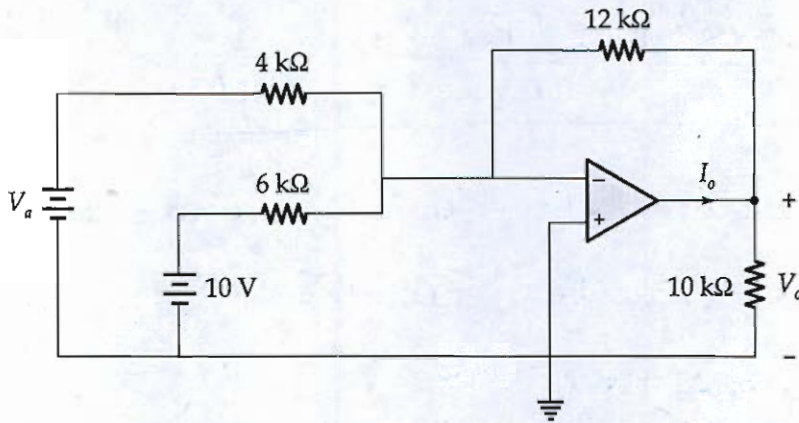Q.2 (c) For the circuit shown below, the op-amp is considered to be ideal.



- (i) For an input voltage  $V_a = 4\text{ V}$ , find the output voltage  $V_o$  and current  $I_o$ .
- (ii) Determine the range of input voltage  $V_a$  for linear operation if the saturation voltage of op-amp is  $\pm 12\text{ V}$ .

[20 marks]

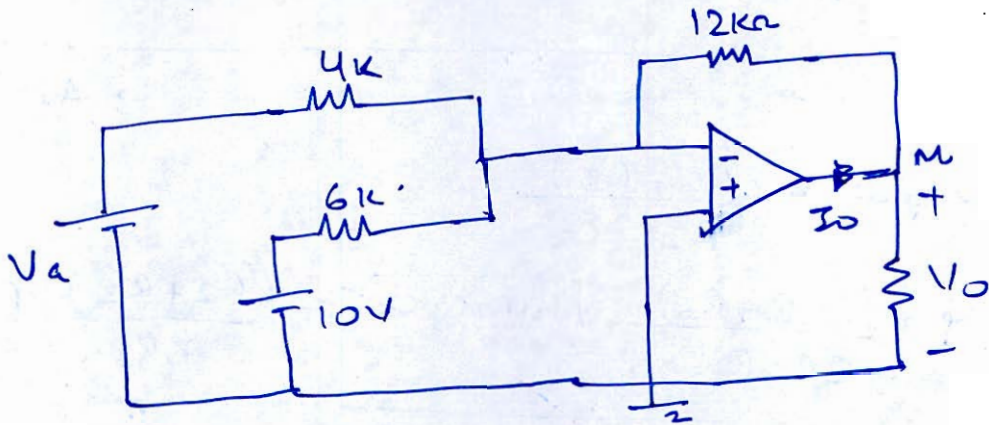

By virtual short concept.

$$V_+ = V_- = 0$$

Apply KCL at inverting terminal of op-amp

$$\frac{0 - V_a}{4} + \frac{0 - 10}{6} + \frac{0 - V_o}{12} = 0$$

$$\frac{-3V_a - 20 - V_o}{12} = 0$$

$$\text{So } V_o = -(3V_a + 20) \quad \text{--- (1)}$$

$$\text{If } V_a = 4V$$

$$\text{So } V_o = -(3 \times 4 + 20) = -32 \text{ volt}$$

f current  $I_o$

Apply KCL at node M.

$$\text{So } I_o = \frac{V_o}{10} + \frac{V_o - 0}{12} = V_o \left[ \frac{1}{10} + \frac{1}{12} \right]$$

$$= V_o \left[ \frac{6+5}{60} \right] = -32 \times \frac{11}{60} = -5.866 \text{ mA}$$

$$\text{So } V_o = -32 \text{ volt}$$

$$I_o = -5.866 \text{ mA}$$

← Ans.

ii) To find Range of  $V_a$  for linear operation

If  $V_{\text{sat}}$  of OPAMP =  $\pm 12V$ .

Now we proceed above by eq<sup>n</sup> (1)

$$V_o = -(3V_a + 20)$$

To find Range of  $V_a$ .

$$V_o + V_{\text{sat}} = +12 = -3(V_{a_{\text{min}}} + 20)$$

$$-4 = V_a + 20$$

$$V_{a_{\text{min}}} = -24 \text{ volt}$$

$$\text{If } V_o - V_{\text{sat}} = -12 = -3(V_a + 20)$$

$$4 = V_a + 20$$

$$V_{a_{\text{max}}} = -16 \text{ volt}$$

So Range of  $V_a = [V_{\text{min}}, V_{\text{max}}]$

$V_a$  lies b/w  $-16$  volt to  $-24$  volt

$$V_{a \text{ min}} = -24 \text{ V}$$

$$V_{a \text{ max}} = -16 \text{ V}$$

$$\boxed{-24 \leq V_a \leq -16}$$


Ans

Range of  $V_a$  for linear operation if  $V_{\text{sat}}$  of OPAMP =  $\pm 12 \text{ V}$



14

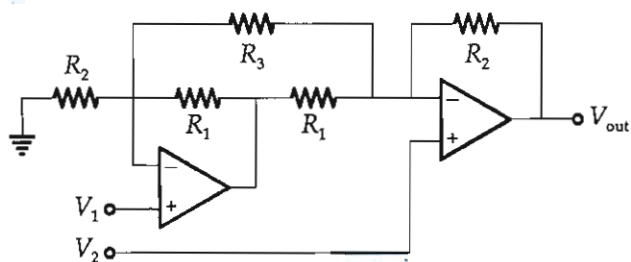Q.3 (a) (i) Consider the circuit shown in figure below.



Assuming the two op-amp to be ideal, calculate the value of  $\frac{V_{out}}{V_2 - V_1}$ .

[12 marks]




- Q.3 (a) (ii) Discuss Matthiessen's rule and explain the influence of the factors affecting resistivity of metals.

[8 marks]




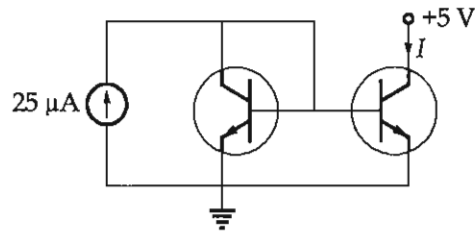- Q.3 (b) (i) The two transistors in the circuit shown below are identical. If  $\beta = 25$ , then find the value of current  $I$ .



[8 marks]

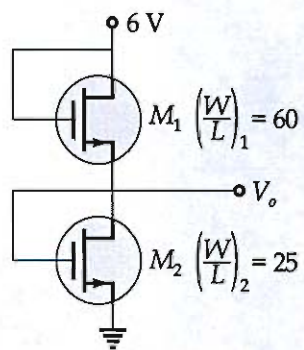Q.3 (b) (ii) Consider the circuit shown in figure below :



If both transistor have parameters  $\mu_n C_{ox} = 40 \mu\text{A}/\text{V}^2$  and  $V_{Th} = 0.9 \text{ V}$  then calculate the output voltage  $V_o$ .

[6 marks]



- Q.3 (b) (iii) Calculate the Fermi energy  $E_{FO}$  at  $0^\circ\text{K}$  for copper and estimate the average speed of the conduction electrons in Cu. The density of Cu is  $8.96 \text{ gm/cm}^3$  and atomic weight is 63.5. Given Avogadro's number is  $6 \times 10^{23}$ .


[6 marks]

- Q.3 (c) A parallel plate capacitor has an area of  $25 \text{ cm}^2$  and the separation between the plates is  $0.3 \text{ mm}$ . The space between the plates is filled with a dielectric having the real part of dielectric constant  $\epsilon'_r = 3$  when subjected to the frequency of  $1.5 \text{ MHz}$ . The loss tangent at this frequency is  $3.8 \times 10^{-4}$ . Find the parameters of the equivalent circuit.
- (i) Parallel R-C circuit.  
(ii) Series R-C circuit.

[20 marks]



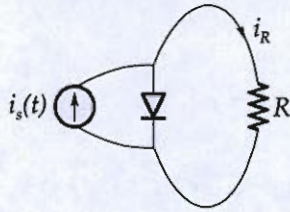- Q.4 (a) (i) The diode in the circuit is ideal. The current sources  $i_s(t) = \pi \sin(3000\pi t)$  mA. Find the magnitude of the average current flowing through the resistor  $R$ .



[10 marks]

$$i_s(t) = \pi \sin(3000\pi t) \text{ mA}$$

To find  $I_{\text{avg}}$  through  $R$ .

Soln

For +ve cycle

Diode is ON

$$i_{\text{avg}} = -i_R = \frac{I_m}{\pi} = \frac{\pi}{\pi} = 1 \text{ mA}$$

$$\text{So } i_{\text{avg}} = i_R = -1 \text{ mA}$$

For -ve half cycle Diode is off

$$\text{So } i_R = 0$$

So Avg. current flowing through resistance

$$R = -1 \text{ mA}$$

↳ Avg

$$I_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \omega t \, d\omega t = \frac{1}{2\pi} \left[ \int_0^{\pi} \pi \sin 3000\pi t \, d\omega t + \int_{\pi}^{2\pi} 0 \, d\omega t \right]$$

$$= \frac{\pi}{2\pi} \left[ -\cos \omega t \right]_0^{\pi} = \frac{1}{2} [-\cos \pi + \cos 0] = 1$$

9


Good Approach

Q.4 (a) (ii) With the help of magnetization characteristics ( $M$  vs  $H$  curves) explain the difference between Type-I and Type-II superconductors.

[10 marks]

M vs H curve for Type I & Type Superconductors

For Type I Superconductors

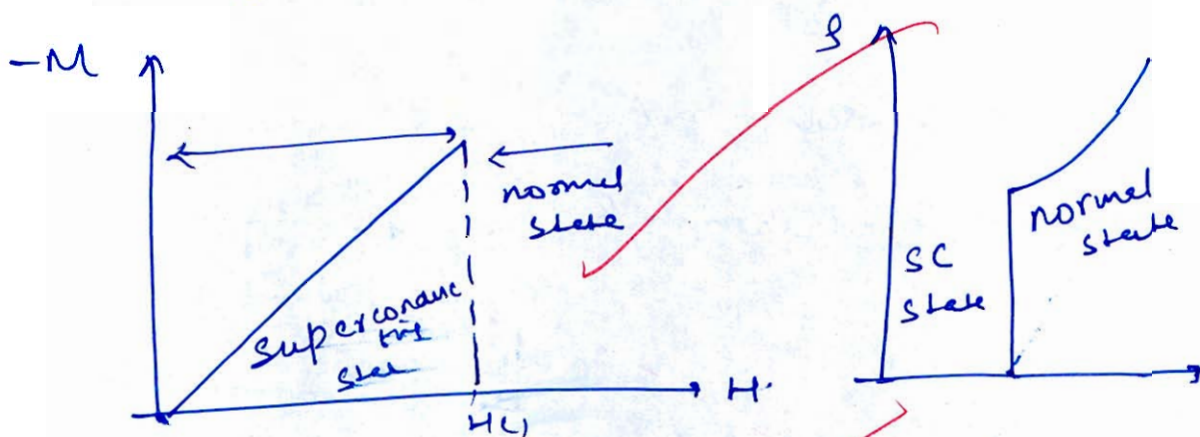

In Type I superconductors

It is for low magnetic field & it follows  
Silsbee Rule & Meissner effect.

Here magnetic field changes abruptly suddenly  
& for Temp below transition or critical Temp.


$H$  (magnetic field strength)  $\uparrow$  linear upto  
 $H_{c1}$  (critical magnetic field)

& After  $H_{c1}$  it enters into normal state

Type I superconductors occur for soft magnetic  
material.

For Ex: NbTi, Nb<sub>3</sub>Al.

For Type II Superconductor

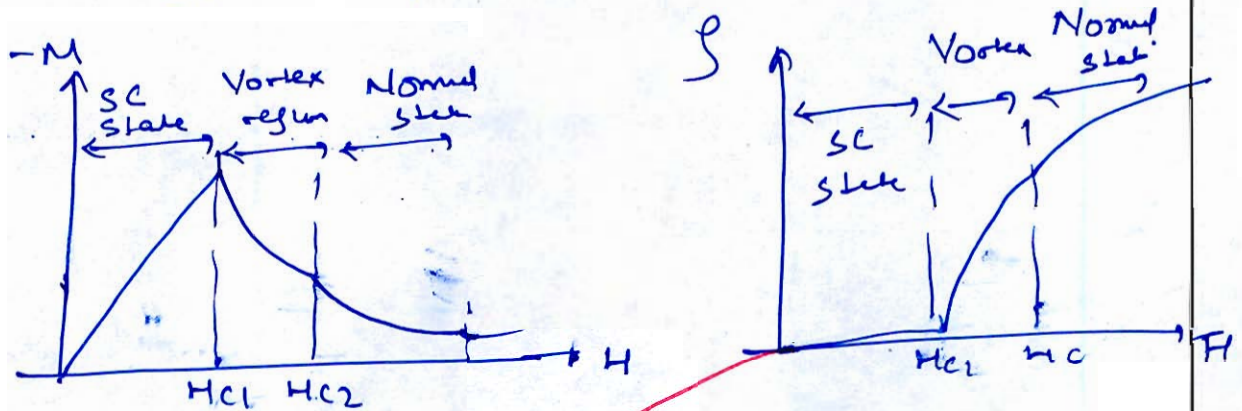

For Type II superconductor: There are two zones

- 1) SC state: Here Magnetic field increases linearly upto  $H_{c1}$  (critical field) then superconductor enter into vortex region.
- 2) Vortex state: Here abruptly changes not happens.

Here  $H_c$  varies slowly transition it decrease & goes upto  $H_{c2}$ .

- 3) while after  $H > H_{c2}$  superconductivity vanishes & material enter from superconducting state to normal state.


& Here magnetic field becomes zero.

These valid for Hard Magnetic material

& Type II Superconductor used for making permanent magnets

Ex: Fe, Co, Ni,  $Nb_3Ti$ ,  $Nb_3Sn$

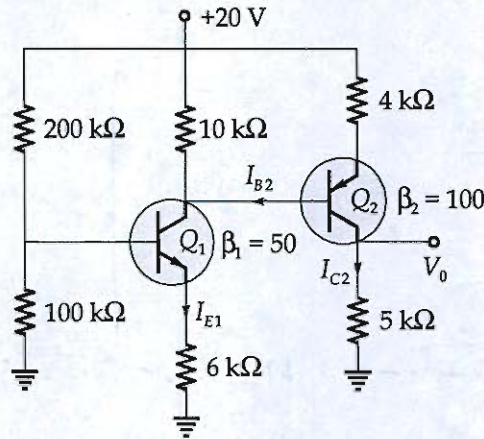
Q.4 (b) Consider the transistor configuration shown below.



Determine:

- (i) Base current of transistor,  $Q_2$ .
- (ii) Collector current of transistor,  $Q_2$ .
- (iii) Emitter current of transistor,  $Q_1$ .
- (iv) Output voltage,  $V_0$ .

[20 marks]

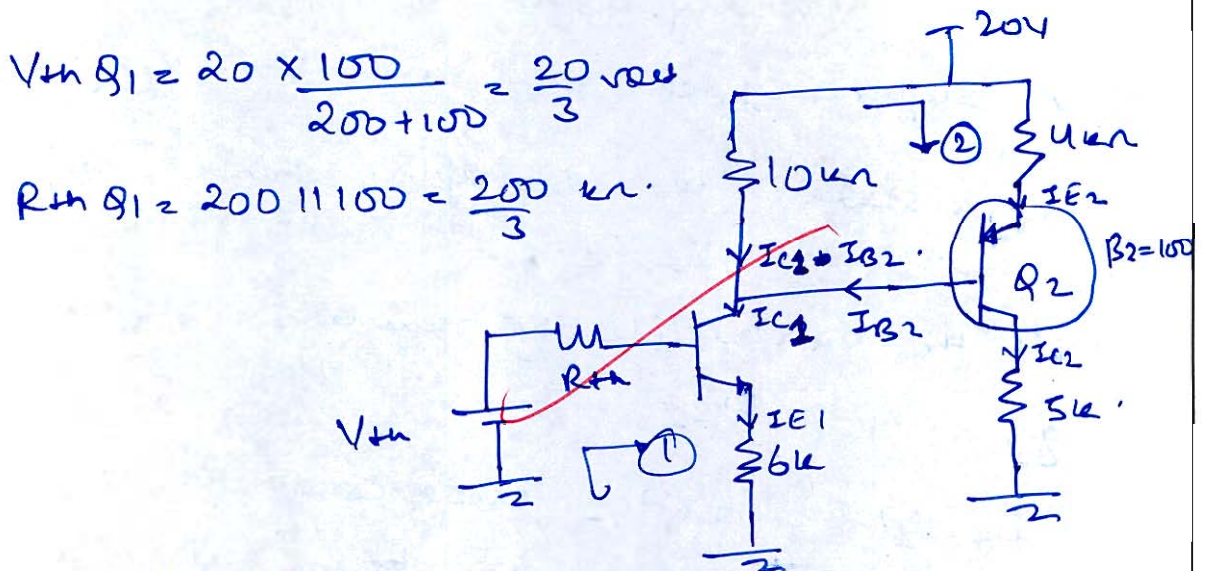

Current in  $10k\Omega$

$$\alpha I_{B2} = I_{C2} \Rightarrow \alpha = I_{C2} - I_{B2}$$

Apply KVL in loop 1

$$V_{th} - I_{B1} R_{th} - V_{BE1} - 6 I_{E1} = 0$$

$$6.67 - I_{B1} (66.67) - 0.7 - 6 (1 + \beta_1) I_{B1} = 0$$

$$6.67 - 66.67 I_{B1} - 0.7 - 306 I_{B1} = 0$$

$$I_{B1} = \frac{6.67 - 0.7}{306 + 66.67} = \frac{5.97}{372.67} = 16.01 \mu A$$

$$\text{So } I_{C1} = \beta_1 I_{B1} = 0.8 \text{ mA}$$

$$I_{E1} = 0.816 \text{ mA}$$

Apply KVL in loop 2.

$$-4I_{E2} - V_{EB2} + 10(I_{C1} - I_{B2}) = 0$$

$$-4I_{E2} - 0.7 + 10(0.8) - 10I_{B2} = 0$$

$$V_{EB2} = 0.7$$

$$8 - 0.7 = 4I_{E2} + 10I_{B2}$$

$$7.3 = [4(1 + \beta_2) + 10] I_{B2}$$

$$I_{B2} = \frac{7.3}{10 + 4(1 + 100)} = 17.63 \mu\text{A}$$

$$I_{C2} = \beta_2 I_{B2} = 1.7632 \text{ mA}$$

$$I_{E2} = 1.78 \text{ mA}$$

So

1) Base current of Transistor Q<sub>2</sub>

$$= I_{B2} = 17.63 \mu\text{A} \quad \leftarrow \text{Ans}$$

2) Collector current of transistor Q<sub>2</sub>

$$= I_{C2} = 1.7632 \text{ mA} \quad \leftarrow \text{Ans}$$

3) Emitter current of Transistor Q<sub>1</sub>

$$I_{E1} = 0.816 \text{ mA} \quad \leftarrow \text{Ans}$$

4) Output voltage  $V_o$

$$V_o = 5 I_{C2} = 5 \times 1.7632 = 8.816 \text{ volt}$$

$$\boxed{V_o = 8.816 \text{ volt}} \quad \leftarrow \text{Ans}$$

18


Good

Approach



- Q.4 (c) In the amplifier circuit shown below, assume  $V_{BE} = 0.7\text{ V}$  and the  $\beta$  of the transistor and the values of  $C_1$  and  $C_2$  are extremely high. If the amplifier is designed such that at the quiescent point its  $V_{CE} = V_{CC}/2$ , where  $V_{CC}$  is the power supply voltage, find its small

signal voltage gain  $\left| \frac{V_{out}}{V_{in}} \right|$ .

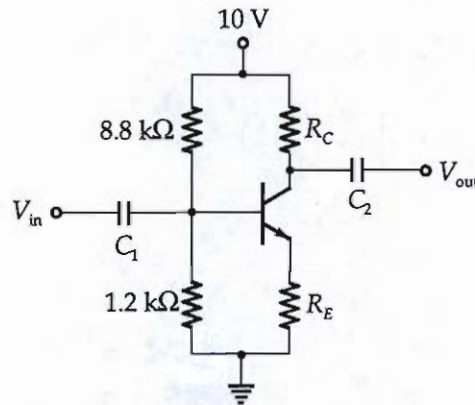

[20 marks]

Given  $V_{BE} = 0.7\text{ V}$ ,  $\beta, C_1, C_2$  high

$$V_{CE} = \frac{V_{CC}}{2}, \quad V_{CC} = 10\text{ V}$$

To find small signal voltage gain  $\left( \frac{V_{out}}{V_{in}} \right)$

sol<sup>n</sup>


DC Transfer Characteristics:-

$$\text{Cap} - \text{DC} \quad X_C = \frac{1}{\omega C} \approx \infty$$

AC supply - Grounded

$$V_{th} = \frac{10 \times 1.2}{8.8 + 1.2} \approx 1.2\text{ V}$$
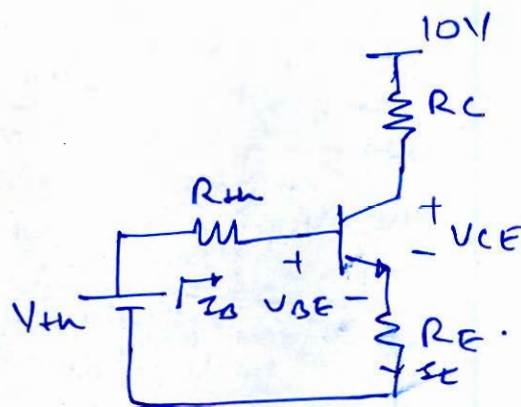
$$R_{th} = 8.8 \parallel 1.2 = \frac{8.8 \times 1.2}{10} = 1.056\text{ k}\Omega$$



Apply KVL inner loop

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

As  $\beta$  high so  $I_B \approx 0$  so  $I_E R_E = V_{th} - V_{BE} = 1.2 - 0.7$

$$\boxed{I_E R_E = 0.5\text{ V}} \quad (1)$$

Apply KVL in outer loop

$$10 - I_c R_c - V_{CE} - I_E R_E = 0$$

$$\text{So } V_{CE} = \frac{V_{CC}}{2} = \frac{10}{2} = 5V$$

$$10 - I_c R_c - 5 - 0.5 = 0$$

$$\boxed{I_c R_c = 4.5 \text{ volt}} \quad (1)$$

$I_E R_E = 0.5$   
(Proved Above)



Divide (1) ÷ (1)

$$\frac{I_E R_E}{I_c R_c} = \frac{0.5}{4.5} \Rightarrow \boxed{\frac{I_c R_c}{I_E R_E} = 9}$$

Now

Draw AC equivalent circuit

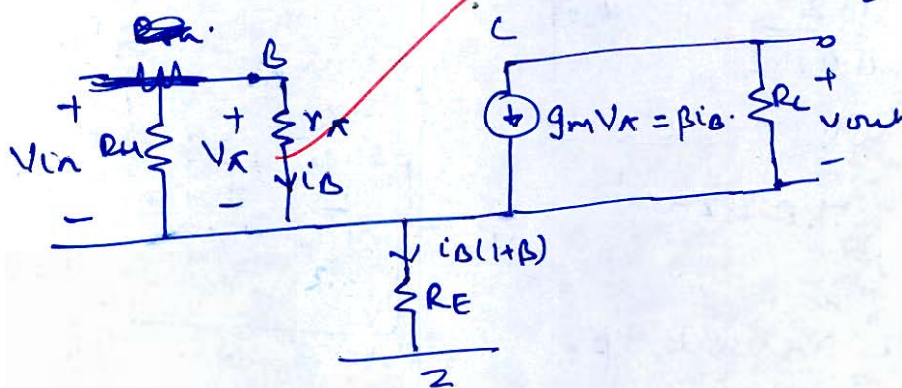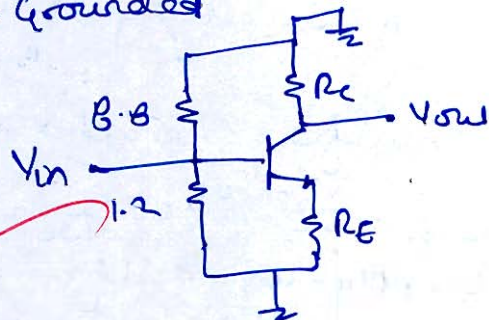Cap  $\rightarrow$  SC, DC supply - Grounded



$$A_v = \frac{V_{out}}{V_{in}}$$

$$V_{out} = -g_m V_x R_C = -g_m r_{\pi} i_b R_C = -\beta i_b R_C$$

$$V_{in} - V_x - V_x - i_b (1 + \beta) R_E = 0$$

$$V_{in} = i_b [r_{\pi} + r_{\pi} + (1 + \beta) R_E]$$

$$\frac{V_{out}}{V_{in}} = \frac{-\beta i_b R_C}{i_b [r_{\pi} + r_{\pi} + (1 + \beta) R_E]}$$

$$= \frac{-\beta R_C}{r_{\pi} + r_{\pi} + (1 + \beta) R_E}$$

$$r_{\pi} = \frac{\beta}{g_m} \Rightarrow g_m = \frac{I_C}{V_T} \Rightarrow r_{\pi} = \frac{\beta V_T}{I_C}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\beta R_C}{\frac{\beta V_T}{I_C} + (1 + \beta) R_E} = \frac{-R_C}{\frac{V_T}{I_C} + \left(\frac{1 + \beta}{\beta}\right) R_E}$$

$$= \frac{-R_C / R_E}{\frac{V_T}{I_C R_E} + \left(\frac{1 + \beta}{\beta}\right)}$$

If  $\beta$  very high  
so  $\frac{1 + \beta}{\beta} \approx 0$

$$\frac{V_{out}}{V_{in}} = \frac{-R_C / R_E}{\frac{V_T}{I_C R_E} + 0 + 1} = \frac{-R_C / R_E}{\frac{V_T + I_C R_E}{I_C R_E}}$$

$$= \frac{-R_C R_E I_C}{R_E (V_T + I_C R_E)} = \frac{-I_C R_C}{V_T + I_C R_E} = \frac{-I_C R_C}{V_T + I_C R_E}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{-g_m R_C R_E}{I_C R_E + 0 + 1}} \quad \leftarrow \text{Ans}$$

Try to  
avoid over writing



## Section B : Electrical Machines-1 + Power Systems-2

Q.5 (a) A monopolar HVDC link energized from a 3- $\phi$ , 50 Hz, 400 kV source produces a DC current of 1000 A with a 6-pulse rectifier and the DC output voltage rectifier is 400 kV. For a delay angle of  $15^\circ$ .

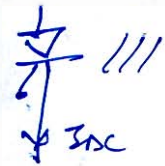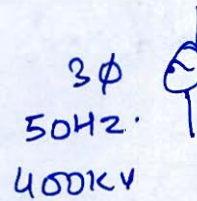- (i) Calculate commutation resistance.  
 (ii) Calculate commutation angle ' $\mu$ '.  
 (iii) If AC voltage is reduced to 200 kV, find commutation angle assuming dc current is constant.

[12 marks]

$I_{DC} = 1000 \text{ A}$   
 6 pulse rectifier  
 $V_{0dc} = 400 \text{ kV}$



For  $\alpha = 15^\circ$

$$V_0 = \frac{3V_{ML}}{\pi} \cos \alpha - 6fL_p I_0$$

$$V_0 = \frac{3 \times 400 \sqrt{2}}{\pi} \cos 15^\circ - 0 = 521.78 \text{ V}$$

i) Commutation Resistance  $\approx R = \frac{V_0}{I_{dc}} = \frac{521.78}{1000}$   
 $\approx 0.52178 \Omega$

(ii)  $V_0 = \frac{3V_{ML}}{\pi} [\cos \alpha + \cos(\alpha + \mu)]$

$$I_0 =$$

$$V_0 = \frac{3 \times 400 \sqrt{2}}{\pi} [\cos \alpha + \cos(\alpha + \mu)]$$

$$I_0 R = 0.52178 \times 1000 = 521.78$$

$$521.78 = 521.78$$

$$I_0 = \frac{V_{ML}}{3\omega L} [\cos \alpha - \cos(\alpha + \mu)]$$

$$V_0 = 400 \text{ kV} = \frac{3V_{ML}}{\pi} [\cos \alpha + \cos(\alpha + \mu)]$$

$$400 = \frac{3 \times 400 \sqrt{2}}{\pi} [\cos 15 + \cos(15 + \mu)]$$

$$0.74 = 0.965 = \cos(15 + \mu)$$

$$15 + \mu = 163.05$$

$$\mu = 88.05^\circ \leftarrow \text{Ans}$$

(21)

$$\text{If } AC = 200 \text{ kV}$$

$$V_0 = 400 = \frac{3 \times 200 \sqrt{2}}{\pi} [\cos 15 + \cos(15 + \mu)]$$

$$4 = 3 \times 0.9 [\cos 15 + \cos(15 + \mu)]$$

$$\cos(15 + \mu) = 0.515$$

$$15 + \mu = 58.96$$

$$\mu = 43.96^\circ \leftarrow \text{Ans}$$

6

- Q.5 (b) An induction motor has an efficiency of 0.9 when the shaft load is 45 kW. At this load, stator ohmic loss and rotor ohmic loss each is equal to the iron loss. The mechanical loss is  $1/3^{\text{rd}}$  of the no load losses. Neglect ohmic losses at no load, and calculate the slip.

[12 marks]

$$P_{sh} = 45 \text{ kW} \quad \eta = 0.9$$

Stator ohmic loss, Rotor ohmic loss = Iron loss

$$\text{Mech. loss} = \frac{1}{3} (\text{No load losses})$$

$$P_{sh} = P_{out} - \text{f & w loss} = P_{dev} - \text{f & w loss}$$

$$P_{dev} = P_g - \text{rotor cu loss} = P_g(1-s)$$

$$P_g = P_{in} - \text{stator cu \& Iron loss}$$

$$\text{Mech loss} = \frac{1}{3} (\text{No load loss}) \Rightarrow$$

$$\text{Mech} = \frac{1}{3} (\text{Iron loss} + \text{Mech loss}) \Rightarrow \text{Iron loss} = 2 \times \text{Mech loss}$$

$$P_{input} = \frac{P_{sh}}{\eta} = \frac{45}{0.9} = 50 \text{ kW}, \text{ losses} = \text{I/P} - \text{O/P} = 50 - 45 = 5 \text{ kW}$$

$$\text{Iron loss} = 2 (\text{Mech losses})$$

$$P_{dev} = P_g - \text{stator ohmic} - \text{rotor ohmic loss} = P_g - 2 \times \text{Iron loss}$$

$$P_{sh} = P_g - 2 \text{ Iron loss} - \text{f & w loss}$$


$$P_d = P_g(1-s)$$

$$s P_g = 5$$

$$s = \frac{5}{50} = 0.1$$

$$\text{slip} = 0.1 \leftarrow \text{Ans}$$


Go through  
the made  
easy selection

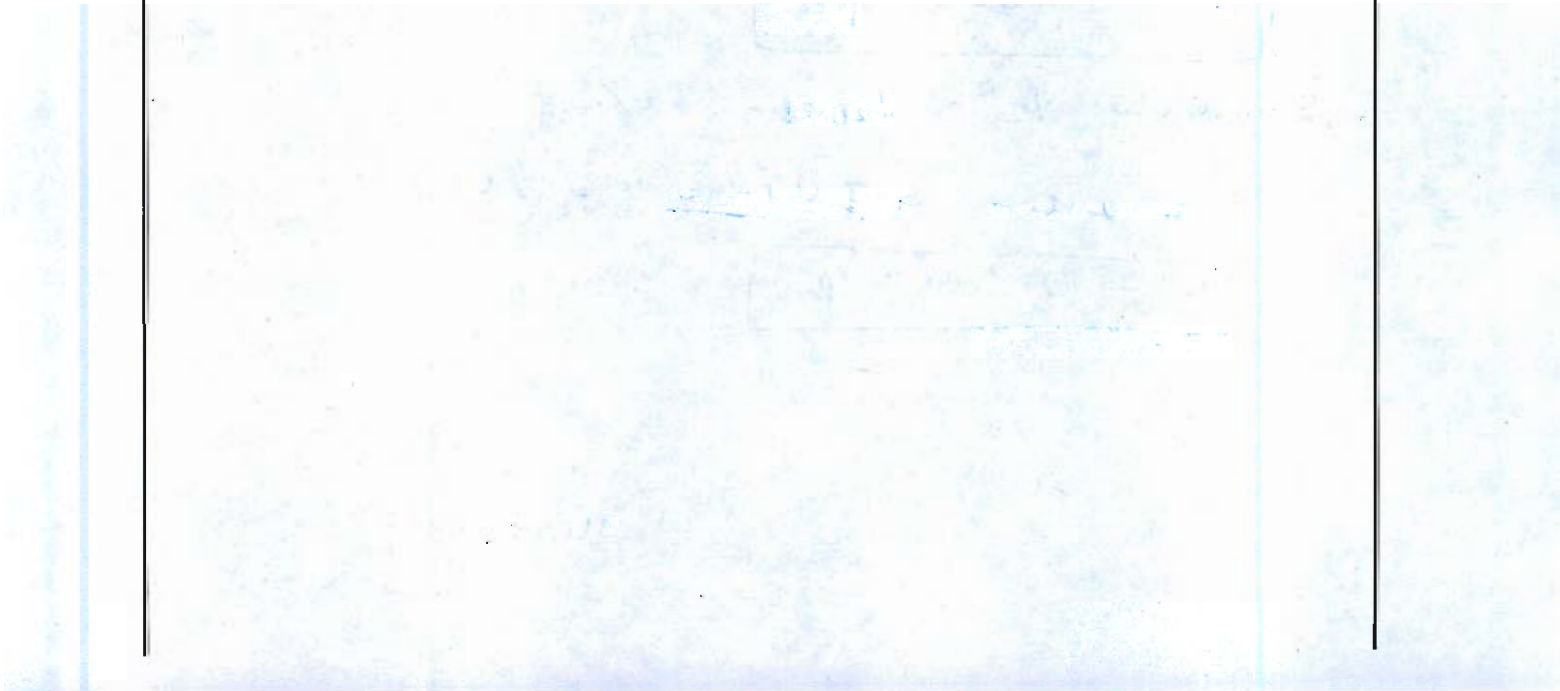

Q.5 (c) For the power system shown in figure, the pu reactances are shown therein. For a solid 3-phase fault on bus 3. Calculate the following :

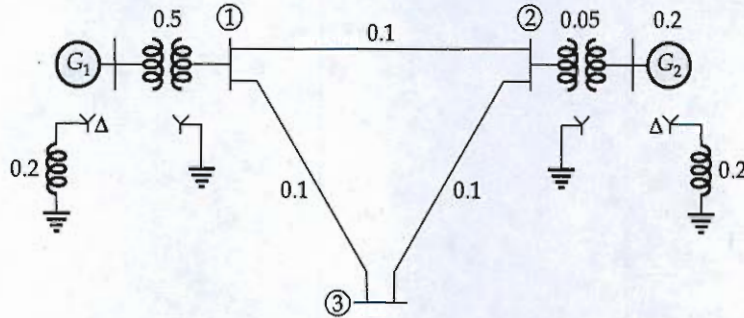- (i) Fault current
- (ii)  $V_1^f$  and  $V_2^f$
- (iii)  $I_{12}^f, I_{13}^f$  and  $I_{23}^f$
- (iv)  $I_{G1}^f$  and  $I_{G2}^f$

Assume pre-fault voltage to be 1 pu. (Where  $f$  represents post fault event)



$Z_{Bus}$  for the above system,  $Z_{Bus} = j \begin{bmatrix} 0.1397 & 0.1103 & 0.1250 \\ 0.1103 & 0.1397 & 0.1250 \\ 0.1250 & 0.1250 & 0.1750 \end{bmatrix}$

[12 marks]

i)  $3\phi$  fault on bus 3.

$$I_f = \frac{V_3}{Z_{33}} = \frac{1 \angle 0^\circ}{j0.1750} = 5.714 \angle -90^\circ$$

(ii)  $V_1^f = V_{1pref} - I_f Z_{13}$

$$= 1 \angle 0^\circ - 5.714 \angle -90^\circ \times 0.125 \angle 90^\circ$$

$$= 1 - 0.714$$

$$V_1^f = 0.2857 \text{ pu}$$

Similarly  $V_2^f = V_{2pref} - I_3 Z_{23}$

$$= 1 \angle 0^\circ - 5.714 \angle -90^\circ \times 0.125 \angle 90^\circ$$

$$V_2^f = 0.2857 \text{ pu}$$

$$(iii) \quad I_{12}^f = \frac{V_1^f - V_2^f}{Z_{12} + Z_k}$$


$$\begin{aligned} V_3^f &= V_3^{oc} - I_3 Z_{33} \\ &= 110 - 5.714 \angle -90^\circ \times 0.175 \\ &= 0 \text{ volt} \end{aligned}$$

$$\text{So } I_{12}^f = \frac{0.2857 - 0.2857}{0.1103 + 0.1} = 0$$

$$I_{13}^f = \frac{V_1^f - V_3^f}{Z_{13} + j0.1} = \frac{0.2857 - 0}{j0.125 + j0.1} = 1.269 \angle -90^\circ$$

$$I_{23}^f = \frac{V_2^f - V_3^f}{Z_{23} + j0.1} = \frac{0.2857}{j0.125 + j0.1} = 1.269 \angle -90^\circ$$

Draw equivalent circuit

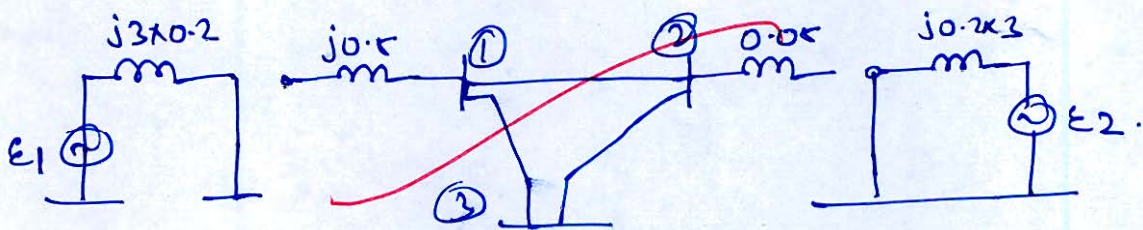

$$i) \quad I_{q1}^f = \frac{E_1}{j0.6} = \frac{1}{0.6} = 1.67 \angle -90^\circ$$

$$I_{q2}^f = \frac{E_2}{j0.6} = 1.67 \angle -90^\circ$$



- Q.5 (d) A 3- $\phi$ , 500 kW, 3.3 kV, 50 Hz, star-connected induction motor works at a full load power factor of 0.7 lag. A delta connected capacitor bank is used to raise the full load power factor to 0.9 lag. Calculate the capacitance of the bank. If each capacitor is rated at 420 V, 50 Hz, compute the capacitance of each unit. The motor efficiency is 86%. If this induction motor is fed by distribution circuit, calculate the percentage saving in the energy lost in this distribution circuit, as the power factor is improved from 0.7 to 0.9 lag.

[12 marks]

3 $\phi$ , 500kW, 3.3kV, 50Hz

Y connected IM  $\cos\phi = 0.7$  lag.

~~$\Delta$  connected cap. Bank.  $\cos\phi_2 = 0.9$  lag.~~

$$P = 500 \text{ kW}$$

$$Q_1 = P \tan\phi = 500 \times \tan(\cos^{-1} 0.7) = 510.10 \text{ kVAR}$$

$$Q_2 = P \tan\phi_2 = 500 \tan(\cos^{-1} 0.9) = 242.161 \text{ kVAR}$$

$$Q_c = P (\tan\phi_1 - \tan\phi_2)$$

$$= 500 (\tan 45.572^\circ - \tan 25.84^\circ) = 267.95 \text{ kVAR}$$

$$\text{Now } Q_c = 3 \omega C_{ph} V_{ph}^2 \tan\phi$$

$$Q_c = 3 \omega C_{ph} V_{ph}^2 \tan\phi$$

$$267.95 = \frac{3 \times 50 \times C_{ph} \times 420^2}{3}$$

$$C_{ph} = \frac{267.95}{3 \times 50 \times 420^2} = 1.611 \mu\text{F}$$

$$\text{Total capacitance of Bank} = 3 C_{ph} = 4.83 \mu\text{F}$$

$$\text{If motor } \eta = 86\%$$

$$P_{in} = \frac{P_{out}}{\eta} = \frac{500}{0.86} = 581.39 \text{ kW}$$

$\eta$ . Saving in energy

$$= \frac{E_2 - E_1}{E_1}$$

$$= \frac{P_2 - P_1}{P_1} = \left( \frac{P_2}{P_1} - 1 \right)$$

$$= \left( \frac{Q_2 / \tan \phi_2}{Q_1 / \tan \phi_1} - 1 \right)$$

$$= \left( \frac{Q_2 \tan \phi_1}{Q_1 \tan \phi_2} - 1 \right)$$

$$= \left( \frac{242.161}{510.10} \frac{\tan 45.872}{\tan 25.84} - 1 \right)$$

$\eta$ . Savy = 100%

5

- Q.5 (e) A 50 Hz, single-phase transformer draws a short circuit current of 30 A at 0.2 pf lag when connected to 16 V, 50 Hz source. What will be the short circuit current and its p.f. when the same transformer is energized from 16 V, 25 Hz source?

[12 marks]

50Hz,  $1\phi$  X<sup>r</sup>  $I_{sc} = 30A$  @ 0.2 pf lag @ 16V, 50Hz  
 $I_{sc} = ?$  if pf = ? if 16V, 25Hz

$$\text{Now } Z = \frac{V}{I} = \frac{16}{30 \angle -\cos^{-1} 0.2} = \frac{16}{30 \angle -78.46}$$

$$= 0.533 \angle 78.46 = 0.1066 + j0.52255$$

If freq. changed.

$$\text{so } X \propto f \Rightarrow \frac{X_2}{X_1} = \frac{f_2}{f_1}$$

$$\frac{X_2}{0.52255} = \frac{25}{50} \Rightarrow X_2 = 0.26127 \Omega$$

$$\text{so } Z_{2\text{new}} = R_2 + jX_2 = 0.1066 + j0.26127$$

$$\text{so } Z_2 = 0.2822 \angle 67.79^\circ$$

$$I_{sc2} = \frac{V}{Z_2} = \frac{16}{0.2822 \angle 67.79} = 56.69 \angle -67.79^\circ$$

$$\text{so } I_{sc} = 56.7 \text{ Amp}$$

$$\text{power factor} = \cos(67.79) = 0.378 \text{ lag} \leftarrow \text{Ans}$$

@ 16V, 25Hz.

11

Good  
Approach



**Q.6 (a)** A 150 kW, 400 V, 8-pole, 50 Hz, star-connected induction motor has the following impedance parameters in ohms per phase referred to stator.

$$r_1 = 0.02 \, \Omega, \quad r_2 = 0.04 \, \Omega, \quad x_1 = x_2 = 0.2 \, \Omega, \quad X_m = 9.8 \, \Omega$$

At rated shaft output, it runs with a slip of 4% and with an efficiency of 93%.

(i) Calculate the rotational and core losses at rated load from the data given above.

(ii) If this motor is driven as a generator at a slip of 4 percent, determine:

1. electric power output,
2. pf at the generator terminals and
3. efficiency.

The induction generator is connected to a distribution system of 400 V.

**[20 marks]**





Q.6 (b) The primary, secondary and tertiary winding of a three-winding transformer are rated as 11 kV, 6 MVA, star/3.3 kV, 3 MVA, star/400 V, 3 MVA, delta respectively. The short circuit tests on this transformer gave the following results:

Secondary shorted ; primary excited : 500 V, 100 A,

Tertiary shorted ; primary excited : 600 V, 100 A and

Tertiary shorted ; secondary excited : 100 V, 200 A

- (i) Find the per unit leakage reactances of the star equivalent circuit. Neglect resistance.
- (ii) The primary is energized at rated voltage and the secondary is open circuited. For a three-phase balanced short circuit at the tertiary terminals, calculate the short circuit current and the secondary terminal voltage.

[20 marks]






Q.6 (c) The fuel cost characteristics of two thermal plants are as under,

$$C_1 = 7700 + 52.8P_1 + 5.5 \times 10^{-3} P_1^2 \text{ Rs./hour}$$

$$C_2 = 2500 + 15P_2 + 0.05 P_2^2 \text{ Rs./hour}$$

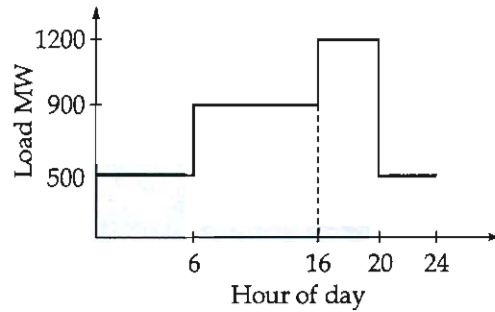The limit of generation for the two units are  $200 \leq P \leq 800$  MW. The load curve is shown in figure below. Find the daily operating schedule to minimize the operating costs. The cost of taking a unit off and then putting it on is Rs. 1000.00.




[20 marks]





- Q.7 (a) In the two-bus system shown in figure below, bus-1 is a slack bus with  $V_1 = 1.0 \angle 0^\circ$  p.u. A load of 100 MW and 50 MVar is taken from bus-2. The line impedance is  $z_{12} = 0.12 + j0.16$  p.u. on a base of 100 MVA. Using Newton-Raphson method, obtain the voltage magnitude and phase angle of bus-2. Start with an initial estimate of  $|V_2|^{(0)} = 1.0$  p.u. and  $\delta_2^{(0)} = 0^\circ$ . Perform two iterations.

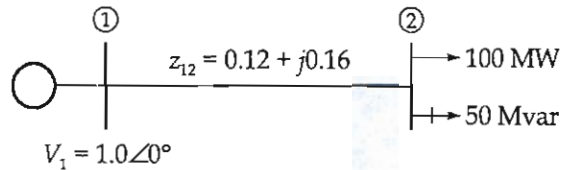

[20 marks]





- Q.7 (b) (i) Compare the overhead distribution system to underground distribution system in regards to deciding factors for selection of above systems as transmission network.  
[10 marks]




- Q.7(b) (ii) Draw basic structure of HVDC transmission. Clearly showing main components of HVDC transmission. Why there is requirement of reactive power at HVDC converter station. How this reactive power demand is fulfilled?

[10 marks]



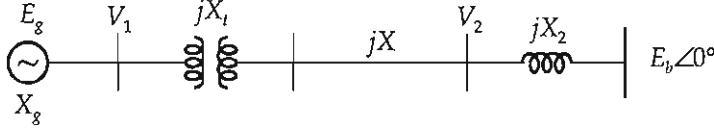- Q.7 (c) A single machine is connected to a load centre through a transmission line as shown in figure. The load centre is represented by a reactance connected to an infinite bus. The generator is initially operating with  $P_e = 1.0$  pu and the magnitudes of voltages  $V_1$  and  $V_2$  are 1.0 pu. Assume  $X_g = 0.3$  pu,  $X_t = 0.1$  pu,  $X = 0.4$  pu and  $X_2 = 0.1$  pu.



- (i) Find the maximum step increase in mechanical power that will not cause transient instability.
- (ii) Find the critical clearing angle and time for a three phase fault at the generator terminal. Generator is initially supplying power of 1.0 pu. Assume that post-fault system is identical to the prefault system. ( $H = 4.0$  sec,  $f_B = 50$  Hz).

[20 marks]





Q.8 (a) The following test data were taken on a 7.5 hp, four-pole, 208-V, 60-Hz, design A, Y-connected induction motor having a rated current of 28 A.

DC test:

$$V_{DC} = 13.6 \text{ V,}$$

$$I_{DC} = 28.0 \text{ A}$$

No-load test:

$$V_T = 208 \text{ V,}$$

$$f = 60 \text{ Hz}$$

$$I_A = 8.12 \text{ A,}$$

$$P_{in} = 420 \text{ W}$$

$$I_B = 8.20 \text{ A}$$

$$I_C = 8.18 \text{ A}$$

Locked-rotor test:

$$V_T = 25 \text{ V,}$$

$$f = 15 \text{ Hz}$$

$$I_A = 28.1 \text{ A,}$$

$$P_{in} = 920 \text{ W}$$

$$I_B = 28.0 \text{ A}$$

$$I_C = 27.6 \text{ A}$$

(i) Sketch the per-phase equivalent circuit for this motor.

(ii) Find the slip at the pullout torque and find the value of the pullout torque itself.


[20 marks]







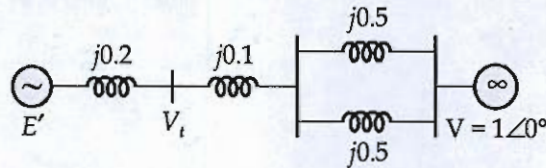- Q.8 (b) (i) Consider the power system shown below. With parallel transmission impedance of  $j0.5\Omega$  and delivered power is 0.8 p.u. when both the terminal voltage of the machine and the voltage of the infinite bus is 1 p.u. Determine the power angle equation of the system during above specified conditions.



- (ii) A 60 Hz generator is supplying 60% of  $P_{\max}$  to an infinite bus through a reactive network. A fault occurs which increases the reactance of the network between the generator internal voltage and the infinite bus by 400%. When the fault is cleared, the maximum power that can be delivered is 80% of the original value. Determine the critical clearing angle in degree considering above condition.

[20 marks]

i)

$$P_{del} = 0.8 \text{ pu}$$

$$V_t = V = 1 \angle 0$$

$$P = \frac{E'V \sin(\delta - 0)}{X_{eq}}$$

$$0.8 = \frac{E' \times 1 \sin \delta}{0.55}$$

$$\boxed{E' \sin \delta = 0.44} \quad (1)$$

$$I = \frac{E' \angle \delta - V_t \angle 0}{j0.2} = \frac{V_t \angle 0 - 1 \angle 0}{j0.35} \quad V_t = 1 \text{ pu}$$

$$E' \angle \delta - 1 \angle 0 = (1 \angle 0 - 1) \frac{20}{35} = \frac{4}{7} \angle 0 - \frac{4}{7}$$

$$E' \angle \delta = \frac{11}{7} \angle 0 - \frac{4}{7}$$

Also Gen. Eq<sup>n</sup>  $E' = V_t + j0.2 I_a$

$$E' \cos \delta + j E' \sin \delta = \frac{11}{7} \cos \theta + \frac{j 11}{7} \sin \theta - \frac{4}{7}$$

compare real & imag. part

$$E' \cos \delta = \left( \frac{11 \cos \theta - 4}{7} \right), \quad E' \sin \delta = \frac{11 \sin \theta}{7}$$

$$\text{So } 0.44 = \frac{11 \sin \theta}{7} \Rightarrow \sin \theta = 0.28,$$

$$\theta = 16.26^\circ$$

$$\text{So } V_t = 1 \angle 16.26^\circ$$

$$\text{So } E' \cos \delta = \frac{11 \cos \theta - 4}{7} \Rightarrow E' \cos \delta = 0.937 \quad \text{--- (2)}$$

$$1^2 + 2^2$$

$$(E' \cos \delta)^2 + (E' \sin \delta)^2 = (0.44)^2 + (0.937)^2$$

$$E' = 1.035$$

$$\text{f } \textcircled{1} \div \textcircled{2} \quad \text{So } \frac{E' \sin \delta}{E' \cos \delta} = \frac{0.44}{0.937} \Rightarrow \tan \delta = 0.469$$

$$\delta = 25.13^\circ$$

$$\text{So } \vec{E} = 1.035 \angle 25.13^\circ \quad \leftarrow A_n$$

60 Hz

$$P_m = 60\% P_{max}$$

If fault occur  $X' = 5X_1 = X_2$

If fault cleared  $P = 0.8 P_{max}$

To find  $\delta_c$

$$P_m = 0.6 P_{max}$$

$$P_{max} \sin \delta = 0.6 P_{max}$$

$$\text{So } \delta = \sin^{-1} 0.6 = 36.86^\circ$$

$$P_{max} = \frac{EV}{X_1}$$

$$P_2 = \frac{E_2 V_2}{X_2} = \frac{EV}{5X_1} = 0.2 P_{m1}$$


$$\delta_1 = \sin^{-1} 0.2$$

$$\text{So } P_{m2} = \frac{EV}{X_2} = \frac{EV}{5X_1} = 0.2 P_{max} = 0.2$$

$$P_{m3} = P_{max} \sin \delta_{m3} = 0.8 P_{max} = 0.8 \times 0.6 P_{max}$$

$$\delta_{m3} = 48.69^\circ \quad \sin \delta_{m3} = 0.48$$
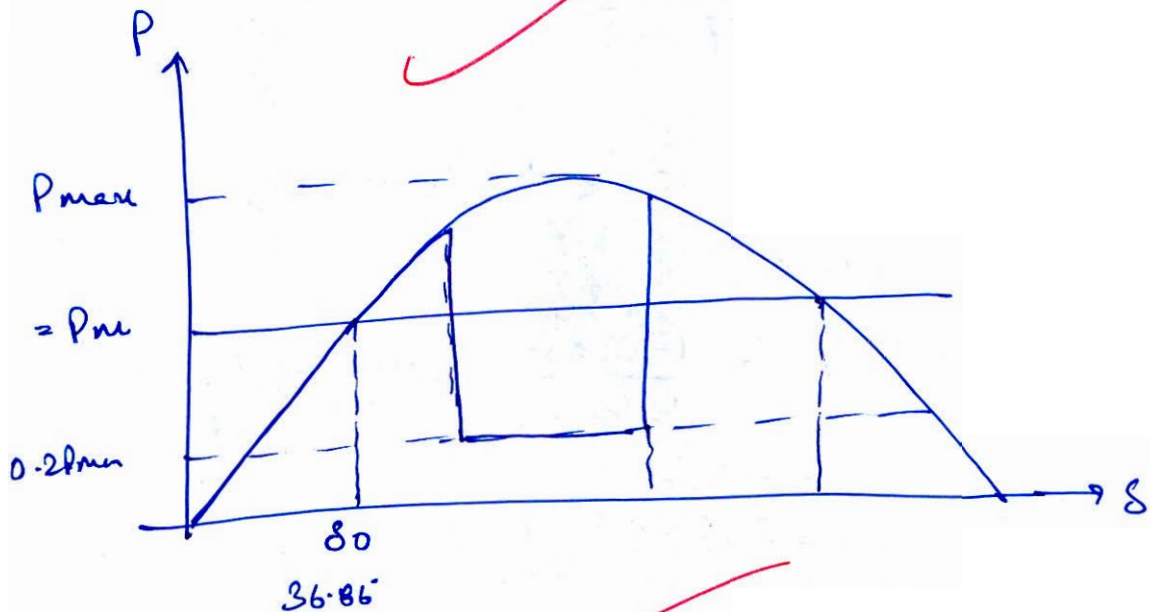
$$\delta_{max} = \pi - \delta_{m3} = 126.86^\circ$$



$$\delta_{cr} = \cos^{-1} \left[ \frac{P_{m2} (\delta_{max} - \delta_0) + P_{m3} \cos \delta_{m3} - P_{m2} \cos \delta_0}{P_{m3} - P_{m2}} \right]$$

$$= \cos^{-1} \left[ \frac{1 (126.86 - 36.86) + 0.8 \cos 126.86 - 0.2 \cos 36.86}{0.8 - 0.2} \right]$$

$$= \cos^{-1} \left[ \frac{1.57 - 0.479 - 0.16}{0.6} \right]$$

Simplify your  
answer

15



Q.8 (c) A 3-phase, 400 V, 50 Hz, star-connected induction motor gave the following test results:  
 No load: 400 V, 7.5 A, 0.135 power factor.  
 Block rotor: 150 V, 35 A, 0.44 power factor.  
 The ratio of standstill reactance of stator and rotor is estimated as 2. If the motor is running at a speed of 960 rpm, determine:  
 (i) net mechanical power output,  
 (ii) the net torque and  
 (iii) efficiency of the motor  
 Assume stator and rotor copper losses to be equal.

[20 marks]

$$Z_{NL} = \frac{V_{NL}}{I_{NL}} = \frac{400/\sqrt{3}}{7.5} \angle 82.24^\circ = 30.79 \angle 82.24^\circ$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{150/\sqrt{3}}{35} \angle 63.89^\circ = 2.474 \angle 63.89^\circ$$


$$\frac{X_s}{X_r} = 2$$

$$\begin{aligned} \text{If } N_r &= 960 \text{ rpm} \\ N_s &= 1000 \text{ rpm} \end{aligned}$$

$$\beta = \frac{N_s - N_r}{N_s} = \frac{40}{1000} = 0.04 = 4\%$$

$$Z_{NL} = R_{NL} + jX_{NL} = 3.837 + j30.841$$
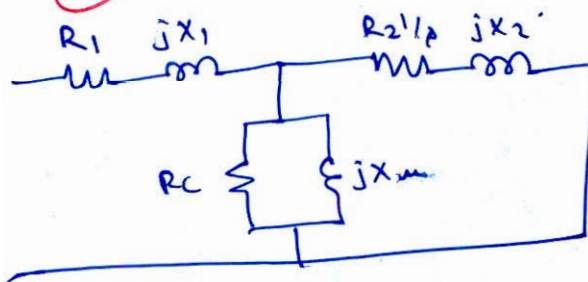
$$Z_{sc} = R_{sc} + jX_{sc} = 1.088 + j2.221$$




6  
 I'm complete  
 solution





## Space for Rough Work

---

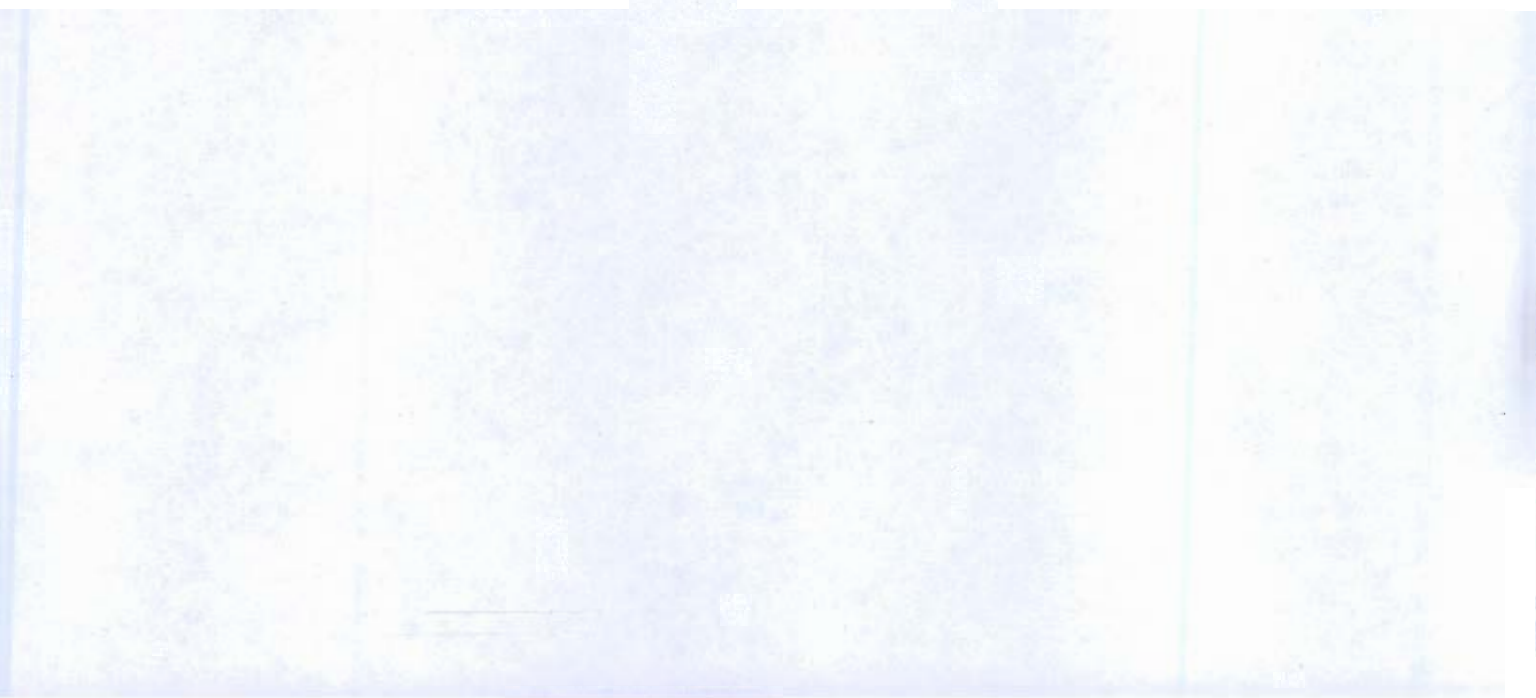

Space for Rough Work

---

1d  
4a - (ii)  
5a  
5d  
8a  
8b  
8c

9a = 8  
3m